

Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

SATELLITE TV EARTH STATION

Build your own for under \$999

UNIDIGITAL CLOCK

Easy to build with unique display

HOUSEHOLD ANDROIDS

Part 2—How to design your own

SWITCHING POWER SUPPLY

Build for your workbench

BETTER TV SOUND


New receiver circuit improves quality

Build it cover story

AUDIO POWER METER

Add-on for your hi-fi system


A
GERNSBACK
PUBLICATION

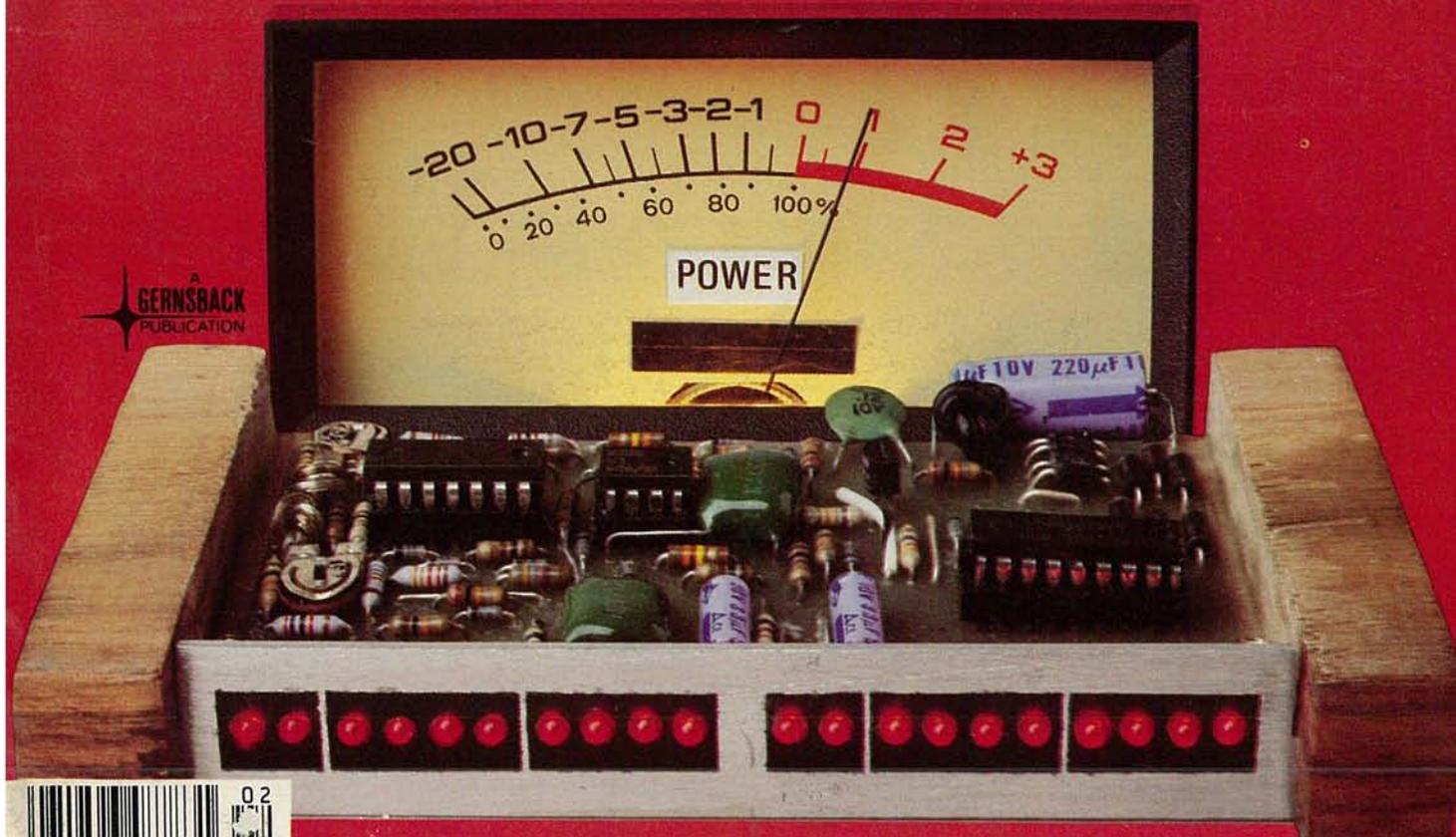


PLUS:

- ★ R.E.A.L. Sound Lab Test Report
- ★ Service Clinic ★ Equipment Reports

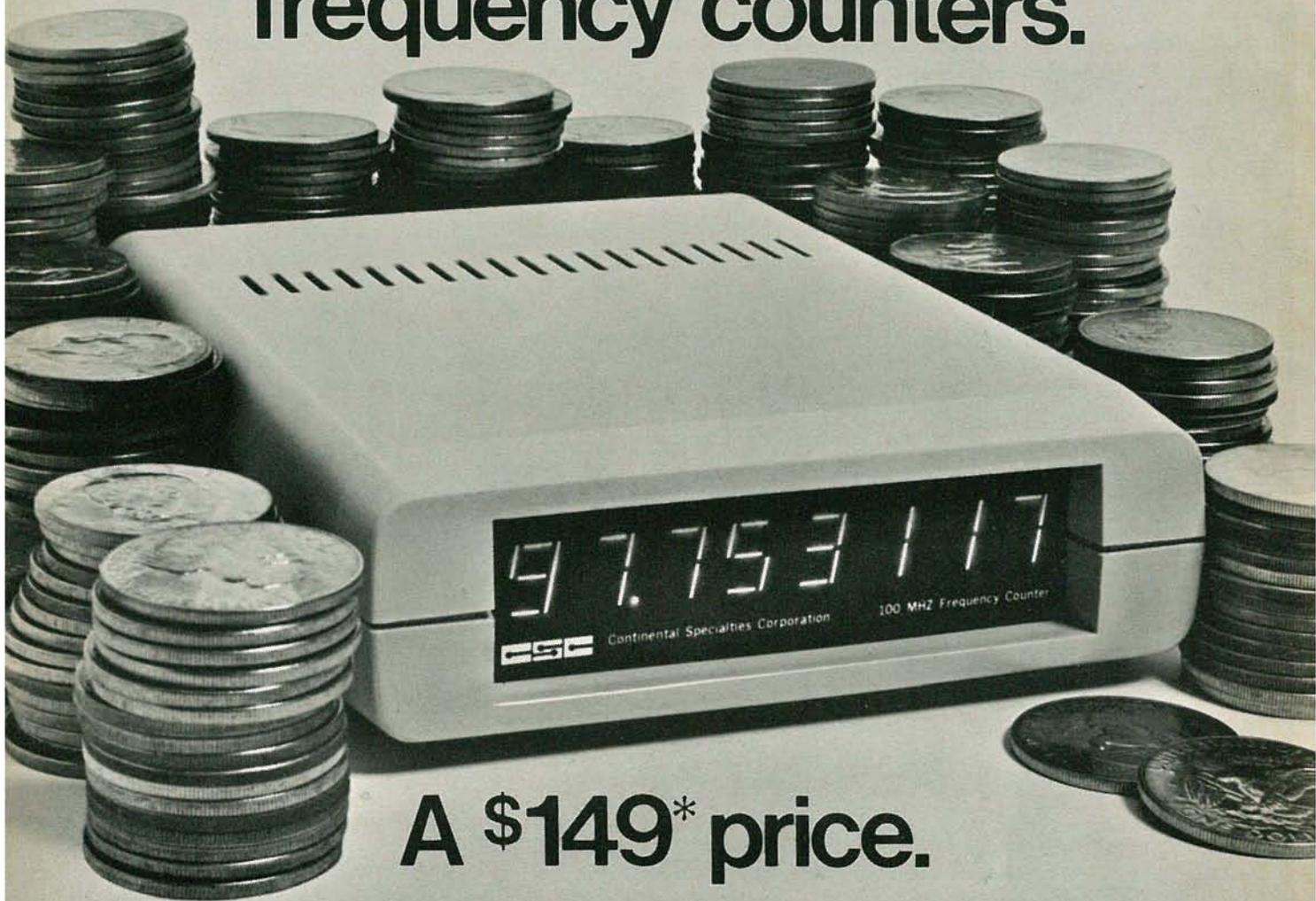Announcing a major breakthrough in \$250 frequency counters.



A \$149* price.

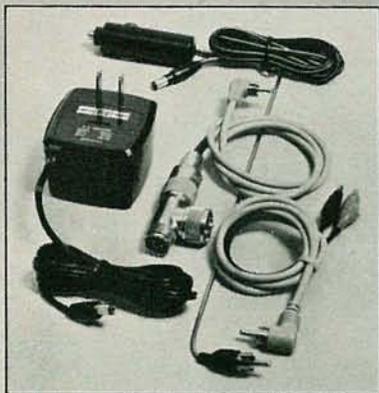

Keep the change! Our MAX-100 is remarkable, even compared to \$250 digital frequency counters. With its turn-on-and-read operating simplicity. Direct 8-digit readings. Big, bright, display. And under-20 Hz to over-100 MHz range (past 500 MHz with optional prescaler).

It has all the features you'd take for granted, even at \$250. Like high sensitivity, accuracy and stability. Lead-zero blanking. Plus visual indications of overflow and low battery. (The flashing low-voltage indication also prolongs the counter's

useful battery life!)

MAX-100 is comfortable anywhere, monitoring nearby RF transmitters with its built-in mini-whip antenna. Or any other CW, AM, or FM signal via clip-lead cable or accessory low-loss tap-off cable. Powered by your choice of alkaline cells or rechargeable nicads with battery eliminator/chargers that operate from car cigarette lighter, 110 or 220 VAC mains.

CSC's incredible MAX-100 solves all your problems but one: what to do with the \$101 change.

Smarter tools for testing and design.

CONTINENTAL SPECIALTIES CORPORATION



Call toll-free for details
1-800-243-6077
8:30AM-5:00PM Eastern Time

70 Fulton Terr., New Haven, CT 06509 (203) 624-3103, TWX 710-465-1227
OTHER OFFICES: San Francisco (415) 421-8872, TWX 910-372-7992
Europe: CSC UK LTD. Phone Saffron-Walden 0799-21682, TLX 817477
Canada: Len Finkler Ltd., Ontario

*Suggested U.S. resale. Available at selected local distributors. Prices, specifications subject to change without notice. © Copyright 1979 Continental Specialties Corporation

CIRCLE 31 ON FREE INFORMATION CARD



Bone FoneTM

A new concept in sound technology may revolutionize the way we listen to stereo music.

The Bone Fone surrounds your entire body with a sound almost impossible to imagine.

You're standing in an open field. Suddenly there's music from all directions. Your bones resonate as if you're listening to beautiful stereo music in front of a powerful home stereo system.

But there's no radio in sight and nobody else hears what you do. It's an unbelievable experience that will send chills through your body when you first hear it.

AROUND YOU

And nobody will know you're listening to a stereo. The entire sound system is actually draped around you like a scarf and can be hidden under a jacket or worn over clothes.

The Bone Fone is actually an AM/FM stereo multiplex radio with its speakers located near your ears. When you tune in a stereo station, you get the same stereo separation you'd expect from earphones but without the bulk and inconvenience. And you also get something you won't expect.

INNER EAR BONES

The sound will also resonate through your bones—all the way to the sensitive bones of your inner ear. It's like feeling the vibrations of a powerful stereo system or sitting in the first row listening to a symphony orchestra—it's breathtaking.

Now you can listen to beautiful stereo music everywhere—not just in your living room. Imagine walking your dog to beautiful stereo music or roller skating to a strong disco beat.

You can ride a bicycle or motorcycle, jog and even do headstands—the Bone Fone stays on no matter what the activity. The Bone Fone stereo brings beautiful music and convenience to every indoor and outdoor activity without disturbing those around you and without anything covering your ear.

SKI INVENTION

The Bone Fone was invented by an engineer who liked to ski. Every time he took a long lift ride, he noticed other skiers carrying transistor radios and cassette players and wondered if there was a better way to keep your hands free and listen to stereo music.

So he invented the Bone Fone stereo. When he put it around his neck, he couldn't believe his ears. He was not only hearing the music

and stereo separation, but the sound was resonating through his bones giving him the sensation of standing in front of a powerful stereo system.

AWARDED PATENT

The inventor took his invention to a friend who also tried it on. His friend couldn't believe what he heard and at first thought someone was playing a trick on him.

The inventor was awarded a patent for his idea and brought it to JS&A. We took the idea and our engineers produced a very sensitive yet powerful AM/FM multiplex radio called the Bone Fone.

The entire battery-powered system is self-contained and uses four integrated circuits and two ceramic filters for high station selectivity. The Bone Fone weighs only 15 ounces, so when worn over your shoulders, the weight is not even a factor.

BUILT TO TAKE IT

The Bone Fone was built to take abuse. The large 70 millimeter speakers are protected in flexible water and crush resistant cases. The case that houses the radio itself is made of rugged ABS plastic with a special reinforcement system. We knew that the Bone Fone stereo may take a great deal of abuse so we designed it with the quality needed to withstand the worst treatment.

The Bone Fone stereo is covered with a sleeve made of Lycra Spandex—the same material used to make expensive swim suits, so it's easily washable. You simply remove the sleeve, dip it in soapy water, rinse and let the sleeve dry. It's just that easy. The entire system is also protected against damage from moisture and sweat making it ideal for jogging or bicycling.

The sleeve comes in brilliant Bone Fone blue—a color designed especially for the system. An optional set of four sleeves in orange, red, green and black is also available for \$10. You can design your own sleeve using the pattern supplied free with the optional kit.

YOUR OWN SPACE

Several people could be in a car, each tuned to his own program or bring the Bone Fone to a ball game for the play by play. Cyclists,

joggers, roller skaters, sports fans, golfers, housewives, executives—everybody can find a use for the Bone Fone. It's the perfect gift.

Why not order one on our free trial program and let your entire family try it out? Use it outdoors, while you drive, at ball games or while you golf, jog or walk the dog. But most important—compare the Bone Fone with your expensive home stereo system. Only then will you fully appreciate the major breakthrough this product represents.

GET ONE SOON

To order your Bone Fone, simply send your check or money order for **\$69.95** plus \$2.50 postage and handling to the address shown below. (Illinois residents add 5% sales tax.) Credit card buyers may call our toll-free number below. Add \$10 if you wish to also receive the accessory pack of four additional sleeves.

We'll send you the entire Bone Fone stereo complete with four AA cell batteries, instructions, and 90-day limited warranty including our prompt service-by-mail address.

When you receive your unit, use it for two weeks. Take it with you to work, or wear it in your car. Take walks with it, ride your bicycle or roller skate with it. Let your friends try it out. If after our two-week free trial, you do not feel that the Bone Fone is the incredible stereo experience we've described, return it for a prompt and courteous refund, including your \$2.50 postage and handling. You can't lose and you'll be the first to discover the greatest new space-age audio product of the year.

Discover the freedom, enjoyment, and quality of the first major breakthrough in portable entertainment since the transistor radio. Order a Bone Fone stereo at no obligation, today.

*Pending FCC approval.

JS&A PRODUCTS
THAT THINK[®]

Dept. RE One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-7000
Call TOLL-FREE 800 323-6400
In Illinois Call (312) 564-7000

©JS&A Group, Inc., 1979

HICKOK LX SERIES MULTIMETERS OBSOLETE YOUR TRUSTY OLD VOM!

Here are the truly inexpensive, no nonsense, high performance DVOM's you've been looking for! Compact. Lightweight. Easy to read, indoors or out. Accurate. Precise. Reliable. Rugged. Safe. Self-contained. Easy to hold and operate with the same hand.

A complete line of inexpensive accessories is available to extend other capabilities far beyond those of a comparably priced VOM.

All the super-durable, high quality professional meter you need for service and maintenance work at an analog price. So why pay as much for analog inaccuracy...or more for digital frills?

Write today for complete details or contact your local Hickok distributor. Better yet, call us toll free, outside Ohio, at 800-321-4664.

LX303 — \$74.⁹⁵

LX304 — \$89.⁹⁵

- Automatic polarity, zero and overrange indication
- Easy-to-read ½" high LCD display
- ½ year battery life in typical use
- 12 oz. including 9V battery
- Withstands 4 ft. drop without loss of accuracy
- Automatic decimal point, built in low battery indicator, diode and transistor testing capability (LX304 only)

Carry it in your pocket, brief case or tool box and enjoy on-the-spot accuracy whenever and wherever you need it.

No need to worry about damage. It's built to take it...so you can take it with you wherever you go.



HICKOK
the value innovator

THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

CIRCLE 59 ON FREE INFORMATION CARD

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS
Electronics publishers since 1908

FEBRUARY 1980 Vol. 51 No. 2

- BUILD**
- 43 **AUDIO POWER LEVEL METER**
Hook it up to your hi-fi and protect your amplifier and speakers against power overload. **Joseph Gorin**
- 47 **SATELLITE TV EARTH STATION**
Build your own backyard installation for under \$1000. **Bob Cooper**
- 56 **VERSATILE SWITCHING REGULATOR**
This circuit can be programmed for step up, step down, positive, negative, voltage and current regulation. **Robert Frosthalm**
- 61 **NOT JUST ANOTHER DIGITAL CLOCK**
5½-inch high single-digit LED readout makes this clock unique. **John D. Warobiew**

ON THE COVER

The LED bar-graph audio power level meter shown is not a wattmeter, but a level indicator that is calibrated to your amplifier's clipping level. Use the device to protect your amplifier and speakers from power overloads. Shown in contrast to the LED bar-graph display is an analog power level meter. Get started building your own LED bar-graph power level meter today. Construction details start on page 43.

- TECHNOLOGY**
- 4 **LOOKING AHEAD**
Tomorrow's news today. **David Lachenbruch**
- 53 **HOUSEHOLD ANDROID**
Hints on how to design your own. **Martin Bradley Weinstein**

- STEREO**
- 66 **UNDERSTANDING TURNTABLE SPECIFICATIONS**
A look at the factors that affect how your records wear and play. **Len Feldman**
- 69 **R.E.A.L. SOUND TESTS TECHNICS CASSETTE DECK**
Technics model RS-M7 rates Very Good.

- VIDEO**
- 71 **JACK DARR'S SERVICE CLINIC**
Automatic brightness limiters. **Jack Darr**
- 72 **SERVICE QUESTIONS AND ANSWERS**
R-E's Service Editor solves technicians' problems.

- EQUIPMENT REPORTS**
- 26 **Speakerlab Model 2.5 Speaker System**
- 32 **Simpson Model 380 Microwave Leakage Tester**
- 34 **SF Model STD-36 Radio Operating Desk**
- 36 **Panasonic Model RF4900 10-Band Receiver**

- DEPARTMENTS**
- | | | | |
|-----|---------------------------|----|---------------|
| 106 | Advertising Index | 22 | Letters |
| 16 | Advertising Sales Offices | 85 | Market Center |
| 16 | Editorial | 84 | New Products |
| 107 | Free-Information Card | 6 | What's News |

ANNUAL INDEX JANUARY—DECEMBER

1979

To present the maximum number of articles to our readers, we have not published the Annual Index as part of this issue. A 4-page brochure containing this index is available for those who need one. To get your free copy, send a *stamped self-addressed envelope (legal size)* to:

Radio-Electronics
Annual Index
45 East 17th Street
New York, NY 10003

Any requests postmarked on or before April 30 are free. After that date there is a 50¢ fee. Questions and comments about anything other than the Index that are included with your request cannot be handled. Send them separately to our Editorial Offices.

Radio-Electronics, (ISSN 0033-7862) Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Controlled Circulation Postage Paid at Concord, NH. One-year subscription rate: U.S.A. and U.S. possessions, \$13.00, Canada, \$16.00. Other countries, \$18.00. Single copies \$1.25. © 1980 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

Seeing & hearing: Medical electronics is growing at an accelerated pace, thanks to microprocessors and super-miniaturization. Two of the newest products are designed as aids to the blind and deaf: (1) IBM plans to offer a talking typewriter this year (1980). Equipped with a voice-synthesis device, the typewriter pronounces the words as they're typed into a magnetic memory. The material can be corrected before it's transferred to paper. IBM says the system has an unlimited vocabulary and will help blind typists produce "error-free copy." Prices of the typewriters will range from \$4,900 to \$7,400, the speech-synthesis unit an additional \$5,300. (2) Working with funds from NASA and Veterans Administration, the Research Triangle Institute in North Carolina is developing a microprocessor-based system to help the deaf lip-read. A trained lipreader can properly identify only about 25% of syllables, but NASA claims the *Autocuer* could increase comprehension to about 90%. The *Autocuer* uses an LED display to project representations of sounds as nine simple patterns in the viewer's field of vision, each pattern corresponding to a different sound. The goal is to build the LSI circuitry into a pair of eyeglasses, using the lenses to project the LED symbols into the wearer's field of vision, where they can be seen alongside the speaker's lips.

Voice-activated: While many American semiconductor manufacturers are preoccupied with speech synthesis, the Japanese are intrigued by what could be considered the opposite—voice activation. At the Japan Electronics Show, Sanyo showed a whole roomful of appliances that respond to the human voice. When someone observes vocally, "it's warm here," an electric fan turns on automatically. "Let's watch TV" is the cue for the television set; "it's dark," activates the lights, and so on.

Combining voice activation with speech synthesis, Toshiba has demonstrated a TV set that it says it plans to introduce in the United States this year. It can be programmed to accept verbal commands from 2 different people, can be ordered to turn on, change channels, and so forth. The TV set has a two-word vocabulary. When a command is accepted, a female voice replies "O.K." When it can't perform as ordered, it requests "repeat."

Video programming: With home videocassette-recorder ownership now past the million mark, there's an attractive new market for pre-recorded cassette programming, principally feature films. Almost every major movie maker is distributing some titles on videocassettes, and most—including Paramount, Allied Artists, Columbia and Warner Brothers—are handling their own distribution. Fotomat is now renting videocassette movies through its more than 3,700 retail outlets. A research company, Esselte Video, estimates that 80 different program sources are now offering a total of 3,500 different programs. Two major video clubs—patterned after the Book-of-the-Month Club—have become established nationwide: Time-Life Video and VidAmerica. The actual size of the home video software market is something of a mystery, and there are estimates that it could go as high as 2 to 3 million cassettes in 1980. The difficulty of estimating is compounded by the uncounted number of bootleg cassettes now on the market.

Pirate cassettes pose a sticky problem because of the ease with which magnetic tape may be duplicated and the big money involved. One source estimates that 50% of the bootlegged titles are copied from cable TV, and many of them show up in the Middle East as well as on the U.S. market. There are reports of a pirate who is making \$4,000,000 a year on bootlegged cassettes. At one point, he paid \$500 for a copy of "The Deerhunter" on 3/4-inch tape and sold \$30,000 worth of 1/2-inch duplicates in Saudi Arabia in four months. The FBI has conducted many raids on allegedly illegal duplicators, but so far has only scratched the surface.

Most legitimate pre-recorded cassettes are encoded to prevent casual copying. This generally involves changing the frequency and amplitude of the vertical sync pulse during the vertical interval. Although this makes copying difficult for non-technical amateurs, the system is easily defeated by the professional bootlegger. These encoding systems have become controversial, since they can throw some home TV sets out of sync—and many videotape program suppliers will exchange encoded tapes for non-encoded ones when there are customer complaints.

How many screens? Another Toshiba marvel, scheduled for introduction this year, is a 25-inch color TV which can display four 10-inch color pictures on its screen simultaneously. It has a built-in frame-grabber to freeze any picture on remote-control command. Two-picture sets were introduced in Europe in 1977 by many manufacturers without great success—they're all off the market now. Sharp is currently selling a color set that can superimpose a small monochrome picture from another channel in the corner of the screen. Sampo has a set with one big color screen and two small black-and-white ones. If people really do want to watch two or more pictures at once, the next step could be the application of the same principle to audio. How about a hi-fi that lets you listen to two musical selections at the same time—one with each ear?

Projection TV multiples: Although total sales of projection TV sets last year probably were equal to only two or three days' production of direct-view sets, the giant screen seems to be a growing part of the business. With the exception of RCA (as of press time), every major American and Japanese TV set maker was offering or preparing to offer projection sets—in addition to specialist companies such as Advent, Kloss Video, Projection Systems Inc. and Muntz. Quality is improving rapidly, thanks largely to improvements in optics, and prices appear to be poised for a decline. Both of these developments probably have been influenced most by the recent introduction of a plastic lens with a speed of F1, which is beginning to rival the quality of glass lenses at a lower price.

Despite the relatively low sales of projection sets and their rather grandiose space requirements, the life-sized screen has captured the public imagination, and it's probable that no other product in history has ever gotten so much publicity per dollar of sales.

DAVE LACHENBRUCH
CONTRIBUTING EDITOR

Dial precise tip temps



with new **Weller** electronic-controlled, variable temperature soldering stations.

Now you can precisely dial-in any soldering tip temperature you want from 350°F to 850°F, and lock the setting, with new Weller Models EC1000 and EC2000 Variable Temperature, Electronically Controlled Stations. No tip changing to change temperatures.

Temperature setting and tip temperature are displayed on a three-digit LED readout (Model EC2000) with a resolution and setability of $\pm 1^\circ\text{F}$. *An exclusive Weller feature!*

Dynamic response to soldering load variation is assured by a high precision platinum sensor—*another Weller exclusive*—that is mounted deep inside the solid copper iron plated tip and by full proportional heater control. If an iron is damaged or misplaced, another one can be plugged into either EC power unit without recalibrating temperature settings. *Still another Weller exclusive.*

Power units are calibrated to within $\pm 10^\circ\text{F}$. Temperature control is maintained over line voltage variations of $\pm 10\%$ and ambient temperature range of 60°F to 110°F.

Thyristor power control with zero voltage thyristor

drive insures that there will be no high voltage spikes or magnetic fields on the soldering tool tip. In addition the power unit is isolated from the A.C. line by a transformer so that only 24 V.A.C. isolated voltage drives the heating element, and the tool tip is grounded through the power unit three-wire line cord. These features combine with the calibrated temperature control to provide ultimate safety for sensitive, costly electronic circuit hand soldering.

Zero crossing control of heater current eliminates RFI/EMI and accurate time proportioning reduces tip temperature hysteresis.

Power unit is furnished with extra large sponge, iron holder, tip holding tray, solder drip shield, circuit breaker and lighted on-off switch. Soldering tool has high temperature plastic handle and heat shield, burn-resistant silicone rubber cord, and locking plug that mates with power unit receptacle. Unit is U.L. listed.

Stations are normally supplied with ETA 1/16" screwdriver tip. Eight other iron plated tips from 1/32" to 3/16" diameter are optional accessories.

In stock at leading electronic distributors nationwide. In-plant, on-the-job demonstrations can be arranged.



The Cooper Group
Electronics Division

BOKER* • CRESCENT* • LUFKIN* • NICHOLSON* • WELLER* • WISS* • XCELITE*
P.O. BOX 728, APEX, NORTH CAROLINA 27502, 919/362-7511

CIRCLE 22 ON FREE INFORMATION CARD

New remote-control TV is commanded by voice

Sanyo Electric has produced a prototype television receiver in which all the functions ordinarily controlled manually—or with various manual remote controls—can be effected by two-word voice commands. The words "television power" for example, turn the set on or off, and "channel 8" tunes it to that channel.

With a two-word system, 16 words, including the numbers from 2 to 13, are sufficient. A two-word format has been found best to assure correct performance. Since the set has been designed for operation by two persons, 32 words are used.

The commands have to be registered on the receiver's memory by the operator, to form a model to which the commands will be compared. The words are registered by throwing a registration switch on the panel and speaking the commands into a microphone on the set. The commands are then stored in memory by an Intel 8085 central processing unit.

When a command is given—either into a remote control radio mike or into the microphone on the set, it is compared with the registered commands in the standard pattern memory, and the command most closely similar to that given by the input voice is executed.

Voice control of devices is the most natural and least complicated, and requires a minimum of effort. Sanyo believes that other home appliances can be controlled by voice, and is working on such products.

New lithium batteries meet wide range of needs

A new line of high-energy lithium batteries has just been announced by Electrochem Industries of Clarence, NY. Three variations have been developed to meet specific customer needs.

The bromine complex (BCX) cells are designed for lightweight, long-life portable power sources for the electronics, the communications, and the photographic industries. Solid-cathode (SCX) cells find special application in the computer field, where

reliable, long-life batteries are needed for such applications as "keep-alive" power supplies for CMOS and NMOS memories. The high-temperature (HiT) cells are designed to deliver continuous power at temperatures as high as 150°C (302°F). They serve in such applications as power sources in high-temperature locations for well-logging.

"We expect the bulk of our business to be in designing primary sources to meet specific customer applications," says Electrochem president, Dr. C. C. Liang.

Satellites will get better, not necessarily bigger

Though some persons have imagined the future advances in satellite communication to lie in the direction of "truly giant satellites" that would have to be assembled and maintained in space, the greatest improvement in future satellite design will be the attainment of longer lifetimes, Hughes Aircraft's Dr. Harold A. Rosen told a meeting at the International Telecommunications Union's *Telecon 79* in Geneva.

Advances in ground technology will also be an important feature in future satellite improvements. The additional of several advanced digital processors to ground equipment has resulted in significant improvement in the transmission of voice, data and video signals by satellite, he reported. A system that compresses bandwidths to about one-tenth, which increases satellite capacity and consequently reduces charges, has been developed. This makes a substantial increase in video conferencing via satellite probable.

The ultimate satellite size will be one that can be launched in one piece and that will reach the end of its normal life unattended, Dr. Rosen believes.

Microprocessor developer to receive Ballantine Medal

The Stuart Ballantine Medal, one of the nation's most important awards for scientific and technical achievement, was awarded last October to Marcian E. (Ted) Hoff, of Intel Corp., Santa Clara, CA., for

his development of the microprocessor. The medal is awarded annually by the Franklin Institute of Philadelphia, and in the past has been bestowed on such persons as John Bardeen, co-inventor of the transistor, and Claude Shannon, developer of information theory.



DR. MARCIAN E. HOFF

Dr. Hoff, in addition to his work on digital microprocessors, contributed to the development of the first high-density computer memory devices, and was also responsible for the development of the first analog microprocessor.

Install-your-own telephones bring trouble to Ma Bell

Since it has become possible for telephone customers to buy their own phones on the open market, the phone company has been troubled with an increasing number of illegally-owned phones. A recent study showed that over half the phones sold at retail are used without phone company knowledge.

To add to the problem, many telephone owners are using phones they obtained illegally. Most phones picked up at flea markets, for example, are suspected to be "hot." The study states: "29.9 percent of the owners of Western Electric phones are using stolen merchandise."

Phone owners may buy decorative phones to replace their present ones, may wish to add extensions, or get extra phones for extension lines already installed. Since (in every state but Massachusetts) the company makes a monthly charge for each subscriber-owned phone, many owners see no reason to report their purchases to the company.

Legal or illegal, unreported phones pose
continued on page 12



NEW LITHIUM BATTERIES, a sampling of custom and off-the-shelf types.

Facts from Fluke on low-cost DMM's

Is this any way to treat a \$129 multimeter?

In the rough world of industrial electronics, even a precision test instrument can get treated like dirt. You need all the ruggedness and dependability you can get in a DMM for field use.

You'll find these qualities and more in the Fluke line of low-cost DMM's. Our DMM's have been dropped from towers, stepped on, and run over by construction equipment. And they've survived because we never cut corners on quality, even on our lowest-priced, six-function Model 8022A Troubleshooter at \$129 U.S.

Take a close look at a low-cost DMM from Fluke and you'll notice tough, lightweight construction that stands up to the hard knocks of life.



Sturdy internal design and high-impact, flame-retardant shells make these units practically indestructible. Right off the shelf, they meet or exceed severe military shock/vibration tests.

Even our LCD's are protected by cast-tempered plastic shields. We use rugged CMOS LSI circuitry for integrity and endurance, and devote a large number of

components to protection against overloading, accidental inputs and operator errors.

We go to these lengths with all our low-cost DMM's to make sure they are genuine price/performance values. You can count on that. Because, that's what leadership is all about.

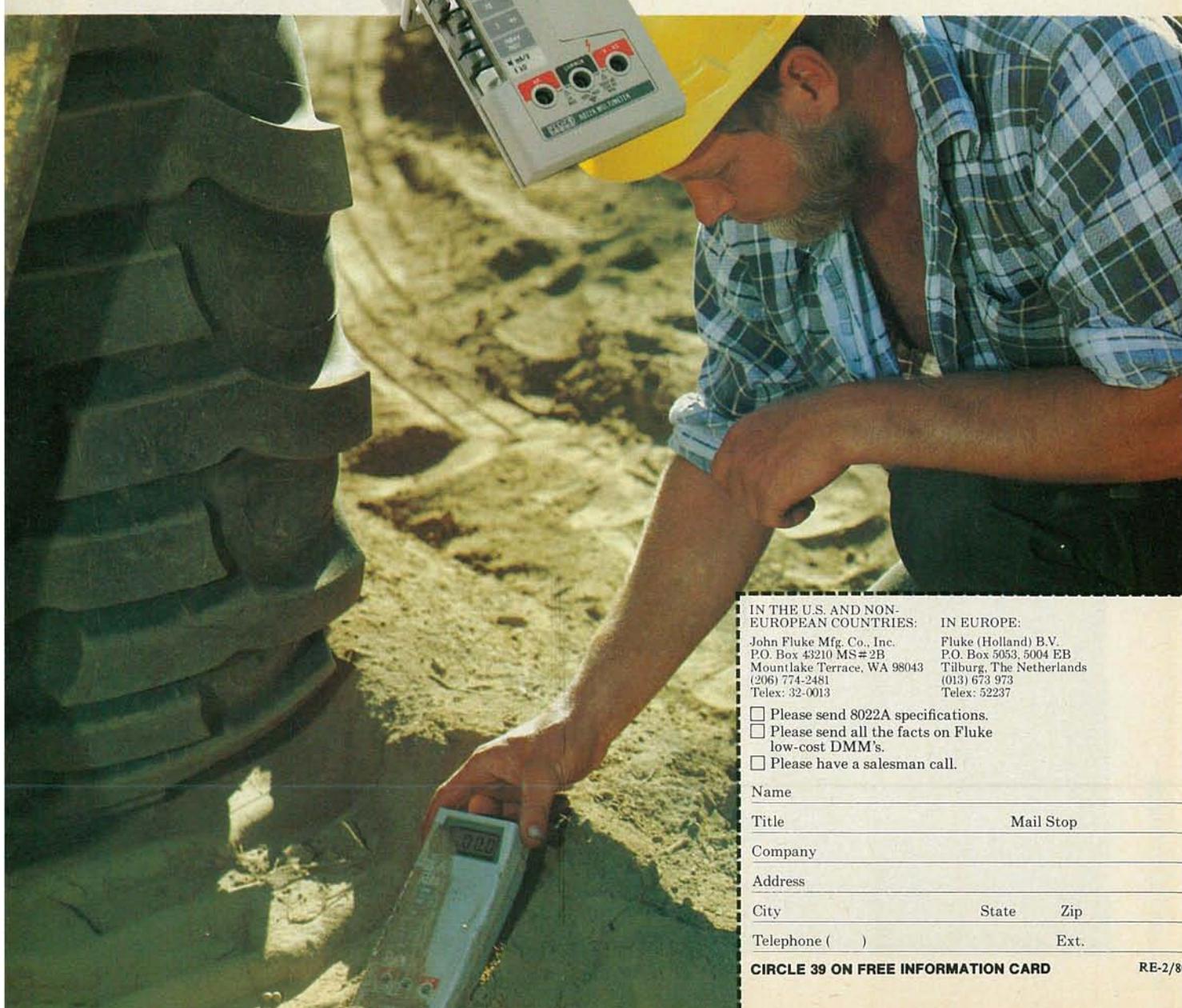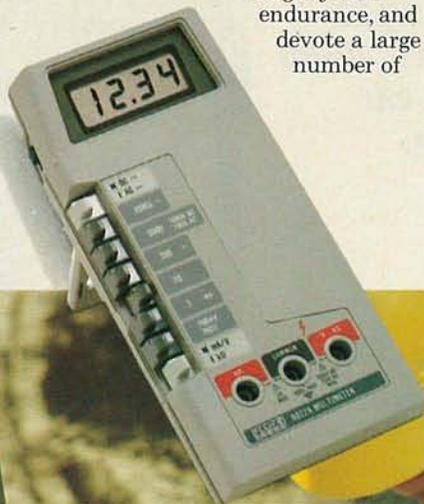For more facts on DMM reliability and where to find it, call toll free **800-426-0361**; use the coupon below; or contact your Fluke stocking distributor, sales office or representative.



IN THE U.S. AND NON-EUROPEAN COUNTRIES:

John Fluke Mfg. Co., Inc.
P.O. Box 43210 MS#2B
Mountlake Terrace, WA 98043
(206) 774-2481
Telex: 32-0013

IN EUROPE:

Fluke (Holland) B.V.
P.O. Box 5053, 5004 EB
Tilburg, The Netherlands
(013) 673 973
Telex: 52237

- Please send 8022A specifications.
- Please send all the facts on Fluke low-cost DMM's.
- Please have a salesman call.

Name _____

Title _____ Mail Stop _____

Company _____

Address _____

City _____ State _____ Zip _____



Telephone () _____ Ext. _____

CIRCLE 39 ON FREE INFORMATION CARD

RE-2/80

New from NRI!
25" color TV that tunes
DIAGONAL
by computer, programs
an entire evening's
entertainment.

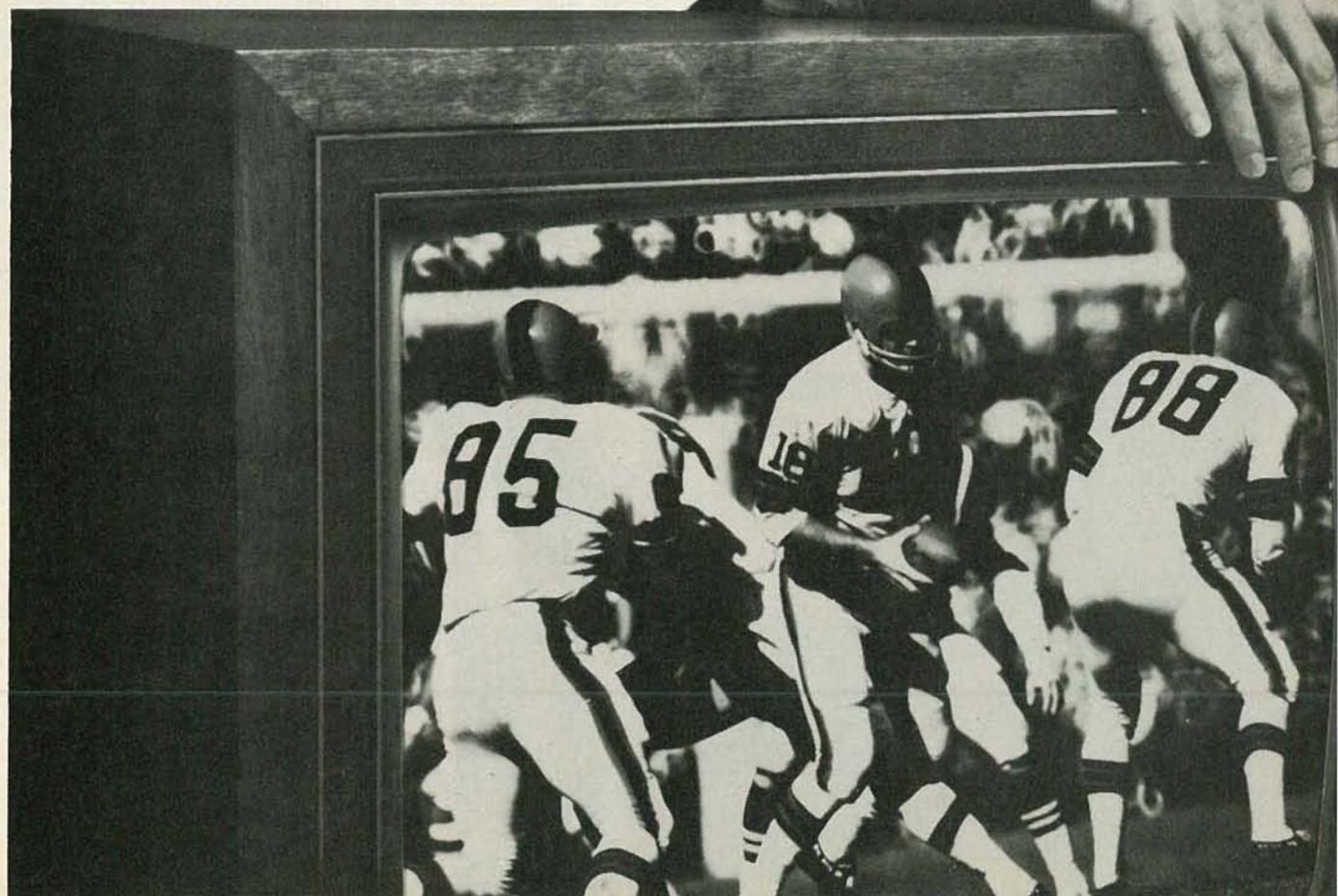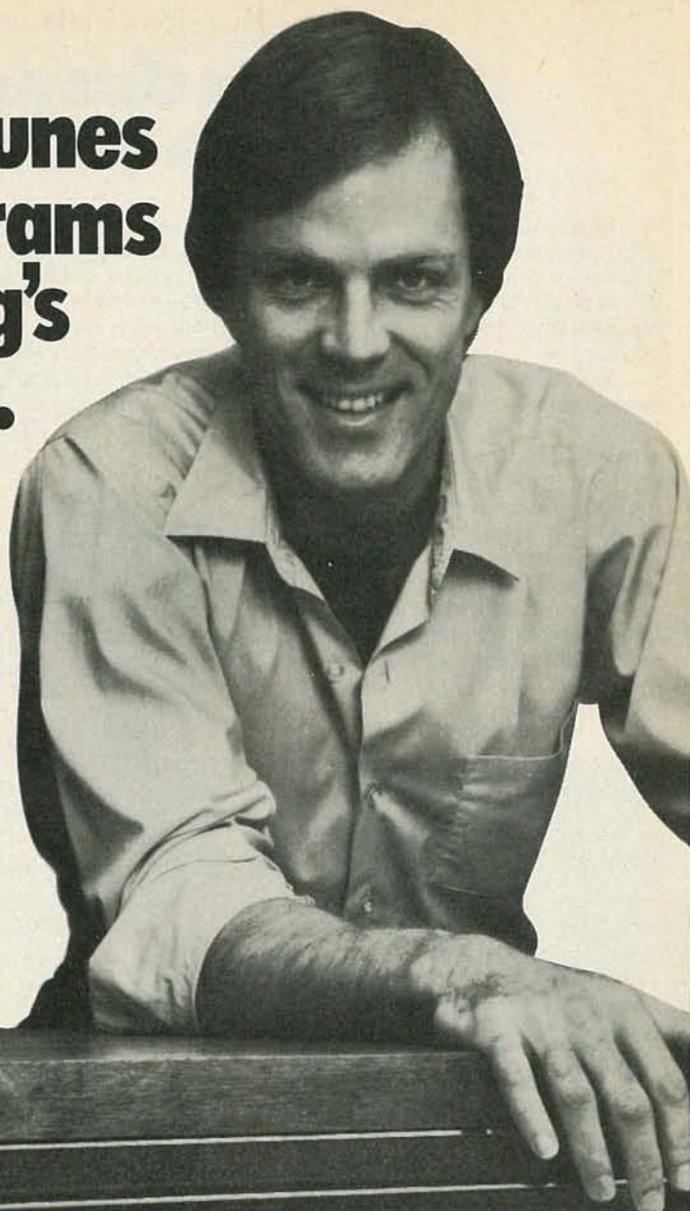Just part of NRI's training in
servicing TV, stereo systems, video
tape and disc players, car
and portable radios.



Only NRI home training prepares you so thoroughly for the next great leap forward in TV and audio... digital systems. Already, top-of-the-line TV's feature digital tuning, computer programming is appearing, and new digital audio recording equipment is about to go on the market.

NRI is the only home study school to give you the actual "hands-on" training you need to handle servicing problems on tomorrow's electronic equipment. Because only NRI includes this designed-for-learning, 25" diagonal color TV with electronic tuning, built-in digital clock, and computer programmer as part of your training. With this advanced feature, you can pre-program an entire evening's entertainment... even key lock it in to control children's viewing.

As you assemble it, you learn how digital tuning systems work, how to adjust and service them. You work with the same advanced features used in the new programmable TV's and video tape recorders. It's exclusive NRI training that keeps you up with the leading edge of technology.

Exclusive Designed-for- learning Concept

The color TV you build as part of NRI's Master Course looks, operates, and performs like the very finest commercial sets. But behind that pretty picture is a unique designed-for-learning chassis...



the only such unit in the world. Rather than retrofit lessons to a hobby kit or an already-built commercial set, NRI instructor/engineers have designed this television so each step of construction is a learning experience.

As you build it, you perform meaningful experiments. You see what makes each circuit work, what it does, how it interacts with other circuits. You even introduce defects, troubleshoot and correct them as you would in actual practice. And you end up with a magnificent, big-picture TV with advanced features. One you can sell or use in your home.

Also Build Stereo, Test Instruments

That's just a start. You demonstrate basic principles and circuits on the unique NRI Discovery Lab,[®] then apply them as you assemble a fine AM/FM stereo receiver, complete with speakers. You also get practical experience as you build your own test instruments, including a 5" triggered sweep oscilloscope, CMOS digital frequency counter, color bar generator, and transistorized volt-ohm meter. Use them for learning, use them later for professional servicing of TV, audio, and video equipment.

Complete, Effective Training Includes Video Systems


Using NRI's exclusive methods, you learn far more than TV servicing. You'll be prepared to work with stereo systems, car radios, record and tape players, transistor radios, short-wave receivers, PA systems, musical instrument amplifiers, electronic TV games, even video tape recorders and tape or disc

video players. Your training covers just about every kind of electronic entertainment equipment available now or in the near future.

And because NRI has unmatched experience gained in over 60 years and a million students worth of training, your course is designed for ease of learning and practical utility. You need no previous experience of any kind. Starting with the basics, exclusive "bite-size" lessons cover subjects thoroughly, clearly, and concisely. "Hands-on" experiments reinforce theory for better comprehension and retention. And your personal NRI instructor is always available for consultation, ready with explanations, answers, and advice.

Send for Free Detailed Catalog... No Salesman Will Call

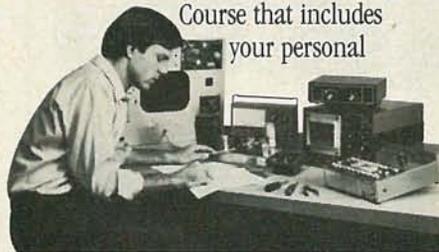Get all the facts on this exciting course and its potential for you by mailing the postage-paid card today. Our free 100-page catalog includes color photos of all kits and equipment, complete lesson plans, convenient time payment plans, and information on other electronics courses. You'll also find out about NRI's new Computer Technology Course that includes your personal



microcomputer. Or Complete Communications with 2-meter transceiver that gets you ready for opportunities in broadcasting, 2-way radio, microwave, and other growing fields. If card has been removed, write to:



NRI Schools
McGraw-Hill Continuing
Education Center
3939 Wisconsin Ave.
Washington, D.C. 20016

what's news

continued from page 6

two problems for the telephone company: lost revenues from monthly charges or from extensions the company might have provided, and additional power problems if too many phones with ringers are added to a local loop.

In many areas, the phone company has actually encouraged customers who move to take out and re-install their own phones. (The company has found that often the cost of sending a man to remove an old phone is greater than the value of the phone.) Customers are thus trained to hook up phones. Modular plugs on all recent installations make the job simple, and more phone owners begin to feel confident about their ability to hook up a "hot" phone.

SATURN PIX STORED IN DIGITS



THE PIONEER SATURN SPACE ENCOUNTER pictures you saw recently on your television screen were assembled from digital storage on disc. The photo above shows a picture being encoded and entered into the still store system for future recall. The process—the ESP-100 Electronic Still Storage System, developed by Adda Corp of Campbell, CA—is microprocessor-controlled and stores color stills in digital form on high-speed, high-capacity computer-fixed disc packs. The stored pictures can then be recalled at any remote location and put on the screen.

Counterfeit video cassettes being sold in the U.S. Northeast

TDK Electronics, a Garden City, NY, manufacturer of audio and video recording products, warns that its SA-C90 cassettes are being counterfeited. Bogus tapes of inferior quality have been offered in the East Coast area for \$2.95, as against the market price of \$5.69.

The counterfeits have a number of differ-

ences from the genuine tapes that enable a buyer or dealer to spot them:

1. **Liner index card:** The printing on the counterfeit is dark and smudgy, the "C90" on the front being especially noticeable. The section detailing performance and warranty information is not found on the counterfeit.
2. **Outer wrapper:** The counterfeits have a nonfunctional cellophane strip for opening, sloppily glued on the top of the wrapper; the genuine cassettes do not.
3. **Norelco box:** The genuine TDK box has a finger indentation at the top for opening. The counterfeit box is plain.
4. **Shell:** The printing on the shell label is dark and of poor quality. The viewing window is smaller and has a raised edge around the outside; the genuine TDK window is flat. There is no production code number on the edge of the shell.
5. **Tape:** Genuine TDK tape is brown; the counterfeit is dark gray.
6. **Carton:** The carton that holds ten tapes is printed in brown only instead of brown and green. It has no lot number stamped on top.
7. **Quality:** The performance and overall sound reproduction of the counterfeit cassettes are significantly inferior to authentic TDK SA-C90 cassettes.

New earth-station antenna cuts interference by 10 dB


A new narrow-beam earth-station antenna exhibited by GTE International Systems at Telecom '79 (Geneva) has a beam so sharp as to make it feasible to position earth stations closer together, as well as permitting closer "parking" of transmitting satellites. The beam width is less than 0.5 degree wide at its 3-dB points as opposed to at least 1 degree for conventional parabolas used in typical earth-stations. Secret of the new antenna is that the horn that picks up the signal reflected from the dish surface is offset, rather than placed at the parabola's focal point. This also increases the gain of the antenna, because the horn is not in the path of the incoming waves, and reduces sidelobes.

The Gregorian-feed configuration coupled with microwave absorption material placed around the circumference of the antenna further reduces the energy coming from the sides, resulting in a reduction of unwanted signal and noise by at least 10 dB. (Because of the offset mounting of the horn, the "dish" departs somewhat from a perfect parabolic shape.)

Since the FCC licenses earth stations on a basis of immunity to interference from

nearby stations, the new antenna with its narrower beam and smaller sidelobes will permit earth stations to be placed closer together.

SOUND MAKES PLASTIC FIBERS

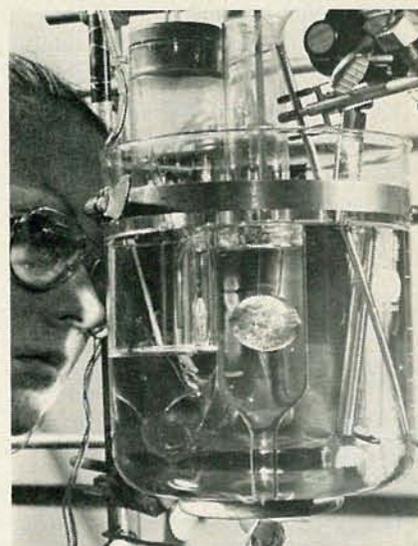

PLASTIC FIBERS STRONGER THAN STEEL are being produced by the Hughes Aircraft Co. laboratories, by vibrating a wire coil in a polymer solution at sonic frequencies and at constant temperature. The material can be seen forming inside the coil in the solution.

Hughes researchers have demonstrated that the fibers can be grown directly on devices to be encapsulated, and thus fill tiny openings and narrow passages often found in resin-encapsulated components. Besides its uses in encapsulation, the new fibers—whose strength per unit weight is several times that of the highest strength steel, show promise for a variety of commercial and industrial applications.

Hughes physicist Joanna Ready is shown making a close-up inspection of the process.

Heath Co. of Benton Harbor is now part of Zenith Corp.

Heath, Michigan-based producer of electronic do-it-yourself kits, instruments, adult educational materials and microcomputer products, has been purchased by and will be operated as a wholly-owned subsidiary of Zenith Corp. New Zenith subsidiaries have been established to operate the 55 Heathkit Electronic Centers in the United States and the Heath business in Canada and Europe.

Heath was founded in 1926 by two aviators, Anthony and Edwards, and originally sold airplane kits. It entered the electronic kit market in 1947. Upon the death of the proprietor, Anthony, in an airplane accident, the company was sold, first to Daystrom, then to Schlumberger interests, from whom it was purchased by Zenith.

R-E



OUR \$69 SOLAR ALARM. A CHALLENGE TO EVERY CHRONOGRAPH IN THE WORLD.

People are bumping into more watch ads these days than at any other point in history.

And if you think companies like Seiko with their \$295 solar alarm chronographs are fighting hard for a place on your wrist, you should see the battle in the Under-\$100-Watch Category.

It's Dog eat Dog. So where did we get the gumption to offer *another* popular-priced mini-genius through the mail? You'd have it too, if you had this watch.

Our \$69 Xernus (its price in stainless) provides every watch and stop-watch function you could ask for (see description below).

Even more important, it offers a level of workmanship and design that you just won't find elsewhere—at even \$20 or \$30 more.

We know, we've looked.

Its display is liquid crystal; the digits are crisp and clear. You get the uncommon convenience of a 24-hour alarm, precise time information for two different time zones. Plus, the latest solar cell technology—to keep your Xernus working for up to 5 years on its original set of batteries. And with an uncanny ± 15 seconds per month quartz accuracy. By the way, Xernus is pronounced *zer'nus*.

Its case, bracelet and back are machined from solid stainless steel. Instead of the thinly plated chrome construction you find on virtually all other chronographs at or near its price.

It's also an incredible 8mm thin.

Much thinner than the Texas Instruments alarm chronograph; much, much thinner than both the widely advertised Advance and Windert. Xernus is even trimmer than the comparably clever \$295 Seiko. By more than 2 mm.

Want more? You get a face crystal that's made from tough, hard mineral glass. Most other chronographs in this price field give you nothing better than scratch-prone plastic.

As a Xernus owner, you can also feel secure about moisture and perspiration. We know, because Xernus has even survived our 12-hour water immersion test.

Save \$60 while Xernus is hungry.

This isn't a small watch company, or even a very new one. In fact, this pioneer in microcomputer timepieces, has

already sold a phenomenal number of chronographs around the world; in countries like Germany, Switzerland and France.

This superb timepiece has been practically everywhere but the U.S. And for that reason, Xernus has agreed to let us offer their chronograph at a dramatic discount. In stainless, it lists for \$129, but you get it at a \$60 saving.

You save even more when you order the Xernus solar alarm in gold (a generous 5 microns over stainless). To be exact, \$70 less than your friends overseas have had to pay.

Each Xernus comes gift-boxed with full instructions, service-by-mail convenience, if needed, and a full one-year guarantee against defects by its manufacturer.


And The Sharper Image gives you two weeks to decide if it's really the watch for you. If not, simply send it back as new for a full and prompt refund. But order now to take advantage of this special introductory price.

Normal time display:




See hours, minutes, seconds (or date), plus AM/PM and day of the week.

Stopwatch display:

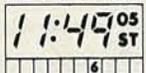

12-hour timing to 1/10 second. Even lap and 1-2 finishes.

Alarm setting display:

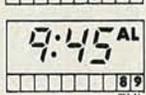

Set for AM or PM. Audible beep lasts a full minute.

Calendar setting display:



Set time/date for 2 time zones. End-of-month adjustment is automatic.

Extra light at night:



Push a button for bright face illumination.

ORDER TOLL-FREE.

Credit card holders may use our toll-free ordering number. Or send check for \$69 for stainless, \$89 for gold plus \$2.50 delivery. (In California, add \$4.14 tax for stainless and \$5.34 for gold).

800 227-3436

In California 800 622-0733

THE SHARPER IMAGE™

260 California St., Dept. XE-118
San Francisco, CA 94111
(415) 788-4747

Sabtronics gives you DMMs and Frequency Counters with more features, better performance and incredibly lower prices

Model 2010A Bench/Portable DMM:

Features: 3½ digit LED display • 31 measurement ranges 6-Functions • 0.1% Basic DCV accuracy • Touch-and-hold capability • Hi-Lo Ohms • 40 Hz to 40 kHz frequency response • Auto Zero, Auto Polarity • Overload protected • Overrange indication • Single chip LSI logic • Laser-trimmer resistor network and ultra-stable band-gap reference for better long term accuracy • Built-in NiCd battery charging circuit.

Brief Specifications: DC Volts 100µV to 1000V in 5 ranges; AC Volts 100µV to 1000V in 5 ranges; DC Current 0.1µA to 10A in 6 ranges; AC Current 0.1µA to 10A in 6 ranges; Resistance 0.1Ω to 20MΩ in 6 ranges; Diode Test Current 0.1µA to 1mA in 3 ranges; Input impedance, 10MΩ on AC and DC volts; Power requirement, 4.5 to 6.5 VDC (4 "C" cells) or optional AC adapter/charger.



\$89.95



Model 2015A Bench/Portable DMM:

Same features and specifications as Model 2010A except with large, 0.5" LCD 3½ digit display.

Optional Accessories

- #AC-115, AC adapter/charger \$7.95
- #THP-20, Touch and Hold Probe \$19.95
- #NB-120 NiCd Battery Set \$17.00

\$109.95


Model 8610A Frequency Counter:

Features: 8-digit LED display • 10 Hz to 600 MHz guaranteed frequency range (5 Hz to 750 MHz typical) • 3 Gate times • 10 MHz TCXO Time base • Auto decimal point • Overflow indicator • Leading zero blanking • Resolution to 0.1 Hz • Built-in charging circuit for NiCd batteries.

Brief Specifications: Frequency Range, switch selectable, 10MHz, 100 MHz, 600MHz • Sensitivity, ± 10mV RMS to 100 MHz, ± 50mV RMS, 100 MHz to 450 MHz; 90mV RMS 450 MHz to 600 MHz • Impedance, 1MΩ, 10 MHz and 100 MHz ranges; 50 Ω 600 MHz range • Gate time (switch selectable) 0.1 sec, 1 sec, 10 sec • Temperature stability, 0.1 ppm/°C • Ageing rate < ± 5 ppm/yr • Accuracy, 1 ppm or 0.0001% • Input protection, 150V RMS to 10 kHz (declining with frequency) • Power Requirement, 4.5 to 6.5V DC @ 300mA (4 "C" cells) or optional AC adapter/charger (7.5 to 9V DC @ 300 mA).

Also available Model 8110A, same as 8610A except maximum frequency is 100MHz and without battery charging circuit:

\$79.95

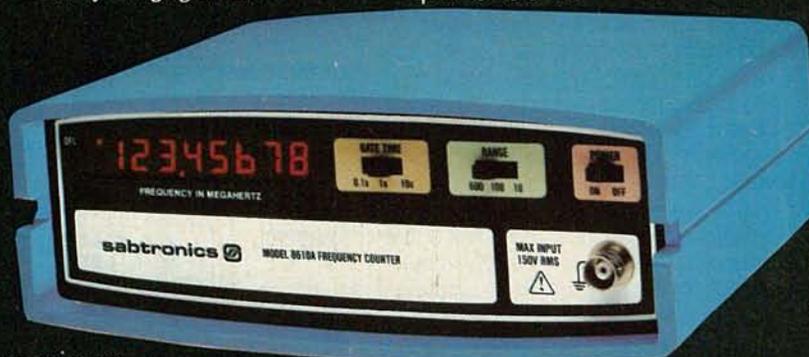

Model 8610A

\$109.95

Making Performance Affordable

sabtronics INTERNATIONAL INC. 

CALL TOLL FREE

1-800-237-5567 (In Continental U.S. only)

Fla. Residents and Foreign Countries Call
(813) 623-2631

Mail in coupon on adjacent page

5709 N. 50th Street M/S 35
Tampa, Florida 33610



Ordering Information

USA - Add \$5.00 per order for shipping & handling. Personal checks have to clear before goods are shipped (allow 2-3 weeks). For faster delivery send cashiers check or money order. 10% deposit for C.O.D. orders. Florida residents add 4% sales tax. CANADA - Add \$7.50 per kit for shipping & handling. No C.O.D. Payment in U.S. funds. OVERSEAS - Add \$21.00 per unit for airmail delivery. Payment by bank draft in U.S. funds.

Sabtronics NEW Hand-held Digital Multimeters. . .

The only thing that beats their performance is their price.

Accurate performance you can rely on, time after time. That's what you expect from a quality DMM. But don't expect to pay as much for it any more. Because now Sabtronics brings you top quality DMMs with *more* features and better accuracy than other comparable units on the market today. And they cost surprisingly less!

We cut the price. Not the quality.

What you get is a precision crafted unit that features single-chip LSI logic, laser trimmed resistor network and a stable band-gap reference element for better long term accuracy. Basic DCV accuracy is 0.1%. The Model 2035A gives you 32 measurement ranges over 6 functions and the Model 2037A an additional two temperature ranges.


First in features. First in price.

Both models feature touch-and-hold capability with the optional probe - it's so convenient, you'll wonder why the expensive models haven't got it yet! And two-terminal input for *all* measurement functions - this eliminates lead switching and makes your job easier. The Model 2037A even has a built-in temperature measuring circuit with a -50°C to

$+150^{\circ}\text{C}$ range (-58°F to $+302^{\circ}\text{F}$) and is supplied complete with the sensor probe. Of course, auto zero, auto polarity and overload protection are standard. And you get 200 hour operation from a single 9V transistor battery. A low battery indicator warns you of the last 20% of battery life. The large, crisp LCD readouts allow easy viewing even in bright sunlight. Your models 2035A & 2037A come with a full one year warranty from Sabtronics International, makers of top quality test equipment.

Biggest value in small DMMs

We are so sure that the Model 2035A and 2037A are the best values available that we offer a money-back guarantee. Examine either unit in your own home for 10 days, and if you are not convinced that it is the best value for your money, return it in its original condition for a prompt and courteous refund of the purchase price (less shipping and handling). Order yours today! Use the convenient order form or call us toll free with your Master Charge or Visa number.

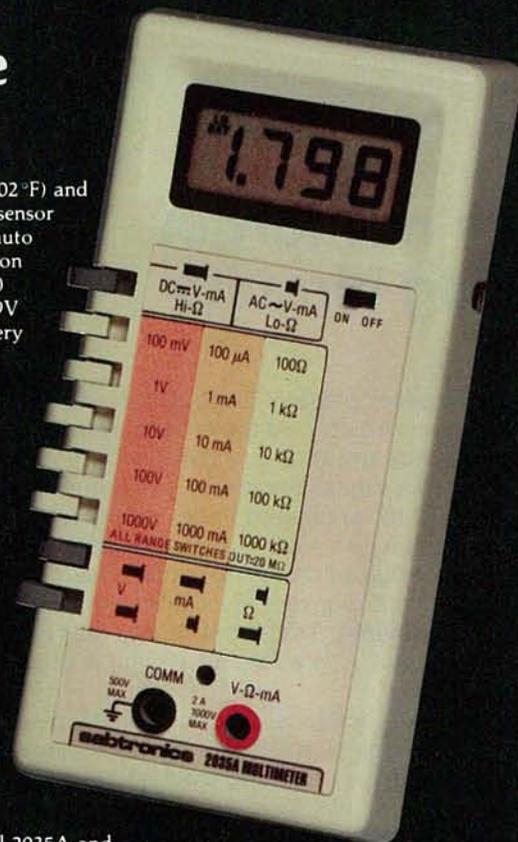

Model 2035A
\$99.95

CALL TOLL FREE
1-800-237-5567 (Continental U.S. only)
Fla. Residents and Foreign Countries Call
(813) 623-2631

or

Mail in coupon
5709 N. 50th Street M/S 35
Tampa, Florida 33610

Making Performance Affordable

sabtronics INTERNATIONAL INC.

BRIEF SPECIFICATIONS:

DC VOLTS: 100 μ V - 1000V, 5 ranges
AC VOLTS: 100 μ V - 1000V, 5 ranges
DC CURRENT: 0.1 μ A - 2A, 5 ranges
AC CURRENT: 0.1 μ A - 2A - 5 ranges
Hi-OHMS: 0.1 Ω - 20M Ω , 6 ranges
Lo-OHMS: 0.1 Ω - 20M Ω , 6 ranges
TEMPERATURE: -50°C - $+150^{\circ}\text{C}$
(-58°F - $+302^{\circ}\text{F}$), 2 ranges
(Model 2037A only)

WEIGHT: 11 oz. (excl. battery)

OVERLOAD PROTECTION: 1000V DC or AC peak all voltage ranges, 250V DC or AC peak all Ohms ranges; 2A/250V fuse all current ranges.

SABTRONICS SERVICE AVAILABLE
IN MOST COUNTRIES OF THE
WORLD

Mail to: Sabtronics International, Inc., 5709 N. 50th Street,
Please send me . . . M/S 35 Tampa, Florida 33610.

Model 2035A Hand-held Multimeter @ \$99.95 each	\$
Model 2037A Hand-held Multimeter @ \$119.95 each	\$
#THP-20 Touch-and-hold Probe(s) @ \$19.95 each	\$
Model 2010A Bench/Portable DMM @ \$89.95 each	\$
Model 2015A Bench/Portable DMM @ \$109.95 each	\$
Model 8110A Frequency Counter @ \$79.95 each	\$
Model 8610 A Frequency Counter @ \$109.95 each	\$
Shipping and Handling @ \$5.00 per unit *	\$
For Delivery in Florida, add 4% Sales Tax	\$

Enclosed Check Money Order Master Charge Visa TOTAL \$
(Allow 2-3 weeks clearance time for personal checks). 10% deposit for C.O.D.
Charge my credit card # _____ Expiry Date _____

Name _____
Street _____ Apt. _____
City _____ State _____ Zip _____
*Continental U.S. only. AK, HI & PR: \$6.00. Canada: \$7.50. Foreign: \$21.00 Airmail.

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback, editor-in-chief and publisher

Larry Steckler, CET, editor

Arthur Kleiman, managing editor

Robert F. Scott, CET, W2PWG,
technical editor

Jack Darr, CET service editor

Leonard Feldman
contributing high-fidelity editor

Karl Savon, semiconductor editor

Herb Freidman, communications editor

David Lachenbruch, contributing editor

Earl "Doc" Savage, K4SDS, hobby editor

Ruby Yee, production manager

Robert A. W. Lowndes, production
associate

Marie J. Stolfi, production assistant

Gabriele Margules, circulation director

Arline R. Fishman,
advertising coordinator

Cover design by Louis G. Rubsamen
Cover photo by Robert Lewis

Radio Electronics is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003
(212) 777-6400
President: M. Harvey Gernsback
Vice President: Larry Steckler
Secretary/Treasurer: Carl A. Gernsback

ADVERTISING SALES

Paul McGinnis
Director of Marketing

EAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
The Ralph Bergen Co.
540 Frontage Road—Suite 361-A
Northfield, Illinois 60093
(312) 446-1444

PACIFIC COAST Mountain States

Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810
Sales Mart Building
1485 Bayshore Blvd., Box 140
San Francisco, CA 94124
(415) 467-0125

Let's not forget analog circuits

Just about every piece of electronic equipment being introduced today contains digital circuitry. At the present rate, it won't be long before every electronic device around us will contain at least one digital circuit. The reasons for this digital explosion are numerous; but perhaps the most noteworthy is that engineers find it easier and economically practical to meet their design goals using digital circuits. Today's IC's closely resemble function modules containing whole circuits. As a result, engineers can design on a block-diagram level rather than be intricately involved with discrete components. That's not to say that designing a digital circuit is easy—its not. But *it is easier* to design a digital circuit than its analog counterpart.

We electronic activists find ourselves becoming more and more involved in designing, prototyping and troubleshooting digital circuits. We read more about them and train ourselves to become digital experts. However, we must not lose sight of the fact that we live in an analog world. As a result, most digital-based devices must interface to analog signals. (I use the word "most" because I don't want to answer dozens of letters pointing out that pocket calculators are digital all the way from keyboard to the seven-segment LED display.) Also, there are many circumstances that don't permit the use of digital circuits. For example, the low-noise amplifier described in our current series on Satellite TV Receivers must handle a 4-GHz input signal. The task of designing a circuit to digitally amplify a 4-GHz signal would be monumental to say the least. So, for the foreseeable future at least, digital circuits will not replace analog circuits entirely.

While we train ourselves to become digital experts, we must also train ourselves to become analog experts. If I were to ask, I'd bet most of you could not describe the circumstances that would require a ground plane on a PC board. Nor would you be able to tell me how large a heat sink is required for a specific transistor output stage. So, while we're having fun and reaping all the benefits we can from digital circuits, let's not forget analog circuits.





ART KLEIMAN
MANAGING EDITOR

An Extraordinary Offer to introduce you to the benefits of Membership in

ELECTRONICS BOOK CLUB

invites you to take
this 1,442-page
Computer Library
for only

\$ **1.99**

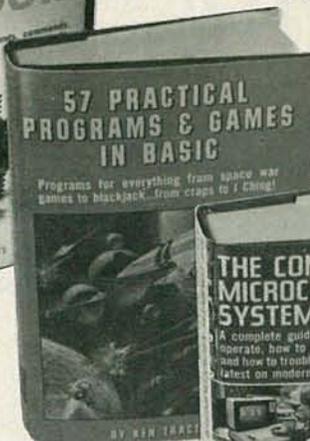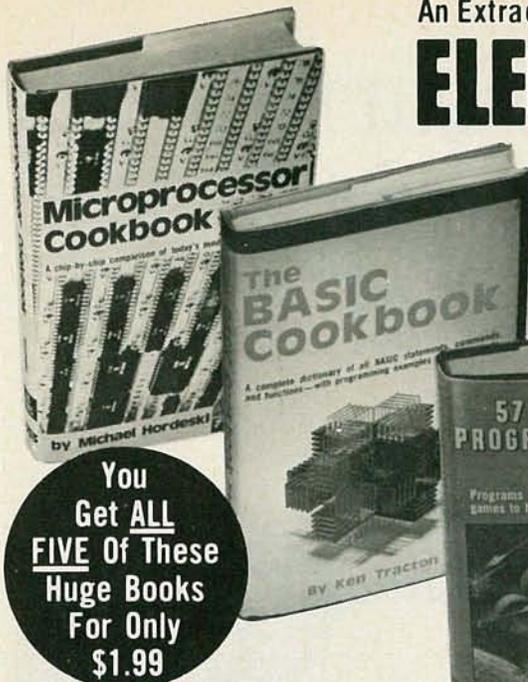

You
Get **ALL**
FIVE Of These
Huge Books
For Only
\$1.99

Microprocessor Cookbook

A chip-by-chip comparison of the most popular modern microprocessors—including programming, architecture, addressing, instruction sets, and applications! You get complete data on what makes up the structure of a microprocessor chip and a microcomputer, how to give instructions, the overall organization of a computer system, and more. Then you get a chip-by-chip profile of modern microprocessors—with thorough discussions of applications, architecture, functions, etc. Included are the Intel 8080, Motorola 6800, Fairchild's F8 family, Zilog Z80, TI's TMS 9900, National Semi SC/MP, Intel's 8021, and many more. 266 pps., 124 illus. List \$9.95

The BASIC Cookbook

A complete dictionary of all BASIC statements, commands, and functions—with programming examples and flowcharts. Thoroughly defines the BASIC vocabulary in alphabetical order, illustrates the definitions with sample programs, and further clarifies the programs with matching flowcharts... plus explaining BASIC system commands. You'll learn how to professionally manipulate and use each BASIC term in a workable program. Also defines programming terms that apply to APL, ALGOL, COBOL, FORTRAN, RPG, PL1, etc. 140 pps., 49 illus. List \$7.95

57 Practical Programs & Games in BASIC

57 of the hardest working, most enjoyable BASIC programs you've ever seen... everything from space war games to blackjack, from craps to I Ching, from arithmetic progression to statistical permutations to one-arm bandits! It's an easy-to-use manual that gives you 57 different simplified BASIC programs... all ready to run! You can program your minibrain for all kinds of fun and games, or for solving many different types of problems. 210 pps., 64 illus. List \$10.95

Complete Microcomputer Systems Hdbk.

A complete guide to microcomputers—how they operate, how to use them, how to program them, and how to troubleshoot, test, and repair them... plus the very latest on modern applications like magnetic bubble memories, computers in networks, computer decision making, simulation and forecasting, teaching machines to learn, robot control, speech synthesizers, digital music, mobile computers, etc. There's extensive coverage of computer problems and how to diagnose and repair them, plus lots of hard debugging data. You'll learn how to find and fix all types of mechanical and electronic troubles—plus how to use test signals and closed loop signals, how to replace chips, how to align disc drives, etc. 322 pps., 147 illus. List \$15.95

The Giant Handbook of Computer Projects

This MAMMOTH 504-page step-by-step guide to building modern computers and accessories—CPUs, memories, I/O hardware, etc.—is a HUGE collection of ready-to-use construction info. It's a builder's dream, with projects, complete schematics, parts lists, and step-by-step construction instructions that let you build your own systems. Also contains a thorough discussion of microprocessors, with comparisons of several units, including the Kim-1, the Z-80, and the 8080, etc... plus data on memory boards, RAM checkout, PROM programmers, memory chips, inexpensive input/output devices, paper tape systems, interfacing with clock chips, and more. 504 pps., 217 illus. List \$15.95

Let us send you this 5-volume, 1,442 page Computer Library as part of an unusual offer of a Trial Membership in Electronics Book Club.

Here are quality hardbound volumes, each especially designed to help you increase your know-how, earning power, and enjoyment of electronics and computers. Whatever your interest in electronics/computers, you'll find Electronics Book Club offers practical, quality books that you can put to immediate use and benefit.

This extraordinary offer is intended to prove to you, through your own experience, that these very real advantages can be yours... that it is possible to keep up with the literature published in your areas of interest, and to save substantially while so doing. As part of your Trial Membership, you need purchase as few as four books during

the coming 12 months. You would probably buy at least this many anyway, without the substantial savings offered through Club Membership.

To start your Membership on these attractive terms, simply fill out and mail the coupon today. You will receive the 5-volume Computer Library for 10-day inspection. YOU NEED SEND NO MONEY. If you're not delighted, return the books within 10 days and your Trial Membership will be cancelled without cost or obligation.

ELECTRONICS BOOK CLUB, Blue Ridge Summit, Pa. 17214

Facts About Club Membership

- The 5 introductory books carry a publisher's retail price of \$60.75. They are yours for only \$1.99 for all 5 (plus postage/handling) with your Trial Membership.
- You will receive the Club News, describing the current Selection, Alternates, and other books, every 4 weeks (13x a year).
- If you want the Selection, do nothing; it will be sent to you automatically. If you do not wish to receive the Selection, or if you want to order one of the many Alternates offered, you simply give instructions on the reply form (and in the envelope) provided, and return it to us by the date specified. This date allows you at least 10 days in which to return the form. If, because of late mail delivery, you do not have 10 days to make a decision and so receive an unwanted Selection, you may return it at Club expense.
- To complete your Trial Membership, you need buy only four additional monthly Selections or Alternates during the next 12 months. You may cancel your Membership any time after you purchase these four books.
- All books—including the Introductory Offer—are fully returnable after 10 days if you're not completely satisfied.
- All books are offered at low Member prices plus a small postage and handling charge.
- **Continuing Bonus:** If you continue after this Trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates plus payment of the nominal sum of \$1.99 will entitle you to a valuable Book Dividend of your choice which you may choose from a list provided Members.

ELECTRONICS BOOK CLUB

Blue Ridge Summit, Pa. 17214

Please open my Trial Membership in ELECTRONICS BOOK CLUB and send my 5-volume Computer Library, invoicing me for only \$1.99 plus shipping. If not delighted, I may return the books within 10 days and owe nothing, and have my Trial Membership cancelled. I agree to purchase at least four additional books during the next 12 months after which I may cancel my membership at any time.

Name _____ Phone _____

Address _____

City _____

State _____ Zip _____

(Valid for new Members only. Foreign and Canada add 15%.) RE-280

CIRCLE 46 ON FREE INFORMATION CARD

“If you’re going to learn electronics, you might as well learn it right!”



“Don’t settle for less. Especially when it comes to career training...because everything else in your life may depend on it. That’s why you ought to pick CIE!”

You've probably seen advertisements from other electronics schools. Maybe you think they're all the same. They're not!

CIE is the largest independent home study school in the world that specializes exclusively in electronics.

Meet the Electronics Specialists.

When you pick an electronics school, you're getting ready to invest some time and money. And your whole future depends on the education you get in return.

That's why it makes so much sense to go with number one... with the specialists... with CIE!

There's no such thing as bargain education.

If you talked with some of our graduates, chances are you'd find a lot of them shopped around for their training. Not for the lowest priced but for the best. They pretty much knew what was available when they picked CIE as number one.

We don't promise you the moon. We do promise you a proven way to build valuable career skills. The CIE faculty and staff are dedicated to that. When you graduate, your diploma shows employers you know what you're about. Today, it's pretty hard to put a price on that.

Because we're specialists, we have to stay ahead.

At CIE, we've got a position of leadership to maintain. Here are some of the ways we hang onto it...

Our step-by-step learning includes "hands-on" training.

At CIE, we believe theory is important. And our famous Auto-Programmed® Lessons teach you the principles in logical steps.

But professionals need more than theory. That's why some of our courses train you to use tools of the trade like a 5 MHz triggered-sweep, solid-state oscilloscope you build yourself—and use to practice troubleshooting. Or a beauty of a 19-inch diagonal Zenith solid-state color TV you use to perform actual service operations.

Our specialists offer you personal attention.

Sometimes, you may even have a question about a specific lesson. Fine. Write it down and mail it in. Our experts will answer you promptly in writing. You may even get the specialized knowledge of all the CIE specialists. And the answer you get becomes a part of your permanent reference file. You may find this even better than having a classroom teacher.

Pick the pace that's right for you.

CIE understands people need to learn at their own pace. There's no pressure to keep up... no slow learners hold you back. If you're a beginner, you start with the basics. If you already know some electronics, you move ahead to your own level.

Enjoy the promptness of CIE's "same day" grading cycle.

When we receive your lesson before noon Monday through Saturday, we grade it and mail it back—the same day. You find out quickly how well you're doing!

CIE can prepare you for your FCC License.

For some electronics jobs, you must have your FCC License. For others, employers often consider it a mark in your favor. Either way, it's government-certified proof of your specific knowledge and skills!

More than half of CIE's courses prepare you to pass the government-administered exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

For professionals only.

CIE training is not for the hobbyist. It's for people who are willing to roll up their sleeves and go to work... to build a career. The work can be hard, sure. But the benefits are worth it.

Send for more details and a FREE school catalog.

Mail the card today. If it's gone, cut out and mail the coupon. You'll get a FREE school catalog plus complete information on independent home study. For your convenience, we'll try to have a CIE representative contact you to answer any questions you may have.

Mail the card or the coupon or write CIE (mentioning name and date of this magazine) at: 1776 East 17th Street, Cleveland, Ohio 44114.



Patterns shown on TV and oscilloscope screens are simulated.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council

YES... I want the best of everything! Send me my FREE CIE school catalog—including details about troubleshooting courses—plus my FREE package of home study information. RE-81

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G. I. Bill information: Veteran Active Duty

MAIL TODAY!

letters

THE EQ-2

We have recently redesigned our graphic equalizer kit mechanically. (That is the one I wrote about in the May 1978 issue.) The new design is wider and lower, and, I think, more attractive. It uses solid walnut end-panels, rather than the previous three-sided cover. As the walnut is now an integral part of the structure, the unit is no longer available without it. By simplifying the unit, we are able still to sell it for \$100 postpaid, despite the inflation of all the parts costs. Your readers may be interested to know that we sell the assembly manual for \$2.50, refundable with purchase of the unit. The circuit and its excellent performance are unchanged.

JOE GORIN

*Symmetric Sound Systems,
1608 South Douglas Avenue,
Loveland, CO 80537*

OOOOOPS!

Regarding "Fifty Years of Electronics:" On the bottom right of page 65 of your October 1979 issue, the CBS tube plants

mentioned were at Danvers and Newburyport, Massachusetts—not Connecticut, as stated there.

Just the same, this is certainly an issue of *Radio Electronics* to keep!

NEIL F. DUNN

Danvers, MA

Right!—Editor

Many oldtimers (and some youngtimers as well) celebrated with Dr. K. Vladimir K. Zworykin his 90th birthday last July, at his Princeton home. He is healthy, alert, and active; so it comes as a surprise that, on page 45 of the 50th anniversary issue of *Radio-Electronics*, Baron Manfred von Ardenne implies that Dr. Zworykin's death had occurred in 1977. We are happy to say that the report is incorrect, and your readers may also be pleased so to learn.

EDWARD W. HEROLD

Princeton, New Jersey

We regret that, in the process, a phrase of Baron von Ardenne's manuscript was misunderstood, resulting in the erroneous report that Dr. Zworykin had died in 1977. We did receive a correction of that error;

unfortunately, we didn't get it in time for us to make any changes in our October issue. We join you in your pleasure at knowing that Dr. Zworykin is alive and well.—Editor.

Your article on logic circuits in the 50th Anniversary issue is very interesting, but the truth table in Fig. 2 for the "simple AND gate" on page 111 may contain an error in its first line. The output symbol given for that line is a binary one when, if my interpretation of the second paragraph under the "AND gate" heading is correct, it should be zero.

From other sources, I understand that the output symbol of an AND gate is obtained by a multiplication of the inputs. Since $0 \times 0 = 0$ in binary multiplication, that also seems to indicate the use of zero for the output in that first line of the table.

Thank you for a fine Anniversary issue.

REGINALD TODD


Kansas City, MO.

The first line of the truth table in chart 2 is incorrect. The output should be a zero instead of a one. Also, the logic symbol is incorrect as it shows a NAND gate. Remove

INTRODUCING... THE

ROAD RUNNER ADMM™

FROM WESTON

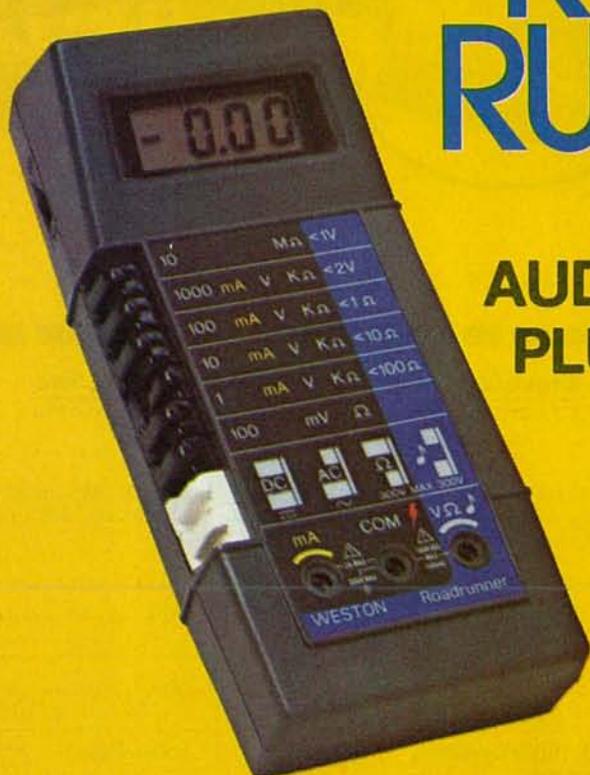

AUDIO RESPONSE™ PLUS DIGITAL DISPLAY

- 5 RANGE AUDIBLE SIGNALING FUNCTION
- RUGGED FIELD SERVICE DESIGN
- 0.5" LCD DISPLAY
- 6 FUNCTIONS
- 29 RANGES

WESTON INSTRUMENTS
THE MEASUREMENT PEOPLE®
614 Frelinghuysen Ave.,
Newark, NJ 07114

SANGAMO WESTON

Schlumberger

the small circle at the output to obtain the correct AND gate symbol.—Editor

HEART MONITOR

In my opinion, a technical magazine (which I consider *Radio-Electronics* to be) should be technically correct. The article on the heart rate monitor is interesting from the electronic point of view but has a technical error. Figure 1 depicts a tracing of an electrocardiogram. The instrument described does not use the electrocardiogram but rather the pulse pressure wave in the finger as a trigger source. The waveform of the pulse pressure wave is more like that shown in the diagram, depending on where it is recorded.



I have used either the electrocardiogram or the pulse pressure wave to trigger a cardiometer. Both work, sometimes one better than the other.

LESLIE P. McCARTY, PH.D.
Research Specialist, Bio-Medical Research
Dow Chemical
Midland, MI

RADAR DETECTORS VS. THE LAW

The legal, moral and constitutional issues are with us again as the rights of citizens to own radar detectors or receiving devices capable of monitoring frequencies assigned to police.

First, by order of the FCC, the radar band is not specifically assigned to police. The Commission has ordered this band to be shared by radio listeners, astronomers, public service agencies, hams and other private and government microwave users. A state agency has no such authority. The twisted misinterpretation of Penal Code MCLA 750.508 cannot and should not be used against a citizen. Police radios are on a different frequency than police radar. The FCC says citizens also have the right to use the radar frequency.

Regardless what the legislators vote on, states don't have the right to regulate federal FCC-controlled monitoring. If anything, the legislature should abolish or rewrite MCLA 750.508. In my opinion, MCLA 750-508 is unconstitutional and discriminatory because it overrides federal law giving the FCC exclusive authority over who uses what frequency, and because it allows one class of individuals to legally receive radar or police signals while all others are excluded. The ACLU (American Civil Liberties Union), the ARRL (American Radio Relay League), the FCC and the citizens of the state of Michigan should make sure the law is changed and the U.S. Constitution followed.

Radar detection has been used and is being used by people of all classes and ages. An Ohio mayor claims that such devices make a driver aware of his speed and slows him down to the legal limit, and says slower speeds lessen accident rates.

Restraints on enforcement (of the Michigan law) could avoid the trouble that happened to a physician who was awakened in

the middle of the night and arrested for having a detector in his car when an officer on patrol spotted it in his driveway!

Some judges and police are divided over this present band as it stands, and a speedy reversal should be enacted. As a tourist from out of state, how would you feel if you were not aware of this "so-called law" banning detectors, there was no posting for same and you were arrested for possession of a detector? This alone is in violation of due process (no signs posted) and federal preemption of the airways.

Radar operates on the Doppler principle, and has come under severe attack recently—especially moving radar. It's a fact that a CB set can trigger a false reading with a whistling tone with readings to 90 mph; reflections from vehicles traveling at slightly different speeds can cause higher readings—this is called "batching." A fast-moving truck behind a slower moving car will register a stronger signal than will the car—and the innocent car will be cited. And how does an officer distinguish a speeder from a nonspeeder in a group?

Drone radar (jamming devices to trigger detectors) that police in some states were using for the past couple of years has been put down by the FCC as being illegal. The misuse of radar and radar laws should be challenged by anyone, and the ACLU should look into all laws past and present. The abuse is placing undue burdens on courts, police and citizens in terms of cost, time, and embarrassment.

While I believe that criminals should be charged and prosecuted, I don't believe

continued on page 25



Unique, New SONIC SENTRY from Delta Blows the Horn on Vehicle Burglary and Intrusion...

...and robs would-be thieves of their most important conspirators... Opportunity, Anonymity, and Concealment. A silent vigilant sentinel, the Sonic Sentry literally blows the horn on any intrusion into the field of harmless, invisible ultrasonic protection that is cast throughout the interior of the vehicle.

Anyone who has a 12-volt vehicle with a horn or other noisemaker, and a hard exterior surface can enjoy Sonic Sentry security. And because it's manufactured by Delta Products, you know it's backed by an established firm with an industry-wide reputation for product integrity and superior service.

Sonic Sentry is meticulously engineered to incorporate the best in ultrasonics with built-in safeguards against false alarm. In addition:

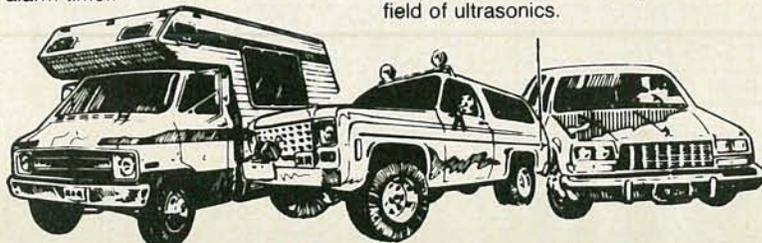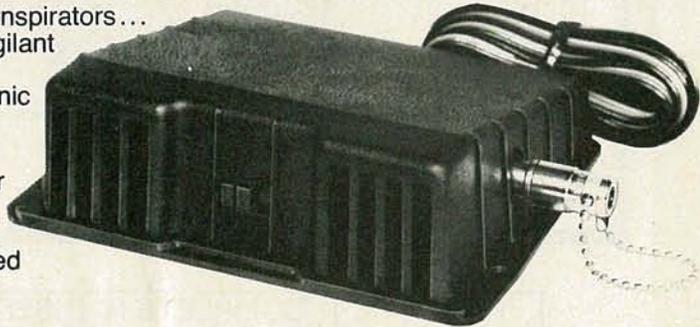1. Installation is easy, involving only three simple wire connections.
2. There are no holes to drill for installation.
3. Sonic Sentry is keyless and includes entry/exit delay, and automatic one minute alarm timer.
4. It protects the interior of any van, camper, mobile home or trailer, as well as automobiles, trucks, etc.
5. Sonic Sentry is the only vehicle ultrasonic designed by a professional electronics company with extensive experience in the field of ultrasonics.



CIRCLE 30 ON FREE INFORMATION CARD

DELTA PRODUCTS, INC.

P.O. Box 1147 630 So. 7th Street,
Grand Junction, Colorado 81501
(303) 242-9000 Dept. RE

Please send complete information about the Sonic Sentry, together with facts on Delta's line of dynamite automotive, motorcycle and security products to:

Please send _____ Sonic Sentry(ies)
\$59.95 plus \$1.00 postage

Check enclosed.

Charge my: Master Charge VISA

Credit Card #	Interbank No.	Exp. Date
	(Master Charge only)	Mo. Year

Name _____
Address _____
City _____ State _____ Zip _____

ITEM NO.
WK-7

CMOS SAFE

IC INSERTION/EXTRACTION KIT

KIT INCLUDES

- MOS-1416 14-16 CMOS SAFE INSERTER
- MOS-2428 24-28 CMOS SAFE INSERTER
- MOS-40 36-40 CMOS SAFE INSERTER
- EX-1 14-16 EXTRACTOR
- EX-2 24-40 CMOS SAFE EXTRACTOR




OK MACHINE & TOOL CORPORATION
3455 CONNER ST., BRONX, N.Y. 10475 U.S.A.
PHONE (212) 994-6600 TELEX NO. 125091



PRINTED IN U.S.A.

PATENT PENDING

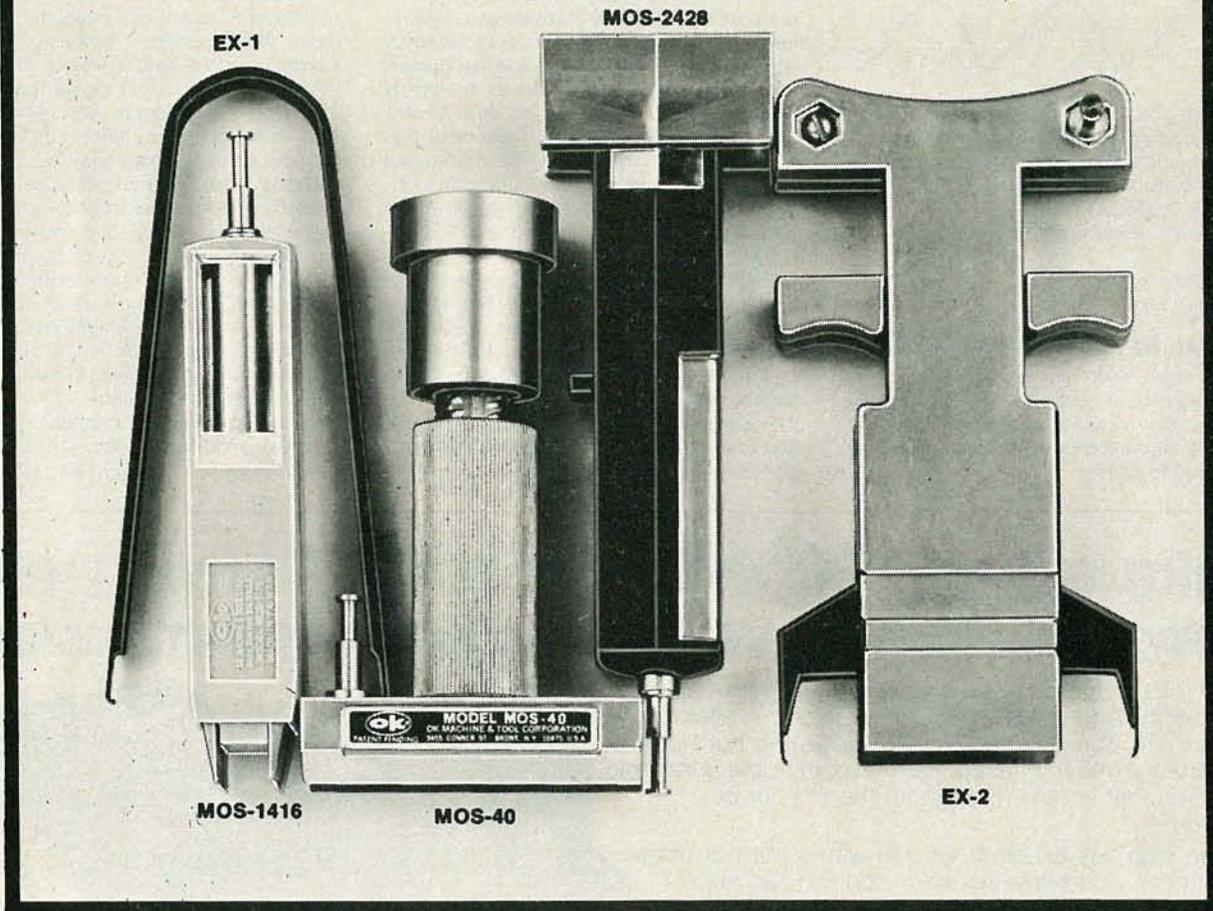

WK-7	COMPLETE IC INSERTER/EXTRACTOR KIT	\$29.95
------	------------------------------------	---------

INDIVIDUAL COMPONENTS

MOS-1416	14-16 PIN MOS CMOS SAFE INSERTER	\$ 7.95
MOS-2428	24-28 PIN MOS CMOS SAFE INSERTER	\$ 7.95
MOS-40	36-40 PIN MOS CMOS SAFE INSERTER	\$ 7.95
EX-1	14-16 PIN EXTRACTOR TOOL	\$ 1.49
EX-2	24-40 PIN CMOS SAFE EXTRACTOR TOOL	\$ 7.95

MINIMUM BILLING \$25.00. ADD SHIPPING CHARGE \$2.00. NEW YORK RESIDENTS ADD APPLICABLE TAX.

OK MACHINE & TOOL CORPORATION 3455 CONNER ST., BRONX, N.Y. 10475 (212) 994-6600/TELEX 125091

LETTERS

continued from page 23

vesting total power in law enforcement at the expense of the ordinary citizen was a principle this country was founded on. The laws are there to be applied equally.

A legal defense fund is being established for test cases and class action suits as needed. Anyone interested can contact the writer of this letter for details.

L. C. MAYNARD

Maycom Communication Products, Inc.

1134 W. John Beers Rd.

Stevensville, MI 49127

ELECTRONIC SYNTHESIZER

I read Mr. A. P. Campione's letter on the electronic synthesizer in your July issue, and was interested in his suggestion about using a tuning fork and a pickup coil for the purpose of generating a C-Major scale.

I suggest that he could get far more accurate results—generating, by the way, complete musical scales (12 notes per octave) for as many octaves as he wishes—by using a Top Octave generator. That is made in integrated circuit form by many companies, such as National Semiconductor and General Instruments. Using that device and driving it with the proper frequency crystal oscillator, one may obtain far more accurate musical frequencies than by using a tuning-fork oscillator. Such a crystal-controlled system is also much lighter and cheaper.

HAROLD ZIBKOFF

Brooklyn, NY

X-BAND MISINFORMATION

Boy, oh boy! Where did Robert E. Williams (Letters, September 1979 *Radio Electronics*, page 24) get his store of misinformation?

I cannot quibble with the first three paragraphs, but the fourth paragraph is full of inaccuracies.

First of all, it is common knowledge (maybe not?) that X-band police radar is on 10.525 GHz \pm 25 MHz and the K band is up around 24 GHz somewhere, not the 9.32-9.5 and 10.5-10.7 GHz ranges as he suggests. (Actually, the only band lower than X is the old S band, which is not used much any more.)

Secondly, if there is an amateur transceiver available for the X band, please let me know where I can find it; I could really use a 10-watt X-band transceiver. I think, just maybe, that he is confused by the common two-meter radios that have a 1 and 10-watt position. Besides, can you really picture a 10-watt X-band signal source? Only TWT's or KPA's can kick out that much punch.

Thirdly, at my last checking with the FCC, pulse is not permitted on the X band, and never has been.

Fourth and last (and what a way to go): Really, when was the last time you measured the same thing coming back as was sent out? Especially at 10 GHz where propagation effects take a bad toll. Are we really supposed to believe that 100 mw comes back after going down the highway several hundred feet, bouncing off a very "scattering" reflector, and coming back another two hundred feet?

ROBERT T. SESTRO

Hunt Valley, MD

Start Computing For Just \$129.95 With An 8085-Based Professional Computer Kit—

Explorer/85

100% compatible with all 8080A and 8085 software & development tools!

No matter what your future computing plans may be, Level "A"—at \$129.95—is your starting point.

Starting at just \$129.95 for a Level "A" operating system, you can now build the exact computer you want. Explorer/85 can be your beginner's system, OEM controller, or IBM-formatted 8" disk small business system... yet you're never forced to spend a penny for a component or feature you don't want and you can expand in small, affordable steps!

Now, for just \$129.95, you can own the first level of a fully expandable computer with professional capabilities—a computer which features the advanced Intel 8085 cpu, thereby giving you immediate access to all software and development tools that exist for both the 8085 and its 8080A predecessor (they are 100% software compatible)—a computer which features onboard S-100 bus expansion—plus instant conversion to mass storage disk memory with either 5-1/4" diskettes or standard IBM-formatted 8" disks.

For just \$129.95 (plus the cost of a power supply, keyboard/terminal and RF modulator, if you don't have them already), Explorer/85 lets you begin computing on a significant level... applying the principles discussed in leading computer magazines... developing "state of the art" computer solutions for both the industrial and leisure environment.

Level "A" Specifications

Explorer/85's Level "A" system features the advanced Intel 8085 cpu, an 8355 ROM with 2k deluxe monitor/operating system, and an 8155 ROM-I/O—all on a single motherboard with room for RAM-ROM/PROM/EPROM and S-100 expansion, plus generous prototyping space.

(Level "A" makes a perfect OEM controller for industrial applications and is available in a special Hex Version which can be programmed using the Netronics Hex Keypad/Display.)

PC Board: glass epoxy, plated through holes with solder mask

- I/O: provisions for 25-pin (DB25) connector for terminal serial I/O, which can also support a paper tape reader... provision for 24-pin DIP socket for hex keyboard/display... cassette tape recorder input... cassette tape recorder output... speaker output... LED output indicator on SOD (serial output) line... printer interface (less drivers)...

- total of four 8-bit plus one 6-bit I/O ports
- Crystal Frequency: 6.144 MHz
- Control Switches: reset and user (RST 7.5) interrupt... additional provisions for RST 5.5, 6.5 and TRAP interrupts onboard
- Counter/Timer: programmable, 14-bit binary
- System RAM: 256 bytes located at F800, ideal for smaller systems and for use as an isolated stack area in expanded systems... RAM expandable to 64k via S-100 bus or 4K on motherboard.

System Monitor (Terminal Version): 2k bytes of deluxe system monitor ROM located at F000 leaving 0000 free for user RAM-ROM. Features include: tape load with labeling... tape dump with labeling... examine/change contents of memory... insert data... warm start... examine and change all registers... single step with register display at each break point, a debugging/training feature... go to execution address... move blocks of memory from one location to another... fill blocks of memory with a constant... display blocks of memory... automatic baud rate selection... variable display line length control (1-255 characters/line)... channelized I/O monitor routine with 8-bit parallel output for high speed printer... serial console in and console out channel so that monitor can communicate with I/O ports.

System Monitor (Hex Version): Tape load with labeling... tape dump with labeling... examine/change contents of memory... insert data... warm start... examine and change all

Netronics R&D Ltd., Dept. RE-2

333 Litchfield Road, New Milford, CT 06776

Please send the items checked below—

- Explorer/85 Level "A" Kit (ASCII Version), \$129.95 plus \$3 p&h.
- Explorer/85 Level "A" Kit (Hex Version), \$129.95 plus \$3 p&h.
- 8k Microsoft BASIC on cassette tape, \$64.95 postpaid.
- 8k Microsoft BASIC in ROM Kit (requires Levels "B," "D," and "E"), \$99.95 plus \$2 p&h.
- Level "B" (S-100) Kit, \$49.95 plus \$2 p&h.
- Level "C" (S-100 6-card expander) Kit, \$39.95 plus \$2 p&h.
- Level "D" (4k RAM) Kit, \$69.95 plus \$2 p&h.
- Level "E" (EPROM/ROM) Kit, \$5.95 plus \$0.4 p&h.
- Deluxe Steel Cabinet for Explorer/85, \$49.95 plus \$3 p&h.
- ASCII Keyboard/Computer Terminal Kit (features a full 128 character set, upper & lower case, full cursor control, 75 ohm video output convertible to baudot output, selectable baud rate, RS232-C or 20 ma. I/O, 32 or 64 character by 16 line formats, and can be used with either a CRT monitor or a TV set (if you have an RF modulator), \$149.95 plus \$2.50 p&h.
- Hex Keypad/Display Kit, \$69.95 plus \$2 p&h.
- Deluxe Steel Cabinet for ASCII Keyboard/Terminal, \$19.95 plus \$2.50 p&h.
- Power Supply Kit ($\pm 8V @ 5$ amps) in deluxe steel cabinet, \$39.95 plus \$2 p&h.
- Gold Plated S-100 Bus Connectors, \$4.85 each, postpaid.
- RF Modulator Kit (allows you to use your TV set as a monitor), \$8.95 postpaid.
- 16k RAM Kit (S-100 Board expands to 64k), \$199.95 plus \$2 p&h.
- 32k RAM Kit, \$329.95 plus \$2 p&h.
- 48k RAM Kit, \$459.95 plus \$2 p&h.
- 64k RAM Kit, \$589.95 plus \$2 p&h.
- 16k RAM Expansion Kit (to expand any of the above up to 64k), \$139.95 plus \$2 p&h each.
- Intel 8085 cpu User's Manual, \$7.50 postpaid.
- Special Computer Grade Cassette Tapes, \$1.90 each or 3 for \$5, postpaid.
- 12" Video Monitor (10 MHz bandwidth), \$139.95 plus \$5 p&h.
- North Star Double Density Floppy Disk Kit (One Drive) for Explorer/85 (includes 3 drive S-100 controller, DOS, and extended BASIC with per-



registers... single step with register display at each break point... go to execution address. Level "A" in the Hex Version makes a perfect controller for industrial applications and can be programmed using the Netronics Hex Keypad/Display.



Hex Keypad/Display.

Hex Keypad/Display Specifications

Calculator type keypad with 24 system defined and 16 user defined keys. 6 digit calculator type display which displays full address plus data as well as register and status information.

Level "B" Specifications

Level "B" provides the S-100 signals plus buffers/drivers to support up to six S-100 bus boards and includes; address decoding for onboard 4k RAM expansion select-able in 4k blocks... address decoding for onboard 8k EPROM expansion select-able in 8k blocks... address and data bus drivers for onboard expansion... wait state generator (jumper selectable), to allow the use of slower memories... two separate 5 volt regulators.



Explorer/85 with Level "C" card cage.

Level "C" Specifications

Level "C" expands Explorer's motherboard with a card cage, allowing you to plug up to six S-100 cards directly into the motherboard. Both cage and cards are neatly contained inside Explorer's deluxe steel cabinet.

Level "C" includes a sheet metal superstructure, a 5-card gold plated S-100 extension PC board which plugs into the motherboard. Just add required number of S-100 connectors

Level "D" Specifications

Level "D" provides 4k or RAM, power supply regulation, filtering decoupling components and sockets to expand your Explorer/85 memory to 4k (plus the original 256 bytes located in the 8155A). The static RAM can be located anywhere from 0000 to EFFF in 4k blocks.

Level "E" Specifications

Level "E" adds sockets for 8k of EPROM to use the popular Intel 2716 or the TI 2516. It includes all sockets, power supply regulator, heat sink, filtering and decoupling components. Sockets may also be used for soon to be available RAM IC's (allowing for up to 12k of onboard RAM).

Order A Coordinated Explorer/85 Applications Pak!

Experimenter's Pak (SAVE \$12.50)—Buy Level "A" and Hex Keypad/Display for \$199.90 and get FREE Intel 8085 user's manual plus FREE postage & handling!

Student Pak (SAVE \$24.45)—Buy Level "A," ASCII Keyboard/Computer Terminal, and Power Supply for \$319.85 and get FREE RF Modulator plus FREE Intel 8085 user's manual plus FREE postage & handling!

Engineering Pak (SAVE \$41.00)—Buy Levels "A," "B," "C," "D," and "E" with Power Supply, ASCII Keyboard/Computer Terminal, and six S-100 Bus Connectors for \$514.75 and get 10 FREE computer grade cassette tapes plus FREE 8085 user's manual plus FREE postage & handling!

Business Pak (SAVE \$89.95)—Buy Explorer/85 Levels "A," "B," and "C" (with cabinet), Power Supply, ASCII Keyboard/Computer Terminal (with cabinet), 16k RAM, 12" Video Monitor, North Star 5-1/4" Disk Drive (includes North Star BASIC) with power supply and cabinet, all for just \$1599.40 and get 10 FREE 5-1/4" minidisquettes (\$49.95 value) plus FREE 8085 user's manual plus FREE postage & handling!

Continental U.S.A. Credit Card Buyers Outside Connecticut

CALL TOLL FREE 800-243-7428

To Order From Connecticut Or For Technical Assistance, Etc. Call (203) 354-9375

sonalized disk operating system—just plug it in and you're up and running!)

\$699.95 plus \$5 p&h.

Power Supply Kit for North Star Disk Drive, \$39.95 plus \$2 p&h.

Deluxe Case for North Star Disk Drive, \$39.95 plus \$2 p&h.

Experimenter's Pak (see above), \$199.90 postpaid.

Student Pak (see above), \$319.85 postpaid.

Engineering Pak (see above), \$514.75 postpaid.

Business Pak (see above), \$1599.40 postpaid.

Total Enclosed \$ _____

(Conn. res. add sales tax) By—

Personal Check M.O./Cashier's

Check Visa MasterCard

Check _____ (Bank # _____)

Acct. # _____

Signature _____ Exp. Date _____

Print Name _____

Address _____

City _____

State _____ Zip _____

Send Me Information

equipment reports

Speakerlab Model 2.5 Speaker System



CIRCLE 101 ON FREE INFORMATION CARD

NOT MANY HI-FI MANUFACTURERS OFFER speaker systems in kit form. One of the manufacturers that does, Speakerlab Inc. (Dept. R-E, 735 N. Northlake Way, Seattle, WA 98103), offers several different models ranging from a miniature bookshelf speaker to large floorstanding systems. So, we decided to assemble their middle-of-the-line "best selling"

system to find out just how difficult it is to put together and how it sounds.

The Speakerlab 2.5 is a three-way acoustic suspension system that measures $26\frac{1}{4} \times 15\frac{1}{4} \times 10\frac{3}{4}$ inches and weighs 56 pounds. The manufacturer's specifications list the impedance at 8 ohms, sensitivity at 91 dB at 1 meter with a 1 watt input, a minimum recommended power amplifier rating of 15 watts-per-channel RMS and a maximum power handling capability of 150 watts-per-channel RMS.

The three drivers include a 10-inch woofer, a 6-inch midrange and a 1-inch dome tweeter. The woofer uses a high-density foam roll suspension, a $1\frac{1}{2}$ -inch diameter voice coil and a 26 ounce magnet. The 6-inch midrange has a butyl rubber surround and the entire driver is housed in a separate sub-enclosure within the speaker system. Crossover frequencies occur at 600Hz and 4 kHz. The L-C crossover network uses switches rather than controls to adjust the level of the tweeter and midrange drivers.

Two enclosures are available for the model 2.5. We received the "utility" enclosure that consists of a 6-mil thick polymer bonded to a $\frac{3}{4}$ -inch thick particle board. The polymer is embossed and printed in an attractive simu-

lated walnut pattern. Also available is an oiled walnut veneer enclosure. The grille cloth extends to the edges on both enclosures and is mounted on a removable frame for easy access to the drivers.

Assembly

Surprisingly few individual pieces make up the Speakerlab 2.5 kit. In fact, a better term would be "partial kit" since so many of the individual pieces come pre-assembled. For example; the top, bottom, both sides and rear panels of the enclosure come pre-assembled. The rear panel also contains the necessary cutout for the crossover network. The front panel contains the required cutouts for the drivers, and the frame that holds the grille cloth is pre-assembled. The crossover network is also pre-assembled and even has push-on connectors on the ends of the wires that connect to the drivers. The only tools that are necessary for assembly are a caulking gun, a pair of scissors and a staple gun.

The assembly manual is well written and clearly illustrated. The first step in assembly is to paint the unfinished wood surfaces black.

continued on page 32

Now, an automotive computer plus cruise control at your fingertips!

This is CompuCruise! The first true computer for your car, truck or RV. It's the most effective and functional cruise control ever designed, PLUS complete trip computing, an efficient fuel management system, and a split-second-accuracy quartz time system.

CompuCruise is a cruise control with a memory. A unique seek-and-hold capability makes highway driving easier and more enjoyable. Fully electronic, making it more accurate and reliable.

CompuCruise is a true computer, constantly reacting via automatic sensors to changing conditions, updating vital data for you every second. Just look at what CompuCruise gives you:

- Time, E.T. Lap timing, Alarm
- Time, Distance, Fuel to arrival
- Time, Distance, Fuel to empty
- Time, Distance fuel on trip
- Current or average MPH, MPG, GPH
- Fuel used, Distance since fillup
- Inside, outside or coolant temp.
- Battery voltage
- English or Metric display

CompuCruise works on foreign or American cars (except Diesel and fuel-injected vehicles). It's priced for the budget-minded, and easily installable by you or your automotive outlet.

Only \$199.95 with Cruise Control, \$159.50 without. Fully warranted for 90 days from date of purchase. Delivered

complete with easy-to-follow installation guide. And backed by a 100% satisfaction guarantee. If not fully satisfied when you receive your unit, return it before installation and your money will be fully refunded without question.

For the name of your nearest dealer, call or write us right now: ZEMCO, 12907 Alcosta Blvd., San Ramon, CA 94583. Phone (415) 838-8060.

Do it today—for a better cruise control and more automotive information than you've ever had before.

 **COMPUCRUISE**



CIRCLE 50 ON FREE INFORMATION CARD

Six professional scopes offer build-it-yourself savings

Save up to 46% when you build it yourself.

Only in the Heathkit Catalog will you find this selection of six professional oscilloscopes, each with its own special features and low price. Compare Heathkit prices with similar assembled scopes and see how much you can save when you build it yourself.

Heathkit Model	Trace	Bandwidth MHz	Vertical Sensitivity*	Delay Lines	Regulated high voltage	Mu-metal shielding	Low kit price
10-4235	dual	DC-35	2mV/cm to 10V/cm	yes	yes	full	\$869.95
10-4510	dual	DC-15	1mV/cm to 5V/cm	yes	yes	full	\$649.95
10-4550	dual	DC-10	10mV/cm to 20V/cm	no	yes	full	\$399.95
10-4555	single	DC-10	10mV/cm to 20V/cm	no	yes	full	\$349.95
10-4205	dual	DC-5	10mV/cm	no	no	partial	\$279.95
10-4105	single	DC-5	10mV/cm	no	no	partial	\$199.95


*Under full bandwidth

Heathkit manuals make kitbuilding easy



Easy-to-follow Heathkit assembly manuals take you step by step from unpacking to final plug-in. Anyone can do it. And when you build it yourself, you can service it yourself.

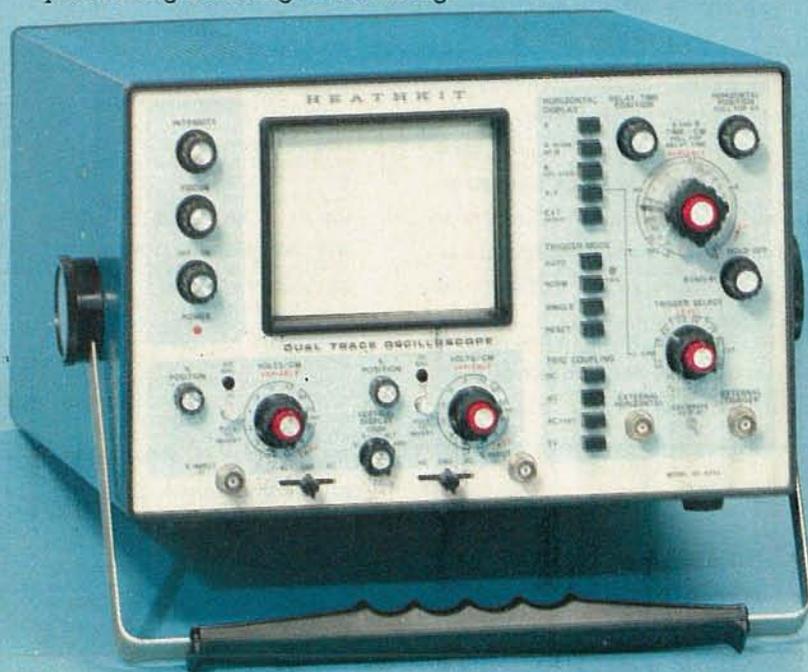Your manual becomes a handy service guide. Replacement parts are readily available from the Heath factory or from Heathkit Electronic Centers. And experienced service techs are just a phone call away to help you during building or servicing.



FREE Catalog



Complete details on Heathkit Oscilloscopes and nearly 400 other Heath electronic kits for your home, work or pleasure are in the new Heathkit Catalog. Send for yours today or pick one up at your Heathkit Electronic Center.

Heathkit®

Heathkit Products are also sold and serviced at Heathkit Electronic Centers (units of Veritechnology Electronics Corporation) in major cities throughout the U.S. See your white pages.

Heath Company, Dept. 020-624, Benton Harbor, MI 49022

GX-373



An introductory Electronics



THE DESIGN AND DRAFTING OF PRINTED CIRCUITS. By D. Lindsey. 196 pp., 100 illus. For everything you need to know and understand about design phases that PC artworks go through, from schematics to the finished PC, your best all-around guide is this fully illustrated new teaching tool.
054/304 Pub. Pr., \$26.95 Club Pr., \$21.00

ELECTRONICS DICTIONARY. Edited by J. Markus. 4th Ed., 768 pp., 1,173 illus., 17,090 terms. With the new edition of this world-renowned dictionary you'll be able to quickly find the meaning and correct usage of any electronics term, no matter how obscure!
404/313 Pub. Pr., \$24.50 Club Pr., \$19.50

HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN. By D. F. Stout. Edited by M. Kaufman. 434 pp., 223 illus. Compact, concise, highly concentrated, and containing a storehouse of information, this one-stop volume will help you solve any op amp circuit problem!
617/97X Pub. Pr., \$29.65 Club Pr., \$17.50

ELECTRONIC DISPLAYS. By E. G. Bylander, Texas Instruments Incorporated, 172 pp., illus. The book describes current electronic displays by family types, discussing all aspects of their operation, application, and circuit requirements. You cover photometry and contrast enhancement, together with the fundamentals of such critical components as mounts and drives, interface requirements, and other necessary engineering information.
095/108 Pub. Pr., \$19.50 Club Pr., \$15.95

DIGITAL FILTERS. By A. Antoniou. 524 pp., illus. This all-inclusive, up-to-date treatment guarantees your thorough understanding of today's digital filters and the theories, techniques, and procedures you'll be using in their analysis, design, and implementation. The book gives you many design examples, together with the numerous possible approaches and engineering tradeoffs relating to their hardware implementation.
021/171 Pub. Pr., \$23.95 Club Pr., \$18.50

BUCHSBAUM'S COMPLETE HANDBOOK OF PRACTICAL ELECTRONIC REFERENCE DATA. By W. H. Buchsbaum, 2nd Ed., 645 pp., 371 illus., 70 tables. It gives you all the technical electronic information you need—from the factual foundations of electronics to the latest technical advances in optoelectronics, large scale integrated circuits, digital logic, microprocessors, and computers. Hundreds of formulas, graphs, charts, and tables.
786/550 Pub. Pr., \$19.95 Club Pr., \$16.95

RADIO HANDBOOK. By W. I. Orr, 21st Ed., 1,135 pp., 1,364 illus. Now completely updated, expanded, and more deserving than ever this profusely illustrated reference gives you everything you need to know to understand, design, use, and experiment with every circuit and piece of equipment. (All recent technological breakthroughs are covered).
772/630 Pub. Pr., \$21.50 Club Pr., \$16.60

TRANSFORMER AND INDUCTOR DESIGN HANDBOOK. By W. T. McLyman, 428 pp., illus. User-oriented throughout, it covers everything from transformer design and inductor design with dc, power inductor design, designing for regulation, inductor design without dc, constant voltage transformer, current and three-phase transformer, to application of magnetic components in power electronics.
786/755 Pub. Pr., \$35.00 Club Pr., \$26.50

ELECTRONICS DESIGNERS' HANDBOOK. Edited by L. J. Giacoletto. 2nd Ed. 2,344 pp., 1,686 illus. Now doubled in size and with 90% of its material new, this famous classic (first edition by Landee, Davis, Albrecht) has been thoroughly revised and updated to give you not only the *how* and the *why* of all your design work but also the *how much* of every design step you take!
231/494 Pub. Pr., \$56.50 Club Pr., \$41.50

STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 11/e. By D. G. Fink and H. W. Beaty. 448 pp., 1,414 illus. A giant in every sense of the word, today's most widely used source of electrical engineering information and data serves you as no other single work available anywhere when you need detailed, accurate, timely, and reliable facts and how-to on the generation, transmission, distribution, control, conversion, and application of electric power.
209/74X Pub. Pr., \$49.50 Club Pr., \$38.00

BE SURE TO CONSIDER THESE IMPORTANT TITLES AS WELL:

LOGIC DESIGNERS' MANUAL. By J. D. Lenk. 784/671 Pub. Pr., \$18.95 Club Pr., \$15.75

CRYSTAL OSCILLATOR DESIGN AND TEMPERATURE COMPENSATION. By M. E. Frerking. 784/973 Pub. Pr., \$16.95 Club Pr., \$13.50

MINICOMPUTER SYSTEMS, 2/e. By R. H. Eckhouse, Jr. 787/026 Pub. Pr., \$21.95 Club Pr., \$17.75

UNDERSTANDING OSCILLOSCOPES AND DISPLAY WAVEFORMS. By K. W. Sessions & W. A. Fischer. 787/786 Pub. Pr., \$17.95 Club Pr., \$14.50

THE SEMICONDUCTOR MEMORY BOOK. By Intel Marketing Communications. 788/391 Pub. Pr., \$14.95 Club Pr., \$12.70


MICROPROCESSOR APPLICATIONS MANUAL. By Motorola Semiconductor Products, Inc. 435/278 Pub. Pr., \$38.00 Club Pr., \$26.50

NATIONAL ELECTRICAL CODE HANDBOOK, 16/e. By J. F. McPartland 456/909 Pub. Pr., \$19.95 Club Pr., \$14.50

SOURCEBOOK OF PROGRAMMABLE CALCULATORS. By Texas Instruments, Inc. 637/466 Pub. Pr., \$16.50 Club Pr., \$12.50

OSCILLOSCOPES. By R. Van Erk. 670/501 Pub. Pr., \$19.50 Club Pr., \$14.50

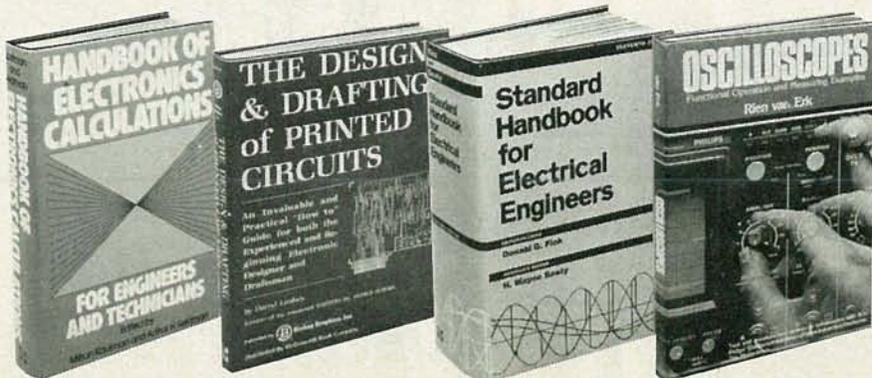NOISE REDUCTION TECHNIQUES IN ELECTRONIC SYSTEMS. By H. Ott. 769/63X Pub. Pr., \$21.25 Club Pr., \$15.50



Offer to new members of the and Control Engineers' Book Club

HANDBOOK OF ELECTRONICS CALCULATIONS FOR ENGINEERS AND TECHNICIANS. Edited by M. Kaufman and A. H. Seidman. 653 pp., 725 illus. This first comprehensive tool of its kind includes hundreds of worked-out problems in analog and digital circuits. Includes more than 700 diagrams, curves, tables, and graphs.
333/920 Pub. Pr., \$24.50 Club Pr., \$18.95

MICROCOMPUTER-BASED DESIGN By J. B. Peatman. Expanded 4th printing, 604 pp., over 400 photos and other illustrations Do all your best day-to-day designs, as well as your supercreative and special designs, around the new microcomputers and the specific "how-to" help you get here!
491/380 Pub. Pr., \$26.95 Club Pr., \$18.95

MICROELECTRONICS Digital and Analog Circuits and Systems By J. Millman. 881 pp., 700 illus. This giant book takes you step by step from a qualitative knowledge of a semi-conductor, to an understanding of the operation of devices, and finally, to an appreciation of how these are combined to form micro-electronic chips.
423/27X Pub. Pr., \$24.50 Club Pr., \$19.50

MINI/MICROCOMPUTER HARDWARE DESIGN. By G. D. Kraft and W. N. Toy. 514 pp., 250 photos, diagrams, figures. The swing is more to designing and using small-scale computers as computing components, this is your guide to doing just that! With what you already know, plus the skills you'll gain here, you'll be way ahead as the whole field of computing moves towards distributed processing element systems!
788/26X Pub. Pr., \$19.95 Club Pr., \$16.95

DIGITAL INTEGRATED CIRCUITS AND OPERATIONAL AMPLIFIER AND OPTOELECTRONIC CIRCUIT DESIGN. Edited by B. Norris. 206 pp., 400 illus. Having this vast amount of case-tested data, proven shortcuts, worked-out circuit designs, and circuit diagrams handy saves you valuable time for your other, more vital, areas of creative design—and cuts down costs in all areas!
637/539 Pub. Pr., \$21.50 Club Pr., \$15.95

INTRODUCTION TO RADAR SYSTEMS, 2/e. By M. I. Skolnik. 698 pp., 244 illus. This new edition of a widely used text on radar from the systems engineer's point of view brings you full discussions of the many major changes that have occurred in the field recently.
579/091 Pub. Pr., \$34.95 Club Pr., \$27.95

ENGINEERING MATHEMATICS HANDBOOK Definitions, Theorems, Formulas, Tables. By J. J. Tuma. 2nd Ed., 394 pp., 226 illus. Now you can use even the most difficult formulas on your pocket calculator for input and/or storage! Literally thousands of formulas were remodeled to facilitate their application to today's pocket calculator operations.
654/298 Pub. Pr., \$21.95 Club Pr., \$17.50

ELECTRONIC ENGINEER'S HANDBOOK. Editor-in-Chief, D. G. Fink. 2,104 pp., 2,026 illus. Huge in every sense, this instant-reference volume gives you every latest essential in the field, 2,100 formulas and equations, a 2,500-item bibliography, and every illustration you need to clarify all of modern electronics!
209/804 Pub. Pr., \$52.50 Club Pr., \$37.50

PRINTED CIRCUITS HANDBOOK, 2/e. By C. F. Coombs, Jr. 256 pp., 327 illus. Blueprints every important phase of printed circuitry. Provides the information you need to establish a production facility and control the processes. A virtual encyclopedia in the field, five major sections cover engineering, fabrication, assembly, soldering, and testing.
126/089 Pub. Pr., \$32.50 Club Pr., \$24.50

ENGINEERING FUNDAMENTALS FOR PROFESSIONAL ENGINEERS' EXAMINATIONS, Second Edition. By L. M. Polentz. 416 pp., 326 illus. Here—in this single volume—you'll find all the latest, most essential material you need to prepare for and pass your state's engineering registration exam. Hundreds of examples and practice problems are all drawn from actual P.E. exams, and were selected because they are representative of the problems that will appear on your exam.
503/80X Pub. Pr., \$23.50 Club Pr., \$16.95

any one
of these great
professional books

for only **\$1.89**

values up
to \$56.50

Special \$1.89 premium
book comes to you
with your first
club selection

Why YOU should join now!

- **BEST BOOKS IN YOUR FIELD**—Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the latest books in your field.
- **BIG SAVINGS**—Build your library and save money too! We guarantee savings of at least 15% off publishers' list prices on every book. Usually 20%, 25% or even higher!
- **BONUS BOOKS**—You will *immediately* begin to participate in our Bonus Book Plan that allows you savings between 70-80% off the publisher's price of many books.
- **CONVENIENCE**—14 times a year you receive the Club Bulletin FREE, fully describing the Main Selection and alternate selections, together with a dated reply card. If you want the Main Selection, you simply do nothing—it will be shipped automatically. If you want an alternate selection—or no book at all—you simply indicate it on the regular reply card and return it by the date specified. You will have at least 10 days to decide. If, because of late mail delivery of the Bulletin you should receive a book you do not want, just return it at the Club's expense.

As a member, you agree only to the purchase of four books (including your first selection) over a two-year period.

MAIL THIS COUPON TODAY

Electronics and Control Engineers' Book Club
PO. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the two books indicated, billing me for my first selection only at the discounted member's price, plus local tax, postage and handling. If not satisfied, I may return the books within 10 days and my membership will be canceled. I agree to purchase a minimum of 3 additional books during the next 2 years as outlined under the club plan described in this ad. Membership in the club is continuous but cancelable by me at any time after the four book purchase requirement has been fulfilled.

Write Code # of PREMIUM selection here	Write Code # of FIRST selection here
<input type="text"/>	<input type="text"/>

Orders from outside the U.S. must be prepaid with international money orders in U.S. dollars.

Signature _____
Name _____
Address _____
City _____
State _____ Zip _____

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members. A postage and handling charge is added to all shipments. **E 33415**




fact:
**a Genuine Shure
 upgrade stylus is
 unquestionably
 the biggest
 bargain in hi-fi**

We strongly urge you to check your stylus for wear at least once a year to protect your records and maintain the highest standards of listening pleasure. Regardless of when (or where) you purchased your Shure cartridge, there is a Genuine Shure replacement stylus available which will bring your cartridge right back to its original specifications. Even better, you may actually be able to improve its performance significantly over the original with a Genuine Shure upgrade stylus...at surprisingly low cost! For example:

IF YOU OWN:	UPGRADE WITH:
 V15 Type III SERIES	 VN35HE Hyperelliptical stylus
 M95 SERIES	 N95HE* Hyperelliptical stylus
 M70 SERIES	 N72EJ Biradial (Elliptical) stylus N72B Spherical stylus
ANY M91, M92, M93	N91ED* stylus
ANY M71, M73, M75	N75 TYPE 2* Series styli
ANY M44 Series	N55E stylus
M3D, M7D	N21D* stylus

*Before purchasing any replacement stylus be certain your turntable is compatible with the tracking force of the stylus you select.

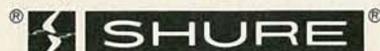**Always insist on a
 Genuine Shure
 replacement stylus.
 Look for the name
 "Shure" on the stylus
 grip.**



Shure Brothers Inc., 222 Hartrey Ave., Evanston, IL 60204
 In Canada: A. C. Simmonds & Sons Limited
 Outside the U.S. or Canada, write to Shure Brothers Inc., Attn. Dept. J6 for information on your local Shure distributor. Manufacturers of high fidelity components, microphones, sound systems and related circuitry.

CIRCLE 61 ON FREE INFORMATION CARD

EQUIPMENT REPORTS
continued from page 26

The top, bottom and sides have the simulated walnut finish. However, the exterior surface of the rear panel is unfinished and should be painted black. Also, the exterior surface of the front panel and the grille cloth frame should be painted to prevent the unfinished wood surfaces from showing through the grille cloth. Flat black latex paint is provided along with a foam paint applicator. Two coats are required for each surface. Each coat took about 1/2-hour to apply with about 1-hour drying time in between. At the end of the first coat, the foam applicator had just about had it. So, in between coats, a trip to the local hardware store was made to purchase a new one. After applying the second coat, the surfaces were allowed to dry overnight.

The next step consists of mounting the mid-range sub-enclosure on the interior surface of the front panel. The sub-enclosure consists of a plastic "cup" with a terminal block and push-on connectors on the ends of the wires that connect to the midrange driver. To mount the sub-enclosures, as well as assembling the rest of the kit, a silicone rubber cement is provided in a cartridge that is used with the caulking gun. The cement is applied to the interior surface of the front panel around the edges of the midrange cutout. The sub-enclosure is then pressed into place.

The crossover network is mounted next using the silicone rubber cement. The cement is applied to the interior surface of the rear panel around the edges of the crossover cutout. The crossover network is then pressed into place. The cement was allowed to dry overnight although the assembly manual stated that the setting time is two hours.

Next, the front panel is cemented into place. First, a brace that extends between the front and rear panels is cemented in place. Then cement is applied to the grooves in the front edges of the enclosure. These grooves permit the front panel to be flush mounted. The front panel is then pressed into place and the cement allowed to dry overnight. The damping material is installed next. A large roll of damping material is cut into three pieces; two large and one small. The two large pieces are rolled up and stuffed into the enclosure. The small piece is rolled up and stuffed into the midrange sub-enclosure. After this is done, the drivers are connected and the system connected to a power amplifier to test each of the drivers. If all the drivers are functioning, they are then cemented in place.

Cement is applied to the exterior surface of the front panel around the edges of the driver cutouts. The drivers are then pressed into place. The cement is allowed to dry overnight and then any excess cement protruding around the edges of the drivers is peeled away.

The final step is to mount the grille cloth. The grille cloth is stretched over its frame and held in place with a staple gun. The frame is attached to the enclosure with push-on fasteners that are provided in each corner of the frame and on the front panel of the enclosure. The frame is simply pressed into place.

How it sounds

Considering the price and size of this speaker system, its performance pleasantly surprised us. We placed a pair of the 2.5's in a medium-sized listening room and listened to a wide variety of program material over a 3 week peri-

od. The speakers were placed on the floor and we found that the "flat" setting of the crossover network provided the best response.

The bass response was surprisingly accurate considering the size of the speaker system. It was not at all boomy, but simply there. As expected, it did not extend into the lower bass regions as it does in some larger, more expensive systems.

Horns and cymbals were reproduced cleanly and brilliantly, attesting to the good frequency and transient response of the tweeter. The Speakerlab 2.5's provided a sense of presence and the stereo imaging was sharp. Overall, we liked the sound of the 2.5's.

If you are looking for a speaker system in this price range, you would be making a mistake not to consider the 2.5's. The complete kit featuring the utility enclosure is \$139.00 each. The same kit with the walnut enclosure is \$159.00. The model 2.5 is also available completely assembled for \$215.00. Or, if you're a real do-it-yourselfer, you can purchase just the drivers and crossover along with plans of the enclosure for \$109.00. The Speakerlab catalog also features individual drivers, crossover networks and publications describing how to design your own speaker systems. **R-E**

**Simpson Model 380
 Microwave Leakage Tester**



CIRCLE 102 ON FREE INFORMATION CARD

MICROWAVE OVEN LEAKAGE IS A HOT SUBJECT, (sorry about that!). Anyone working with microwave ovens must have testers that can detect leakage, and make sure that this leakage is below the Performance Standards of the U.S. Department of Health, Education and Welfare. The HEW standards call for a maximum of 1.0 mW per-square-centimeter at any point that is 5 cm from the oven's external surfaces prior to purchase. After purchase and use, the leakage limit goes up to 5 cm-per-square-centimeter.

Simpson Electric Company (853 Dundee Avenue, Elgin, IL 60120) has developed the model 380 microwave leakage tester. The tester is a self-contained instrument, calibrated at 2450 MHz. It has four power-density ranges: 0-2.5 mW per-square-centimeter; 0-10 mW per-square-centimeter; 0-25 mW per-square-centimeter; and 0-100 mW per-square-centimeter, with an accuracy on all ranges of ± 1.0 dB. The ranges are selected by a handy thumbwheel knob designed for using your right thumb.

For special testing, it provides two response *continued on page 34*



This \$13.00 technical library gives you specifications for 60 solid-state linear products and detailed instructions for scores of circuits

LEARN ABOUT LINEARS FROM THE INDUSTRY LEADER. EXAR MANUFACTURES HUNDREDS OF THOUSANDS OF LINEAR CHIPS EVERY WEEK. YOU'LL FIND THEM IN PRODUCTS RANGING FROM STEREO AMPLIFIERS TO REMOTE CONTROLLED MODEL RACECARS. Now you can share Exar's wide-ranging technical expertise. This technical library, written and prepared by Exar's engineering staff, contains complete technical information on operational amplifiers, function generators, phase-locked loops and timers as well as application notes and technical articles explaining how to incorporate these circuits into devices of your design.

Function generator data book: Fundamentals and specifics on IC oscillators.

Specifications, diagrams and cross references. Covers fundamentals of waveform generators and choosing the right oscillator, plus detailed specifications.

Operational amplifier data book: How they work, how to choose them, how to use them.

Definitions of op amp terms, basic applications, and active filter design, as well as cross references and detailed product specifications.

Phase-locked loop data book: Everything you need to know about the PLL.

Learn to choose the right PLL circuit and how to use it in state-of-the-art applications from wireless intercoms to modems.

Timer data book: From one-shot timers to programmable timer-counters.

Timer and timer-counter facts from fundamentals through detailed application notes. Includes complete specifications for a range of micropower timer circuits.

Applications data book: From FSK modems to electronic music synthesizers.

How to use Exar's devices in circuits including a universal sinewave converter, a single-chip frequency synthesizer, a dual tone decoder and more: Seventeen separate applications in all.

Applications dictionary: How to find the right product for your applications.

A compact but comprehensive selection guide listing IC applications and recommended IC devices.

Exar product guide: Details on IC products at your fingertips.

Complete summary of specs and information on Exar's wide product line, listed by product categories.

Semi-custom design brochure: How to develop your own custom ICs.

Complete description of Exar's unique linear and digital semi-custom IC design technology. Lets you design specialized ICs on prefabricated I²L or bipolar master chips, at low cost in a matter of weeks.

Easy to order and inexpensive too.

This complete technical library, eight separate and complete publications in all, bound in a handsome custom binder, costs only \$13.00. Each order must be accompanied by \$2.00 to cover postage and handling. To order, simply fill out the coupon, enclose your check or money order, and mail to Exar, 750 Palomar Ave., Sunnyvale, CA 94086.



Please send _____ copies of your Technical Library at your special price of \$13.00 each. With my order I enclose \$2.00 for postage and handling.

_____ x \$13.00 = _____
NO. OF TECHNICAL LIBRARIES ORDERED PRICE EACH TOTAL

California residents add 6% sales tax.

Plus \$2.00 per order, postage & handling. \$2.00

TOTAL ENCLOSED by check or money order. _____

Name _____ Phone _____

Address _____

City _____ State _____ Zip _____

Exar Integrated Systems, 750 Palomar Ave., Sunnyvale, CA 94086

RE 2-80

Put Professional Knowledge and a COLLEGE DEGREE

in your Electronics Career through

HOME STUDY



Earn Your DEGREE

No commuting to class. Study at your own pace, while continuing your present job. The Grantham home-study program leads first to the A.S.E.T. and then to the B.S.E.T. degree. Our free bulletin gives complete details. Write for *Bulletin 80*.

Grantham College of Engineering
2500 So. LaCienega Blvd.
Los Angeles, California 90034

GRANTHAM'S FCC LICENSE STUDY GUIDE
—377 pages, 16 FCC-type practice tests, 1465 questions with answers and discussions—covering third, second, and first class radiotelephone license exams. Preparation for each separate class of license is presented in a separate section of the book. \$15.65 postpaid. Order from: GSE Publications, P.O. Box 35499, Los Angeles, Ca. 90035

EQUIPMENT REPORTS

continued from page 32

times: 1.2 seconds maximum (Fast) and 3.0 seconds (Slow). The meter scale is calibrated in two arcs, 0–2.5 and 0–10. The response time in the FAST mode is well below the minimum specification called for in the HEW standard that reads "90% of maximum reading within 3.0 seconds." The range accuracy also meets the HEW standards at ± 1.0 dB.

A special probe comes with the *model 380*. This probe measures a full 13 inches long, and has a coiled cord that extends to 43 inches and retracts to only 6 inches. The probe plugs into the top of the *model 380* case, and the plug has a screw locking ring. The probe tip houses the microwave detector, which is a pair of cross-polarized antenna/thermocouples. The electromagnetic field that is being read induces a current in the antennas. This current is dissipated in the thermocouples and converted into heat, which, in turn, causes the thermocouples to generate a small DC voltage. This voltage is amplified and displayed on the meter.

The probe head has a special cone-shaped plastic cover, which is exactly 5 centimeters thick at all points. The probe head is simply held in contact with the surface of the unit being tested, and there you are. The plastic cover is removable and can be replaced if it is damaged.

The *model 380* is a two-hand instrument; one hand holds the meter and the other the probe. With the long probe, you can keep away from possible radiation. The manual warns that the instrument should be turned on and zeroed before the test is made. If you observe a

reading above 100 mW while you are still approaching the unit, stop! Something has to be repaired immediately—before you can make further tests.

The zero-adjust control is a thumbwheel 10-turn potentiometer on the right side of the case. This control is also used for a quick probe-test. Zero the *model 380* with the probe connected (in a location with zero radiation, of course). Then, disconnect the probe; if the meter stays on zero, the probe is defective. It should jump backward off-scale.

The slow 3.0-second response time is provided so you can test home-type ovens that have stirrer mechanisms and similar devices. These devices can cause a reading to fluctuate. By switching to the slow mode, the fluctuation can be eliminated for a more accurate reading. The *model 380* can also be used for any industrial application that involves microwave heating or drying, etc. For safety's sake radiation leakage levels on these units should be read at stated intervals.

The *model 380* comes in a neat plastic carrying case that looks like an attache case. The case is foam-lined with holes cut to fit the meter, probe, cable, manual, and even a couple of spare 9-volt batteries. The batteries fit in a compartment on the back of the case, with a cover held on by two screws. The case even has a neat plastic nametag with space for name and address, etc.

This is a beautifully made instrument that should be invaluable. It carries a suggested list price of \$270. **R-E**

SF STD-36 Radio Operating Desk




CIRCLE 103 ON FREE INFORMATION CARD

IN SPITE OF THE ENORMOUS NUMBER OF MANUFACTURERS of consumer electronic equipment, very few manufacturers are making anything to set it on! Naturally, tables may be fabricated from plywood and composition board, wooden doors may be called into service or even old kitchen tables will do in a pinch. When money is no object, the affluent buyer can go to an office supply store and purchase a desk. But amateur radio installations have special requirements. Usually, there are numerous pieces of peripheral equipment as well. SWR meters, antenna matchboxes, clocks, receivers, transmitters, antenna rotators, microphone . . . all take up considerable room. While a spacious wrap-around console would be nice, it

continued on page 36

This is easy- anyone can solder- WITH KESTER SOLDER

KESTER SOLDER

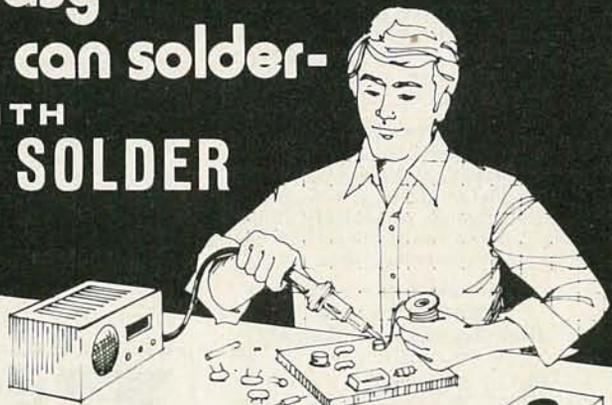

Handymen! Hobbyists! DO-IT-YOURSELFERS!

Let Kester Solder aid you in your home repairs or hobbies. For that household item that needs repairing — a radio, TV, model train, jewelry, appliances, minor electrical repairs, plumbing, etc. — Save money — repair it yourself. Soldering with Kester is a simple, inexpensive way to permanently join two metals.

When you Solder go "First Class" — use Kester Solder.

For valuable soldering information send self-addressed stamped envelope to Kester for a FREE Copy of "Soldering Simplified".



KESTER SOLDER

Litton 4201 WRIGHTWOOD AVENUE/CHICAGO, ILLINOIS 60639

CIRCLE 9 ON FREE INFORMATION CARD

For the Best and Latest in Computer Technology... Look to Howard W. Sams & Co., Inc.

There's something for everyone—from those who want to discover what computers are all about to those who are already utilizing computers and programming. The fundamentals . . . programming . . . interfacing . . . logic—we are the complete knowledge source for home, business, educational and professional users.

The "Starters"



How to Buy & Use Minicomputers and Microcomputers
by Barden.

A single source to buying and using a computer in your home or business to handle recreational or practical tasks from playing games to setting up a burglar alarm. 240 pages, No. 21351, \$9.95

The Howard W. Sams Crash Course in Microcomputers
by Frenzel.

new

The first complete crash course in microcomputers for everyone—from the average consumer to the Doctor of Science. 264 pages, No. 21634, \$14.95

Getting Acquainted With Microcomputers
by Frenzel.

Gives you a complete working knowledge of the microcomputer—organization, operation, and programming. 288 pages, No. 21486, \$8.95

Fundamentals of Digital Computers (2nd Ed.)
by Spencer.

Unravels the mysteries of computers and programming. 320 pages, No. 21534, \$9.95

Introduction to Microcomputers for the Ham Shack
by Helms.

Gives the radio amateur an opportunity to be in the forefront of utilizing and developing techniques in "computerations." 96 pages, No. 21681, \$4.95

Prepub Offer—Save 10% (expires 3/31/80)

Microcomputer Primer, (2nd Ed.)
by Waite and Pardee.

new

Completely revised and broadened to reflect the latest advances in microprocessor technology from the new 8-bit microprocessors to solderless breadboards. An excellent starting point for all those interested in computers. Approximately 368 pages, No. 21653, Prepub price—\$10.75. Regular Price—\$11.95

The "Programmers"

How to Program Microcomputers
by Barden.



A popular, complete guide to assembly language programming of the Intel 8080, Motorola MC6800, and MOS Technology MCS 6502 Microprocessors. 256 pages, No. 21459, \$8.95

BASIC Programming Primer

by Waite and Pardee.
Covers everything from getting organized to writing a game program. 240 pages, No. 21586, \$8.95

DEBUG: An 8080 Interpretive Debugger
by Titus and Titus.

Covers program operation and how it's applied to program development and testing. 112 pages, No. 21536, \$4.95

6502 Software Design
by Scanlon.

new

Tells how to program for the 6502 assembly language. Approximately 288 pages, No. 21656, \$9.95*

8080/8085 Software Design, 2 volumes
by Titus.

new

Volume 1 gives you an introduction to assembly language programming. 336 pages, No. 21541, \$9.50—Volume 2 is a unique, one-of-a-kind, computer science book for the design engineer. Written in Intel machine code. 352 pages, No. 21615, \$9.95

Two-volume set No. 21659, \$17.50

TEA: An 8080/8085 Co-Resident Editor-Assembler
by Titus.

new

256 pages, No. 21628, \$8.95

The "Computer Technology" Leaders



The Z-80 Microcomputer Handbook
by Barden.

Gives current and prospective users a one-stop source to Z-80 technology—hardware and software aspects and instrumentation problems. 304 pages, No. 21500, \$8.95

Using the 6800 Microprocessor
by Poe.

Acquaints you with the hardware and software of the "6800" fun machine. 176 pages, No. 21512, \$6.95

Computer Graphics Primer
by Waite.

new

Shows how to create your own graphic affects—from detailed drawings to moving figure animation. Approximately 184 pages, No. 21650, \$12.95

Microcomputers for Business Applications
by Barden.

Explains the various types of microcomputers available, points out pitfalls to avoid, and defines computer-related terms, or "buzzwords" in easy-to-understand language. 256 pages, No. 21583, \$8.95.

"Interfacing" Bookshelf



Microcomputer-Analog Converter Software & Hardware Interfacing
by Titus, Titus, Rony, and Larsen.

Concepts and techniques of interfacing digital computers to analog devices. 288 pages, No. 21540, \$9.50

TRS-80 Interfacing
by Titus.

new

Interfacing & Scientific Data Communications Experiments
by Rony, Larsen, Titus & Titus.

new

160 pages, No. 21546, \$5.95

Microcomputer Interfacing With the 8255 PPI Chip
by Goldsbrough.

new

224 pages, No. 21614, \$8.95

Z-80 Microprocessor Programming & Interfacing, 2 Volumes
by Nichols, Nichols & Rony.


new

800 pages, No. 21611, \$21.95.

Introductory Experiments in Digital Electronics and 8080A Microcomputer Programming and Interfacing, 2 Volumes,
by Rony, Larsen, and Titus.

new

912 pages, No. 21552; \$20.95

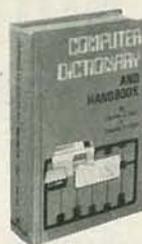

"Reference" Library

Computer Dictionary & Handbook (3rd Ed.)
by Sippl and Sippl.


new

The best and latest resource for anyone involved in computers or computer applications. over 900 pages; No. 21632 \$25.95

Computer Dictionary (3rd Edition)
by Sippl and Sippl.

Over 12,000 entries, 640 pages, No. 21652, \$11.95*

"Logic" Cookbooks

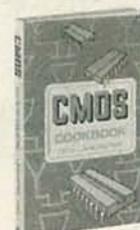

CMOS COOKBOOK

The well-known author, Don Lancaster presents an information-packed guide to this low-cost, fun-to-work with digital logic family. 416 pages, No. 21398, \$10.50

TTL Cookbook
by Lancaster.

336 pages, No. 21035, \$9.50

The Cheap Video Cookbook
by Lancaster.

256 pages, No. 21524, \$5.95

IC Op-Amp Cookbook

by Jung. 592 pages, No. 20969, \$12.95

RTL Cookbook

by Lancaster. 240 pages, No. 20715, \$6.50

TV Typewriter Cookbook

by Lancaster. 256 pages, No. 21313, \$9.95

IC Converter Cookbook

by Jung. 576 pages, No. 21527, \$13.95

* Tentative price

Look to Sams . . . In the world of computers

ORDER FORM

HOWARD W. SAM'S & CO., INC.
4300 WEST 62ND STREET, P.O. BOX 7092
INDIANAPOLIS, INDIANA 46206
(317) 298-5400

Indicate quantity in boxes above and complete ordering information below:

Sub Total _____

Add local sales tax where applicable _____

GRAND TOTAL _____

Bill Me (Shipping and Handling Charge will be added)

Payment Enclosed (No Shipping Handling Charge)

Check Money Order

Master Charge

Bank Americard/Visa

Exp. Date _____

Account No. _____

Interbank No. _____
(Master Charge Only)

Minimum Credit Card Purchase \$10.00 **565**

Please send free 1980 Computer Book Catalog.

Signature _____

Name _____
Last Middle First

Address _____

City _____ State _____ Zip _____

Prices subject to change without notice. All books available from local Sams Distributor. Offer good in U.S. only

Note: Distributor, computer store and dealer inquiries are welcome.

CIRCLE 37 ON FREE INFORMATION CARD

BUILD A MASTERPIECE OF SOUND



percussion and sustain. Wersi's famous string orchestra and bass guitar. Exclusive Sound Computer for 32-128 "One Stop Sounds" (total organ presets). Transposer. And lots more.

Build your own masterpiece of sound. No technical knowledge required. Just follow the clearly illustrated, easy to understand instructions. Step by step. Choose from at least 10 models. (Also factory assembled.)

Send \$6.00 with coupon for your Wersi Demo-Package (LP with 104-page color catalog).



Wersi has combined select features of the electronic music field, added its own creations and years of research by top engineers and musicians, to produce an incomparable line of organs.

Space-age technology. True-to-life voicing with full drawbar system. Polyphonic

Wersi Electronics, Inc. or Wersi Organs & Kits RE280
1720 Hempstead Road 14104 E. Firestone Blvd.
Lancaster, PA 17601 Santa Fe Springs, CA 90670

Enclosed is \$6.00 for my Demo-Package (LP with 104-page color catalog.)

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE 20 ON FREE INFORMATION CARD

THIS VISE IS CATCHING.

Catch PanaVise. It tilts, turns and rotates your work exactly where you want. Add our new Tray! It catches small parts you drop, separates tools, and keeps parts sorted. The Tray's wide 8 1/4" diameter of cast metal gives 'no-tip' stability, and has 6 slip resistant neoprene feet. Catch all the PanaVise combinations at your distributors now. Write for FREE brochure and distributor list.

PANA VISE®

Dept. CE 11
2850 29th St.
Long Beach, CA 90806

Shown:
#315 Circuit Board Holder, #300 Base, #312 Tray Base Mount.



CIRCLE 49 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 34

isn't very practical. A multi-tiered console would be just the thing to put all operating controls within easy reach.

SF Amateur Radio Services is now offering a series of radio operating desks, featuring different styles, colors, and sizes. The desk we decided to sample was the model *STD-36*, a 36" wide, walnut finished standard model. Other models range from unfinished (\$135) to solid walnut (\$275). In addition, the handsome line is now supplemented with a series of consoles for home computers. Any of the styles and sizes may be furnished in walnut, teak, or clear lacquer. All models are finished in oil stain with two coats of clear lacquer. Metal braces are finished in baked black enamel. The braces themselves are fabricated from 1" square 18-gauge steel. At present, delivery may be expected within three weeks of receipt of order.

Our *STD-36* arrived in two shipping cartons. Packing was adequate, and no marring or scratching of the components was evident and no components were lost.

The desk is a semi-kit. All pieces are completely finished, and drilled for assembly. Our kit included 11 wood shelves and panels, 6 metal legs and braces, and a bag of hardware. To assemble the kit, what we needed to provide was glue, a standard screwdriver, a hammer, and a pick (to set a couple of pilot holes for two small screws).

As beautifully designed and prefabricated as the desk is, we had considerable difficulty in assembling the unit. A job which shouldn't have taken much more than an hour turned into several hours. The difficulty was that although engineering drawings are supplied, there are no instructions whatever provided. No parts count, no description, no helpful step-by-step instructions or other hints. At one point we had to tear a subassembly apart after gluing it, and start all over again. Although SF Amateur Radio Services shows a picture of the assembled unit in their advertising, none is supplied with the kit. As a result, unless the buyer has one of the promotional flyers that features a large picture of a typical unit, he has to guess at what the finished product should look like.

The various subassemblies are securely held in place by eighteen 1/4-inch socket head screws provided. Matching T nuts are used to draw the assembly snugly in place. An Allen wrench is included in the semi-kit in order to torque up the screws.

Once finally assembled, the desk is quite substantial. It is built to withstand at least 200 pounds of equipment, and resists shear with its internal braces.

When properly assembled, the handsome desks from SF lend an elegance to the decor of a hobby communications installation. The model *STD-36* Radio Desk has a \$149.95 suggested retail price and is available from SF Amateur Radio Services, 4384 Keystone Avenue, Culver City, CA 90230. **R-E**

Panasonic Model RF4900 10-Band Receiver

WHILE MOST OF US THINK OF PANASONIC AS A consumer appliance manufacturer of TV sets, calculators and the like, the company does
continued on page 38

BK PRECISION**PHILIPS****TRIPLETT****VIZ****LEADER****HICKOK****Hitachi****Simpson****FLUKE****Non-Linear Systems****DORIC****DATA PRECISION****SUPER SPECIAL****HICKOK 385
500MHz COUNTER**Reg 419⁹⁵**NOW 199⁹⁵**

LIMITED QUANTITIES

**Model LBO-520
30 MHz Dual Trace
Scope with Delay Line**

List Price \$1100

\$879⁹⁵**High Sensitivity.
Wide Bandwidth.****Single Shot Trigger. P-D-A CRT.**

- 5mV sensitivity facilities accurate signal viewing from low level sources.
- Built-in delay line makes it easy to view the leading edge of a pulse.
- Single shot trigger (CH-1, CH-2) captures transient phenomena — no guesswork, no "double-takes".

**PORTABLE
OSCILLOSCOPES**

BATTERY OPERATED

NLS Non-Linear Systems**MS-15****Single Trace 15MHz
Reg. price \$349.
\$299⁹⁵****MS-215****Dual Trace 15 MHz
Reg. price \$465.
\$399⁹⁵****MS-230****Dual Trace 30MHz
Regular price \$598.
\$499⁹⁵****New Portable Digital Capacitance Meter****BK PRECISION****MODEL 820**

Call For Our Price


- Measures capacitance from 0.1pF to 1 Farad
- Resolves to 0.1pF
- 10 ranges for accuracy and resolution
- 4 digit easy-to-read LED display
- 0.5% accuracy
- Special lead insertion jacks or banana jacks
- Fuse protected
- Uses either rechargeable or disposable batteries
- Overrange indication

8020A

- 26 Ranges—5 Functions plus New Conductance Function for up to 10,000 M Ω Leakage Measurements
- Extensive Overload and Transient Protection
- Rugged Construction—2 Year Warranty
- Hi/Lo Power Ohms for In-circuit Resistance and Diode Testing
- 10 M Ω AC/DC Input Impedance Doesn't Load Circuit
- 200 Hour, 9V-Battery Life—Low Battery Indicator
- Large LCD Readout—2000 Counts
- 0.1% Basic dc accuracy
- One Hand Operation
- Complete with Battery and Test Leads

The new Fluke 8020A continues the standard of excellence set by the highly successful 8000A multimeter family. Many features set the 8020A apart as a truly exceptional instrument. Twenty-four ranges and 5 functions include measuring capability up to 1000V dc, 750V ac, 2A ac/dc and 20 M Ω . Hi/LO ohms are included for in-circuit resistance and diode test capability. In addition, a new Conductance function allows resistance and leakage measurements up to 10,000 M Ω , a must for circuit board work and component checking.

The 8020A has been designed with the user in mind and features exclusive one-hand operation. For harsh service environments, the 8020A has a ruggedized case and extensive overload/transient protection backed up by a 1-year warranty. Long term stability (1-year calibration cycle) is excellent with only three cal adjustments. Up to 200 hours of continuous operation can be expected from a single 9V alkaline battery.

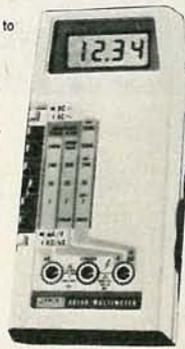**NOW
\$169.****FREE CASE WITH 8020A**

0.1% Basic dc accuracy

New Low Distortion Function Generator**BK PRECISION****MODEL 3010**

- Generates sine, square and triangle waveforms
- Variable amplitude and fixed TTL square-wave outputs
- 0.1 Hz to 1MHz in six ranges
- Push button range and function selection
- Typical sine wave distortion under 0.5% from 0.1Hz to 100kHz
- Variable DC offset for engineering applications
- VCO external input for sweep-frequency tests

New Sweep/Function Generator**BK PRECISION****MODEL 3020**

- Four instruments in one package—sweep generator, function generator, pulse generator, tone-burst generator.
- Covers 0.02Hz-2MHz
- 1000:1 tuning range
- Low-distortion high-accuracy outputs
- Three-step attenuator plus vernier control
- Internal linear and log sweeps
- Tone-burst output is front-panel or externally programmable

**THE TEST EQUIPMENT SPECIALISTS****TOLL FREE HOT LINE****800-223-0474**

54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

**ADVANCE
ELECTRONICS**

FEBRUARY 1980

37

EQUIPMENT REPORTS
continued from page 36

produce a quality line of receivers called the *Command Series*.

The 10-band model *RF4900* is the top of the line, and it is an eye opener! Its exceptionally handsome styling—a black military-style cabinet with chrome trim—features a brilliant 4-digit fluorescent display that works accurately on all frequency ranges. The receiver tunes continuously from 525 kHz through 30 MHz (AM/CW/SSB), and from 88 MHz through 108 MHz (FM).



CIRCLE 104 ON FREE INFORMATION CARD

A dual-speed main tuning drive makes frequency selection a snap. There is, however, some dial backlash that must be tolerated. RF preselection is self-tracking, so manual peaking is unnecessary.

Transparent, high-fidelity sound is heard through the internal speaker on FM. For communications, the IF selectivity can be switched from wideband to narrowband. Separate treble and bass controls allow audio contouring as desired; and a calibrated S-meter doubles as a battery tester.

The automatic noise limiter is moderately effective against impulse noise, but more clipping would be desirable. Three separate antennas are required for the 0.525–3-MHz, 3–30-MHz and FM ranges.

A separate main tuning dial is used on the lowest frequency range that provides very rapid tuning, making accurate dialing a little touchy. A high number of images can be heard throughout the 0.525–3-MHz range.

In the frequency range from 3–30 MHz, the model *RF-4900* is a different receiver. Images are nearly undetectable even in the most crowded portion of the frequency spectrum; this may be attributed to up-conversion of the double superheterodyne design. A variable beat-frequency oscillator pitch control allows the adjustable selection of LSB/USB modes, and a front-panel trimmer provides easy frequency calibration.

The unit's up-conversion capability substantially reduces IF images. A crystal-controlled first oscillator provides remarkable stability; good enough in most cases to copy teletype signals as well as SSB and CW signals. Band switching is very positive. There are no erratic switch contacts to cause instability.

It's a pleasure to tune through all the frequency ranges and not have to continually peak a preselector control; tracked RF tuning makes this possible.

A separate RF gain control can be adjusted to reduce pumping on CW or SSB signals, as well as to cut down background interference. It can provide up to 45-dB signal attenuation. An antenna trimmer may be adjusted to accommodate variations in antenna impedance for optimum matching.

Although most users will power the receiver on 120 VAC, battery operation is provided. Power consumption is 10 watts.

The dial lights and frequency display can be switched off to conserve power during battery operation (eight D cells are required). A 12-volt jack is accessible on the rear apron for mobile use and front-panel jacks are included for an external speaker (or earphones), a recorder output and an audio input to make use of the excellent internal 2-watt amplifier. The metal wrap-around cabinet provides distinctly superior shielding.

Sensitivity is reasonably good. Remember, the general use of reasonably large antennas for the shortwave frequencies makes exceptionally high receiver sensitivity unnecessary.

The model *RF-4900* is a pleasure to use, and a worthy competitor in the growing field of general-coverage receivers. It is available for a suggested retail price of \$499.95 from Panasonic Company, One Panasonic Way, Secaucus, NJ 07094. **R-E**



"Somehow, this garage-opener has gotten on a zipper frequency."

**THE BIG PLUS +
Graphic Equalizer**

ASSEMBLED

\$200⁰⁰

KIT

\$120⁰⁰



LOADED with Quality Features!

- Stereo . . . Eleven Bands Per Channel • Extremely Low Noise & Distortion • LED Peak Indicators • Center Detent ("flat") sliders • Built-in "record" Switching • Line and Microphone Level Inputs/Outputs • Regulated Power Supply • Fully Guaranteed • Horizontal or Vertical Cabinets • Kit or Fully Assembled • Plus Much, Much More!

Absolutely equals or exceeds overall performance and features of any graphic equalizer made today!

AARON-GAVIN INSTRUMENTS, INC.


17231 Corla Avenue Tustin, California 92680

Yes! I've enclosed \$ _____, RUSH me: cabinet send brochure
 _____ assembled equalizers at \$200.00, p.p.d. _____ unassembled equalizer kits at \$120.00, p.p.d. Horizontal (flat) Vertical (up-right)
 California residents include 6% sales tax Visa & Master Charge orders accepted
 Name _____ Card No. _____ Bank _____
 Address _____ Exp. Date _____ No. _____
 City _____ State _____ Zip _____

Dealer inquiries invited

CIRCLE 23 ON FREE INFORMATION CARD

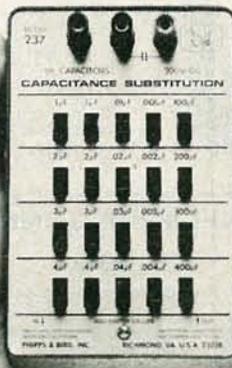**NOW YOU CAN SUBSTITUTE
CAPACITANCE AT THE
FLICK OF A SWITCH**



Phipps & Bird's new capacitance substitution unit is no bigger than your hand, yet has a 5-decade capacitance range. A special discharge feature makes it safe for use with sensitive circuits; a strong metal case makes it sturdy for all applications.

Don't guess: switch to certainty. By Phipps & Bird.



PHIPPS & BIRD, INC.

Manufacturers of Scientific Instruments
P.O. Box 27324 Richmond, Virginia 23261
(804) 264-7590

Please send _____ units at \$95 each. (Check enclosed, less 5% cash discount—Phipps & Bird will pay shipping charges.)

Please send _____ units at \$95 each, COD. (Phipps & Bird will pay COD & shipping charges.)

Name: _____

Firm: _____

Address: _____

City, State, Zip: _____

CIRCLE 62 ON FREE INFORMATION CARD

Innovations

The sharpest picture ever achieved in big-screen projection TV


The new Heathkit Screen Star sets a new standard in picture quality for big-screen projection TV. The finest F1.0 lenses you can buy produce one of the clearest, brightest pictures ever.

Imagine watching all your favorite TV movies and sports events on a big 6-foot diagonal screen. Heathkit's three-tube projection gives you brighter, more vivid color. And it's a lot easier to build than conventional TV's.

A complete computer system in one compact unit

The Heathkit All-In-One Computer takes the guesswork out of selecting a balanced computer system. It includes built-in floppy storage, smart terminal, heavy-duty keyboard, 12-key numeric pad, Z80 CPU, and 16K RAM expandable to 48K—all in one compact unit.

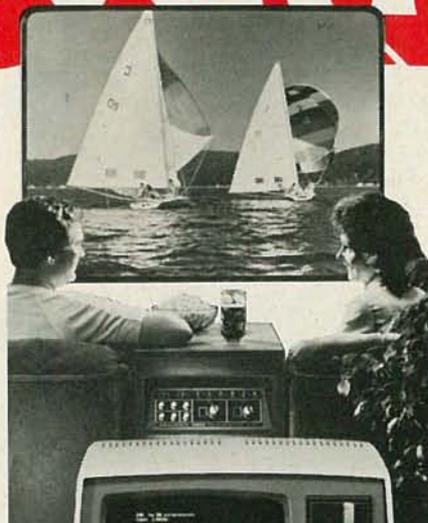Two Z80 microprocessors mean terminal and computer never share power. So both can operate faster on more complex programs. And there's no better way to learn about computers than to build one yourself.



Heathkit®

If coupon is missing, write Heath Co.,
Dept. 020-622,
Benton Harbor, MI 49022

Heathkit Products are also sold and serviced at Heathkit Electronic Centers (units of Veritechnology Electronics Corporation) in major cities throughout the U.S. See your white pages.

The only computerized home weather station for instant, up-to-the-minute weather reports

Just push a button for reliable weather information anytime you need it with the unique Heathkit Weather Station.

It gives you digital readouts of F or C temperatures, wind speed in miles or kilometers per hour or in knots, wind direction, barometric pressure, date and time of day, even the wind chill factor.

This microprocessor-based weather computer has memory to store data and precision infra-red sensing devices built into the outdoor transmitter. And it's very easy to build.

The finest stereo receiver ever introduced by one of the leaders in audio technology

It's loaded with luxury features that let you adjust your music to your preference.

Special features include a Precision

Tuning System (PTS) that automatically corrects mistuning. 5-section FM tuning capacitor gives you maximum rejection of unwanted signals for lower noise, cleaner sound. Digital frequency readout, center tune meter, and flywheel loaded tuning are just a few of the luxury touches. Complete specifications are in the latest Heathkit Catalog.

FREE CATALOG

See all the newest innovations in build-it-yourself kits in the latest free Heathkit Catalog. It contains nearly 400 exciting kits for your home, work or pleasure. Send today.



Send to: Heath Company, Dept. 020-622,
Benton Harbor, MI 49022

Yes, please send me a Heathkit Catalog.
I am not currently receiving your catalogs.

Name _____

Address _____

City _____ State _____

CL-725A Zip _____

HITACHI OSCILLOSCOPES

Single and dual trace, 15 and 30 MHz. All four high sensitivity Hitachi oscilloscopes are built to demanding Hitachi quality standards and are backed by a 2-year warranty. They're able to measure signals as low as 1mV/division (with X5 vertical magnifier). It's a specification you won't find on any other 15 or 30 MHz scopes. Plus: Z-axis modulation, trace rotation, front panel X-Y operation for all four scope models, and X10 sweep magnification. And, both 30 MHz oscilloscopes offer internal signal delay lines. For ease of operation, functionally-related controls are grouped into three blocks on the color coded front panel. Now here's the clincher: For what you'd expect to pay more, you actually pay less. Suggested list price of our top line V-302 dual trace 30 MHz is only \$945.00. The other models comparably less. Check our scopes before you decide.

Hitachi...The measure of quality.

- V-302 30 MHz Dual Trace \$945.00
- V-301 30 MHz Single Trace \$745.00
- V-152 15 MHz Dual Trace \$695.00
- V-151 15 MHz Single Trace \$545.00



Hitachi Denshi America, Ltd.

For more information, contact
Hitachi Denshi America, Ltd.,
175 Crossways Park West, Woodbury, N.Y. 11797
(516) 921-7200.



More sensitive to your input.

CIRCLE 32 ON FREE INFORMATION CARD

ping less often. By watching the power-level meter, frequent clipping can be observed and the level turned down to prevent it. This power-level meter is actually a *voltage* rather than power-reading device, as virtually all solid-state power amplifiers clip at a constant voltage (independent of load impedance), especially during transients, and therefore measuring voltage is a viable method of measuring maximum power.

A power-level meter can be used to compare the dynamic range of program sources (and explain much of the difference between FM broadcasts and records). It can help you set up the balance of your system. Since it is fast and peak-responding, it can be modified (see the construction section of this article) to aid in setting tape recording levels. But, like a seconds readout on a digital clock, it is very useful for making you feel good about your equipment's operation and just plain fun to watch.

How It Works

A new LED driver IC (LM3914) from National Semiconductor has allowed a truly low-cost circuit design which, when combined with the economies of kit construction, allow the PLM to sell in kit form for only \$42. The LED driver IC takes an analog input and drives up to ten LED's in a bar-graph mode with constant current. It also provides a reference voltage. A block diagram is shown in Fig. 1.

The use of this IC for both channels with a "free" multiplexing technique allows the entire circuit to be constructed on a tiny 2 × 4-inch PC board and housed in a single piece of 3/4-inch walnut 5 1/2 inches wide and 2 5/16 inches deep—less than 0.1 board foot—thus saving lots of the cost and adding the elegance of smallness.

The complete schematic is shown in Fig. 2. Right and left channels operate identically. I'll use the right channel in discussing the circuitry. Pot R2 adjusts the gain of the system so that the highest LED indicates clipping in the amplifier. If the voltage of the wiper of R2 is positive (I'll call this voltage V_{in}), pin 4 of IC1 will go negative until the voltage on the anode of D1 is $-R5/R4$ times V_{in} . Since negative feedback always keeps pin 1 of IC1-b at zero volts, the current through

R6 then is $-V_{in} \frac{R5}{R4 \times R6}$. This is twice as great as the current in R7 ($V_{in}/R7$) but of opposite polarity, making the net current approximately $-V_{in}/R7$. If V_{in} is negative, pin 4 of IC1-a goes positive by about 0.6 volt to keep pin 6 at zero volts. Diode D1 then is non-conducting, and there is no voltage on, nor current through, R6. The net current through R6 and R7 then is $V_{in}/R7$. IC1-a and its resistors thus form an active rectifier, such that the current is always $-|V_{in}|/R7$. In this way, the circuit responds equally to positive and negative peaks.

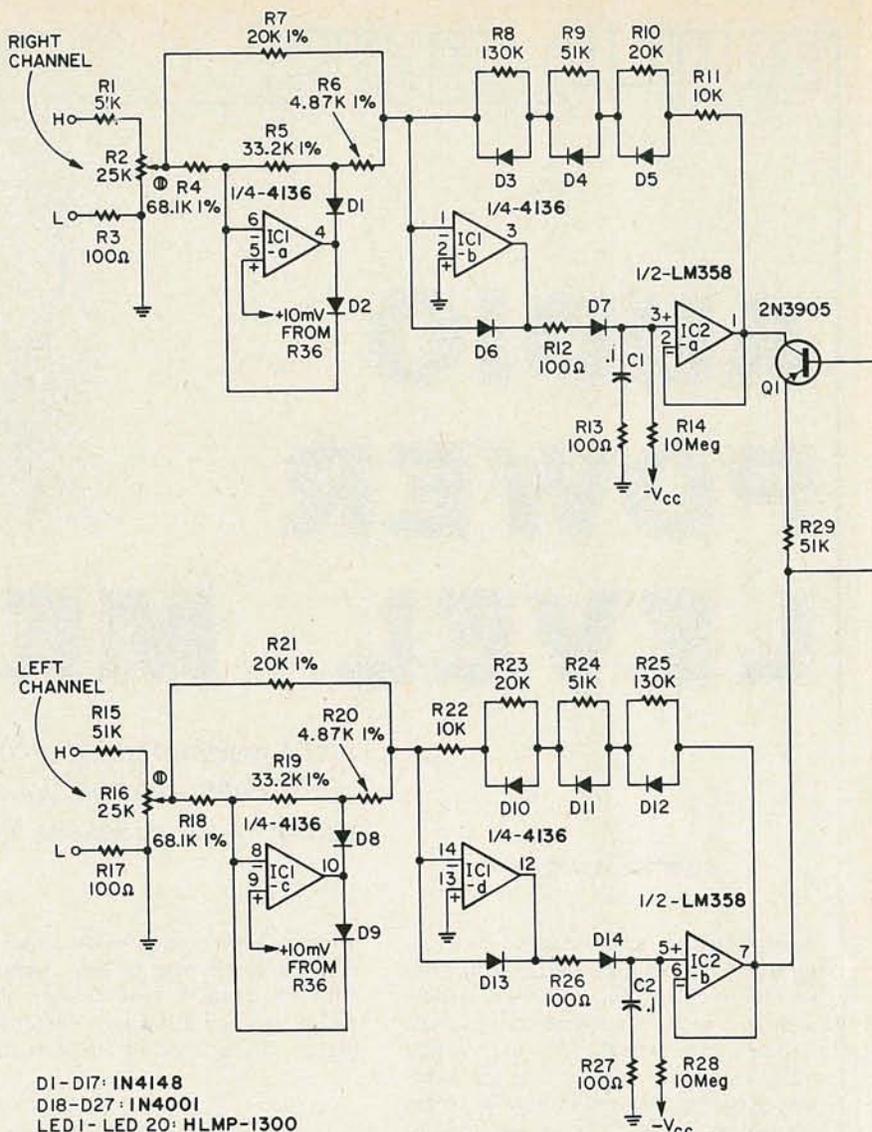


FIG. 2—COMPLETE SCHEMATIC of the LED power-level meter. The LED's in the two channels are multiplexed at a 60-Hz rate by half-sine voltages from the power transformer


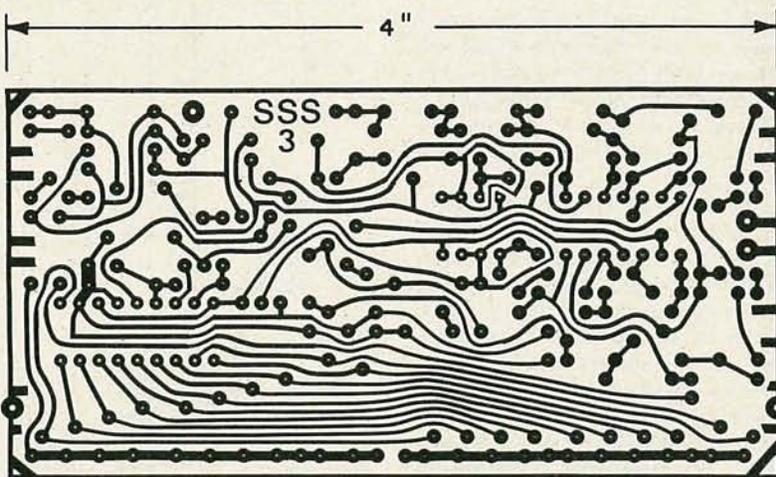


FIG. 3—FULL-SIZE FOIL pattern for the printed-circuit board. The single-sided design makes copying easy.

The rest of the circuit forms a peak detector and logarithmic converter. Resistors R8 through R11 and D3 through D5 are wired so that their current vs. voltage response is approximately logarithmic. Therefore, if the logarithm of the output voltage is less than the input, IC1-

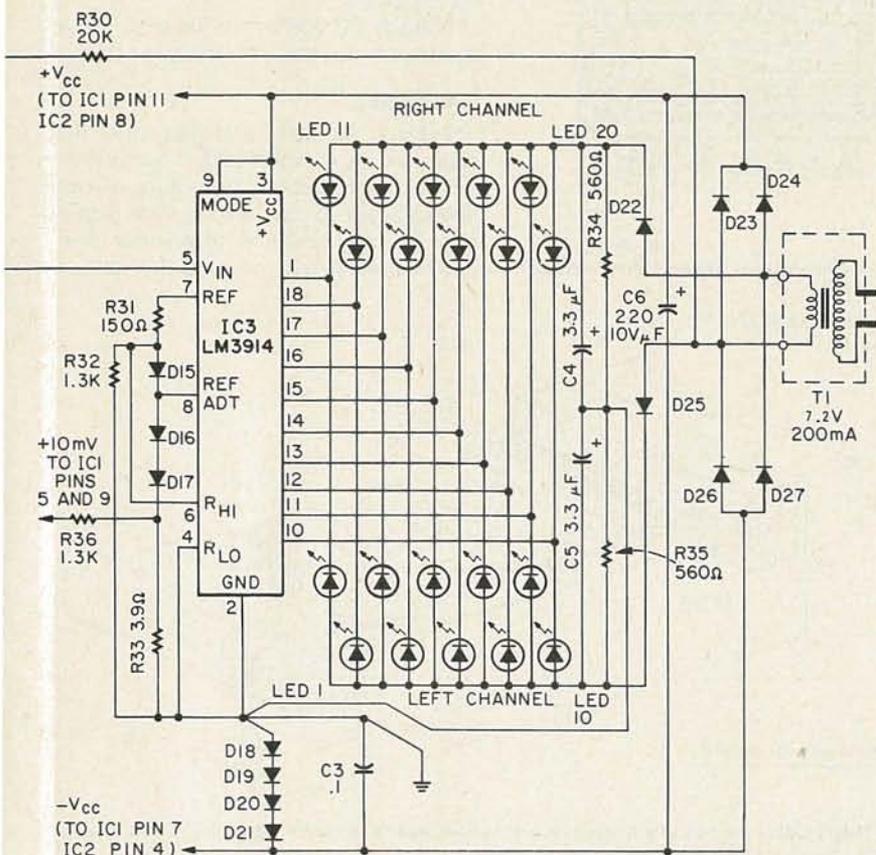b pin 3 will turn on D7 and charge up C1 until the output voltage is equal to the log of the input. If the log of the input is less than the voltage on C1, IC1-b will turn on D6 and C1 will slowly discharge through R14. Capacitor C1 then can charge very fast and discharge very slow-



ly, allowing the eye to see peaks that don't exist for very long.

The right channel or left channel is routed to the LED driver IC depending on the polarity of the 60 Hz power input. If the power input is positive, D22 provides current to the right channel LED's, and the low voltage on the bottom side of the transformer pulls current through R30 to turn on Q1 and short the right channel output to the input of IC3. For negative transformer outputs, Q1 is turned off and the left channel is connected to IC3 through R29, and the left channel LED's are turned on through D25. Thus, the right channel and left channel operate alternatively 60 times a second, too fast for the eye to notice.

The LED's used should be high-efficiency T-1 (3.18 mm, 0.125 inch diameter) LED's, as the average current through each is limited to about 10 mA. Xciron's XC-309-R and Hewlett-Packard's HLMP-1301 both have typical and minimum brightnesses of 2 and 1 mcd (millicandela—a unit of brightness) at 10 mA, respectively, and thus are recommended. Monsanto's MV5774 is .75 mcd min. The 209 series of LED's is not rec-

ommended as the typical brightness is usually only .5 mcd at 10 mA and many manufacturers don't even specify minimums. Also, high-efficiency types have even greater advantages in pulsed applications, which is how they run here due to the multiplexing.

Diodes D23, D24, D26 and D27 form a full-wave rectifier that charges C6, the main power supply capacitor. Capacitor C6 can be small because the large LED currents do not come from it, just the power supply currents of the IC's. The power supply current of IC3, as well as any LED currents, flow out pin 2 of IC3 and through D18-D21. This biases the point defined to be ground at about 2.5 volts above the negative side of D6 and creates the dual supplies necessary to run IC1 and IC2. It also reduces the voltage across the outputs of IC3 by 2.5 volts, thus reducing the power dissipation.

Construction

The use of a PC board is almost mandatory unless you decide on a different mechanical design than mine. Should you wish to redesign the system, keep LED leads short, and C4 and C5 must have

PARTS LIST

All resistors 1/4 watt, 5% unless otherwise noted

- R1, R9, R15, R24, R29—51,000 ohms
 - R2, R16—25,000 ohms trimmer potentiometer
 - R3, R12, R13, R17, R26, R27—100 ohms
 - R4, R18—68,100 ohms, 1%
 - R5, R19—33,200 ohms, 1%
 - R6, R20—4,870 ohms, 1%
 - R7, R21—20,000 ohms, 1%
 - R8, R25—130,000 ohms
 - R10, R23, R30—20,000 ohms
 - R11, R22—10,000 ohms
 - R14, R28—10 megohms
 - R31—150 ohms
 - R32—1300 ohms
 - R33—3900 ohms
 - R34, R35—560 ohms
 - R36—13,000 ohms
 - C1, C2—0.1 μ F, polyester film, 10%
 - C3—0.1 μ F ceramic disc
 - C4, C5—3.3 μ F, 50 volts, electrolytic
 - C6—220 μ F, 10 volts, electrolytic
 - Q1—2N3905
 - D1—D17—1N4148
 - D18—D27—1N4001
 - LED1—LED20—HLMP-1300 series LED's (Hewlett-Packard)
 - IC1—4136 quad op-amp (Exar, Fairchild, TI or equal)
 - IC2—LM358 low-power dual op-amp (National)
 - IC3—LM3914 dot/bar display driver (National), Radio Shack catalog No. 276-1707
 - T1—wall-plug transformer, 7.2 volts AC, 200 mA
- Miscellaneous: walnut cover, aluminum front panel, PC board, mounting hardware.

Note: The following parts are available from Symmetric Sound Systems, 912 Knobcone Place, Loveland, CO 80537. Complete kit model PLM-1 with unfinished walnut case and unpainted front panel \$42.00. Semi-kit model PLM-SK consisting of PC board, IC1, IC2 and T1 \$15.00. Both prices include postage in North America. Colorado residents add 3% tax. The semi-kit will not be available after September 30, 1980. No other separate parts or different combinations are available.

short leads to pin 2 of IC3 and the LED anodes. A note about the layout is in order. The "circles" (the unbroken trace from pin 2 that completely encircles the three pads connected to pin 3) around pins 3 and 5 of IC2 are a "guard;" they reduce leakage from these inputs through any contamination of the PC board on humid days. It is still wise to clean these areas with flux remover after assembly. If you are building without a PC board, D7, C1, R14 and IC2 pin 3 should all be soldered together in mid-air, away from any breadboard surface.

Construction with a PC board (Figs. 3 and 4) is straightforward. Load the resistors first, then the trimmers, diodes, LED's, capacitors and IC's. Because of the large number of polarity sensitive devices (almost everything but the resistors), extreme care must be exercised


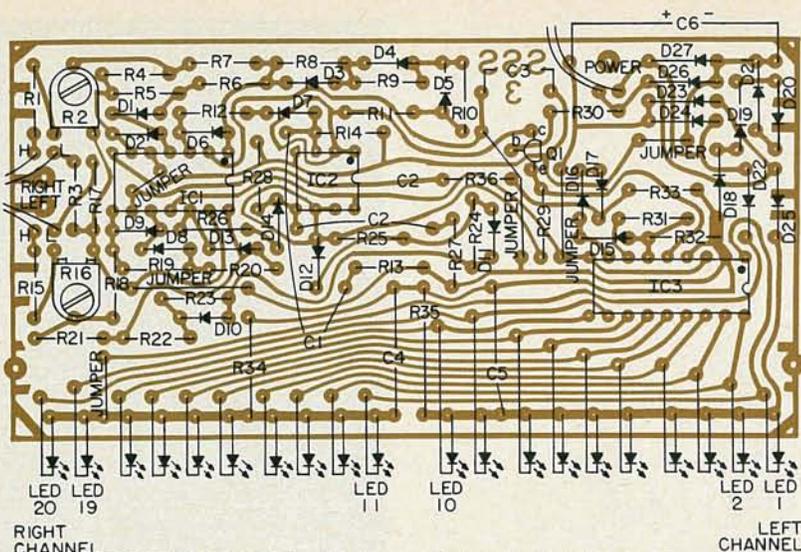


FIG. 4—COMPONENT PLACEMENT guide. Be sure that you include the six jumpers that must be installed.

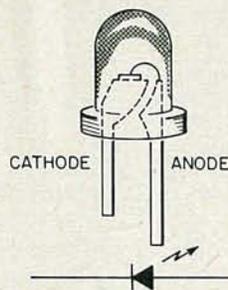

THE CATHODE IS THE SHORTER LEAD, IT IS THE BASE UPON WHICH THE LED CHIP SITS. THERE MAY BE A COLORED DOT NEXT TO THE LEAD, OR AN ABERRATION IN THE CASE DIAMETER.

FIG. 5—OUTLINE of a typical T-1 size LED shows how the diode is polarized.

when mounting components. The LED's are particularly easy to reverse, see Fig. 5 for polarity clues.

The LED's should be mounted as close as possible to flush with the PC board's edge for a uniform appearance. Some LED's might not have long enough leads for the holes on LED 7-10, in which case another lead can be soldered into the board and then onto the LED lead that was not long enough. Leads of all compo-

TABLE 1

Number of LED's lit	Right	Input Left
10	0 dB	0 dB
9	-2.22	-2.15
8	-4.90	-4.78
7	-7.87	-7.53
6	-10.96	-10.46
5	-14.16	-13.52
4	-17.44	-16.67
3	-21.03	-19.84
2	-24.62	-23.32
1	-28.28	-26.61

Frequency Response

Left: 0-20 kHz @ -.75dB
Right: 0-20 kHz @ -.73dB

Pulse Response

Both channels with 2 dB in 40μs.

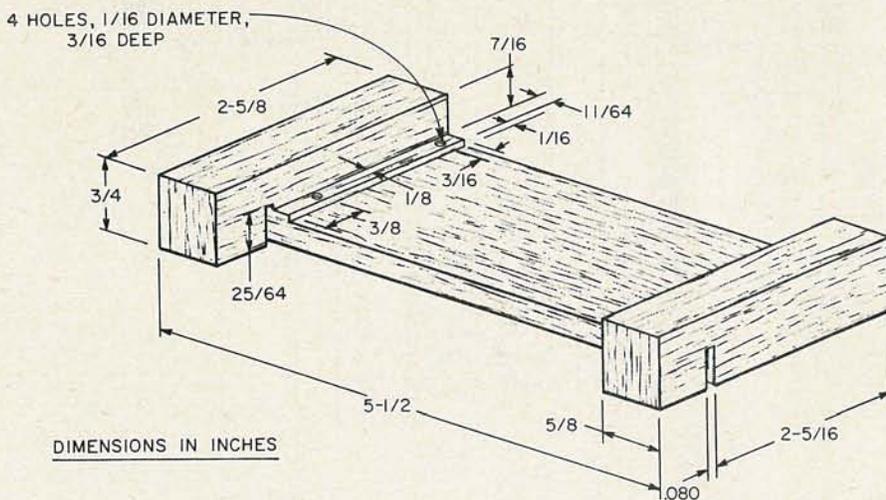


FIG. 6—THE CASE is cut out of a single piece of 3/4-inch walnut or similar hardwood. Work can be done with a table or radial-arm bench saw.

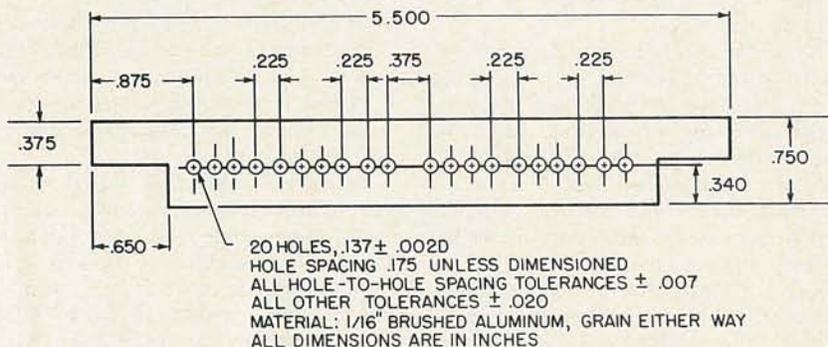


FIG. 7—THE FRONT PANEL is formed from a sheet of 1/16-inch brushed aluminum.

nents should be cut very short after soldering because of the small clearance below the board. The construction of the walnut case and brushed aluminum as shown in Figs. 6 and 7, respectively.

Use No. 24 speaker wire for connections to the right and left channels and power transformer. Pass the wires through the holes in the PC board from the foil side and knot them on the component side. The knot will serve as a strain relief. Then solder the leads into the PC Board. The polarity is very important on

the speaker connections; use the copper-colored side for low (L) and be sure to connect it to the ground or low side of the speaker terminals. A polarity error could damage R3 and R17 and the PC board.

Should you wish to use the PLM in a low-level circuit (such as at the tape monitor jacks) instead of at the speaker terminals, substitute a jumper for R1 and R15, and lift the ground pins of R3 and R16 off the board.

Slip the PC board into the case, screw it into position, and you are ready to go.


Calibration

Table 1 shows the performance of the calibrated prototype PLM. Your instrument can be calibrated in either of two ways when used with a solid-state amplifier. To use the PLM to monitor calibrated peak power, an oscillator and an

accurate AC meter are required for calibration. Disconnect your speakers and drive your power amplifier with the oscillator at 1 kHz. Adjust the oscillator level until the amplifier output voltage is V_{out} (RMS) equals $\sqrt{P \times 8}$ where P is the power level in continuous watts desired for the maximum indication on the PLM and 8 is the load impedance in ohms. For example ($V_{out} = 28.3$ volts for $P = 100$ watts, 20 volts for $P = 50$ watts, etc.). Connect the PLM inputs to the amplifier

continued on page 81

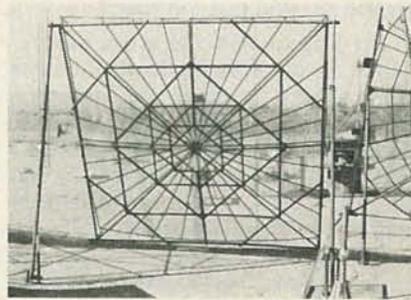LOW COST BACKYARD SATELLITE TV EARTH STATION



TEN FOOT SWAN SPHERICAL is almost opaque although aluminum screen mesh reflector surface is in place. Note Swan's use of squares and spokes to create sandwich layers that rigidly support antenna and reflective surface. Antenna tilt is handled by telescopic rear support rods with lower-ground-rip on hinges.

Now you can build your own Satellite TV Earth Station in your own backyard for less than \$999. This month we'll take a look at antenna design and how a spherical antenna can be built and erected.

ROBERT B. COOPER, JR.

IN THE AUGUST, SEPTEMBER AND OCTOBER 1979 issues of **Radio-Electronics**, we discussed the evolution of the geostationary satellite service for North America and described the basics of its operation. In the January issue we looked at the hardware in the receive portion of the system and discussed the various approaches to hardware design. We are now ready, with this foundation, to begin the task of designing your first satellite television earth receiving terminal.

Design versus cost

If money is no object, you probably are more apt to buy a private satellite terminal than to build one (or portions of one). A list, current through the preparation of this article, of firms specializing on a national or regional basis in the sale of complete TVRO receiving systems (either 'turn-key installed' or on a hardware piece by piece basis) appears in Table 1. The bottom line is that you can purchase a first-rate commercial grade terminal for around \$5,000 in hardware costs (and install it yourself) or have the job done for you with every wire in place and every nut and bolt secured for less than \$10,000.

By building the terminal yourself, you are able to look carefully at the many design variations available and thus select the various module and sub-assembly approaches that best

suit your own needs and talents. And in fact, because there are so many excellent designs around, we have already engaged in a bit of this selection process for you. We will lead you step-by-step through the various choices so that you will wind up with a complete terminal that best fits your needs.

Our approach is not to follow any single design philosophy. The *Howard Terminal* system, widely copied and very good in performance, may be a bit on the complicated side for a non-experienced builder. The *Coleman*

Terminal, originally largely assembled from surplus (Bell-system discarded) microwave equipment, is in turn perhaps too much of a hit-and-miss proposition since the builder must locate many suddenly hard-to-find second hand microwave pieces to make it all play.

The antenna portion is a similar case in point. Six months ago you had three choices; *locate* a surplus or used parabola, *buy* a new parabola, or, *build* a parabola. Many hundreds of people were turned onto satellite TV and then subsequently turned off because they couldn't locate a surplus parabola, didn't have the spare cash to purchase a new parabola, and felt unqualified to construct a homebrew one. Now, with the passage of time, a really low-cost, high-performance *non-parabolic* antenna has made its appearance, we shall shortly see.

Our design philosophy here will be to simply borrow the best technology that exists at this time from several different sources. We'll make you this promise. Over the next few issues of **Radio-Electronics**, you'll learn how to build your own complete terminal, including antenna, an ultra-low noise GaAs-FET LNA, and a twenty-four-channel frequency-agile receiver that ends up at VHF channel 3, 4 or 5 with a modulated NTSC RF output for under \$1,000. You read right ... the whole,

TABLE 1

Suppliers currently offering turn-key-installed home satellite receiving terminals and those who also offer hardware for do-it-yourself installations (*):

1. **Channel One, Inc.**, 68 Avalon, Newton, MA 02168
2. **HOMESAT, Inc.**, 3845 Pleasantdale Rd., Atlanta, GA 30340 (*)
3. **Gardiner Communications Corp.**, 1980 S. Post Oak Rd., Houston, TX 77056 (*)
4. **Microdyne-AFC**, 627 Lofstrand Lane, Rockville, MD 20850 (*)
5. **Satellite Television Systems**, Box 11249, Reno, NV 89510
6. **USTC**, P.O. Drawer 'S', Afton, OK 74331
7. **Spacecoast Research**, Dept. B, Box 442, Altamonte Springs, FL 32701

complete terminal, including antenna, for under \$1,000.

Where do you put the gain?

There is passive and active gain required in the system. In the antenna portion (passive gain) the minimum gain required is a function of where your location falls on the satellite's EIRP pattern (see the September and October 1979 issues for a complete explanation). For discussion, we'll say you need at least 40 dB of passive gain in the system. That's a ten-foot minimum reflector surface any way you cut it. However, a 12-foot surface is even more desirable.

The decision on how much gain to design into the active portion (i.e., the LNA and the receiver) is more difficult to make. That's because we need signal gain for two reasons:

1. To amplify the 4 GHz signal voltage to a level where the demodulator can recover video (and audio) from the satellite signal, and.
2. To overcome (or override) the receiving system noise temperature.

Ideally, system noise temperature is set entirely by the low-noise capabilities of the first LNA stage(s). In the real world, the noise factor for the system is typically set by this *plus* the internal noise figure of the receiver stages. There are two types of 'noise' to be considered in the receiving system. Every amplifier stage (even a video amplifier) has a noise factor. However, when computing noise figure, it is often convenient to look at any device in the receiver that has 'loss' as a noise source as well. In this regard, a mixer stage (i.e., a stage that converts one incoming frequency to another outgoing frequency) has loss and therefore it contributes 'noise' to the overall system.

In modern receivers there are two approaches to getting the 4-GHz satellite input signal down to a low enough frequency where the modulation contained on the carrier can be demodulated to baseband. A single conversion receiver (i.e., the Coleman approach) takes you from 4 GHz to an IF of 70 MHz in a single conversion (or mixing) step. A double-conversion receiver gets you to 70 MHz from 4 GHz in two steps; the first typically takes you down into the 1.2-GHz region (although the selection of a high IF is entirely up to the receiver designer and could be any place from 500 MHz to 2,000 MHz) while the second mixes on down to the pretty much standard 70-MHz region.

The design approach we are going to follow here is the single-conversion option. However, this is offered with the understanding that in some ways the performance of a double-conversion receiver is superior to the single-con-

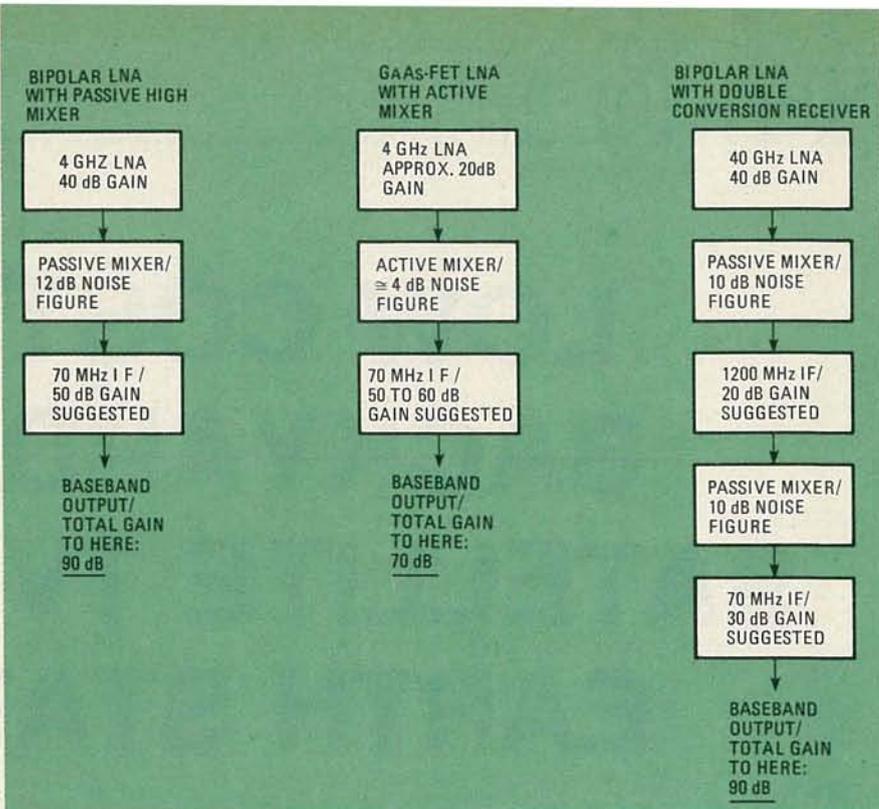


FIG. 1—GAIN REQUIREMENTS for three receiver approaches. Single-conversion receiver with bipolar LNA and passive mixer is shown in a. Single-conversion receiver with GaAs FET LNA and GaAs FET active mixer is shown in b. Double-conversion receiver with a bipolar LNA is shown in c.

version design set forth. In a double-conversion receiver, image rejection, stability and perhaps even selectivity can be better than in a single-conversion design. But, double-conversion techniques are more costly. They require that you have access to test equipment that you probably do not have available (adjusting and aligning a 1.2 GHz high IF does require some equipment not commonly available); and for home use, the trade offs seem to favor the single-conversion approach.

At the risk of oversimplifying the rationale for choosing a single-conversion approach, see Figure 1. Here we see that double conversion has a price tag attached to its 'perhaps' superior performance; you need more total system gain in order to make the double-conversion system perform properly. And gain not only costs money in parts and time, it also increases the complexity of the receiver.

Note in Fig. 1 that we are looking at:

1. A single-conversion receiver using a bipolar LNA and a totally passive mixer (left hand side); the gain required is 90 dB.
2. A double-conversion receiver using a bipolar LNA; the gain required is 90 dB (minimum).
3. A GaAs-FET LNA front end followed by a GaAs-FET active mixer that single-converts down to the 70 MHz IF; the gain required is 70 dB.

In all fairness, one could design a double-conversion receiver with an active GaAs-FET high mixer and this would in turn reduce the total gain re-

quirements of the system since our 40 dB of LNA gain is largely predicted upon the noise-factor contribution of that first mixer stage (the one that gets us away from 4 GHz). However nobody has yet done this and as we are sticking with proven designs at this point the comparison of gain requirements remains valid for now.

What does all of this mean? Simply this. If you wish the system-noise temperature to be determined by the first LNA stage(s), and we do, we have to build enough total gain into the system at 4 GHz to insure that the noise contribution of that first mixer is overridden by the LNA stage(s) in front of it. By replacing the passive mixer (the mixer that gets us away from 4 GHz down to a lower IF) with an active mixer, we shift the noise contribution (i.e., mixing loss) of the first mixer out of the loss column and replace it with a gain or in the worse case a unity-gain device that makes no *significant* contribution to the system-noise factor. So where we previously required gobs of gain at 4 GHz to overcome the noise factor or mixing loss of the high (or only) mixer stage, we now require much more modest amounts of gain to establish our LNA first-stage noise figure as the primary noise factor in our electronic receiving system.

Electronic gain is least expensive to come by at the lowest frequency to be used in the RF portion (the 70 MHz IF) but unfortunately we cannot place all of the gain here. Some gain must go at 4 GHz as well. In Fig. 2 we see two options open to us.

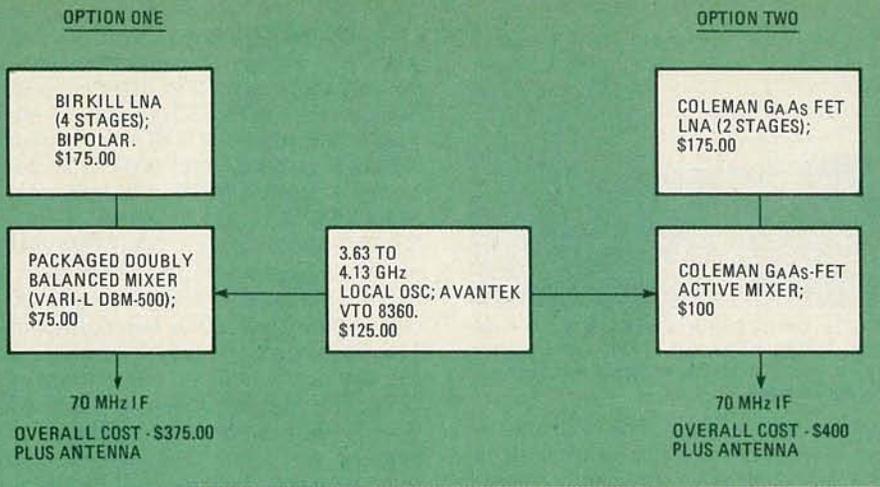


FIG. 2—TWO DESIGN APPROACHES to receiving satellite broadcasts. The Birkill approach is shown in option 1 while the Coleman approach is shown in option 2.

1. As the balance of this article installment shall show, the most cost-effective approach to the antenna today is the *Swan Spherical TVRO* antenna. If you are not a particularly sharp trader or buyer you will still be hard pressed in most sections of the U.S.A. to spend more than \$300 building this antenna.
2. In option one (Fig. 2) we could build a four-stage bipolar LNA (the so-called Birkill HXTR series LNA named after its developer Steve Birkill), follow this with a state-of-the-art doubly-balanced (passive) mixer such as the VARI-L DBM 500 4 GHz to 70 MHz (IF) package, and end up at 70 MHz with a total cost to that point of \$675 including the antenna.
3. In option two (Fig. 2) we can build a two-stage Coleman GaAs-FET LNA and follow this with a single-stage Coleman GaAs-FET active mixer, again ending up at a 70 MHz IF for a total material cost of \$700 including the antenna.

This would seem to suggest that the two approaches in getting 4 GHz energy out of the air and down to a manageable IF such as 70 MHz are very similar in cost. The truth is that the option-one approach has probably just about come to a resting place in costs (for the next year or so) while the GaAs-FET-approach is still largely dependent upon the \$80 to \$100 price tags on the GaAs-FET's themselves. With GaAs-FET prices starting to tumble, the cost of this approach may well be down another \$100 or so before spring. That's one reason to seriously consider this approach. Another more compelling reason is that this approach uses far fewer devices overall; and as those Murphy Law believers know well, the more stuff you cram into a box, the more apt something is to go wrong when you can least afford the time or expense to fix it. Note that in both approaches we are using a newly avail-

able Avantek VTO 8360 oscillator module to provide the local-oscillator drive to our chosen mixer. We'll look more closely at the VTO 8360 in the next part of this series of articles.

Finally, in Fig. 3, we see how we are going to process the 70 MHz IF signal and what it is going to cost us. We have some gain stages at 70 MHz, a demodulator to extract the video modulation from the 70 MHz IF signal along with a few relatively simple baseband processing circuits, a demodulator to create audio from our 6.8 (or 6.2) MHz aural subcarrier, a VHF modulator to convert our baseband video and audio back to a NTSC compatible VHF TV channel (such as channel 3, 4 or 5) and a power-supply section which will provide operating voltages for the system. The total system cost (if you want to start budgeting your pennies now) is as follows:

1. Swan Spherical TVRO Antenna; \$300 (or less)
2. 4 GHz front end to 70 MHz IF segment; \$375 to \$400
3. 70 MHz IF, baseband processing and VHF TV channel modulator with power supply; \$250.

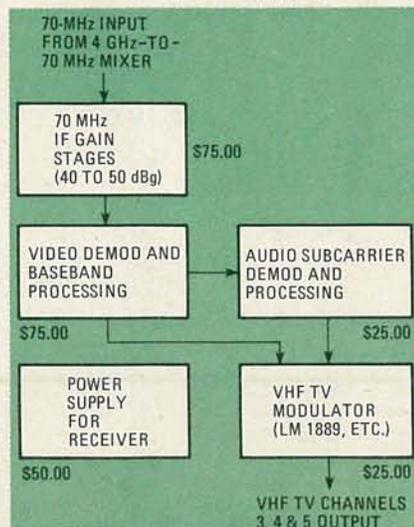


FIG. 3—METHOD AND COSTS of converting the 70-MHz IF to a VHF RF signal suitable for connecting to the antenna terminals of a TV receiver.

That brings us sufficiently in under \$1,000 to allow you to indulge in some packaging of the system following a card cage approach if you wish and still have a little change left over for unexpected expenses.

Swan spherical TVRO antenna

There are several excellent reasons why the Swan TVRO antenna design is the best and most logical choice for the home builder:

1. **Materials**—Everything called for can be procured locally. Steel or aluminum pipe, tubing (round or square stock) plus aluminum window screening, and common hardware such as machine bolts, are all that is required for the reflector system. The feed-antenna is constructed from galvanized sheet metal.
2. **Cost**—\$300 Give or take very little. Although, if you are a good shopper in metal yards you might shave as much as \$100 from the total cost.
3. **Complexity**—Far less complex to create the 'spherical surface' design than to create a comparable parabolic surface. The principle is easy to grasp and uncomplicated to duplicate.

These factors alone should make the antenna very appealing. However there is a golden bonus with the spherical sections; the antenna is capable of 'looking at' many satellites at the same time. See Fig. 4.

The spherical antenna has such a gentle curve to its surface that it can "see" a 40 degree wide portion (or span) of the orbit belt effectively. The antenna is fixed, permanently, on the ground with the center pointed in a predetermined direction. We'll see how that works shortly. Every geostationary point-source in front of the antenna has a focus point out in front of the reflector surface. But this focus point changes for different angles of arrival. A satellite located directly on boresight will have its focal point directly in front of the center of the Spherical surface while a satellite west of the boresight point will focus slightly east of the center point. Conversely, satellites east of the boresight focus slightly west of the center point.

With this geometry, one moves the location of the focal- or feedpoint-antenna (left and right along a line parallel to the reflector surface) to switch from one satellite to another satellite. If you can leave the reflector stationary and move only the focal-point (or pickup) antenna, could you not actually install two or more pickup antennas so as to simultaneously receive two or more satellites? The answer is yes; something that cannot be done with a normal parabolic antenna.

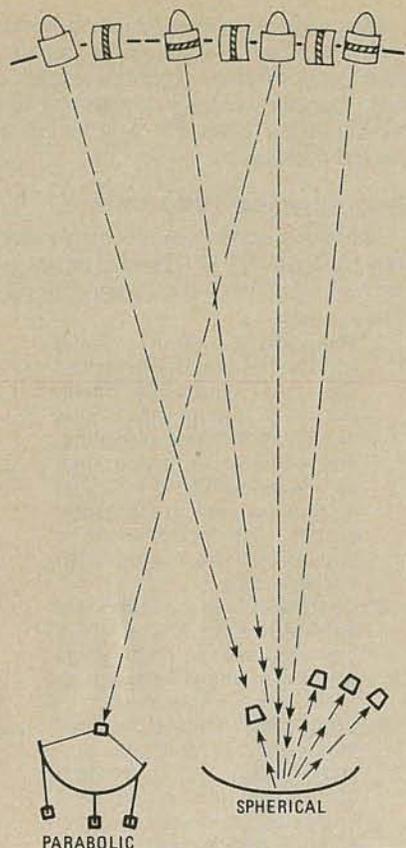


FIG. 4—PARABOLIC VERSUS SPHERICAL antennas. Normal parabolic dish antenna focuses all incoming energy onto a single focus point and as a result receives only one satellite at a time. To receive a different satellite the parabolic antenna must be redirected. The less radical curvature of a spherical antenna permits simultaneous reception of numerous satellites spread over up to 40 degrees of sky arc. Different satellites within the 40-degree arc can be received by moving the focus-point antenna or multiple satellites can be simultaneously received by using multiple focus point antennas.

How does it work?

Both the parabolic and the spherical reflector surfaces work on the same principle. The reflector surface is curved, in both dimensions. A 'cup' is formed and the center of the cup on a parabolic is directly in line with the satellite. All of the energy that is intercepted by the reflector surface is redirected towards a central focus-point. In a good efficiency parabolic antenna, approximately 55% of the total energy intercepted by the reflector surface ends up within the feed- or focal-point antenna.

But, the curve of the spherical antenna is very shallow; it is curved (or indented) sufficiently to cause the energy to focus but not so curved as to cause the RF energy to only focus when the reflector's center and the satellite are in-line together. In Fig. 4, we have a slightly exaggerated illustration of the primary difference between the parabolic (on the left) and the spherical reflector surfaces. The parabolic, because of its boresight requirement, 'sees' only a single satellite (or



FIG. 5—THREE SWAN SPHERICALS at the Bisbee, Arizona test range of Oliver Swan. From left to right, 14-footer, 10-footer and huge 19-footer on right.

spot in the sky) at a time. The spherical sees every satellite location along the orbit belt over a region ± 20 degrees from boresight (the center of the reflector straight ahead). Actually, the spherical surface can 'see' farther than that but the focal-point antenna has difficulty recovering wavefront energy offset from the boresight heading by more than 20 degrees. Look closely at Fig. 4; several separate feed-point antennas (the squared-off cups) are in place, each receiving energy from a separate satellite along the belt. Figure 5 shows three spherical antennas.

Aiming the antenna

If the spherical can see a 40-degree portion of the orbit belt, how do you decide where to center or 'boresight' the reflector surface? Most logically, you want the antenna to look (effectively) at as many satellites as possible. If one of those satellites is to be RCA's SATCOM FI (located now at 136 degrees west), it follows that since all other U.S. and Canadian satellites are east of that point, the 40-degree arc taken in by the spherical shall have as its most western point 136 degrees. That says that the boresight or center shall be 20 degrees less than 136 degrees

(136-20) or 116 degrees. And this suggests your useful view will extend from 96 degrees west to 136 degrees west. Which takes in WESTAR I at 99 degrees, the three ANIKs (of which ANIK-B at 109 degrees is the most important), SATCOM FI at 119 degrees, WESTAR II at 123.5 degrees, COMSTAR I at 128 degrees, SATCOM FIII at 132 degrees and FI at 136 degrees. Since you have nothing between 96 (the eastern end when boresighted at 116 degrees) and 99 degrees, and FI at 136 degrees contains a fair amount of (cable TV related) video, it might be wise to shift the boresight a couple of degrees west to say 118 degrees so as to be sure that the important FI bird is well within the visible orbit belt for the antenna.

How do you do this? Drive a stake in the ground representing where you would like the center of the reflector to be. Use a surveyor's transit or quality compass and find *true* north. That's true north, *not* magnetic north; you'll have to correct for the difference in your area. The local airport control tower can tell you what your correction factor is. Drive a second stake so that the first one and the second one make a corrected-for-magnetic-north line that runs north and south.

Now take a transit or quality protractor and determine from your location a point in the sky that is over the equator 118 degrees west of Greenwich. Drive a third stake in line with the first stake and the line between stake 1 and 3 will be your boresight line. Left, or east (for northern hemisphere readers) 20 degrees and right (west) 20 degrees will be the extent of your orbit arc view with the Swan spherical antenna.

Now to create the spherical reflector surface. The photos here show how Oliver Swan, who developed the an-

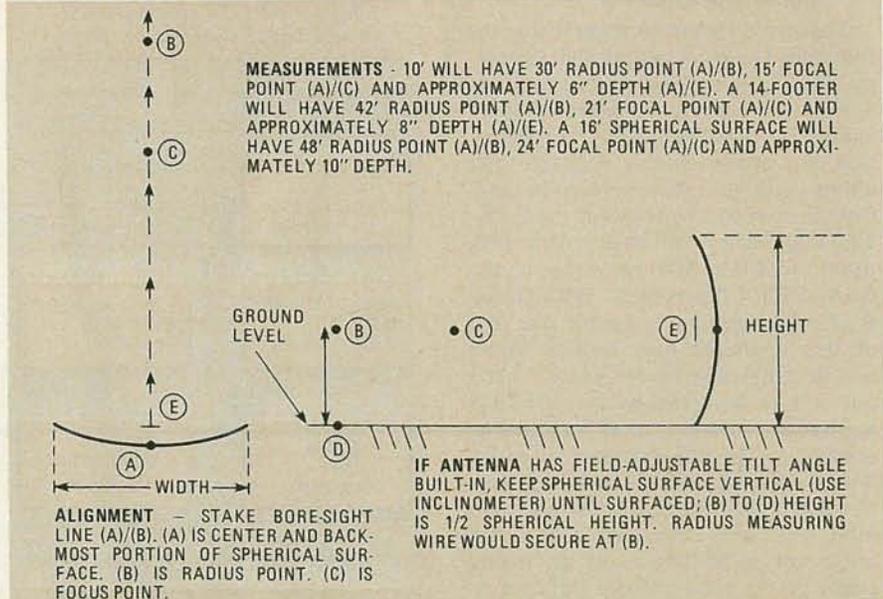


FIG. 6—DETERMINING RADIUS point and focal point of the spherical reflector surface. The spherical reflector surface is as high as it is wide.

tenna, has assembled them in the past. A detailed construction manual is available but an alert person can quickly see what is involved:

1. A ten-foot spherical antenna will have the gain of a 12-foot 55%-efficient parabolic antenna. A 14-foot spherical will have the gain of a 16-foot parabolic. A 16-foot spherical will operate like an 18-foot parabolic. (The height of the spherical surface is the same as the width. Therefore, when we speak of a 12-foot spherical surface, the surface is actually 12 feet high by 12 feet wide.)
2. All initial ground-staking measurements are made with three reference points; the center of the reflector-surface

point (point A in Fig. 6), the radius point (point B in Fig. 6) and ultimately the focal point (point C in Fig. 6). The radius-point distance is three times the desired width or aperture of the spherical; a 30-foot radius for a 10-foot reflector surface. The focal point (which will become important after the reflector is completed) is 1.5 times the aperture (or 1/2 the radius point) and this is where your feed-horn pickup antenna will mount.

Having established the boresight line and the radius measurement point, create a system to measure within 1/16 of an inch from the radius point to any point on the reflector surface. The radius-point tie-down for the measur-

ADDITIONAL SATELLITE DATA

Satellite television enthusiasts interested in learning more about the mechanics of satellite TV reception, and the wide variety of hardware and programming options available may find one or more of interest:

1. **Satellite Study Package**—Designed to gently lead you into the world of geostationary satellite communications; includes 72-page handbook that explains in lay terms the complete satellite TV story, shows how the system works, what services are available, lists dozens of sources for hardware and equipment. Plus includes 22 x 35-inch four-color two-sided wall chart depicting all 30-plus TV carrying geostationary satellites, what each carries and how each operates. Order "Satellite Study Package" for \$15 (first class mail shipment) in U.S. and Canada, \$20 elsewhere (in U.S. funds) from: Satellite Television Technology, P.O. Box 2476, Napa, CA 94558.
2. **Satellite Terminal Construction Manuals**—Three separate manuals designed to help you build your own TVRO terminal. *Swan Spherical TVRO Antenna* manual completely describes the spherical TVRO antenna system with elaborate photos and drawings. *Howard Terminal* manual describes complete bipolar LNA system plus 24-channel frequency agile (tuneable) receiver using off the shelf parts and state-of-the-art technology. Very high quality receiver that can be duplicated (with bipolar LNA) for well under \$1,000 in parts. *Coleman TD-2* manual describes starting off with surplus electronic equipment and building complete terminal for approximately \$500; but, also includes Robert

Coleman-designed GaAs-FET LNA stages, active GaAs-FET mixer and Avantek tuneable LO package. Manuals are priced at \$30, each in U.S. and Canada, \$35 each elsewhere (U.S. funds); or order all three manuals for package price of \$80 from: Satellite Television Technology, P.O. Box G, Arcadia, OK 73007.

3. **Satellite Seminars**—A series of three-day seminars held periodically throughout the year at various U.S. locations; current *Satellite Private Terminal Seminar* (SPTS) is being held February 5, 6 and 7 in Miami, Florida. Conducted as a teaching seminar with course instructors, course guide books, manuals included, plus exhibits from satellite TV hardware manufacturers. Sessions are evenly divided between the technology of building low-cost terminals and business sessions designed to help people enter the field of marketing private terminals to homeowners. Next session after Miami is scheduled for San Francisco Bay Area of California in June. For information contact: SPTS '80, P.O. Box G, Arcadia, OK 73007 (405-396-2574).
4. **Satellite TV Monthly Publication**—A monthly magazine prepared in a newsletter format; *Coop's Satellite Digest* is edited and published by Bob Cooper. Mailed first class mail, covers the latest changes in satellite programming, satellite operations, and the technical progress of the low-cost receiving terminals. Subscription price is \$50 per year in U.S. and Canada, \$75 (in U.S. funds) elsewhere from: *Coop's Satellite Digest*, P.O. Box G, Arcadia, OK 73007. Sample copy for \$5.00.

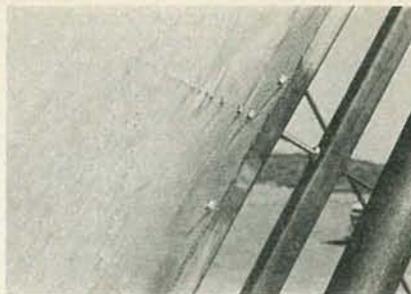


FIG. 7—SPHERICAL SHAPE is created by gently shaping the contour with 10x24 adjusting screws spread from center of reflector surface outward along spokes. Actual tweaking is done with a measuring device extended from radius point stretched taut to antenna surface.

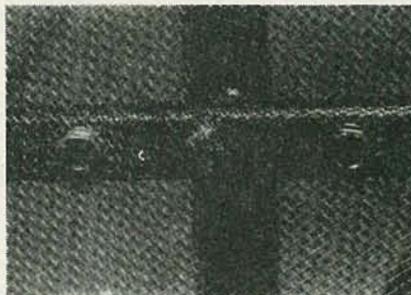


FIG. 8—SURFACE IS COVERED with aluminum window screen and tacked into place at 2- to 3-inch intervals with self-tapping metal screws.

ing wire/tape must be 50% of the height of the spherical reflector surface (if the width is 10 feet, the height will be 10 feet; which places the radius point tie-down 5 feet above ground, at a distance of 3 times the aperture of the antenna out along the boresight line).

To create the spherical curvature the framework for the reflector surface needs to be adjustable so that you can pull in the surface area to the 1/16-inch accuracy required using the radius point as a measurement tie-down. Swan's approach is shown here photographically; 2- and 4-inch 10:24 machine screws are simply adjustable jack screws that allow the outermost square tubing pieces to flex slightly to achieve the required curvature. See Fig. 7.

Surfacing of the spherical is handled with common aluminum window screening. Using 32- to 36-inch-wide material (it must be aluminum or metal to be reflective), the holes should be no more than 1/8th inch across to maximize the reflector surface efficiency and minimize RF signal leakage through the surface. Figure 8 shows how the screen is attached to the frame.

There are a few caveats concerning the construction of your own Swan spherical antenna:

1. Be accurate. The gain of the antenna is directly related to the care put into the surface accuracy. In turn, the surface accuracy (as measured from the radius point such that every point on the reflector's covered surface is within a $\pm 1/16$ th inch accuracy of all other points on the surface) is

a result of the care you put into the supporting structure. The framework must be rigid, capable of taking wind (and, if applicable, ice) loads and advisably, easy to work with.

2. Be careful. No unsupported surface areas on the antenna should be larger than approximately 5 inches by 5 inches. Think of the surface as a gi-

gant patchwork quilt rather than a single reflector surface. Each patch is an area of some dimension and shape supported on three or four sides by tubular steel members on the backside. The total surface is the sum of all of the patches added together and the accuracy of the sum is the final result of how closely the flat

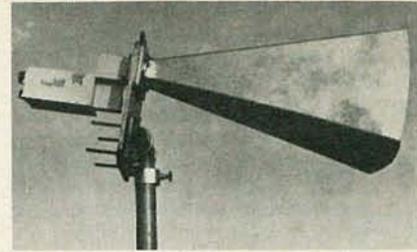


FIG. 11—DEEP-THROAT FEEDHORN (right) with commercial LNA (left). Feedhorn is constructed from galvanized steel, uses carefully welded seams following the pattern shown in Fig. 10. Flange at rear (narrow) end of feedhorn tapers to mate with WR-229 flange on input to LNA.

(i.e. non-curved) surface of each patch is within the $\pm 1/16$ -inch accuracy required. So think out the support structure carefully and design it so that you have no patch areas larger than say 5 inches on a side.

The feed theory

The feedhorn is a very unusual design and there are proprietary rights of value here for the developer Oliver Swan. Suffice to say that the basic spherical antenna shown has phase *advance* (as in lead) while the feedhorn has phase delay. The advance of the reflector surface is self correcting with the delay of the special feedhorn as long as the incoming plane wavefront is within ± 20 degrees of the antenna's boresight. It is this phase relationship which falls apart beyond the 20-degree-off-boresight point, destroying the effectiveness of the antenna system over off-boresight points beyond the 20 degree limits.

Keep in mind that the focus point varies for different azimuth angles of arrival. Remember that a signal from a satellite located dead-on the boresight path will be directly in front and in the middle of the antenna. But, signals from satellites stationed to the left or right of boresight will arrive at a focus point right and left (i.e., reversed) from the center boresight point.

There is also one other factor to be aware of in designing the antenna system; tilt angle. As shown in Fig. 9 the designer can decide just where he wants his signal above ground (i.e., how close to the ground or how high up) by changing the up-and-down angle of the reflector surface. For discussion, a reflector surface straight up and down is said to be perpendicular to the earth. In fact this is how you build and surface it regardless of the ultimate tilt angle that is to be used. After construction, on hinged pieces, the antenna is tilted back to the desired tilt angle for your location. A simple string and plumb-bob can be used to establish a vertical reference line and an inexpen-

continued on page 83

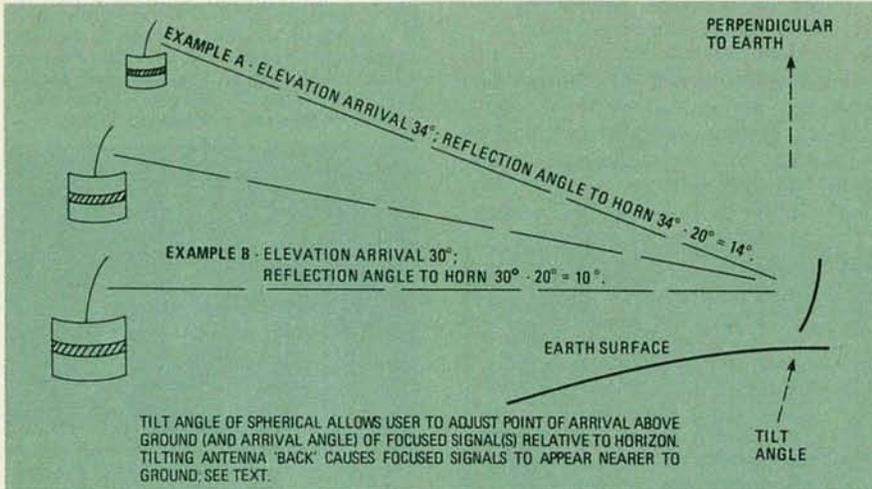


FIG. 9—TILTING THE SPHERICAL reflector surface back permits the user to adjust the angle of the reflected signals with respect to the ground.

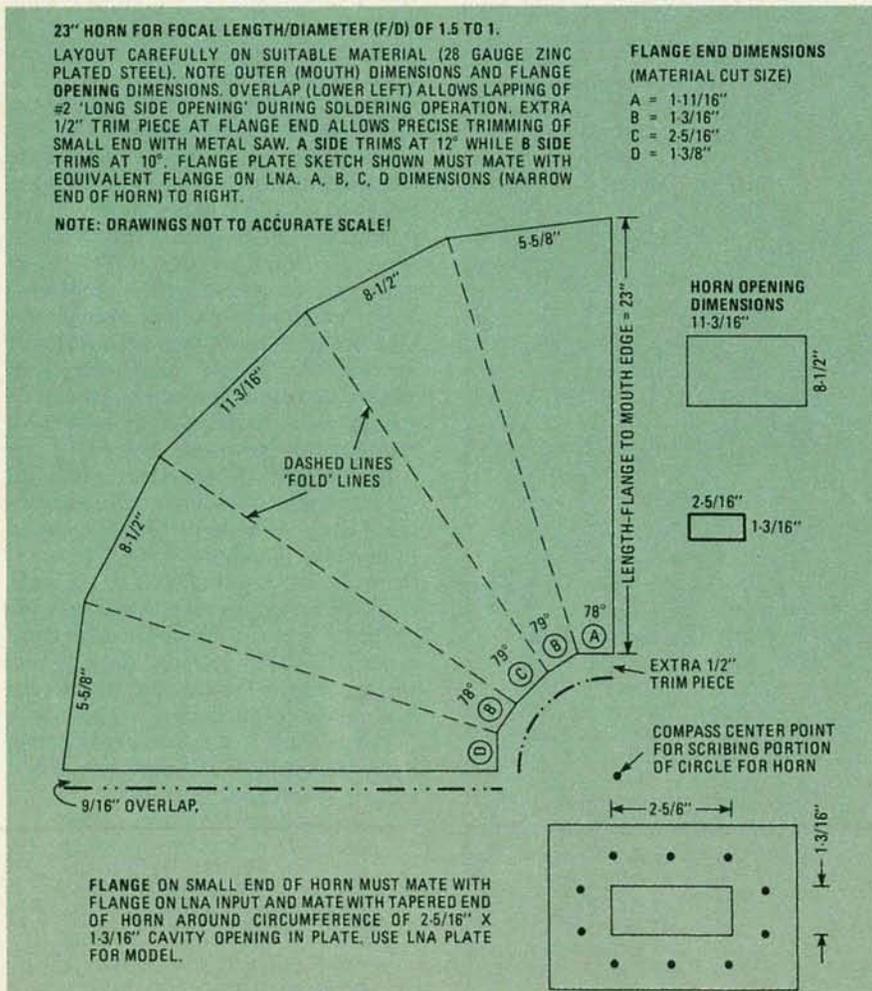


FIG. 10—23-INCH HORN PATTERN shows how to cut and form horn of focal-point antenna out of sheet metal.

DESIGN YOUR OWN ANDROID

Part 2—If you've wished for an intelligent robot to do your chores, you'll be interested in some design problems and their solutions.

MARTIN BRADLEY WEINSTEIN

LAST MONTH WE BEGAN THIS SERIES ON android design with definitions of relevant terms and discussions of physical and mechanical goals. Now, we'll take a look at how we can satisfy the design goals.

Defining the problem of vision

Exactly what can we hope to accomplish by providing our machine with a visual input? For that matter, what should we *want* to accomplish?

We have set collision avoidance as one of our goals. So we might ask that obstacle recognition be assigned to a visual subsystem.

We have to locate both external objects and the position of manipulator arms and hands in three-dimensional space. That certainly is a visual task, and one that calls for binocular parallax vision.

In addition to observing objects as obstacles, there are a given number of objects we will want our machine to be able to recognize and identify. Those include doors, doorknobs, stairways, and power receptacles at the very least.

If we were to deal with even as complex an image as a low-grade video camera yields, we would need enormous amounts of very fast memory and huge chunks of processor time.

Would we be as well off with something as crude as a 64×64 or even 32×32 pixel array?

Figure 3 shows a portrait of the author, adapted from a photograph using high

contrast techniques and mezzo dot inking. The artistry was performed by John Scavnicky, to give credit where it is due. Figure 4 shows the same portrait resolved into a 32×32 array of single-bit (black/white) data.

Is that 1K array fine enough for object recognition? That depends on what you want your machine to be able to do. A 4K array might be better, and we might want to consider more than one bit of video. But you can get the 32×32 array by scanning a CCD or photodiode matrix!



FIG. 3—RESOLUTION is a significant parameter to consider when designing the visual system. The above is a high contrast portrait of the author.

There are other simple digital scanning techniques available, too, which we hope to cover in future articles.

Is one picture worth 1000 bits?

If we wanted our visual system to see any given image exactly, time after time, we could establish a mask within its memory and match every incoming image

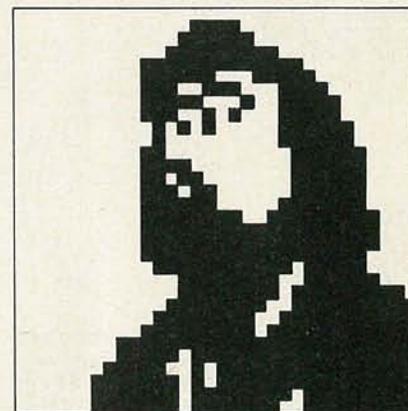


FIG. 4—WHAT THE ANDROID SEES. Above shows the portrait in Fig. 3 resolved into a 32×32 array of single-bit black-and-white data.

until one matched perfectly. That approach might be valid, for example, if we wanted our machine to recognize dollar bills placed in a receiving tray that was always centered at arm's length.

So even with the reduced data requirements of a fairly crude scan, we will want

to include some mechanism—probably in software—for extracting salient features and applying them to the recognition task.

Of great help in this task is a memory scheme called Content-Addressable Memory, or CAM. One company, Semi-onics (41 Tunnel Road, Berkeley, CA 94705) has available a 4K byte static CAM board for Z-80 and 8080 systems called REM, for Recognition Memory. The board itself is \$325, a 4K firmware package of REM routines another \$80.

Content Addressable Memory, as its name implies, is an arrangement of standard memory with a large number of logic gates which permits the memory to be searched according to its contents.

All CAM in a system is searched in parallel. The search can be designed to extract either all data identical to a search cue, or all data in a set corresponding to a subset used as a search cue (for example, from a personnel file, all blonde-haired blue-eyed former employees from California), or the data most closely matching the search cue.

Because the search is conducted in parallel, it is very fast. And the ability to score for closest match makes it particularly useful to pattern recognition tasks.

Depth perception

Let's make two assumptions: first, that our visual information is addressable from the perspective of a defined X-Y matrix; and second, that we can use identical feature extraction software on each of two image sensors.

Then, if we arrange the two electronic "eyes" so that they can rotate separately from the platform they sit on, and the platform can rotate; and if we arrange so that the "cross-eye" angle from perpendicular is kept complementary and equal;

TWO ROTATING CAMERA PLATFORMS, LINKED FOR JOINT MOTION

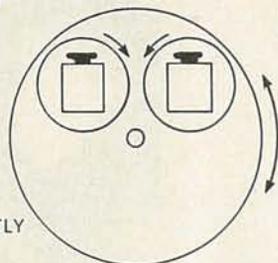


FIG. 5—OVERHEAD VIEW OF SENSOR PLATFORM. Sensor platform rotates while both cameras are mounted on platforms that also rotate.

we can use a simplified version of simple geometry to determine the distance to an object, and the direction, plus the object's height.

Figure 5 shows one possible arrangement of a sensory platform in the android's "head." The left and right camera turntables could be linked by gears or belts, if desired, or electronic means could be employed.

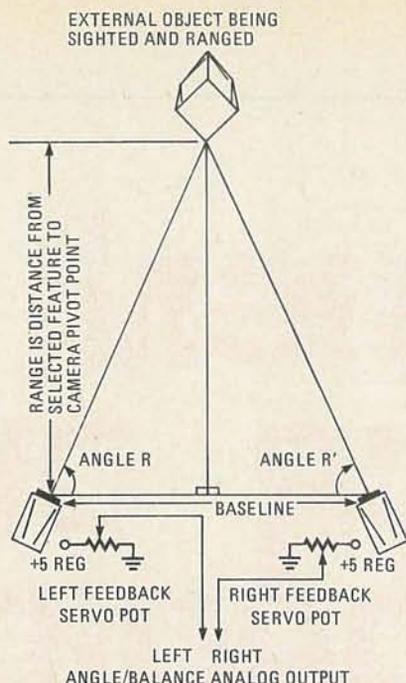


FIG. 6—PARALLAX RANGE MECHANISM can be used to calculate range information.

The servo feedback pots in Figure 6, for example, could provide the necessary inputs to a circuit designed to drive independent motors until equal angles balance the circuit.

The baseline of Figure 6 is the distance between the pivot points of the two cameras. A little trigonometry shows that the distance to the external object being sighted and ranged is equal to half the baseline times the tangent of Angle R, as long as Angle R and Angle R' are equal.

To attain that condition, we can compare the X-Y matrix address of any single extracted feature in the two cameras. When R and R' are equal and the grid addresses are equal, range information is just one more step away.

That last step involves digitizing the servo outputs. For best results, a logarithmic taper pot arranged with its compression highest when Angle R approaches 90° can serve as the servo feedback pot. An 8-bit analog-to-digital converter then addresses a ROM lookup table to give either calculated or actual measured values for range.

Figure 7 shows one possible elevation adjusting platform, permitting our machine to look up about 30°, straight ahead, or down—as steeply as straight

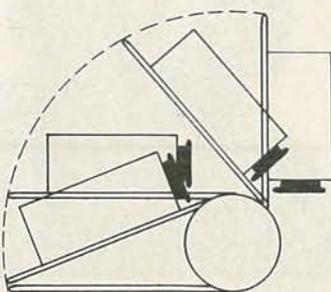


FIG. 7—ELEVATION ADJUSTING PLATFORM can be used to determine object's height above ground.

down, 90°. Again, the digitized output of a potentiometer can be applied to calculate both the object's distance from the machine and its height above ground.

Track drive design

We said earlier that the ability to negotiate a stairway would have to be one of our design criteria, as stairways were a special but common obstacle in our human environment.

Another is doorways. If there is a standard for doorways—a point that appears more and more moot the more you investigate it—it seems to be 30 inches in width. But often, the heel of the open door occupies two inches of that space, so a robot more than about 27 inches wide would be folly.

Still another significant obstacle commonly encountered is the narrow, usually 36-inch, hallway—and especially 90° corners in such hallways.

Those three hazards—stairs, doors, and halls—can help us define the maximum dimensions and geometry for our machine, and especially its drive.

Stairway geometry

We are going to make a marginally dangerous assumption: We will assume that the robot will never encounter a case

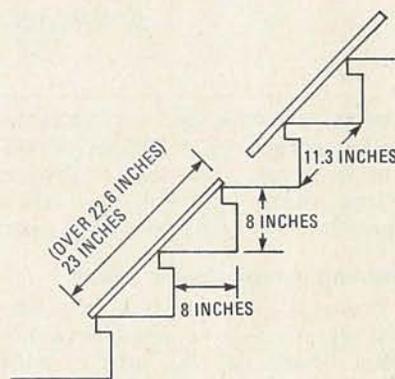


FIG. 8—NEGOTIATING standard 45 degree 8-inch stairway can be difficult.

worse than a "standard" 45° 8-inch step stairway.

Figure 8 shows a model of such a stairway, 8 inches step height (rise) and 8 inches step offset (tread). Note that the offset lip at the top edge of each step does not affect the following calculations.

The linear distance from corner to corner along a climbing diagonal is 8 times the square root of 2, or roughly 11.3 inches. Good design sense requires that the drive contact at least two step corners at any time, which requires a "grounded contact" length of just over twice this distance, or roughly 22.6 inches. So let's set 23–24 inches as the minimum dimension for the base of our vehicle's track.

Next we face the problem of getting the little monster to leave a level surface and climb that initial step. The configuration in Figure 9 shows our approach to the problem.

Here, the first surface to contact the

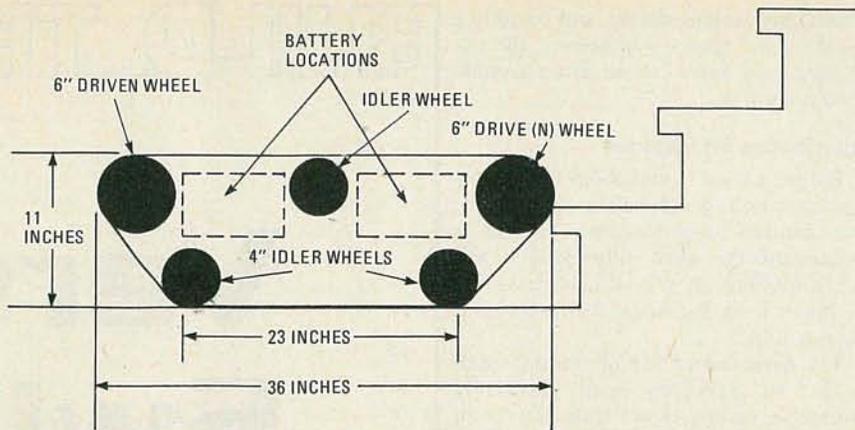


FIG. 9—STAIRWAY PROBLEM might be solved with the above track drive mechanism. The geometry of the mechanism is such to permit the android to climb standard 8-inch stairs.

step corner is the track at roughly the 4 o'clock position on the front drive wheel. The forward motive thrust pushing the vehicle then more or less makes the drive wheel "roll uphill."

The idler wheels are spring tensioned in narrow slots and permit some vertical motion. Notice that on first approach, the track surface approaches the step corner at about a 35° angle. As the front drive (or *driven*, depending on your point of view) wheel climbs, the weight of the vehicle is lifted from the front idler wheel, allowing it to drop to the bottom of its travel slot, with pressure maintained by spring tension. That increases the contact area of track-against-step (especially on a carpeted step), aiding the climb.

For a more natural understanding of the interactions here, buy yourself a small plastic model tank kit, preferably motorized.

The top track dimension (here, 36 inches) results from calculations of the necessary height of the step contact point and the necessary approach angle of the track. Plus a trip down the hall.

Tight corners

The tight corner we talked about earlier, 90° in a 36-inch-wide hallway, is one of the most ticklish situations our vehicle is ever likely to encounter; indeed, it might require the addition of some sort of electronic "curb feelers" to avoid scarring the walls.

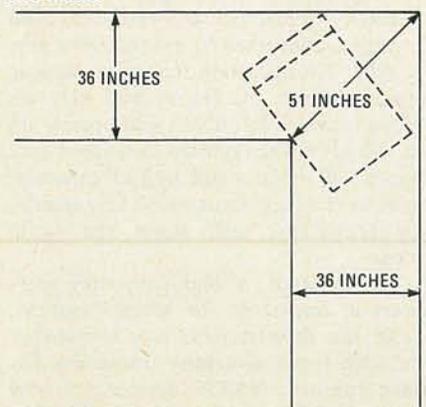


FIG. 10—NEGOTIATING A 90 DEGREE TURN in a narrow hallway is also difficult.

Figure 10 shows the situation in question. It also includes a red herring: the 51-inch diagonal dimension has nothing to do with the available turning circle area. Used as a diameter, it describes a circle whose circumference exists outside the hallway walls at all but four points.

The circle we are interested in exists within those walls, and has a diameter equal to the hallway width, or 36 inches.

The dotted rectangle at the corner shows the most critical part of the turn as vehicles both 36 and 40 inches long (by 27 inches wide) would negotiate it.

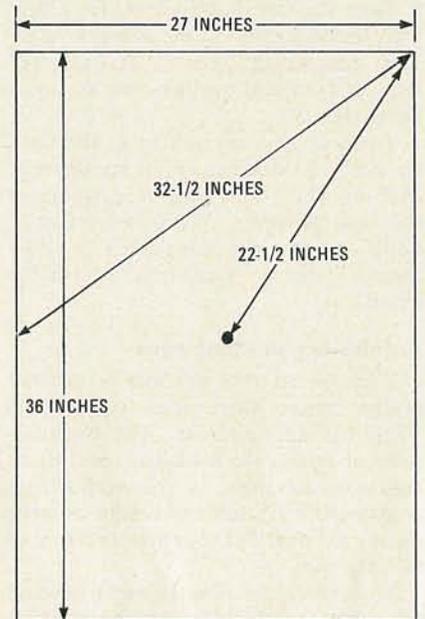


FIG. 11—DIMENSIONS and turning radius of track drive mechanism.

The problem reduces quite nicely to the geometry shown in Figure 11. We must turn the vehicle so that the pivot for the turn is midway along one flank. That yields a turning radius of approximately 32½ inches, a tight enough squeeze in a 36-inch circle.

That *must* be done with the inside track moving more slowly than the outside track. To run it the same speed but in the opposite direction makes the vehicle pivot about its geometric center. And while that is a nice stunt for dancers, and

certain other vehicle tasks, here it would yield a turning diameter of 45 inches. This makes almost any kind of turn an impossible maneuver.

Experimentation in a clear, chalked-off area is urged.

Leaning and trunk rotation

It is good design practice for stability in any vehicle to keep the center of gravity close to the ground. That involves either designing wide, flat configurations—like sports cars—or assigning most of the mass of the vehicle to its lowest quarters.

Unquestionably, the most massive components of our machine are going to be its batteries and charger, its track drive and drive motors, and its supporting framework. Refer back to Fig. 9 to see where the batteries and drive motors might be located within the base of the unit to insure good stability.

One method of adjusting a center of gravity is by adjusting the geometry of the mass. One splendid example of this phenomenon, which you may be experiencing even now, is leaning. The upper body can be made to lean forward or backward to maintain equilibrium as the robot goes up and down stairs.

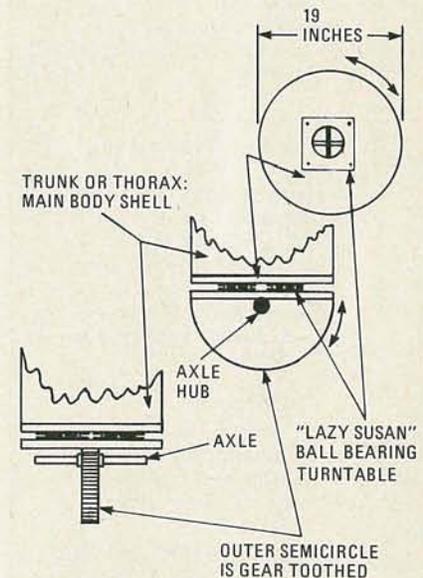


FIG. 12—THE TRUNK OR THORAX of the android should be affixed to the drive mechanism in such a way as to permit both twisting and leaning. The above shows one possible mounting configuration.

Figure 12 illustrates the mechanics that can permit the upper torso of the robot to lean forward or backward while preserving freedom of rotational motion.

The 19-inch shell diameter was arrived at by assuming that manipulator arms on each side could be trimmed to protrude no more than 4 inches from each shoulder, which conserves the 27-inch overall width.

Figure 13 proposes a fishbowl-shaped head to enclose the sensory platform of Fig. 5. Since that area really ought to also enclose a microphone or two, a headlight,

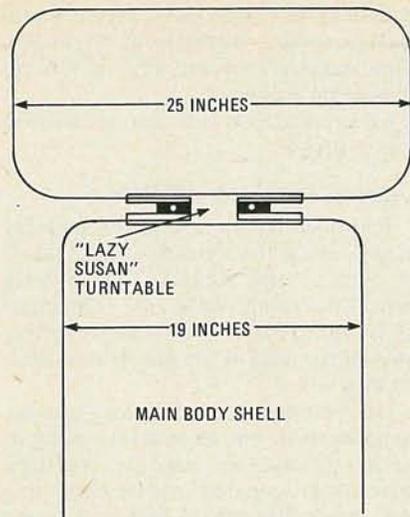


FIG. 13—THE HEAD or sensory platform rests atop the main body shell and rotates independently of the body and of the TV cameras that serves as the robot's eyes.

TABLE II

I. Overseer processor

- A. Receives instructions from humans
 - 1. Voice
 - 2. Keyboard
 - 3. Override (panic)
- B. Responds to alarm conditions
 - 1. Collision
 - 2. Entrapment
 - 3. Low energy
- C. Sets immediate operational goals
 - 1. Responds to instructions
 - 2. Responds to alarm conditions
 - 3. Maps immediate area
 - a. Analyzes visual inputs
 - b. Analyzes contact inputs
 - 4. Learns about new objects
 - a. Learns to recognize by sight
 - b. Learns to recognize by name
 - c. Asks questions, may format answers
 - 5. Searches for and locates known objects, enhances map
 - 6. Learns new operations (e.g., vacuuming rug or pouring a cola).
 - 7. Performs subset of known operations

II. Intelligent peripherals

- A. Visual subsystem
 - 1. Obstacle recognition
 - 2. Free path recognition
 - 3. Object recognition
 - 4. Range calculation
 - 5. Mapping input
- B. Drive subsystem
 - 1. Collision, obstacle avoidance
 - 2. Mapping
 - 3. Navigation
 - 4. Drive motor control
- C. Speech recognition subsystem
- D. Speech synthesis subsystem
- E. Left, right manipulator control subsystem
- F. Future features

a SODAR ranging device, and possibly a speaker, and speech synthesizer, the enclosure may prove to be more trouble than it's worth.

Distributed intelligence

Before a word is said about the following approach to providing intelligence and control to a machine, you must understand that such information is entirely speculative. We, at least, have yet to prove it in hardware. Perhaps you'll beat us to it.

The basic theory behind our approach is that no reasonably small, reasonably affordable computer available now or in the near future is smart enough, or fast enough, to handle all of the information analysis and control systems an android requires without botching the job badly and often.

We resort instead to multiprocessing. Here, relatively inexpensive single-IC microcomputers are used to simplify the overall task by providing preprocessing at each of the I/O (input/output) on-board "peripherals."

(We're planning on the CMOS version of the 8048/8031 family now being introduced by Intersil, who are interested in supporting our one specific effort with a generous amount of hardware and software cooperation.)

Thus the visual subsystem, for example, provides data to the central "overseer" controlling processor at a rate and level of complexity equivalent to, say, a keyboard.

Table II gives an outline of the tasks for each of those centers of intelligence, each of which may also be using more than one processor. We would prefer to build and test the subsystems to prove them out before going into any further detail.

A definitely un-final word

There is no area of robot or android design where there isn't tremendous room for improvement. The contributions of innovative hobbyists can inspire enormous advances in this technology. And there is no detail of design or technology too small for your attention to it to be welcome.

The android we hope to watch develop from the groundwork you see here will be an infant. Your dog will have more intelligence, more agility, and possibly more practical value.

Until, that is, someone suggests some improvement to our design, or some application of it to improve the non-human condition.

Write us. Suggest techniques or hardware. Suggest tasks for robots or androids to perform. Be supportive or critical. Tell us whether or not you're interested in more information on androids and robots. Or have your android write us. The day isn't all that far away.

R-E

BUILD THE Vers Swit

ROBERT FROSTHOLM*


TWO PREVIOUS ARTICLES ON SWITCHING Power Supplies (June and July 1979 issues of **Radio-Electronics**) dealt with the basics of switching regulator theory and presented several typical circuits using IC's for basic DC-to-DC conversion. This article will present a universal regulator that can be programmed with simple jumper wires for step up, step down, or an inverting output. It is much more than the simple DC-to-DC converters discussed earlier. This approach to switching regulator design incorporates all the essential protection and control circuitry needed to maintain high efficiencies and a fully protected system.

The heart of the design is a new Switched Mode Power Supply Control circuit, the Signetics NE5560N. Unlike the simple DC-to-DC circuits on the market, this IC was developed as a "Power Supply System Controller." The following description will bare this out in detail while providing insight into the operation of the regulator.

Figure 1 shows a block diagram of the NE5560. A quick glance tells you it's much more than a DC-to-DC circuit. The oscillator consists of a highly stable sawtooth generator. The frequency is determined by an external resistor and external capacitor connected to ground from pins 7 and 8. The operating frequency range is specified from 50 Hz to 100 kHz although most NE5560N's will operate up to 150-kHz. The regulator described here uses a 20K resistor and .003 μ F capacitor to achieve an approximate 30 kHz oscillator frequency, well above the audio range.

The capability of high-frequency operation is important for several reasons. First, the threshold for new technology for high-speed switching transistors has been reached. VMOS devices are now

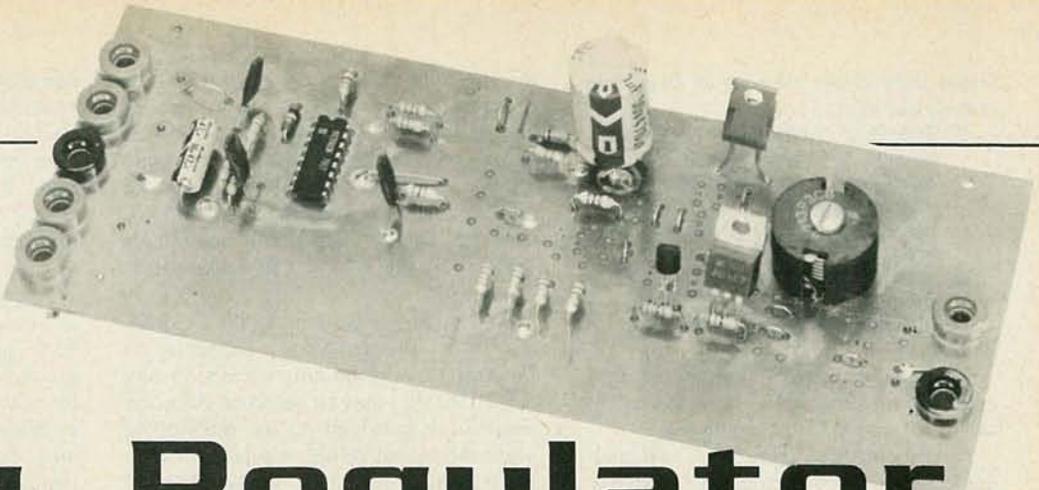*Strategic Marketing Manager, Standard Linear Products, Signetics Corp. Sunnyvale, CA.



atile ching Regulator

The switching-type voltage regulator offers much greater efficiency than conventional regulated supplies. This design lets you invert the output polarity or program the output for step-up or step-down.

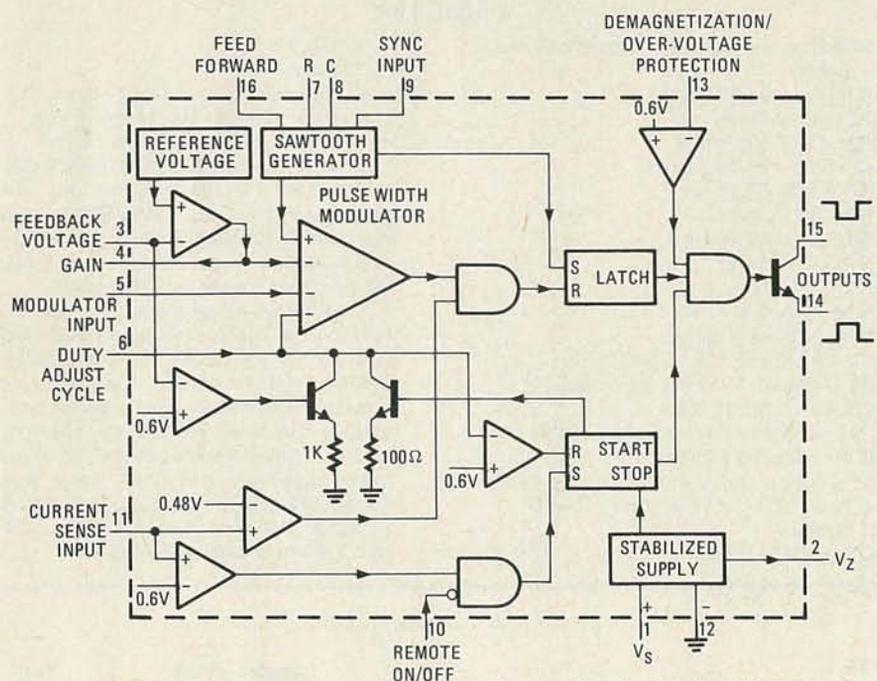


FIG. 1—BLOCK DIAGRAM of the control circuit shows the array of protective circuit features.

commercially available along with fast-recovery diodes making extremely high power switching regulators smaller, lighter, and less expensive than ever before. High-frequency operation also means small energy storage elements i.e. greatly reduced magnetics (transformers and chokes) resulting in further size, weight and cost reductions.

The ability to synchronize the oscillator to an external TTL signal is important in switching power supply design. Although it is not necessarily applicable in this project, the pin is available and brought out on the board for experimentation purposes. The oscillator can be synchronized to a frequency lower than the free-running frequency as determined by the external resistor and capacitor connected to pins 7 and 8. For example, in a video display system it is desirable to sync

the switcher to the horizontal deflection signal to minimize noise and beat signal problems.

There are two basic techniques to vary output pulses to the switching elements. Many DC-to-DC converters use a frequency-modulation technique that is easy to achieve but hard to control. The system described here uses a pulse-width modulation scheme that allows precise cycle-by-cycle control of the output. The duty cycle range of the NE5560 is 0 to 98%.

With pins 5 and 6 not connected and a low feedback voltage on pin 3, the output pulse will have approximately a 98% duty cycle. In switched-mode power supplies, large output duty cycles can cause problems, especially in forward converters (see box) where duty cycles in excess of 50% can cause the magnetics to saturate.

For this reason it is important to be able to control the maximum duty cycle. Applying a DC voltage to pin 6 of the NE5560 controls the duty cycle maximum limit. This relationship is illustrated in Fig. 2.

Establishing a maximum duty cycle is best done with a resistor divider from V_z

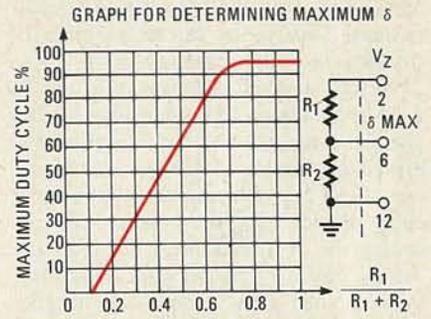


FIG. 2—THE RATIO of R1 to R2 determines the maximum duty-cycle δ of the system.

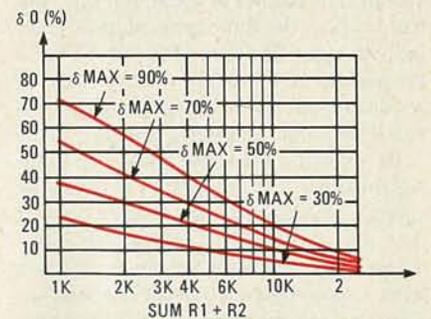


FIG. 3—THE FALLBACK minimum duty-cycle is a function of the original maximum duty-cycle and the total resistance of R1 and R2.

(pin 2) to pin 6 and pin 6 to ground. This technique takes advantage of another pair of resistors internal to the NE5560 that then form a bridge with the two external resistors and biases pin 6 with a stable DC voltage. This configuration allows pin 6 to also be used to set a minimum duty cycle when a loop fault occurs. Resistors R1 and R2 have been selected at 10K. These may be modified to experiment with dif-

ferent duty cycles so long as two basic criteria are kept:

1. The duty cycle must be large enough to insure that at maximum load and minimum input voltage, the resulting feedback voltage to pin 3 must exceed 0.6 volts.
2. It must be small enough to limit the amount of energy to the output stage when a loop-fault occurs.

The relationship of the minimum duty cycle and maximum duty cycle to the values of R1 and R2 is shown in Fig. 3.

Another critical feature of switched-mode power supply design is to be able to control the duty cycle during "power up" conditions—to gradually increase the amount of power to the load until full output is reached. An electrolytic capacitor from pin 6 to ground will provide this function. During "power up" C1 (Fig. 4) is initially discharged. When power is applied C1 begins to charge through R1 and the voltage on pin 6 gradually increases to its final value (determined by R1 and R2).

Capacitor C1 serves another important function; that of protecting the entire system when an over-current condition exists. The output current is monitored by pin 11 on the NE5560. This pin senses a rise in voltage across a sense resistor (R15-R18 in parallel) indicating a rise in current. This feature can be examined in the step-up configuration (Fig. 4).

In actuality four 2.2-ohm resistors are used in parallel in this application so that you can experiment with the over-current protection feature of the IC. With only one of the 2.2-ohm resistors in place, the effect of increasing the load current (reducing the load resistance) increases the voltage on pin 11 greater than .48 but less than .6 volt. This activates an internal comparator that in turn resets an internal latch and shuts off the pulse to the output switch. The feature of cycle-by-cycle control reduces the duty cycle of each pulse individually. The new duty cycle is a function of how quickly the over-current condition can cause a greater than .48-volt drop across the sense resistor.

By reducing the sense resistance (adding the other three 2.2-ohm resistors) the voltage sensed will now exceed .6 volt that activates another comparator internal to the NE5560 which in turn sets a latch that completely inhibits the output. The latch also turns on a transistor whose collector is connected internally to pin 6. This discharges C1. When the voltage on C1 drops below .6 volt, another comparator resets the latch. Capacitor C1 then begins to charge creating the soft-start effect of gradually increasing duty cycles. If the fault condition remains the procedure repeats itself. This is called the "hiccup mode." In major systems it is not advised to let a system oscillate in the hiccup mode for long periods of time.

Use of the remote on/off (pin 10) can

prevent this problem. A simple CMOS counter can be used to sense hiccups by connecting the input to the slow-start capacitor (C1), programming for some number of counts (i.e. 5, 10 etc.) and the output can then be connected to pin 10. This way with a permanent major fault the entire system will be shut down after say five hiccups.

Switching-power supplies use feedback techniques to sense what's happening at the output and internally correct for any deviations that may be detected. An error amplifier is provided on the NE5560 to sense the output voltage sampled through R3 from the divider R4-R5 (see Fig. 4). The gain of the error amplifier is controlled by the feedback resistor R6. Capacitor C3 is for loop compensation. Typical open-loop gain of the error-sense amplifier is 60 dB.

Special protection features not found in any other control circuit include a

completely protected loop. If for some reason the loop opens, an internal current source pulls pin 3 voltage up giving the false impression that the output voltage is high. This information is then delivered to the pulse-width modulator and the duty cycle is reduced to a safe level preventing a runaway condition.

A second safety feature on the loop protects the system in the event the feedback loop somehow gets shorted to ground. In this case an internal comparator senses that the amplifier input (pin 3) is below 0.6 volt. This too reduces the duty cycle by affecting the pulse-width modulator. A shorted loop also results in the soft-start capacitor being discharged through an internal 1K resistor. This short remains as long as the voltage on pin 3 remains below 0.6 volt. This results in a greatly reduced duty cycle (a function of the forced voltage on pin 6) further protecting the switching power supply.

PARTS LIST

Resistors 1/4 watt, 10% unless otherwise noted


- R1, R2—10,000 ohms
- R3—1000 ohms
- R4, R7—3600 ohms
- R5, R12—20,000 ohms
- R6—100,000 ohms
- R8—8200 ohms
- R9, R13—2000 ohms
- R10—180 ohms
- R11—68 ohms
- R14—360,000 ohms
- R15-R18—2.2 ohms
- C1—47 μ F, 16 volts, electrolytic
- C2—470 μ F, 50 volts, electrolytic
- C3-C5—.003 μ F disc
- D1—BYW29-150 (Amperex) or equivalent
- IC1—NE5560N (Signetics)
- L1—0.9 mH inductor (Ferroxcube 2213 PL00-3C8 pot core and 2213 F1D bobbin)
- Q1—BU407 (SGS)

- Q2—2N3638A
- Q3—2N2222A

Miscellaneous—double-sized PC board, 3 feet of No. 18 enameled magnet wire, nylon screw and nut for mounting L1.

Note: A kit of two 2213 PL00-3C8 pot cores (two are required for one enclosed inductor) and a 2213 F1D bobbin is available for \$3.00 including postage and handling, from Elna Ferrite Labs, PO Box 395, Woodstock, NY 12498.

A complete kit of parts (No. SMP-1) to build the power supply as described is available for \$36.50. A boost kit No. SMP-2 includes higher power drive transistors and larger pot core for converting the basic SMP-1 for approximately 3 amperes output; \$13.50. California residents add 6 1/2% sales tax. Order these kits from Advanced Analog Systems PO Box 24, Los Altos, CA 94022. Phone: (408) 377-7148.

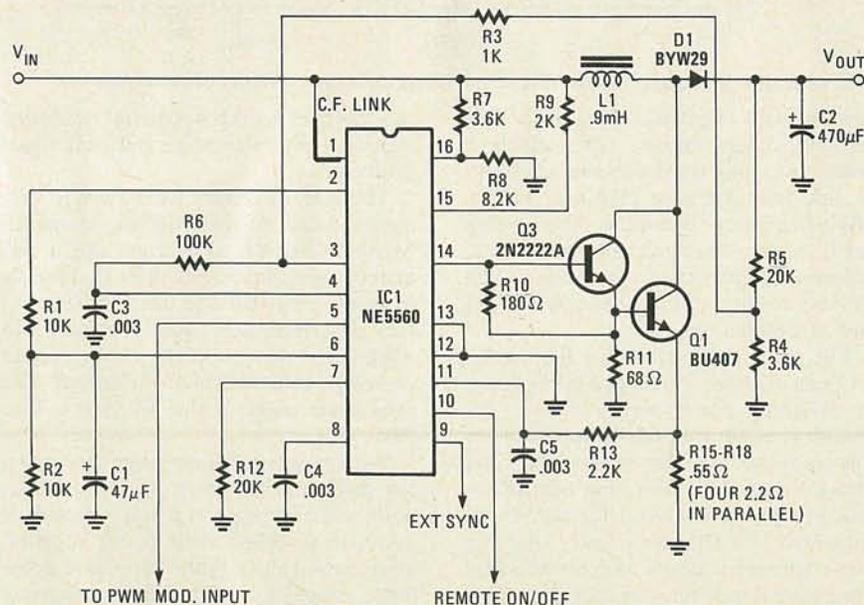

These two protective features can be investigated by looking at the output duty cycle with a scope while opening then shorting the loop.

While the feedback loop looks at the output and tries to compensate for changes due to such things as load variation, a *feedforward* circuit looks at the input line and modifies the duty cycle to compensate for line variations. Resistors R7 and R8 sample the input voltage to the feedforward circuit (pin 16.) When the voltage on pin 16 exceeds an internal reference voltage (V_z , typically 8.4 volts), the charging current for the timing capacitor on pin 8 is increased. The higher the voltage the larger the charging current and consequently the shorter the duty cycle. Conversely, if the voltage on the feedforward pin decreases, the duty cycle increases to compensate for the

change. Ideally, the NE5560 should be operated with the feedforward in its active area, i.e. between V_z and V_{cc} , so that it has plenty of headroom to compensate for variations in the line voltage, up or down. The feedforward function improves the line regulation of the switching power supply by almost a factor of 15.

Another area where protection must be provided against a fault is the switching regulator output. Of primary concern is the power switching elements. Excessive currents, due to output shorts, shorted windings in a choke or transformer etc., can quickly destroy the switching transistor.

Two types of output problems can develop. The first, excessive current, was discussed earlier and was resolved with the aid of pin 11. The second is saturation of the magnetics, especially critical in for-

ward-converter transformers. Pin 13 is used to sample the voltage present in the transformer. Again its output is a comparator with a 0.6-volt threshold which, when activated, will completely inhibit the output pulse until the saturation problem goes away and the voltage drops below 0.6 volt.

Since switched-mode power supplies operate at extremely high efficiencies they can easily control very high power systems where low voltages are not necessarily available to power the NE5560. This potential problem is overcome due to a unique ability of the NE5560 to operate in either a *voltage-fed* (conventional operation) or a *current-fed* mode. When only high voltages (30 volts or above) are available, the IC can be current-driven through a limiting resistor. In this mode internal Zener diodes will limit the drop across the NE5560 to typically 23 volts at 10-mA and 30 volts at 30 mA. A provision for the limiting resistor is made by removing the link connecting pin 1 to V_{in} on Figs. 4, 5, and 6 and inserting a proper resistor with sufficient power dissipation.

Voltage-fed and current-fed modes

The NE5560 operates with either a forced voltage or forced current as the primary power. In the current-fed mode where V_{in} is greater than 30 volts, a series resistor (or current source) is placed between the power source supplying the device and pin 1. [The current-fed (CF) link is removed and replaced by the resistor.] This resistor or current source must be selected to provide a minimum of 10 mA and a maximum of 30 mA. An extra capacitor from pin 1 to ground may be needed to filter noise.

When operated in the current-fed mode, an internal shunt regulator limits the voltage on pin 1 to about 23 volts—this voltage varies from one IC to another and ranges from 20 to 30 volts.

In the voltage-fed mode supply voltage V_{in} must be greater than 9.5 volts (to make the IC active) and less than 18 volts to guard against exceeding the shunt regulator's 20-volt maximum. With V_{in} connected to pin 1 through the CF link. In this mode the IC draws about 8.5 mA.

Remember that any current drawn from pin 2 (V_z) must ultimately come from pin 1 and should be added to the 8.5 mA.

Construction

This switching regulated power supply, although designed primarily as a learning tool to familiarize oneself with the three unique modes of operation, does have practical applications as a supply. Both the switching transistor Q1 (BU407) and the switching diode D1 (BYW29) are capable of switching currents in excess of 5 amps at voltages greater than 100 volts.

The actual current capabilities of the

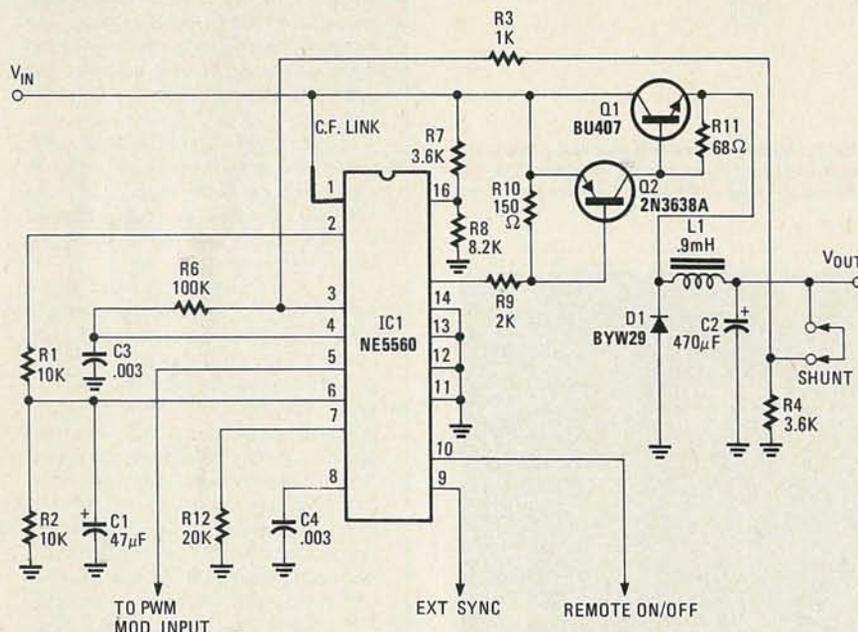


FIG. 5—STEP-DOWN CONFIGURATION. Output is approximately 3.75 volts. Substitute a resistor for the shunt and output can be increased by 1 volt for each 1000 ohms of resistance inserted.


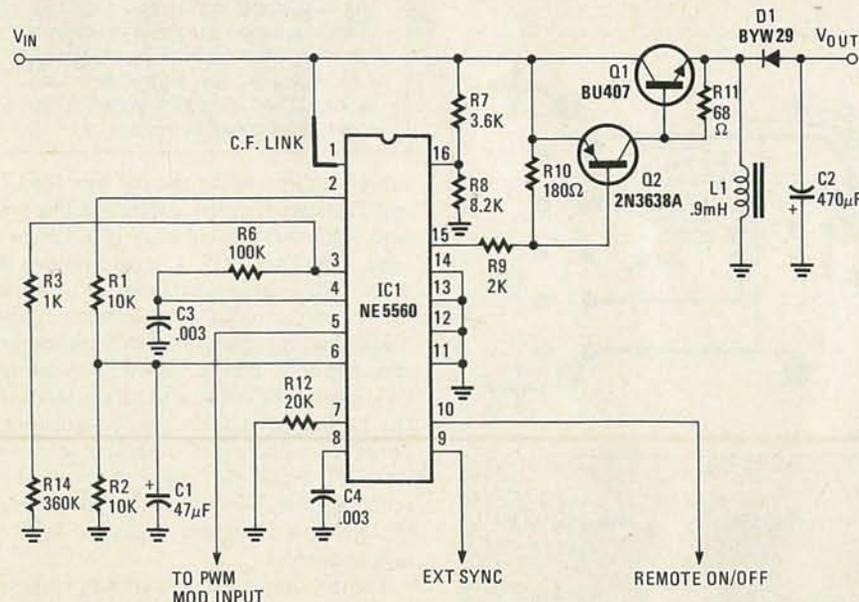


FIG. 6—INVERTING CONFIGURATION. Output voltage polarity is opposite that of the input. This circuit delivers -5 volts.

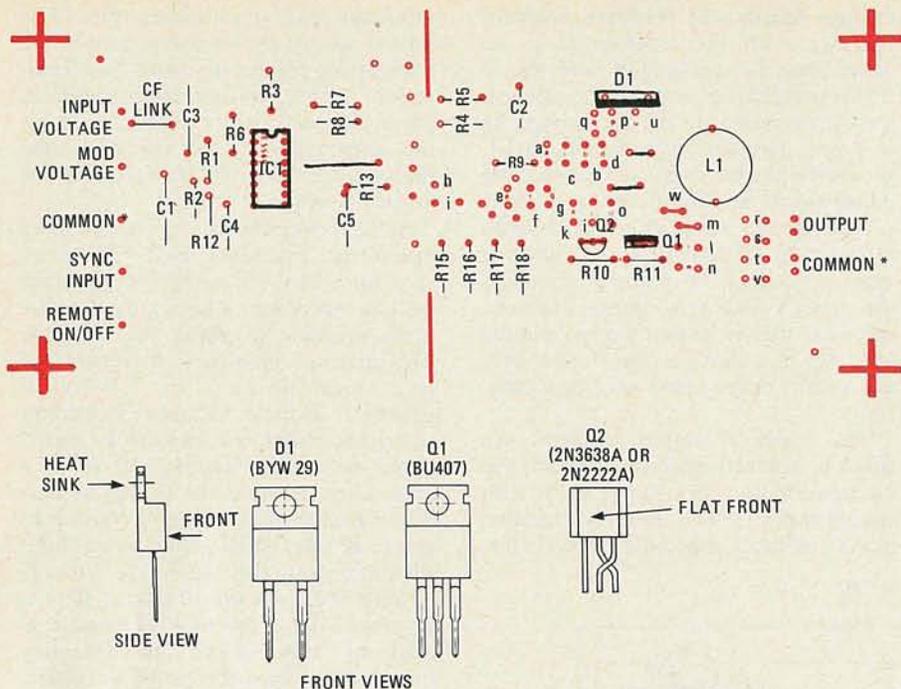

FORWARD VS. FLYBACK

There are two basic types of converters used in Switched Mode Power Supplies: the *forward converter* and the *flyback converter*. In both types of converters an inductor is used as an energy-storage element. In the forward converter the inductor is connected in series with the load. Thus energy is passed to the load and the coil during the "ON" condition of the output transistor. In the flyback converter the coil is connected in parallel with the load. Energy is stored in the coil during the "ON" period and transferred to the load during the "OFF" period. These are sometimes known as series or parallel converters respectively. Each approach has its advantages and disadvantages. In the forward converter, for example, the switching transistor conducts current to the load only during the "ON" condition, and the peak value of V_{CE} that the device must withstand is only equal to the input DC voltage. Also the inductor can be smaller and the capacitor has a lower ripple current to deal with. Disadvantages include difficulty in achieving isolation from the input and the full input DC being applied to the load in the event of a shorted switching transistor.

The advantages of the flyback converter are the opposite of the disadvantages of the forward converter. Input/output isolation is very easy to achieve by adding a secondary to the inductive element. Also it is not necessary to protect the load against excess voltage in the event of a shorted switching transistor. Disadvantages complement the advantages of the forward converter. The peak value of V_{CE} the switching transistor must withstand is the sum of the input DC voltage and the output voltage ($V_{CE} = V_{in} \max + V_o$). Thus both the inductor and diode have to pass higher peak current and withstand higher peak voltage. The inductor is larger and the capacitor must pass higher ripple current. And of course the higher switching voltages and currents generate increased amounts of noise.

supply are limited by the pot core for L1 and oscillator frequency selected. The pot core used for the inductor is a Ferro-cube, type 2213-3C8. The core volume is 2 cm^3 . The bobbin is wound with 14 turns of No. 18 enameled wire (approximately 3 feet) leaving approximately 3 inches for connection to the PC board. Depending on the gauge of the wire used, the holes of the PC board may have to be enlarged. Nominal inductance of the pot core is .9 mH. Trade-offs may be made by reducing this inductance, and increasing the oscillator frequency to achieve higher output currents.

Table 1 shows how maximum current is affected by oscillator frequency and the inductance of L1. Another way to in-

continued on page 80

FIG. 7—COMPONENT LOCATION DIAGRAM. Be sure that both common leads (input and output) are soldered to the top side of the ground plane. Note the pin-outs for D1, Q1 and Q2. The board layout makes it necessary to transpose two leads on Q2. The heatsink sides of Q1 and D1 should be toward the center of the PC board.

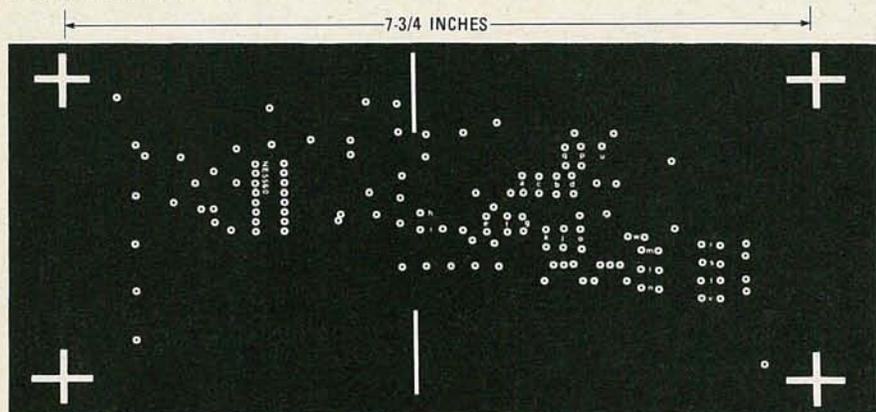


FIG. 8—TOP SURFACE of the PC board is used as a ground-plane. Note that only the circles and lettering are etched away.


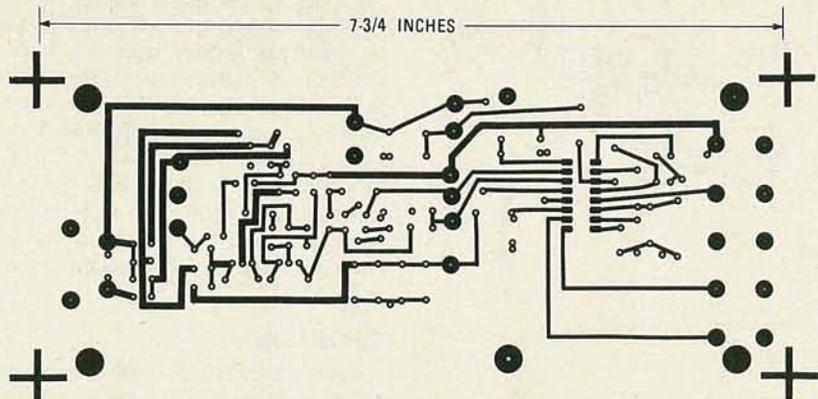


FIG. 9—FOIL PATTERN for the under side of the board.

TABLE 1

Oscillator Freq	No. of Turns	Inductor	Max Current
20 kHz	14	.9 mH	300 mA
40 kHz	10	.5 mH	500 mA
80 kHz	7	.25 mH	700 mA

Not Just Another DIGITAL CLOCK

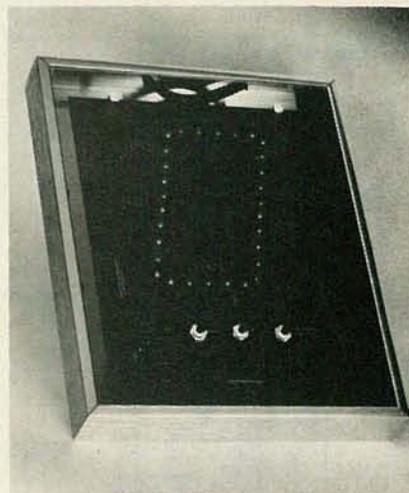

Digital electronic clocks are no longer a novelty, except when they are designed in an unusual format. This electronic digital clock is unique in that hours and minutes are flashed sequentially in a specific pattern on a single 7-segment display nearly five inches high.

JOHN D. WAROBIEW

DIGITAL CLOCKS ARE CERTAINLY PLENTIFUL thanks to the many large-scale integrated circuits currently being produced by several major electronics manufacturers. This clock uses one of the readily available LSI clock IC's, but what makes it unique is the novel approach used to display the time. Instead of the four small 7-segment displays that can be found on most digital clocks, this clock has one 7-segment display that is nearly five inches high. The time is flashed sequentially on the single readout in a specific pattern. The pattern is set so that the time is easily interpreted but it also gives an intriguing effect, especially to those who haven't been told that this strange device is really a clock!

The bright readout is clearly visible, even from across a large room. In addition, the completed clock is less than one inch thick. This means the project can be placed in a standard picture frame and hung on a wall to make an attractive addition to anyone or office.

Circuit description

The basis of the circuit (Fig.1) is the MM3518 clock IC. This device contains all the logic required to set and maintain a 4-digit representation of the time, with the timebase derived from the 60-Hz AC line frequency. It also provides 7-segment outputs that are multiplexed for each digit through a 3-line input code.

The supporting circuitry selects the proper code in the correct sequence. The

555 timer is wired in an astable mode and used to provide a clocking signal to the CD4060 counter (IC3). The 4060 is a 14-stage ripple binary counter/divider and oscillator that gives a repeating binary count of 0 to 15 on its Q5, Q6, Q7 and Q8 outputs. The count is used to alternately select each of the eight output lines of a CD4051 analog switch. Only four of

the eight lines are used. These are combined in a diode matrix to generate the codes on the MM5318 to flash properly the sequence of digits and blanks in the display. (See Fig. 1 and Table 1.) The blank intervals are developed during the periods that the four unused output lines of the CD4051 are selected.

Since the clock IC is normally intended

TABLE 1

Count	4060 Outputs	4051 Line Selected	MM5318 Inputs XYZ	Time Digit Displayed
0	000 0	0	000	Blank
1	000 1	Inhibit	000	Blank
2	001 0	1	000	Blank
3	001 1	Inhibit	000	Blank
4	010 0	2	111	Tens Hours
5	010 1	Inhibit	000	Blank
6	011 0	3	011	Unit Hours
7	011 1	Inhibit	000	Blank
8	100 0	4	000	Blank
9	100 1	Inhibit	000	Blank
10	101 0	5	101	Tens Minutes
11	101 1	Inhibit	000	Blank
12	110 0	6	100	Unit Minutes
13	110 1	Inhibit	000	Blank
14	111 0	7	000	Blank
15	111 1	Inhibit	000	Blank

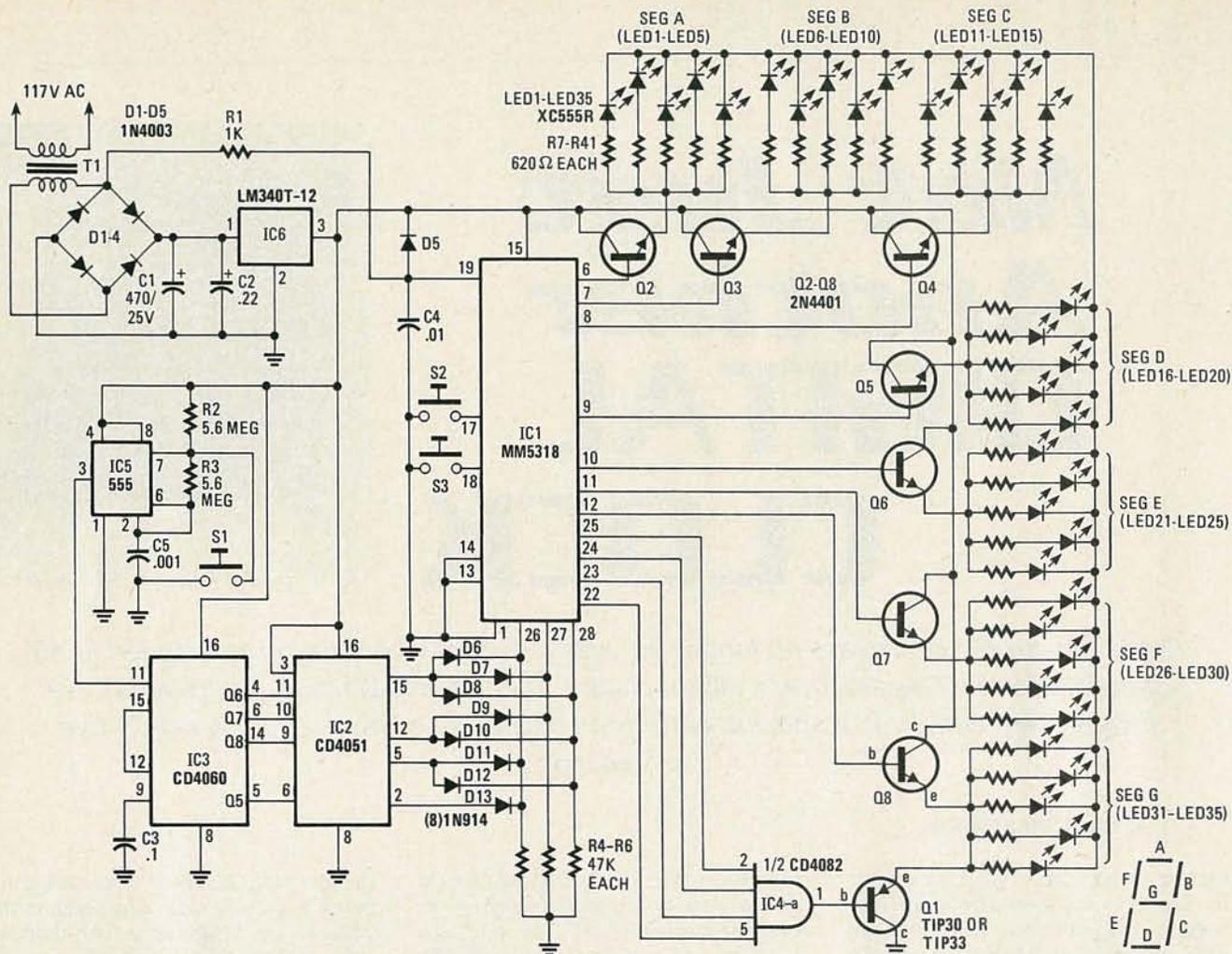


FIG. 1—SCHEMATIC DIAGRAM OF THE FLASHING CLOCK. The readout is a 7-segment numeric display with each segment consisting of five jumbo LED's.

to drive four separate displays, the digit-select lines are combined by the CD4082 AND gate so they all activate the single readout.

Construction

The printed circuit board makes assembly fast and straightforward. The foil pattern is in Fig. 2 and component positions are shown in Fig. 3. Begin by installing and soldering the six jumpers. Diodes and resistors are done next, making sure to observe diode polarities as indicated. A low-profile IC socket should be used for the MM5318 clock IC. Sockets for the other integrated circuits are optional. Note that pin 1 of all IC packages is oriented in the same direction on the board. Bend the leads of the voltage regulator and the TIP30 transistor so that they lie flat against the board when soldered in place.

The seven NPN transistors (Q2-Q8) are in two groups; three on the left and four on the right. Be sure to follow the lead orientation indicated for each group. Capacitors C1 and C2 are polarized and must both be installed in the proper direction for the clock to work correctly. Check the parts layout diagram carefully when installing the 35 LED's. The flat

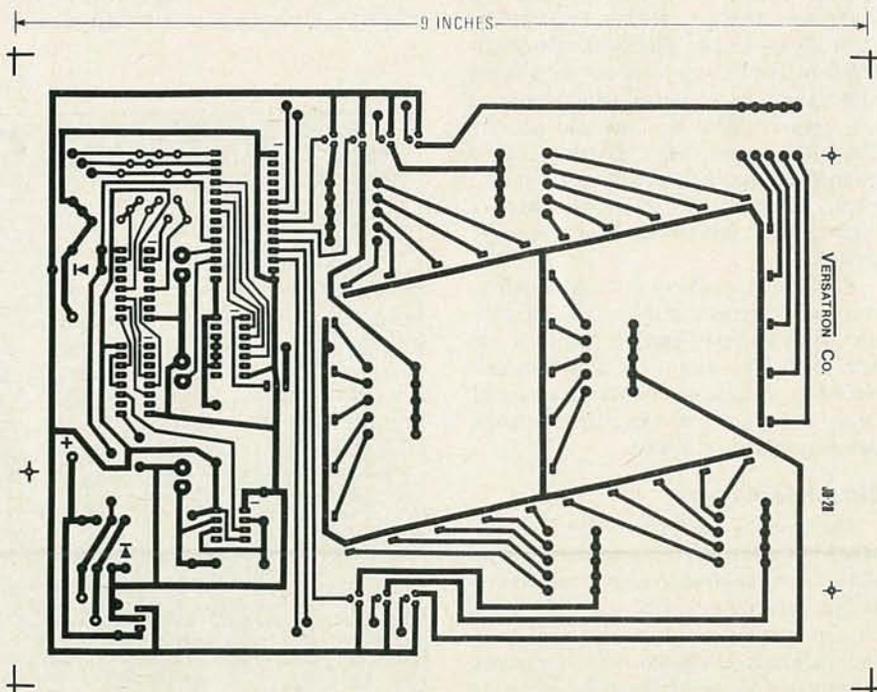


FIG. 2—PRINTED-CIRCUIT FOIL PATTERN is easy to duplicate photographically or by other means. An etched and drilled board is available at a moderate cost.

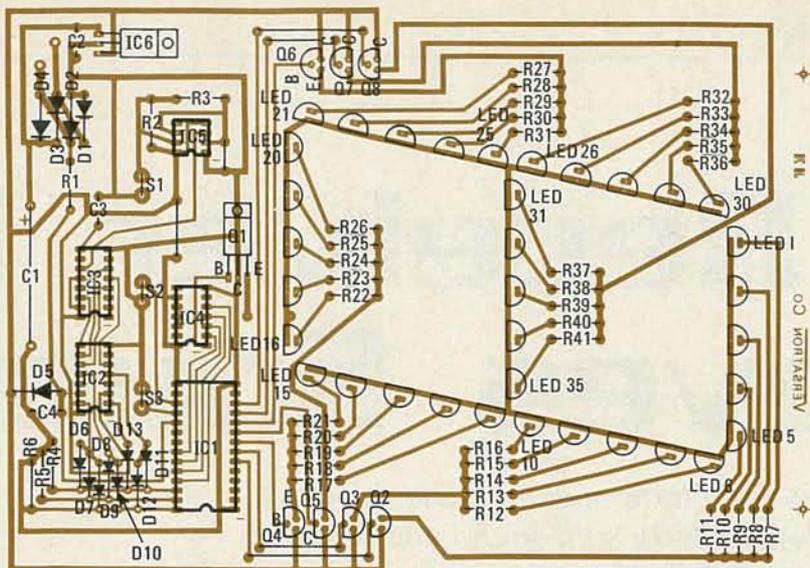


FIG. 3—COMPONENT PLACEMENT LAYOUT. Be careful and check the polarity of each diode and LED before installing it in the board. Use exceptional care when handling the COS/MOS IC's. They are easily damaged by static electricity.

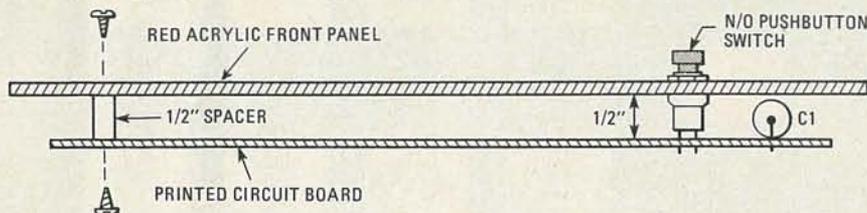


FIG. 4—DRILLING GUIDE for the front panel. The two holes near the top are for mounting screws and spacers. The ones at the bottom are for the three pushbutton switches.

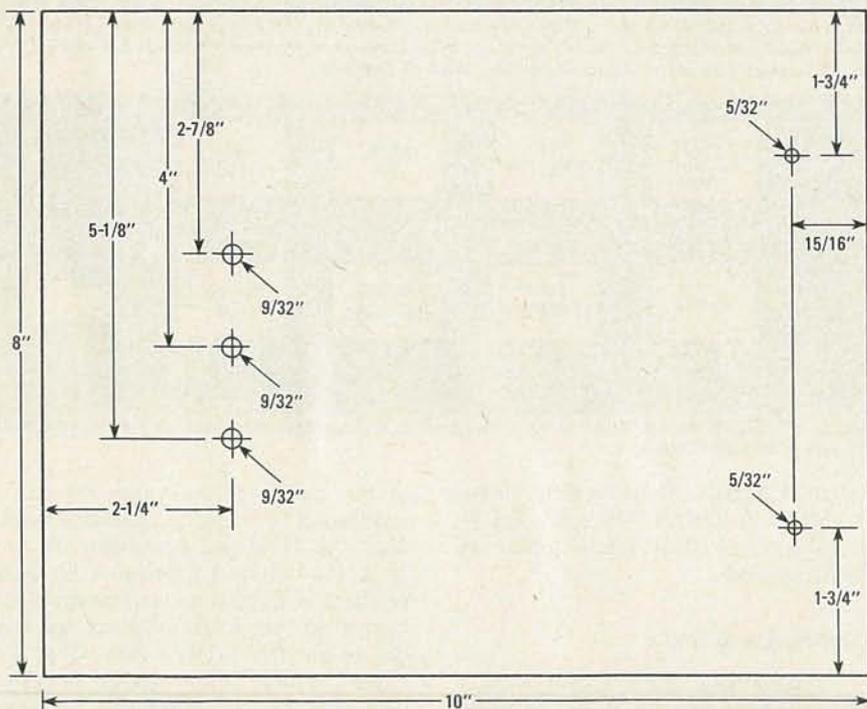


FIG. 5—SIDE VIEW shows how the panel and PC board go together. Adjust the switch heights carefully before soldering the switch to the PC board.

side indicates the proper orientation and corresponds to the flat spot on the base of each LED.

Install two 1/2-inch plastic standoffs in the holes at the top edge of the circuit

board. (The drilling guide is in Fig. 4.) These are used to hold the acrylic front panel parallel in front of the clock. The three pushbutton switches are installed as shown in Fig. 5. They must be soldered at

PARTS LIST

Resistors 1/4 watt, 5% carbon unless otherwise noted

- R1—1000 ohms
- R2, R3—5.6 megohms
- R4—R6—47,000 ohms
- R7—R41—620 ohms
- C1—470 μ F, 25 volts, electrolytic
- C2—0.22 μ F, 35 volts, dipped tantalum
- C3, 0.1 μ F, 50 volts, ceramic disc
- C4—.01 μ F, 50 volts, ceramic disc
- C5—.001 μ F, 50 volts, ceramic disc
- D1—D5—1N4003 rectifier diode
- D6—D13—1N914 switching diode
- IC1—MM5318 digital clock (National)
- IC2—CD4051 8-line analog switch (RCA— analog multiplexer/demultiplexer)
- IC3—CD4060 14-stage ripple-carry binary counter (RCA)
- IC4—CD4082 dual 4-input AND gate (RCA)
- IC5—555 timer
- IC6—LM340T-12 positive 12-volt regulator (National)
- Q1—TIP30 or TIP32 pnp transistor (Texas Instruments)
- Q2—Q8—2N4401 or equal
- LED1—LED35—jumbo red LED (XC555R or equal)
- S1, S2, S3—push-button switches, normally open, PC mount
- T1—plug-type transformer: 12 VAC, 930 mA (Dormeyer model PS-7204)
- Miscellaneous: 28-pin low-profile IC socket, two 1/2-inch long standoffs and screws, 8 in. x 10 in. sheet of 1/8 in. thick red acrylic plastic.

Note: The following kit and parts may be ordered from Versatron Co., PO Box 23573, Pleasant Hill, CA 94523. Phone 415-935-2419:

No. JD-28 PC board, drilled and etched \$13.00

8 x 10 inch metal frame \$4.95

Complete No. JD-28 clock kit (includes all parts except metal frame) \$49.95. California residents add appropriate tax.

the proper height so they protrude through the front panel correctly.

Feed the transformer leads through the hole on the lower edge of the circuit board, starting from the foil side. Tie a knot in the leads so they cannot get pulled back through the hole and then install and solder the ends in the proper locations. This keeps the wires from becoming detached if they are accidentally pulled sharply.

Checkout

Before installing the 5318 clock IC and acrylic front panel, recheck all components against the location guide in Fig. 3. Double check polarities and positioning of the integrated circuits and LED's. Turn the board over and carefully check for any solder bridges. If all components appear to be installed properly, insert IC1 and plug in the transformer.

Operation

When the clock is plugged in and set to

continued on page 81

New Receiver Circuit Improves Sound

New design for interference-free television sound combines early-TV split-sound and today's intercarrier sound techniques. The result; no more sync buzz.

ROBERT F. SCOTT
TECHNICAL EDITOR

FROM THE EARLY DAYS OF COMMERCIAL television until around mid-1950, television receivers used "split-sound" or "parallel-sound" signal processing. That is, the sound IF carrier was "split" off from the composite IF video signal at the tuner output (Fig. 1) or at some point in the video IF amplifier chain. The sound and video IF carriers then followed "parallel" paths to the video and sound detectors. The sound IF was usually between 21.25 and 21.6 MHz—we called it megacycles, then—and the video IF carrier was 4.5 MHz away in the 25.75-26.1-MHz range.

Usually, the nearer the sound takeoff point was to the tuner output the more elaborate was the sound IF system. When the sound takeoff was at the output of the first video IF amplifier, it was not uncommon to find two or three sound IF amplifiers and one or more FM limiters ahead of the sound detector. In those days, the ratio detector was just coming to the fore and the "better" sets still used the Foster-Seeley FM discriminator.

The split-sound TV receiving system had a number of drawbacks. One of the most annoying to the viewer was that a slight drift in the local oscillator frequency caused the sound to distort or drop out completely. This was because the sound IF bandwidth was 400 kHz and an oscillator drift of only 200 kHz was enough to throw the carrier out of the passband. The higher the channel, the more noticeable was the problem of drift. The other drawback was cost. Split-carrier sets had several more tubes and associated circuitry than intercarrier sets.

For example, when a typical split-sound TV set was tuned to Channel 13 (video carrier 211.25 MHz; sound carrier 215.75 MHz) the local oscillator was tuned to 236.75 MHz. This developed a video IF at 25.50 MHz and sound IF car-

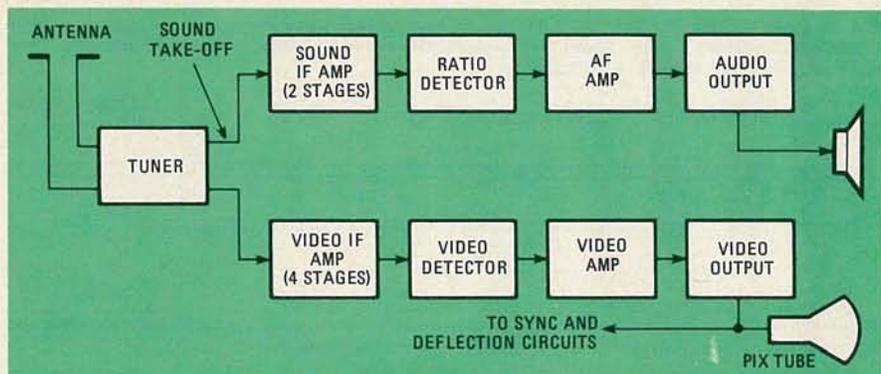


FIG. 1—BLOCK DIAGRAM of the IF circuit arrangement used in the Admiral 30A1 chassis, a popular 1949 model. In it, the sound take-off point was in the tuner. In many other models of this vintage, the sound take-off was at the output of the first video IF amplifier.

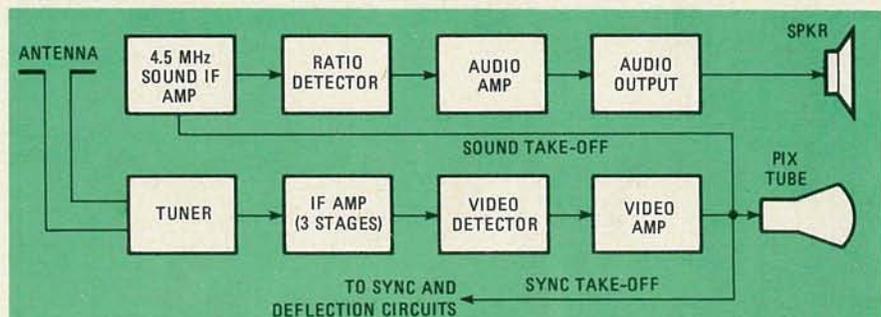


FIG. 2—INTERCARRIER SOUND block diagram. This arrangement was used in the Admiral 20X1 chassis produced in 1950.

rier at 21.00 MHz. If the oscillator drifted to 236.95 or 236.55 MHz (only .084%) sound was lost while picture quality was still acceptable.

Intercarrier sound

The advantage of intercarrier sound is that it does not depend on a precise local oscillator frequency for reception of the sound signal. A block diagram of a typical intercarrier sound set is shown in Fig. 2. The intercarrier sound IF carrier frequency is 4.5 MHz—the precise spacing between the sound and video carrier frequencies on all stations using NTSC TV standards. The 4.5-MHz intercarrier beat developed

at the output of the video detector is modulated by the same signal that modulated the TV sound transmitter. To produce the 4.5-MHz intercarrier IF sound carrier, the TV circuits were designed and aligned so the sound carrier was about 20 dB below the video carrier. This was done because, in the heterodyning process, the resultant difference frequency has the exact modulation as the weaker of the two beating signals.

So, if in an intercarrier TV receiver the oscillator drifts 200 kHz high or low, the video and sound IF carriers will both be shifted. But, the difference between them will still be 4.5 MHz—the frequency of the intercarrier sound carrier signal.

Understanding TURNTABLE SPECIFICATIONS



Part 2—A record player is far from the simple mechanical device it appears to be. If it is not properly designed, you won't get the best from your hi-fi system. A good turntable is essential to top performance.

LEN FELDMAN

CONTRIBUTING HI-FI EDITOR

LAST MONTH I DISCUSSED SOME OF THE design considerations involved in insuring optimum performance of the pickup arm/cartridge combination. That discussion was based upon information supplied by Thorens, the Swiss turntable manufacturer. Now, I would like to examine some of the design elements involved in the turntable drive and suspension systems of a record player, again based upon information that I obtained during my recent visit to the Thorens engineering and production facilities.

In evaluating turntable performance, most audiophiles look to three published specifications: rumble, wow-and-flutter, and speed accuracy. Indeed, under ideal laboratory conditions, these are the only three specifications that would ordinarily have to be considered. But most of us do not play records under ideal laboratory conditions and, what's worse, the records we play are anything but perfect, especially in recent years. Certainly, susceptibility to acoustic feedback is a fourth quality of any turntable system that the prospective purchaser should consider. We will examine the importance of a turntable's suspension system presently, but for the moment, let's discuss turntable rumble.

It is not uncommon to run across two turntables, one that boasts of a rumble figure in excess of 70 dB, while another claims a much more modest 50 dB or even less. Listening to records on both turntables may show that the turntable having the lesser rumble figure may actually produce less noise than the one having the higher figure.

The National Association of Broadcasters (NAB) formulated a method of

rumble measurement in 1964. In the NAB measurement system, only those frequencies between 10 Hz and 250 Hz are included at their full amplitude when making the measurement. Below 10 Hz, a filter rolls off response of the measurement system at a rate of 6 dB-per-octave, while the 3-dB-cutoff at the high end of the range is at 500 Hz with a slope of 12 dB-per-octave above the range. The weighting curve, as it is called, is shown in Fig. 1. An associated test record, having a reference level of 1.4 cm-per-sec peak recorded velocity in lateral modulation at 100 Hz also contains a "silent groove" following the reference signal. The rumble, or signal-to-noise ratio, is expressed as the difference between the reading obtained on a standard VU meter when the modulated groove is playing and the reading observed during playing of the silent groove.

Two additional rumble measurement

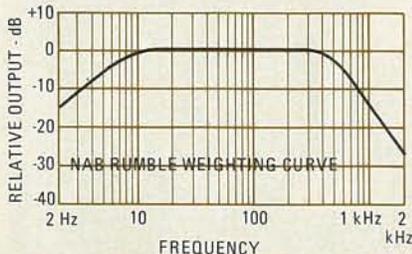


FIG. 1—THE NAB WEIGHTING CURVE used with a test record to measure turntable rumble.

standards were developed by DIN (the German Standards organization). Their standard, DIN 45-539 uses two different weighting networks, as illustrated in Fig. 2. Curve "A", (the unweighted DIN rumble weighting curve) is practically

equivalent to the NAB curve. Curve "B" however, used for making a weighted, or DIN "B" measurement, attempts to deliver test results or numbers that correspond as nearly as possible to the subjective impression of rumble. Because human hearing is less sensitive to low frequencies than to mid-frequencies, the filter attenuates the low frequencies at a rate of 12 dB-per-octave on each side of a center frequency, 315 Hz.

The DIN test record, 45-544 used in

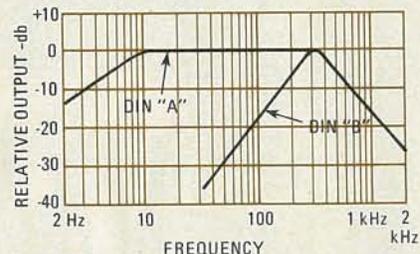


FIG. 2—TWO RUMBLE WEIGHTING CURVES developed by DIN, the German standards organization.

making DIN rumble measurements contains a 315-Hz reference signal recorded at a velocity of 5.42 cm-per-sec (single channel) in addition to the required "silent groove."

In 1966, CBS Laboratories (now known as CBS Technology Center) developed a new weighting curve for measurement of rumble. High-frequency rolloff used in this weighting curve is almost identical to that used in the DIN standard; but at low frequencies, a dropoff of only 6 dB-per-octave is used. The test record developed for this measurement system, known as RRLL (Relative Rumble Loudness Level) has a 100-Hz reference tone recorded at 5 cm-per-sec later-

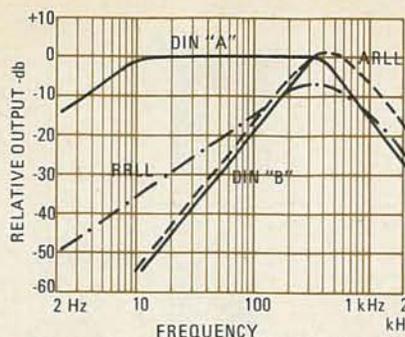


FIG. 3—FOUR POPULAR RUMBLE WEIGHTING CURVES. Text explains their uses and why they differ.

ally and readings are made on an RMS responding meter. This new reference frequency at reference level results in a fundamental difference of readings (compared with the 315-Hz reference level used in DIN) of 7 dB, even before you take into account the difference in the weighting curves.

Finally, there is the ARLL (*Audible Relative Loudness Level*) used by some laboratories and publications. This one starts out using the basic NAB procedure, but adds a filter that corresponds to the standard "A" weighting network used in sound-level meters and in making IHF signal-to-noise measurements for amplifiers, tuners, etc. The four most popular weighting curves have been superimposed in Fig. 3 to give readers some idea how widely rumble measurement may vary, from system to system, both because of differences in reference levels against which the residual noise is measured and because of the differences in the weighing curves themselves. Clearly, there is no way to meaningfully compare an NAB rumble figure with a DIN "B" specifica-

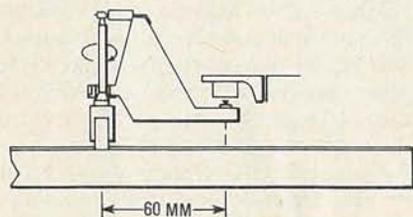


FIG. 4—NEW RUMBLE TEST ADAPTOR, by Thorens, consists of a spindle and a swiveled platform to support the pickup cartridge of the turntable system under test.

tion, or a DIN "A" result against an RLL result. The important point here is that when you compare rumble figures of competing products you make sure that both figures were arrived at using the same test procedure. The IHF (*Institute of High Fidelity*) is now trying to arrive at a standard to be used by the high-fidelity industry, but until that standard is adopted and used, it's up to the consumer to beware of specsmanship. Needless to say, most turntable manufacturers in recent years tend to favor the DIN "B" method simply because it yields higher dB numbers. Unfortunately, infrasonic rumble components, though inaudible as such (and therefore not included in the DIN "B" method) can have a serious

effect on sound reproduction. This is especially true with the new DC amplifiers that amplify signals down to "0 Hz". Severe rumble components in the 6-Hz to 12-Hz region, as we pointed out last month, can aggravate pickup-arm resonance problems. Also, large woofer cone excursions at subsonic frequencies, though in themselves inaudible, can push the speaker cone out of its linear operating region, thereby introducing IM distortion at audible frequencies.

New Rumble Measurement Instrument

Rumble measurements are further complicated by the fact that rumble is also contained in the test records themselves, besides being generated by turntable drive mechanisms. Engineers at Thorens discovered that the average rumble of many of the rumble test records popularly used was approximately the same as that of many high quality turntable systems. The record may therefore contribute as much to the rumble measurement as the turntable itself. For this reason, Thorens developed a new device (Fig. 4) to replace the test record for rumble measurements. Figure 5 shows the Thorens Rumble Test Adaptor being used to check a Thorens TD-126 Mk III turntable.

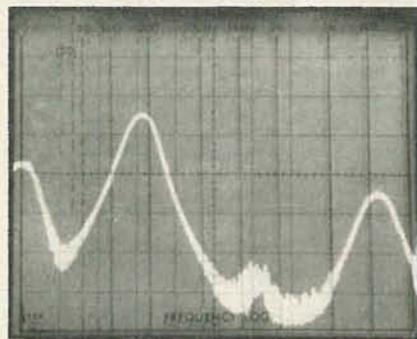


FIG. 5—ILLUSTRATION shows the Thorens rumble test adaptor in actual use. A special test record is used.


ble. The device consists essentially of two elements: a spindle and a swiveled frame, upon which the stylus of the pickup cartridge is placed. The spindle, which is rigidly connected to the turntable shaft, is carefully polished and plated, first with copper and then with nickel. The bearing contact is equipped with high-polymer parts. The two elements of the Rumble Test Adaptor are rigidly connected, allowing any vibration or noise to be transmitted to the pickup cartridge for subsequent measurement. The test record seen in Fig. 5 is now used only to establish a reference level against which to measure the rumble value. The construction of the bearing of this device enables vibrations in both vertical and lateral directions of each stereo channel to be detected.

Whether rumble is measured this way or with a test record, a great deal of information can be gained with the aid of a spectrum analyzer, since it is important to know the content (frequencies) of the rumble as well as its overall single-number value. Using the Rumble Test

Adaptor just described, we tried to analyze the rumble content of a typical high-quality turntable that uses a synchronous 1800-RPM motor and belt drive. Even using a low-noise, hum-free (we thought) setup in the tests we were plagued by hum and some noise pickup which threatened to mask the results. To differentiate between electrically generated hum and noise and low-frequency rumble content, we therefore made two plots on the analyzer. The first, shown in Fig. 6-a is a linear sweep from 0 Hz to 200 Hz (20 Hz per linear horizontal division on the scope face) taken with the arm at rest, but with the turntable rotating (motor on). The peak at the extreme left of the display is the "zero beat" of the analyzer and may be ignored. Approximately three divisions to the right is the expected peak at 60 Hz (line frequency) and to the right we see a second major peak at 180 Hz (third harmonic of the line frequency). A much



a

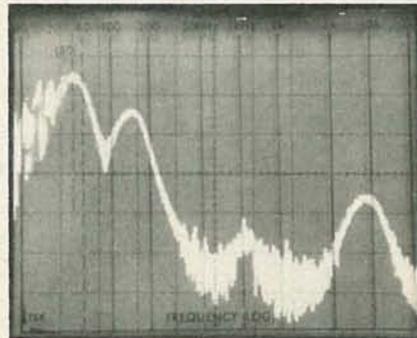

b

FIG. 6—SPECTRUM ANALYZER RECORDS. The trace at a was made with pickup arm at rest while turntable was rotating. Trace at b was made with pickup resting on platform of the test adaptor.

lower amplitude peak is also detectable at 120 Hz (second harmonic of 60 Hz).

Compare these results with those obtained when the stylus was positioned on the frame of the Thorens Rumble Test Adaptor while the turntable revolved, as shown in Fig. 6-b. The first thing we notice is a brand new peak at 30 Hz which is actually taller than the "hum" peak at 60. If you divide the rotation of the motor (1800 RPM) by 60 seconds, sure enough you come up with 30 Hz. In other words, a severe rumble component is being contributed by the motor on a once-per-revolution basis. Even more interesting are additional spikes observed at the extreme left of the display, in the region below 20

TABLE 1

Turntable	Test Record	Rumble Adaptor
Average direct-drive model	-46 dB	-60 dB
High-quality direct drive with quartz speed control	-48 dB	-51 dB
Thorens TD 126 Mk III	-50 dB	-72 dB

Hz. These spikes, too, are greater in amplitude than the electrically generated hum noise observed earlier and one or more of them may well lie in the exact frequency region of pickup-arm/cartridge resonance. Clearly, a single meter measurement of rumble, by whatever standard, could not disclose this much information about the nature of the noise itself.

Thorens maintains that their new Rumble Test Adaptor can provide help in explaining the audible differences between various turntables which, using test records to establish rumble figures, come up with rumble figures which at first glance are not significantly different. As proof of this, they offer a summary of measurements made the "old" (test record) way and using their Rumble Test Adaptor. The summary is shown in Table 1 and note that, in all cases, the more severe DIN "A" (unweighted) measurements were used.

Improving Turntable Suspensions

The fourth factor which determines the quality and performance of a turntable system is its suspension system. Unfortunately, few manufacturers of turntables are able to say much about their

efforts in this direction, largely because the quality of a suspension system does not lend itself to a measurement. Acoustic feedback, whether it be a continuously howling sound when volume is turned up too loud, or partial feedback which falls short of that extreme but nevertheless causes coloration of reproduced sound, is a problem known to all-too-many audio buffs. Acoustic feedback may be airborne (sound waves from the speaker vibrate against the turntable's structure and are picked up by the stylus riding in a record groove) or it may result from vibration carried through the floor, the surface upon which the turntable is mounted, etc.

The classical floating suspension system, shown in Fig. 7, does offer a number of advantages such as high insensitivity to solid-borne vibrations above 20 Hz and great immunity to mechanical and acoustic feedback. However, there are also disadvantages. It is sensitive to ultra-low frequency disturbances, such as those transmitted to the turntable from the movement of people on a wood floor or from external jolts. Studies have shown that when this conventional suspension system is used, choosing a low resonant frequency for the system is not sufficient for

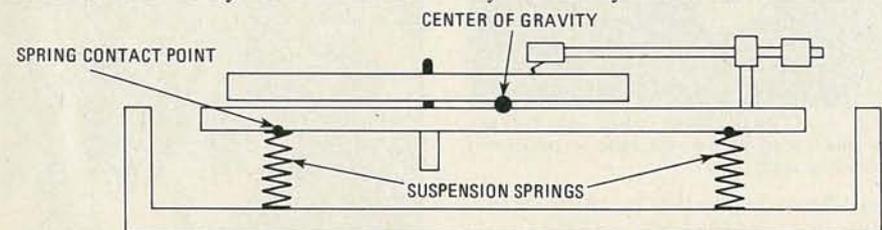


FIG. 7—TYPICAL TURNTABLE SUSPENSION SYSTEM as it appears when at rest.

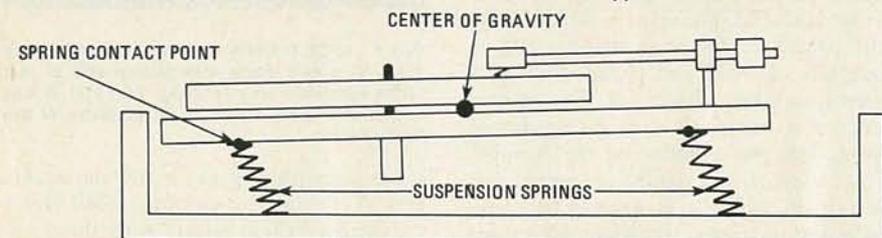


FIG. 8—HORIZONTAL DEFLECTION of the typical turntable mounting board causes complex rotational and vertical movements.

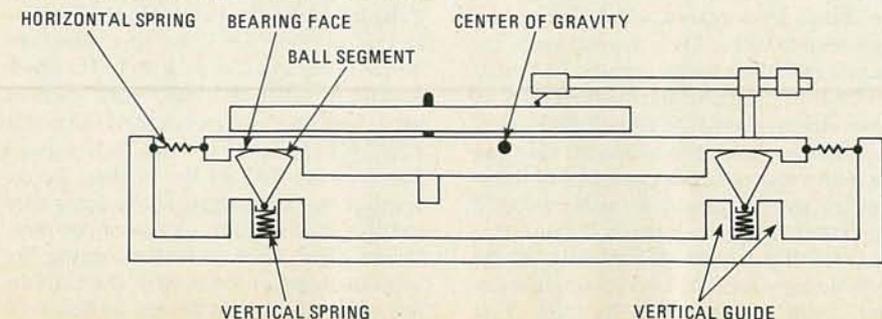


FIG. 9—BASIC DRAWING of the Thorens Ortho-Inertial turntable suspension system.

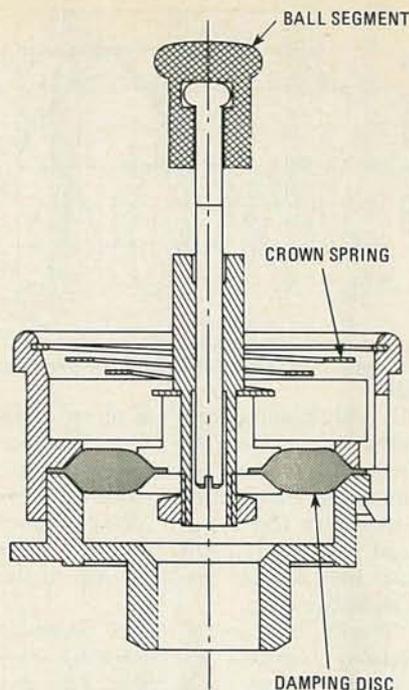


FIG. 10—CROSS-SECTION view of the ball-segment mounting arrangement used by Thorens.

achieving optimum behavior. Difficulties arise when so-called "mode conversion" effects take place. For example, a simple horizontal excitation may produce an intricate combination of translational and rotational displacements. Figure 8 illustrates such an effect in a conventional suspension system.

According to Thorens, their newly developed *Ortho-Inertial* suspension system eliminates many of these problems. The suspension system is illustrated in simplified form in Fig. 9. The chassis of the turntable is supported by ball-segment bearings and by separate spring elements for horizontal and vertical displacements. The bearing faces on the chassis are in the same plane as the center of gravity and each ball segment bearing is supported at its midpoint by a spring possessing freedom only in the vertical direction. A detailed cross-sectional view is shown in Fig. 10.

If this system is set into motion by a horizontal excitation, the chassis rolls over the ball segments. Since the center of gravity and the bearing faces lie in the same plane, no rotational motion occurs. Furthermore, since the height of the chassis does not change when it rolls over the ball segments, the vertical springs retain their fixed length and vertical displacement does not take place. The ball-segment bearings are fabricated of rubber and afford isolation and damping of disturbance frequencies within the audio range. This reduces the turntable's sensitivity to acoustic feedback as well.

It has been repeated in print many times that all a turntable has to do is rotate at a constant speed and so so quietly. As you can see from this and last month's discussion of pickup arm design, that is more easily said than done. R-E

REAL SOUND

Technics Model RS-M7 Cassette Deck



1
CIRCLE 107 ON FREE INFORMATION CARD

WHEN MONEY IS NO OBJECT IT IS FAIRLY EASY to find a stereo cassette deck that can deliver recorded results that are almost indistinguishable from the original program source. But what happens if you are on a limited budget and want to purchase a low-cost cassette deck that provides good basic performance for under \$200? Technics (Panasonic Company, 1 Panasonic Way, Secaucus, NJ 07094) appears to have provided the answer with the low-cost model RS-M7 stereo cassette deck.

This front-loading unit, shown in Fig. 1, is one of the lowest-priced decks we have tested that include Dolby circuitry. The gold-colored aluminum front panel contains a POWER on/off pushbutton switch and a stereo headphone jack on the left. A swing-down cassette compartment door permits the easy insertion and orientation of tape cassettes. Just below the cassette door are seven mechanically operated piano-key-type transport controls, including pause, record, play, rewind, fast forward, stop and eject. The PLAY and STOP pushbuttons are somewhat larger than the other controls, for quick visual identification, and in order to activate the record mode, both the RECORD and PLAY pushbuttons must be depressed simultaneously.

A three-digit tape counter is located at center-panel together with a reset pushbutton, and just below the counter are three toggle switches. The first switch turns the Dolby circuitry on or off. The middle switch selects line or microphone inputs, while the third switch with three positions selects proper equalization and bias levels for normal (ferric-oxide), ferri-chrome and chromium-dioxide or high-bias ferric-cobalt tapes.

Record-level controls for each channel are concentrically mounted below a pair of record-level meters that are calibrated from -20 dB to +5 dB. Dolby level is indicated as +3 dB on the scales, and since this level is standardized at 200 nWb-per-meter, this places Technics' arbitrary "0-dB record level" at approximately 142 nWb-per-meter.

Between the record-level meters is an LED

indicator light that glows red when the tape deck is in the record mode, while at the lower right of the panel are a pair of microphone input jacks. The rear panel contains a pair of line input and line output jacks.

The model RS-M7 uses 12 transistors in addition to the four IC's. A single tape head is used for record and playback, and a double-gap ferrite head is provided for tape erasure.


Lab measurements

For our laboratory measurements, we used Maxell UD-XLI tape as our ferric-oxide tape sample, Sony Duad tape for FeCr tape and TDK-type SA tape for measurements using the CrO₂ tape setting. Results of these lab measurements are shown in Table 1.

Frequency response when Maxell tape was used is shown in Fig. 2 for a record-playback level of -20 dB relative to the arbitrary 0-dB point on the level meters. While the manufacturer deserves a mild rebuke for not publishing tolerance figures (\pm dB's) in their frequency-response specifications, we found that the frequency response between the -3-dB rolloff points, was nearly as good as the Technics claims that omit tolerance values.

Both the ferri-chrome tape sample and the cobalt-ferric high-bias tape sample performed a bit better in record/play response, with the 3-dB rolloff point occurring at 14 kHz for each tape sample, as shown in Figs. 3 and 4.

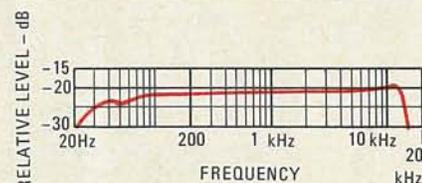Using our standard test tape TDK No. AC-337, which contains spot frequency signals from 40 Hz to 12.5 kHz, we measured playback-only response. The results are shown in



2

RADIO-ELECTRONICS AUDIO LAB

REAL SOUND

RATES


TECHNICS RS-M7
CASSETTE DECK

VERY GOOD


Copyright © Gernsback Publications Inc., 1979

Fig. 5 and were flat within ± 1 dB over the 40-Hz to 12.5-kHz range.

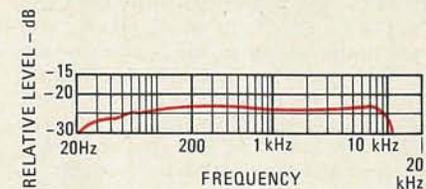While the maximum recording level for 3% total harmonic distortion seems to be incredibly high (+11 dB for standard tape, +8 dB for cobalt-ferric tape), you must remember that these levels are referenced to 0 dB on the tape deck's own meters and the recording level that Technics chose for the 0-dB mark is lower than on many other tape decks. Even if you



3

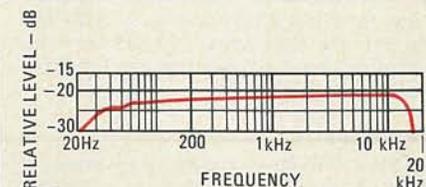


4

MANUFACTURER'S PUBLISHED SPECIFICATIONS:


Frequency Response: standard tape, 30 Hz to 14 kHz; CrO₂/FeCr tape, 30 Hz to 15 kHz. **Wow and flutter:** 0.08% WRMS. **Signal-to-Noise Ratio:** with CrO₂ tape or equal, 56 dB (below maximum record level) without Dolby; 66 dB (above 5 kHz) with Dolby. **Fast Forward or Rewind Time (C-60 Cassette):** 86 seconds. **Bias Frequency:** 80 kHz. **Input Sensitivity:** line, 60 mV; microphone, 0.25 mV. **Microphone Impedance:** 400 to 10,000 ohms. **Output Level:** 0.42 volt. **Headphone Output Level:** 65 mV (8-ohm impedance). **Power Requirements:** 120 volts, 50 to 60 Hz, 19 watts. **Dimensions:** 16 $\frac{1}{8}$ W \times 5 $\frac{1}{2}$ H \times 9 $\frac{1}{8}$ inches D. **Weight:** 10 lbs. **Suggested Retail Price:** \$175.

subtract 3 dB from the measurements and assume a standard 0-dB level of 200 nWb-per-meter, the tape deck's headroom is very good, at least when used with these high-quality tapes.

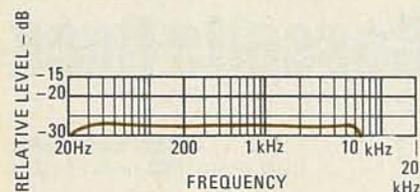
We subjected the RS-M7 to a two-tone IM distortion test, using a pair of 9-kHz and 10-kHz tones at a 0-dB peak recording level. For comparison Fig. 6 shows the components of the signal source. The spectrum analyzer was swept linearly rather than logarithmically, and the sweep is 2 kHz-per-horizontal division. The 9-kHz and 10-kHz tones are centered in



5

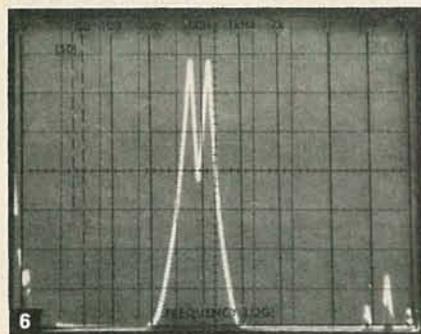

6

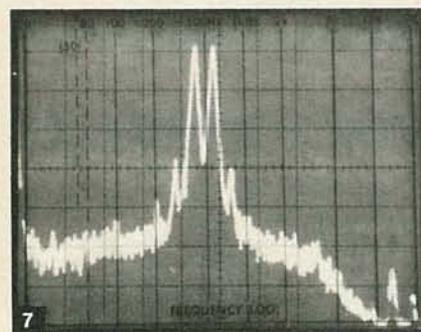

7

the display. Disregard the small peaks on the right.

Figure 7 shows the playback signals recorded on the tape sample at 0-dB record levels. Note that in addition to the noise floor, two or more distinct IM signals are now visible—one at 8 kHz, the other at 11 kHz. These signals are respectively 31 dB and 33 dB below the test tones. To calculate the two-tone IM distortion under these conditions, 3 dB must be added to the level of either test tone to establish an equivalent peak level of the reference signal so that the two distortion values are, in effect, 34 dB and 36 dB below the reference level. Summing these two distortion values results in a net distortion level that is 32.24 dB below the reference level, corresponding to an IM distortion level of 2.44%.

Summary

Our overall product evaluation is shown in Table 2, together with summary comments. The model RS-M7 cassette deck performed extremely well for its low price. Our R.E.A.L. sound rating of very good must be considered in the light of that price, and it reflects the fact that as recently as two years ago cassette decks at this quality level might easily have cost between \$250 and \$300.

R-E

TABLE 1

Manufacturer: Technics by Panasonic

Model: RS-M7

RADIO-ELECTRONICS PRODUCT TEST REPORT CASSETTE TAPE DECK MEASUREMENTS

	R-E Measurements	R-E Evaluation
FREQUENCY RESPONSE MEASUREMENTS		
Frequency response, standard tape (Hz-kHz ± dB)	30-13, 3	Good
Frequency response, CrO ₂ tape (Hz-kHz ± dB)	40-14, 3	Very good
Frequency response, other (see text) (Hz-kHz ± dB)	35-14, 3	Good
DISTORTION MEASUREMENTS (RECORD/PLAY)		
Harmonic distortion at -3 VU (1 kHz) (%)	1.0/1.0	Excellent
Harmonic distortion at 0 VU (1 kHz) (%)	1.0/1.0	Excellent
Harmonic distortion at +3 VU (1 kHz) (%)	1.0/1.1	Excellent
Level for 3% THD (dB)	+11/+8	Excellent
SIGNAL-TO-NOISE RATIO MEASUREMENTS		
Standard tape, "Dolby" off (dB)	59	Very good
Standard tape, "Dolby" on (dB)	68	Very good
Hi-bias tape, Dolby off (dB)	61	Very good
Hi-bias tape, Dolby on (dB)	69	Very good
MECHANICAL PERFORMANCE MEASUREMENTS		
Wow and flutter (% WRMS)	0.04	Excellent
Fast wind and rewind time, C-60 tape (seconds)	90	Fair
COMPONENT MATCHING CHARACTERISTICS		
Microphone input sensitivity (mV)	0.25	
Line input sensitivity (mV)	50	
Line output level (mV)	350	
Phone output level (mV)	54 (8 ohms)	
Bias frequency (kHz)	80	
TRANSPORT MECHANISM EVALUATION		
Action of transport controls		Good
Absence of mechanical noise		Very good
Tape head accessibility		Very good
Construction and internal layout		Good
Evaluation of extra features, if any		Good
CONTROL EVALUATION		
Level indicator(s)		Good
Level control action		Good
Adequacy of controls		Good
Evaluation of extra controls		Good
OVERALL TAPE DECK PERFORMANCE RATING		Very good

TABLE 2

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Technics by Panasonic

Model: RS-M7

OVERALL PRODUCT ANALYSIS

Retail price	\$175
Price category	Low
Price/performance ratio	Excellent
Styling and appearance	Very good
Sound quality	Very good
Mechanical performance	Good

Comments: In evaluating a stereo cassette deck such as the Technics model RS-M7 one must, above all, keep in mind its low price. Just a year or two ago, a cassette deck with a suggested retail price of \$175 equipped with Dolby noise reduction and the more-than-adequate level of performance obtained from this unit would have been considered a near miracle. Of course, this unit lacks some of the sophisticated features found on costlier decks, but the features it does have make you quickly realize that all the basics are there. For a mechanically operated transport system, the mechanism operates smoothly and quietly. It has the important auto-stop feature when end of tape is reached, so that idler wheel-to-capstan pressure is released when you are not there to turn off the machine. While there are no user-accessible adjustments for Dolby calibration, our test unit has been almost perfectly factory-adjusted for proper Dolby noise-reduction tracking, and the noise-reduction capability of the built-in Dolby circuitry was fully as great as it is on much more expensive tape decks.

Recordists who consider overall frequency response to be the major specification may find this unit's response a bit disappointing; but those who are more knowledgeable will realize that in this budget design, Technics has managed an intelligent trade-off and balance between frequency response, distortion and signal-to-noise ratios that results in as good sounding a tape deck as could possibly be achieved at this price level. Then, too, when you consider that not many years ago a wow-and-flutter figure of 0.1% WRMS was considered to be quite good even in expensive tape decks, Technics' achievement of 0.04% in this deck is all the more remarkable.

In sum, the model RS-M7 stereo cassette deck offers very good basic tape recording facilities, and with the money you would save by purchasing it, you can afford to use the best cassette tapes available.

service clinic

Here's an automatic brightness limiter circuit problem with a strange twist.

JACK DARR, SERVICE EDITOR

THE IDEA FOR THIS MONTH'S CLINIC CAME from a Magnavox T995-01 chassis that involved a good but incomplete diagnosis, and a lot of work; and the story has a pure Alfred Hitchcock ending.

After replacing a bad high-voltage tripler, everything was fine. The high-voltage was normal, etc. Only one problem: no raster. Off we went. After some tests, we wound up in the *Low Level Video* module (LLV), which contains the video amplifiers and the automatic brightness limiter stage. Figure 1 shows a simplified schematic of this module.

Note that the automatic brightness limiter transistor is shown with +1.4 volts on the collector. It measured about +10 volts. This transistor controls the maximum brightness automatically by sensing the beam current. As the beam current increases, the automatic brightness limiter transistor (Q6) goes farther into conduction. Transistor Q6 affects the bias on the video amplifier transistor, Q4. From the voltages, it was apparent that the video amplifier and video driver were cut off. The collector voltage on Q5 was

zero. (Here's an oddity: on the RGB module we did read some video signal. Only about 25 volts P-P, instead of the normal 100 volts plus. Evidently, this was simply leaking through the cutoff transistor, by capacitance.)

Transistor Q6 seemed to be leaky. By replacing this, we got a raster and a good picture. (Now comes the kicker!) However, while the brightness control did work, putting the raster out at one end, at the other end the raster was far too bright. The video was burned out. The video amplifier and video driver has apparently been cut off, but now we had no automatic brightness limiter action at all. Re-checking, we found that someone had forgotten to solder the collector of the transistor Q6; it was open. Fixing this, we found that we were back right where we started! The collector of Q6 measured +10 volts and the video was cut off. Back to the drawing board.

The automatic brightness limiter circuit isn't complex, but it is interesting. In normal operation, transistor Q6 is cut off. At a "typical" beam current, it does nothing.

Its base is clamped at +23.5 volts by a 1K resistor to the emitter and the +24 volt line. A connection from the base goes outside the module to dropping resistor R18. See Fig. 1. This is in the return circuit for the high voltage winding of the flyback transformer so that the beam current flows through it, to ground. This voltage is mixed with the fixed bias. (According to Ohm's Law, at the maximum beam current of 1500 microamps, this should develop about -49.5 volts. A median beam current of say 750 μ A should develop about +25 volts.)

At maximum drop, this voltage bucks the +23.5 volts, and if it goes far enough negative, it develops a net negative bias on the base of Q6. Since this is a PNP transistor, it turns on, and it in turn cuts off the video amplifier. As we laid out this circuit in a simplified form, we found an oddity. Resistor R18, the dropping resistor, is actually in two different circuits at the same time. One is in the +23-volt clamp circuit and the other is in the high voltage beam current return. So, it's a kind of "one-resistor matrix" that develops not one but two voltage drops at the same time. Rather, this is the sum of the two. If it's to work, this must be just enough to cut off the transistor Q6 with average beam current.

So here we were; obviously it was not doing it. We had a good transistor in the brightness limiter stage, and all other resistors checked out. What was left? Might be a change in value of R18 under load. Capacitor C10 was checked and found good. In desperation, we removed R18 and tacked in a 50K pot. By varying this, we did find a setting where things worked. This value turned out to be almost exactly 35.0 K. Checking the resistor stock dug up one with exactly this value. It worked. However, something kept tapping me on the shoulder! I had a queasy feeling that we had not fixed it, but simply "jury-rigged it." I was right.

Checking back to the Magnavox Service News, I read the circuit description. Going farther, I read the whole thing. On the next page, there was a note on brightness problems due to ABL overconduction! Woops! Just what we had. The note said: "be sure to check R5, 820K, 4.9W, which is in the ground-return circuit of the high voltage/Scan Sweep module, on the far side of the mother board. Checking R5, it seemed to be OK. So, we

continued on page 78

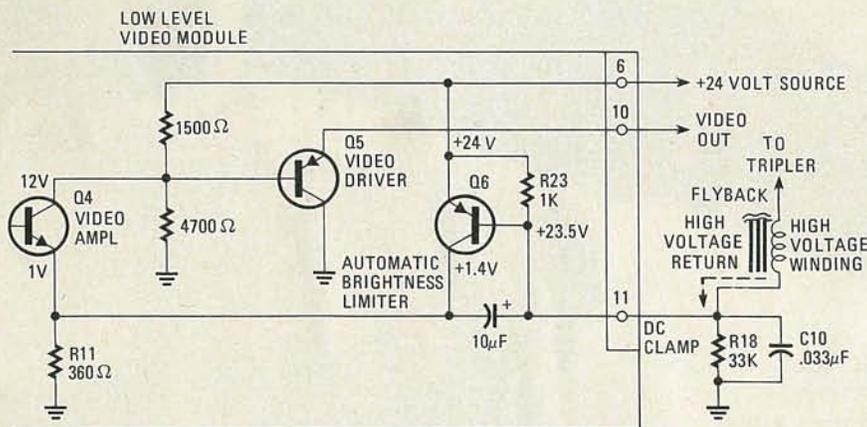


FIG. 1

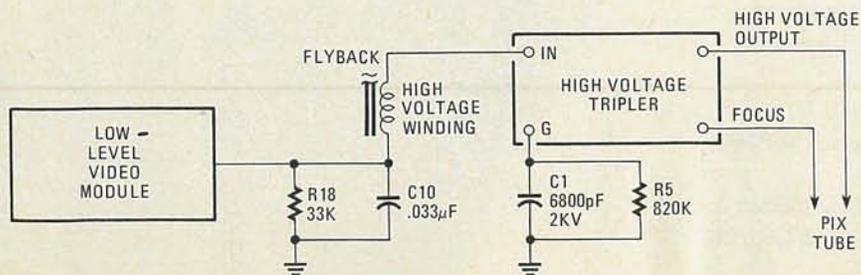


FIG. 2

EQUIPMENT AND TRAINING NO OTHER SCHOOL CAN MATCH.

**NTS HOME TRAINING INVITES YOU TO EXPLORE MICROCOMPUTERS,
DIGITAL SYSTEMS AND MORE, WITH STATE-OF-THE-ART EQUIPMENT
YOU ASSEMBLE AND KEEP.**

Without question, microcomputers are the state of the art in electronics. And NTS is the only home study school that enables you to train for this booming field by working with your own production-model microcomputer.


We'll explain the principles of troubleshooting and testing your microcomputer and, best of all, we'll show you how to program it to do what you want.

You'll use a digital multimeter, a digital logic probe and other sophisticated testing gear to learn how to localize problems and solve them.

Send for the full color catalog in the electronics area of your choice—discover *all* the advantages of home study with NTS!

NTS also offers courses in Auto Mechanics, Air Conditioning and Home Appliances. Check card for more information.

1.

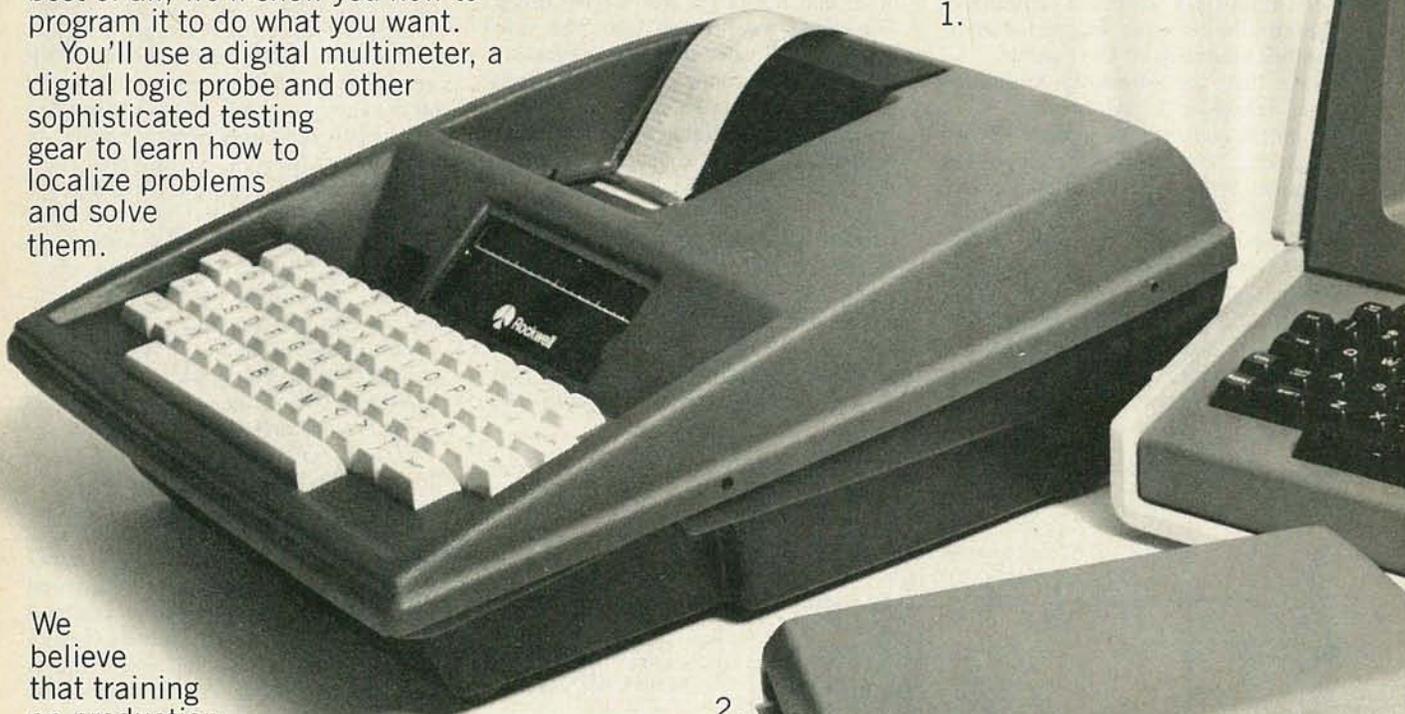

We believe that training on production-model equipment, rather than home-made learning devices, makes home study more exciting and relevant. That's why you'll find such gear in all 14 of NTS's electronics programs.


For instance, to learn Color TV Servicing, you'll build and keep the 25-inch (diagonal) NTS/HEATH digital color TV.

In Audio Electronics, you'll be able to assemble your own NTS/HEATH digital stereo receiver with 70 watts per channel.

But no matter which program you choose, NTS's Project Method of instruction helps you quickly acquire practical know-how.

2.



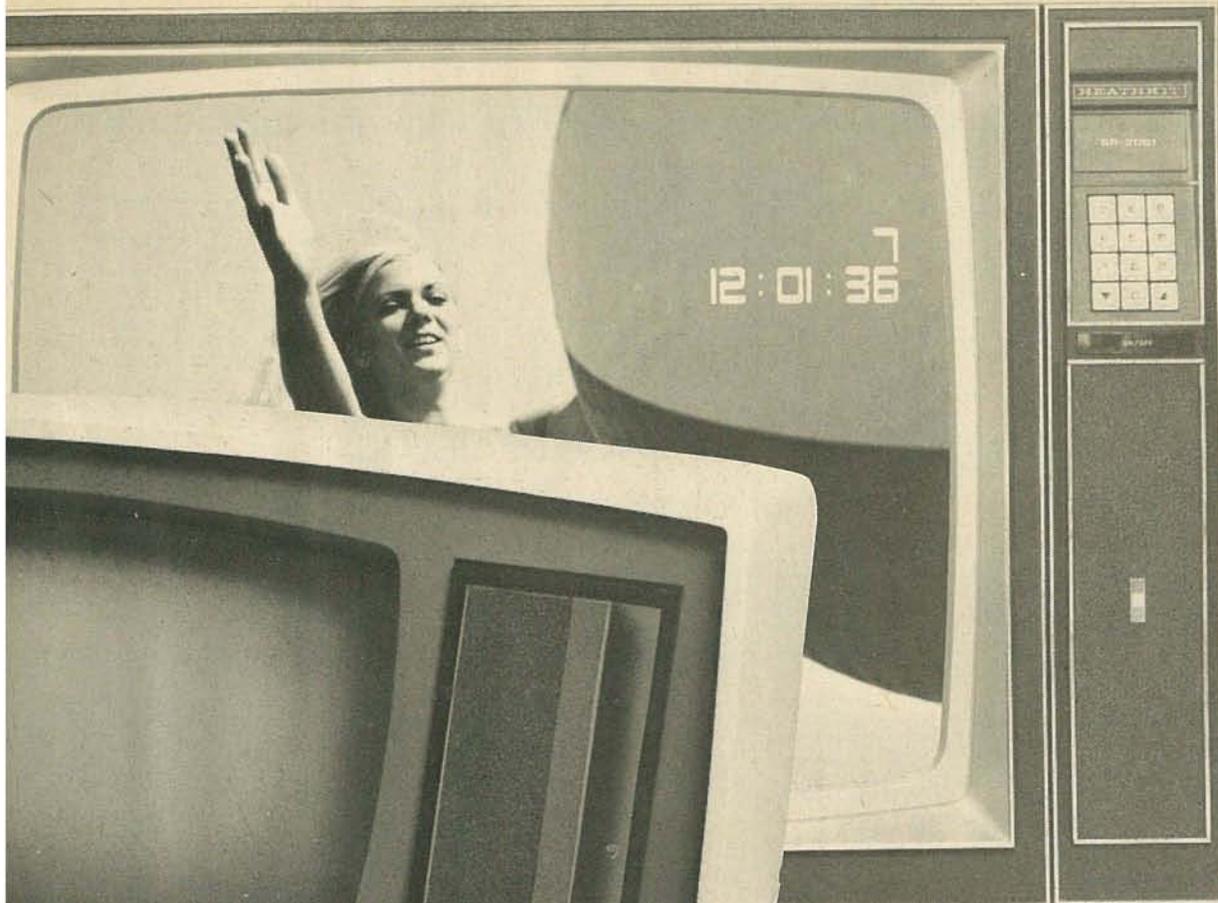

Simulated TV Reception

4.

3.



1. The NTS/Rockwell AIM 65

Microcomputer A single board unit with on-board 20 column alphanumeric printer and 20 character display. A 6502-based unit 4K RAM, expandable. 2. **The NTS/KIM-1**

Microcomputer A single board unit with 6 digit LED display and on-board 24 key hexadecimal calculator-type keyboard. A 6502 based microcomputer with 1K RAM, expandable.

3. **The NTS/HEATH H-89 Microcomputer** features floppy disk storage, "smart" video terminal, two Z80 micro-processors, 16K RAM memory, expandable to 48K. 4. **The NTS/HEATH GR-2001 Digital Color TV (25" diagonal)** features specialized AGC-SYNC muting, filtered color and new solid-state high voltage tripler rectifier.

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 South Figueroa St., Los Angeles, Calif. 90037

**NO OBLIGATION. NO SALESMAN WILL CALL.
APPROVED FOR VETERAN TRAINING.**

NTS Training Programs
in Consumer and
Industrial Electronics



NATIONAL TECHNICAL SCHOOLS

4000 South Figueroa Street, Dept. 206-020
Los Angeles, California 90037

Please rush FREE color catalog on course checked below

- | | |
|---|--|
| <input type="checkbox"/> MicroComputers/MicroProcessors | <input type="checkbox"/> Audio Electronics |
| <input type="checkbox"/> Communications Electronics | <input type="checkbox"/> Auto Mechanics |
| <input type="checkbox"/> Digital Electronics | <input type="checkbox"/> Air Conditioning |
| <input type="checkbox"/> Color TV Servicing | <input type="checkbox"/> Home Appliances |

Name _____ Age _____


Address _____

Apt. _____ City _____

State _____, Zip _____

- Check if interested in G.I. information.
 Check if interested ONLY in classroom training in Los Angeles.

Function Generator Kit

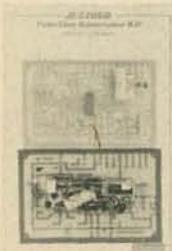

Provides three basic waveforms: sine, triangle and square wave. Frequency range from 1 Hz to 100K Hz. Output amplitude from 0 volts to over 6 volts (peak to peak). Uses a 12V supply or a $\pm 6V$ split supply. Includes chip, P.C. Board, components & instructions.

JE2206B \$19.95

Digital Thermometer Kit



Dual sensors — switching control for indoor/outdoor or dual monitoring. Continuous LED .8" ht. display. Range: $-40^{\circ}F$ to $199^{\circ}F$ / $-40^{\circ}C$ to $100^{\circ}C$. Accuracy $\pm 1^{\circ}$ nominal. Set for Fahrenheit or Celsius. Simulated walnut case. AC wall adapter included. Size: $3\frac{1}{4}''$ h x $6-5/8''$ w x $1-3/8''$ d.

JE300 \$39.95

Digital Stopwatch Kit




Use Intersil 7205 Chip. Plated thru double-sided P.C. Board. Red LED display. Times to 59 minutes, 59.99 seconds with auto reset. Quartz crystal controlled. Three stopwatches in one: single event, split (cumulative) and taylor (sequential timing). Uses 3 penlite batteries.

Size: $4.5''$ x $2.15''$ x $.90''$

JE900 \$39.95

4-Digit Clock Kit

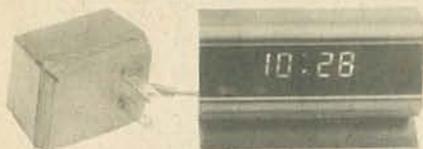

Bright .357" ht. red display. Sequential flashing colon. 12 or 24 hour operation. Black extruded aluminum case. Pressure switches for hours, minutes and hold functions. Includes all components, case and wall transformer. Size: $3\frac{1}{4}''$ x $1\frac{1}{4}''$

JE730 \$14.95

6-Digit Clock Kit



Bright .300 ht. common cathode display. Uses MM-5314 clock chip. Switches for hours, minutes and hold functions. Hours easily viewable to 20 ft. Simulated walnut case. 115VAC operation. 12 or 24 hour operation. Includes all components, case and wall transformer. Size: $6\frac{1}{2}''$ x $3-1/8''$ x $1\frac{1}{4}''$

JE701 \$19.95


Jumbo 6-Digit Clock Kit



Four .630" ht. and two .300" ht. comm. anode displays. Uses MM5314 clock chip. Switches for hrs., mins., and hold functions. Hours viewable to 30 ft. Sim. walnut case. 115VAC operation. 12 or 24 hour operation. Incl. all components, case and wall transformer. Size: $6\frac{1}{2}''$ x $3-1/8''$ x $1\frac{1}{4}''$

JE747 \$29.95

Regulated Power Supply Kit

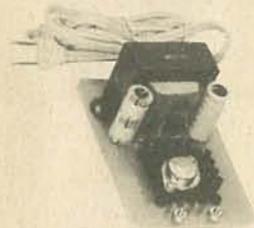

Uses LM309K. Heat sink provided. PC board construction. Provides solid 1 amp @ 5 volts. Includes components, hardware & instructions. Size: $3\frac{1}{2}''$ x $5''$ x $2\frac{1}{2}''$ h

JE200 \$14.95


Multi-Voltage Board Kit



ADAPTS TO JE200 SUPPLIES $\pm 5V$, $\pm 9V$ and $\pm 12V$ Independent load rating at single terminal. $\pm 12V$: 160mA, $\pm 9V$: 200 mA, $-5V$: 250mA. DC/DC converter with +5V input. Toroidal hi-speed switching XMFR. Short circuit protection. PC board construction. Piggy-back to JE200 board. Size: $3\frac{1}{2}''$ x $2''$ x $9/16''$ h

JE205 \$12.95

Variable Power Supply Kit

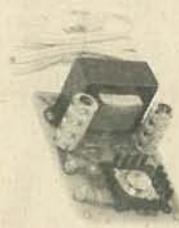

Full 1.5 amp @ 5-10V output. Up to .5 amp @ 15V output. Heavy duty transformer. Three-terminal I.C. voltage regulator. Heat sink provided for cooling efficiency. PC board construction. 120VAC input. Size: $3\frac{1}{2}''$ x $5''$ x $2\frac{1}{2}''$ h

JE210 \$19.95


62-Key ASCII Encoded Keyboard Kit



The JE610 ASCII KEYBOARD KIT can be interfaced into most any computer system. The JE610 kit comes complete with an industrial grade keyboard switch assembly (62-keys), IC's, sockets, connector, electronic components and a double-sided printed wiring board. The keyboard assembly requires +5V @ 150mA and $-12V$ @ 10mA for operation. Features: 60 keys generate the full 128 characters, upper and lower case ASCII set. Fully buffered. Two user-define keys provided for custom applications. Caps lock for upper case-only alpha characters. Utilizes a 2376 (40-pin) encoder read-only memory chip. Outputs directly compatible with TTL/DTL or MOS logic arrays. Easy interfacing with a 16-pin dip or 18-pin edge connector.

JE610 \$79.95

Hexadecimal Encoder Kit

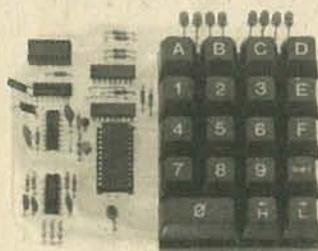

FULL 8-BIT LATCHED OUTPUT — 19-KEY KEYBOARD

The JE600 ENCODER KEYBOARD provides two separate hexadecimal digits produced from sequential key entries to allow direct programming for 8-bit microprocessor or 8-bit memory circuits. Three (3) additional keys are provided for user operations with one having a bistable output available. The outputs are latched and monitored with 9 LED readouts. Also included is a key entry strobe. Features: Full 8-bit latched output for microprocessor use. Three user-define keys with one being bistable operation. Debounce circuit provided for all 19 keys. 9 LED readouts to verify entries. Easy interfacing with standard 16-pin IC connector. Only +5VDC required for operation.

JE600 \$59.95

(Prices Subject To Change)

CIRCLE 17 ON FREE INFORMATION CARD

Jim-pak[®] electronic components

One-Stop Component Center AUTHORIZED DISTRIBUTORS


ALABAMA Cropwell Huntsville Mobile ALASKA Anchorage Anchorage ARIZONA Flagstaff Sierra Vista Yuma ARKANSAS Little Rock CALIFORNIA Anaheim Azusa Bellflower Berkeley Brea Buena Park Buena Park Chula Vista Cypress Davis El Monte Fontana Fresno Glendale Harbor City Hawaiian Gardens Hollywood La Habra Lancaster Long Beach Mission Viejo Modesto Modesto Monterey Morro Bay National City Oceanside Oxnard Palmdale Palo Alto Palo Alto Pasadena Paso Robles Redding Sacramento Sacramento Salinas San Carlos San Diego San Diego San Fernando San Francisco San Jose San Jose San Luis Obispo San Rafael Santa Barbara Santa Cruz Santa Fe Springs Santa Maria Santa Rosa South Lake Tahoe Suisun City Sunnyvale Torrance Torrance Vacaville Vallejo Van Nuys Walnut Creek Westminster Whittier Whittier COLORADO Aurora Colorado Springs Denver Denver CONNECTICUT Avon Bridgeport Milford New Haven Westport DELAWARE New Castle FLORIDA Ft. Lauderdale Gainesville Hialeah Lakeland Lakeland Miami Miami Oakland Park Orlando Panama City Pensacola Tampa Tampa	Tucker Bros. Industrial Electronic Supply Lafayette Radio Electronics The Electronic Company TV Mart Jim's Audio & Stereo Repair B & S Electronics Yuma Electronics Southern Electronics Company Heathkit Electronic Center Amco Electronics Earl's Hobby Shop Al Lasher Electronics Century Electronics Ford Electronics S.J. Electronics Lion Electronics SCR Electronics Paradyne Consumer Electronics Kimball & Stark Fontana Electronics Sparky Electronics Eagle Electronics Buff's Electronics Carson Electronics Pacific Radio Exchange A.B.C. Electronics Consumer Electronics Scott Radio Supply Inc. Tower Electronics Corp. Computer Magic Pacific Radio Zackit Coast Electronics Willy's Electronics Electronic Center Dow Radio Radio Shack A.S.C. Palmdale U.S. Electronics Zack Electronics Dow Radio Inc. Mission Electronics Radio Mart Heathkit Electronic Center Zackit Salinas Radio J&H Outlet Store Radio Shack A.S.C. Mira Mesa Byte Shop San Fernando Electronics Zack Electronics Peninsula Electronic Supply Inc. United Radio & TV Supply Mid-State Electronic Supply Electronics Plus Lombard Electronics Santa Cruz Electronics Industrial Electronics Cap's Communications Electronics Inc. CalPine Electronics Byte Shop Sunnyvale Electronics SE Electronics Inc. Torrance Electronics D.C. Electronics Zackit Thrifty Electronics Supply Inc. MicroSun Computer Center JK Electronics D & S Electronics Whittier Electronics Company Aurora Electronics Centennial Electronics Inc. Amptec Inc. Mt. Coin Distributing Co. Heathkit Electronic Center Bridgeport Computer Daz Electronics Customized Computer Systems Computerworks Delaware Amateur Supply Computers For You Lafayette Radio Heathkit Electronic Center Lakeland Specialty Electronics Herman Electronics N & G Distributors Lafayette Radio Southeast Micro-Data Corp. Bay-Mar Electronics Inc. Grice Electronics Inc. AMF Electronics Microcomputer Systems	GEORGIA Atlanta Atlanta Columbus Stone Mountain HAWAII Aiea Honolulu IDAHO Boise Caldwell ILLINOIS Carbondale Decatur Evanston Groveland Mount Prospect Niles Normal Peoria Peoria Rockford Schaumburg Skokie Villa Park INDIANA East Chicago Evansville Gary IOWA Ames Clinton Davenport Des Moines Des Moines KANSAS Hutchinson Kansas City Mission Salina Wichita KENTUCKY Lexington Louisville Louisville Richmond LOUISIANA Baton Rouge Baton Rouge Baton Rouge Houma Lake Charles Metairie New Orleans MARYLAND Annapolis Baltimore Baltimore Baltimore Baltimore Churchville Damasus Frederick Glen Burnie Hagerstown La Vale Rockville Rockville Silver Spring Towson Towson Towson Towson	Atlanta Computer Mart CompuShop Radio Wholesale Coleman's Electronics Delcoms Hawaii Integrated Circuit Supply Custom Electronics A-Gem Supply Inc. Picks Electronics Main Street Computer Co. Tri-State Electronic Corp. Moyer Electronics Tri-State Electronic Corp. Computer Land B-N Computer Works Computer Land of Peoria Warren Radio Co. Computer Store of Rockford Data Domain of Schaumburg Liliput Computer Melvin Electronics Acro Electronics Corp. Hutch & Son Inc. Calumet Electronic Supply Electronic Supply Inc. Bridge Electronics Computer Center Memory Bank Gifford Brown Incorporated Radio Trade Supply Co. Hutchinson Electronics Electronic Surplus Sales Heathkit Electronic Center Electronics Inc. Amateur Radio Equipment Co. Radio Electronic Equipment Co. Peerless Electronic Equipment Co. Madison County Electronics Davis Electronics Supply Co. Menard Electronics Inc. Pelican Electronics Pelican Electronics Pelican Electronics Wm. B. Allen Supply Co. J & M Electronics Inc. American Distributing Co. Everything Electronic Harco Electronics Tritronics Inc. Churchville Electronics Damasus CB Frederick Computer Products Inc. Revacto Custom Computing Inc. J & M Electronics Computer Workshop Heathkit Electronic Center Computers Etc. Bayneville Electronic Inc. Computers, Etc. Computers Unlimited Heathkit Electronic Center Heathkit Electronic Center Pittsfield Radio Co. Inc. Computer Mart Inc. Heathkit Electronic Center RM Electronics Inc. E & B Electronics Inc. Lafayette Radio Ann Arbor Ann Arbor Bay City Canton Clawson Detroit East Detroit East Lansing Flint Flint Garden City Grand Rapids Grand Rapids Grand Rapids Jackson Lansing Livonia Livonia Midland Milan Muskegon Niles Oak Park	MICHIGAN (Continued) Pontiac Port Huron Saginaw St. Clair Shores Sterling Heights Traverse City Traverse City MINNESOTA Duluth Hopkins Minneapolis St. Paul Winona MISSOURI Bridgeton El Dorado Springs Florissant MONTANA Billings Bozeman Great Falls NEBRASKA Lincoln Lincoln North Platte Omaha Omaha NEVADA Las Vegas NEW JERSEY Cherry Hill Fair Lawn Ocean Pennsauken Pompton Lakes Ramsey Vineland NEW MEXICO Farmington NEW YORK Albany Albany Albany Bloomington Buffalo Carland Endwell Ithaca Jamestown Kingston Kingston Kingston Middletown Newburgh New York New York Orchard Park Peekskill Poughkeepsie North White Plains Rensselaer Rochester Troy Utica Vestal Wappingers Falls White Plains NORTH CAROLINA Greenville Morehead City Raleigh NORTH DAKOTA Fargo Fargo OHIO Cincinnati Cincinnati Cincinnati Columbus Reynoldsburg Toledo Toledo Wickliffe Youngstown OKLAHOMA Oklahoma City Oklahoma City Oklahoma City Tulsa OREGON Albany Beaverton Corvallis Eugene Gresham Portland Salem Salem PENNSYLVANIA Bradock Chambersburg Drexel Hill Drums Erie Paoli Electronic Supply Main TV Radio Electronics Inc. Electronic Mart Bell Electronics Lafayette Radio Traverse City Electronic Supply Northwest Radio of Duluth Inc. Heathkit Electronic Center Pal Electronics Heathkit Electronic Center Hiawatha Electronics Inc. Forsythe Computers Beckman Electronics Computer Country Conley Radio Supply Electronic Service & Distributing Inc. Arts Electronics Altair Computer Center Scott Electronic Supply Inc. Scott Electronic Supply Corp. Heathkit Electronic Center Omaha Computer Store Century 23 The Computer Emporium Heathkit Electronic Center Heathkit Electronic Center Lafayette Radio Computer Corner Typetronic Computer Store Lafayette Radio Electronics Micro-Computer Service Fort Orange Electronics Action Audio Inc. Greylock Electronics Stansifer Radio Co. Inc. Radio Equipment Corp. Action Audio Inc. Computer Tree Inc. Action Audio Inc. Warren Radio Heathkit Electronic Center Action Audio Inc. Greylock Electronics Action Audio Inc. Action Audio Inc. Aristo Craft Manhattan Equipment Corp. Radio Equipment Corp. Action Audio Inc. Greylock Electronics Heathkit Electronic Center Com-Tech Electronics Heathkit Electronic Center Trojan Electronics Am-Com Electronics Harvey Electronics Action Audio Inc. The Computer Corner Pair Electronics Baer Electronic Systems Byte Shop of Raleigh The Computer Company S & S Electronics Mead Electronics Heathkit Electronic Center Heathkit Electronic Center Universal Amateur Radio Heathkit Electronic Center Amateur Electronic Supply Ross Radio Company Bits, Bytes & Micros Heathkit Electronic Center Trice Wholesale Electronics High Technology Oregon Ham Sales Norvac Electronics Zero-Gee Books Eugene Amateur Radio Supply Miller Electronics Portland Radio Supply Comm-Shack Computer Pathways Leff Electronics Sunrise Electronic Distributing Kass Electronics Distributors Mr. D's Digital Electronics Warren Radio Personal Computer Corporation	PENNSYLVANIA (Continued) Philadelphia Philadelphia Phoenixville Pittsburgh Pittsburgh Wilkes Barre York RHODE ISLAND Cranston Pawtucket Warwick TENNESSEE Clarksville Cookeville Nashville Nashville Knoxville Memphis Memphis Memphis Nashville Oakridge Tullahoma TEXAS Beaumont Dallas Dallas Dallas Fort Worth Houston McAllen McAllen San Antonio San Antonio UTAH Midvale Provo Salt Lake City Salt Lake City VERMONT Essex Junction VIRGINIA Alexandria Alexandria Arlington Blacksburg Charlottesville Colonial Heights Falls Church Hampton McLean Norfolk Norfolk Portsmouth Richmond Vienna Virginia Beach Warrington WASHINGTON Bellevue Everett Kennewick Longview Moses Lake Pasco Richland Seattle Seattle Seattle Spokane Tacoma Tacoma WEST VIRGINIA Morgantown Morgantown Wheeling WISCONSIN West Allis Heathkit Electronic Center Resco Electronics (Market St.) Stevens Electronics Heathkit Electronic Center Tydings Company Hamline Electronics G.Y.C. Company Jabbour Electronics City Jabbour Electronics City Heathkit Electronic Center Masstronics Wagnon's Stereo Center Electra Distributing Co. Shields Electronics Supply Inc. Bluff City Electronics Sare-Rose & Spencer Electronics Warren Radio Company Eddie Warner's Parts Company National Electronics H & H Electronics Co. Inc. Electro-Hut CompuShop Heathkit Electronic Center Ram Micro Systems The Ingenuity Concept Interactive Computers Broadway Electronics Carlos Franco Electronics Appliance & Equipment Co. Sherman Electronics Supply Inc. Heathkit Electronic Center Alpine Electronic Supply Co. Best Distributing Computerland of Salt Lake Lafayette Radio Computers Plus Inc. Heathkit Electronic Center Arlington Electronic Wholesalers Scotty's Radio & TV Inc. Graves Electronics Southside Radio Comm. Crossroad Electronics Electronic Sales Inc. Tyson's Computer Emporium Avec Electronics Corp. Norfolk Priest Electronics Electronics Unlimited Avec Electronics Corp. Electronic Equipment Bank Heathkit Electronic Center Radio Shack ABC Communications ABC Communications C & J Electronics Inc. Progress Electronics Ron's Electronics Riverview Electronics C & J Electronics ABC Communications Amateur Radio Supply Empire Electronics Personal Computers C & G Electronics Northwest Radio Supply The Computer Corner Electro Distributing Co. Inc. Lafayette Radio Associate Store Olson Electronics CompuShop Alberta Ltd. Elwest Technical Services Ltd. CompuShop House of Computers NewBear Computing Store Marianas Electronics Sonitel, S.A. Tropelco, S.A. Applied Digital System Inter-Trade (P.T.E.) Ltd. Sys-Tech LSI Electronics HB Interkomponent The Hobby Centre
---	--	--	--	--	---

For Distributor Information, write or phone JIM-PAK[®] 1355 Shoreway Road, Belmont, CA 94002 (415) 592-8097

NEW and UNIQUE—

A big cookbook collection of every calculation you need in electronics

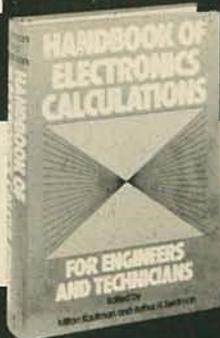440 problems and solutions plus 725 illustrations connect you with the right answers in all your analog and digital circuit work!



HANDBOOK OF ELECTRONICS CALCULATIONS FOR ENGINEERS AND TECHNICIANS

Edited by Milton Kaufman, Pres., Electronic Writers and Editors, Inc., and Arthur H. Seidman, Prof., Electrical Engineering, Pratt Institute

653 pages 725 illustrations \$24.50

In true *everything-you-need-to-know* style, this new and unique master catalog of calculations covers virtually every important topic in every important discipline in the field—from microprocessors, communications systems, and operational amplifiers to active filters, microwaves, thick-film technology, and computer-aided circuit design!

75% of the book is specific problems and their solutions (440 in all), and 25% is simple explanation of these solutions. All put together in the most immediately useful, logical, and complete form possible.

Its 653 pages and 24 chapters—all written by experts—add up to an invaluable problem-solving, time-saving reference for all around, everyday, on-the-job use.

OTHER IMPORTANT NEW BOOKS IN YOUR FIELD

HANDBOOK FOR ELECTRONICS ENGINEERING TECHNICIANS

Edited by Milton Kaufman and Arthur H. Seidman. Perry J. Sheneman, Associate Editor.

A quick, reliable guide to the latest methods, materials, applications, and data. 560 pp., 695 illus., \$25.50

ELECTRONIC GAMES

By Walter H. Buchsbaum and Robert Mauro.

All the current technical know-how you need to design, program, and troubleshoot electronic games. 335 pp., illus., \$17.50

PERSONAL COMPUTING: Hardware and Software Basics

Electronics Book Series.

A veritable smorgasbord of languages, programming, and applications basics for popular personal-computer microprocessor chips. 226 pp., illus., \$14.95

Available at your local bookseller, or—use this coupon for

FREE 15-DAY EXAMINATION

McGraw-Hill Book Company
P.O. Box 400, Hightstown, New Jersey 08520



Please send me the book(s) checked for 15 days on approval. At the end of that time I will remit for the book(s) I keep, plus local tax, postage and handling, and return the unwanted book(s) postpaid.

- Kaufman & Seidman: Handbook of Electronics Calculations (33392-0) \$24.50
- Kaufman & Seidman: Handbook for Electronics Engineering Technicians (33401-3) \$25.50
- Buchsbaum & Mauro: Electronic Games (08721-0) \$17.50
- Electronics Book Series: Personal Computing (19151-4) \$14.95

Name _____

Street _____

City _____ State _____ Zip _____

This order subject to acceptance by McGraw-Hill

SAVE MONEY—Remit in full with this order, plus local tax, and McGraw-Hill pays all regular postage and handling costs. Return books in 15 days for full refund if not completely satisfied.

Offer good only in the U.S. and Canada

23-A583-4276-3

SERVICE CLINIC

continued from page 71

replaced it just for luck. This fixed it. The "rest" of the circuit, the part we didn't see or think of, is shown in Fig. 2. This resistor is evidently in the high voltage beam-current circuitry; so, it has a very definite affect on its operation. There's the Alfred Hitchcock ending. We were really very happy to find it.

The moral is this. If you have a stage that controls something else, and its parts are all good, then stop suspecting the controller, and suspect the circuit that controls the controller. In other words, the voltage or current or frequency that operates the control circuitry! This applies to a lot of stages! **R-E**

service questions

TRANSISTOR BLOWS

The horizontal-output transistor was blown in this Sylvania EO-2. I replaced it, and now the horizontal driver runs very hot and the output takes far too much current. Do you have anything in your files on this?—W. G., Mena, AR.

Oddly enough, yes! Check C428, the coupling capacitor into the horizontal-output transistor. If this capacitor is leaky or shorted, that will do it. While you're at it, also check Q500 in the DC voltage-regulator circuit; if this is leaky, the excessively high voltage on the +160-volt line will also cause troubles.

VOLTAGE REGULATOR

Help! After 20 years of TV service I finally ran into one that has me baffled. This Panasonic model T-124A (made for J.C. Penney) works fine at 70 volts AC, but at 90-110 VAC it blows the horizontal-output transistor. I tried using several transistors with higher breakdown ratings, but they went too.—G. S., Brookfield, WI.

I think we have a very good clue here. If the set works (safely) at a greatly reduced line voltage and blows things at normal voltage, the most likely thing would be a regulator problem.

Check the +105-volt source with a reduced line voltage. Run the line voltage up until this voltage reads exactly +105. Now very carefully increase the line voltage. If this +105 volts goes UP, watch out!

This indicates that the voltage regulator is not working at all. Raise the supply voltage and you raise everything in the high-voltage stage. The most likely cause is a shorted pass transistor.

SOLID-STATE TROUBLES

Have I got a tough dog. It's a solid-state black-and-white TV set, and I'm not familiar with solid-state sets. I get the full B+ voltage of +163 at all test points in this circuit. There's no high voltage and no low voltages. Can you help?—T. S., Everett, MA.

Stand by for an instant course in solid-state troubleshooting. Your readings show the B+ voltage supply is normal, but it is obviously drawing no current at all. Check the horizontal-output transistor with an ohmmeter. With the positive lead to the base, you should get a low resistance reading to both base and collector. Reverse the leads and put the negative lead to the base; you should get a high reading on collector and base. I strongly suspect the transistor (an NPN) is open.

If so, check ALL the loads on the flyback, including the rectifier diode that develops these voltages for the transistor circuits. Before you turn the set on after replacing the output transistor, plug it into a variable voltage transformer. Place the current meter in series with the B+ voltage, and a DC voltmeter across it. Bring the voltage up slowly and watch for any excess current drain. If you see it, stop and fix it! **R-E**

Sony Wrote the Book on VTR— Now It's on Tape!

Until now, learning about video recorders meant poring over very technical textbooks—if you could find them. Or enrolling in a highly specialized school.

But with the new Sony Basic Video Recording Course, you can easily learn everything about video tape recording using video itself as a teaching tool. At your own pace, whenever it's most convenient for you. The Sony course clearly demonstrates the theory, operation and characteristics of every major VTR unit. Including EIAJ, Betamax, VHS, U-matic, Quad and SMPTE Types A, B and C.

You'll learn everything from the fundamentals of magnetism to the sophisticated processes used in color recording. And at the end of each lesson you'll find a thorough self-review test, so you can be sure you fully understand each subject before going on to the next one.

You can order a preview tape, individual tapes on a specific subject or the entire course in Betamax or U-matic format.

COURSE CONTENTS:

The course consists of eight color video cassettes ranging from 23 to 30 minutes in length and eight supplementary booklets:

1. ELEMENTS OF MAGNETIC RECORDING, 2. VIDEO RECORDING, 3. SCANNER SYSTEMS, 4. TAPE FORMATS, 5. TAPE TRANSPORTS, 6. SCANNER SERVOS, 7. LUMINANCE PROCESSING, 8. COLOR SIGNAL PROCESSING.

The Sony Basic Video Recording Course will make you an expert on video tape recording. Whether you already own, sell or service video equipment or just have an electronics background and want to understand how it really works—this course is what you've been waiting for.

It would be hard to find a better teacher than the leader in the field—SONY.



Sony Basic Video Recording Course

I'm interested in learning VTR technology. Please send me:

BASIC VIDEO RECORDING COURSE

(8 cassettes/booklets, customized album and binder supplied)

Betamax 1 hr. 2 hr. \$395.00

(Reg. price \$503.00)

3/4" U-matic \$487.00

These prices available for limited time only. (Reg. price \$623.00)

INDIVIDUAL LESSONS

(Price per cassette/booklet)

Betamax 1 hr. 2 hr. \$61.00

3/4" U-matic \$76.00

Circle lesson # and indicate quantity desired in space provided.

1 __, 2 __, 3 __, 4 __, 5 __, 6 __, 7 __, 8 __,

PREVIEW TAPE

Betamax 1 hr. 2 hr. \$12.50

U-matic \$28.00

Add appropriate sales tax and \$1.75 per cassette (\$14.00 for complete course) for handling and shipping. (UPS in continental U.S. If outside, add \$15.00 for export charges, plus collect freight charges; special handling is extra.) Make check or money order payable to Sony Corporation. If charging to your Sony account, fill in number and enclose purchase order.

For phone orders, call: (213) 537-4300 Ext. 474 or visit your local Sony dealer.

We honor VISA or Master Charge via phone or mail.

Name _____

Address _____

City _____ State _____

Zip Code _____ Phone # _____



VISA/Master Charge Number _____

Exp. Date _____

Signature _____

Mail to: Sony Video Products Company, Tape Production Services, 700 W. Artesia Blvd., Compton, California 90220.


NOTE: Tapes returnable if defective when received. Please allow two weeks for delivery.

SONY VIDEO COMMUNICATIONS

Sony, Betamax and U-matic are registered trademarks of the Sony Corp.

Three supplies in one

the auto-tracking B&K-PRECISION 1650

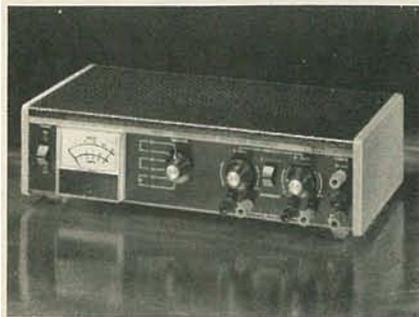

Model 1650 \$300

- Functions as three separate power supplies
- 5V DC, 5A fixed output
- Two separate (A and B) 0 to 25VDC outputs at 0.5A
- B supply can be set to track A supply directly or in any ratio from 0 to 100%
- All terminals are fully isolated in all modes
- Outputs may be connected in series or parallel
- Fully automatic, current limited overload protection

The B&K-PRECISION 1650 was designed to fill your bench power needs for both linear and digital circuitry. The exclusive opto-isolator controlled automatic tracking circuit allows the B output to precisely track voltage changes of the A supply, while maintaining complete electrical isolation.

Available for immediate delivery at your local B&K-PRECISION distributor.

B&K PRECISION

DYNASCAN CORPORATION

6460 West Cortland Street
Chicago, Illinois 60635 • 312/889-9087

In Canada: Atlas Electronics, Ontario
Int'l. Sls: Empire Exp., 270 Newtown Rd., Plainville, L.I., NY 11803

CIRCLE 43 ON FREE INFORMATION CARD

SWITCHING REGULATOR

continued from page 60

crease the output current is to increase the core volume of the inductor (larger pot core). When attempting to achieve higher currents, the drive circuitry to the switching transistor may have to be replaced with devices that provide more base drive to the BU407 (Q1). Recommended replacement for the 2N3638A (Q2, Fig. 5) is a 2N2905A; Q3, a 2N2222A is useful as it is. Reduce R9 to 510 ohms and the four 2.2-ohm sense resistors should be replaced with an equivalent resistance of .1 ohm.

The step-up configuration (Fig. 4) is designed for approximately 24 volts output. This can be altered by replacing R5 (20K) with another value resistor (or potentiometer). The output changes about 1 volt for every 1000-ohm change in R5.

The step-down configuration (Fig. 5) has a nominal output of about 3.75 volts. This value can be raised by replacing the jumper wire shown at the output with a resistor. The output voltage will increase beyond the point where the output voltage is within 5 volts of the input voltage.

When investigating the inverting mode (Fig. 6), the polarity of C2 must be reversed from the other modes.

TABLE 2

Step Down

Short: B,C,G,H,J,L,M,T,U

Step Up

Short: A,D,I,K,N,O,P,Q,S,W

Inverting

Short: B,C,G,H,J,L,M,R,V

Note that R14 is 360K for this configuration. In the two other modes it is called R4 and is 3.6K.

Table 2 shows which jumpers need to be installed to create step-up, step-down, or inverting output. These links are shown in the component layout diagram of Fig. 7.

All holes on the board not relieved by artwork should have the wire soldered to both top and bottom sides. Components with grounded ends have holes for this purpose. Be sure to solder to the top side ground plane. Complete artwork for the double sided PC board is provided in Figs. 8 and 9. If the modulation input (pin 5) is not used, solder pins 5 and 6 together.

The 3C8 ferrite material used in the pot core for L1 is quite brittle so take care not to drop the parts because they will shatter. Also when mounting the core be sure not to overtighten the mounting screw as that, too, could be the cause of an unpleasant cracking problem. **R-E**

★ **FREE!** ★



NEW CATALOG OF HARD-TO-FIND PRECISION TOOLS

Jensen's new catalog is jam-packed with more than 2000 quality items. Your single source for hard-to-find precision tools used by electronic technicians, scientists, engineers, instrument mechanics, schools, laboratories and government agencies. This popular catalog also contains Jensen's world-famous line of more than 40 tool kits. Send for your free copy today!

JENSEN TOOLS INC.

1230 S PRIEST DR. TEMPE, AZ 85281

CIRCLE 7 ON FREE INFORMATION CARD

BIG 2 1/2" DISPLAY!



SOLID STATE CLOCK/CALENDAR KIT

0101 Displays time of day, date or alternate between both automatically. May be connected to 8 ohm speaker for alarm clock. Operates from 120 VAC 60 Hz.

\$49.95 Walnut case extra, \$24.95

AUTO CLOCK CALENDAR KIT




\$29.95
\$39.95 assembled

0106 Displays either hours and minutes, month and day, or seconds. Requires only 2 mA of current while ignition is off. Also operates on 9V battery. Mounts easily in compact two-inch enclosure (Not included)

UNIVERSAL DESIGNER KIT

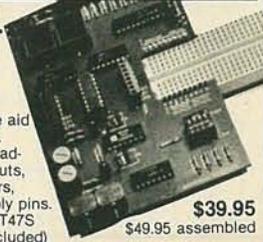6100 Indispensable aid to digital IC design. 2 pushbuttons, 2 read-outs, 4 switch outputs, 8 LEDs, 2 generators, 2 counters, 5V supply pins. Shown with CSC QT47S Breadboard (not included)



\$39.95
\$49.95 assembled

SEND FOR
FREE
8-PAGE
CATALOG

Add \$2.50 per order postage and handling.



PACCOM

14905 N.E. 40th Street, R-2
Redmond, WA 98052 (206) 883-9200

CIRCLE 24 ON FREE INFORMATION CARD

LEVEL METER

continued from page 46

output, and adjust R2 and R16 until the highest LED lights up at half its maximum brightness.

To use the PLM as a clipping indicator, disconnect your speakers from your amplifier while leaving the PLM connected to the output. Dial your tuner to an FM rock station (these are usually the most compressed and limited stations) and turn your volume control all the way up. Adjust R2 and R16 until the highest LED just barely lights up. Then turn them higher by about 20% of the total angle they have been turned. When you reconnect your speakers, the highest LED will represent transient clipping of your amplifier.

When using the PLM with a vacuum-tube amplifier, always connect a load of approximately the right value (8 ohms for example) across the output in the first calibration technique. Vacuum-tube amplifiers are not safe to use without a load, and full-power sinewave testing with speakers connected isn't good either for the speakers or your ears! The second calibration procedure isn't of much use with vacuum-tube amplifiers, as they clip very differently. This wraps it up. Use and enjoy!

R-E

DIGITAL CLOCK


continued from page 63

the proper time, it displays the time by flashing the digits sequentially through a single seven-segment display. The sequence of digits is: HHxMMxxx where x represents a blanked pause period. (The clock features leading-zero blanking so the sequence can also be: xHxMMxxx)

The three pushbutton switches on the front panel are, from left to right, S1, S2 and S3. Switch S1 is a "freeze" button and will stop the flashing sequence anywhere in its cycle. Switch S2 is the slow-set button and S3 is fast time set.

Upon plugging in the power transformer, the clock comes up in an undefined state and usually flashes two zeros. Pressing S3 for approximately 1 second will toggle the counters and put the clock in a correct timekeeping state. Now the correct time can be set.

This is best done by watching whatever time is currently sequencing so you can identify the first hour digit and anticipate when it will flash again on the next cycle. By depressing S1 at just the right instant, you can "capture" the hour digit in the display and hold it there by continuing to hold down S1. (This may take a few tries for someone who has never set the time before). With the hours digit captured in the display, simultaneously depressing S3 will advance that digit at the rate of 1

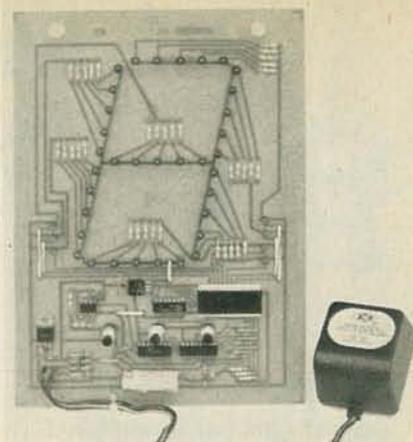


TOP VIEW of the PC board as it appears when the red plastic panel is removed. The six jumpers are clearly visible.

hour per second. When the hours are properly set, release S3 and S1 to continue the flashing cycle. Now S1 is used again, this time to capture the tens of minutes digit. S2 or S3 may be used to advance that digit to the proper setting. Then repeat the procedure once more for the unit minutes, this time using S2 to set that digit.

The procedure is complicated to describe, but with a little practice becomes very simple to do. This clock "grows on you" and attracts lots of attention so you had better be prepared to build others for your friends.

R-E

This chip changed your life.

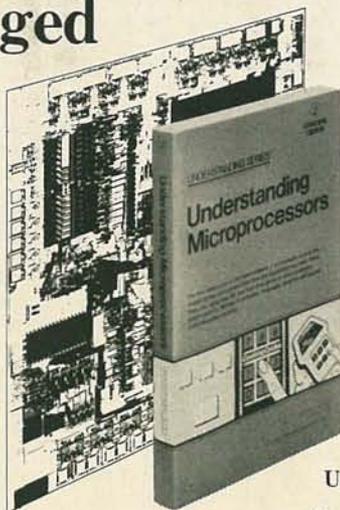

This book tells you how. And why.

Understanding Microprocessors.
From the Texas Instruments Learning Center. 288 pages. \$4.95.


Learn quickly and easily about the explosive impact microprocessors have had on electronics technology.

How the "miracle chip" works to make those things you use everyday — calculators, appliances, microwave ovens, stereos, tv, automobiles — even toys and games — do the remarkable things they do.

Understanding Microprocessors is the latest addition to the Texas Instruments Understanding Series.[™]

All TI Understanding Series books are ideal for those who want to learn about today's technology — without having to devote years to the study.

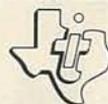Written in bright, clear, down-to-earth language, and fully illustrated, you'll find these books to be invaluable tools for your personal entry into the microelectronics revolution. See coupon for all details.



- LCW8161 **Basic Electricity and DC Circuits** \$19.95
1026 pages. Building blocks for a thorough working knowledge of DC circuits.
- LCB3361 **Understanding Solid-State Electronics** \$3.95
270 pages — New 3rd edition. Individualized approach for learning microelectronic basics.
- LCB3311 **Understanding Digital Electronics** \$3.95
265 pages. The springboard for a look into the fascinating world of today's electronic logic devices, circuits and systems.
- LCB4023 **Understanding Microprocessors** \$4.95
288 pages. For the newcomer to microprocessors. What they are, what they do and how they work.
- LCB3321 **Understanding Calculator Math** \$3.95
224 pages. Unlocks the real power of your handheld calculator — loaded with practical applications.

Add sales tax, except AK, DE, MT, NH, OR.

Mail check or money order to Texas Instruments, P.O. Box 3640, M/S 84, Dallas, Texas 75285.

Orders in Continental U.S. shipped prepaid. Foreign orders: Prepaid in U.S. dollars only. Include shipping costs.

Prices subject to change without notice. RE280

Name _____

Address _____

City _____ State _____ Zip _____

TEXAS INSTRUMENTS
INCORPORATED


BE SWITCHED

EXCLUSIVE SHELDAHL FLEXSWITCH® KIT

Yours for only \$10.00

Put your imagination and a scissors to work to make the switch you want. Modify the .030 thick, non-tactile panel into a water/dust resistant switching module. Kit includes design guidelines, instructions, membrane switching panel, flexcircuit connector, press-on nomenclature and RFQ checklist.

© 1980 Sheldahl, Inc.

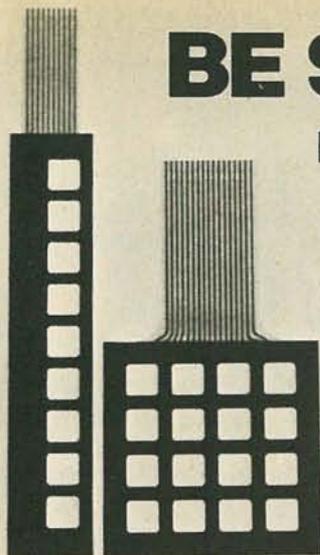

See your local distributor, or order by mail.

Please send me 16 key kit(s) short to ground crosspoint

9 key kit(s) short to ground crosspoint

I enclose \$10 in check or money order for each kit order.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____



Sheldahl

Mail to:
Sheldahl Inc.
Electrical Products Division
P.O. Box 170
Northfield, MN 55057

SOUND QUALITY *continued from page 65*


parallel sound system, the signal-to-noise ratio is improved to better than 50 dB and that when the scene has a predominantly white background with black lettering, the signal-to-noise ratio is still about 40 dB better than in a conventional intercarrier sound system.

Siemens recently announced the TDA 4280 IC, a modified version of the TDA 2840 that includes a video output terminal for feeding video recorders and has electronic record/play switching circuits that can be controlled by voltages developed in the recorder.

We have not found any indication that quasi-parallel sound technology has been adapted, or is even being considered, in the U.S. But, we feel sure that, if this new technique is as good as promised and has no hidden drawbacks, you can expect quasi-parallel sound to be featured in some mid-1980 and later models, particularly now that network TV sound quality has been upgraded and there is a valid reason to improve receivers' sound systems. **R-E**

Have regular medical check-ups.

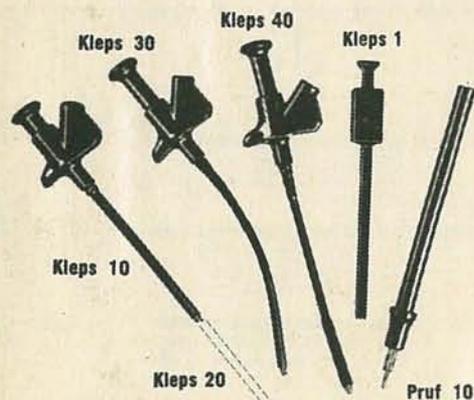American Heart Association
We're Fighting For Your Life



Clever Kleps

Test probes designed by your needs—Push to seize, push to release (all Kleps spring loaded).

Kleps 10. Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4¾" long.

Kleps 20. Same, but 7" long.

Kleps 30. Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long.

Kleps 40. Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or bare lead. 6¾" long.

Kleps 1. Economy Kleps for light line work (not lab quality). Meshing claws. 4½" long.

Prof 10. Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½" long.

Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.



Available through your local distributor, or write to:

RYE INDUSTRIES INC.

128 Spencer Place, Mamaroneck, N.Y. 10543

In Canada: Rye Industries (Canada) Ltd.

CIRCLE 8 ON FREE INFORMATION CARD



How to Get the Most Out of Your Heath® Computer

The Heath Company is the only firm in the computer industry with an exclusive charter to serve the home user and hobbyist. Its plans for the 80s were the subject of a report in the November issue of *Buss: The Independent Newsletter of Heath Co. Computers*. Highlights covered included the future of the H8, the software situation, and a half dozen products planned for the new decade. *Buss* interviewed Heath's new computer product line manager who explained that since the firm's takeover by Zenith: "The ball game has changed and the rules have changed."

How these changes affect users of Heath® computers will be a primary focus of *Buss* in the months ahead. Since April 1977 it has been covering new computer products coming from Benton Harbor. *Buss* is not a company-controlled publication, so it can deal with the weaknesses of Heath® products as well as their strengths. It features news of compatible hardware and software from other vendors. It emphasizes candid accounts of owners' experiences with their systems. Their discoveries save readers headaches—and money. *Buss* also carries hardware modifications developed by readers. It recently offered subscribers plans to convert the H9 to display 24 lines.

Recent issues have included: A program to produce lower case H14 output from upper case H9 input • Microsoft BASIC review • 32K & 64K memory boards for H8 • H89 review • H8 bus expansion • Local users' groups • H11 software notes • Godbout products for H8 • 8080 Assembly Language Learning Program errors • H8 software sources • FOR SALE listings

Between issues *Buss* subscribers have another way of getting up-to-date information: a phone number to call for a recorded bulletin.

Buss is mailed first class (by air mail outside North America). You have the choice of starting with the latest issue or available back issues (about 10). Payment must be in U.S. dollars payable on a U.S. bank. Refund guaranteed if not satisfied.

Issues	U.S. & Canada	Overseas
12	\$ 9.97	\$15.00
18	14.47	20.00
24	17.87	25.00

Buss

325-E Pennsylvania Ave., S.E.
Washington, DC 20003

CIRCLE 56 ON FREE INFORMATION CARD

SAVE \$5

Radio-Electronics

ADAPTIVE NOISE FILTER
No fit-add-on you build!

SATELLITE TV RECEPTION
A new DX circuit

Build your own
AC POLARITY CHECKER
Don't get zapped!

TV ADD-ON GADGETS
Do they really work?

WIRING SYSTEMS
Easy ways to build projects

Build this 40-watt
PRECISION DMM
with true RMS and temperature



PLUS:

New FM Tuner Circuits
2 R.E.A.L. Lab Test Reports
Nobby Corner • Equipment Reports • Service Clinic

AND RECEIVE 2 YEARS OF RADIO-ELECTRONICS AT HOME.

The option is yours! You can have the next 12 or 24 excitement-packed issues of Radio-Electronics delivered to your door each month, and save up to \$5 of the newsstand price while enjoying the convenience of home delivery. And you'll enjoy all the news of electronics you get in Radio-Electronics: projects to build, new-equipment test reports, computer technology, servicing tips, and all your favorite columnists on solid state, hobbies, hi-fi, servicing and computers. Check out the money-saving subscription offers on the coupon below, and check off the one that suits you best. It's the best move you can make today, or for the next three years.

Clip & Save Today

(please print)

Name _____

Address _____

City _____ State _____ ZIP _____

Indicate the offer you prefer:

1 Year—12 issues ONLY \$13.00
(You save \$2.00 off newsstand price.)

2 Years—24 issues ONLY \$25.00
(Save More! \$5.00 off newsstand price.)

Payment enclosed (Send one extra issue)

Bill me

Check here if this is a new subscription.

Check here if you are extending or renewing your subscription.

Extra Shipping: Canada \$3.00 per year, all other countries \$5.00 per year.

Mail to: **Radio Electronics**

SUBSCRIPTION DEPT., P.O. BOX 2520
BOULDER, COLO. 80322 40BO

These rates are not guaranteed after 9 months.

SATELLITE TV continued from page 52

sive protractor can be used when adjusting the tilt angle.

Remember that the spherical can look at signals off boresight ± 20 degrees and with a corresponding repositioning of the focus point antenna you can receive different satellites (or alternately look at more than one satellite simultaneously with multiple feed horns). The same thing is true with the vertical ('tilt') angle. It reciprocates. If at your location the angle of arrival of the incoming signal is 34 degrees and the reflector is vertical (perpendicular to the earth), the focused energy will leave the reflector going down towards the ground at a 34-degree angle as well. Since this would result in your having to point the feedhorn antenna 'up' at the reflector at a 34-degree angle, it might also result in your having to dig a hole in the ground to properly drop the feedhorn-antenna 1.5 times the antenna aperture away from the antenna. The obvious solution is to tilt the antenna back. If the antenna is tilted back 20 degrees (the base stays on the ground, the top tilts backward) then your 34-degree elevation arrival angle will leave the antenna at an angle of 14 degrees ($34-20=14$) with respect to the ground. This will raise the focus point up above ground level and reduce the upward tilt required for the feed antenna. In any case, the same ± 20 -degree reception ability we find true with incoming signals left and right of the boresight line also holds true with the tilt angle. This simply says that you must have your tilt angle at least within 20 degrees of the highest arrival (elevation) angle of the incoming signals. A computer derived chart customized for your location was footnoted in the October 1979 issue. You need one before you can start laying out your antenna!

The feedhorn dimensions are given in Fig. 10. The feedhorn is flanged so as to mount directly to the type WR-229 waveguide flange found on the input side of most LNA's. Study the feedhorn drawing shown in Fig. 10 carefully and the photo in Fig. 11. Material is galvanized sheet metal and accuracy required is ± 0.1 inch.

Note: The preceding material may not prove sufficiently detailed for the novice in this field. The *Swan Spherical TVRO Antenna* manual is some 30 pages in length and provides complete step-by-step instructions for those uncomfortable with the brevity of this quick outline.

Next month we will give details on construction of the LNA (low noise amplifier) plus the VTO 8360 tunable oscillator and GaAs-FET active mixer assembly. **R-E**



endeco soldering & desoldering equipment

SOLDERING IRONS

Pencil style. Safety light. Two heats — 20w and 40w. 6 tips. Unbreakable handle. 2 and 3 wire neoprene cords.

DESOLDERING IRONS

Pencil style. Safety light. Some operate at 40w, idle at 20w. 8 tip sizes. 2 and 3 wire neoprene cords.

SOLDERING & DESOLDERING KITS

Everything needed to solder or desolder or both. All in a handy lifetime metal box with hasp.

See your distributor or write...

Enterprise Development Corp.

5127 E. 65th St. • Indianapolis IN 46220
PHONE (317) 251-1231

CIRCLE 25 ON FREE INFORMATION CARD

NEW FOR THE '80'S FROM BIA PROTEUS I™ PROGRAMMABLE PRESET LEAD SYNTHESIZER

- 2 exponential VCO's with Sync.
 - Noise source
 - 24 dB/octave low pass VCF
 - Wide range LFO
 - Wide range ADSR envelope generator
 - 3 octave digital keyboard
 - 16 programmable presets with ni-cad battery backup
 - Preset data and address port provided.
 - Liberal patch over hardware points
- QUESTIONS? How easy is it to assemble? How powerful and versatile? What are the interfacing details? The PROTEUS USING/ASSEMBLY MANUAL set answers these questions and many more.
Price—\$10.00 refundable with purchase.



No. 8750 PROTEUS KIT \$399.00;
Assembled \$499.00
(shipped freight collect)

- () Send the 8750 Kit, \$399.00 enclosed.
- () Send the 8750 assembled, \$499 enclosed.
- () TELL ME MORE, send the 8750 Assembly & Using manual, \$10 enclosed.
- () Send FREE Catalog.

Name: _____

Address: _____

City: _____ State: _____ Zip: _____

BIA Electronics Dept. 2-R, 1020 W. Wilshire
Okla. City, OK 73116

CIRCLE 60 ON FREE INFORMATION CARD

FEBRUARY 1980

new products

More information on new products is available. Use the Free Information Card inside the back cover.

DIGITAL METER, model LC53, the "Z Meter", is a fully autoranged tester that checks capacitors and inductors for value and performance ability. Capacitor values are checked from 1 pF to




CIRCLE 151 ON FREE INFORMATION CARD

200,000 μ F with 1% accuracy; inductor values are checked from 1.0 μ H to 10 H with 2% accuracy. A leakage test measures capacitor leakage to 10,000 μ A in 12 voltage steps. Capacitors are

automatically discharged after the test. The test also detects dielectric absorption and deformed capacitors, which can then be reformed by the power supply. Inductors are checked for quality by a test that detects faulty coils. The unit can also check rectifiers and detect breakage in transmission lines. Price is \$695.—Sencore, Inc., 3200 Sencore Dr., Sioux Falls, SD 57107.

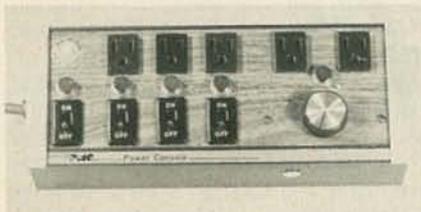MULTIPLE OUTLET BOXES, is a line of 8 Underwriters Laboratories' listed models, some with special features. These lightweight aluminum units all have 5 or 9 receptacles, 15-amp circuit breakers, AC on/off switches, and indicator



CIRCLE 152 ON FREE INFORMATION CARD

lights. Two models feature surge suppressors that can absorb excess energy above 130 volts RMS, and one model has AC motor speed control for devices up to 6 amps. A fourth unit has a light dimmer that can control lamps up to 600 watts. All models include a 6-foot line cord and can be mounted anywhere. Prices range from \$28.50 to \$74.50.—PMC Industries, Inc., 1043 Santa Florencia, Solana Beach, CA 92075.

DIGITAL RESISTANCE SUBSTITUTER, model RS-200 R-Box, provides fast, error-proof method of setting resistance from 0 ohm to 9 megohms. The unit uses 7 color-coded thumbwheel switches to dial in the desired resistance available across two banana-jack binding posts; the resistors used are 1% tolerance, 1/2-watt rated and



CIRCLE 153 ON FREE INFORMATION CARD

serially tied. The *model RS-200* comes in a rugged high-impact plastic case and measures 3¹⁵/₆₄ × 3³/₃₂ × 2¹¹/₆₄-inches. Suggested retail price: *model RS-200*, \$89.95.—IET Labs, Inc., 761 Old Country Rd., Westbury, NY 11590.

ANTI-STATIC SPRAY, Stat-Free, eliminates static, dust and dirt from electronic equipment without adverse effect on any substance. Can be used on computer equipment, workbenches and tools



CIRCLE 154 ON FREE INFORMATION CARD

and is useful on panel meters and oscilloscope faces to prevent inaccurate readings. Available in 16 ounce cans. Price is \$2.98.—Chemtronics, Inc., 681 Old Willets Path, Hauppauge, NY 11787. R-E

PTS 8001 Component Analyzer



Solid state component tester works in or out of circuit. Simple hook-up to any standard oscilloscope. High, medium and low range switch for matching the impedance of the component being tested. Dealer Net \$54.95

See the Yellow Pages for the Stocking Distributor or PTS Servicenter Nearest You.



PTS ELECTRONICS, INC.
The Only Name You Need To Know

P.O. Box 272 Bloomington, IN 47402 812-824-9331

CIRCLE 54 ON FREE INFORMATION CARD

For
faster
service

USE
ZIP
CODE

on
all
mail

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services) **\$1.50 per word (no charge for zip code)** . . . minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) **85¢ per word** . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 5% discount for 6 issues, 10% for 12 issues within one year, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e., August issue closes May 26). When normal closing date falls on Saturday, Sunday, or a holiday, issue closes on preceding working day.

PLANS & KITS

CONSTRUCTION plans for profitable business ideas. Catalog \$1.00. **GARLING**, 438 N. Garfield Street, Lombard, IL 60148

ELECTRONICS completed kits. No wiring. FM mic. VU meter. Touch control switch. Programmable music block. Wheel fortune game. Etc. Save up to 50%. Write for free catalog today. Postcard will do. **SUPERTRONICS INC.**, 39 Bowery, Box 88, New York, NY 10002

AUDIO mixers, preamps, meters. Schematics, construction guides. SASE brings free list. **PAM ELECTRONICS**, 3424 Memorial St., Alexandria, VA 22306

BOOST CB/HAM modulation/range. Free information—plus plans/kits catalog. **"SKIPPER"**, Box 130-F2, Paradise, CA 95969

ELECTRONIC organ kits. The ultimate design. Sounds like a pipe organ. Build it to sell or build it to keep. Models for churches, homes, clubs, pizza parlors. Send \$1.00 for demo record and catalog. **DEVTRONIX**, Dept. 70, 6101 Warehouse Way, Sacramento, CA 95826

FREE KIT Catalog

AUTORANGE DIGITAL CAP-METER KIT. Still the best for only \$74.95 contains **TEST & EXPERIMENTER'S EQUIP.**
Phone 415-447-3433
 Write or Phone for FREE CATALOG. Average 1 minute Saturday call is 21¢.
DAGE SCIENTIFIC INSTRUMENTS
 BOX 1054R LIVERMORE CA 94550

TRS-80 controls lights, motors, appliances anywhere in the house with your TRS-80 and BSR system X-10. Complete plans \$5.95. Add 16 input and output ports plans \$7.95. Information \$1.00. **DAPAR ELECTRONICS**, 17 Jennings St., Springfield, MA 01119

NEGATIVE ion generator plans. Build yourself with easy-to-get parts and save 50% to 75%. Includes ozone check. \$5.00 to **LUNATRIX**, Box 891, Yucaipa, CA 92399

PRINTED circuit boards from sketch or artwork. Kit projects. Free details. **DANOCINTHS INC.**, Box 261, Westland, MI 48185

NR-2 adaptive noise filter kit as featured in Radio-Electronics August, September issues. Reduces audio noise 12 dB. Works with all program sources; tape, or FM broadcast. Even works with Dolby systems. \$69.95. Free information. Dealer inquiries invited. **ADVANCED AUDIO SYSTEMS**, P.O. Box 24, Los Altos, CA 94022

POWER supply, regulated kit, limited supply 5V-1 to 3 amps out, 110V/220V in, all parts in schematic, supplied except PC board and bleeder lamp. \$11.50/unit, plus \$2.00 shipping and handling, 6% California tax. **SHOCK CO.**, P.O. Box 4332, Vellajo, CA 94590

GRAPHIC EQUALIZER

TWELVE bands/channel \$100 kit. still available; see May 1978 R/E cover story or write: **SYMMETRIC SOUND SYSTEMS**, 912 Knobcone Place, Dept. R, Loveland, CO 80537

SATELLITE TV FOR THE HOME

Our receiver lets you get over 75 channels of television directly from the satellites! HBO, Showtime, super stations, sports and movies from around the world. Works Anywhere—



FCC licensing no longer required.

3 WAYS TO GO

- **Buy complete**—our 24-channel tunable receiver, LNA and feed, only \$1,600.
- **Assemble**—our kit, all parts included, 2-day project.
- **Construct**—from our new step-by-step plans—SAVE!

Complete details covered in our Home Earth Station manual. Send \$7.95 today (refundable against any purchase), or call our 24-hr. C.O.D. Hotline: (305) 869-4283.

SPACECOAST RESEARCH
 P.O. Box 442, Dept. T, Altamonte Springs, FL 32701

EDUCATION & INSTRUCTION

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure \$1.00. **NEGEYE LABORATORIES**, Box 547-RE, Pennsboro, WV 26415

UNIVERSITY degrees by mail! Bachelors, Masters, Ph'D's . . . Free revealing details. **COUNSELING**, Box 317-RE2, Tustin, CA 92680

BROADCASTING! Start your own radio station at home, school, church! Become a DJ! Free information. **"BROADCASTING"**, Box 130-F2, Paradise, CA 95969

ELECTRONIC MUSIC

ELECTRONIC music and home recording in Polyphony magazine. Advanced applications, interviews, projects, computer music. Sample, \$1.50. Subscription (6 issues), \$8 US/\$10 foreign. **POLYPHONY**, Box R20305, Okla. City, OK 73156.

4 one **CAPACITANCE METER** 1pF to 999KµF
 in **FREQUENCY COUNTER** 35MHz
 kit **SQUARE WAVE GEN.** 1Hz to 99KHz—
OHMMETER—3.58MHz Xtal—Regulated PS—Five .8" Readouts—Low cost TTL Circuits—Automatic Decimal Placement—Be **AMAZED**—Satisfaction Guaranteed. Purchase the plans, etched P.C. board 4-3/4" by 6-3/4" and front panel decal for \$15.29! **BAGNALL ELECTRONICS**, 179 May Street, Fairfield, Conn. 06430

To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$1.50 per word (minimum 15 words) to:

Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003

ORDER FORM

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$10.

() Plans/Kits () Business Opportunities () For Sale
 () Education/Instruction () Wanted ()

Special Category: \$10

(PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.)

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

AM-FM-STEREO

Convert Your Car Into A Concert Hall!

AM-FM-MONO

AUTOMATIC RADIO

MADE BY THE AUTO RADIO SPECIALISTS!!

Models May Vary

PUSH BUTTONS

AM-FM-MULTIPLEX

19⁹⁵ \$100 STEREO AUTO RADIO

\$2 for Shpg.

No. 5744R

UNBELIEVABLE

FACTORY CLOSEOUT! — One of America's largest independent manufacturers of automobile radios has given up which we announced in Nov. 1979 Radio Electronics & Popular Electronics magazines. We've been fortunate in acquiring more of the last auto radios in production. These are AM-FM-MPX-Stereo sets...designed for new cars. All are tested 100% operational and come with knobs & 5 push buttons. Ideal for installing in your auto, van, camper, boat or any other place 12 VDC is available.

NEWS ITEM! — Auto stereo has become as sophisticated as home hi-fi — and nearly as expensive. You can spend \$300 for simple components—which means stereo can be out of reach for many folks and 2nd cars. If you want a stereo sound system, you can start with the purchase of a \$100 radio for only a mere \$19.95 at Delta. The radios are designed for small interior of your car that has the combination of the hard plastic and soft upholstered surfaces. It is the perfect radio for a top-sounding stereo system.

14⁹⁵ AM-FM

AUTOMATIC RADIO-FM

SAME RADIO as above except it is not stereo! Excellent FM reception; picks up stations with weak signals! Complete with metal top plate, push buttons and front bezels.

\$2 for Shpg. BUY OF A LIFETIME!

No. 5745R

Quality Speakers For Above Radios

AT SURPLUS PRICES!




60010 5730 60013 60011

Delta No.	Size	Type	Ohms	Watts	Magnet	Mfg. Ctrs.	Each
<input type="checkbox"/> 60010R	9x6	Oval	8	10	2-3/4" Rd.	6 1/4 x 4 3/4"	\$7.95
<input type="checkbox"/> 5730R	6	Round	8	3	2-3/8"	5-5/8"	5.95
<input type="checkbox"/> 60013R	5	Round 4 & 8	12	3"	Rd.	3-7/8"	7.95
<input type="checkbox"/> 60014R	5	Round 4 & 8	12	3-1/2"	Rd.	3-7/8"	9.95
<input type="checkbox"/> 60011R	4x6	Oval	8	10	2-5/8" Sq.	5 1/4 x 3"	5.95
<input type="checkbox"/> 60026R	4x6	Oval	8	10	2-3/8" Rd.	5 1/4 x 3"	5.95

•• High compliance stereo speakers

NEW!

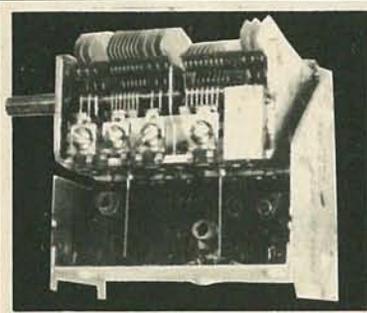

BUILD YOUR OWN STEREO RADIO.....

KLH FRONT END Tuner

Your Choice:

4.95

2 TYPES AVAILABLE

FM FM-AM

No. 60006R No. 60007R

"The Heart of A Receiver"....We have acquired a number of front end tuners....made for KLH—one of the audio giants....for use in its sophisticated receivers. These tuners contain the mechanical & electronic sections. The electronic section consists of an RF amplifier, oscillator and mixer. FM output from the tuner is 10.7 MHz, and the AM output is 455 KHz. Both types operate on 12VDC, and draw approx. 12 ma. Tuning capacitor on FM models has a vernier for fine tuning. Entire unit is shielded.

High Power TRANSFORMER

29⁹⁵ RARE FIND!

Delta No. 6996R

\$100 Value

This transformer is one of the most versatile high power transformers we have ever sold. It has 6 heavy duty windings, and a dual tapped primary. It has isolation winding rated at over 630 VA, plus 5 other windings. Proper selection of the primary taps will allow the various secondary voltages to be varied by ± 15%. The transformer may be used on 115 or 230 volts, by putting the primaries in series or parallel. All output voltages may be reduced half if the primary windings are placed in series and operated on 115 volts. We provide a data sheet showing many of the voltage possibilities of this flexible transformer. Listed are the rated voltages. These currents are extremely conservative. We have drawn as much as 25% more, still keeping with our own ratings. Wt. 39 lbs. 6 1/2" x 5 1/2" x 7 1/2"

- Secondary
- | | | |
|---------------------|---------------------|--------------------|
| 1 — 115V @ 5.5 Amps | 3 — 15V @ 4.5 Amps | 5 — 15V @ 5.0 Amps |
| 2 — 32V @ 1.4 Amps | 4 — 11V @ 1.75 Amps | 6 — 15V @ 5.0 Amps |

For computers, high power amps, lab supplies, bench supplies, etc.

MAIL-ORDER ADDRESS:



FREE 120-PC SURPLUS CATALOG

DELTA ELECTRONICS

176 SECOND AVE. WALTHAM, MASS.

02154

Minimum Order \$8.00

TEL. (617) 388-4705



Limited Quantity.

12V Power Supply \$12⁹⁵

• 12 Volt Power Supply 1 Amp. Adjustable from 10.8 to 13 volts. Mig by Power Conversion Prods. Crystal Lake, Ill. Primary & secondary both fused. On-Off switch. Mounted on steel plate 9" x 9". No. 5743R

MICRO COMPUTERS

TRS-80 micro computers by Radio Shack at 15% discount. Also have software for business systems. **MICRO MANAGEMENT SYSTEMS**, Downtown Shopping Center Plaza, Cairo, GA 31728 (912) 377-7120

SATELLITE TELEVISION

RECEIVE secret satellite television. Complete plans \$25.00, information \$4.40. **TELE-TEC**, 8688 Royal Drive, Noblesville, IN 46060

INVENTIONS

LEARN how to offer your invention for sale or license. Free booklet outlines procedures, royalty rates, requirements. **KESSLER SALES CORPORATION**, C-312, Fremont, OH 43420

Burglar-Fire Protection

Protect Your Life, Home, Business, Auto, etc.

- Our catalog shows how. Install your own alarm systems and devices and save \$555. We offer FREE write-in engineering service.

FREE CATALOG Lowest Prices on Reliable, High-Quality Alarm Systems and Devices

Burdex Security Co. Box 82802-RE Lincoln, Ne. 68501

BUSINESS OPPORTUNITIES

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESS-ES**, 92-R, Brighton 11th, Brooklyn, NY 11235

BECOME a semiconductor distributor full or part time. Here is a rare opportunity to engage yourself with one of America's leading suppliers of original Japanese semiconductors and exact replacement parts. Sell directly to retail outlets, repair shops, service technicians and manufacturers. Complete product line, backed up by a 40 million dollar inventory, priced to sell up to 50% lower than the leading replacement line. All products guaranteed. No investment required. Live wires only. Write to: **NEW-TONE ELECTRONICS INTERNATIONAL**, P.O. Box 1739, Bloomfield, NJ 07003

NEW tax loopholes discovered. Everyone eligible. Unique ideas. Free facts. **ULC**, Box 359 BC, Clarkston, GA 30021

WHOLESALE, bearcat scanners, C.B.s, stereos, speakers, top brands Fuzzbuster, Cobra President, Pioneer, Jensen, Regency. \$3.00 brings catalog price list to: **T & D Associates**, North Side Square, Paris, IL 61944

PASS FCC EXAMS

The Original FCC Tests-Answers exam manual that prepares you at home for FCC First and Second class Radiotelephone licenses. Newly revised multiple-choice exams cover all areas tested on the actual FCC exam. Plus "Self-Study" Ability Test. Proven! \$9.95 postpaid. Moneyback Guarantee.



COMTECH PRODUCTIONS
Radio Engineering Division

P.O. Box 26348 E
San Francisco, CA 94126

WANTED

MARCHANT mechanical calculator Model 10MR, \$100.00. **LEONARD WOODALL**, 3811 Dempster, Dallas, TX 75211

TREMENDOUS BUYS In New And Gov't Surplus Equipment

Dial Telephone "SUPER BUY"

• Save us the labor costs of cleaning and polishing and save \$55 on standard dial telephones. Work on any commercial system. Complete. (no parts missing) in good working order. Your choice of desk or wall models. These are take-outs from commercial service (not toys). Instructions furnished.



Wall Model: #715-WB1
Desk Model: #715-BE1
\$7.95 PREPAID IN U.S.A.
Does not include HAWAII, ALASKA, P.R.
PRICE EACH

FREE CATALOG Shows BIG SAVINGS On

- ELECTRONICS • ELECTRICAL • ALARM SYSTEMS • TELEPHONES • PUMPS
- BINOCULARS • GEAR MOTORS • WINCHES • SURVEYING INSTRUMENTS
- GENERATORS • COMPRESSORS • HYDRAULICS • POWER TOOLS • WELDERS
- POWER PLANTS • CHEMICAL SPRAYS • TAPFASINGS • MANY OTHERS

Surplus Center Box 82209-RE Lincoln, Ne. 68501

Low Cost...High Performance

DIGITAL MULTIMETER



\$99.95 WIRED

Low cost, high performance, that's the DM-700. Unlike some of the hobby grade DMMs available, the DM-700 offers professional quality performance and appearance at a hobbyist price. It features 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3 1/2 digit, 1/2 inch high LED display, with automatic decimal placement, automatic polarity, and overrange indication. You can depend upon the DM-700, state-of-the-art components such as a precision laser trimmed resistor array, semiconductor band gap reference, and reliable LSI circuitry insure lab quality performance for years to come. Basic DC volts and ohms accuracy is 0.1%, and you can measure voltage all the way from 100 μ V to 1000 volts, current from 0.1 μ A to 2.0 amps and resistance from 0.1 ohms to 20 megohms. Overload protection is inherent in the design of the DM-700, 1250 volts, AC or DC on all ranges, making it virtually goof proof. Power is supplied by four 'C' size cells, making the DM-700 portable, and, as options, a nicad battery pack and AC adapter are available. The DM-700 features a handsome, jet black, rugged ABS case with convenient retractable tilt bail. All factory wired units are covered by a one year limited warranty and kits have a 90 day parts warranty.

Order a DM-700, examine it for 10 days, and if you're not satisfied in every way, return it in original form for a prompt refund.

Specifications

DC and AC volts: 100 μ V to 1000 Volts, 5 ranges
 DC and AC current: 0.1 μ A to 2.0 Amps, 5 ranges
 Resistance: 0 Ω to 20 megohms, 6 ranges
 Input protection: 1250 volts AC/DC all ranges fuse protected for overcurrent
 Input impedance: 10 megohms, DC/AC volts
 Display: 3 1/2 digits, 0.5 inch LED
 Accuracy: 0.1% basic DC volts
 Power: 4 'C' cells, optional nicad pack, or AC adapter
 Size: 6"W x 3"H x 6"D
 Weight: 2 lbs with batteries

Prices

DM-700 wired + tested	\$99.95
DM-700 kit form	79.95
AC adapter/charger	4.95
Nicad battery pack	16.95
Probe kit	3.95

TERMS: Satisfaction guaranteed or money refunded, COD, add \$1.50. Minimum order \$6.00. Orders under \$10.00, add \$3.75. Add 5% for postage, insurance, handling. Overseas, add 15%. NY residents, add 7% tax.



600 mHz COUNTER



\$99.95 WIRED

The CT-70 breaks the price barrier on lab quality frequency counters. No longer do you have to settle for a kit, half-kit or poor performance, the CT-70 is completely wired and tested, features professional quality construction and specifications, plus is covered by a one year warranty. Power for the CT-70 is provided by four 'AA' size batteries or 12 volts, AC or DC, available as options are a nicad battery pack, and AC adapter. Three selectable frequency ranges, each with its own pre-amp, enable you to make accurate measurements from less than 10 Hz to greater than 600 mHz. All switches are conveniently located on the front panel for ease of operation, and a single input jack eliminates the need to change cables as different ranges are selected. Accurate readings are insured by the use of a large 0.4 inch seven digit LED display, a 1.0 ppm TCXO time base and a handy LED gate light indicator.

The CT-70 is the answer to all your measurement needs, in the field, in the lab, or in the ham shack. Order yours today, examine it for 10 days, if you're not completely satisfied, return the unit for a prompt and courteous refund.

Specifications

Frequency range: 10 Hz to over 600 mHz
 Sensitivity: less than 25 mv to 150 mHz
 less than 150 mv to 600 mHz
 Stability: 1.0 ppm, 20-40°C; 0.05 ppm/°C TCXO crystal time base
 Display: 7 digits, LED, 0.4 inch height
 Input protection: 50 VAC to 60 mHz, 10 VAC to 600 mHz
 Input impedance: 1 megohm, 6 and 60 mHz ranges 50 ohms, 600 mHz range
 Power: 4 'AA' cells, 12 V AC/DC
 Gate: 0.1 sec and 1.0 sec LED gate light
 Decimal point: Automatic, all ranges
 Size: 5"W x 1 1/2"H x 5 1/2"D
 Weight: 1 lb with batteries

Prices

CT-70 wired + tested	\$99.95
AC adapter	4.95
Nicad pack with AC adapter/charger	14.95
Telescopic whip antenna, BNC plug	7.95
Tilt bail assembly	3.95
CT-70 Kit Form	75.95

ramsey electronics

BOX 4072, ROCHESTER, N.Y. 14610
 PHONE ORDERS CALL
 (716) 271-6487

100W CLASS A POWER AMP KIT

Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low T.I.M. stereo pre-amp.

Specifications:

- Output power: 100W RMS into 8-ohm
125W RMS into 4-ohm
- Frequency response: 10Hz - 100 KHz
- T.H.D.: less than 0.008%
- S/N ratio: better than 80dB
- Input sensitivity: 1V max.
- Power supply: $\pm 40V$ @ 5 amp



TA-1000 KIT
\$51.95
Power transformer
\$15.00 each

SANWA

COMPACT - LIGHTWEIGHT - ULTRA SLIM
BATTERY CHECKER - LED TESTER

T-55D (w/o temp probe) \$44.50
T-55THD (temp probe) \$66.50

SPECIFICATIONS

Ranges

DC Voltage: 150mV, 500mV, 1.5V, 6V, 15V, 50V, 250V, 1kV (All 20k Ω /V)
25kV *Using HV probe)
DC Current: 50 μ A, 2.5mA, 25mA, 250mA (500mV drop)
AC Voltage: 15V, 500V, (9k Ω /V)
AC Current: 6mA, 6A (2V and 55mV drop)
Resistance: 10k Ω 100k Ω
1M Ω 5M Ω (max. calbtn)
100 Ω 1k Ω
10k Ω 50k Ω (mid scale)
10k Ω 100k Ω

Load Current: 30mA 3mA 300mA

Load Voltage: 3V 3V 3V

Decibels: -10 to +55dB

Batt Check: 0.9 to 1.5V (10 Ω load)

LED Check: (Available)

Temperature: -50° to +100°C and 0° to +200°C
Probe not supplied with T-55D)

Accuracy

DC Voltage: $\pm 2.5\%$ f.s.d.

DC Current: $\pm 2.5\%$ f.s.d.

Batt Check: $\pm 2.5\%$ f.s.d.

AC Voltage/Power on 1.5V range: $\pm 5\%$ f.s.d.

AC Voltage/Power above 15V range: $\pm 3.5\%$ f.s.d.

AC Current: $\pm 5\%$ f.s.d.

Resistance/Temperature: $\pm 3\%$ of arc

Dimensions: 146 x 97 x 28mm thick

Weight: 240g

Instrument supplied with Batteries 1.5V (UM-3 or R6)x2

Fuse & Spare: 500mA 250V

Temperature Probe: (T-55THD only)

NEW MARK III 9 Steps 4 Colors LED VU

Stereo level indicator kit with arc-shape display panel!!! This Mark III LED level indicator is a new design PC board with an arc-shape 4 colors LED display (change color from red, yellow, green and the peak output indicated by rose). The power range is very large, from -30dB to +5dB. The Mark III indicator is applicable to 1 watt - 200 watts amplifier operating voltage is 3V - 9V DC at max 400 MA. The circuit uses 10 LEDs per channel. It is very easy to connect to the amplifier. Just hook up with the speaker output!

IN KIT FORM \$18.50

MARK II SOUND ACTIVATED SWITCH KIT

A new designed circuit employed 2 I.C., a DPDT relay with a led indicator. A condenser microphone comes with the kit. The relay can handle up to 200 watts contact to allow to control most things. Just click the finger, the relay will close, the second click will release it. Sensitivity can be adjusted by an on board trim-pot. Operating voltage 9V D.C. TY-18
\$8.50 PER KIT



MARK IV 15 STEPS LED POWER LEVEL INDICATOR KIT

This new stereo level indicator kit consists of 36 4-color LED (15 per channel) to indicate the sound level output of your amplifier from -36dB \sim +3dB. Comes with a well-designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply is 6 \sim 12V D.C. with THG on board input sensitivity controls. This unit can work with any amplifier from 1W to 200W!

Kit includes 70 pcs. driver transistors, 38 pcs. matched 4-color LED, all other electronic components, PC board and front panel.



MARK IV KIT \$31.50

30W + 30W STEREO HYBRID AMPLIFIER KIT

It works in 12V DC as well! Kit includes 1 PC SANYO STK-043 stereo power amp. IC LM 1458 as pre amp, all other electronic parts, PC Board, all control pots and special heat sink for hybrid. Power transformer not included. It produces ultra hi-fi output up to 60 watts (30 watts per channel) yet gives out less than 0.1% total harmonic distortion between 100Mz and 10KHz.



\$32.50 PER KIT

BATTERY POWERED FLUORESCENT LANTERN

MODEL 888 R


FEATURES

- Circuitry: designed for operation by high efficient, high power silicon transistor which enable illumination maintain in a standard level even the battery supply drops to a certain low voltage.
- 9" 6W cool/daylight miniature fluorescent tube.
- 8 x 1.5V UM-1 (size D) dry cell battery.
- Easy sliding door for changing batteries.
- Stainless reflector with wide angle increasing lamination of the lantern.



\$10.50 EA

STEREO AMPLIFIER

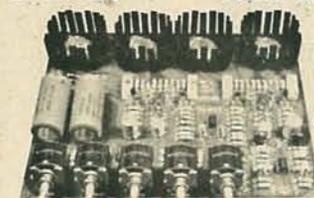

60 W

60 W

COMPLETED UNIT - NOT A KIT!

OCL pre amp. & power stereo amp. with bass, middle, treble 3-way tone control. Fully assembled and tested, ready to work. Total harmonic distortion less than 0.5% at full power. Output maximum is 60 watts per channel at 8 Ω . Power supply is 24 - 36V AC or DC. Complete unit. Assembled \$49.50 ea.
Power transformer \$ 8.50 ea.

5W AUDIO AMP KIT

2 LM 380 with Volume Control

Power Suply 6 18V DC

ONLY \$6.00 EACH



PROFESSIONAL PANEL METERS



A. 0-50UA 8.50 ea.
B. 0-30VDC 8.50 ea.
C. 0-50VDC 8.50 ea.
D. 0-3ADC 9.00 ea.
E. 0-100VDC 9.00 ea.

All meters white face with black scales. Plastic cover.

0.5" LED ALARM CLOCK MODULE

ASSEMBLED! NOT A KIT!

Features: • 4 digits 0.5" LED Displays • 12 hours real time format • 24 hours alarm audio output • 59 min. countdown timer • 10 min. snooze control.



ONLY \$7.00 EACH

SPECIAL TRANSFORMER
FOR CLOCK
\$1.50 EACH

DIGITAL AUTO SECURITY SYSTEM

4 DIGITS
PERSONAL CODE!!

SPECIAL \$19.95



- proximity triggered
- voltage triggered
- mechanically triggered

This alarm protects you and itself! Entering protected area will set it off, sounding your car horn or siren you add. Any change in voltage will also trigger the alarm into action. If cables within passenger compartment are cut, the unit protects itself by sounding the alarm.

3-WAY PROTECTION!

All units factory assembled and tested - Not a kit!

A NEW LED ARRAY AND DRIVER FOR LEVEL METERS

This series covers a wide range of level indication uses, output and input voltage, time related change, temperature, light measurement and sound level. The problem of uneven brilliance often encountered with LED arrangements as well as design problems caused by using several units of varying size are substantially reduced. 12 LEDs in one bar:

LED ARRAY
GL-112R3 Red, Red, Red \$5.50
GL-112N3 Green, Yellow, Red \$6.50
GL-112M2 Green, Green, Red \$6.50
GL-112G3 Green, Green, Green \$6.50



LED DRIVERS

1R 2406G is an I.C. specially designed to drive 12 LED. The number of LED is lineally illuminated according to the control voltage input terminal 21. Operating voltage is 9 12V D.C. \$5.35 EACH

PROFESSIONAL FM WIRELESS MICROPHONE

TECT model WEM-16 is a factory assembled FM wireless microphone powered by an AA size battery. Transmits in the range of 88-108MHz with 3 transistor circuits and an omni-directional electric condenser. Element built-in plastic tube type case; mike is 6 1/4" long. With a standard FM radio, can be heard anywhere on a one-acre lot; sound quality was judged very good.

\$16.50

FLASHER LED

Unique design combines a jumbo red LED with an IC flasher chip in one package. Operates directly from 5V-7V DC. No dropping resistor needed. Pulse rate 3Hz @ 5V 20mA.


2 for \$2.20

LCD CLOCK MODULE!

• 0.5" LCD 4 digits display • X'tal controlled circuits • D.C. powered (1.5V battery) • 12 hr. or 24 hr. display • 24 hr. alarm set • 60 min. countdown timer • On board dual back-up lights • Dual time zone display • Stop watch function.

NIC1200 (12 hr) \$24.50 EA.

NIC2400 (24 hr) \$26.50 EA.

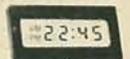

MINI-SIZED I.C. AM RADIO

Size smaller than a box of matches!

Receives all AM stations.

Batteries and ear phones included.

Only \$10.50




12 DC MINI RELAY

6V SPDT 2 AMP 1.30
12V SPDT 3 AMP 1.60
12V DPDT 2 AMP 2.50
12V 4PDT 3 AMP 3.50



LINEAR SLIDE POT

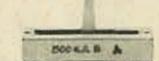500 Ω SINGLE
Metal Case 3" Long
2 FOR \$1.20



CONDENSER MICROPHONE

Sub-Mini Size
FET Transistor Built-in \$2.50 each



FLUORESCENT LIGHT DRIVER KIT



With Case Only
\$6.50 Per Kit

12V DC POWERED
Lights up 8 ~ 15 Watt Fluorescent Light Tubes. Ideal for camper, outdoor, auto or boat. Kit includes high voltage coil, power transistor, heat sink, all other electronic parts and PC Board, light tube not included!

THE MOST ADVANCED TIMEPIECE OF ITS KIND IN THE WORLD!

LCD Quartz Alarm Chronograph with calendar and dual time zone!! Watch is the same as Seiko but you pay a lot more for the name!



One Year Full Warranty

- 24 hour alarm • Chronograph counts up to 12 hrs., 59 mins. 59.9 sec. • Precision of chrono up to 1/10 sec. indicated by 10 moving arrows!! • Lap time (with chrono running uninterrupted) • Time displays by LCD for hour, min., sec., day, date of the week and AM/PM. • Calendar gives out date-day
- Dual time zone for any two cities of the world at your own choice. • With light switch to allow you to see the time in the dark!

Regular Price \$85.50
SPECIAL \$49.95

ELECTRONIC DUAL SPEAKER PROTECTOR



Cut off when circuit is shorted or over load to protect your amplifier as well as your speakers. A must for OCL circuits.

KIT FORM
\$8.75 EA.

"FISHER" 30 WATT STEREO AMP



Super Buy
Only \$18.50

MAIN AMP (15W x 2)
Kit includes 2 pcs. Fisher PA 301 Hybrid IC all electronic parts with PC Board. Power supply \pm 16V DC (not included). Power band with (KF 1% \pm 3dB). Voltage gain 33dB. 20Hz - 20KHz.

SUPER 15 WATT AUDIO AMP KIT

Uses STK-015 Hybrid Power Amp
Kit includes: STK-015 Hybrid IC, power supply with power transformer, front Amp with tone control, all electronic parts as well as PC Board. Less than 0.5% harmonic distortion at full power $\frac{1}{2}$ dB response from 20-100,000 Hz. This amplifier has QUASI — Complementary class B output. Output max is watt (10 watt RMS) at 4 Ω . ONLY \$23.50 each



HICKOK LX303 DIGITAL LCD MULTIMETER



• 3 $\frac{1}{2}$ digits display • 200 hours 9V battery life • Auto zero; polarity; overrange indication • 100MV DC F.S. sensitivity • 19 ranges and functions • D.C. volt: 0.1 MV to 1000V • A.C. volt: 0.1 V to 600 V • Resistance: 0.1 Ω to 20 M Ω • D.C. current: 0.01 A to 100 MA

OUR PRICE \$71.45

PUSH-BUTTON SWITCH



N/Open Contact
Color: Red, White, Blue, Green, Black
3/\$1.00
N/Close also Available
50c each
LARGE QTY. AVAILABLE

HEAVY DUTY CLIP LEADS



10 pairs — 5 colors Alligator clips on a 22" long lead. Ideal for any testing.
\$2.20/pack

MANY SOUND DECISIONS!

Solid state sound indicator operating voltage 6V DC 30mA. Small size approximately $\frac{3}{4}$ "x $\frac{1}{4}$ ".
Model EB2116 (Continuous)
Model EB2126 (Slow Pulse)
Model EB2136 (Fast Pulse)

\$3.60 EACH



ELECTRET CONDENSER MICROPHONE W TIE-CLIP

Sensitivity: 65dB \pm 3dB (At 1KHz)
Impedance: 600 OHM Freq. Response: Material: Aluminum 50 15,000 Hz
Cord: 10 ft. Length \$19.50 EACH

ELECTRONIC ALARM SIREN COMPLETE UNIT

Ideal for use as an Alarm Unit or hookup to your car back-up to make a reverse indicator. Light Output up to 130dB. Voltage supply 6 12V

AU-999 \$7.50

Sub Mini Size PANEL METER
500 UA
ONLY \$1.60 ea.

TRANSFORMERS ALL 117 VOLT INPUT

30V	4 AMP	\$8.50 EA.
36V CT	3 AMP	\$10.50 EA.
48V CT	3 AMP	\$10.50 EA.
24V CT	3 AMP	\$10.50 EA.
24V CT	0.8 AMP	\$2.50 EA.
12V CT	0.5 AMP	\$2.50 EA.
12V CT	120 MA	\$1.80 EA.

AC POWER SUPPLY Wall Type Transformer

12V AC	Output 200 MA	\$2.75 EA.
16V CT AC	Output 100 MA	\$2.10 EA.
6V DC	Output 120 MA	\$1.90 EA.
12V DC	Output 100 MA	\$1.90 EA.

ULTRASONIC SWITCH KIT



Kit includes the Ultra Sonic Transducers, 2 PC Boards for transmitter and receiver. All electronic parts and instructions. Easy to build and a lot of uses such as remote control for TV, garage door, alarm system or counter. Unit operates by 9-12 DC. \$15.50

COMPLETE TIME MODULE

0.3" digits LCD Clock Module with month and date, hour, minute and seconds. As well as stop watch function!! Battery and back up light is with the module. Size of the module is 1" dia. Ideal for use in auto panel, computer, instrument and many others!
\$8.95 EACH

SOUND ACTIVATED SWITCH

All parts completed on a PC Board SCR will turn on relay, buzzer or trigger other circuit for 2 - 10 sec. (adjustable). Ideal for use as door alarm, sound controlled toys and many other projects. Supply voltage 4.5V 9V D.C. 2 for \$3.00

FM WIRELESS MIC KIT

It is not a pack of cigarettes. It is a new FM wireless mic kit! New design PC board fits into a plastic cigarette box (case included). Uses a condenser microphone to allow you to have a better response in sound pick-up. Transmits up to 350 ft! With an LED indicator to signal the unit is on #FMM2 KIT FORM \$7.95



REGULATED DUAL VOLTAGE SUPPLY KIT

\pm 4 30V DC 800 MA adjustable, fully regulated by Fairchild 78MG and 79MG voltage regulator I.C. Kit includes all electronic parts, filter capacitors, I.C. heat sinks and P.C. board.

\$12.50 PER KIT

3 AA size fast charge (4 hours) NI-CD by Sanyo. All brand new and fresh 450 mah per cell. Limited supply. \$5.40 PER PAK

BECKMAN FET LIQUID CRYSTAL DISPLAY

Overall size 2" x 1.2" 0-5" characters reflective type.

Model 737-01 — for clock 4 digits with PM, alarm, snooze, colon indicators.
Model 739-04 — for panel meter 4 digits.

Model 739-03 — for panel meter 3 $\frac{1}{2}$ digits with \pm sign and over range indicator.

All displays include zeber connectors and front bezel. With data sheets.
Your choice — any model \$7.50 EACH

POWER SUPPLY KIT

0-30V D.C. REGULATED
Uses UA723 and ZN3055 Power TR output can be adjusted from 0-30V, 2 AMP. Complete with PC board and all electronic parts.
Transformer for Power Supply, 0-30 Power Supply
2 AMP 24V x 2 \$8.50 \$10.50 each

I.C. TEST CLIPS

Same as the E-Z clips \$2.75
With 20" Long Leads
In Black and Red Colors per pair

SOUND GENERATOR I.C.

Creates almost any type of sound — gun shot, explosion, train, car crash, star war, birds, organ ext. A built-in audio amplifier provides high level output. Operates from one 9V battery, 28 pin dip; we supply the datas. \$2.90 EACH

ELECTRONIC SWITCH KIT

CONDENSER TYPE
Touch On Touch Off
uses 7473 I.C. and 12V relay
\$5.50 each

1 WATT AUDIO AMP

All parts are pre-assembled on a mini PC Board. Supply Voltage 6 9V D.C. SPECIAL PRICE \$1.95 ea.

LOW TIM DC STEREO PRE-AMP KIT TA-10 20

Incorporates brand-new D.C. design that gives a frequency response from 0Hz — 100KHz \pm 0.5dB! Added features like tone defeat and loudness control let you tailor your own frequency supplies to eliminate power fluctuation!
Specifications: • T.H.D. less than .005% • T.I.M. less than .005% • Frequency response: DC to 100KHz \pm 0.5dB • RIAA deviation: \pm 0.2dB • S/N ratio: better than 70dB • Sensitivity: Phono 2MV 47K/Aux. 100MV 100K • Output level: 1.3V • Max. output: 15V • Tone control: bass \pm 10dB @ 50Hz/treble \pm 10dB @ 15Hz • Power supply: \pm 24 D.C. @ 0.5A
Kit comes with regulated power supply, all you need is a 48V C.T. transformer @ 0.5A
ONLY \$44.50
X'former

SOLID STATE ELECTRONIC BUZZER

Mini size 1" x $\frac{3}{4}$ " x $\frac{3}{4}$ "
Supply voltage 1.5V - 12V
Ideal for Alarm or Tone Indicator
\$1.50 each



FORMULA INTERNATIONAL INC.

	SHIPPING AND HANDLING CHARGES	2/80
Inside California	Under \$50.00 purchase 10% Over \$50.00 purchase 15%	Send \$1.00 For Detailed Catalogue
Outside Calif. (includes Mexico & Canada)	15% 20%	
Overseas	25% 30%	
Minimum Order \$10.00/Calif. Residents Add 6% Sales Tax.		
Phone Orders Accepted on Visa or MC ONLY. NO C.O.D./Store Hours 10-7 Mon. thru Sat.		
12603 CRENSHAW BLVD., HAWTHORNE, CA 90250		
PHONE: (213) 973-1921 • (213) 679-6162		

Buyers Worldwide Are Clamoring For Our

1¢ MORE GETS U 2

40-TWO WATT RESISTORS, carbo-films, carbons, some 5%ers, (#456).....	1.29	80 for 1.30
50-TERMINAL STRIPS, asst'd solder and screw types, 2 lugs & up, (#334).....	1.29	100 for 1.30
1-WATCH GUTS, LED, who knows how good, micro-digital bonanza, (#5115).....	1.29	2 for 1.30
10-1000V 1A RECTIFIERS, IN4007, epoxy case, axial leads, (#5926).....	1.29	20 for 1.30
6-25 WATT PLASTIC POWER, 2N6100 series, TO-220, 200bvcb0, 3A, (#1786).....	1.29	12 for 1.30
4-CALCULATOR AC JACKS, 3 terminals, takes mini plug, (#2316).....	1.29	8 for 1.30
65-PRE-FORM 1/4 WATTERS, popular values, for PC appl., (#2444).....	1.29	130 for 1.30
200-PC BOARD PARTS, boards loaded w/100% parts, hobby bonanza, (#5946).....	1.29	400 for 1.30
40-LOW NOISE RESISTORS, 1/8 & 1/2 W, oxide & magnetic film, (#220).....	1.29	80 for 1.30
40pc-SEMI-CON SURPRISE, asst. zeners, diodes, etc. untested, (#226).....	1.29	80 for 1.30
20-TRANSISTOR ELECTROLYTICS, asst. voltages from 5-100 mid, (#453).....	1.29	40 for 1.30
1-LASCR OPTO COUPLER, type HT11C3, mini plug, (#5700).....	1.29	2 for 1.30
10-UPRIGHT ELECTROS, 100% asst'd values and voltages, (#5900).....	1.29	20 for 1.30
2-GE 3W AUDIO AMP, type PA-263 IC, chip, mono, (#1522).....	1.29	4 for 1.30
1-MERCURY TILT SWITCH, N.C. rated 24VDC @ .05A, w/leads, (#5686).....	1.29	2 for 1.30
50-CAP SPECIAL, asst. values in mylar, mica, ceramic, disc, etc. (#3775).....	1.29	100 for 1.30
40-FEEDTHRU CAPACITORS, used for ham, RF, VHF circuitry, (#5668).....	1.29	80 for 1.30
40-PLASTIC TRANSISTORS, asst'd untested and hobby, (#2604A).....	1.29	80 for 1.30
6-6V INDICATORS, w/leads, test lamp manufacturers excess, (#5893).....	1.29	12 for 1.30
4-12 VOLT LAMPS, w/leads, popular voltage, 100% of uses, (#5942).....	1.29	8 for 1.30
1-12 VDC SOLENOID, similar to Guardian 16-P, w/plunger, 1/4" stroke, (#6013).....	1.29	2 for 1.30
1-TV AUDIO SHIELDED CABLE, 2 cond. 15 ft. w/RCA phone plugs, (#5812).....	1.29	2 for 1.30
10-POWER TAB TRANSISTORS, NPN, plastic, TO-220, (#5629).....	1.29	20 for 1.30
6-PRECISION TRIM POTS, asst'd singles and multi-turns, untested, (#3389).....	1.29	12 for 1.30
20-IN4148, 4 NANO, SWITCHING DIODE, axial leads, 10mA, 100%, (#308).....	1.29	40 for 1.30
2-5-1V STUD ZENER, 10W, DO-4, 5%, tol. Motorola 10M5 or equiv. (#5287).....	1.29	4 for 1.30
4-PUSHBUTTON ALARM SWITCH, 125 VAC 1A SPST, NC, (#5289).....	1.29	8 for 1.30
6-CABLE & PLUG SET, 2 cond. 3.5mm mini plug w/6 polarized cable, (#5737).....	1.29	12 for 1.30
5-"SUPER" 2N2222, NPN, ICBO:60V, hfe:100 W @ 2A, TO-92, 100%, (#5952).....	1.29	10 for 1.30
10-RESISTOR NETWORKS, assorted values in dips and singles, (#5699).....	1.29	20 for 1.30
4-VARACTOR DIODES, var. tuner capacitance, 20-50 pf, (#5887).....	1.29	8 for 1.30
50-PRECISION RESISTORS, 1/2, 1, & 2 watts, 1%, assorted types, (#363).....	1.29	100 for 1.30
60-CERAMIC CAPS, asst'd val. & styles, incl: tubulars, NPO's, etc. (#590).....	1.29	120 for 1.30
30-MOLEX CONNECTORS, nylon, asst'd styles, colors, & # of cond. (#5835).....	1.29	60 for 1.30
4-ROCKER SWITCHES, DPDT, solder eyelet terminals, (#3302).....	1.29	8 for 1.30
1-RELAY, BABCOCK 6VDC, SPST, plastic case (#5807).....	1.29	2 for 1.30
1-25 AMP BRIDGE RECTIFIER, 50 volts, 100%, (#5948).....	1.29	2 for 1.30
50-IN4000 RECTIFIERS, epoxy, axial leads, untested, (#2594).....	1.29	100 for 1.30
30pc-HEAT SHRINK, Thermo-fit, useful asst. of sizes, shrinks 50% (#5248).....	1.29	60 for 1.30
10-SLIDE SWITCHES, SPST, SPDT, etc. all shapes and sizes, (#5927).....	1.29	20 for 1.30
25-DT1's, 100% prime, asst'd flip flops, etc., marked, (#3709).....	1.29	50 for 1.30
10-MAN-3's, 7 segment, w/bubble magnifier, 100% material, (#3842).....	1.29	20 for 1.30
4-PL-259 COAX PLUG, mates to SO-239, Amphenol, (#5231).....	1.29	8 for 1.30
1-LITE SENSITIVE UNIJUNCTION TRANSISTOR, programmable, (#5719).....	1.29	2 for 1.30
100-PRE-FORMED 1/4 WATTERS, popular values, some 5 & 10 %ers, (#1060).....	1.29	200 for 1.30
4-PHOTO ELECTRIC DARLINGTON TRANSISTORS, (#3276).....	1.29	8 for 1.30
40-POWER RESISTORS, assorted types, includes 2 to 10 watters, (#228).....	1.29	80 for 1.30
15-NE-2 LAMPS, neon red, for 110VAC, less resistor, (#1435).....	1.29	30 for 1.30
30-"CRIMP-ON" TERMINALS, rings and spades, for # 12-20 wire, (#3955).....	1.29	60 for 1.30
50-ONE-WATT RESISTORS, popular assort, some 5%ers, 100% of uses, (#3844).....	1.29	100 for 1.30
30-FT. WIRE-WRAP WIRE, 30 gauge, insulated, continuous length, (#3803).....	1.29	12 for 1.30
6-SPDT MICRO SLIDE SWITCH, only 3/7" cube, for PC mount, (#3429).....	1.29	20 for 1.30
10-PR-RCA PLUGS & JACKS, for audio, speakers, etc. (#402).....	1.29	20 for 1.30
5-2N3055 HOBBY TRANSISTORS, TO-3, (#3771).....	1.29	10 for 1.30
6-SINGLE PIN MICRO GREEN LEDS, 3V, 10 mils, "pin heads", 100%, (#6126).....	1.29	12 for 1.30
6-JUMBO RED LEDS, 1.5-3 V @ 10 mA, 100% material, 100% of uses, (#2135).....	1.29	12 for 1.30
6-MAGNETIC DISCS, shatter-resistant Plastalloy, 13/16" dia. (#6099).....	1.29	12 for 1.30
5-PHOTO CELLS, Vactec 900, disc type, R: 2K ohm (dark) w/leads, (#6135).....	1.29	10 for 1.30
1-12VDC SPDT RELAY, 180 ohm coil, 25 mA, 1x1 1/2" sealed, (#5937).....	1.29	2 for 1.30
10-VOLUME CONTROLS, asst. values, audio, and switch too! (#592).....	1.29	20 for 1.30
60-PRE-FORMED DISC CAPS, handy assortment of values, marked, (#1181).....	1.29	120 for 1.30
10-AXIAL ELECTROS, assorted values and capacitance, (#5901).....	1.29	20 for 1.30
2-DOUBLE-SIDED PC BOARDS, 3"x12" high quality G-10 glass, (#5694).....	1.29	4 for 1.30
60-TUBULAR CAPACITORS, asst'd 1000mf to 1mf to 600 WVDC, (#35A219).....	1.29	120 for 1.30
6-MICRO MINI REED SWITCHES, 1" long, for alarms, relays, etc., (#1258).....	1.29	12 for 1.30
10-TANTALUM ELECTROS, asst'd mini, axial, hermetically sealed, (#5848).....	1.29	20 for 1.30
50-DISC TYPE CAPS, incl: 1/2, 1, & 2 watts, 1%, mylar, ceramics, asst'd values, (#437).....	1.29	100 for 1.30
60-COILS & CHOKES, asst'd RF, OSC, IF, parasitic types, (#35A297).....	1.29	120 for 1.30
6-SWITCHCRAFT PHONO JACKS, hi-Q, chassis mount, teflon base, (#5119).....	1.29	12 for 1.30
30-SUBMINI IF TRANSFORMERS, asst. slug tuned, shielded, (#35A9).....	1.29	60 for 1.30
40-ADJUSTABLE FERRITE CORES, center cut for hex adjust, (#5701).....	1.29	80 for 1.30
10-PC TRIMPOTS, screwdriver adjust, assorted values, (#3346).....	1.29	20 for 1.30
25-4" CABLE TIES, plastic, like Ty-wrap style, (#5217).....	1.29	50 for 1.30
5-CRYSTALS, max include: CB, ham various shapes and sizes, (#5716).....	1.29	10 for 1.30
3-MICRO SWITCHES, SPST, NO contacts, plunger style, solder tabs, (#5785).....	1.29	6 for 1.30
65-MOLEX SOCKETS, "on-a-strip" for 8-40 pin ICs, (#1609).....	1.29	130 for 1.30
6-PAIRS 9V BATTERY CLIPS, w/red & black color-coded leads, (#2852).....	1.29	12 for 1.30
6-LM340T VOLTAGE REGULATORS, 5 to 24 volts, TO-220, (#5897).....	1.29	12 for 1.30
40-POLYSTYRENE CAPACITORS, asst'd values and voltages, (#1052).....	1.29	80 for 1.30
15-THERMISTORS, resistors that change with the temperature, (#2048).....	1.29	30 for 1.30
65-1/4 WATT RESISTORS, asst'd values, metal film, marked, (#5797).....	1.29	130 for 1.30
10-MODULAR SWITCHES, Centralab "push-on" type, up to 4PDT, (#3150).....	1.29	20 for 1.30
5-"MOTOR MOTORS", small, high speed, asst'd sizes, 3-6VDC, (#2551).....	1.29	10 for 1.30
50-MICAS asst. sizes n-shapes, incl: "silvers" test, (#373).....	1.29	100 for 1.30
10-TRANSISTOR SOCKETS, for npn and pnp types, (#3845).....	1.29	20 for 1.30
4-HOBBY VOLTAGE REGULATORS, LM-309, 320, 340's, TO-3, (#3330A).....	1.29	8 for 1.30
12-PANEL SWITCHES, assorted slides, rotaries, modulators, etc. (#295).....	1.29	24 for 1.30
60-RESISTOR SPECIAL, 1/4 to 1 watt, carbons, carbo-films, etc. (#35896).....	1.29	120 for 1.30
65-HALF WATT RESISTORS, asst'd carbons, carbo-films, various values, (#454).....	1.29	130 for 1.30
10-SINGLE PIN MV-54 MICRO-MINI LEDS, diffused red lens, (#1802).....	1.29	20 for 1.30
15-HUMBUCKER CONTROLS, assorted values, manufacturers dump, (#3807).....	1.29	30 for 1.30
1-POWER TAB TRIAC, 100% prime, 400 V 10 A, TO-220, (#6216).....	1.29	2 for 1.30

DON'T FORGET



USE
YOUR
READER
SERVICE
CARD

DELTRONIKS

1. EMM 4200A, 4K Static RAMs, Ceramic A local memory boards manufacturer closed. We bought the new memory boards and took these 4200A static RAMs out. They are tested and 90-day guaranteed 100% good.


- Prime tested 4200A 4K RAMs \$5.50 ea., 32/\$160.00, 300 pieces or more \$4.50 ea.
2. 16K Dynamic RAMs (200 ns) for TRS-80, Apple II, Sorcerer. Removed from memory boards. Gtd. good. Set of 8 chips (ltd. qty.)..... \$32.00
3. Power SCR's (GEC50A) 100 volts @ 110 amps..... \$6.95 ea.
4. Squirrel Cage Fans (Howard) ..\$7.00 ea.
5. Power Diode 1N1202A, 200 volt @ 12 amp..... 4 for \$1.00
6. LM 323 5 Volt 3 amps, voltage regulator 4.95 each or 10/\$45.00.
7. Super Saver. Micro PD411, Ceramic 4K x 1 dynamic RAMs..... 8 for \$10.00.



DELTRONIKS

5151 BUFORD HIGHWAY D28
ATLANTA, GA 30340
404-458-4690

CIRCLE 48 ON FREE INFORMATION CARD

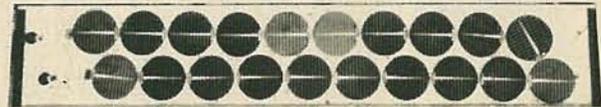

Electricity from the sun.
5 Volt panel 1/4 amp \$50 2.5 Volt panel 1/2 amp \$40
GIANT 3 1/2 inch cell, delivers 1 amp \$8.50
Above cell with special motor & prop, runs in sun \$10.25

LOGIC power supplies, unused, solid state construction.
5 Volt 4 amp \$35 5 Volt 15 amp \$45 5 Volt 25 amp \$45
5 volt 35 amp \$50 12 Volt 15 amp \$40



SEE IN THE DARKNESS
IR viewer, portable, new with choice of one lens...close up, telephoto or gen. purpose.
Requires 6 volt DC btry. \$250

PRINTER CENTRONICS #101
Visually OK, with head.
Sold as is..... \$600.00

Shipping extra on all merchandise

Meshna Inc., PO Box 62, E. Lynn, Mass. 01904



"TIE-PIN" CONDENSER MIKE
\$3.95

2 for \$3.96

ULTRASONIC TRANSDUCER
\$3.98 Each

2 for \$3.99

HIGH-GAIN ONE ARM BANDIT MIKES

Only \$14.99

2 FOR \$15

Take one hand command of your mobile or base rig with High-Gain One-Arm Bandit Mike. ON OFF VOLUME, SQUELCH, CHANNEL SELECTOR, SPEAKER, and DIGITAL DISPLAY are all conveniently located where your fingers do the talking. Comes with 8 ft. insulated, color coded, coiled cable, (separate) for easy integration into any type of rig. Size: 4 1/2" x 2 1/2" x 1 1/2". Wt. 9 oz. No. 92CUS886

SEND FOR FREE CATALOG
POLY PAKS
P.O. BOX 942-R2
SO. LYNNFIELD, MA 01940

HOW TO ORDER
We honor MASTERCARD, VISA, check, and COD, (25% down). Order by phone or mail \$4. Please state Cat. No. & description, name & month of magazine. Canadian: add \$5, Foreign: add \$10 (US funds). Excess will be returned. TERMS: add postage. RATED: Net-30. Phone: (617) 245-3828

CIRCLE 34 ON FREE INFORMATION CARD

CIRCLE 14 ON FREE INFORMATION CARD

DIGI-KEY CORPORATION

TOLL FREE 1-800-346-5144

MINN., AK., HI. RESIDENTS 218-681-6674

DON'T FORGET OUR DISCOUNTS WHEN COMPARING PRICES

I.C.'S • RESISTORS • TRANSISTORS • CAPACITORS • DIODES • I.C. SOCKETS & PINS • SWITCHES
CLOCK MODULES • OPTOELECTRONICS • BREADBOARDING & TESTING DEVICES • DRAFTING SUPPLIES
DATABOOKS • HEAT SINKS • WIRE • TOOLS... AND MORE... WRITE FOR FREE CATALOG...

TIME-TEMPERATURE PROGRAMMABLE MODULE

USE PROGRAMMABLE FOR:

- 12 to 34 Hour Display
- 100 to 1000°C. Set with variable range of temperature sensor
- 100 to 1000°C. Set with variable range of temperature sensor
- 100 to 1000°C. Set with variable range of temperature sensor



FEATURES

- 12 to 34 hour display with red LED
- 100 to 1000°C. Set with variable range of temperature sensor
- 100 to 1000°C. Set with variable range of temperature sensor
- 100 to 1000°C. Set with variable range of temperature sensor

TEXAS INSTRUMENTS I.C. SOCKETS

SOLDER TAIL DIP SOCKETS

- Low profile
- New grip design for maximum retention force
- Redundant contact points
- YOUR CHOICE - "TIN OR GOLD"
- Choice of 20 mil. or 28 mil. solder tail sockets



TIN PLATED WIRE WRAP

Series C-19 200 Microinches Tin

Part No.	Description	1	10	100
740120	8 pin wire-wrap, tin	33	2.52	24.00
740121	14 pin wire-wrap, tin	38	2.76	25.00
740122	18 pin wire-wrap, tin	43	3.00	26.00
740123	24 pin wire-wrap, tin	48	3.24	27.00
740124	30 pin wire-wrap, tin	53	3.48	28.00
740125	36 pin wire-wrap, tin	58	3.72	29.00
740126	42 pin wire-wrap, tin	63	3.96	30.00
740127	48 pin wire-wrap, tin	68	4.20	31.00
740128	54 pin wire-wrap, tin	73	4.44	32.00
740129	60 pin wire-wrap, tin	78	4.68	33.00
740130	66 pin wire-wrap, tin	83	4.92	34.00
740131	72 pin wire-wrap, tin	88	5.16	35.00
740132	78 pin wire-wrap, tin	93	5.40	36.00
740133	84 pin wire-wrap, tin	98	5.64	37.00
740134	90 pin wire-wrap, tin	103	5.88	38.00
740135	96 pin wire-wrap, tin	108	6.12	39.00
740136	102 pin wire-wrap, tin	113	6.36	40.00
740137	108 pin wire-wrap, tin	118	6.60	41.00
740138	114 pin wire-wrap, tin	123	6.84	42.00
740139	120 pin wire-wrap, tin	128	7.08	43.00
740140	126 pin wire-wrap, tin	133	7.32	44.00
740141	132 pin wire-wrap, tin	138	7.56	45.00
740142	138 pin wire-wrap, tin	143	7.80	46.00
740143	144 pin wire-wrap, tin	148	8.04	47.00
740144	150 pin wire-wrap, tin	153	8.28	48.00
740145	156 pin wire-wrap, tin	158	8.52	49.00
740146	162 pin wire-wrap, tin	163	8.76	50.00
740147	168 pin wire-wrap, tin	168	9.00	51.00
740148	174 pin wire-wrap, tin	173	9.24	52.00
740149	180 pin wire-wrap, tin	178	9.48	53.00
740150	186 pin wire-wrap, tin	183	9.72	54.00
740151	192 pin wire-wrap, tin	188	9.96	55.00
740152	198 pin wire-wrap, tin	193	10.20	56.00
740153	204 pin wire-wrap, tin	198	10.44	57.00
740154	210 pin wire-wrap, tin	203	10.68	58.00
740155	216 pin wire-wrap, tin	208	10.92	59.00
740156	222 pin wire-wrap, tin	213	11.16	60.00
740157	228 pin wire-wrap, tin	218	11.40	61.00
740158	234 pin wire-wrap, tin	223	11.64	62.00
740159	240 pin wire-wrap, tin	228	11.88	63.00
740160	246 pin wire-wrap, tin	233	12.12	64.00
740161	252 pin wire-wrap, tin	238	12.36	65.00
740162	258 pin wire-wrap, tin	243	12.60	66.00
740163	264 pin wire-wrap, tin	248	12.84	67.00
740164	270 pin wire-wrap, tin	253	13.08	68.00
740165	276 pin wire-wrap, tin	258	13.32	69.00
740166	282 pin wire-wrap, tin	263	13.56	70.00
740167	288 pin wire-wrap, tin	268	13.80	71.00
740168	294 pin wire-wrap, tin	273	14.04	72.00
740169	300 pin wire-wrap, tin	278	14.28	73.00
740170	306 pin wire-wrap, tin	283	14.52	74.00
740171	312 pin wire-wrap, tin	288	14.76	75.00
740172	318 pin wire-wrap, tin	293	15.00	76.00
740173	324 pin wire-wrap, tin	298	15.24	77.00
740174	330 pin wire-wrap, tin	303	15.48	78.00
740175	336 pin wire-wrap, tin	308	15.72	79.00
740176	342 pin wire-wrap, tin	313	15.96	80.00
740177	348 pin wire-wrap, tin	318	16.20	81.00
740178	354 pin wire-wrap, tin	323	16.44	82.00
740179	360 pin wire-wrap, tin	328	16.68	83.00
740180	366 pin wire-wrap, tin	333	16.92	84.00
740181	372 pin wire-wrap, tin	338	17.16	85.00
740182	378 pin wire-wrap, tin	343	17.40	86.00
740183	384 pin wire-wrap, tin	348	17.64	87.00
740184	390 pin wire-wrap, tin	353	17.88	88.00
740185	396 pin wire-wrap, tin	358	18.12	89.00
740186	402 pin wire-wrap, tin	363	18.36	90.00
740187	408 pin wire-wrap, tin	368	18.60	91.00
740188	414 pin wire-wrap, tin	373	18.84	92.00
740189	420 pin wire-wrap, tin	378	19.08	93.00
740190	426 pin wire-wrap, tin	383	19.32	94.00
740191	432 pin wire-wrap, tin	388	19.56	95.00
740192	438 pin wire-wrap, tin	393	19.80	96.00
740193	444 pin wire-wrap, tin	398	20.04	97.00
740194	450 pin wire-wrap, tin	403	20.28	98.00
740195	456 pin wire-wrap, tin	408	20.52	99.00
740196	462 pin wire-wrap, tin	413	20.76	100.00

INTEGRATED CIRCUITS

7400 TTL 74000 S.T.L. 4000 CMOS LINEAR I.C.'S

Part No.	Description	1	10	100
7400	7400 TTL	1	10	100
7401	7401 TTL	1	10	100
7402	7402 TTL	1	10	100
7500	7500 TTL	1	10	100

WIRE-WRAPPING WIRE

PRE CUT - PRE STRIPPED

Wire for Wire Wrapping, AWG-30 (0.25 MM) KINAX

Wire for Wire Wrapping, AWG-30 (0.25 MM) KINAX

Part No.	Description	1	10	100
7401	7401 Wire	1	10	100
7402	7402 Wire	1	10	100
7403	7403 Wire	1	10	100
7404	7404 Wire	1	10	100
7405	7405 Wire	1	10	100
7406	7406 Wire	1	10	100
7407	7407 Wire	1	10	100
7408	7408 Wire	1	10	100
7409	7409 Wire	1	10	100
7410	7410 Wire	1	10	100
7411	7411 Wire	1	10	100
7412	7412 Wire	1	10	100
7413	7413 Wire	1	10	100
7414	7414 Wire	1	10	100
7415	7415 Wire	1	10	100
7416	7416 Wire	1	10	100
7417	7417 Wire	1	10	100
7418	7418 Wire	1	10	100
7419	7419 Wire	1	10	100
7420	7420 Wire	1	10	100
7421	7421 Wire	1	10	100

INTERNATIONAL ELECTRONICS UNLIMITED

JUMBO RED LED .20" diffused	10/\$1.00	.4" ORANGE LED DISPLAY 7 segment RHD	\$1.19ea 10/\$7.95
SUBMIN RED LED .125" diffused	25/\$2.00	MAN4610 - common anode	25/\$17.50
JUMBO GREEN LED .20" diffused	7/\$1.00	MAN4640 - common cathode	100/\$65.00
SUBMIN GREEN LED .125" diffused	25/\$2.85	.4" ORANGE overflow ±1 MAN4630 - common anode	\$.89ea 10/\$5.95
VOLTAGE COMPARATOR LM311 8 pin DIP	\$.69ea 10/\$5.90 100/\$47.50	.3" RED LED DISPLAY 7 segment RHD	\$.99ea 10/\$7.95
UART 1602B	\$3.95ea 10/\$35.00 100/\$275.00	XAN72 (MAN72 equiv) common anode	\$.99ea 10/\$7.95 25/\$17.50 100/\$65.00

CLOCK CHIP MM5375AA 4-6 digit 60hz 12hr alarm 24 pin	\$1.95 10/\$17.50 100/\$150.00	RETRIGGERABLE MONOSTABLE MULTIVIBRATOR - ONE SHOT 9601 14 pin DIP	\$.40ea 10/\$3.50 100/\$25.00
CLOCK CHIP MM5385N 4 digit 50/60hz 12hr alarm 40 pin	\$1.65ea 10/\$12.50 100/\$100.00	DUAL ONE SHOT 9602 16 pin DIP	\$.50ea 10/\$4.50 100/\$35.00
DUAL DIFFERENTIAL COMPARATOR LM1414 14 pin DIP	\$.95ea 10/\$8.50 100/\$75.00	IC BREADBOARD	\$1.15ea 10/\$10.00 100/\$75.00

QUAD PROGRAMMABLE OP AMP XR4202 16 pin DIP	\$1.75 10/\$15.00 100/\$125.00	METAL FILM RESISTORS ± 1% 1/4w std. decade values 10 ohm - 475K, 1M ohm 1/8w only Total Qty. Each pk-10 pk-25 pk-100 1-999 \$.25 1.75 2.25 7.50 1000- .10 .40 2.50 20.00	
---	--------------------------------------	---	--

DIODES 1N4148 400mw 15/\$1.00 100/\$5.00 1N4001 rectifier 12/\$1.00 100/\$7.00 1N4007 rectifier 10/\$1.00 100/\$9.00		CARBON FILM RESISTORS ± 5% 1/4w or 1/2w 1 ohm - 5.6M ohm 5.6M ohm - 15M ohm 1/2w only 1-1000 \$.10 .45 3.00 1000- .10 .40 2.50 20.00	
---	--	--	--

SHIFT REGISTERS tri-state dual 100 bit static 2510 - 14 pin tri-state dual 200 bit static 2511 - 14 pin 10/\$5.00 25/\$11.50 100/\$35.00		Payment by check, M.O., UPS-COD, M/C or VISA. Add \$1.00 shipping/handling in US, Canada & Mexico. Other countries \$1.00 + 5% of order. California residents add sales tax. Minimum order \$10.00	
---	--	--	--

TRANSISTORS 2N3904 NPN TO-92 10/\$1.50 2N3906 PNP TO-92 25/\$3.00 100/\$11.00			
--	--	--	--

INTERNATIONAL ELECTRONICS UNLIMITED

225 BROADWAY, JACKSON, CA 95642
phone 209 223 3870

CIRCLE 57 ON FREE INFORMATION CARD

MICRO MART

552 Summit Ave.
Westfield, N.J. 07090
(201) 654-6008

MOTION DETECTOR Completely assembled on circuit board with capacitors Specs and application notes included—4.95 3 1/2" x 2 x 1 1/4" case with mtng tabs/3.00	
CRYSTALS — 3.579545 MHz 99c 6.0 MHz 2.95	
JUMBO LED's Green, 7/1.00 Yellow, 7/1.00 Red, 10/1.00 100/13.00 100/13.00 100/9.00	
MOUNTING CLIPS—12/1.00	
7 SEG Displays (comp. grade) 3"/95¢ 6"/1.45 (specify ann. or cath.)	
LAMPS 1/2" clear with 12" leads, 3/1.00	
DIPPED TANTALUMS 47µf 35V (1" leads) 10/1.00	
SUPER SUB MINI LYTICS (1" rad. leads, by Nichicon) 1000µf 50V (1 1/2" x 1/4" W), 75¢ or 10/6.00 47µf 25V (1/2" x 1/4" W), 10/\$1.00	
COMPUTER GRADE TWIST LOCKS 3200µf 50V (ideal for power supplies) 1.00 1000µf 50V—1.00 1000µf 185V—2.00	
DISCS .001 1KV 25/1.00, 1.50V 15/1.00	
C & K SWITCH square mini mom. P.B./panel mt. 1.00	
TV Knobs 10/1.00	
CRT HARNESS 1.75 for 25" color picture tube, with spark gap	
Self adhesive rubber bumpers 25/1.00	
6.3V 1.2 Amp Transformer—1.75	
LOOK OHM POT by CTS Linear taper, long nylon shaft, 4/1.00	
CONDENSER MIKE 1.50	
8035 Microprocessor, 17.00	
INTERFACE CHIP-D8243 16 line I/O extender for all single chip µPs 5.75	

BRAND NEW ITEM FREQUENCY COUNTER CHIP ICM 7225 IPL (40 pin), with on board dividers, decoders/drivers. 18.95-specs included	
TTL (prime) 7447 7474, 7492 any 3/1.00	
FAIRCHILD 556 timers — 85¢, 7/5.00	
IN 4001's (comp. grade), 15/1.00	
ZENER DIODES 20V 1 amp 10/1.00	
BRIDGES 1 1/2 amp/50, 6 amp/2.00, 25 amp/1.00	
LINEAR	
LM 233K 4.00 LM 1303 70	
LM 300H 70 LM 1304 95	
LM 301AN 30 LM 1305 1.15	
LM 307H 50 LM 1307 60	
LM 307 30 LM 1307E 90	
LM 308H 85 LM 1310 1.75	
LM 308 85 LM 1391 2.00	
LM 310 80 LM 1414 1.50	
LM 311H 80 LM 1800 70	
LM 317K 2.75 LM 1808 2.50	
LM 318H 1.10 LM 1820 2.50	
LM 320K 15 1.10 LM 1828 2.00	
LM 320K 12 1.10 LM 1830 2.25	
LM 324 1.10 LM 1841 2.50	
LM 325 1.35 LM 1848 2.00	
LM 339J 1.00 LM 1889 2.50	
LM 340K 12 1.00 LM 2111 1.15	
LM 341P 12 80 LM 2113 1.75	
LM 343H 3.50 LM 2907 2.00	
LM 373 2.50 LM 2917 2.00	
LM 377 2.00 LM 3046 60	
LM 380 1.00 LM 3054 1.50	
LM 381 1.25 LM 3064 2.00	
LM 384 1.50 LM 3065 2.50	
LM 386 1.20 LM 3067 2.50	
LM 389 1.20 LM 3070 2.50	
LM 390 1.65 LM 3071 2.00	
LM 746 2.50 LM 3075 1.25	
LM 748CN 30 LM 3089 1.25	

Terms: MICRO-MART accepts Visa, MC, and telephone COD'S. Foreign orders \$50.00 minimum plus shipping-US funds only. Orders under \$10.00 include \$2.00 for shipping/handling. All components guaranteed or money refunded. Immediate shipping. N.J. residents add 5% sales tax.
MICRO-MART • 552 SUMMIT AVE., WESTFIELD, N.J. 07090 • (201) 654-6008

CIRCLE 33 ON FREE INFORMATION CARD

ALARM CLOCK KITS: 4 Digit .5"

Here it is! The first of several quality kits we have been asked for: Here is what you get — unbelievable as it may sound...

- 1 National - 5375AA Clock Chip
- 1 Bowmar Clock Stick Readout (L.E.D.) 4 digit - 1/2"
- 13 Transistors
- 2 Push Buttons for time set
- 2 Toggle Switches for alarm
- 1 Filter cap
- 4 1N4000 series diodes
- 1 1N4148
- 2 Disc caps
- 29 Resistors
- 1 Transducer (Speaker) for Alarm Plug In
- 1 LED Lamp for alarm indicator Transformer \$1.50

NEW!
\$9.99

ORDER
KIT
CK-100AC

P.C. Board \$2.25

D.C. MODEL

Same as above except it includes 60 Hz timebase.

This Kit Includes:

- 1 National 5375AA Clock Chip
- 1 Bowmar Clock Stick Readout - (L.E.D.) 4 digit - 1/2"
- 12 Transistors
- 2 Push Buttons for time set
- 2 Disc caps
- 27 Resistors
- 1 MOV
- 1 60 Hz time base

NEW!
\$12.75

ORDER
KIT
CK-100DC

P.C. Board \$2.25



We bought 350,000 LED's.
And you get the savings.

Reds, greens, yellows, orange, small, medium, large.
Bags of 25 - mixed \$2.75. That's only 11¢ each. Compare
this bargain up to twice our price.

FACTORY PRIME

BI - Polar LED 59¢ ea. or 10 for \$5

LAB-BENCH VARIABLE POWER SUPPLY KIT
5 to 20 VDC at 1 AMP. Short circuit protected by current
limit. Uses IC regulator and 10 AMP Power Darlington. Very
good regulation and low ripple. Kit includes PC Board, all
parts, large heatsink and shielded transformer. 50 MV. TYP.
Regulation. \$15.99 KIT

Sonalert® on P.C. Board

Direct from a radar detector manufacturer! 4-741 on a board
- plus 12 capacitors, trim pot and many usable components
plus a Mallory Sonalert® - well worth the price of the board
alone - while they last - \$2.50 ea.

**MICRO MINI
TOGGLE SWITCHES**
6 for \$5 with hardware.



**99¢
EACH**

16K DYNAMIC RAM CHIP
WORKS IN TRS-80 OR APPLE II
VERY LIMITED STOCK! "MAGAZINE SPECIAL" - 8/\$79.50

Digital Research: Parts
(OF TEXAS)

P.O. BOX 401247B GARLAND, TEXAS 75040 • (214) 271-2461

TERMS: Add 50¢ postage, we pay balance. Orders under \$15 add 75¢ handling.
No C.O.D. We accept Visa, MasterCard and American Express cards. Tex.
Res. add 5% Tax. Foreign orders (except Canada) add 20% P&H. 90 Day Money
Back Guarantee on all items. Write for our free catalog full of many useful
bargains.

TEST EQUIPMENT, TOOLS, TELEPHONE DEVICES, AUTO STEREO PRODUCTS

We will beat any advertised price!

Logic Probe

- Compact circuit powered
- Detects pulses as short as 50 μ sec
- DTL/TTL/HTL/CMOS compatibility

Model LP-1
\$44.95



Function Generator

- Model 2001
Reg. \$185.95
- Sine, square, triangle and separate TTL square wave output



100 MHz 8-Digit Counter

- 20 Hz to 100 MHz range
- LED display
- Fully automatic

Model MAX100 \$150.00



Preassembled Proto Boards

- Model PB-104
\$49.95
- Fully assembled breadboard contains four OT-59S sockets, seven OT-59B bus strips and four 5-way binding posts



Proto Board with Built-in Power Supplies

- Regulated
- Short-proof

Model PB-203A
\$129.95



3 1/2-Digit 0.1% Digital Capacitance Meter

- 9 ranges from 1999 pF to 199.9 μ F
- 0.1% of reading accuracy
- Auto over and under range indication



Model 3001
Reg. \$190.00
\$170

Portable Digital Capacitance Meter

- Measures capacitance from 0.1pF to 1 Farad
- Resolves to 0.1pF
- 10 ranges for accuracy and resolution
- 4 digit easy-to-read LED display
- 0.5% accuracy

BK PRECISION



Model 820



- ## 3 1/2-Digit DMM with LCD Readout
- 0.1% DC accuracy
 - 0.5% LCD display for high readability
 - 100 μ V / 100nA, 0.01 Ω resolution
 - Battery life of over 100 hours
 - Shielded to stay accurate in RF fields
 - Low battery warning

Model 2815

Dual Trace 5" 30 MHz Triggered Scope

- Rise time 11.7 nS or less
- Built-in signal delay line
- Flat response with smooth rolloff past 30 MHz
- 5mV/cm vertical sensitivity
- Probes included



Model 1479P

Call for Discount Prices

DIGITAL MULTIMETERS



Sinclair
PDM 35
Reg. \$69.95
\$49.95



Hickok
LX 303
\$69.50



Beckman
TECH 310
22 M Ω input resistance
10 Amp AC-DC
1500V Overload
6KV Transient Protection
2 year battery life
\$130.



Simpson 461
Complete with nickel-cadmium batteries, AC charger adapter, test leads
\$149.95

LEADER



RF Wide Band Signal Generator
Model LSG-16
Solid state FET oscillator circuitry
100 kHz to 100 MHz freq. range
300 MHz on harmonics

25 MHz Dual Trace Time Base



with Calibrated Variable Delay
Model LBO-515A with probes
1 μ sec to 5 sec built-in delay

Transistorized LCR Bridge

Model LCR-740

- Highly accurate 3 digit readout
- Operates on one 9V battery or with AC adapter
- Measures inductance, capacitance, resistance and loss factor.



20 MHz Dual Trace Oscilloscope

Model LBO-508A with probes
Call for Discount Prices



TECHNICIAN AIDS

Weller Xcelite

Attache Style

Model TC100-ST
Reg. \$471
\$279.95




Service Master

Model 99-SM
Reg. \$69.95
\$47.50



EDSYN SOLDAPULLT[®] Desoldering Tool

Model DS017
\$15.95

 

ISORTIP Cordless Soldering Iron


Model 7800
\$29.95

Thermal-Spot Circuit Tester

Model 5800
Finds faulty components quickly and easily

Weller Controlled Output Soldering Station

Model WTCPN
Reg. \$77.50
\$49.95

 

Econo-Lamp

- Spring balanced arms
- Tension control knobs
- Baked enamel finish
- Colors: Red, Yellow, Blue, Black, Oyster White
- UL for 60W

Model XL-334A
\$16.95

Magnifier Lamp

Precision ground and polished magnification lens
Model MG10A
\$49.95

CAR STEREO PRODUCTS

In-Dash Car Stereos



8-Track Tape Player with AM/FM/MPX Radio
Model C-777
\$52.50



Auto Reverse Cassette Tape Player with AM/FM/MPX Radio
Model CAS-999
\$79.95



Cassette Tape Player with AM/FM/MPX Radio
Model CAS-888
\$57.50

Stereo Power Booster

Model POW-40
40W stereo
20W per channel
Bass boost
\$24.95



6" x 9" 3-Way Speaker

Model BP2000-69TR
20 oz. ceramic magnet
\$14.95 ea.

Miniature High Fidelity 3-Way Stereo Speakers

MINI speakers
MAXI sound
Model HF-9
\$69.50
Reg. \$149.95



- Die-Cast Aluminum
- Long Throw Woofer
- Soft Dome Tweeter
- Extended Midrange Speaker
- 80-20,000 Hz
- 50W, 8 ohms

BK PRECISION

30 MHz Portable Frequency Counter

Model 1827
Reg. \$130.00
\$65

HICKOK Digital CB In-Line Tester

Model 388
Measures all 4 transmitter output characteristics
Frequency
Power
SWR
Modulation %
\$169.95



SPECIALS


RCA-VIZ Super Chro-Bar

Model WR-538A
Reg. \$129.95
\$89.95



RC Circuit Box

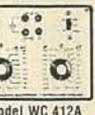36 resistors (15 Ω to 10 M Ω)
18 capacitors (100 pF to 0.22 μ F)
Reg. \$49.95
\$42.
includes test leads



Chess Challenger 7

7 levels of play
40W stereo
\$74.90



CANON Calculator Portable Printer with Adding Machine Tape

Model P10-D
\$69.98



Portable Oscilloscopes

15 MHz Dual Trace Triggered Miniscope

Model MS-215
Reg. \$435.00
\$369.95



15 MHz Triggered Miniscope

Model MS-15
Reg. \$319.00
\$269.95

30 MHz Dual Trace Triggered Miniscope

Model MS-230
Reg. \$559.00
\$479.95

TELEPHONE DEVICES

MURAPHONE Cordless Telephone System

Reg. \$89.95
\$74.95

CODE-A-PHONE Telephone Answering

Model 1550 Automatic Dialing
Reg. \$399.95
\$279.95

Model 1400 Call Control
Reg. \$349.95
\$199.95

Model 1500 Call Control
Reg. \$349.95
\$249.95

GTE Flip-Phone
\$37.95



BSR X-10 Remote Control for Lights & Appliances



4 Pc Standard Starter Kit
One (1) Standard Command Console
Two (2) Lamp Modules
One (1) Appliance Unit
Reg. \$87.95
\$79.50

5 Pc Ultrasonic Starter Kit
One (1) Deluxe Ultrasonic Command Console
One (1) Hand Held Remote Unit
Two (2) Lamp Modules
One (1) Appliance Unit
Reg. \$112.95
\$99.95

Lamp Modules \$14.50
Standard Command Console \$36.00
Appliance Modules \$14.50
Ultrasonic Command Console with Hand Held Remote \$59.95

FORDHAM

855 Conklin St. Farmingdale, N.Y. 11735
Master Charge BankAmericard VISA
COD Check Money Order

N.Y. State residents add appropriate sales tax
TOLL FREE (800) 645-9518
in N.Y. State call (516) 752-0050

Govt. SURPLUS ELECTRONIC EQUIPMENT CATALOG

New ITEMS... New BARGAINS!
FREE UPON REQUEST!
 Send today for FREE copy of CATALOG — and Supplement! • Dept. RE

FAIR RADIO SALES
 1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

Telephone Listening Device

Record telephone conversations in your office or home. Connects between any cassette or tape recorder and your telephone or telephone LINE. Starts automatically when phone is answered. Records both sides of phone conversation. Stops recorder when phone is hung up. This device is not an answering service.



Each \$18.95
 Qty. Disc Avail.

Super Powerful Wireless Mic

10 times more powerful than other mics. Transmits up to 1/4 mile to any FM radio. Easy to assemble kit. 15V battery (not incl.)
 Call (305) 725-1000 or send \$18.95 + \$1.00 shipping per item to USI Corp., P.O. Box RE-2052, Melbourne, FL 32901. COD's accept. For catalog of transmitters, voice scramblers and other specialty items, enclose \$2.00 to USI Corp.



size 2"x3"x1/2"


FULL-RANGE SPEAKER SYSTEM



1199
 PR.
 Reg. ~~14.99~~
 SP-638

- Mar-Proof Walnut Vinyl Finish Over Particle Board
- 17 1/4 x 10 x 4 1/4"
- 8 Ohms •17 lbs.

FM/AM TUNER CHASSIS

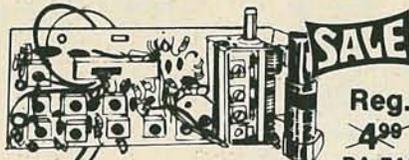

Reg. ~~4.99~~
 RA-744

- Wires into Any Amplifier Auxiliary Input
- Requires 8.2 VDC
- With Schematic
- 2 Gang Tuning Capacitor
- 6 x 2 1/4 x 2 1/4" •1 lb.

3.99

TELEDYNE ELECTRET CONDENSER MIKE



5.99
 MK-104
 Reg. ~~6.99~~

- For Cassette or PA Use •Low Impedance
- Omnidirectional. W/on-off switch. 3.5mm mini plug & 2.5mm micro plug. 5-ft. cable. Wt. 2 lbs.

LOCKMOUNT



1.79
 AU-149
 Reg. ~~2.79~~

- For Under-Dash Mtg. of CB's, Radios & Players
- Anti-Theft Protection •2 lbs.

NI-CAD BATTERY

SUB "C" Size

AS LOW AS **39¢** Ea. 59¢
 Lots of 4 49¢ ea.
 Lots of 8 39¢ ea.

- 1.2 VDC Each
- Rechargeable Over and Over •Shpg. wt. 1/4 lb.

5 VOLT POWER SUPPLY



99¢
 BA-363 Reg. ~~1.99~~

- 5 VDC @ 160mA with 2.5mm Micro Plug
- Shipping Weight 1 Pound

CARBON FILM 1/4W-5% Resistors

| OHMS |
|------|------|------|------|------|------|------|------|
| 2.7 | 11 | 47 | 200 | 820 | 3600 | 15K | 62K |
| 3.0 | 12 | 51 | 220 | 910 | 3900 | 16K | 68K |
| 3.3 | 13 | 56 | 240 | 1000 | 4300 | 18K | 75K |
| 3.6 | 15 | 62 | 270 | 1100 | 4700 | 20K | 82K |
| 3.9 | 16 | 68 | 300 | 1200 | 5100 | 22K | 91K |
| 4.3 | 18 | 75 | 330 | 1300 | 5600 | 24K | 100K |
| 4.7 | 20 | 82 | 360 | 1500 | 6200 | 27K | 110K |
| 5.1 | 22 | 91 | 390 | 1600 | 6800 | 30K | 120K |
| 5.6 | 24 | 100 | 430 | 1800 | 7500 | 33K | 130K |
| 6.2 | 27 | 110 | 470 | 2000 | 8200 | 36K | 150K |
| 6.8 | 30 | 120 | 510 | 2200 | 9100 | 39K | 160K |
| 7.5 | 33 | 130 | 560 | 2400 | 10K | 43K | 180K |
| 8.2 | 36 | 150 | 620 | 2700 | 11K | 47K | 200K |
| 9.1 | 39 | 160 | 680 | 3000 | 12K | 51K | 220K |
| 10 | 43 | 180 | 750 | 3300 | 13K | 56K | 240K |

HIGH QUALITY... LOW O.E.M. PRICE

5 for .25 10 for .40 100-\$1.60 - 1000.
 one one at \$14.
 value value 100 per value




CMOS BOARD \$2.95
 CONTAINS:
 4553 3 digit decade counter
 4511 4bit latch 7 seg. decoder
 driver for LED display
 4060 oscillator w/14 stage binary counter.
 4011 CMOS gate
 2 switches, resistors, capacitors.
 10 x 10 x 1 1/2"

HOLIDAY BONUS

good till Jan. 31, 1980
 With prepaid orders for \$60 or more we ship free a NATIONAL MA 1002E 4 digit AC alarm Clock module—U.S. orders only



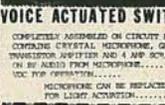VOICE ACTUATED SWITCH 95¢ ea
 COMPLETELY ASSEMBLED ON CIRCUIT BOARD IN SHIELDING CAN. CONTAINS: MICROPHONE, OSCILLATOR, TRANSDUCER, AMPLIFIER AND 4 AMP. SOL. RELAY. 25 TURNS ON BY ADDRESS FROM MICROPHONE. REQUIRES 5-15 VDC. TOP OPERATING.
 MICROPHONE CAN BE REPLACED BY CONVENTIONAL FOR LIGHT ACTIVATION.



P.U.T. PROGRAMMABLE UNIJUNCTION
 Prime 2N6026
 50¢ ea. ten \$4. 100-\$30
 Motorola ea. 1982




DIP BRIDGE 50¢ ea.
 1A, 100V
 Vero VM18
 ten \$4. 100-\$30
 removed from boards



DIODE ARRAY 1 IN914's
 20 PIN PACKAGE WITH PIN SPACED 1/8" 90° STRAIGHT HOUSING
 35¢ ea
 10-\$3
 special 40¢ ea
 10-\$3.50
 \$32-100
 CLAIREX PHOTOCONDUCTOR CELL



VIBRASONIC dual delay \$12.95

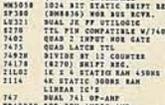

REED RELAY 5V 500 ohm spst \$1.25 ea



DIP TRIMMER 12 TURN 1/4 x 1/4 5K or 200K only mfg. DALE \$1.50 FOR \$4



1/4 WATT RESISTORS 10 ea. .300, 1.8K, 3.9K, 6.8K, 11K 43K, 68K, 240K - 5 percent tol. 80 FOR \$4



POTTER BRUMFIELD TYPE KHP RELAY 4PDT 3AMP 24VDC 650 ohms or 120VAC 10.5MA please specify coil required. \$2.00



Numeric Display 1/4" Single Digit CaSP LED COMMON CATHODE WITH RED OR GREEN COMPACT-10 DIGITS IN 7.5mm PANEL WIDTH HIGHLY LEGIBLE BRIGHTNESS CHARACTEREASILY READ WITHIN 10FT OVER A WIDE VIEWING ANGLE LOW PWR DREST AT TYPICAL BRIGHTNESS LEVELS. 65¢ each - 10 for \$5.95



VARO SEMICONDUCTOR 18 AMP 50V 1000V .90 ea. 10 for \$7.50 100-\$65

PO BOX 41778 SEND FOR FREE FLYER TODAY
 Sacramento California 95841
 35 minimum order, add \$3 handling charge to orders less than \$10. We pay post or UPS on domestic orders over \$10. . . . SAC MC and VISA accepted, \$15 minimum and shipping is added. . . . open accounts accepted from government entities and large priced firms. SAME DAY SHIPMENT—telephone (916) 334-2161 4811 Myrtle Avenue, Sacramento, CA 95841

BABYLON ORDER NOW! ELECTRONICS

CIRCLE 52 ON FREE INFORMATION CARD

Dept. R-2 260 S. Forge St. Akron, Ohio 44327

NAME	ADDRESS	CITY	STATE	ZIP
Qty	Stk #	Description	Price Ea	Total

CHARGE CARD ORDERS OVER \$25
CALL FREE 1-800-321-2424
 OHIO RESIDENTS CALL 1-216-535-1800
 Tax Postage Total



FREE!
 Please send me a free subscription to Olson Value Packed Catalog. (Within the Continental USA Only)

RADIO-ELECTRONICS

Active Electronic Sales Corp.



Zilog

Z8001 \$195.00 16 Bit CPU with segmented address space to 8 Megabytes.

Z8002 \$150.00 16 Bit CPU with non segmented address space to 64K bytes.

Z8000DB \$1500.00 A complete single board Z8000 microcomputer system. Contains the Z8002 microprocessor, 16K words of dynamic RAM, 2K word monitor PROM, dual serial interfaces, four counter/timers and 32 programmable parallel I/O lines.

**All Products Stocked in Depth
Largest Zilog Inventory**

Z80-CPU 2.5 MHz \$ 9.95	Z80-DMA 2.5 MHz \$28.85
Z80A-CPU 4.0 MHz 11.95	Z80A-DMA 4.0 MHz 33.60
Z80-PIO 2.5 MHz 7.20	Z80-SIO/O 2.5 MHz 36.00
Z80A-PIO 4.0 MHz 8.40	Z80A-SIO/O 4.0 MHz 39.50
Z80-CTC 2.5 MHz 7.20	Z80-SIO/1 2.5 MHz 36.00
Z80A-CTC 4.0 MHz 8.40	Z80A-SIO/1 4.0 MHz 39.50
	Z80-SIO/2 2.5 MHz 36.00
	Z80A-SIO/2 4.0 MHz 39.50

MICROPROCESSOR CHIP SETS

Part No.	Price	Part No.	Price	Part No.	Price
8080A	\$5.95	6800	\$6.95	6502	\$9.95
8085	12.95	6802	11.95	6504	9.95
				6505	9.95
8212	2.95	6810	3.95		
8214	3.95	6820	3.95	6520	6.95
8216	2.95	6821	3.95	6522	9.95
8224	3.45	6850	4.25	6532	13.95
8226	2.25	6852	3.95	6551	13.95
8228	4.98				
8238	4.98				
8251	6.95	1802LE	9.95	1854LE	6.95
8253	14.95	1824LE	3.50	1856LE	1.95
8255	5.75	1852LE	1.50	1858LE	1.95
8257	10.95	1853LE	1.45	1859LE	1.50
8259	14.95				

METAL POWER TRANSISTORS

Homotaxial — Best Quality

2N3054	.65	60V	NPN	TO-66
2N3055	.69	70V	NPN	TO-3
2N3442	1.50	160V	NPN	TO-3
2N3771	1.95	50V	NPN	TO-3
2N3772	1.95	100V	NPN	TO-3
2N3773	2.50	160V	NPN	TO-3

Universal SCR

C106D	.34	400V	5.0 AMP	TO-220
--------------	-----	------	---------	--------

MOS MEMORIES

MOS Static RAM's

Part No.	Price
2101	\$1.95
1K (256 x 4) 350ns 22 PIN	
2102LFPC	1.19
1K (1K x 1) Low Power 350ns 16 PIN	
2102LHPC	1.29
1K (1K x 1) Low Power High Performance 250ns 16 PIN	
2102-1PC	0.94
1K (1K x 1) 450ns 16 PIN	
2102-2PC	0.89
1K (1K x 1) 650ns 16 PIN	
P2111-2S	2.25
1K (256 x 4) 250ns 18 PIN	
P2112-3S	2.25
1K (256 x 4) 350ns 18 PIN	
2114L	\$4.95
Low Power 4K (1024 x 4) 300 ns	

MOS Dynamic RAM's

416-5	9.95
16K (16K x 1) 300ns 16 PIN	
TMS4060-30	2.95
4K (4K x 1) 300ns 22 PIN	
TMS4060-20	3.95
4K (4K x 1) 200ns 22 PIN	

UART's

AY5-1013A	4.50
0 to 40K BAUD 40 PIN	
AY3-1015	5.50
0 to 30K BAUD 40 PIN Single 5V supply	

1K CMOS RAM

5101	3.95
1K (256 x 4) 450ns 22 PIN Low Power	

4K CMOS RAM

P4315-45L	14.95
4K (4K x 1) 450ns 18 PIN	

SHIFT REGISTERS

3341PC	4.95
FIFO 700 KHz	
3341APC	5.50
FIFO 1 MHz	
3342PC	4.95
64 Bit Shift Register	
3347PC	4.95
80 Bit Shift Register	

ECL RAM

10410ADC/HM2106	1.95
256 x 1 Bit Fully Decoded 15ns 16 PIN	

LINEAR I.C.'s

LM301N-8	.34	LM739CN-14	1.29
LM307N-8	.29	LM741CN-8	.29
LM308CH	.95	LM747CN-14	.59
LM311N-8	.59	LM748CN-8	.39
LM324N	.59	TBA810DAS	1.29
LM339N	.99	LM1458N-8	.49
LM348N-14	.55	LM1488N-14	.69
LM358N-8	.99	LM1489N-14	.29
LM555N-8	.59	LM3403N-14	.99
LM556N-14	.49	LM3900N	.59
LM723CN-14	.49	LM4136N-14	.99
LM725CN-8	1.25		

Special of the Month

EPROM

C2708-65/4708-6 \$6.90

1K (1K x 8) 650 ns



1980 IC MASTER

JUST RELEASED over 2700 PAGES

Complete integrated circuit data selector. Master guide to the latest I.C.'s including microprocessors and consumer circuits. 45,000 device types listed. 5,000 new device types added. Complete new section on MPU boards & Systems.

Free Quarterly Updates

Special \$59.95



SOUND & MUSIC GENERATOR I.C.

Creates almost any type of sound, from music to gunshots and explosions. High level on amp output. 28 pin DIP. Operates from one 9V battery. With data.

"Lowest Price Offered Anywhere"

SN76477N (.600" centers) \$2.49

SN76477NF (.400" centers) \$2.29

"New small package"



MICROCOMPUTER BOARDS

NEC MICROCOMPUTERS \$299.00

TK80A

Based on the 8080A the board has both 1K RAM and 1K electrically erasable PROM expandable to 4K x 8 and 8K x 8 on board. Complete with keypad with 25 real keys and 8 bright .500" digits for display.

Rockwell International \$375.00

AIM65

As a learning aid AIM65 gives you an assembled, tested and warranted R6502 based microcomputer system with a full sized keyboard, an alphanumeric 20 character display and uniquely, an alphanumeric 20 column thermal printer. An on board Advanced Interface Monitor program provides extensive control and program development functions. 1K RAM.

L.E.D. LAMPS

LED209	T-1 3 mm Red	.09
LED211	T-1 3 mm Green	.19
LED212	T-1 3 mm Yellow	.14
LED220	T-1 1/2 5 mm Red	.11
LED222	T-1 1/2 5 mm Green	.24
LED224	T-1 1/2 5 mm Yellow	.16

DISPLAYS

FND357	.375" Common Cathode	1.09
FND367	.360" Common Cathode (high brightness)	1.29
FND500	.500" Common Cathode	1.09
FND507	.500" Common Anode	1.09
FND560	.500" Common Cathode (high brightness)	1.29
FND567	.500" Common Anode (high brightness)	1.29
DL704	.300" Common Cathode	1.29
DL707	.300" Common Anode	1.29
DL747	.630" Common Anode	2.29


ISOLATORS

ILD74	Dual Opto Isolator	1500V	1.29
ILQ74	Quad Opto Isolator	1500V	3.95
MCT6	Dual Opto Isolator	1500V	1.29
TIL111	Opto Coupler	1500V	.69
4N26	Opto Isolator	2500V	.59
4N28	Opto Isolator	500V	.59
4N29	Opto Isolator	2500V	.69
4N32	Opto Isolator	2500V	.69

TEXAS INSTRUMENTS Low Profile Sockets

Lowest prices anywhere for the highest quality, an unbeatable combination. Over one million pieces in stock.

Contacts	Price	Contacts	Price
8 PIN	.08	22 PIN	.22
14 PIN	.12	24 PIN	.24
16 PIN	.14	28 PIN	.28
18 PIN	.18	40 PIN	.40
20 PIN	.20		

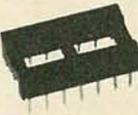

Synertek® SYM-1

\$239.00

Fully assembled, tested, documented and expandable. Powerful 6502 8-bit microprocessor. 6-digit hex LED display. KIM-1 hardware compatibility. Single plus 5V power requirements.

Texas Instruments TM990/189 UNIVERSITY MODULE

\$333.00

A complete learning aid that in conjunction with the Tutorial Text offers hands on experience with microprocessors, I/O, memory and assembly language programming. Offers advanced features such as 45 key alphanumeric keyboard, a powerful instruction set, multiply and divide, vectored interrupts, single bit I/O manipulation parallel I/O and 7 addressing modes.

MINIMUM ORDER \$10.00 + ADD \$2.00 TO COVER POSTAGE & HANDLING

Foreign customers please remit payment on an international bank draft or international postal money order in American dollars.




Active Electronic Sales Corp.

P.O. BOX 1035 FRAMINGHAM, MASSACHUSETTS 01701

Over-the-counter sales.
12 Mercer Rd., Natick, Mass 01760
Behind Zayres on Rte 9
Telephone Orders & Enquiries (617) 879-0077

IN CANADA

5651 FERRIER ST. MONTREAL, QUEBEC H4P 2K5
Tel. (514) 731-7441

4800 DUFFERIN ST. DOWNSVIEW, ONTARIO M3H 5S9
Tel. (416) 661-1115

BAXTER CENTRE 1050 BAXTER ROAD OTTAWA, ONTARIO K2C 3P2
Tel. (613) 820-9471

3070 KINGSWAY VANCOUVER, B.C. V5R 5J7
Tel. (604) 438-3321

CIRCLE 18 ON FREE INFORMATION CARD

4500v 9Watt DC SUPPLY
ZOWIE!
L-550
BACK AGAIN

WE HAVE ACQUIRED A FEW HUNDRED MORE OF THESE FINE HIGH VOLTAGE SUPPLIES, SPEC. FOR CRT SUPPLIES, HI VOLTAGE EXPERIMENTS, BUC ZAPPERS, ION GENERATORS, COMMERCIAL QUALITY, 115V AC IN, 4500V DC AT 200mA OUT. OVERALL SIZE 3.7" x 4.2" x 2.5" HIGH.

WE ALSO HAVE ACQUIRED A SMALL QUANTITY OF 6KV AND 12KV NEW DC SUPPLIES.

\$7.95 EA
PLEASE WRITE FOR INFO.

+\$1.75 SHIPPING

4.5-20 PF CERAMIC TRIMMER
L-251
HIGH-Q SILICON ON CERAMIC TRIMMER IS 1/4" DIA BY 1/4" HIGH, 5/16" HIG CENTER.

2/51
10/54.50
100/54.00

600 V 15A TRIAC
MCA TYPE 400MA
1/4" PRIME SIZED MOUNT TRIAC IN A HAND-TO-FIT VOLTAGE AND CURRENT RATED (10/11/11)

\$1.95 EA
10/517.50
100/515.50

5 TURN 100K LINEAR POT
UNUSUAL 5 TURN POT IS A CARBON UNIT FITTED WITH A BALL BEARING IN DUCTION (5000TH) LINEAR TAPER.

60c EA
10/5.50
100/5.50

Clock/Radio Timers
D-2000

BRAND NEW, HFD BY GENERAL TIME, 115VAC, 60 Hz, WITH A SWITCHED OUTPUT, SHELF MOUNTED, 5-5/8" x 2-1/2". NO HANDS SUPPLIED.

49c EA
10/14.50
100/14.00

18v 85mA WALL TRANSFORMERS
USE FOR CLOCKS, CHIRPS, OR WHATSOEVER, OUTPUT IS OPEN TERMINALS.

\$1.75 EA
10/515

MOLDED TO-3 SOCKETS
HIGHEST QUALITY WITH RAISED SHOLDER, TAP-PCD .625, AT THE PRICE OF CHEAP WAFER TYPES.

3/51
10/52.75
100/25

9 VOLT BATTERY CLIPS
FET STANDARD 9 VOLT "TRIM-SISTOM" BATTERY 4" LEADS, HANDY TO HAVE AROUND.

10/91
100/89

120 VAC 10 AMP Hash Filter
NEW, HFD BY CDE. UNIT HAS 3 MERR LINE COORD & PLUG IN, WIRE LEADS OUT. REMOVES NOISE FROM LINE.

\$2.98
10/525

SINGLE TURN PC TRIMMERS
APPROX 5/8" DIA
HORIZONTAL MT.
VERTICAL MT.

100 Ω
250 Ω
1K
10K
25K
100K
1MEG

5/51
50/59

1 MEG AUDIO TAPER W/SWITCH
L-1011
6/51
100/515

1-12pf CERAMIC TRIMMER
MULTI TURN

49c

ICL 7107 3 1/2 DIGIT VOLTMETER
on-a-chip
\$11.95 WITH DATA

RHYTHM GENERATOR ROM
\$1.75
10/515
100/120

PRE PROGRAMMED ROM HAS SEVERAL RHYTHM PATTERNS STORED THAT ARE "WALKED OUT" WITH A COUNTER (0-999 & COME) CHANGE PATTERNS WITH A SWITCH. WITH DATA, PIN TO PLAY WITH IT! D-8308

HERBERT'S RELIANT TAPE AMPLIFIER PC BOARD
\$2.98
2/15.50

12vac Power in - SW Audio out
Tape head, mic, aux. inputs
150 Hz F.
Sold as-is, Complete & New.

PHOTOTRANSISTOR
FPT-100
49c

N-CHANNEL J-FET
39c

ANTENNA PLUG & JACK
A-5411
AS USED ON AUTO RADIOS, GOOD ABOVE 150 MHz.

39c
10 Sets \$3.00
100 Sets \$25

"FIRE SALE"
ASSEMBLED & TESTED
PHOTOELECTRIC TYPE
117vac - NO BATTERY TO BUY!
4A 400v SCR OUTPUT

SMOKE ALARM
G-1012

"HOT" DEAL ON THE COULDS (LESS BELL) FROM A FIRE DEPT. OF SMOKE ALARM. BOARD CAN BE EASILY PUT INTO SERVICE AS A SENSITIVE SMOKE DETECTOR, OR USED FOR A NUMBER OF LIGHT SENSITIVE TASKS SUCH AS BURGLAR ALARMS, LIGHT RELAYS, EVEN FLASHERS! TO USE, CONNECT 117VAC DIRECTLY TO BOARD. CURRENT DRAIN IS ONLY 100mA. AND ATTACH A LAMP BELL, BUZZER, LAMP, ETC., UP TO 4 AMPS. TO THE OUTPUT. AS LONG AS A SMALL AMOUNT OF LIGHT IS ALLOWED TO FALL ON THE PHOTOTRANSISTOR, THE UNIT REMAINS "OFF". AS SOON AS THE LIGHT DROPS BELOW A MINIMUM LEVEL, THE OUTPUT BEGINS TO CYCLE ON & OFF AT 1/2 HZ RATE (UNTIL IT IS CHANGED TO CAUSE OUTPUT TO RETURN OR INSTEAD OF PULSING). ALARM FEATURES: PEACH INDICATION, SENSITIVE FET, SCR OUTPUT, PHOTOTRANSISTOR, ASSEMBLED & TESTED, WITH SCHEMATIC.

\$1.79
2/53

8 AA CELL BATTERY HOLDERS
2-1/4" x 90 x 1-1/8"
50c EA
10/14.50
100/14.00
G-1509

Visit Our STORE
2083 12TH ST. SARASOTA, FL
Lots of unadvised Specials!

DIAMONDBACK ELECTRONICS COMPANY
P. O. BOX 18095
SARASOTA, FLA. 33578
(813) 953-8828

*** FREE CATALOG ***

ALL MERCHANDISE 100% GUARANTEED
MINIMUM ORDER \$5
FL RESIDENTS ADD 4% SALES TAX
PLEASE INCLUDE SUFFICIENT POSTAGE

CIRCLE 42 ON FREE INFORMATION CARD


10 HOUR TAPE RECORDER

Top quality AC-DC cassette recorder, modified to provide 5 continuous hours of recording and playback of true fidelity, distortion-free sound on each side of cassette for a total of 10 hours. Unit has many special built-in features. TDK D-C180 cassette supplied. **\$155.00***



PHONE RECORDING ADAPTER

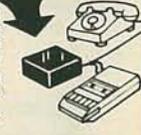Record incoming and outgoing calls automatically with this all solid state unit connected to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up, making a permanent record. Easily installed. No monthly charges. FCC APPROVED **\$24.50***



VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Excellent adjustable sensitivity. Voices or other sounds activate recorder. Uses recorder mike or remote mike. 2 1/4 x 1 3/4 x 3/4" **\$24.95***



AMAZING ELECTRONIC MICRO MINI MIKE

Among world's smallest, solid state, self contained WIRELESS MIKE. Mercury Bat. furn. Picks up most sounds and transmits without wires up to 300 ft. thru FM Radio. Tuneable. Use as mike, amp., alarm & alert system, baby sitter, hot line, etc. 2-1/4 x 3/4 x 1/2" **\$24.95*** FCC Approved



Phone call Adapter \$24.50*, VOX \$24.95*, MIKE \$24.95*. (* plus \$1.00 ea. postage & handling), 10 hr. Recorder \$155.00* (* plus \$4.00 postage & handling). California residents add tax. Mail Order, VISA, M/C, cod's okay, quantity discounts available. Money back guarantee. Free data.

AMC SALES, Dept. 19 9335 Lubec St., Box 928 Downey, CA 90241, Phone (213) 869-8519

CIRCLE 53 ON FREE INFORMATION CARD

ULN2001 High-current Drivers, Darlington's **75c**

P1103A 1024X1 Dynamic RAM **24c**

MH0026CJ DUAL CLOCK DRIVER **\$1.00**

8216 BUS DRIVER **\$1.99**

MODEL 7016A 16K DYNAMIC MEMORY ADD-ON

THE 7016A IS A 16K MEMORY ADD-ON FOR THE APPLE II* OR TRS-80*. THE KIT INCLUDES JUMPERS AND INSTRUCTION

California Computer Systems
Model 7016A **\$109.95**

2114L 1024 X 4 RAM **450ns \$4.75**

78H05 5 AMP 5 VOLT REGULATOR IN TO-3 PKG **\$6.95**

2716 450ns single+5V TI, HIT, INT, SGS 16K EPROM **\$38.50**

TASA's Solid State Micro Proximity Keyboards

Full 128 position 8-bit ASCII output plus continuous strobe parity select
Completely solid state, washable sealed construction
55 micro proximity sensor positions, three color coded to function
Immune to static charge or external noise
Low power requirement: 18V DC, 35mA (0.65 watt), built-in regulator

Additional TASA Model 55 Keyboard Features

- Tough polycarbonate surface, sealed from environment, fully resistant
- Built-in electronic link type and two-way return
- Electronic keypress to lock "key"
- Signal amplifier built-in, approximately 1 mips/second, no bounce
- Parallel output: Active pull-down direct TTL compatible (line read), open collector type
- CMOS compatible with pull-up resistor
- Continuous strobe and locked state signals for easy timing or logging
- Standard 0.156 inch center (3.96mm) 16 position dual in-line max. cable length connector

General Description

The TASA Model 55 and all other TASA keyboards are fully static CMOS based systems, combining the cost advantage of absolute simplicity of construction with fully integrated, complete circuitry for a "dumb" micro keypad. The built-in sealed electronics of the Model 55 ASCII keyboard enables full function capability in an enclosed 8 bit (8 pin) parallel output that is completely verified, processed and optimized, ready to connect directly to a systems data bus.

\$7500 FROM STOCK

Model 2016B 16K STATIC MEMORY

*** FULLY STATIC OPERATION ***
*** USES 2114 TYPE STATIC RAMS ***
*** +8 VDC INPUT AT LESS THAN 2 AMPS ***
*** BANK SELECT AVAILABLE BY BANK PORT AND BANK BYTE ***
*** PHANTOM LINE CAPABILITY ***
*** ADDRESSABLE IN 4K BLOCKS IN 4K INCREMENTS ***
*** 4K BLOCKS CAN BE LOCATED ANYWHERE WITHIN 64K BANK ***
*** MAY BE USED AS A 4K, 8K, 12K OR 16K MEMORY BOARD ***
*** LED INDICATORS FOR BOARD/BANK ACTIVE INDICATION ***
*** SOLDER MASK ON BOTH SIDES OF BOARD ***
*** SILK SCREEN WITH PART AND REFERENCE DESIGNATION ***

ASSEMBLED & TESTED California Computer Systems **\$297.95**

63011J 256X4 PROM **\$265**

SOROC TERMINAL 1Q 120 **\$759.00**

8038C VCO Waveform Gen w/sine **\$2.75**

7400 TTL	7400 TTL CON'T		
7400	.18	74107	.35
7408	.21	74141	.85
7410	.18	74155	.80
7412	.34	74157	.80
7413	.65	74161	.85
7416	.32	74165	.85
7420	.20	74175	.90
7425	.30	74181	1.35
7427	.32	74195	.95
7437	.28	74279	.75
7438	.28	74367	.75
7440	.18	74393	1.95
7451	.18		
7454	.18	74LS00	.40
7454	.18	74LS03	.35
7474	.35	74LS09	.55
7475	.55	74LS20	.40
7485	.85	74LS26	.50
7490	.40	74LS27	.45
7492	.50	74LS74	.99
7493	.50	74LS122	.55
7495	.70	74LS157	1.50

T.I./M.M.I.

74LS240	74LS241	74LS244
74LS240	IN	74LS244
74LS243	STOCK	74LS373
74LS374	LIMIT TO EACH	\$2.45

I.C. MASTER 1979 **\$34.95**

2708 450ns AMD, SGS 1024X8 EPROM **\$8.50**

MISC TTL CON'T			
74LS165	1.65	LM556	.85
74LS197	.75	LM711N/H	.38
74S03	.65	LM720N	2.75
74S05	.65	LM723N	.55
74S51	.60	LM725H	3.25
74S182	.99	LM733N	.95
		LM741N/H	.35
LM102H	3.00	LM747N	.80
LM108H	4.50	LM3900	.75
LM300H	1.25	TRANSISTORS	DIODES
LM301N	.35	2N2222A	5/1.00
LM311N	.79	2N2907A	5/1.00
LM320T5	1.25	2N3055	.85
LM320M5	1.25	2N3904	6/1.00
LM320T12	1.25	2N3906	6/1.00
LM320T15	1.25	2N4401	6/1.00
LM322N	1.75	2N4403	6/1.00
LM323K	5.50	IN4003	15/1.00
LM320K5	5.00	IN4005	12/1.00
LM340T5	1.25	IN4007	10/1.00
LM340T12	1.25	IN4148	20/1.00
LM340T15	1.25	1N5237B	10/1.00

CSC Logic Probe Kit. **\$17.95**

Complete, easy-to-follow instructions help make this a one-night project.

CONCORD COMPUTER COMPONENTS

1973 SO. STATE COLLEGE - ANAHEIM, CA. 92806

Visa - Master Charge
Check or M.O.
No COD

(714) 937-0641

Minimum Order-10.00
Add 1.50 for Frt.
Cal. Res. add 6%

CIRCLE 51 ON FREE INFORMATION CARD

AVAILABLE NOW!

ONLY \$3.95
Add \$1.00 for shipping

JAPANESE TRANSISTOR SUBSTITUTION MANUAL



An invaluable Japanese to Japanese substitution guide for approximately 3000 transistors

- Covers the 2SA, 2SD, 2SC and 2SK series
- Introduction includes a guide to understanding Japanese transistors
- A 90 page 8 1/2" by 11" soft cover book

PARTS PROCUREMENT PROBLEMS

FUJI-SVEA Has the Largest Inventory of Original Japanese Parts Anywhere

Seeking Original Japanese Replacement Parts for CB, TV and Stereo Repair Use?

TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9	TYPE	25-UP	10-24	1-9
2SA 473	.45	.55	.60	2SB 346	.30	.35	.40	2SC 693F	.20	.27	.30	2SD 234	.60	.70	.80				
2SA 483	2.00	2.20	2.50	2SB 367	1.10	1.25	1.40	2SC 696	1.00	1.20	1.30	2SD 235	.60	.70	.80				
2SA 484	1.50	1.75	1.95	2SB 368B	1.80	2.00	2.25	2SC 708	1.30	1.45	1.60	2SD 261	.35	.40	.45				
2SA 485	1.40	1.60	1.80	2SB 379	.70	.80	.90	2SC 710	.20	.27	.30	2SD 287	2.50	2.70	2.90				
2SA 489	1.10	1.25	1.40	2SB 381	.30	.35	.40	2SC 711	.20	.27	.30	2SD 300	4.50	5.00	5.60				
2SA 490	.80	.90	.90	2SB 400	.30	.35	.40	2SC 712	.20	.27	.30	2SD 313	.60	.70	.80				
2SA 493	.45	.53	.59	2SB 405	.30	.35	.40	2SC 715	.30	.35	.40	2SD 315	.60	.70	.80				
2SA 495	.30	.35	.40	2SB 407	.80	.90	1.00	2SC 717	.35	.40	.45	2SD 325	.60	.70	.80				
2SA 496	.50	.64	.70	2SB 415	.30	.35	.40	2SC 727	1.00	1.20	1.30	2SD 330	.60	.70	.80				
2SA 497	1.00	1.20	1.30	2SB 434	.80	.90	1.00	2SC 730	3.00	3.20	3.40	2SD 350	3.80	4.00	4.40				
2SA 505	.50	.64	.70	2SB 435	.90	1.10	1.20	2SC 731	2.50	2.70	2.90	2SD 380	5.20	5.40	5.95				
2SA 509	.30	.35	.40	2SB 440	.80	.90	1.00	2SC 732	.20	.27	.30	2SD 381	.85	1.00	1.10				
2SA 525	.50	.64	.70	2SB 449	1.30	1.45	1.60	2SC 733	.20	.27	.30	2SD 424	3.80	4.00	4.40				
2SA 530	1.50	1.70	1.90	2SB 461	.90	1.10	1.20	2SC 734	.20	.27	.30	2SD 425	.90	1.00	1.10				
2SA 537A	1.50	1.70	1.90	2SB 463	.90	1.10	1.20	2SC 735	.20	.27	.30	2SD 426	3.10	3.30	3.60				
2SA 539	.40	.45	.50	2SB 471	1.10	1.25	1.40	2SC 738	.20	.27	.30	2SD 427	1.80	2.00	2.25				
2SA 545	.53	.59	.64	2SB 472	2.10	2.25	2.80	2SC 756A	1.50	1.80	2.00	2SD 525	.90	1.10	1.20				
2SA 561	.30	.35	.40	2SB 473	.80	.90	1.00	2SC 756B	1.50	1.80	2.00	2SD 526	.60	.70	.80				
2SA 562	.30	.35	.40	2SB 474	.70	.80	.90	2SC 763	.35	.40	.45	2SK 198L	1.50	1.60	1.80				
2SA 564A	.20	.27	.30	2SB 481	.90	1.10	1.20	2SC 772	.30	.35	.40	3SK 22Y	1.40	1.60	1.80				
2SA 565	.70	.80	.90	2SB 482	.60	.70	.80	2SC 773	.35	.40	.45	3SK 39	.90	1.10	1.20				
2SA 566	2.50	2.70	3.00	2SB 507	.80	.90	1.00	2SC 774	1.00	1.20	1.30	3SK 40	.90	1.10	1.20				
2SA 606	1.00	1.20	1.30	2SB 509	1.10	1.20	1.30	2SC 775	1.40	1.60	1.80	3SK 41	1.30	1.45	1.60				
2SA 607	1.10	1.25	1.40	2SB 511	.70	.80	.90	2SC 776	2.00	2.20	2.50	3SK 45	1.30	1.45	1.60				
2SA 624	.70	.80	.90	2SB 514	.70	.80	.90	2SC 777	3.00	3.20	3.50	AN 203	1.50	1.70	1.90				
2SA 627	3.10	3.30	3.60	2SB 523	.70	.80	.90	2SC 778	2.90	3.20	3.40	AN 214O	1.50	1.70	1.90				
2SA 628	.30	.35	.40	2SB 526C	.70	.80	.90	2SC 781	1.90	2.10	2.40	AN 239	4.20	4.40	4.90				
2SA 634	.40	.45	.50	2SB 527	.90	1.10	1.20	2SC 783	2.10	2.50	2.80	AN 247	2.50	2.70	3.00				
2SA 640	.30	.35	.40	2SB 528D	.70	.80	.90	2SC 784	.30	.35	.40	AN 274	1.50	1.75	1.95				
2SA 642	.30	.35	.40	2SB 529	.70	.80	.90	2SC 785	.35	.40	.45	AN 313	3.00	3.20	3.40				
2SA 643	.30	.40	.45	2SB 530	3.20	3.40	3.70	2SC 789	.80	.90	1.00	AN 315	.60	.70	.80				
2SA 653	1.90	2.10	2.40	2SB 531	1.80	2.00	2.25	2SC 790	.80	.90	1.00	BA 511A	1.80	2.00	2.25				
2SA 659	.35	.40	.45	2SB 536	1.00	1.20	1.30	2SC 793	2.00	2.20	2.50	BA 521	1.90	2.10	2.40				
2SA 661	.50	.64	.70	2SB 537	1.00	1.20	1.30	2SC 799	2.00	2.20	2.50	HA 1151	1.50	1.75	1.95				
2SA 663	3.65	3.80	4.20	2SB 539	3.20	3.40	3.70	2SC 828	.20	.27	.30	HA 1156W	1.60	1.80	2.00				
2SA 666	.35	.40	.45	2SB 541	3.20	3.40	3.70	2SC 829	.20	.27	.30	HA 1306W	2.00	2.20	2.50				
2SA 671	.80	.90	1.00	2SB 554	5.00	6.00	6.60	2SC 830H	2.50	2.70	3.00	HA 1335	1.80	2.00	2.25				
2SA 672	.30	.35	.40	2SB 556	3.20	3.40	3.70	2SC 838	.35	.40	.45	HA 1339A	2.50	2.70	3.00				
2SA 673	.35	.40	.45	2SB 557	2.10	2.50	2.80	2SC 839	.30	.35	.40	HA 1342A	2.50	2.70	3.00				
2SA 678	.35	.40	.45	2SB 561B	.35	.40	.45	2SC 853	.70	.80	.90	HA 1362W	2.50	2.70	3.00				
2SA 679	4.20	4.40	4.90	2SB 564	.40	.53	.59	2SC 867	3.20	3.40	3.70	HA 1366W	2.50	2.70	3.00				
2SA 680	4.20	4.40	4.90	2SB 595	1.10	1.40	1.50	2SC 867A	3.20	3.40	3.70	LA 4031P	1.80	2.00	2.25				
2SA 682	.80	.90	1.00	2SB 596	1.10	1.40	1.50	2SC 870	.35	.40	.45	LA 4032P	1.80	2.00	2.25				
2SA 683	.30	.35	.40	2SB 600	5.00	6.00	6.60	2SC 871	.35	.40	.45	LA 4051P	1.80	2.00	2.25				
2SA 684	.35	.40	.45	2SC 183	.40	.53	.59	2SC 895	4.20	4.40	4.90	LA 4400	1.90	2.10	2.40				
2SA 695	.40	.53	.59	2SC 184	.40	.53	.59	2SC 897	2.00	2.20	2.50	LA 4400Y	2.00	2.20	2.50				
2SA 697	.40	.53	.59	2SC 185	.30	.35	.40	2SC 898	2.50	2.70	3.00	LA 4420	2.00	2.20	2.50				
2SA 699A	.50	.64	.70	2SC 283	.40	.53	.59	2SC 900	.20	.27	.30	LD 3001	2.00	2.20	2.50				
2SA 705	.40	.53	.59	2SC 284	.80	.90	1.00	2SC 923	.20	.27	.30	M5 1513L	2.00	2.20	2.50				
2SA 706	.85	1.00	1.10	2SC 317	.40	.53	.59	2SC 929	.20	.27	.30	STK 011	3.80	4.00	4.40				
2SA 715	.60	.70	.80	2SC 352A	2.00	2.20	2.50	2SC 930	.20	.27	.30	STK 013	7.60	8.00	8.80				
2SA 719	.30	.35	.40	2SC 353A	1.40	1.60	1.80	2SC 941	.20	.27	.30	STK 015	4.20	4.40	4.90				
2SA 720	.30	.35	.40	2SC 367	.60	.70	.80	2SC 943	.35	.40	.45	STK 435	4.50	5.00	5.60				
2SA 721	.30	.35	.40	2SC 369	.30	.35	.40	2SC 945	.20	.27	.30	STK 439	7.90	8.00	8.80				
2SA 725	.30	.35	.40	2SC 370	.20	.27	.30	2SC 959	1.00	1.20	1.30	TA 7045M	2.00	2.20	2.50				
2SA 726	.30	.35	.40	2SC 371	.30	.35	.40	2SC 971	.70	.80	.90	TA 7055P	2.00	2.20	2.50				
2SA 733	.20	.27	.30	2SC 372	.20	.27	.30	2SC 982	.70	.80	.90	TA 7061AP	.90	1.10	1.20				
2SA 738	.40	.53	.59	2SC 373	.20	.27	.30	2SC 983	.50	.64	.70	TA 7062P	1.10	1.25	1.40				
2SA 740	1.50	1.70	1.90	2SC 374	.30	.35	.40	2SC 1000	1.50	1.80	2.00	TA 7203P	2.50	2.70	2.90				
2SA 743A	.85	1.00	1.10	2SC 375	.30	.35	.40	2SC 1012	1.30	1.45	1.60	TA 7204P	2.00	2.20	2.50				
2SA 744	4.20	4.40	4.90	2SC 377	.30	.35	.40	2SC 1013	.50	.64	.70	TA 7205P	1.60	1.80	2.00				
2SA 745R	3.80	4.00	4.40	2SC 380	.20	.27	.30	2SC 1014	.50	.64	.70	TA 7222P	3.40	3.55	3.90				
2SA 747	4.20	4.40	4.90	2SC 381	.35	.40	.45	2SC 1017	.80	.90	1.00	TA 7310P	1.30	1.45	1.60				
2SA 748	.70	.80	.90	2SC 382	.35	.40	.45	2SC 1018	.60	.70	.80	TBA 8105H	1.90	2.10	2.40				
2SA 750	.35	.40	.45	2SC 383	.35	.40	.45	2SC 1030	1.80	2.10	2.40	TC 5080P	5.00	5.20	5.80				
2SA 755	.80	.90	1.00	2SC 387A	.35	.40	.45	2SC 1047	.35	.40	.45	TC 5081P	3.00	3.20	3.40				
2SA 756	2.30	2.40	2.65	2SC 388A	.40	.53	.59	2SC 1051	3.40	3.55	3.90	TC 5082P	4.40	3.55	3.90				
2SA 758	3.40	3.55	3.90	2SC 394	.20	.27	.30	2SC 1060	.70	.80	.90	UHC 001	4.20	4.40	4.90				
2SA 764	3.80	4.00	4.40	2SC 403	.30	.35	.40	2SC 1061	.70	.80	.90	UHC 002	4.20	4.40	4.90				
2SA 765	3.10	3.30	3.60	2SC 430	.50	.64	.70	2SC 1076	30.00	35.00	39.00	UHC 003	4.20	4.40	4.90				
2SA 774	.45	.50	.55	2SC 454	.35	.40	.45	2SC 1079	3.40	3.55	3.90	UHC 004	4.20	4.40	4.90				
2SA 777	.50	.64	.70	2SC 458	.20	.27	.30	2SC 1080	.30	.35	.40	UHC 005	5.00	5.40	5.90				
2SA 794A	.60	.70	.80	2SC 460	.35	.40	.45	2SC 1096	.45	.55	.60	uPC 20C	2.10	2.50	2.80				
2SA 798	.50	.55	.60	2SC 461	.35	.40	.45	2SC 1098	.50	.64	.70	uPC 563	1.90	2.10	2.40				
2SA 814	.70	.80	.90	2SC 478	.60	.70	.80	2SC 1111	2.10	2.50	2.80	uPC 575C2	1.30	1.45	1.60				
2SA 815	.60	.70	.80	2SC 481	1.30	1.40	1.50	2SC 1114	4.20	4.40	4.90	uPC 576	1.90	2.10	2.40				
2SA 816	.50	.64	.70	2SC 482	1.10	1.25	1.40	2SC 1115	2.50	2.70	3.00	uPC 592H	.70	.80	.90				
2SA 818	.70	.80	.90	2SC 484	1.30	1.40	1.50	2SC 1116	3.20	3.40	3.70	uPC 1001H	1.90	2.10	2.40				
2SA 837R	2.50	2.70	2.90	2SC 485	1.30	1.40	1.50	2SC 1116A	3.40	3.55	3.90	uPC 1008C	4.20	4.40	4.90				
2SA 839T	1.30	1.45	1.60	2SC 486	1.30	1.40	1.50	2SC 1124	.80	.90	1.00	uPC 1020H	1.90	2					

Continuity Tester and Flashlight



Convenient versatile tool for quickly checking continuity of dead circuits, switches, appliances, cords, fuses, motors, control equipment, coils and panel boards. Also tests circuits for low-resistance shorts and helps identify wires in multi-wire cables. Dozens of other uses. Plus the added convenience of a handy, durable flashlight. Uses two AA size penlight batteries (not furnished). Insulated clip prevents accidental shorting to case. Alligator clip has 48" lead with plug.

RT300 **\$7.95**

CONTINENTAL SPECIALTIES


Logic Monitor



The Logic Monitor allows you to check logic levels on all 16 pins of a ny DTL, TTL, or CMOS device. It has a typical input impedance of 100K ohms and weighs a mere 3 oz. (85 grams). It has an input volt. range of 4V to 15V and draws a max. of 100mA@10V

LM-1 **\$70.00**

Proto Clips

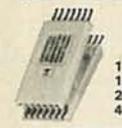

14-PIN CLIP	PC-14	\$ 4.50
16-PIN CLIP	PC-16	\$ 4.75
24-PIN CLIP	PC-24	\$10.00
40-PIN CLIP	PC-40	\$16.00

Proto Boards



PB-6	\$17.95
PB-100	19.95
PB-101	22.95
PB-102	26.95
PB-103	44.95
PB-104	55.95
PB-203	99.95
PB-203A	155.00
PB-203A-Kit	131.00

Jumbo 6-Digit Clock Kit



- Four .630" ht. and two .300" ht. common anode displays
- Uses MM5314 clock chip
- Switches for hours, minutes and hold functions
- Hours easily viewable to 30 feet
- Simulated walnut case
- 115VAC operation
- 12 or 24 hr operation
- Includes all components, case and wall transformer
- Size: 6 1/4" x 3 1/4" x 1 1/4"

JE747 **\$29.95**

JE701



- Bright .300 ht. comm. cathode display
- Uses MM5314 clock chip
- Switches for hours, minutes and hold modes
- Hrs. easily viewable to 20 ft.
- Simulated walnut case
- 115 VAC operation
- 12 or 24 hr. operation
- Incl. all components, case & wall transformer
- Size: 6 1/4" x 3 1/8" x 1 1/4"

6-Digit Clock Kit **\$19.95**


Regulated Power Supply



Uses LM309K. Heat sink provided. PC board construction. Provides a solid 1 amp @ 5 volts. Can supply up to +5V, +9V and +12V with JE205 Adapter. Includes components, hardware and instructions. Size: 3 1/2" x 5" x 2 1/4"

JE200 **\$14.95**

ADAPTER BOARD

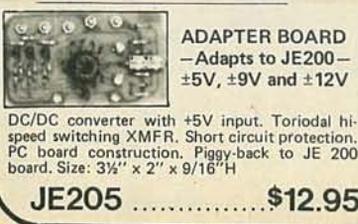

Adapts to JE200—±5V, +9V and ±12V

DC/DC converter with +5V input. Toroidal hi-speed switching XMF8. Short circuit protection. PC board construction. Piggy-back to JE 200 board. Size: 3 1/2" x 2" x 9/16" H

JE205 **\$12.95**

MICROPROCESSOR COMPONENTS

8080/8088 SUPPORT DEVICES		MICROPROCESSOR MANUALS	
8080A CPU	\$ 7.95	M-280 User Manual	\$7.50
8212 8-Bit Input/Output	3.25	M-CDP1802 User Manual	7.50
8214 Priority Interrupt Control	5.95	M-2850 User Manual	5.00
8216 Bi-Directional Bus Driver	3.49		
8224 Clock Generator/Driver	3.95		
8228 Bus Driver	3.49		
8228 System Controller/Bus Driver	4.95	2513(2140) Character Generator(upper case)	\$9.95
8238 System Controller	5.95	2513(2021) Character Generator(lower case)	9.95
8251 Prog. Comm. I/O (USART)	14.95	2516 Character Generator	10.95
8253 Prog. Interrupt Controller	14.95	MMS230M 2048-Bit Read Only Memory	1.95
8255 Prog. Paraph. I/O (PPI)	9.95		
8257 Prog. DMA Control	19.95		
8259 Prog. Interrupt Control	19.95		
8080/8088 SUPPORT DEVICES		ROM'S	
MC6800 MPU	\$14.95	1101 25X1 Static	\$1.49
MC6802CP MPU with Clock and Ram	24.95	1103 1024X1 Dynamic	.95
MC6810AIP 128X8 Static Ram	5.95	2101(8101) 25X4 Static	3.95
MC6821 Paraph. Inter. Adapt (MC6820)	7.49	2102 1024X1 Static	1.75
MC6828 Priority Interrupt Controller	12.95	2112 1024X1 Static	1.95
MC6830L8 1024X8 Bit ROM (MC6830-S)	14.95	2114 1024X4 Static 450ns low power	4.95
MC6850 Asynchronous Comm. Adapter	7.95	2114-3 1024X4 Static 300ns low power	11.95
MC6852 Synchronous Serial Data Adapt.	9.95	2114-4 1024X4 Static 450ns low power	10.95
MC6860 4-500 bps Digital MODEM	14.95	2114-5 1024X4 Static 300ns low power	11.95
MC6882 2400 bps Modulator	14.95	5101 25X4 Static	7.95
MC6880A Quad 3-State Bus. Trans. (MC6876)	2.25	5280/2107 4096X1 Dynamic	4.95
		7459 18X4 Static	1.75
MICROPROCESSOR CHIPS—MISCELLANEOUS		745200 25X1 Static Tristate	4.95
Z80(780C) CPU	\$14.95	93421 25X1 Static	2.95
Z80A(780-1) CPU	16.95	UPD414 4K Dynamic 16 pin	4.95
Z801802 CPU	18.95	(MK4027) UPD416 16K Dynamic 16 pin 250ns	9.95
2050 MPU	19.95	UPD416 16K Dynamic 16 pin 250ns	9.95
6502 CPU	11.95	(MK4116) TMS4044-4K Static	14.95
8035 8-Bit MPU w/clock, RAM, I/O lines	19.95	45H 1024X4 Static	14.95
8085 CPU	19.95	TMS4044-4K Static	9.95
TMS9900JL 16-Bit MPU w/hardware, multiply & divide	49.95	2117 16,384X1 Dynamic (house marked)	41.00
SHIFT REGISTERS		PROM'S	
MMS500H Dual 25 Bit Dynamic	5.50	MMS262 2KX1 Dynamic	4/1.00
MMS500H Dual 50 Bit Dynamic	50		
MMS504H Dual 16 Bit Static	.50	1702A 2048 FAMOS	\$5.95
MMS506H Dual 100 Bit Static	.50	2716HTEL 16K* EPROM	59.95
MMS10H Dual 64 Bit Accumulator	.89	M252516 16K* EPROM	49.95
MMS101H 500/512 Bit Dynamic	3.95	(2716) *Requires single +5V power supply	
2524T 1024 Dynamic	4.95	M25232 4KX3 EPROM	89.95
2518 Hex 32 Bit Static	2.95	2708 8K EPROM	10.95
2522 Dual 132 Bit Static	2.95	2716 T1 16K** EPROM	29.95
2524 512 Static	.99	**Requires 3 voltages, -5V, +5V, +12V	
2525 1024 Dynamic	2.95	5303 2048 FAMOS	14.95
2527 Dual 256 Bit Static	4.00	6301-1(7811) 1024 Tristate Bipolar	3.49
2528 Dual 250 Static	4.00	6330-1(7802) 256 Open C Bipolar	2.95
2529 Dual 240 Bit Static	2.95	82523 32X8 Open Collector	3.95
2532 Quad 80 Bit Static	6.95	82515 4096 Bipolar	19.95
3241 File	2.49	825123 32X8 Tristate	3.95
74LS670 4X4 Register File (TriState)	4.49	74186 512 TTL Open Collector	9.95
		74188 256 TTL Open Collector	3.95
		745287 1024 Static	2.95
UART'S			
A-Y-S-1013 30K BAUD	5.95		

JE600 HEXADECIMAL ENCODER KIT



FEATURES:

- Full 8 bit latched output for micro-processor use
- 3 User Define keys with one being bi-stable operation
- Debounce circuit provided for all 19 keys
- LED readout to verify entries
- Easy interfacing with standard 16 pin IC connector
- Only +5VDC required for operations

FULL 8 BIT LATCHED OUTPUT—19 KEYPAD

The JE600 Encoder Keyboard provides two separate hexadecimal digits produced from sequential key entries to allow direct programming for 8 bit microprocessor or 8 bit memory circuits. Three (3) additional keys are provided for user operations with one having a bistable output available. The outputs are latched and monitored with LED readouts. Also included is a key entry strobe.

JE600 **\$59.95**
Hexadecimal Keypad only **\$14.95**

62-KEY ASCII ENCODED KEYBOARD KIT



FEATURES:

- 60 Keys generate the full 128 characters, upper and lower case ASCII set
- Fully buffered
- 2 user-define keys provided for custom applications
- Caps lock for upper case only alpha characters
- Utilizes a 2376 (40 pin) encoder read only memory chip
- Outputs directly compatible with TTL/DTL or MOS logic arrays
- Easy interfacing with a 16-pin dip or 18-pin edge connector

JE610 **\$79.95**
62-Key Keyboard only . . . **\$34.95**

HICKOK LX303 Portable LCD Digital Multimeter



Big 3 1/2 inch high, 3 1/2" Digital Liquid Crystal Display • Over 200 hours of operation with a 9V battery
Automatic zero, polarity and average indication • 1000V DC F.S. sensitivity • 1% basic accuracy
19 ranges and functions • Rugged Cyclone® case and removable cover, stores test lead set.
* Full one year warranty.

SPECIFICATIONS: DC volts 8 ranges 0.1mv to 1000V Accuracy: ±0.5% (0.1V to 10V) ±0.5% (10V to 100V) ±0.5% (100V to 1000V) AC Volts 100V to 500V Accuracy: ±1.0% (10V to 100V) ±1.0% (100V to 500V) Resistance 10 Ohm to 20M Ohm Accuracy: ±1.0% (10 Ohm to 100 Ohm) ±1.0% (100 Ohm to 10K Ohm) ±1.0% (10K Ohm to 20M Ohm) Capacitance 10 pF to 100µF Accuracy: ±1.0% (10 pF to 10 nF) ±1.0% (10 nF to 10 µF) DC Current 10 ranges 10µA to 1000mA Accuracy: ±1.0% (10µA to 10mA) ±1.0% (10mA to 100mA) ±1.0% (100mA to 1000mA) DC Voltage and Resistance 0.1V to 1000V Accuracy: ±1.0% (0.1V to 10V) ±1.0% (10V to 100V) ±1.0% (100V to 1000V) READ RATE: 200/sec

PART NO.	DESCRIPTION	PRICE
RC-3	115V AC ADAPTER	7.50
CC-3	PADEDED CARRYING CASE	7.50
VP-10	210 DC PROBE ADAPTER (Up to 10K)	14.95
VP-40	40V DC PROBE	35.00
CS-1	10 Amp DC Current Shunt	14.95

LX303 Digital Multimeter **\$74.95**

\$10.00 Min. Order — U.S. Funds Only
Calif. Residents Add 6% Sales Tax
Postage — Add 5% plus \$1 Insurance (if desired)

Spec Sheets — 25¢
1980 Catalog Available — Send 41¢ stamp

Jameco ELECTRONICS

PHONE ORDERS WELCOME
(415) 592-8097

MAIL ORDER ELECTRONICS — WORLDWIDE
1355 SHOREWAY ROAD, BELMONT, CA 94002
ADVERTISED PRICES GOOD THRU FEBRUARY

FREE 1980 CATALOG

The Incredible "Pennywhistle 103"



\$139.95 Kit Only

The Pennywhistle 103 is capable of recording data to and from audio tape without critical speed requirements for the recorder and it is able to communicate directly with another modern terminal for telephone "hamming" and communications. In addition, it is free of critical adjustments and is built with non-precision, readily available parts.

Data Transmission Method Frequency-Shift Keying, full-duplex (half-duplex selectable).
Maximum Data Rate 300 Baud.
Data Format Asynchronous Serial (return to mark level required between each character).
Receive Channel Frequencies 2025 Hz for space; 2225 Hz for mark.
Transmit Channel Frequencies Switch selectable: Low (normal) = 1070 space, 1270 mark; High = 025 space; 2225 mark.
Receive Sensitivity -48 dbm acoustically coupled.
Transmit Level -15 dbm nominal. Adjustable from -8 dbm to -20 dbm.
Receive Frequency Tolerance Frequency reference automatically adjusts to allow for operation between 1800 Hz and 2400 Hz.
Digital Data Interface EIA RS-232C or 20 mA current loop (receiver is isolated and non-polar).
Power Requirements 120 VAC, single phase, 10 Watts.
Physical All components mount on a single 5" by 9" printed circuit board. All components included.
Requires a VOM, Audio Oscillator, Frequency Counter and/or Oscilloscope to align.

TRS-80 16K Conversion Kit

Expand your 4K TRS-80 System to 16K.
Kit comes complete with:
• 8 each UPD416-1 (16K Dynamic Rams) 250NS
• Documentation for conversion

TRS-16K **\$75.00**

JUST WRAP™



30 AWG wire • .025" square posts
Daisy chain or point-to-point • Built-in cut off
Includes 50 ft. wire • No stripping or slitting required—just wrap

Part No.	Wire Color	Price
JW-1-B	Blue	\$14.95
JW-1-W	White	14.95
JW-1-Y	Yellow	14.95
JW-1-R	Red	14.95

JUST WRAP™ Replacement Wire

Part No.	Color	Price
R-JW-B	Blue	50 ft. roll \$2.98
R-JW-W	White	50 ft. roll 2.98
R-JW-Y	Yellow	50 ft. roll 2.98
R-JW-R	Red	50 ft. roll 2.98

JUST WRAP™ Unwrap Tool \$3.49



JUST WRAP™ Kit • 50 ft. ea.; blue, white, red, yellow wire
• JUST WRAP Tool • Unwrapping Tool

JWK-6 **\$24.95**

Vacuum Vise



Vacuum-based light-duty vise for small components and assemblies. ABS construction. 1 1/2" jaws, 1 1/4" travel. Can be permanently installed.

VV-1 **\$3.49**


EPROM Erasing Lamp



- Erases 2708, 2716, 1702A, 52030, 52040, etc.
- Erases up to 4 chips within 20 minutes.
- Maintains constant exposure distance of one inch
- Special conductive foam liner eliminates static build-up
- Built-in safety lock to prevent UV exposure
- Compact — only 7-5/8" x 2-7/8" x 2"
- Complete with holding tray for 4 chips

UVS-11E **\$69.95**

JOYSTICK

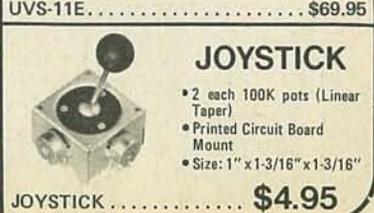

- 2 each 100K pots (Linear Taper)
- Printed Circuit Board Mount
- Size: 1" x 1-3/16" x 1-3/16"

JOYSTICK **\$4.95**

7400 TTL

SN7400N	.16	SN7473N	.35	SN74180N	.80
SN7401N	.18	SN7474N	.35	SN74181N	.80
SN7402N	.18	SN7475N	.40	SN74182N	.80
SN7403N	.18	SN7476N	.40	SN74183N	.80
SN7404N	.18	SN7477N	.50	SN74184N	.80
SN7405N	.20	SN7478N	.50	SN74185N	.80
SN7406N	.20	SN7479N	.50	SN74186N	.80
SN7407N	.20	SN7480N	.50	SN74187N	.80
SN7408N	.20	SN7481N	.50	SN74188N	.80
SN7409N	.20	SN7482N	.50	SN74189N	.80
SN7410N	.20	SN7483N	.50	SN74190N	.80
SN7411N	.25	SN7484N	.50	SN74191N	.80
SN7412N	.25	SN7485N	.50	SN74192N	.80
SN7413N	.25	SN7486N	.50	SN74193N	.80
SN7414N	.25	SN7487N	.50	SN74194N	.80
SN7415N	.25	SN7488N	.50	SN74195N	.80
SN7416N	.25	SN7489N	.50	SN74196N	.80
SN7417N	.25	SN7490N	.50	SN74197N	.80
SN7418N	.25	SN7491N	.50	SN74198N	.80
SN7419N	.25	SN7492N	.50	SN74199N	.80
SN7420N	.25	SN7493N	.50	SN74200N	.80
SN7421N	.25	SN7494N	.50	SN74201N	.80
SN7422N	.25	SN7495N	.50	SN74202N	.80
SN7423N	.25	SN7496N	.50	SN74203N	.80
SN7424N	.25	SN7497N	.50	SN74204N	.80
SN7425N	.25	SN7498N	.50	SN74205N	.80
SN7426N	.25	SN7499N	.50	SN74206N	.80
SN7427N	.25	SN7500N	.50	SN74207N	.80
SN7428N	.25	SN7501N	.50	SN74208N	.80
SN7429N	.25	SN7502N	.50	SN74209N	.80
SN7430N	.25	SN7503N	.50	SN74210N	.80
SN7431N	.25	SN7504N	.50	SN74211N	.80
SN7432N	.25	SN7505N	.50	SN74212N	.80
SN7433N	.25	SN7506N	.50	SN74213N	.80
SN7434N	.25	SN7507N	.50	SN74214N	.80
SN7435N	.25	SN7508N	.50	SN74215N	.80
SN7436N	.25	SN7509N	.50	SN74216N	.80
SN7437N	.25	SN7510N	.50	SN74217N	.80
SN7438N	.25	SN7511N	.50	SN74218N	.80
SN7439N	.25	SN7512N	.50	SN74219N	.80
SN7440N	.25	SN7513N	.50	SN74220N	.80
SN7441N	.25	SN7514N	.50	SN74221N	.80
SN7442N	.25	SN7515N	.50	SN74222N	.80
SN7443N	.25	SN7516N	.50	SN74223N	.80
SN7444N	.25	SN7517N	.50	SN74224N	.80
SN7445N	.25	SN7518N	.50	SN74225N	.80
SN7446N	.25	SN7519N	.50	SN74226N	.80
SN7447N	.25	SN7520N	.50	SN74227N	.80
SN7448N	.25	SN7521N	.50	SN74228N	.80
SN7449N	.25	SN7522N	.50	SN74229N	.80
SN7450N	.25	SN7523N	.50	SN74230N	.80
SN7451N	.25	SN7524N	.50	SN74231N	.80
SN7452N	.25	SN7525N	.50	SN74232N	.80
SN7453N	.25	SN7526N	.50	SN74233N	.80
SN7454N	.25	SN7527N	.50	SN74234N	.80
SN7455N	.25	SN7528N	.50	SN74235N	.80
SN7456N	.25	SN7529N	.50	SN74236N	.80
SN7457N	.25	SN7530N	.50	SN74237N	.80
SN7458N	.25	SN7531N	.50	SN74238N	.80
SN7459N	.25	SN7532N	.50	SN74239N	.80
SN7460N	.25	SN7533N	.50	SN74240N	.80

Cromemco Incorporated

8K Bytesaver II

Memory Capacity: 8K bytes
Memory Type: 2708 PROM or equivalent.
Memory Access Time: 450 nanoseconds
Wait States at 2MHz: none required
Wait States at 4MHz: one per machine cycle
Bus: S-100
Power Requirements: +5V @ 0.8A
 +18V @ 0.2A
 -18V @ 0.2A
Operating Environment: 0-55°C.

Cromemco's 8K BYTESAVER® card provides a built-in programmer for the popular 2708 PROM and has the capacity for a full 8K bytes of PROM memory storage. The BYTESAVER® II also offers a number of new features including convenient switch selection of board address and Cromemco's powerful memory bank selection. The BYTESAVER® II is assembled and tested (Model 8KBS-W) for \$245.

Assembled
8KBS-W \$245.00

TELEPHONE/KEYBOARD CHIPS

A-Y-5-9100	Push Button Telephone Dialer	\$14.95
A-Y-5-9200	Repertory Dialer	14.95
A-Y-5-9300	CMOS Clock Generator	4.95
A-Y-5-9400	Keyboard Encoder (88 keys)	14.95
HD0165	Keyboard Encoder (16 keys)	7.95
HD0166	Keyboard Encoder (16 keys)	7.95
74C323	Keyboard Encoder (16 keys)	7.95

ICM CHIPS

ICM7045	CMOS Precision Timer	24.95
ICM7205	CMOS LED Stowatch/Timer	19.95
ICM7207	Oscillator Controller	7.50
ICM7208	Seven Decade Counter	19.95
ICM7209	Clock Generator	6.95

NMOS READ ONLY MEMORIES

MC6571	128 X 9 X 7 ASCII Shifted with Greek	13.50
MC6574	128 X 9 X 7 Math Symbol & Pictures	13.50
MC6575	128 X 9 X 7 Alpha Control Char Gen	13.50

MISCELLANEOUS

TL074CN	Quad Low Noise Bi-Fet Op Amp	2.49
TL494CN	Switching Regulator	4.49
TL496CP	Single Switching Regulator	1.75
11C80	Divide 10/11 Prescaler	19.95
95F90	Hi-Speed Divide 10/11 Prescaler	11.95
95F91	Photo-Darlington Opto Isolator	14.95
95F92	Tot Pole Freq. Generator	17.50
MS00240	MS00240 MOS clock driver	3.75
DS0026CH	2.7V red num. display w/driver. logic chip	10.95
TL308	TV Camera Sync. Generator	14.95
MN5320	4 1/2 Digit DPM Logic Block (Special)	25.00
LD110/111	3 1/2 Digit A/D Converter Set	25.00
MC14433P	3 1/2 Digit A/D Converter	13.95

LITRONIX ISO-LIT 1

Photo Transistor Opto-Isolator
(Same as MCT 2 or 4N25)
49¢ each

SN 76477

SOUND GENERATOR
Generates Complex Sounds
Low Power - Programmable
\$3.95 each

TV GAME CHIP AND CRYSTAL

ATV 9-8500-1 and 2.01 MHz Crystal (Chip & Crystal)
Includes score display, 6 games and select angles, etc. **7.95/set**

EXAR

XR205	\$8.40	XR224CP	1.50
XR210	4.40	XR224A	4.25
XR215	4.40	XR256A	3.20
XR220	1.55	XR256B	2.99
XR225	1.55	XR256C	1.25
XR230	1.55	XR256D	1.25
XR235	1.55	XR256E	1.25
XR240	1.55	XR256F	1.25
XR245	1.55	XR256G	1.25
XR250	1.55	XR256H	1.25
XR255	1.55	XR256I	1.25
XR260	1.55	XR256J	1.25
XR265	1.55	XR256K	1.25
XR270	1.55	XR256L	1.25
XR275	1.55	XR256M	1.25
XR280	1.55	XR256N	1.25
XR285	1.55	XR256O	1.25
XR290	1.55	XR256P	1.25
XR295	1.55	XR256Q	1.25
XR300	1.55	XR256R	1.25
XR305	1.55	XR256S	1.25
XR310	1.55	XR256T	1.25
XR315	1.55	XR256U	1.25
XR320	1.55	XR256V	1.25
XR325	1.55	XR256W	1.25
XR330	1.55	XR256X	1.25
XR335	1.55	XR256Y	1.25
XR340	1.55	XR256Z	1.25

DIODES

TYPE	VOLTS V	PRICE	TYPE	VOLTS V	PRICE
1N4745	3.3	400M	1N4002	100 PIV 1 AMP	12/10
1N751	5.1	400M	1N4003	200 PIV 1 AMP	12/10
1N752	5.6	400M	1N4004	400 PIV 1 AMP	12/10
1N753	6.2	400M	1N4005	600 PIV 1 AMP	10/10
1N754	6.8	400M	1N4006	800 PIV 1 AMP	10/10
1N755	7.5	400M	1N4007	1000 PIV 1 AMP	10/10
1N756	8.2	400M	1N4008	500 PIV 2 AMP	6/10
1N757	9.0	400M	1N4009	1000 PIV 2 AMP	6/10
1N758	10.0	400M	1N4010	1500 PIV 2 AMP	6/10
1N759	11.0	400M	1N4011	2000 PIV 2 AMP	6/10
1N760	12.0	400M	1N4012	2500 PIV 2 AMP	6/10
1N761	13.0	400M	1N4013	3000 PIV 2 AMP	6/10
1N762	14.0	400M	1N4014	3500 PIV 2 AMP	6/10
1N763	15.0	400M	1N4015	4000 PIV 2 AMP	6/10
1N764	16.0	400M	1N4016	4500 PIV 2 AMP	6/10
1N765	17.0	400M	1N4017	5000 PIV 2 AMP	6/10
1N766	18.0	400M	1N4018	5500 PIV 2 AMP	6/10
1N767	19.0	400M	1N4019	6000 PIV 2 AMP	6/10
1N768	20.0	400M	1N4020	6500 PIV 2 AMP	6/10
1N769	21.0	400M	1N4021	7000 PIV 2 AMP	6/10
1N770	22.0	400M	1N4022	7500 PIV 2 AMP	6/10
1N771	23.0	400M	1N4023	8000 PIV 2 AMP	6/10
1N772	24.0	400M	1N4024	8500 PIV 2 AMP	6/10
1N773	25.0	400M	1N4025	9000 PIV 2 AMP	6/10
1N774	26.0	400M	1N4026	9500 PIV 2 AMP	6/10
1N775	27.0	400M	1N4027	10000 PIV 2 AMP	6/10
1N776	28.0	400M	1N4028	10500 PIV 2 AMP	6/10
1N777	29.0	400M	1N4029	11000 PIV 2 AMP	6/10
1N778	30.0	400M	1N4030	11500 PIV 2 AMP	6/10
1N779	31.0	400M	1N4031	12000 PIV 2 AMP	6/10
1N780	32.0	400M	1N4032	12500 PIV 2 AMP	6/10
1N781	33.0	400M	1N4033	13000 PIV 2 AMP	6/10
1N782	34.0	400M	1N4034	13500 PIV 2 AMP	6/10
1N783	35.0	400M	1N4035	14000 PIV 2 AMP	6/10
1N784	36.0	400M	1N4036	14500 PIV 2 AMP	6/10
1N785	37.0	400M	1N4037	15000 PIV 2 AMP	6/10
1N786	38.0	400M	1N4038	15500 PIV 2 AMP	6/10
1N787	39.0	400M	1N4039	16000 PIV 2 AMP	6/10
1N788	40.0	400M	1N4040	16500 PIV 2 AMP	6/10
1N789	41.0	400M	1N4041	17000 PIV 2 AMP	6/10
1N790	42.0	400M	1N4042	17500 PIV 2 AMP	6/10
1N791	43.0	400M	1N4043	18000 PIV 2 AMP	6/10
1N792	44.0	400M	1N4044	18500 PIV 2 AMP	6/10
1N793	45.0	400M	1N4045	19000 PIV 2 AMP	6/10
1N794	46.0	400M	1N4046	19500 PIV 2 AMP	6/10
1N795	47.0	400M	1N4047	20000 PIV 2 AMP	6/10
1N796	48.0	400M	1N4048	20500 PIV 2 AMP	6/10
1N797	49.0	400M	1N4049	21000 PIV 2 AMP	6/10
1N798	50.0	400M	1N4050	21500 PIV 2 AMP	6/10
1N799	51.0	400M	1N4051	22000 PIV 2 AMP	6/10
1N800	52.0	400M	1N4052	22500 PIV 2 AMP	6/10
1N801	53.0	400M	1N4053	23000 PIV 2 AMP	6/10
1N802	54.0	400M	1N4054	23500 PIV 2 AMP	6/10
1N803	55.0	400M	1N4055	24000 PIV 2 AMP	6/10
1N804	56.0	400M	1N4056	24500 PIV 2 AMP	6/10
1N805	57.0	400M	1N4057	25000 PIV 2 AMP	6/10
1N806	58.0	400M	1N4058	25500 PIV 2 AMP	6/10
1N807	59.0	400M	1N4059	26000 PIV 2 AMP	6/10
1N808	60.0	400M	1N4060	26500 PIV 2 AMP	6/10
1N809	61.0	400M	1N4061	27000 PIV 2 AMP	6/10
1N810	62.0	400M	1N4062	27500 PIV 2 AMP	6/10
1N811	63.0	400M	1N4063	28000 PIV 2 AMP	6/10
1N812	64.0	400M	1N4064	28500 PIV 2 AMP	6/10
1N813	65.0	400M	1N4065	29000 PIV 2 AMP	6/10
1N814	66.0	400M	1N4066	29500 PIV 2 AMP	6/10
1N815	67.0	400M	1N4067	30000 PIV 2 AMP	6/10
1N816	68.0	400M	1N4068	30500 PIV 2 AMP	6/10
1N817	69.0	400M	1N4069	31000 PIV 2 AMP	6/10
1N818	70.0	400M	1N4070	31500 PIV 2 AMP	6/10
1N819	71.0	400M	1N4071	32000 PIV 2 AMP	6/10
1N820	72.0	400M	1N4072	32500 PIV 2 AMP	6/10
1N821	73.0	400M	1N4073	33000 PIV 2 AMP	6/10
1N822	74.0	400M	1N4074	33500 PIV 2 AMP	6/10
1N823	75.0	400M	1N4075	34000 PIV 2 AMP	6/10
1N824	76.0	400M	1N4076	34500 PIV 2 AMP	6/10
1N825	77.0	400M	1N4077	35000 PIV 2 AMP	6/10
1N826	78.0	400M	1N4078	35500 PIV 2 AMP	6/10
1N827	79.0	400M	1N4079	36000 PIV 2 AMP	6/10
1N828	80.0	400M	1N4080	36500 PIV 2 AMP	6/10
1N829	81.0	400M	1N4081	37000 PIV 2 AMP	6/10
1N830	82.0	400M	1N4082	37500 PIV 2 AMP	6/10
1N831	83.0	400M	1N4083	38000 PIV 2 AMP	6/1

SEND FOR FREE CATALOG THIS MONTH'S SPECIALS

COMPUTER GRADES FACTORY FRESH

330,000 uf @ 5 VDC	\$2.00
150,000 uf @ 6 VDC	\$1.75
63,000 uf @ 7 VDC	\$1.00
7,000 uf @ 6 VDC	\$.35

ROTRON 3 BLADE COOLING FANS



- used but fully tested
- 4-5/8 x 4-5/8 x 1 1/2" Cat. No. 1161

ROTRON BISCUIT® FAN

\$9.45

The only air moving device that fits inside a 1 1/2" rack panel mounted instrument. High performance and low noise level.



Cat. No. 1510

TERMS: Add Postage
MINIMUM ORDER: \$10.00
Mastercharge and Visa accepted.

P.O. Box 2361R
Woburn, MA 01888
TEK-EL Corp.



NEW RETAIL STORE

27 GILL ST., WOBURN, MA 01801
Store & Warehouse open 9-5 Sat 9-1
Tel 617-935-7328

CIRCLE 36 ON FREE INFORMATION CARD

STEREO GRAPHIC EQUALIZER & PREAMP



Assembled & tested \$109.15
No additional components necessary for 12 VDC operation

- American made
- Glass epoxy Double sided p.t.h. circuit board
- ALLEN BRADLEY Type M conductive plastic volume control
- Adjustable input sensitivity: .3V to 3V RMS (Bourns MFT Dual trimmer)
- BIFET II Op amps: low noise, 13V/uS (TL074)
- Bourns 2% Resistor networks
- 1% Metal film resistors
- Instrument-type min. toggle switch (on-off-22 db mute)
- 2 accurate clipping lights: one on preamp stage, one on EQ stage
- All 3 LED's are Hi-brightness types (8mcd at 20mA DIFFUSED)
- Wiring & mtg. info included

80 WATT STEREO POWER AMPLIFIER

Assembled & tested circuit board.
American made \$67.89 (Class B) \$61.90
Ready to mount to heat sinks. Requires 27V split supply, 125W.
40W/ch 8 ohm Class AB .08% THD at 20 khz, full power (2% Class B)
Slew Rate 33V/uS, low TIM VI limiting

POWER SUPPLY KIT FOR ABOVE

Includes 125W xfmr, filter caps, rect, scheme \$33.00
Transformer only \$27.00 Schemo \$1.00
NE541 80V Audio Power Driver \$3.80
TIP 31A npn, TIP 32A pnp 60V compl. drivers \$5.1
TIP 35A npn 25A 60V output \$1.65
TIP 36A pnp compl to above \$1.73
VARO 331X 100V 3A FAST RECOVERY rect \$5.3
MR 751 6A 50V rect \$8.3
4700uF/35V filter \$1.50
The brightest LED! Stanley SBR 5531 8mcd@20mA diff \$5.5
ALLEN BRADLEY type M cond. plastic dual Aud. taper 100K, 1 cm cube 3mm (1/8") shaft w/mtg. hdw \$3.75
ALL PARTS PRIME, NO SURPLUS. MANY OTHER PARTS AVAILABLE. SEND \$1.00 FOR FLYER (WE INCL. WITH ORDER). \$10.00 MIN. ORDER
ONE DAY SHPMT 24 HOUR ORDER LINE (209) 577-4256 VISA/M.C. QB ELECTRONICS 2131 STONE MODESTO, CA 95351

CIRCLE 45 ON FREE INFORMATION CARD

CompuPro™ continues to deliver.

NEW YEAR SPECIAL: 16K DYNAMIC RAMS — 8/\$64!!

250 ns (4 MHz), 16K dynamic RAMs Expand memory in TRS-80™ I and II, Exidy, Apple, new PET, Heath H89, etc. Add \$3 for 2 dip shunts plus instructions for TRS-80™ expansion. Hurry... quantities are limited at this special price.

*TR-80 is a trademark of the Tandy Corporation.

MEMORY!

Choose from unkit (sockets, bypass caps pre-soldered in place), assembled, or boards qualified under our high-reliability Certified System Component (CSC) program (200 hour burn-in, extensive testing, immediate replacement in event of failure within 1 year of invoice date).

Name	Basic Items	Unit	Atom	CSC
8K Ecomoram** IIA	S-100	\$149	\$179	\$239
16K Ecomoram IV	S-100	\$289	\$339	\$429
16K Ecomoram VIIA-16	S-100	\$299	\$349	\$439
24K Ecomoram VIIA-24	S-100	\$419	\$499	\$605
16K Ecomoram IX-16	Dig Grp	\$319	\$379	n/a
32K Ecomoram IX-32	Dig Grp	\$559	\$639	n/a
32K Ecomoram X	S-100	\$549	\$669	\$789
32K Ecomoram XI	SBC/BLC	n/a	n/a	\$1050
16K Ecomoram XIII-16	S-100 (1)	\$349	\$419	\$519
24K Ecomoram XIII-24	S-100 (1)	\$469	\$539	\$649
32K Ecomoram XIII-32	S-100 (1)	\$579	\$699	\$849
16K Ecomoram XIV	S-100 (2)	\$299	\$359	\$459
16K Ecomoram XV-16	H8 (3)	\$329	\$395	n/a
32K Ecomoram XV-32	H8 (3)	\$599	\$729	n/a

**Ecomoram is a trademark of Godbout Electronics.
(1) Compatible with all bank select systems (Cromenco, Alpha Micro, etc.) addressable on 4K boundaries.
(2) Extended addressing (24 address lines) Single bank addressable on 4K boundaries.
(3) Bank select option for implementing memory systems greater than 64K.

TERMS: Call res add tax. Allow 5% for shipping, excess refunded. VISA / Mastercharge * call our 24 hour order desk at (419) 562-0036. C.O.D. with street address for UPS. Prices good through cover month of magazine.

GODBOUT


GODBOUT ELECTRONICS
Bldg. 725, Oakland Airport, CA 94614

CIRCLE 40 ON FREE INFORMATION CARD

BULLET ELECTRONICS

PO Box 401244R
Garland TX 75040

SE 01 Sound Effects Kit \$16.95

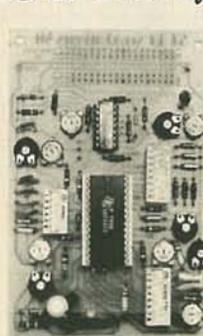

The SE-01 is a complete kit that contains all the parts to build a programmable sound effects generator. Designed around the new Texas Instruments SN76477 Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SLF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3 1/2" x 5" PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosions, Phasor Guns, Steam Trains, or almost any infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts, assembly manual, programming charts, and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100mW amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included).

- 76477 CHIP IS INCLUDED. EXTRA CHIPS \$2.95 EACH
- \$16.95 LESS SPEAKER & BATTERY

From T.I.: TL490 BAR/DOT DRIVER IC. Drives 10 LED's with adjustable analog steps. Units are cascadable up to 10 (100 steps). Drives LED's directly. Great for voltage, current, or audio displays. Similar in features to LM3914 with specs and circuit notes.

2.95

NEW!



NEW ITEMS

LM3046	(CA3046) Transistor Array	.75
RCA 40430	400V 6A TRIAC TO-66	.75
CA3086	RCA Transistor Array	.80
MC1438R	Power Op Amp/Driver	.50
1N4148	Prime, Full Lead	100/2.50
LM3302	Quad Comparator	.89
2SC1849	High Freq NPN TO-92	6/1.00
MPS A20	NPN GEN PUR	8/1.00

XAN SUPER DIGITS

.6" JUMBO LED
7 SEGMENT
RED

99¢



6640 COMMON ANODE
6920 COMMON CATHODE

NOW A SUPER READOUT AT A SUPER BUY! These are factory fresh prime LED readouts, not seconds or rejects as sold by others. Compare our price and send for yours today, but hurry, the supply is limited! SPECIFY: COMMON ANODE OR COMMON CATHODE

POTENTIOMETER ASSORTMENT

A mix of new, panel mount 3/8" bushing pots in various values. Some dual, some with switches.

10/2.00

1/2W RESISTOR ASSORTMENT

A good mix of 5% and 10% values in both full lead and PC lead devices. All new, first quality.

(Asst) 200 pieces/2.00

SLIDE SWITCH ASSORTMENT

An outstanding bargain. Includes miniature and standard sizes and multi-position units. All new first quality, name brand switches. Try one pack and you'll reorder more. SPECIAL — 12 for \$1.20 (Assortment)

PARTS

301 OP AMP & LEAD CAN	3/1.00
723 VOLT REG. 10 LEAD CAN	.50
*13741 FET INPUT 741 MINI DIP	3/1.10
30,000 @ 15V COMPUTER GRADE	2.10
2N4400 NPN GEN. PURPOSE	8/1.00
2N4402 PNP COMPLIMENT	8/1.00
2N6028 P.U.T. W/SPCS	.50
LM380 2W AUDIO IC W/SPCS	1.00
LM377 DUAL LM380 W/SPCS	2.50
*7815 VOLT REG. 1A 15V	.60
IL1 OPTO ISOLATOR MINI DIP	.60
*MEM 831 DUAL GATE MOSFET.	
DIODE PROTECTED, SIMILAR TO 40573	.50
MV1524 VARICAP DIODE 10 PFD	.40
1N4003 1A 200V DIODE	15/1.00
TIP30 TAB PNP POWER	3/1.00
*MC1351P FM IF DISC IC	.50

*INDICATES ITEM IS 'HOUSE NUMBERED'

LED'S

JUMBO GREEN	4/89
JUMBO RED	5/89
MEDIUM RED (1/4")	.15
MEDIUM GRN OR YELLOW	.16

7 WATT AUDIO AMP KIT

SMALL SINGLE HYBRID IC AND COMPONENTS FIT ON A 2" x 3" PC BOARD (INCLUDED). RUNS ON 12 VDC. GREAT FOR ANY PROJECT THAT NEEDS AN INEXPENSIVE AMP. LESS THAN 3% THD @ 5 WATTS. COMPATIBLE WITH SE-01 SOUND KIT. \$5.95


6 DIGIT AUTO/VAN CLOCK

- LARGE 1/2" CHARACTERS (LED)
- QUARTZ XTAL TIMEBASE
- ALARM & SNOOZE OPTIONS
- NOISE FILTERING
- EASY TO ASSEMBLE
- 4" x 3" x 1 1/2"
- DRILLED & PLATED PC BOARDS

\$16.95 COMPLETE KIT 12 VDC

ULTRASONIC RELAY KIT

INVISIBLE BEAM WORKS LIKE A PHOTO ELECTRIC EYE. USE UP TO 25 FT APART. COMPLETE KIT. ALL PARTS & PC BOARDS. \$21.50

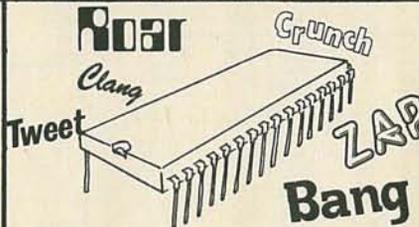

AY3-8910 PROGRAMMABLE SOUND GENERATOR

The AY3-8910 is a 40 pin LSI chip with three oscillators, three amplitude controls, programmable noise generator, three mixers, an envelope generator, and three D/A converters that are controlled by 8 BIT WORDS. No external pots or caps required. This chip hooked to an 8 bit microprocessor chip or Buss (8080, Z80, 6800 etc.) can be software controlled to produce almost any sound. It will play three note chords, make bangs, whistles, sirens, gunshots, explosions, bleets, whines, or grunts. In addition, it has provisions to control its own memory chips with two IO ports. The chip requires +5V @ 75ma and a standard TTL clock oscillator. A truly incredible circuit.

\$14.95 W/Basic Spec Sheet (4 pages)

60 page manual with S-100 interface instructions and several programming examples, \$3.00 extra

NPN HIGH VOLTAGE 2.00

VCEO = 450 VDC IC = 3A (5A Peak)
FOR TV HORIZONTAL SECTIONS; HIGH VOLTAGE REGULATORS
REPLACES: 2N5076, 2N5077, 2N5838, 2N5665, BDY94, BU126, 2SC2121, 2N5840, 2SC1046, 2N5666, TIP568 AND MANY OTHERS.

- NO C.O.D.'S
- SEND CHECK M.O. OR CHARGE CARD NO.
- PHONE ORDERS ACCEPTED ON VISA AND MASTERCARD ONLY. (214) 278-3553

- ADD 5% FOR SHIPPING
- TX. RES. ADD 5% STATE SALES TAX
- FOREIGN ORDERS ADD 10% (EXCEPT CANADA)

(20% AIRMAIL) U.S. FUNDS ONLY
catalog free on request

Radio Shack — Your No. 1 Parts Place™

Low Prices and New Items Every Day!

Low-Power Schottky ICs

Low As **49¢**

- 100% Prime
- Guaranteed Specs

Improved 5-volt logic devices use Schottky diode technology for minimum propagation delay and high speed at minimum power.

Type	Cat. No.	ONLY
74LS00	276-1900	.49
74LS02	276-1902	.59
74LS04	276-1904	.59
74LS08	276-1908	.49
74LS10	276-1910	.59
74LS13	276-1911	.99
74LS20	276-1912	.59
74LS27	276-1913	.59
74LS30	276-1914	.59
74LS32	276-1915	.69
74LS47	276-1916	1.29
74LS51	276-1917	.59
74LS73	276-1918	.69
74LS74	276-1919	.69
74LS75	276-1920	.99
74LS76	276-1921	.79
74LS85	276-1922	1.29
74LS90	276-1923	.99
74LS92	276-1924	.99
74LS93	276-1925	.99
74LS123	276-1926	1.19
74LS132	276-1927	.99
74LS151	276-1929	.99
74LS157	276-1930	1.19
74LS161	276-1931	1.49
74LS164	276-1932	1.49
74LS175	276-1934	1.19
74LS192	276-1935	1.49
74LS193	276-1936	1.49
74LS194	276-1937	1.49
74LS196	276-1938	1.59
74LS367	276-1935	1.19
74LS368	276-1936	1.19
74LS373	276-1943	2.39
74LS374	276-1944	2.39

4000-Series CMOS ICs

Type	Cat. No.	EACH
4001	276-2401	.69
4011	276-2411	.69
4012	276-2412	.79
4013	276-2413	.99
4017	276-2417	1.69
4020	276-2420	1.69
4021	276-2421	1.69
4023	276-2423	.69
4027	276-2427	.99
4028	276-2428	1.29
4046	276-2446	1.89
4511	276-2447	1.69
4049	276-2449	.79
4050	276-2450	.79
4051	276-2451	1.49
4066	276-2466	1.39
4070	276-2470	.79
4518	276-2490	1.49
4543	276-2491	1.99

All Prime from Major Semiconductor Manufacturers. Specs and Pin Out Diagram Included with Each Device.


MC14553 3-Digit BCD Counter IC **2⁹⁹**

CMOS chip replaces over 8 separate ICs in a digital display circuit. Input pulse shaping. Master reset pin. 16-pin DIP. 276-2498 2.99

RAM Memory ICs **2⁴⁹**

Low As **2⁴⁹**
 2102 1024 x 1 Array. Low-cost static memory chip. 16-pin DIP. Buy 8 and save!
 276-2501 2.49 Ea. or 8/14.95
 2114L 1024 x 4 Array. NMOS static RAM. 18-pin DIP. 276-2504 10.99


NEW! Rectangular LED Lamps

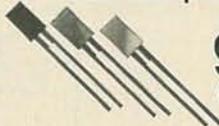

99¢
Pkg. of 2

High-brightness. Can be stacked vertically or horizontally. Max. forward current: 30 mA. Typical forward voltage: 2.5.
 276-070. Red. 2.99¢
 276-071. Green. 2.99¢
 276-072. Yellow. 2.99¢


NEW! Pair of LED Digits

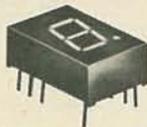

1⁹⁸

These 10mm 7-segment, red displays are ideal low-cost readouts for any projects. For multiplexed or direct drive. Max. forward current: 45mA/segment.
 Common Anode. 276-1643 2/1.98
 Common Cathode. 276-1644 2/1.98

NEW! Oscillator/Divider IC

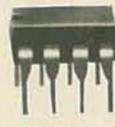

2⁶⁹

CMOS IC with 17 binary divider stages produces a highly stable 60 Hz square wave. Uses a TV 3.58 MHz crystal reference. Very low power operation over wide 3-15VDC range. 8-pin DIP.
 276-1769 2.69
 3.58 MHz Crystal 2.99

LED Bar/Dot Display Driver



3⁴⁹

LM3914N. Features 10 adjustable analog steps, bar or dot display mode. Current-regulated LED outputs. 8 to 25VDC supply. 18-pin DIP. 276-1707 3.49
 LM3915N. As above but with 3 dB log steps. 276-1708 3.49

NEW! Silicon Solar Cells



Low As **5⁹⁹**

High Efficiency

Convert light to electrical power. All deliver 0.45V at rated current. Use several in series/parallel for higher voltages or current.
 276-122. 1/2 3" cell. Rated 500 mA ... 5.99
 276-123. Full 3" cell. Rated 1 amp ... 8.99

Hall-Effect Sensors



1⁹⁸ Pkg. of 3

Open-Collector Output


Detects magnetic fields electronically. 750 gauss "on" threshold. Constant amplitude independent of frequency. Similar to type ULN 3006. Ideal for tach, position sensing, pulse counting. 5 to 16V supply. TO-92 case. With data.
 276-1646 Pkg. of 3/1.98

Unique LEDs



A Tri-Color. Displays red, green, yellow. Uniform light output of 0.6 mcd. Forward voltage: 2.2VDC. Max. current: 25mA. T1-¼ case style.
 276-035 1.39
 B Red Flasher. Operates directly from 5VDC power source. Pulse rate: 3 Hz. Max. current: 20 mA at 5VDC.
 276-036 1.29

10 Assorted Mini Reed Switches

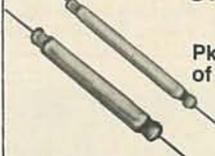

Pkg. of 10 **1⁹⁸**

Hermetically sealed. Gold-plated contacts close when magnetic field is present. Includes mini and micro types.
 276-1610 Pkg. of 10/1.98

Permanent Magnet Motors



99¢ Pkg. of 2

Up to 10,000 RPM at no load. Long leads for easy hook-up. Motor is 1 1/2 x 7/8". Shaft, 3/16 x 1/4".
 273-206 2/99¢

12/24-Hr. LCD Clock Module

19⁹⁵




Actual Size

24-Hour Alarm Shows Time/Day/Date

Complete clock module — just add switches and battery! 0.25" LCD display has built-in backlight, alarm set, PM and snooze indicators. Operates up to a year on single 1.5V battery. Accuracy: ± 13 seconds per month. 277-1005 19.95

Top Octave Synthesizer IC

NEW!
6⁹⁹

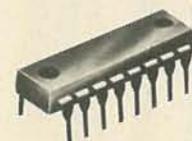


S50240. PMOS oscillator/frequency divider chip generates 13 equal-tempered notes from C₃ to C₆ to form the heart of any electronic keyboard instrument. CMOS compatible square wave outputs have 50% duty cycle for driving additional dividers or voice filters. Operates from single supply from 11 to 16 volts. 16-pin DIP.
 276-1780 6.99

4" Cooling Fan

12⁹⁵

Super Quiet Operation

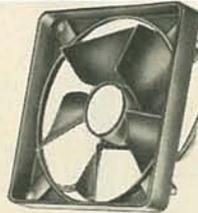

Ideal for cooling power supplies, microcomputers, hi-fi and Ham gear. Delivers up to 70 CFM. Diecast venturi. U.L. recognized motor. For 120VAC, 60 Hz.
 273-241 12.95

Dual Analog Delay IC

10⁹⁵

Continuously Variable—Many Audio Applications



SAD1024A. "Bucket Brigade" device has 2 separate 512-stage shift registers which can be used independently or in combination. Provides continuously variable electronic delay for complex audio signals to create reverb, echo, phase shift, chorus and vibrato effects. Reliable NMOS design operates from single supply. With applications circuits and data. 16-pin DIP. 276-1761 10.95

WHY WAIT FOR MAIL ORDER DELIVERY?
 IN STOCK NOW AT OUR STORE NEAR YOU!

Radio Shack®

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102
 OVER 7000 LOCATIONS IN 40 COUNTRIES

CIRCLE 10 ON FREE INFORMATION CARD

FEBRUARY 1980

101



NEW PRODUCTS!

Super Color S-100 Video Kit \$99.95
Expandable to 256 x 192 high resolution color graphics. 6847 with all display modes computer controlled. Memory mapped. 1K RAM expandable to 6K. S-100 bus 1802, 8080, 8085, 280 etc.

Gremlin Color Video Kit \$59.95
32 x 16 alpha/numerics and graphics; up to 8 colors with 6847 chip; 1K RAM at E000. Plugs into Super Elf 44 pin bus. Not expandable to high resolution Graphics.

Elf II Adapter Kit \$24.50
Plugs into Elf II providing Super Elf 44 and 50 pin bus plus S-100 bus expansion (With Super Expansion). High and low address displays, state and mode LED's optional \$18.00.

1802 16K Dynamic RAM Kit \$149.00
1802/S-100 expandable to 32K. Hidden refresh w/clocks up to 4 MHz w/no wait states Addl. 16K RAM \$79.00.

Quest Super Basic

Quest, the leader in inexpensive 1802 systems announces another first. Quest is the first computer worldwide to ship a full size Basic for 1802 systems. A complete function Super Basic by Ron Center including floating point capability with scientific notation (number range $\pm 1.7E^{99}$), 32 bit integer ± 2 billion; Multi dim arrays; String arrays; String manipulation; Cassette I/O. Save and load, Basic, Data and machine language programs; and over 75 Statements, Functions and Operators.

programs. Cassette version in stock now. ROM versions coming soon with exchange privilege allowing some credit for cassette version.

Super Basic on Cassette \$40.00

Tom Pittman's 1802 Tiny Basic Source listing now available. Find out how Tom Pittman wrote Tiny Basic and how to get the most out of it. Never offered before. \$19.00

S-100 4-Slot Expansion \$9.95

Super Monitor VI.1 Source Listing \$15.00

Coming Soon: Assembler, Editor, Disassembler, DA/AD, Super Sound/Music, EPROM programmer.

Easily adaptable on most 1802 systems. Requires 12K RAM minimum for Basic and User



RCA Cosmac Super Elf Computer \$106.95

Compare features before you decide to buy any other computer. There is no other computer on the market today that has all the desirable benefits of the Super Elf for so little money. The Super Elf is a small single board computer that does many big things. It is an excellent computer for training and for learning programming with its machine language and yet it is easily expanded with additional memory, Full Basic, ASCII Keyboards, video character generation, etc.

A 24 key HEX keyboard includes 16 HEX keys plus load, reset, run, wait, input, memory protect, monitor select and single step. Large, on board displays provide output and optional high and low address. There is a 44 pin standard connector slot for PC cards and a 50 pin connector slot for the Quest Super Expansion Board. Power supply and sockets for all IC's are included in the price plus a detailed 127 pg. instruction manual which now includes over 40 pgs. of software info. including a series of lessons to help get you started and a music program and graphics target game.

Before you buy another small computer, see if it includes the following features: ROM monitor; State and Mode displays; Single step; Optional address displays; Power Supply; Audio Amplifier and Speaker; Fully socketed for all IC's; Real cost of in warranty repairs; Full documentation.

Many schools and universities are using the Super Elf as a course of study. OEM's use it for training and research and development.

The Super Elf includes a ROM monitor for program loading, editing and execution with SINGLE STEP for program debugging which is not included in others at the same price. With SINGLE STEP you can see the microprocessor chip operating with the unique Quest address and data bus displays before, during and after executing instructions. Also, CPU mode and instruction cycle are decoded and played on 8 LED indicators.

Remember, other computers only offer Super Elf features at additional cost or not at all. Compare before you buy. Super Elf Kit \$106.95. High address option \$8.95. Low address option \$9.95. Custom Cabinet with drilled and labelled plexiglass front panel \$24.95. Expansion Cabinet with room for 4 S-100 boards \$41.00. NiCad Battery Memory Saver Kit \$6.95. All kits and options also completely assembled and tested.

An RCA 1861 video graphics chip allows you to connect to your own TV with an inexpensive video modulator to do graphics and games. There is a speaker system included for writing your own music or using many music programs already written. The speaker amplifier may also be used to drive relays for control purposes.

Questdata, a 12 page monthly software publication for 1802 computer users is available by subscription for \$12.00 per year.

Super Expansion Board with Cassette Interface \$89.95

This is truly an astounding value! This board has been designed to allow you to decide how you want it optioned. The Super Expansion Board comes with 4K of low power RAM fully addressable anywhere in 64K with built-in memory protect and a cassette interface. Provisions have been made for all other options on the same board and it fits neatly into the hardware cabinet alongside the Super Elf. The board includes slots for up to 6K of EPROM (2708, 2758, 2716 or TI 2716) and is fully socketed. EPROM can be used for the monitor and Tiny Basic or other purposes.

subroutines allowing users to take advantage of monitor functions simply by calling them up. Improvements and revisions are easily done with the monitor. If you have the Super Expansion Board and Super Monitor the monitor is up and running at the push of a button.

A 1K Super ROM Monitor \$19.95 is available as an on board option in 2708 EPROM which has been preprogrammed with a program loader/editor and error checking multi file cassette read/write software, (relocatable cassette file) another exclusive from Quest. It includes register save and readout, block mode capability and video graphics driver with blinking cursor. Break points can be used with the register save feature to isolate program bugs quickly, then follow with single step. The Super Monitor is written with

Other on board options include Parallel Input and Output Ports with full handshake. They allow easy connection of an ASCII keyboard to the input port. RS 232 and 20 ma Current Loop for teletype or other device are on board and if you need more memory there are two S-100 slots for static RAM or video boards. Also a 1K Super Monitor version 2 with video driver for full capability display with Tiny Basic and a video interface board. Parallel I/O Ports \$9.85, RS 232 \$4.50, TTY 20 ma I/F \$1.95, S-100 \$4.50. A 50 pin connector set with ribbon cable is available at \$15.50 for easy connection between the Super Elf and the Super Expansion Board.

Power Supply Kit for the complete system (see Multi-volt Power Supply).

Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

INTEGRATED CIRCUITS

7400TL	LM233K-5	5.95	CD4021	1.25
7400N	LM230K-12	5.00	CD4022	1.10
7400N	LM230K-15	5.00	CD4023	1.10
7400N	LM230T-5	1.80	CD4024	1.10
7400N	LM230T-8	1.80	CD4025	1.10
7400N	LM230T-12	1.80	CD4026	1.10
7400N	LM230T-15	1.80	CD4027	1.10
7400N	LM234N	1.15	CD4028	1.10
7400N	LM234N	1.15	CD4029	1.10
7400N	LM234N	1.15	CD4030	1.10
7400N	LM234N	1.15	CD4178	1.10
7400N				

SOUND EFFECTS GENERATOR BASIC KIT

Now CHANEY ELECTRONICS MAKES IT POSSIBLE TO BUILD YOUR OWN SOUND EFFECTS GENERATOR WITHOUT SPENDING A FORTUNE. WE SUPPLY YOU WITH THE TIGER 500 SOUND CHIP, PLUS AN ETCHED AND DRILLED GLASS EPoxy PC BOARD WITH SCHEMATICS AND LAYOUT INSTRUCTIONS. THIS BOARD MAKES IT SIMPLE TO BUILD A GENERATOR CAPABLE OF PRODUCING SOUND, LOCOMOTIVE, SIRENS, AIRPLANES, GLOCKS, ETC. DOES NOT REQUIRE DIP SWITCHES OR OTHER EXPENSIVE UNUSUAL COMPONENTS. YOU SUPPLY ONLY A FEW STANDARD RESISTORS, CAPACITORS, SWITCHES, POTS, SPEAKERS, 2N2222 TRANSISTOR AND 9V BATTERY.

BASIC KIT CONTAINING TIGER 500, PC BOARD AND INSTRUCTIONS ONLY \$5.95

2N2222 TRANSISTOR FOR ABOVE \$2.98 EA
IF YOU HAVE ALREADY PURCHASED THE TIGER 500 CHIP YOU MAY BUY THE PC BOARD AND INSTRUCTIONS ONLY. C23885 \$4.00

LASER SLAVE TRIGGER KIT

WE SUPPLY ALL THE COMPONENTS PLUS SCHEMATIC TO MAKE A SENSITIVE SLAVE TRIGGER WHICH WILL FIRE YOUR SLAVE STROBE WHEN YOU TRIGGER YOUR MASTER STROBE. C23888 \$1.50

LED Flasher Kit

Simple to build kit uses the popular 555 timer IC to generate flash from a 9V battery. LED comes complete with all parts, including the PCB which is not included. C23887 \$2.49

6VDC Xenon Flasher Kit

Battery operated Xenon flasher. Includes all parts and approx. 100' of 1/4" dia. 6VDC wire with all parts & PC board. (See battery) C23889 \$8.00

Digital Counting Module

Used for air traffic control and other applications. Includes all parts and approx. 100' of 1/4" dia. 6VDC wire with all parts & PC board. (See battery) C23890 \$1.79

120 VAC Xenon Strobe Kit

Complete variable speed xenon light kit. Contains all parts, PC board, lens and instructions. C23911 \$7.50

Wheel of Fortune

Popular game device uses LED's and transistors. Includes all parts and approx. 100' of 1/4" dia. 6VDC wire with all parts & PC board. (See battery) C23892 \$8.99

LED Panel Mounting Kit

12 sets for \$1.00

OPTO ISOLATORS

YOUR CHOICE \$49¢ EACH

RO170 Rectifier

100 for \$15.00

GE Sub-C Nicad

\$2.00

Tube Specials

2 for \$1.00

Alco Knob

2 for \$1.00

Horse shoe Tube

\$3.95

CHANEY electronics inc.

P.O. BOX 27038, DENVER, CO. 80227 (303) 781-5750

Send for our free giant catalog of unique items!!!



save on gas!

Enjoy the benefits of 20% better gas mileage, quicker starting, elimination of tune-ups, reduced pollution, and 50,000 miles on plugs and points.

Update your car with a TIGER solid state electronic ignition system. Easily installed in 30 minutes... even on new cars.

Tiger 500 CD Assembled \$49.95
Simplikit \$29.95

Postpaid USA.
Master Charge & BankAmericard accepted.

Tri-Star Corporation

Phone (303) 243-5200
P.O. Box 1727
Grand Junction, Colorado 81501

POTTER BRUMFIELD 4 PDT RELAYS

- 14 pin style
- 3 amp contacts
- 24 volt d.c. or 120 volt a.c. coil
- Used but fully tested

\$1.25 each
specify coil voltage
LARGE QUANTITIES AVAILABLE

REED RELAYS

9-15 VOLT D.C. NORMALLY OPEN

CONTACTS:
1 amp max. switch
2 amp max. carry

BODY SIZE:
approx. 1 inch long
1/4 inch high

S.P.S.T. 1500 ohm coil \$1.15 each
D.P.S.T. 1200 ohm coil \$1.30 each
3.P.S.T. 750 ohm coil \$1.50 each

2244 EDGEBOARD CONNECTOR TIN SOLDERABLE .156" x .200"

LARGE QUANTITIES AVAILABLE \$1.35 each 10 for \$12.50

LINEAR SLIDE POTS

- approx. 1 1/2 inch long
- 1 3/8 inch slide
- 10K or 20K

50¢ each SPECIFY VALUE

10 MEG POTS

- Standard 1/2 Watt Size
- 1/4" Dia
- 25 For \$5.00 4 For \$1.00

50K AUDIO SLIDE POTS

Knobs for Slide Pots 20¢ each 75¢ Each

- 3-1/2 inch long
- 2-3/4 inch slide

COMPUTER GRADE CAPACITORS

All Brand New

- 63,000 mfd 15 vdc 3" x 6" \$2.00
- 6,000 mfd 75 vdc 3" x 4" \$2.00
- 3,000 mfd 150 vdc 2 1/2" x 4 1/2" \$2.00
- 1,700 mfd 150 vdc 2 1/2" x 4 1/2" \$2.00
- 100,000 mfd 6 vdc 2 1/2" x 4 1/2" \$2.00

1 OHM 175 WATT WIRED WOUND RESISTOR

\$1.75 each

8 1/4" long, 1-1/8" dia.

C-H D.P.D.T. PRINTED CIRCUIT MIX TOGGLE

\$1.50 each
10 for \$12.50

- 6 amps @ 125 vac
- on-on

HOUSE MARKED DARLINGTON TRANSISTOR

SPECIFY 5 AMPS 65 WATTS FOR 80 VOLTS

SIMILAR: TIP 121NPN TIP 122 PNP T0220

HOUSE MARKED DARLINGTON TRANSISTOR

16 Amps 60 Volts 150 Watts

Similar to: M.J4030 PNP M.J4033 NPN \$1.50 each

Specify NPN for PNP

ALL ELECTRONICS CORP.

905 S. Vermont Ave. SEND FOR OUR FREE CATALOG
Los Angeles, CA 90006
(213) 380-8000

Store & Warehouse Hours
9 AM - 5 PM
Monday thru Friday
Saturday
10 AM - 3 PM

TERMS

- Quantities Limited
- Min. Order \$10.00
- Add \$1.50 Shipping USA
- Call for Add. 8% Prompt Shipping

CIRCLE 63 ON FREE INFORMATION CARD

CIRCLE 13 ON FREE INFORMATION CARD

CIRCLE 15 ON FREE INFORMATION CARD

CMOS (DIODE CLAMPED)	
4001	22 4024 - 75 4028 - 45 74C93 - 95
4002	22 4025 - 22 4071 - 10 74C151 - 175
4007	27 4027 - 45 4072 - 25 74C157 - 175
4009	45 4028 - 85 4021 - 22 74C160 - 175
4010	45 4029 - 95 4516 - 10 74C161 - 175
4011	22 4030 - 25 4918 - 125 74C163 - 100
4012	22 4032 - 65 74C164 - 100
4013	40 4042 - 35 74C173 - 130
4014	120 4044 - 35 74C202 - 27 74C174 - 130
4015	100 4045 - 35 74C203 - 27 74C175 - 130
4016	45 4046 - 195 74C10 - 27 74C192 - 130
4017	105 4049 - 75 74C14 - 120 74C193 - 140
4018	80 4050 - 45 74C20 - 27 74C194 - 140
4019	45 4052 - 100 74C42 - 90 74C202 - 50
4020	110 4051 - 110 74C73 - 75 74C214 - 190
4021	110 4053 - 110 74C74 - 50
4022	110 4055 - 125 74C83 - 130
4023	22 4056 - 70 74C86 - 50

PRINTED CIRCUIT BOARD

4" x 6" DOUBLE SIDED EPOXY BOARD 1/16" thick \$5.60

EPOXY glass vector board 1/16" thick with 1/10" spacing \$1.95

VERIPAX PC BOARD \$12.95
Our new Prototyping board is a hi density 4 1/2 x 6 1/2" single sided 1/16" G-10 board. It will hold 40, 24, 16 (34 units), 14 x 8 pin IC's. There are three buses, +5V, ground and a floating buss. There is a pad for a TO-220 regulator. There is a 22 pin edge connector with 156" spacing.

7 WATT LD-65 LASER DIODE IR \$8.95

25 watt Infra Red Pulse (SG 2006 equiv.)
Laser Diode (Spec sheet included) \$24.95

MINIATURE MULTI-TURN TRIM POTS

100, 2K, 5K, 10K, 20K, 1Meg, \$.75 each \$32.00

2N 3820 P FET \$ 45
2N 5457 N FET \$ 45
2N2646 UJT \$ 45
ER 900 TRIGGER DIODES 4 \$1.00
2N 6028 PROG UJT \$ 65

FP 100 PHOTO TRANS. \$ 50
RED, YELLOW, GREEN
LARGE LED'S 2" 6/\$1.00
RED/GREEN BIPOLAR LED'S 2" .95
TTL-118 OPTO-ISOLATOR \$.75
MCT-6 OPTO ISOLATOR \$.80
1 WATT ZENERS: 3.3, 4.7, 5.1, 5.6, 9.1, 10, 12, 15, 18, or 22V 6/\$1.00

Silicon Power Rectifiers

PRV	1A	3A	12A	50A	175A	240A
100	06	14	35	90	370	500
200	07	20	40	130	425	650
400	09	25	65	150	650	950
600	11	30	80	200	850	1250
800	15	35	100	250	1050	1650
1000	20	45	125	300	1250	2000

SAD 1024 a REDICOM 1024 stage analog "Bucket Brigade" shift register. \$9.95

IN 4148 (IN914) 15/\$1.00
1 or .01 of 25V ceramic disc caps. 16/\$1.00, \$5.00/100

REGULATORS

323K - 5V 3A \$.75
309K \$ 1.60
723 \$.50
320T \$.15

340K - 12, 15 or 24 V \$.95
340T - 5, 6, 8, 12 \$.75
24V5 - 15, 18 or 24V5 130 \$ 1.30
78M05 \$.75

TRANSISTOR SPECIALS

2N6233-NPN SWITCHING POWER \$1.95
MRF-8004 a CB RF Transistor NPN \$.75
2N3772 NPN Si TO-3 \$1.00
2N4908 NPN Si TO-3 \$1.00
2N5095 PNP Si TO-92 \$4.50
2N3137 NPN Si RF \$.55
2N3919 NPN Si TO-3 RF \$1.50
2N1420 NPN Si TO-5 \$3/5.00
2N3767 NPN Si TO-66 \$.70
2N2222 NPN Si TO-18 \$ 5/1.00
2N3055 PNP Si TO-3 \$.80
2N3904 NPN Si TO-92 \$6/81.00
2N3906 PNP Si TO-92 \$6/81.00
2N5296 NPN Si TO-220 \$.50
2N6109 PNP Si TO-220 \$.55
2N3638 NPN Si TO-5 \$5/1.00
MPS14 NPN Si \$4/81.00

TTL IC SERIES

7400	17	7400	37	74155	75
7401	17	7472	36	74157	85
7402	17	7473	35	74161	80
7403	17	7474	42	74162	120
7404	20	7475	48	74163	82
7405	24	7476	45	74164	85
7406	33	7480	45	74165	85
7408	27	7483	60	74170	160
7409	24	7485	75	74173	130
7410	17	7486	42	74174	80
7411	22	7487	60	74175	75
7412	22	7490	50	74176	75
7413	42	7491	55	74177	75
7414	20	7492	50	74180	75
7415	33	7493	50	74181	150
7416	37	7494	60	74182	150
7420	17	7495	60	74183	150
7425	45	7496	60	74191	120
7426	33	7497	35	74192	79
7427	25	7498	35	74194	85
7428	17	7499	39	74195	85
7432	27	74123	42	74196	85
7437	27	74126	46	74197	85
7438	27	74128	45	74209	75
7440	17	74145	75	74216	45
7441	85	74148	110	74225	225
7442	50	74152	80	74232	106
7445	70	74151	65	74241	105
7447	60	74153	55	74242	120
7448	75	74154	110	74248	110

NO. 30 WIRE WRAP WIRE SINGLE STRAND 100' \$1.40

ALCO MINIATURE TOGGLE SWITCHES
MTA 106 SPDT \$ 1.05
MTA 206 DPDT \$ 1.70
MTA 206 P-DPDT CENTER OFF \$ 1.85
MEO 206 P-DPDT CENTER OFF \$ 1.95
LEVER SWITCH \$ 1.85

TRIACS

PRV	1A	10A	25A
100	45	30	155
200	80	130	210
400	130	190	310
600	200	275	430

SCR'S

PRV	1A	6A	35A
100	45	60	140
200	80	130	210
400	130	190	310
600	200	275	430

DAC-08BC - 8 bit DAC - \$9.95

8" DISKETTES --- HARD SECTOR \$1.75, 10/\$16.00

CRYSTALS \$3.45 ea.
2.000 MHz 8.144 MHz
4.000 MHz 8.000 MHz
3.57 MHz 10.000 MHz
5.000 MHz 20.000 MHz
6.000 MHz

UNIVERSAL 4Kx8 MEMORY BOARD KIT \$69.95

32-2102-1 fully buffered, 16 address lines, on board decoding for any 4 of 64 pages, standard 44 pin buss, may be used with F-8 & KIM

SILICON SOLAR CELLS

4" diameter, 4V at 1 AMP.....\$10.00

LED READOUTS

FC8 8024 4 digit DL-707 C.A. 3" \$ 7.50
C.C. 8" display \$5.95 DL 747 C.A. 6" \$1.50
FD 503 C.C. 5" \$5.85 HP3400 3" C.A. \$1.95
FND S10 C.C. 5" \$5.85 HP3405 8" C.C. \$1.95

SOLID STATE SALES

P.O. BOX 74D
SOMERVILLE, MASS. 02143 TEL. (617) 547-7053

WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM

TERMS: FOB Cambridge, Mass. Send Check or Money Order. Include Postage, Minimum Telephone, C.O.D. Purchase Order or Charge \$20.00. Minimum Mail Order \$5.00.

CIRCLE 21 ON FREE INFORMATION CARD

COMPARE THESE PRICES!

POPULAR COMPONENTS INC.

OFFERS YOU:

- MONEY SAVING DISCOUNT PRICES
- HARD TO GET COMPONENTS
- TOP SELECTION OF FIRST QUALITY POPULAR COMPONENTS
- ALL COMPONENTS GUARANTEED TO BE FACTORY PERFECT (MONEY BACK GUARANTEE)

UARTS	
AY-5-1013A	\$4.20
TR1602B	3.90
AY-3-1015D	5.20
AY-3-1014A	6.75
TELECOMMUNICATIONS	
AY-5-9100	Push Button Telephone Dialler Circuit 13.95
AY-5-9200	Repertory Dialler 13.95
AY-5-9500	C-MOS Generator 4.25
GENERATOR/ENCODERS	
RO-3-2513	Character Generator (upper or lower case) 8.80
AY-5-2376	Keyboard Encoder 12.10
AY-5-3600	Keyboard Encoder 12.95
8080/8035/8085 SUPPORT CHIPS	
UPD8080AFC	8-Bit N-Channel Microprocessor 5.85
UPD8085AC	Single Chip 8-Bit N-Channel Microprocessor 12.75
UPD8035	Single Chip 8-Bit Microcomputer 18.95
UPD8155C	2048 Bit Static MOS RAM with I/O Ports & Timer 18.95
UPB8212C	8-Bit I/O Port 3.95
UPB8214C	Priority Interrupt Controller 3.90
UPB8216C	4-Bit Parallel Bidirectional Bus Driver 3.95
UPB8224C	Clock Generator & Driver for 8080A Processor 2.85
UPB8226C	4-Bit Parallel Bidirectional Bus Driver 3.35
UPB8228C	8080A System Controller & Bus Driver 3.95
UPB8238C	8080A System Controller & Bus Driver 3.95
UPD8243C	I/O Expander for Single Chip 8-Bit Microcomputer 9.90
UPD8251C	Prog. Communication Interface 6.60
UPD8253C	Prog. Interval Timer 13.95
UPD8255C	Prog. Peripheral Interface 6.60
UPD8257C	Prog. DMA Controller 16.95
UPD8259C	Prog. Interrupt Controller 14.90
MICROPROCESSOR CHIPS	
UPD780C(Z80)	8-Bit N-Channel Microprocessor—Z80 compatible 13.50
UPD780C(Z80A)	8-Bit N-Channel Microprocessor—Z80 compatible (4MHz) 15.95
CONTROLLER CHIPS	
UPD765	Single/Double Density Floppy Disk Controller 59.95
FD1771B	Single Density Floppy Disk Controller 59.95
FD1791B	Dual Density Floppy Disk Controller (IBM compatible) 59.95
CRT5027	CRT Controller 39.95
UPD372D	Floppy Disk Controller 39.95
RAMS	
UPD2102ALC-4	1024 Bit Fully Decoded Static MOS RAM (low power) 2.60
UPD2101ALC-4	1024 Bit (256x4) Static MOS RAM with separate I/O (low power) 2.75
UPD2111ALC-4	1024 Bit (256x4) Static MOS RAM with common I/O & output disable (low power) 3.50
2114UCB	4K Static RAM 450ns 6.95
UPD2147D	4K x 1 Bit Static RAM 14.75
UPD4104C	4K x 1 Bit NMOS RAM 11.85
UPD5101C-E	1024 Bit (256x4) Static CMOS RAM 4.35
UPD4114C	4K Dynamic RAM 4.95
UPD416C	16K (16384x1) Bit Dynamic MOS RAM 12.75
BAUD RATE GENERATORS	
COM5016	Dual Baud Rate Generator 15.50
COM5036	Dual Baud Rate Generator 15.50
BR1941L	Dual Baud Rate Generator 9.80
PROM	
C2716	TMS2516 UV Prom 44.75
SOUND GENERATOR	
SN76477	Complex Sound Generator 3.65
ASTRO	
COM1671	Asynchronous/Synchronous Receiver-Transmitter 24.50
LINEAR	
SG3524M/J	Switching Regulator Converter 5.40

TO ORDER: Specify part number, name, price & quantity. Check or money order must accompany order. Add \$1.75 for postage & handling. New York State residents add 7% sales tax. Foreign Customers: Payment must be in U.S. dollars by international postal money order or cashier's check. Add 20% for shipping & handling.

FREE WITH EACH ORDER. WE WELCOME INQUIRIES FROM MANUFACTURERS, DISTRIBUTORS, & INSTITUTIONS. NO C.O.D., MINIMUM ORDER \$10.00.

(PRICES GOOD THRU FEBRUARY 15, 1980)

Order Today from:
POPULAR COMPONENTS INC.
 1145 WALT WHITMAN RD.
 P.O. BOX 866 DEPT. RE20
 MELVILLE, N. Y. 11747

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number Page

53	AMC Sales	96
23	Aaron-Gavin Instruments	38
16	Active Electronics	95
—	Advance Electronics	37
3	Advanced Computer Products	105
15	All Electronics	104
11	American Antenna	Cov. 4
43	B & K Precision Dynascan Corp.	80
52	Babylon Electronics	94
—	Bagnall Electronics	85
—	Karel Barta	102
—	Bullet Electronics	100
—	Burdex Security	86
56	Buss	82
41	CFR Associates	102
63	Chaney Electronics	104
—	CIE-Cleveland Institute of Electronics	18-21
—	Command Productions	86
51	Concord-Computer Components	96
31	Continental Specialties	Cov. 2
22	Cooper Group-Electronics Div.	5
—	Dage Scientific	85
28	Delta Electronics	86
30	Delta Products	23
48	Deltroniks	90
42	Diamondback Electronics	96
12	Digi-Key	91
—	Digital Research Corporation (DRC)	92
47	Electronic Supermarket	102
—	Electronics & Control Engineer's Book Club—McGraw-Hill Book Div.	28-31
46	Electronics Book Club (TAB)	17
25	Enterprise Development Corp.	83
—	Exar	33
—	Fair Radio Sales	94
39	Fluke	7
—	Fordham Radio Supply	93
27,64	Formula International	88-89
66	Fuji-Svea	97
40	Godbout Electronics	100
—	Grantham College of Engineering	34
67,4	Heath	27,41
59	Hickok Electrical Instruments	2
32	Hitachi-Denshi	42
55	Hobby World	102
—	Information Unlimited	102
57	International Electronics	92
—	JS & A	1
18,19	Jameco Electronics	98-99
7	Jensen Tools	80
17	Jim-Pak	76-77
9	Kester Solder	34
—	Lakeside Industries	102
38	McGraw-Hill Book Company	78
14	Meshna	90
33	Micro Mart	92
—	National Radio Institute (NRI)—Div. of McGraw-Hill	8-11
—	National Technical Schools	72-75
58	Netronics	25
29	O.K. Machine & Tool	24
—	Olson Electronics	94
5	Optoelectronics	Cov. 3

60	PAIA	83
54	PTS Electronics	84
24	Pac Com	80
49	Panavise	36
62	Phipps & Bird	38
34	Poly Paks	90
26	Popular Components	106
45	QB Electronics	100
6	Quest	103
10	Radio Shack	101
35	Ramsey Electronics	87
8	Rye Industries	82
—	Sabtronics	14-15
37	Howard W. Sams	35
—	Sharper Image	13
—	Sheldahl	82
61	Shure Brothers	32
21	Solid State Sales	104
65	Sony Video Products	79
—	Spacecoast Research	85
—	Surplus Center	86
36	Tek-El	100
—	Texas Instruments	81
13	Tri-Star	104
—	USI	94
20	Wersi Electronics	36
2	Weston Instruments	22
50	Zemco	26

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE

name (please print)

address

city state zip code

Mail to: Radio-Electronics
 SUBSCRIPTION DEPT., P.O. BOX 2520,
 BOULDER, COLO. 80322

When quality counts

Do not be fooled by the low prices, these brand new lab quality frequency counters have important advantages over instruments costing much more. The models 7010 and 8010 are not old counters repackaged but 100% new designs using the latest LSI state-of-the-art circuitry. With only 4 IC's, our new 7010 offers a host of features including 10 Hz to 600 MHz operation, 9 digit display, 3 gate times and more. This outperforms units using 10-15 IC's at several times the size and power consumption. The older designs using many more parts increase the possibility of failure and complexity of troubleshooting. Look closely at our impressive specifications and note you can buy these lab quality counters for similar or less money than hobby quality units with TV xtal time bases and plastic cases!

Both the new 7010 and 8010 have new amplifier circuits with amazingly flat frequency response and improved dynamic range. Sensitivity is excellent and charted below for all frequencies covered by the instruments.

Both counters use a modern, no warm up, 10 MHz TCXO [temperature compensated xtal oscillator] time base with external clock capability - no economical 3.579545 MHz TV xtal.

Quality metal cases with machine screws and heavy gauge black anodized aluminum provide RF shielding, light weight and are rugged and attractive - not economical plastic.

For improved resolution there are 3 gate times on the 7010 and 8 gate times on the 8010 with rapid display update. For example, the 10 second gate time on either model will update the continuous display every 10.2 seconds. Some competitive counters offering a 10 second gate time may require 20 seconds between display updates.

The 7010 and 8010 carry a 100% parts and labor guarantee for a full year. No "limited" guarantee here! Fast service when you need it too, 90% of all serviced instruments are on the way back to the user within two business days.

We have earned a reputation for state-of-the-art designs, quality products, fast service and honest advertising. All of our products are manufactured and shipped from our modern 13,000 square foot facility in Ft. Lauderdale, Florida.

When quality counts...count on Optoelectronics.

MODEL 8010 1 GHz

CIRCLE 5 ON FREE INFORMATION CARD

MODEL 7010 600 MHz



- 100% U.S.A. FACTORY ASSEMBLED
 - 100% PARTS & LABOR YEAR GUARANTEE
 - CERTIFIED NBS TRACEABLE CALIBRATION
 - EXTERNAL CLOCK INPUT
 - DISPLAY HOLD FUNCTION
 - 9 RED LED DIGITS .4" HIGH
 - .1 Hz RESOLUTION
 - 0.1 PPM 10 MHz TCXO TIME BASE
 - LAB/PORTABLE-AC ADAPTER INCLUDED
 - 1 MEGOHM & 50 OHM INPUTS
 - STATE-OF-THE-ART LSI DESIGNS
 - COMPREHENSIVE USER MANUAL PROVIDED
- COMPACT SIZES—7010- 1-3/4" Hx4-1/4" Wx5-1/4" D 8010- 3" Hx7-1/2" Wx6-1/2" D

MODEL	\$ PRICE	RANGE 10Hz to	LED DIGITS	SENSITIVITY				GATE TIMES	RESOLUTION			TCXO TIME BASE		EXT CLOCK INPUT	NI-CAD BATT PACK
				25-250 MHz	50 OHM INPUT 250-450 MHz	450 MHz-1GHz	HI-Z INPUT 10Hz - 60 MHz		12 MHz	50 MHz	MAX. FREQ.	20°-40° C	FREQ.		
7010 * 7010.1	145.00 225.00	600 MHz	9	5-20 mV	10-30 mV	20-40 mV to 600 MHz	1-10 mV	{3} .1, 1, 10 SEC	.1 Hz	1 Hz	10 Hz 600 MHz	1 PPM 0.1 PPM	10 MHz	YES OPTION \$25.	YES OPTION \$15.
8010 * 8010.1	325.00 405.00	1 GHz	9	1-10 mV	5-20 mV	10-25 mV	1-10 mV	{8} .01-20 SEC	.1 Hz	1 Hz	10 Hz 1 GHz	1 PPM 0.1 PPM	10 MHz	YES STD	YES OPTION \$39.

* Has precision 0.1 PPM TCXO time base.

MODEL 7010
#7010 600 MHz Counter - 1 PPM TCXO \$145.00
#7010.1 600 MHz Counter - 0.1 PPM TCXO \$225.00

OPTIONS
#NI-Cad-701 Ni-Cad Battery Pack & charging circuitry
Installs inside unit \$ 15.00
#EC-70 External Clock input, 10 MHz \$ 25.00
#CC-70 Carry Case, Padded Black Vinyl \$ 8.95

MODEL 8010
#8010 1 GHz Counter - 1 PPM TCXO \$325.00
#8010.1 1 GHz Counter - 0.1 PPM TCXO \$405.00
#8010.1-13 1.3 GHz Counter - 0.1 PPM TCXO \$495.00

OPTIONS
#NI-Cad-801 Ni-Cad Battery Pack & charging circuitry
Installs inside unit \$ 39.00
#CC-80 Carry Case, Padded Black Vinyl \$ 9.95

ACCESSORIES
#TA-100 Telescope Ant with Right Angle BNC \$ 9.95
#P-100 Probe, 50 ohm, 1x \$13.95
#P-101 Probe, Lo-Pass, Audio Usage \$16.95
#P-102 Probe, Hi-Z, General Purpose \$16.95



ORDER FACTORY DIRECT • CALL TOLL FREE



Optoelectronics inc

5821 N.E. 14th Avenue, Fort Lauderdale, Florida 33334

1-800-327-5912

FROM FLORIDA (305) 771-2051/2

TERMS: Orders to U.S. and Canada, add 5% for shipping, handling and insurance to a maximum of \$10.00. All other orders add 10%. C.O.D. collection fee \$1.00. Orders under \$15.00 add extra \$1.00 handling. Regular checks must clear before order is shipped. Florida residents add 4% sales tax.

In one year our **K40** antenna has become the largest selling CB antenna in the world!

1. It's the most expensive ...

2. It's made better...

3. It's proven best!

...Here's what the leading CB publications said.

\$42.50 suggested retail

And when you pay more, you expect more!

MORE PERFORMANCE:

The K40 is guaranteed to transmit further or receive clearer than any antenna it replaces. We know it will. We've tested it with 771 CB'ers just like you for one year.

MORE FLEXIBILITY:

You can fit your K40 to any mounting surface. It will fit any vehicle you'll ever own! That includes choppers, dune buggies, gutters, mirror mounts, luggage racks, trunks, hatchbacks, through roofs, semis, pick ups and RV's.

MORE QUALITY:

It's not imported. It's not made in Taiwan, Korea or Japan. It's American made in an American town. It's made with better materials that cost more and by professional people we pay more. And we designed it right here in the U.S.A.

*Including optional mounts at extra cost.

... This Antenna is so **DYNAMITE** you receive a ...

DOUBLE GUARANTEE

GUARANTEE I: The K-40 will transmit farther and receive more clearly than the antenna it replaces or the customer will receive a prompt and full refund from the Registered K-40 Dealer who installed and tuned it.

GUARANTEE II: Unconditionally guaranteed for 12 months. Guaranteed against cracking, chipping, or rusting. Guaranteed against mechanical failure. Guaranteed against electrical failure. Guaranteed against accidental breakage. No exclusions. No gimmicks. For a full 12 months.



CB TIMES: "... it's not often that a product bursts onto the market scene, dominates and improves CB'ing for everyone. American Antenna and the K40 are doing it—repeated tests showed the K40 could out-perform the major competitive brands."

RADIO-ELECTRONICS: "The results of our tests showed that, in three different positions of the monitoring receiver, the model K40 equaled or out-performed the competitive antenna. Apparently, American Antenna's advertising is not merely Madison Avenue showmanship."

PERSONAL COMMUNICATIONS: "... an impressive 95% of the trials, the K40 out-performed the existing mobile antennas. We had to try one for ourselves."

"... in every case, the K40 either equaled or out-performed its competitor."

"No ifs, ands, or buts! The K40 Antenna from American Antenna would have to be just about the best antenna around."

CB MAGAZINE: "Introduced in October, 1977, the K40 quickly became the top seller and in mid 1978, became the number one selling antenna in the nation."

...Here's what CB'ers all across the country said.

ANTENNA SPECIALISTS: "... truck driver and CB'er for 10 years ... 50% further than my M410 'Big Momma'."

—J.H. Collett, 207 McFee, Bastrop, LA

AVANTI: "I'm an electronic technician with a Second Class FCC license ... I was able to transmit 70% further and tune the SWR 75% lower than my Avanti."

—H.R. Castro, VRB, Monserrate D-67, Salinas, Puerto Rico

PAL: "... 20% better in transmission and reception than my 5/8 wave Pal Firestick."

—John A. Blum, Box 446, Zellenople, PA

SHAKESPEARE: "... I've been a CB'er for three years and the K40 is the best I've ever had. Better in reception and transmission than my Shakespeare."

—H. Bachert, Jr., 15 King Rd., Park Ridge, NJ

HUSTLER: "Compared to my Hustler XBLT-4, the K40 can consistently transmit 40% further and the reception was better. The K40 is the perfect way to complete a CB system."

—Jerome R. Brown, 7800 S. Linder, Burbank, IL

GOOD STUFF FOR PROS ONLY!



(SPECIAL NOTE)
IF YOU'RE A BEGINNER:

Our K40 Dealers will be happy to sell you any of the older style and less expensive antennas that are great bargains for any beginning CB'er.

AMERICAN ANTENNA
ELGIN, IL 60120

© COPYRIGHT AMERICAN ANTENNA 1979

K40
POWER!

... Sold exclusively by **3500** American K40 Dealers throughout the U.S. & Canada.

CIRCLE 11 ON FREE INFORMATION CARD