

48783

**NEW!
DIRECT-ETCH
FOIL PATTERNS INCLUDED**

**BUILD AN
ELECTRONIC
PEST REPELLER**

**\$1.95 JULY 1985
IN CANADA \$2.25**

Radio— Electronics®

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE

**Build a PC-compatible
computer and
save \$2000**

**Tune up your car with R-E's
digital dwell/tachometer**

**How to choose satellite-TV
equipment that's
right for
you**

**Service your cordless
phone with R-E's
troubleshooting guide**

**Step-by-step
guide to
installing
your own
TVRO**

**How to interface
different
digital
logic
families**

**A
GERNSBACK
PUBLICATION**



**Special 16-page section:
COMPUTERDIGEST**

PLUS:

- ★ **New! Robotics column**
- ★ **New Ideas**
- ★ **State-Of-Solid-State**
- ★ **Service Clinic**
- ★ **Drawing Board**
- ★ **Equipment Reports**



Now! Tek quality and expert advice are just a free phone call away!

The industry standard in CRT performance.

Crisp, easy-to-read, bright CRT; 14kV accelerating potential, provides high writing rate and small spot size. Full size 8x10 cm display for measurement accuracy.

Display controls are flexible and easy to use.

Separate intensity controls reduce blooming in alternate sweep mode. Focus tracking minimizes control adjustment and BEAM FIND eliminates confusion.

Vertical system provides measurement assurance.

Flat transient response and high accuracy ensures true reproduction of your signals. Fast risetime and high bandwidth is well suited for a variety of measurement.

Perform delayed sweep measurements accurately and easily.

Both sweeps can be displayed alternately making differential measurements easy and accurate (1%). An interlocking SEC/DIV control simplifies set-up.

Stable hands-off triggering.

P-P AUTO detects signal peaks, then sets the trigger level for you. Display asynchronous signals using VERT MODE triggering. Independent TV field and line selection.

Front panel laid out by function for ease of use.

Color coding aids the user in operation. Functions and modes are placed logically. All nomenclature is clearly labeled, and protected behind a scratchless Lexan surface.



1-800-426-2200

Our direct order line gets you the industry's leading price/performance portables... and fast answers from experts!

The 60 MHz single time base delay 2213A, the 60 MHz dual time base 2215A and the 100 MHz dual time base 2235 offer unprecedented reliability and affordability, plus the industry's first 3-year warranty* on labor and parts, CRT included.

The cost: just \$1275 for the 2213A, \$1525 for the 2215A, \$1750 for the 2235.† Even at these low prices, there's no scrimping on performance. You

have the bandwidth for digital and analog circuits. The sensitivity for low signal measurements. The sweep speeds for fast logic families. And delayed sweep for fast, accurate timing measurements. All scopes are UL Listed and GSA approved.

You can order, or obtain literature, through the Tek National Marketing Center. Technical personnel, expert in scope applications, will answer your questions and expedite delivery. Direct orders include comprehensive 3-year warranty*, operator's

manual, two 10X probes, 15-day return policy and worldwide service backup.


**Order toll free:
1-800-426-2200,
Ask for Rick.**

In Oregon, call collect: (503) 627-9000. Or write Tektronix, Inc. P.O. Box 1700 Beaverton, OR 97075

Tektronix®
COMMITTED TO EXCELLENCE

Where's Your **ELECTRONICS** Career Headed?

your move!

 

The Move You Make Today Can Shape Your Future

Yes it's your move. Whether on a chess board or in your career, you should plan each move carefully. In **electronics**, you can *move ahead* faster and further with a

B. S. DEGREE

Put professional knowledge and a COLLEGE DEGREE in your electronics career. Earn your degree through independent study at home, with Grantham College of Engineering. No commuting to class. Study at your own pace, while continuing your present job.

The accredited Grantham non-traditional degree program is intended for mature, fully employed workers who want to upgrade their careers . . . and who can successfully study electronics and supporting subjects through

INDEPENDENT STUDY, AT HOME

Free Details Available from:

Grantham College of Engineering
10570 Humbolt Street
Los Alamitos, California 90720

Independent Home Study Can Prepare You

Study materials, carefully written by the Grantham staff for independent study at home, are supplied by the College, and your technical questions related to those materials and the lesson tests are promptly answered by the Grantham teaching staff.

Recognition and Quality Assurance

Grantham College of Engineering is accredited by the Accrediting Commission of the National Home Study Council.

All lessons and other study materials, as well as communications between the college and students, are in the English language. However, we have students in many foreign countries; about 80% of our students live in the United States of America.

Grantham College of Engineering R7-85
10570 Humbolt Street, Los Alamitos, CA 90720

Please mail me your free catalog which explains your B.S. Degree independent-study program.

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

NEW!

Uniden®

Bearcat®



Scanners

Communications Electronics™, the world's largest distributor of radio scanners, introduces new scanners and scanner accessories from J.I.L., Regency and Uniden/Bearcat. Chances are the police, fire and weather emergencies you'll read about in tomorrow's paper are coming through on a scanner today.

NEW! Regency® MX7000-H

List price \$699.95/CE price \$449.00
10-Band, 20 Channel • Crystalless • AC/DC
 Frequency range: 25-550 MHz, continuous coverage and 800 MHz, to 1.2 GHz, continuous coverage. In addition to normal scanner listening, the MX7000 offers CB, VHF, and UHF TV audio, FM Broadcast, all aircraft bands (civil and military), 800 MHz communications, cellular telephone, and when connected to a printer or CRT, satellite weather pictures.

NEW! Regency® MX5000-H

List price \$599.95/CE price \$354.00
Multi-Band, 20 Channel • No-crystal scanner
Search • Lockout • Priority • AC/DC
Selectable AM-FM modes • LCD display
World's first continuous coverage scanner
 Frequency range: 25-550 MHz, continuous coverage. Never before have so many features come in such a small package. The Regency MX5000 mobile or home scanner has continuous coverage from 25 to 550 MHz. That means you can hear CB, Television audio, FM broadcast stations, all aircraft bands including military and the normal scanner bands, all on your choice of 20 programmable channels.

NEW! Regency® MX4000-H

List price \$629.95/CE price \$394.00
Multi-Band, 20 Channel • No-crystal scanner
Search • Lockout • Priority • AC/DC
Selectable AM-FM modes • LCD display
 Bands: 30-50, 118-136, 144-174, 440-512, 800-950 MHz. The Regency MX4000 gives coverage in the standard VHF and UHF ranges with the important addition of the 800 MHz, and aircraft bands. It features keyboard entry, multifunction liquid crystal display and variable search increments.

NEW! Regency® Z60-H

List price \$379.95/CE price \$249.00
8-Band, 60 Channel • No-crystal scanner
 Bands: 30-50, 88-108, 118-136, 144-174, 440-512 MHz. Cover your choice of over 15,000 frequencies on 60 channels at the touch of your finger.

NEW! JIL SX-400-H

List price \$799.95/CE price \$499.00
Multi-Band, 20 Channel • No-crystal Scanner
Search • Lockout • Priority • AC/DC
 Frequency range: 26-520 MHz, continuous coverage. With optionally equipped RF converters 150KHz-3.7 GHz. The JIL SX-400 synthesized scanner is designed for commercial and professional monitor users that demand features not found in ordinary scanners. The SX-400 will cover from 150 KHz to 3.7 GHz, with RF converters. Order the following RF converters for your SX-400 scanner. **RF-1030-H** at \$259.00 each for frequency range 150 KHz.-30 MHz. USB, LSB, CW and AM. (CW filter required for CW signal reception); **RF-5080-H** at \$199.00 each for 500-800 MHz.; **RF-8014-H** at \$199.00 each for 800 MHz.-1.4 GHz. Be sure to also order **ACB-300-H** at \$99.00 each which is an antenna control box for connection of the RF converters. Add \$3.00 shipping for each RF converter or antenna control box. If you need further information on the JIL scanners, contact JIL directly at 213-926-6727 or write JIL at 17120 Edwards Road, Cerritos, California 90701.

SPECIAL! JIL SX-200-H

List price \$499.95/CE special price \$189.00
Multi-Band - 16 Channel • No-Crystal Scanner
 Frequency range 26-88, 108-180, 380-514 MHz. The JIL SX-200 scanner tunes military, F.B.I., Space Satellites, Police and Fire, Drug Enforcement Agencies, Defense Department, Aeronautical AM band, Aero Navigation Band, Fish & Game, Immigration, Paramedics, Amateur Radio, Justice Department, State Department, plus other thousands of radio frequencies most other scanners can't pick up. The SX-200 has selectable AM/FM receiver circuits, tri-switch squelch settings - signal, audio and signal & audio, onboard AC power supply - DC at 12 volts built-in, quartz clock - bright vacuum fluorescent blue readouts and dimmer, dual level search speeds, tri-level scan delay switches, 16 memory channels in two channels banks, receive fine tune (RIT) ± 2KHz., dual level RF gain settings - 20 db pad, AGC test points for optional signal strength meters. All in all, the JIL SX-200 gives you more features for the money than any other scanner currently on sale. Order your JIL SX-200 scanner at this special price today.

Regency® HX1000-H

List price \$329.95/CE price \$209.00
6-Band, 30 Channel • No Crystal scanner
Search • Lockout • Priority • Scan delay
Sidelit liquid crystal display • Digital Clock
 Frequency range: 30-50, 144-174, 440-512 MHz. The new handheld Regency HX1000 scanner is fully keyboard programmable for the ultimate in versatility. You can scan up to 30 channels at the same time. When you activate the priority control, you automatically override all other calls to listen to your favorite frequency. The LCD display is even sidelit for night use. A die-cast aluminum chassis makes this the most rugged and durable hand-held scanner available. There is even a backup lithium battery to maintain memory for two years. Includes wall charger, carrying case, belt clip, flexible antenna and nicad battery. Order your Regency HX1000 now.

Bearcat® 100-H

The first no-crystal programmable handheld scanner.
 List price \$449.95/CE price \$229.00
8-Band, 16 Channel • Liquid Crystal Display
Search • Limit • Hold • Lockout • AC/DC
 Frequency range: 30-50, 138-174, 406-512 MHz. The world's first no-crystal handheld scanner has compressed into a 3" x 7" x 1 1/4" case more scanning power than is found in many base or mobile scanners. The Bearcat 100 has a full 16 channels with frequency coverage that includes all public service bands (Low, High, UHF and "T" bands), the 2-Meter and 70 cm. Amateur bands, plus Military and Federal Government frequencies. Wow...what a scanner!
 Included in our low CE price is a sturdy carrying case, earphone, battery charger/AC adapter, six AA ni-cad batteries and flexible antenna. Order your scanner now.

QUANTITY DISCOUNTS AVAILABLE

Order two scanners at the same time and deduct 1%, for three scanners deduct 2%, four scanners deduct 3%, five scanners deduct 4% and six or more scanners purchased at the same time earns you a 5% discount off our super low single unit price.

NEW! Regency® HX2000-H

The World's First 800 MHz. Handheld Scanner
 List price \$569.95/CE price \$359.00
7-Band, 20 Channel • No-crystal scanner
Priority control • Search/Scan • AC/DC
Sidelit liquid crystal display • Memory backup
 Bands: 118-136, 144-174, 440-512, 800-950 MHz. The HX2000 scanner operates on 120V AC or 6 VDC. Scans 15 channels per second. Size 3" x 7" x 1 1/2". Includes wall charger, carrying case, belt clip, flexible antenna and nicad batteries. Selectable AM/FM modes.

OTHER RADIOS AND ACCESSORIES

RD55-H Uniden Visor mount Radar Detector	\$119.00
RD95-H Uniden Remote mount Radar Detector	\$139.00
BC 300-H Bearcat 50 channel scanner	\$344.00
BC 20/20-H Bearcat 40 channel scanner	\$274.00
BC 210XL-H Bearcat 18 channel scanner	\$209.00
BC 260-H Bearcat 16 channel mobile scanner	\$274.00
BC 201-H Bearcat 16 channel scanner	\$189.00
BC 180-H Bearcat 16 channel scanner	\$164.00
BC-WA-H Bearcat Weather Alert†	\$39.00
DX1000-H Bearcat shortwave receiver	\$499.00
PC22-H Uniden remote mount CB transceiver	\$99.00
PC55-H Uniden mobile mount CB transceiver	\$59.00
Z10-H Regency 10 channel scanner	\$149.00
Z30-H Regency 30 channel scanner	\$169.00
Z45-H Regency 45 channel scanner	\$199.00
MX3000-H Regency 30 channel scanner	\$219.00
C403-H Regency 4 channel scanner	\$69.00
R106-H Regency 10 channel scanner	\$99.00
HX650-H Regency 6 channel handheld scanner	\$99.00
HX-650P-H HX650 with batt., case, crystal certs.	\$124.00
RH250B-H Regency 10 channel VHF transceiver	\$379.00
RPH410-H 10 ch. handheld no-crystal transceiver	\$399.00
BC10-H Battery charger for Regency RPH410	\$79.00
EC10-H Programming tool for Regency RPH410	\$20.00
SMRH250-H Service man. for Regency RH250	\$20.00
SMRU150-H Service man. for Regency RU150	\$20.00
SMRPH410-H Service man. for Regency RPH410	\$20.00
B-4-H 1.2 V AAA Ni-Cad batteries (set of four)	\$9.00
A-135C-H Crystal certificate	\$3.00
FB-E-H Frequency Directory for Eastern U.S.A.	\$12.00
FB-W-H Frequency Directory for Western U.S.A.	\$12.00
A60-H Magnet mount mobile antenna	\$35.00
A70-H Base station antenna	\$35.00

Add \$3.00 shipping for all accessories ordered at the same time.
 Add \$12.00 shipping per shortwave receiver.
 Add \$7.00 shipping per scanner and \$3.00 per antenna.

BUY WITH CONFIDENCE

To get the fastest delivery from CE of any scanner, send or phone your order directly to our Scanner Distribution Center. Be sure to calculate your price using the CE prices in this ad. Michigan residents please add 4% sales tax or supply your tax I.D. number. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. All sales are subject to availability, acceptance and verification. All sales on accessories are final. Prices, terms and specifications are subject to change without notice. All prices are in U.S. dollars. Out of stock items will be placed on back-order automatically unless CE is instructed differently. A \$5.00 additional handling fee will be charged for all orders with a merchandise total under \$50.00. Shipments are F.O.B. Ann Arbor, Michigan. No COD's. Most products that we sell have a manufacturer's warranty. Free copies of warranties on these products are available prior to purchase by writing to CE. Non-certified checks require bank clearance.

Mail orders to: Communications Electronics, Box 1045, Ann Arbor, Michigan 48106 U.S.A. Add \$7.00 per scanner for U.P.S. ground shipping and handling in the continental U.S.A. For Canada, Puerto Rico, Hawaii, Alaska, or APO/FPO delivery, shipping charges are three times continental U.S. rates. If you have a Visa or Master Card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-USA-SCAN. In Canada, order toll-free by calling 800-221-3475. WUI Telex CE anytime, dial 671-0155. If you are outside the U.S. or in Michigan dial 313-973-8888. Order today.

Scanner Distribution Center™ and CE logos are trademarks of Communications Electronics Inc.

† Bearcat is a registered trademark of Uniden Corporation.
 ‡ Regency is a federally registered trademark of Regency Electronics Inc. AD #041585-H


Copyright © 1985 Communications Electronics

For credit card orders call
1-800-USA-SCAN

COMMUNICATIONS
ELECTRONICS INC.

Consumer Products Division

 P.O. Box 1045 □ Ann Arbor, Michigan 48106-1045 U.S.A.
 Call 800-USA-SCAN or outside U.S.A. 313-973-8888



- BUILD THIS**
- 43 PC COMPATIBLE COMPUTER**
You can put together a computer that's compatible with the IBM PC without paying IBM's price. And since the motherboard can be bought already assembled, anyone can do it! **Elliott S. Kanter**
- 55 DIGITAL TACH/DWELL METER**
Now you can tune up your car like a professional with this easy-to-build, easy-to-use meter. **David Demers**
- 67 PC SERVICE**
Our new feature lets you etch a printed-circuit board directly from the page.

RADIO

- 78 ANTIQUE RADIOS**
Antique radios use tubes!
Richard D. Fitch

VIDEO

- 12 VIDEO NEWS**
A review of the fast-changing video scene.
David Lachenbruch
- 80 SERVICE CLINIC**
Testing capacitors without a capacitor tester. **Jack Darr**
- 81 SERVICE QUESTIONS**
R-E's Service Editor answers your questions.

COMPUTERS

- Following page 72 **COMPUTER DIGEST**
Optical character-recognition—and lots more.

EQUIPMENT REPORTS

- 26 Vidicraft Detailer III Image Enhancer**
- 33 Sabadia Export Corporation EZ Board**

DEPARTMENTS

- 104 Advertising and Sales Offices**
- 104 Advertising Index**
- 105 Free Information Card**
- 14 Letters**
- 83 Market Center**
- 36 New Products**
- 6 What's News**

- TECHNOLOGY**
- 47 KNOW BEFORE YOU BUY**
Part 2. If you're thinking of buying a satellite-TV receiving station, read this before you talk to the salesmen. **Bob Cooper, Jr.**
- 51 INSTALLING YOUR TVRO**
Once you get your TVRO home, what do you do with it? You install it—with our help. **Bob Cooper, Jr.**
- 58 SERVICING CORDLESS TELEPHONES**
Part 3. In the final installment of this article, we look at how to service the base unit. **Christopher Kite**
- 66 ROBOTICS**
Getting started with robotics...and our new column. **Mark J. Robillard**

- CIRCUITS AND COMPONENTS**
- 61 ULTRASONIC PEST-REPELLERS**
Get rid of your pests electronically. **Robert F. Scott**
- 63 DESIGNING WITH DIGITAL IC's**
How to interface different logic families together. **Joseph J. Carr**
- 69 DESIGNER'S NOTEBOOK**
Do-it-yourself test equipment. **Robert Grossblatt**
- 72 DRAWING BOARD**
Using the 5101 CMOS RAM. **Robert Grossblatt**
- 74 NEW IDEAS**
Telephone off-hook alarm.
- 76 STATE OF SOLID STATE**
A new series of CMOS counters. **Robert F. Scott**

COVER 1



You might think that building a computer is not too easy. That may be true if you start from scratch. But if you build it by interconnecting subassemblies, nothing could be easier. For example, the computer shown on our cover can be assembled in about an hour using nothing but a screwdriver!

While that may bother some of the electronics-construction purists among our readers, let us point out that there are several real advantages to buying your computer in subassemblies. First, you can save money. Second, you don't have to buy your system all at once—you can add to it as cash flow permits. If you want, you can even buy a bare motherboard and really assemble your computer piece-by-piece. Either way, you end up with an IBM-compatible computer without paying for the name.

NEXT MONTH

THE AUGUST ISSUE IS
ON SALE JULY 4

SEE IN THE DARK

Build an infrared viewer and see what you've been missing.

BUILD A PRINTER BUFFER/CONVERTER

This handy circuit is a parallel-to-serial converter, a serial-to-parallel converter, and a 64K printer buffer.

DON'T TRUST THE WEATHERMAN

Build your own computer-controlled weather station and become better than the professionals.

HOW TO HOOK UP YOUR VCR

Hooking up your VCR can get rather complex as you add more equipment, cable service, etc. We'll show you how to do it the right way!

COMB FILTERS

We'll examine in detail an often-neglected but very important part of your TV.

AND LOTS MORE!

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Radio-Electronics

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback, editor-in-chief
Larry Steckler, EHF, CET, publisher

EDITORIAL DEPARTMENT

Art Kleiman, editor

Brian C. Fenton,
technical editor

Carl Laron, WB2SLR,
associate editor

Robert A. Young, assistant editor

Julian S. Martin, editorial associate

Byron G. Wels, editorial associate

Jack Darr, CET, service editor

Robert F. Scott,
semiconductor editor

Herb Friedman,
communications editor

Earl "Doc" Savage, K4SDS,
hobby editor

Bob Cooper, Jr. satellite-TV editor

Robert Grossblatt, circuits editor

David Lachenbruch,
contributing editor

Mark J. Robillard, robotics editor

Bess Isaacson, editorial assistant

PRODUCTION DEPARTMENT

Ruby M. Yee, production manager

Robert A. W. Lowndes,
editorial production

Dianne Osias, advertising production

Karen Tucker, production traffic

CIRCULATION DEPARTMENT

Jacqueline P. Weaver,
circulation director

Rita Sabalis,
assistant circulation director

Jacqueline Allen, circulation assistant

Radio-Electronics is indexed in
Applied Science & Technology Index
and *Readers Guide to Periodical Literature*.

Microfilm & Microfiche editions are
available. Contact circulation depart-
ment for details.

Advertising Sales Offices listed
on page 104.



The best DMM in its class just got better.



The Fluke 80TK. One innovation leads to another.

First there was the 70 Series, which set a new standard for low-cost, high-performance, Fluke-quality multimeters.

And now, another first. The Fluke 80TK K-type Thermocouple Converter. A temperature measurement device that adds instant temperature measurement capabilities to the 70 Series DMMs.

Or any DMM, for that matter.

Feature for feature, the versatile 80TK is the most affordable unit of its kind. For quick comparison readings, it can measure °C or °F at the flick of a switch. It includes a built-in battery test. And the availability of 3 Fluke probes give you the flexibility to measure any


form of temperature, from freezer to furnace, with just one base unit.

No other thermocouple converter we know of offers DMM users so much for so little. Just \$59, including a general-purpose bead probe.

So even if you don't own a Fluke 70 Series multimeter, the 80TK will help the DMM you're now using measure up when things get hot. Or cold.

For your nearest distributor, call toll-free **1-800-227-3800, ext. 229**, day or night. Outside the U.S., call 1-402-496-1350, ext. 229.

 FROM THE WORLD LEADER
IN DIGITAL MULTIMETERS.



Surface, immersion and general-purpose probes with "mini" thermocouple connectors are available for the Fluke 80TK.

80TK SPECIFICATIONS

Temperature Measurement Range
-50 to 1000°C
-58 to 1832°F
Battery Life: 1600 Hours (9V)

FLUKE[®]

WHAT'S NEWS

Jack Wayman inducted into Electronics Industry Hall of Fame

Jack Wayman, senior vice president of the Electronic Industries Association (EIA) was inducted into the Electronics Industry Hall of Fame at the Winter Consumers Show in Las Vegas last January. Mr. Wayman has been involved in the electronics industry for more than 35 years—22 of those years as an officer of EIA.

The Electronics Industry Hall of Fame was established in 1967 by the National Electronics Association to recognize individuals who have made outstanding contributions to the science and industry of electronics. It is organized in four major categories: inventor/scientist, industrialist/manufacturer, communications, and organizational leaders.

Hall of Fame members include scientist/inventors Guglielmo Marconi, Nikola Tesla, and John Bardeen; manufacturer/industrialists David Sarnoff, George

Westinghouse, and Morris L. Finneburgh, Jr., and in the communications category, Howard W. Sams, Hugo Gernsback, and John F. Rider.

In presenting the honor, Larry Steckler, president of the Hall of Fame and publisher of **Radio-Electronics** Magazine, said: "For more than 20 years, Jack has spearheaded the success and growth of the consumer electronics industry. His tireless energy helped to build a strong Consumer Electronics Group within the EIA and develop the summer and winter Consumer Electronics Shows into the nation's largest trade exhibitions."

Peter McCloskey, EIA president, stated: "We at EIA are proud of Jack, not only for this major personal recognition but for his numerous achievements on behalf of the consumer electronics industry."



JACK WAYMAN, ELECTRONICS INDUSTRY HALL OF FAME'S NEWEST MEMBER, receives his certification from Larry Steckler (center) President of the Hall of Fame and publisher of *Radio-Electronics*, and Peter McCloskey (right) President of the Electronics Industries Association.

New speech-processing IC produces natural sound

Scott Instruments Corp of Denton, TX, has introduced the *Corretechs* signal processor, the first, they say, designed specifically for processing speech. With this announcement, Scott joins the ranks of such companies as TI, NEC, and General Instrument in producing a high-speed signal processor for speech processing applications.

Unlike earlier devices, Scott's signal processor is capable of pitch-synchronous waveform analysis, is noise resistant, and yields strong acoustic clues for phonetic segmentation. The processor outputs information for pitch extraction, speech compression and speech resynthesis. The resulting speech, says Scott, is natural sounding with speaker identity and inflection preserved.

New database handbook for high technology

A new scientific and technical database handbook put out by Technical Insights Inc., of Fort Lee, NJ, is a directory to more than 500 key scientific and technical databases scattered throughout the world. It is intended to make immediately available sources that the high technology professional otherwise could waste much time searching for.

It includes, says the publisher, virtually all the important machine-readable science and technology databases—whether available online or on tapes—from both U.S. and foreign sources.


Designed for high-technology professionals, corporate managers, scientists, and engineers, the *R&D Database Handbook* is available from Technical Insights, Inc., P.O. Box 1304, Fort Lee, NJ 07024.

R-E

BK PRECISION DYNASCAN CORPORATION BREAKS THE PRICE BARRIER WITH THESE HIGH PERFORMANCE OSCILLOSCOPES

**100 MHz Dual Trace/
Dual Time Base**

- 1 mV/div sensitivity
- 23 calibrated sweeps
- Rectangular CRT with internal graticule and scale illumination
- Signal Delay Line

 


Model 1580

\$995

Does not include probes
(\$60.00 a pair when purchased with scope)

QUANTITIES ARE LIMITED

 

- 77**
- 0.3% Accuracy
 - Manual or Autorange
 - 10A + mA Range
 - Beeper
 - "Touch-Hold" Function

Sale (with holster)
\$119⁹⁵

WE CARRY A FULL LINE OF FLUKE MULTI-METERS. IN STOCK NOW

Sale ends July 85

FLUKE 70 SERIES MULTIMETERS

- Analog Display • Rotary Knob • Volts AC & DC • Resistance to • 32 MΩ • 10 Amps • Diode Test • 3200 Counts • Fast Autoranging • Function Annunciators in Display • Power-Up Self Test • 2000+ Hour Battery Life w/ Power Down "Sleep Mode" • New Test Leads • VDE & UL Approval



Sale
\$89⁹⁵

75

- 0.5% Accuracy
- Manual or Autorange
- 10A + 300 mA



Sale
\$79⁹⁵

73

- and free C70 holster
- 0.7% Accuracy
 - Autorange Only
 - 10 Amp Only



TOLL FREE HOT LINE
800-223-0474

212-730-7030

26 WEST 46th STREET, NEW YORK, N.Y. 10036

THE TEST EQUIPMENT SPECIALISTS

ADVANCE ELECTRONICS

Train for the Fastest Growing Job Skill in America

Only NRI teaches you to service and repair all computers as you build your own 16-bit IBM-compatible micro

As computers move into offices and homes by the millions, the demand for trained computer service technicians surges forward. The Department of Labor estimates that computer service jobs will actually *double* in the next ten years—a faster growth than any other occupation.

Total System Training

As an NRI student, you'll get total hands-on training as you actually build your own Sanyo MBC-550-2 computer from the keyboard up. Only a person who knows *all* the underlying fundamentals can cope with *all* the significant brands of computers. And as an NRI graduate, you'll possess the up-to-the-minute combination of theory and practical experience that will lead you to success on the job.

You learn at your own convenience, in your own home, at your own comfortable pace. Without classroom pressures, without rigid night-school schedules, without wasted time. Your own personal NRI instructor and NRI's complete technical staff will answer your questions, give you

New from NRI—the only home study course that trains you as you assemble a top-brand computer!



After you construct this digital logic probe, you'll install the "intelligent" Sanyo detached keyboard, with its dedicated microprocessor.

You next assemble the power supply into the main unit of the computer. Using the digital multimeter, you check all keyboard connections and circuits.

After you install the disk drive and monitor, you'll make a backup copy of the MS-DOS operating disk, explore the 8088 microchip and additional circuits.

guidance and special help whenever you may need it.

The Exciting Sanyo MBC-550-2—Yours To Keep

Critics hail the new Sanyo as the "most intriguing" of all the IBM-PC compatible computers. It uses the same 8088 microprocessor as the IBM-PC and the MS/DOS operating system. So, you'll be able to choose thousands of off-the-shelf software programs to run on your completed Sanyo.

As you build the Sanyo from the keyboard up, you'll perform demonstrations and experiments that will give you a total mastery of computer operations and servicing techniques. You'll do programming in BASIC language. You'll prepare interfaces for peripherals such as printers and joysticks. Using utility programs, you'll check out 8088 functioning. NRI's easy step-by-step instructions will guide you all the way right into one of today's fastest growing fields as a computer



service technician. And the entire system, including all the bundled software and extensive data manuals, is yours to keep as part of your training.

How the pro computer critics rate the Sanyo 550:

"Sanyo BASIC is definitely superior to IBM Microsoft... lets you use two or three keystrokes for entering BASIC commands."

—MICROCOMPUTING Magazine

"...compares favorably with the IBM PC, even surpassing it in computational speed..."

—COMPUTERS & ELECTRONICS Magazine

Your NRI Course Includes a Sanyo MBC-550-2 Computer with 128K RAM, Monitor, Disk Drive, and "Intelligent" Keyboard; The NRI Discovery Lab®, Teaching Circuit Design and Operations; a Digital Multimeter; Bundled Spread Sheet and Word Processing Software Worth \$1500 at Retail—and More.

"I went to have a look at the MBC-550... what I found made me an owner the next day!"

—Bill Sudbrink, BYTE Magazine

100-Page Free Catalog Tells More

Send the postage-paid reply card today for NRI's big 100-page color catalog, which gives you all the facts about NRI training in Microcomputers, Robotics, Data

Communications, TV/Video/Audio Servicing, and other growing high-tech career fields. If the card is missing write to NRI at the address below.

NRI SCHOOLS

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue, NW
Washington, DC 20016

We'll Give You Tomorrow.

IBM is a Registered Trademark of International Business Machine Corporation.



VIDEO NEWS



DAVID LACHENBRUCH
CONTRIBUTING EDITOR

• **8mm vs. Everything Else.** The big battle raging in the VCR world now is for the place of the new 8mm format in the scheme of things. With all of the original Beta group adding VHS-format recorders—Sanyo, Toshiba, NEC, Zenith, Marantz—only the inventor of Beta, Sony, has not gone over to the enemy camp. And Sony obviously is staking its future on 8mm.

In Japan, Sony has introduced an attractive camera-recorder combination (camcorder) in the 8mm format. Although it's a one-piece unit, its construction reveals that it probably is the forerunner of a home deck, since the recorder part of the unit seems designed to be produced as a separate part. There's further evidence of that in the PAL version just introduced in England. It has a two-speed switch, to permit playing at half speed. Thus, the "two-hour" cassettes due this summer could permit four-hour playing. Four hours is enough for most movies, and movies mean home decks—not necessarily camcorders.

Behind the scenes, there are reports that Sony is planning a full line of 8mm products—camcorders, home decks, and completely new recorder items. There's a persistent rumor of a very tiny deck or camcorder in the works, far smaller than the current Japanese product, which already is quite small. Sony officials in the past have talked of the possibility of equipping future TV sets with a drawer or slot into which a tiny deck may be inserted, and easily removed for portable use.

And remember that Sony started the entire Walkman craze. Is there lurking, perhaps, in the future a Video Walkman—a tiny, compact pocket VCR with an 8mm cassette and LCD or flat-tube color screen that would let commuters watch their favorite movies on the way to work?

• **Beta's Future.** Much concern is expressed that Sony and its partners may drop Beta. We don't think that that is likely. Beta was the first format, and still is the home-VCR format for many pioneers and purists. So if 8mm should

become Sony's "people's format" of the future, it's reasonable to assume that Beta will continue as the deluxe format for those who appreciate quality. Sony is in the process of introducing Super-Beta, a new version of Betamax with high-band color, excellent for dubbing and with a picture that can be appreciated by an electronics connoisseur. It is extremely likely that Beta will move from its place as today's low-end format to tomorrow's aristocratic high-end format—hi-fi and high-band, a semi-pro setup for those who really appreciate quality in home videotaping. Evidence of that trend is shown in Sony's newest deck in Japan. It's hi-fi stereo and high-band, of course, and it has a special professional-type crank-dial for variable slow and fast motion in both directions. And it's called the "Beta Pro."

• **Stereo TV Sound.** Although very little stereo programming for TV is currently available—indeed, two of the three commercial networks aren't well-equipped to distribute it to most of their affiliates—the concept of multichannel TV sound (MTS) must already be considered a success. In early April, some 32 stations were already equipped to broadcast in stereo. They were mostly in major markets, and could be received in 34,000,000 TV homes, or 40 percent of all TV homes in the continental U.S. The raw material for stereo TV listening now exists. All that is needed now is programming. In the meantime, most equipped stations are broadcasting in synthesized stereo.

• **Sony and Others.** Sony is pursuing a new tack by helping prime the pump for other manufacturers. In the past, almost all products emanating from the Sony factories bore the Sony brand name. (An exception was the Beta VCR line that Sony made for Zenith; Zenith showed its gratitude by switching to VHS models made by JVC.) Now, however, Sony is making 8mm camcorders for sale under various brand names, including Fuji, Pioneer, and Yashica. **R-E**

VIDEO ACCESSORIES

■ Highest quality ■ Highest performance ■ Lowest prices

bp VIDEO-CINE CONVERTER

The BP Video-Cine Converter is an optical device that allows the easy transfer of slides, 8mm or 16mm movie film to VCR tape. The Video-Cine Converter's precision optics put the image from your movie or slide projector on a high-contrast, rear projection screen. Your video camera shoots that image, can color-correct faded pictures, add narration to other sound. Can be used with any video camera or slide projector. If your video camera lacks close-up capability, you will need a macro lens attachment.

MODEL V-1701 **\$34⁹⁵**



FOR ULTIMATE VIEWING

TEKNIKA

WIRELESS REMOTE CONTROL TV TUNER & CABLE CONVERTER WITH VOLUME CONTROL

Model 6510
\$169⁹⁵



Wireless remote control with volume for cable TV, VHF-UHF antenna systems upgrades any TV to 140 channel capability.

- Works with any TV set
- Quick, easy installation
- Off-air and cable compatible
- Quartz frequency synthesizer tuning
- Direct access/memory scan selector
- Ultra-compact, hand-held wireless remote control



61 CHANNEL WIRELESS REMOTE CONTROL

Model V7661 **\$79⁹⁵**



Wireless remote control on/off, channel selection and fine tuning.

- Works with any TV
- 61 channel capability
- Microcomputer controlled PLL operation
- Converter panel controllable for channel up, down, on/off, fine tuning.
- LED display
- Compatible with CATV systems.



STABILIZER/IMAGE ENHANCER/RF CONVERTER/VIDEO FADER/2-WAY DISTRIBUTION AMPLIFIER

Model V1880 **\$99⁹⁵**




Hook-up cable kit
\$11.75

The most versatile, all-in-one video processor. Can be used as a video guard remover for video tapes, enhancer, video to RF converter, professional video fade in and out and a dual output distribution amplifier.



VIDEO SWITCH

 

Model V4804 **\$49⁹⁵**

Record a pay channel while viewing a standard channel. You can also connect an antenna/cable, VCR, video disc player, home computer and video game.



VIDEO TAPE REWINDER

Model V7777 VHS **\$49⁹⁵**

Model V7778 BETA **\$49⁹⁵**



Reduce wear and tear of your VCR heads with the AC powered circuit protected rewinders, LED power-on indicators.

Phone orders accepted. Ask for our FREE catalog.

Fordham

260 Motor Parkway, Hauppauge, NY 11788

Toll Free
800-645-9518
In NY State 800-832-1446

Service and Shipping Charge Schedule

FOR ORDERS	ADD
\$25-250	\$4.50
\$251-500	\$6.50
\$501-750	\$8.50
\$751-1,000	\$12.50
\$1,001 and up	\$15.00

LETTERS

WRITE TO:

LETTERS
Radio-Electronics
200 Park Ave South
New York, NY 10003

OOOOOPS!

In our article "Computer-Controlled Robot Arm" in the May 1985 issue, we let a rather embarrassing error get into print. Notice that the power and ground lines are shorted together at each motor. Also note that the inputs and outputs of IC3 are reversed. Shown here is a section of the circuit as it should be. Figure 2 in the May issue also shows the correct configuration.

We're sorry those errors got past us, and we hope that they did not cause too many problems.—*Editor*

 


FIG. 1

VIDEO CAMERAS


I thank you for the article about lightweight video cameras. It was refreshing to see that topic covered. One thing I expect from **Radio-Electronics**, however, is accurate reporting, especially regarding the technical aspects of a subject. While most of the details discussed in the article were correct, one glaring error and a few omissions were present, and I'd like to clear those up.

First of all, horizontal resolution does not refer to the number of horizontal scanning lines in the picture, as stated in the article. All

WAVETEK®

Our 2 MHz Function Generator has an unlimited range.

Model 20 not only covers the .002 Hz to 2.1 MHz frequency range, it covers the world. With internal NiCad batteries,* you can take Model 20 anywhere and get triggered, gated or continuous waveforms—sines, squares, and triangles up to 20 volts peak to peak. It recharges from wall transformer (included) or external source from 12 to 25 VDC or 10 to 18 VAC. Model 20 also has many of the features you would expect from the industry leader in function generators, including VCG input connector for external sweep or FM, step attenuator to -80dB, and a TTL pulse output. The price is just \$395. For a data sheet or to order, call or write Wavetek San Diego, P.O. Box 85265, 9045 Balboa Ave., San Diego, CA 92138. Phone (619) 279-2200; TWX (910) 335-2007. *Batteries not included.

 

CIRCLE 257 ON FREE INFORMATION CARD

If you love your present soldering system - you're using our SA-3

OK Industries listened to you and
then designed the station you wanted.
The SA-3 temperature controlled
soldering station has proved to be the
most reliable soldering system
available today! Temperature
accuracy is controlled by a J-type
thermocouple, and the 24 volt, 48
watt low leakage iron is grounded for
protection of sensitive MOS and
MOS circuitry. The compact unit is
extremely simple to use and features
weighted power and heater indicators,
slide switch temperature control, and
operating indicating meter.

Spike-free, zero
voltage heater
switching.

Extremely fast
response and
recovery time.

Non-burn silicone
soldering iron cord.

Model SA-3-115 115 VAC
Model SA-3-230 230 VAC



3455 Conner Street, Bronx, New York, 10475, U.S.A.
Telex 125091 OK NYK. Telex 232395 OK NY UR.
Phone (212) 994-6600.
Fax: 212-994-4755.

CIRCLE 265 ON FREE INFORMATION CARD

NTSC-type video signals (which all those cameras produce) are composed of 525 horizontal scanning lines, interlaced 2:1 each field (263.5 lines per field times 2 fields per frame). Therefore, the number of horizontal scanning lines is determined by the number of vertical picture elements. In tube cameras, all 525 are present, but CCD cameras omit a few (the Sony has 491), because they are lost to TV overscan anyway.

Horizontal resolution refers to

the number of dots that can be placed next to each other on a line before they blur together. It is primarily a function of a camera's high-frequency response. When taken over the entire picture, those dots form (you guessed it), vertical lines, and are called TV lines. The more dots possible, the sharper the picture, as it can contain more pixels per image. (Remember, the number of vertical picture elements is always limited to 525 anyway).

What about the quality of the various cameras? There is certainly more to video quality than minimum illumination and resolution! While I realize that you are not in the ratings business, I feel that anyone who had actually tried any of those cameras would have had a few things to say. For example, the Panasonic *PK-410* and *PK-450* do make excellent pictures in very low light, but the diagonal striped color filter is somewhat visible on bright vertical-picture elements (such as a window edge) in any light, but especially in low light. Also, the Konica *CV-301* is especially susceptible to green streaking on moving dim-picture elements. Furthermore, that camera uses a tube called a Cosvicon (see page 51 for a picture of the camera), not a "Cosvision" as stated in the article. The camera is also available from Sharp (they make it for Konica) and they call their tube a Newvicon.

The wording to describe features is inconsistent, making comparison difficult. One camera is said to have "15mm-75mm zoom lens", while another has "6x zoom". Also, some features are mentioned on some cameras, but omitted on others. For instance, what is the resolution of the Panasonic cameras? It isn't mentioned. Also, the *PK-450* has built-in time and date display. That isn't mentioned either.

For that matter, some manufacturers are omitted altogether. Why go into detail in describing Quasar cameras, when they are identical to those from Panasonic (both are made by Matsushita, which owns both companies), yet omit Toshiba altogether? What about Sharp?

I expect more from **Radio-Electronics** than a simple trotting out of manufacturers' literature, and I usually get it. Please continue to be a *technical* magazine. Don't stoop to shallow consumer "overview" articles with too-little substance.

MICHAEL JAY GEIER
Allston, MA

MORE TROUBLESHOOTING NEEDED

Mr. Steckler answers his own question ("Letters", **Radio-Elec-**
continued on page 22

No-trouble troubleshooting

Using computers is one thing. Repairing them is another. With a basic knowledge of electronics and Sams service data, repairing computers is no trouble at all.

For in-depth computer analysis and repair, choose Sams **COMPUTERFACTS™**. They're similar to Sams **PHOTOFACT®** and provide detailed schematics and parts data for even your most intricate computer repairs.

For simple computer maintenance and troubleshooting, use Sams **Troubleshooting and Repair Guides**. They provide a "problem-solution" approach to servicing with flowcharts explaining each procedure step-by-step.

Together they make computer servicing quick and easy. And both cover today's most popular computers including Apple®, IBM® and Commodore.™

Service computers the easy way with Sams service data. Visit your local

Sams dealer. Or call our toll-free number and ask for Operator 131.

Commodore 64 Troubleshooting & Repair Guide, No. 22363, \$18.95
IBM PC Troubleshooting & Repair Guide, No. 22358, \$18.95
Apple II Plus/IIe Troubleshooting & Repair Guide, No. 22353, \$19.95

Over 30 **COMPUTERFACTS** available for Apple, ATARI®, Commodore, Epson®, Hitachi®, IBM, Osborne®, Panasonic®, Rana Elite, Sanyo®, Texas Instruments and Zenith®. Ask your Sams dealer for details.

800-428-SAMS
In Indiana, call 317-298-5566

SAMS

Howard W. Sams & Co., Inc.
4300 West 62nd Street
Indianapolis, IN 46268



CIRCLE 268 ON FREE INFORMATION CARD

TEST INSTRUMENTS

LOWEST PRICES
OFF-THE-SHELF
DIRECTLY TO YOU

CALL TOLL FREE
FOR FAST DELIVERY

800-645-9518

In New York State 800-832-1446

HITACHI 35 MHz DUAL TRACE OSCILLOSCOPE

Model V-355
\$599⁹⁵

(Reg. \$899.95)
Probes included.



- Thin, lightweight, compact
- Large 6" rectangular, internal graticule CRT
- Autofocus

FREE! LOGIC PROBE
BP LP189
(\$40.00 VALUE)
with purchase of
Model V-355

A.W. SPERRY 20 MHz DUAL TRACE OSCILLOSCOPE

Model 620C
\$399⁹⁵

(Reg. \$449.95)
Probes included.



- Built-in component checker
- High sensitivity X-Y mode
- Internal graticule CRT

HITACHI 100 MHz QUAD TRACE DELAYED SWEEP OSCILLOSCOPE

Model V-1050F
\$1249⁹⁵

(Reg. \$1980)
Probes included.



- Large 6" rectangular CRT w/internal graticule
- Delayed alternate and single sweep functions
- Autofocus

B&K 60 MHz TRIPLE TRACE OSCILLOSCOPE

Model 1560
\$899⁹⁵

(Reg. \$1150)
Probes included.



- 1 mV/div sensitivity
- 22 calibrated sweeps
- Rectangular CRT w/internal graticule & scale illumination
- Autofocus

FORDHAM SWEEP FUNCTION GENERATOR

Model FG-801
\$199⁹⁵

(Reg. \$299.95)
Test Leads included.

- 7 frequency ranges, 0.2Hz to 2MHz
- Accuracy to $\pm 5\%$

SPECIAL PRICE!

FORDHAM 550 MHz FREQUENCY COUNTER

Model FM-8
\$169⁹⁵

(Reg. \$249.95)

- Completely assembled, pre-tested, pre-calibrated
- High intensity 8-digit LED display



FLUKE 3½ DIGIT MULTIMETERS & VOLTMETERS



Model 73 **\$69⁹⁵**

- Resistance, AC/DC current/voltage
- 6 functions including diode test
- 0.7% DC accuracy
- Current range to 10A, AC/DC

Model 75 **\$89⁹⁵**

- All features of Model 73, plus
- 7 functions including diode and continuity beeper
- 3 current ranges - 10A, 320 mA, 32 mA
- 0.5% DC accuracy

Model 77-F **\$119⁹⁵**

- All features of Model 75, plus
- "Touch-Hold" function
- 0.3% DC accuracy

ASK FOR OUR FREE CATALOG!

PHONE ORDERS ACCEPTED




SERVICE & SHIPPING CHARGE SCHEDULE FOR ORDERS

ORDER VALUE	ADD
\$25-250	\$4.50
\$251-500	\$6.50
\$501-750	\$8.50
\$751-1,000	\$12.50
\$1,001 and up	\$15.00

Fordham

260 Motor Parkway, Hauppauge, New York 11788

POWERFUL TRAINING CAREERS IN PC

 

Learn PC Servicing By Assembling Your Own NTS/HEATH HS-151 16-Bit Desk-Top Computer

This is the most powerful and versatile Personal Computer ever offered in any home study course, and NTS Intrinsic Training gets you right down into the heart of it. You learn how microcomputers function, and how they operate to solve problems. Your program includes a wide variety of tests and projects you perform as you build this remarkable PC, circuit board by circuit board. There is no better way to learn PC servicing. Lessons, texts and equipment are completely integrated to make your training easier to understand, more practical, and applicable to many other types of computers.

A Rewarding Career in PC Servicing Lies Ahead.

The world of computers is constantly expanding. Industrial and business applications of computers show every sign of consistent growth. In fact, the market for PC's will expand to an expected 3.7 million units this year, and by the end of the decade the entire computer market worldwide will pass the trillion dollar mark.

These sales figures point to continued growth in the peripherals market, networking, modems, printers, and a host of other "add-ons" needing installation technicians and skilled service-maintenance personnel. It's a career field with dynamic potential, and NTS PC Training is aimed right at it.

Your Training Includes Test and Other Equipment

Most NTS courses include test equipment to teach you the uses and applications of such units as Digital Logic Probes, Digital Multimeters, Trans/Diode Testers, and the like. The NTS Compu-Trainer is included in several courses to familiarize you with principles involved in circuitry used in a wide variety of computer types and brands. You perform hundreds of experiments with it, learning the how and why of computer operation. NTS courses are designed to prepare you for jobs in electronics where you can grow with the experience you receive in the field. It's the kind of training that keeps pace with developments, assuring you of a solid foundation on which to build a career.

The Exciting NTS/HEATH 16-Bit HS-151 is Loaded with Features:

- A. 128KB RAM user memory on board, expandable to 640KB.
- B. 16-Bit 8088 microprocessor accepts advanced software and speeds word processing; also allows selection from the huge library of IBM* software.
- C. IBM-compatibility with *MS-DOS operating system.
- D. 5.25-inch floppy disk drive, double density, IBM formatted, stores up to 360KB. (Expandable to dual-disk drive, and optional 10.5MB hard-disk drive.)
- E. Four open IBM-compatible slots provide for future expansion, printer, modem, etc. Will accept most peripheral boards designed for the IBM PC.
- F. Two video outputs for color or monochrome display monitor. Your NTS course includes a high-resolution monitor displaying 80 characters by 25 lines, or graphics.

FOR POWERFUL SERVICING



G. Editing capabilities help you insert or delete characters and lines, erase, jump or smooth scroll, plus several other convenience features.

H. The NTS/HEATH HS-151 is complete with full-function keyboard, calculator-style keypad, and typewriter format.

NTS Training Takes You Beyond Equipment Assembly.

Field service personnel are required to analyze and solve problems, many times on the spot. Whether the problem is in the disk-drive or the monitor, the memory or the power input, you learn how to spot the difficulty and take steps to resolve it. Your NTS course includes test equipment, and teaches you how to use it.

Three courses, one starting with basics, and two different advanced courses for those with previous experience, give you a choice of programs suited to your particular needs. You learn how to program this advanced computer with excel-

lent support material. And, equally important, the NTS/HEATH HS-151 enjoys a reputation backed by a major American manufacturer. There is no substitute for first-class equipment, and you keep it to use for years in your home or business.

NTS TRAINING PROGRAMS COVER MANY AREAS OF ELECTRONICS:

Robotics: Build the NTS/HEATH Hero 1 Robot as you learn Robotic programming technology. This field is at the leading edge of electronics.

Video Technology: Learn circuit diagnostics and digital principles as you build one of the most advanced color TV sets available. Your course also covers VTR's, computer fundamentals, solid-state devices.

Industrial and Microprocessor Technology: Train in microprocessor and automation applications, lasers, and basic industrial robotics.

TV & Radio Servicing: Acquire a foundation in the use and application of both analog and digital test equipment in the TV servicing field. Learn to service Color and monochrome monitors, troubleshoot receivers, and maintain entire systems.

Basic Electronics is a course designed to give you an over-view of electronics. It is particularly helpful to electronic sales personnel, and those wishing to get into technical writing.

NTS Intronix training programs are practical, and job-oriented. You train on field-type equipment, and lessons and texts are tested and proved in our Resident School in Los Angeles. This assures you of understandable lessons and texts, as well as projects which get right to the heart of your subject. NTS, now in its 80th year, continues to offer economical training at the leading edge of Electronics.

*IBM is a trademark of International Business Machines Corp. *MS is a trademark of Microsoft Corp.

If card is missing, write directly to the School at the address below stating the course in which you are interested. A FREE color catalog and all details will be sent to you by return mail.

NTS NATIONAL TECHNICAL SCHOOLS

TECHNICAL TRADE TRAINING SINCE 1905
Resident and Home-Study Schools

4000 South Figueroa Street
Los Angeles, CA 90037-9988

FREE high tech catalog



A trustworthy guide to what's new in electronics and computers.

For many years the illustrated Heathkit Catalog has been a guide to new and exciting kit products for people like you to build. To enjoy and learn from them, while saving money in the process. What sets the Heathkit Catalog apart is its range of high quality products and accurate information to help make your buying decisions easy. If you've never tried kit-building, you have an absorbing new experience in store as you create products you'll take pride in.

Send for free catalog If coupon is missing, write Heath Company, Dept. 020-312 Benton Harbor, Michigan 49022



Mail to: Heath Company, Dept. 020-312
Benton Harbor, Michigan 49022
Please send me my **FREE HEATHKIT CATALOG.**

Name _____
Address _____
City _____ State _____ Zip _____

Heathkit products are also displayed, sold and serviced at 64 Heathkit Electronic Centers nationwide. Consult telephone directory white pages for location. Operated by Veritechnology Electronics Corporation, a wholly-owned subsidiary of Zenith Electronics Corporation. CL-778C



CIRCLE 86 ON FREE INFORMATION CARD

LETTERS

continued from page 16

tronics, December 1984), when he tells us that he deprecates replacing a \$500.00 module for the sake of a 25-cent part. I'll bet he wouldn't throw away his \$500.00 VCR without spending an appropriate amount of time, money, or both on its repair either. Naturally, with the electronics-value content of automobiles rising greatly, and since we are electronics people, we're the ones who want to explore the inner workings of new technology for a number of reasons ranging from simple curiosity to profit seeking.

The marketplace, not the manufacturer, is the only real determinant of value in general and the marketplace will also ultimately determine what is or is not repairable—including plug in modules.

I'm sure most Radio-Electronics readers own an automobile that represents a substantial investment. Near universal ownership of items such as autos, and clothes dryers, make for general reader interest. We all want to be sure we're getting a good value electronics-wise when we make that big purchase and I'm sure many readers will also want to know about troubleshooting and repair—especially when the difference between repair and replacement is a couple of C-notes or more.

DONALD J. SABO
Peekskill, NY

MANUAL NEEDED

I would appreciate your help with this matter: I have acquired a portable tube tester. The only problem is that I don't have the instruction manual and the unit is useless without it. I have been told that the company that manufactured the unit is probably out of business. The tube tester is a model 85, made by the Superior Instrument Company.

If you, or one of your readers, could find out any information on where I might get the instruction manual, I would greatly appreciate it.

BRUCE G. ST. JULIEN
5300 Lyndell Ave.
Portage, IN 46368

R-E

ATTENTION TV TECHNICIANS

Diehl Engineering, the same people who conceived, designed and now manufacture **Super Tech** diagnostic computers for analyzing start up, shut down, flyback and flyback related circuits, now has something else that will make your job faster, easier and much more profitable.



A NEW PUBLICATION

You might say that our monthly **Technician / Shopowner** newsletter is an all out training program for those who are already working in the TV service industry, as well as for those who soon plan to be doing so.

Each month we take at least one concept, circuit or function and totally dissect it. We then explain every conceivable aspect in plain and simple English. When we are finished, you not only understand the operation, you also understand how the operation, "inter-reacts" with all of the other circuits that it is related to.

Once every aspect of operation has been explained, we show you how to break the subject down into sections. Then, show you how to troubleshoot each section on an individual basis.

Because of the manner in which our publication is written, the subject knowledge that is gained in each monthly issue is so broad, that it "spills over" into your every day troubleshooting routine.

Our **Technician/Shop owner** monthly newsletter is 100% devoted to the TV technician. It contains nothing but pertinent information on TV repair. We do not sell advertising space. Those who subscribe, do so because of its technical content, which we pledge to be far superior to anything else that you can obtain.

Each monthly issue (manual) contains up to 68 pages filled with schematics, diagrams and illustrations that relate to the very circuits that you are seeing today. We do not teach this year's chassis, we realize that you are seeing sets that are five, ten or even fifteen years old.

Our newsletter is not a collection of part numbers that cause specific problems in specific chassis when they fail. Instead, we explain what each individual component in a given circuit does, what purpose it serves, and what effect it will have if and when it fails.

Our subscribers can look at any resistor, any capacitor, any diode, any transformer, etc., in any circuit, and know exactly what purpose it serves. They will know what turns the circuit on, what turns it off, why and when such action occurs, and what happens if a specific action does not occur.

Our subscribers will no longer have to be content to know that R421 causes a particular chassis to shut down if it becomes open, they will know **why** it does.

Our subscribers will no longer run around in circles hoping to stumble over a "bad" component, they will know **exactly** what they are looking for, and --- how to find it!

When it comes to troubleshooting color TV sets, we have introduced more, innovative techniques than any other firm in the world (including manufacturers).

In case that amuses you, consider this:

Everyone else in the industry is telling you to probe here and there in this chassis, there and somewhere else in another chassis, in hopes of isolating the actual circuit that has failed. Conventionally, one specific technique that works for one chassis may do nothing but smoke components in the next.

Yet, while others have been teaching "conventional" techniques (usually a different one for each chassis), we at **Diehl Engineering**

designed a computer that will isolate the defective stage in any hi-voltage circuit that employs a horiz output transistor (including Sony). With our **Super Tech** computer, you push the same four buttons no matter which set you are working on. Any brand, any age any chassis, Super Tech will give you an **accurate** answer.

We are not implying that those who teach "conventional" techniques are technically incompetent. Far from it, some of them are brilliant! We simply have a new and much easier way of looking at things. Ours is easier to understand and far more versatile. Because of the manner in which we present it, the retention level is also higher (according to those who are now using our literature).

Any staff that can design a computer that can analyze **any** hi-voltage circuit (except for those which use a trace and retrace SCR i.e. RCA CTC 40-81) must surely have a thorough knowledge of **all** circuits. Soon we will release similar computers for vertical and audio circuits, another for tuner, IF, AGC, video, blanking, ABL, Chroma, matrix and CRT, and still another for troubleshooting VCR!

The point is, we at **Diehl** engineering understand circuitry. We also know how to **explain** circuitry in such a way that it is easily understood.

Each month's issue is printed in the form of a manual. Each manual is pre-drilled so that it can be filed in a 3 ring binder for instant reference (the 3 ring binder is not provided).

The First Issue covers resistors, capacitors, diodes, inductors, transistors, IC chips and time constant circuitry. It explains how each component works, why it works, why it fails, and how each component relates to the overall circuit, all in plain and simple, down to earth, everyday English, without the use of mathematical formulas. After reading this issue, you can look at any component in any circuit and **truly** understand **what** it does, **why** it does it and what will happen if it doesn't do it; right down to each individual resistor, capacitor, and diode.

The Second Issue covers SCR driven hi-voltage circuits such as those used in RCA CTC 40-81, Philco, Coronado, Bradford, etc. After reading this issue, this circuit will become no more complex than simple amplifier. Over 30 illustrated schematics are used to teach this circuit in absolute detail. Such things as HV regulator functions, shut down features, etc. are thoroughly explained.

The Third Issue covers RCA LV regulator circuits (CTC 85 and up). It explains how each individual component operates, what it does, when it does it and, how to effectively troubleshoot the overall circuit.

Our no paid advertising policy makes our newsletter a little more expensive, but it also gives us "cover to cover" space for nothing but pertinent technical information on TV service. At \$9.95 per issue, a twelve month subscription costs only \$119.40. Very economical, considering that its technical content is equal to a "full blown" study course on TV repair. If you wish, you may try the first three issues for only \$21.00 (just seven dollars per issue, a savings of \$8.85 off the regular price).

For immediate service on C.O.D., Visa, or Master Charge orders:

Phone (806) 359-1824 or (806) 359-0329.

If you are looking for help --- we have it!

Diehl Engineering, 6004 Estacado Lane, Amarillo, Texas 79109.

Circle (267) on Reader Service Card.

RAG


ELECTRONICS, INC.

New and Used Electronic Test Equipment
Sales • Service • Rental • Leasing

➤ Polaroid DS-34

Now you can get an instant picture in black & white or color from any oscilloscope screen. Includes CRT hood.
*Large hoods also available to fit computer terminals and CAD/CAM screens.

\$369.00

 

LEADER Instruments Corporation

Audio Sine/Square Wave Generator

- Distortion from <0.03%
- 10 Hz to 1 MHz

\$259.00



LAG-120B



BK PRECISION

FUNCTION GENERATOR

\$189.00

MODEL 3010

- Sine, square and triangle output
- Variable and fixed TTL outputs
- 0.1 Hz to 1 MHz in six ranges
- Typical distortion under 0.5% from 1 Hz to 100 KHz
- Variable DC offset
- VCO input for sweep tests

POWER SUPPLIES

GLOBAL SPECIALTIES TRIPLE OUTPUT POWER SUPPLY




MODEL 1301

\$198.00

- Fully regulated triple output
- Fixed 5VDC, 1A
- V1 + 5 VDC to 18 VDC .5A
- V2 - 5 VDC to 18 VDC .5A
- Fully automatic current limiting

BK PRECISION TRIPLE OUTPUT POWER SUPPLY

 

MODEL 1650

\$319.00

- Functions as three separate supplies
- Exclusive tracking circuit
- Fixed output 5 VDC, 5A
- Two 0 to 25 VDC outputs at 0.5A
- Fully automatic, current-limited overload protection
- + and - terminals of each output are fully isolated, in all modes
- All three outputs may be connected in series or parallel for higher voltage or current

VIZ

MULTI-FUNCTION COUNTER




MODEL WD-755

\$259.00

- 5 Hz to 125 MHz
- 8 Digit LED Display
- Period Measurement 5 Hz to 2 MHz
- Totalizes to 99,999,999 Plus Overflow
- Frequency Ratio Mode
- Time Interval Mode
- Switchable Attenuator & Low Pass Filter

 ELECTRO INDUSTRIES, INC. Precision Test Instruments



DC POWER SUPPLY

\$125.00

MODEL 3002A/0-30 VDC/0-2A

PROBE MASTER Oscilloscope Probes

MODEL	ATTENUATION	BAND WIDTH (MHZ)	PRICE
2904	10X	100	\$35.00
2901	10X/1X	100/5	\$39.00
2205	10X	250	\$59.00
2960	10X	60	\$30.00

STACO ENERGY PRODUCTS CO.

VARIABLE TRANSFORMER

\$145.00



MODEL 3PN1010V

RAG CARRIES THE COMPLETE STACO VARIABLE TRANSFORMER LINE
CALL US WITH YOUR REQUIREMENTS.

DIGITAL CAPACITANCE METER



- Battery operated
- 3 1/2 digit LCD display
- Range 1 PF to 2,000 UF
- 0.2% basic accuracy

GLOBAL MODEL 3000
\$139.00

CALL US TOLL FREE

1-800-732-3457

IN CALIFORNIA TOLL FREE

1-800-272-4225

- Master Charge
- VISA ■ COD
- Money Order
- Check



ADD FOR SHIPPING AND INSURANCE

\$0 to \$250.00	\$4.50
\$251.00 to \$600.00	\$6.50
\$601.00 to \$750.00	\$8.50
\$751.00 to \$1000	\$12.50
over \$1000.00	\$15.00

COD's extra (required 25% deposit)

RAG ELECTRONICS, INC. / 21418 Parthenia Street / Canoga Park, CA 91304 / 1-818-998-6500


SCOPE SPECTACULAR



PORTABLE OSCILLOSCOPES



Model V-212 shown

 

Model V-1050F shown

MODEL V-212

DC to 20 MHz, 1 mV/div, Dual Trace
Features 6" Rectangular CRT
Full 2 year parts and labor warranty (w/two X10 probes).

\$461.00

MODEL V-222

DC to 20 MHz, 1 mV/div, Dual Trace, D.C. offset for DMM Output, Verticle Mode Trigger
6" CRT (w/two X1/X10 probes).

\$536.00

MODEL V-422

DC to 40 MHz,
other features same as V-222 (w/two X1/X10 probes)

\$694.00

MODEL V-1050F

DC to 100 MHz, .5 mV/div, Quad Trace, Delayed Sweep, Full T.V. Triggering, alternate time base (w/two X10 probes)

\$1276.00


MODEL V-650

DC to 60 MHz, 1 mV/div, triple trace, delayed sweep, Full T.V. Triggering, variable trigger hold-off (w/two X10 probes)

\$956.00




PORTABLE OSCILLOSCOPES

 

MODEL SS-5702

DC - 20MHz, 5 mV/div
Dual trace
6 inch rectangular internal graticule CRT.
Includes 2 each X1/X10 probes and full factory warranty; 2 years on parts, labor and CRT.

\$535.00

 


MODEL SS-5705

DC to 40MHz
Vertical and horizontal deflection accurate within $\pm 2\%$. CRT acceleration voltage 12KV. 3 channels, 6 traces. High precision calibrator ($\pm 1\%$). Fastest sweep rate: 10 ns.

- High sensitivity 1 mv/div
- CH1 signal output
- Beam finder
- Delayed sweep
- Alternate time base
- 2 ea. X1/X10 Probes

\$899.00

 

MODEL 5711

DC to 100MHz (typically over 120 MHz), 5 mV/div, True 4 channel input, eight trace, Delayed sweep, alternate time base, CRT acceleration voltage 20 KV, (w/saddle bag, front cover, 2 ea. X10 probes).

\$1695.00

MODEL 5711 D

(5711 with counter and DMM).

\$2495.00

CIRCLE 126 ON FREE INFORMATION CARD

Small size.
Small price.



DM10 . . . \$39.95*

Don't settle for an analog multimeter. Now, for the same low price you can have a reliable digital multimeter that's easier to use, easier to read, and is three times more accurate.

- DCV accuracy 0.8% of reading
- 1/2" LCD digits
- 5 Functions (ohms, DCA, ACV, DCV, Diode check)
- Overload protection (250V in ohms)
- 250 Hour battery life.

This is the ideal carry-one-anywhere meter. Tool box, glove box, shirt pocket. Whenever you need to make a measurement, you're ready.

Also available, featuring a continuity beeper, is the DM10B for only \$49.95.*

Both models include a 9V battery, safety test leads, and operator's manual.

Get one now at your local Beckman Industrial distributor. *Suggested list price.

Beckman Industrial
A subsidiary of Emerson Electric Co.
630 Puente Blvd.
Brea, Calif. 92621

Beckman Industrial™

EQUIPMENT REPORTS

Vidicraft Detailer III Image Enhancer

Improve your VCR's
performance with this
versatile accessory



CIRCLE 5 ON FREE INFORMATION CARD

IT USED TO BE THAT THE WORD "VIDEO" meant nothing more than TV to most people. But, since the advent of VCR, all that has changed. And with those changes has come a change in what we are willing to accept in terms of video quality.

These days, very few are content to "just accept" the video quality provided by our home set-ups. Instead, we are always seeking ways to improve the image that is displayed on our monitors or receivers. One way to achieve a noticeable improvement is with a video amplifier or enhancer. Those units increase picture detail and sharpness by boosting or amplifying the higher frequencies in a video signal. The high frequencies is where much of the fine detail of a video picture is located.

We recently looked at the *Detailer III*—one of the newest video enhancers from Vidicraft (0704 S.W. Bancroft St., Portland, OR 97201).

The *Detailer III*

The *Detailer III* is a video enhancer that is designed to improve the performance of VCR's, videocameras, and videodisc players. As with all other such units, this enhancer's performance is greatly influenced by the quality of the material with which it used. In other words: The better the source, the better the results. When, for instance, the unit is

used to enhance a tape of a quality over-the-air signal, dramatic increases in picture quality will result. On the other hand, use with a third-generation VHS tape recorded at the machine's slowest speed will produce minimal results.

One reason that the law of diminishing returns holds so strongly when it comes to video is that the same high frequencies that hold so much of the picture detail also contain much of the interference that is commonly called snow. Thus, when you enhance detail, you also enhance snow. In order to minimize that increase in snow, most video enhancers are equipped with some sort of noise-reduction system. The one contained in the *Detailer III* is two-fold.

One part of the noise-reduction system in this unit is Vidicraft's VNX circuit. That noise-reduction circuit suppresses certain low-amplitude, high-frequency enhancements. As such, it seems to perform the exact opposite of the unit's enhancement function. But the VNX system uses a different set of thresholds. The result is a reduction of snow at the expense of some of the increased detail, but the overall result is an improved picture.

The second noise-reduction system is "black noise reduction". That system reduces the level of

continued on page 32

LITTLE THINGS MEAN A LOT

As the first company to make solderless breadboards, it's not necessarily what makes the best. It's all the little things you don't see, like our spring clip terminals, that make us the best. **AP PRODUCTS ACEBOARDS** so you can rely on reliability. From our large ACEBOARD to our smallest with over 5000 tie points, to a single tie point block, our spring clip terminals give you nothing but good, solid contact on every connection. They accommodate a wide variety of leads and have the best electrical properties, because our springs are solid alloy, not plated metal. We've even developed enough normal force to break through any oxides which could occur on solder plated leads. You've come to trust our test clips for the same reason. Since one bad connection can ruin a whole circuit, we pay close attention to how well our spring clip terminals sit within the insulator cell areas. Spring clip edges are never exposed at the insertion window.

Leads won't buckle, clips won't oxidize, it all adds up to longer life.

Even from the outside there's more to an ACEBOARD than meets the eye. Our durable Acetal Copolymer plastic body is a

good insulator with excellent dielectric properties. And special manufacturing techniques in the insertion of the contacts into the plastic body insure that your Breadboard will always remain flat. No skimping or planned obsolescence here. Again, just good solid contact on every connection.

Turn our breadboard body over...and you'll discover another key to its reliability. The double-sided adhesive foam you'll

see there is more than a pressure sensitive mount. It also insulates to prevent shorts and seals the bottom of the individual spring clip cells.

If solder shavings from resistors or component leads drop into the cell, they can't spread into other cells to short them out.

Take a close look at our ACEBOARDS. AP PRODUCTS has the biggest and most complete line of ACEBOARD sizes. It's also our commitment to you that if your ACEBOARD doesn't

work perfectly, bring it back to your AP PRODUCTS distributor. He'll replace it, no hassles.

To help you see for yourself what a big difference the little things make, we're offering you a 10% discount on the entire AP PRODUCTS ACEBOARD/Breadboard line.

Just fill out the coupon and present it to your AP PRODUCTS distributor.

For the name of the distributor nearest you, call TOLL FREE (800) 321-9668. In Ohio, call collect: (216) 354-2101.



AP PRODUCTS INCORPORATED

1325 Progress Parkway, Box 540
Mentor, Ohio 44060, (216) 354-2101
FAX: 810-425-2250
In Canada, call Lenbrook Electronics • (416) 477-7722

CIRCLE 76 ON FREE INFORMATION CARD

10% OFF

The purchase price of any size ACEBOARD or Breadboard product.

Your Name _____



Address _____

City _____ State _____ Zip _____

Dealer Name _____

ACEBOARD # _____

  Limit 5 ACEBOARDS or Breadboards per coupon. Offer valid only at participating AP PRODUCTS distributors. RE 785



What can you do Just about

CIE can show you how.

Computer technology. Satellite communications. Cable television. Cellular radio. Digital electronics. Robotics. Just a few of the hottest career areas in electronics. The ones everybody is talking about. The ones that are changing the way we live, the way we do business, the way we entertain ourselves. The best way to start a career in any of them? By learning the basic electronics theory and principles of how they work from CIE.

Join a leader.

Leading the world in specialized electronics training, CIE is the largest school of its kind with over 25,000 students at home and abroad. And with over 50 years of experience teaching electronics to thousands of men and women through proven



methods of independent study **without** classroom sessions.

Learn as much as you want, when you want.

Whether you're interested in learning new skills or upgrading old ones, earning a diploma or an A.A.S. degree, CIE can match your needs with courses and programs that let you start where you want, go as far as you want from a basic beginner course all the way to CIE's Associate in Applied Science Degree in Electronics – a comprehensive program that prepares you for advanced electronics careers.

Custom training equipment helps you learn.

  CIE believes in the importance of learning by



with electronics? anything.

doing. So most of our courses include specialized training laboratories keyed to specific lessons for practical experience through teaching experiments. Our CIE Microprocessor, for example, comes fully assembled and ready to use to teach you how a computer CPU works through a series of experiments you perform on your own.

Are you ready?

If you're ready to do something now about your future, there's no waiting to enroll with CIE. Get all the information you need to enroll simply by calling us toll-free at **1-800-321-2155** (in Ohio, 1-800-362-2105). Or mail in the handy reply coupon or card to Cleveland Institute of Electronics, 1776 East 17th Street, Cleveland, Ohio 44114.

CIE World Headquarters

Cleveland Institute of Electronics, Inc.
1776 East 17th Street • Cleveland, Ohio 44114

- Please send me your CIE Off-Campus Studies Catalog, including details about the Associate Degree program. I understand there is no cost for the catalog and a CIE representative may call, but there is no obligation.

Print Name _____

Address _____ Apt. No. _____

City _____ State _____ Zip _____

Age _____ Area Code/Phone No. _____/ _____

Check box for G.I. Bill bulletin on Educational Benefits

- Veteran Active Duty

MAIL TODAY!

RE13

EQUIPMENT REPORTS

continued from page 26

enhancement in the dark areas of the picture. In those areas, increases in detail are not particularly noticeable, but increases in snow are.

One interesting feature of the *Detailer III's* enhancement system is the SPLIT SCREEN function. That allows you to use a front-panel control to split the picture into en-

hanced and unenhanced regions. That allows you to easily examine the effect of the enhancer on the video signal.

Other features of the unit include a four-input switching system and a distribution amplifier. Both features are capable of handling stereo audio as well as video. The unit's input and output connectors are all located on the rear panel. Included among those are four video inputs, four stereo (or mono) audio inputs, four video

	Vidicraft					Detailer III				
OVERALL PRICE										
EASE OF USE										
INSTRUCTION MANUAL										
PRICE/VALUE										
	1	2	3	4	5	6	7	8	9	10
	Poor		Fair			Good			Excellent	

outputs, and four stereo (or mono) audio outputs. Also on the rear panel are three accessory loop input/output connectors. Those allow additional video and audio accessories, such as a video processor or a stereo synthesizer, to be easily interfaced with the system. Any accessory placed in the loop will process any input selected. Input selection is done from the front panel. The selected input is indicated by a front-panel LED.

The *Detailer III* is an extremely versatile device. One indication of that is the number of interconnection schemes presented in the unit's manual. Set-ups with as many as eight permanently connect VCR's are outlined.

Speaking of the manual, it does an excellent job of showing you how to get the most out of the unit. All of the numerous hook-up schemes are illustrated in painstaking detail, and front-panel settings are both described and shown. Newcomers to video have not been forgotten by the manufacturer; sections covering such basic topics as the differences between the various types of connectors used in video set-ups have been included. Unfortunately, as is the case with many similar pieces of equipment, those more technically inclined have been overlooked; no technical details (theory of operation, schematic, etc) on the unit are provided. Additionally, only rudimentary troubleshooting information is provided.

On the whole, we are very pleased with the *Detailer III*. Its flexibility and performance should put it at the top of any serious video hobbyist's shopping list. The unit, which is covered by a twoyear warranty, has a suggested retail price of \$349.

R-E

Because they are built to last... Global breadboarding sockets are guaranteed for a lifetime.


For more than a decade, Global Specialties' solderless breadboarding has set the standard for quality, durability and dependable performance. Now, we offer a lifetime guarantee. If a Global breadboarding socket fails to perform according to your needs, you merely return it to Global Specialties. We will send you a replacement free of charge. *No questions asked.*

This unconditional guarantee is offered because our breadboarding sockets provide outstanding performance, indefinitely. All of our sockets are made in the United States in our own factory, employing the latest equipment, manufacturing methods and quality control procedures. Each socket and bus strip is molded of high quality plastic material to provide superior strength and durability. Precision-formed contacts and tie-points made from nickel-silver assure excellent contact every time.

Seven sockets and three bus strips are included in our QT Series. Our new UBS-100 and UBS-500 models and our Experimentor line include socket and bus strip contact arrangements in single modular breadboards.

The industry's largest selection, unmatched quality and economy have earned Global solderless breadboarding sockets the reputation for being number one with professionals, hobbyists and students. Now, the unconditional lifetime guarantee is your assurance that when you buy from Global you receive maximum durability and trouble-free performance. Unlike some manufacturers who require that you purchase by mail, our nationwide network of distributors permits you to see and inspect our products before you buy.

 See your electronics distributor or for the name of your local distributor, call our . . . Customer Service Department, toll-free 1-800-572-1028.



Introducing the UBS Series



Two new solderless breadboarding sockets have been added to the Global line. The new UBS-100 is now the largest socket in the line, with 840 tie-points and the smaller UBS-500 has 430 tie-points. Each includes two rows of bus strips on each side for power and ground connections and the UBS sockets are made of the highest grade plastic material to insure maximum resistance to warping and breaking.




GLOBAL SPECIALTIES
An Interplex Electronics Company

70 Fulton Terrace
New Haven, CT 06512-1819
(203) 624-3103 TWX: 710-465-1227

Sabadia Export Corporation eZ Board

 Solderless breadboard system for use with your personal computer



CIRCLE 6 ON FREE INFORMATION CARD

MANY PERSONAL-COMPUTER MANUFACTURERS have provided for future expansion of their machines by supplying some type of expansion slot. At that slot, all of the signals to and from the micro-processor are made available. And many enterprising manufacturers have taken advantage of the availability of those expansion slots to devise add-on accessories to expand a computer's capabilities.

But you are not necessarily limited to the add-on circuitry developed for you by others. As long as you have access to those lines, there are an almost unlimited number of circuits that you can build. There is, however, a difference between having access to those lines, and having easy access to them.

But having easy access to those lines has now become much, well, easier, thanks to the Sabadia Export Corporation's (PO Box 1132, Yorba Linda, CA 92686) eZ Board. That product is a solderless breadboarding system that allows you to develop and build your own circuits, and interface them with your computer via its expansion slot.

The eZ Board

eZ Boards are available for three different computer systems. Those are the Apple IIe (and II and II+), IBM PC, and Commodore computers. The unit we examined was for use with the Apple IIe, and

KeproClad

by Kepro Circuit Systems, Inc.™

Over Spending For One Professional Quality PCB?

Kepro, a major manufacturer for over 25 years of PCB prototyping and short run equipment and supplies now offers you a solution - KeproClad.

KeproClad copperclads either meet or exceed NEMA standards and come either unsensitized with marking pen or photosensitized with developer included for fine line professional boards in minutes. Both types come in a variety of sizes.

You only need a single board, so why buy more than you need, and why send your designs out? Especially when KeproClad is so easy. Just follow the simple steps to a hassle free, inexpensive professional quality Printed Circuit Board.

The KeproClad line also features a photo reversing kit for making negative film, etching chemistry, tin plating solution and photo flood lamp. And of course, you can get art, shears, drills and other equipment and supplies from Kepro your one stop source to PCB equipment and supplies.

If you need Professional quality PCB's call your local distributor and ask for KeproClad. If your distributor doesn't carry KeproClad call or write us. We will put you in touch with the distributor nearest you.

KEPRO CIRCUIT SYSTEMS, INC.
630 Axminister Drive., Fenton, MO 63026-2992
In MO 314-1630 Toll Free 800-325-3878

CIRCLE 266 ON FREE INFORMATION CARD

SEE YOUR DEALER TODAY

FROM



HERE'S A TIP THAT'S PERFECT!

AM/FM AUTO RADIO AND CB

'Firestik' II

GOLDEN SERIES

BARE-HANDS TUNABLE
"NO TOOLS NEEDED"
HIGH PERFORMANCE ANTENNAS

ALSO ANTENNAS FOR
CORDLESS TELEPHONES
MONITOR SCANNERS

Dealer & Distributor Inquiries Invited
SEND FOR FREE CATALOG

'Firestik' Antenna Company
2614 East Adams/Phoenix, AZ 85034

Name _____

Street _____

City _____

State _____ Zip _____

Serving the CB and
Communications Market Since 1962.

5-YEAR REPLACEMENT WARRANTY

CIRCLE 100 ON FREE INFORMATION CARD

100 MHz

3 CHANNELS . . . \$1,495



- Alternate Time Base
- Simultaneous Trigger View
- 2 ns/div, Max Sweep

- Multimode Display
- P-P Auto Trigger
- Nationwide Sales and Service

5% discount when you call Tom and order direct.

(800) 421-5334

KIK #3 in scope sales

Offer good thru 7/31/85.
MasterCard and Visa accepted.

17819 S. Figueroa St., Gardena, CA 90248
(213) 515-6432

CIRCLE 254 ON FREE INFORMATION CARD

that is the one that we'll describe here.

The *eZ Board* system for the Apple is made up of three parts. Of course, there is the main breadboard unit, which contains the solderless breadboarding strips. Also provided is a system-bus interface card, which is inserted into one of the Apple's expansion slots. The third component is a length of flat ribbon cable that is used to connect the two.

The system-bus interface card is

made up of a connector for the ribbon cable and a gold-plated card-edge connector.

The main breadboard, or development board, contains a connector for the ribbon cable, tie points for all of the expansion-bus signals and supply voltages, four bus strips, and three solderless breadboard strips. The breadboard strips can accommodate up to 24, 14-pin DIP IC's. Also located on the development board is a DIP switch with 4 SPST switches.

Audio/video to go

In the studio. On the set. Or in the workshop. Take along Sams books and you'll always have the audio/video engineering knowledge you need in your hands—wherever you go.

Sams audio/video books cover it all. From production to equipment servicing. You'll learn about the state-of-the-art in cameras, video discs, editing systems, cable television, audio equipment, and more. And you'll learn how to choose the right components and equipment to design your own systems.

You'll get more out of Sams books. Because we put more into them. More charts, pictures and technical descriptions. All organized for quick, easy reference.

For the best books on audio/video, go for Sams. Visit your local Sams dealer. Or call our toll-free

number and ask for Operator 132.

Video Cameras: Theory and Servicing, No. 22382, \$14.95
Cable Television, No. 21755, \$13.95
Sound System Engineering, No. 21156, \$21.95
Handbook for Sound Engineers, No. 21983, \$44.95
Principles of Digital Audio, No. 22388, \$15.95
Principles of Solid State Power Conversion, No. 22018, \$44.95
The Video Guide, No. 22051, \$18.95

800-428-SAMS

In Indiana, call 317-298-5566

SAMS

Howard W. Sams & Co., Inc.
 4300 West 62nd Street
 Indianapolis, IN 46268



CIRCLE 269 ON FREE INFORMATION CARD

The supplied 50-conductor ribbon cable is 18 inches long, which allows you at least some degree of freedom in positioning the development board. The connectors on the ribbon cable mate with those on the development board and system-bus interface card to assure error-free connections between the board and the computer.

Options

For greater flexibility, the manufacturer offers two valuable options for the *eZ Board*. Use of those options will help you get the most out of your unit.

One of those is a buffer/decoder board. That board provides buffers for the address and data lines, as well as an address-decode/chip-enable line to the circuitry on the development board. Having such

	SABADIA eZ Board									
OVERALL PRICE	1	2	3	4	5	6	7	8	9	10
EASE OF USE	1	2	3	4	5	6	7	8	9	10
INSTRUCTION MANUAL	1	2	3	4	5	6	7	8	9	10
PRICE/VALUE	1	2	3	4	5	6	7	8	9	10
	Poor		Fair			Good			Excellent	

a circuit between the computer and the *eZ Board* is important, as it greatly minimizes the chances of harming your computer with your experiments.

If the buffer/decoder board is not purchased, a buffer/decoder circuit should be incorporated into your design. But, while the circuit for the buffer/decoder is simple, and is provided in the unit's excellent instruction manual (more on that later), it does take up room on the development board. Using the buffer/decoder board frees that otherwise occupied space up for your circuitry. If it is purchased, the buffer/decoder board takes the place of the system-bus interface board.

The other option is an expansion breadboard module. It uses the same solderless breadboarding strips as found on the development board, and allows larger circuits to be accommodated. That allows for the construction of very

large circuits since as many additional modules as needed for that circuit may be used.

The manual supplied with the unit is not fancy, but it gets the job done nicely. In addition to some basic information about the board, the manual goes into a bit of detail about the Apple computer and the 6502 microprocessor that it uses. (We examined the Apple version.)

Also included in the manual are two basic circuits to get you started using the *eZ Board*. Those are a parallel port and a joystick interface. Both circuits are thoroughly explained, and schematics, parts lists, theory of operation sections, testing procedures, and software listings are provided to make building and using the circuits easier.

Like the manual, the unit itself is not fancy, but it gets the job done. Our only complaint was that while all of the power and signal lines are clearly identified on the development board, that identification is merely printed on strips of paper that are glued to the board. It would have been nice to see a more permanent method used.

As to prices, the *eZ Board*, which is available directly from the manufacturer, sells for \$124.95, the buffer/decoder board for \$49.95, and the expansion modules for \$19.95 each. In addition, there is a \$5.00 shipping and handling charge on all orders. **R-E**



"I can't believe it—a whole trunk full of radio parts, but not a single piece of wire."


DON'T FORGET



USE
YOUR
READER
SERVICE
CARD

DUAL TRACE OSCILLOSCOPES

 
(TWO QUALITY 10:1 HOOK ON PROBES INCLUDED)



SALIENT FEATURES:
SINGLE SWEEP
DELAYED TRIGGERING SWEEP
DELAY TIME BECOMES DIM.
SWEEP STARTS AT TIME DELAYED.
ALT. TRIGGER FOR TWO
NON-SYNCHRONIZED SIGNALS.

BRIEF SPECIFICATIONS:
DEFLECTION FACTOR:
5MV/DIV. — 10V/DIV.
1MV/DIV. (5X gain)
RISE TIME: Less than 10ns.
TIME BASE: 0.1µs — 0.5µs/DIV.

DX5035 35MHz \$527.00

 

SALIENT FEATURES:
DELAY LINE TO PERMIT
ANALYSIS OF RISE TIMES.
DELAYED TRIGGER SWEEP
FEATURE AS DX5035.
WIDE FREQUENCY BAND
WIDTH, SCALE ILLUMINATION.

BRIEF SPECIFICATIONS:
DEFLECTION FACTOR:
5MV/DIV. — 5V/DIV.
1MV/DIV. (5X gain)
RISE TIME: Less than 8ns.
TIME BASE: 0.2µs — 0.5µs/DIV.

DX5045 45MHz \$789.95

ALSO AVAILABLE: DUAL TRACE OSCILLOSCOPES WITH PROBES INCLUDED.
DX5020 20MHz AT **\$379.95** DX5015S 15MHz AC/DC
OPERATED AT **\$510.00**.

TERMS:

One year limited warranty on parts and labor.
Satisfaction guaranteed, or return unit in original form for refund
within 10 days from date merchandise received.
California residents add 6½% sales tax.
Orders shipped UPS, add \$8.50 for shipping handling and insurance.

TO ORDER: CALL COLLECT **(714) 594-7131** VISA,
MONEY ORDER, MASTERCARD, C.O.D. (REQUIRED 25% DOWN)

DELTA DELTAX DYNAMIC INC.
20955 E LYCOMING ST., WALNUT, CALIF. 91789, TELEX: 503749 DELTAX

CIRCLE 271 ON FREE INFORMATION CARD

40 MHz 3 MODELS FROM \$695



5% discount when you call Tom and order direct.

- 3 CH, Alternate Time Base
Simultaneous Trigger View \$895
- 2 CH, Single Time Base \$695
- 2 CH, Delayed Sweep \$795
- P-P Auto Trigger
- Nationwide Sales and Service

(800) 421-5334

KIK

Offer good thru 7/31/85.
MasterCard and Visa accepted.

17819 S. Figueroa St., Gardena, CA 90248
(213) 515-6432

CIRCLE 255 ON FREE INFORMATION CARD

JULY 1985

35

60MHz or 100MHz scope?

Look at all the
features of
B&K-PRECISION's
60MHz 3-trace model!



Model 1560 \$1150

With most of the features you would expect to find on 100MHz scopes, the Model 1560 is the ideal scope for situations where a 100MHz unit is not essential.

Check these features:

- 1 mV/div sensitivity
- Signal delay line
- Video sync separators
- X-Y operation • Z axis input
- 16 kV accelerating voltage
- X10 sweep magnification
- Delayed sweep/dual time base
- Single sweep • Auto focus
- V mode - displays two signals unrelated in frequency
- Sum & difference capability
- Channel 1 output
- Includes probes

For \$950, the 40MHz, Model 1540 has all the same features, except it is dual trace with 12kV accelerating voltage.

In stock for immediate delivery from your B&K-PRECISION Distributor.

BK PRECISION
DYNASCAN
CORPORATION

6460 West Cortland Street
Chicago, Illinois 60635 • 312/889-9087
International Sales: 6460 W. Cortland St., Chicago, IL 60635
Canadian Sales: Atlas Electronics, Ontario
South and Central American Sales:
Empire Exporters, Plainville, NY 11903

CIRCLE 77 ON FREE INFORMATION CARD

NEW PRODUCTS



CIRCLE 11 ON FREE INFORMATION CARD

PORTABLE RADIO, model *RF-B600*, is a digital-frequency communications receiver. Ten-key direct-access tuning makes finding a station as easy as pressing the numbered buttons corresponding to the desired frequency's number. (To tune to 95.7 on the FM band, for example, just press the "9," "5," decimal point, and "7" buttons.) The nine-memory, scan/seek function stops at every station in either frequency direction for approximately five seconds before continuing. The seek function automatically searches for the

strong-signal stations, remaining there until the function's button is pushed again.


Other features include a five-digit fluorescent digital readout, RF gain control, a 3½" PM dynamic speaker, universal voltage adaptor, and AC power cord. The system operates on eight "D"-size batteries (not included), and three "AA"-size batteries (not included) for memory backup.

The model *RF-B600* has a suggested price of \$549.95.—**Panasonic**, One Panasonic Way, Secaucus, NJ 07094.

DIGITAL STORAGE OSCILLOSCOPE, model *LBO-5825*, is a 2-channel model that has a 2K-word memory, a 5-MHz maximum sampling rate, and pre-trigger view capability. X-Y recorder output terminals are provided for use with a plotter, and simul-

taneous display of real time and stored waveforms are possible. Other features include roll function, memory protect, external clock provision, and automatic chop/alternate model select.

 The model *LBO-5825* is designed for such applications as



CIRCLE 12 ON FREE INFORMATION CARD

stress analysis, shock and vibration testing, power-line transient monitoring, and computer glitch problems. It may also be used for production-line environments, because a stored reference waveform can be compared to an alignment waveform, expediting final adjustment of equipment by the technician.

The model LBO-5825 is priced at \$3,850.00.—**Leader Instruments Corporation**, 380 Oser Avenue, Hauppauge, NY 11788.

AUDIO ISOLATION TRANSFORMER, the AUD-IT, is intended for use in 600 ohm, line level applications where the user needs to isolate an audio input/output signal, or remove power-line hum caused by ground loops. The



CIRCLE 13 ON FREE INFORMATION CARD

AUD-IT features two isolated RCA connectors for quick termination, compact size (2" x 2" x 1.25"), a color-coded metal enclosure, and built-in mounting tabs. It is priced at \$39.95.—**V.A.M.P. Inc.**, PO Box 411, Los Angeles, CA 90028.

BENCH MATS, *StopSlip Pads*, are durable, flexible plastic, green in color, with a high co-efficient of friction against other dry materials. They can withstand rough handling, are highly noise-absorb-

ing, and protect work surfaces from scratching. They also prevent parts of any shape from rolling, sliding, or creeping, regardless of the force exerted on them. The friction characteristic of the material never diminishes, and you will find that keeping them clean is a simple matter. Just use mild soap and water; that is all that is necessary.

StopSlip Pads are available in pre-cut sizes one foot square and up, or in rolls ready to cut with scissors for the user's own require-




CIRCLE 14 ON FREE INFORMATION CARD

ments. Retail prices start at \$9.90 for a 10-inch square.—**Solder Absorbing Technology, Inc.**, South End Bridge Circle, Agawam, MA 01001.

R-E

Radio-Electronics

 SPECIAL REPRINT
BUILD A BACKYARD SATELLITE TV RECEIVER



NEWLY EXPANDED 1985 EDITION
Includes Antenna Rotator and
RF Converter for Stereo
Build Your Own and Save Dollars

Don't miss out again!

Send away today for your 36-page booklet containing a complete reprint of all seven articles in the series on Backyard Satellite TV Receivers by Robert B. Cooper, Jr.

This all-inclusive report give you all the data you need to build your own Backyard Satellite TV Receiver.

- TELLS ALL ABOUT domestic satellite communications, with full details on how you can pull those elusive TV signals from space.
- LEGAL REQUIREMENTS, technical

specifications, and how you, the home constructor, can meet them. Find out what mechanical and electronics skills you need.

- RECEIVER CHARACTERISTICS, technical details and specifications, along with examples of actual receivers built at comparatively low cost.

■ ANTENNA DESIGN... and exactly how you can build a spherical antenna, while keeping total earth-station cost for the complete system under \$1,000.

- THE FRONT END is critical when you build your own system. We help you explore several different approaches to making one

that will work for you.

- RECEIVER-SYSTEM hardware, and how it goes together to bring you direct-from-satellite TV reception in your own home.

To order your copy:

Complete coupon and enclose it with your check or money order for \$7.00, plus \$1.00 for postage and handling. We will ship your reprint within 6 weeks of receipt of your order. All others add \$4.00 for postage. New York State residents must add 58¢ sales tax.

Radio-Electronics

Satellite TV Reprints
45 East 17th Street
New York, N.Y. 10003

Please print

(Name)

(Street address)

(City)

(State)

(Zip)

I want _____ reprints (at \$7.00 each, plus \$1 for handling & First Class postage.
I have enclosed \$ _____ N.Y. State residents must add sales tax. (U.S. and Canada only)

Professional Books That Help You Get Ahead—And Stay Ahead!

Join the **Electronics and Control Engineers' Book Club**® and...

- Keep up with current technology
- Sharpen your professional skills
- Be ready for new career opportunities
- Boost your earning power

THE MCGRAW-HILL COMPUTER HANDBOOK: Applications, Concepts, Hardware, Software. Edited by H. Helms. 992 pp., 475 illus. Everything you need to know about today's computer science and engineering is here in this massive treasure trove of information. Covers everything from Boolean algebra to hardware selection techniques to artificial intelligence. 279/721 Pub. Pr., \$84.50 Club Pr., \$52.95

TRANSDUCERS: Theory and Applications. By J.A. Allocca and A. Stuart. 497 pp., 328 illus. Thoroughly describes and illustrates the theory and operation of all important transducers used in industrial, communication, medical, and other applications. Photographs, drawings, and diagrams are included throughout this outstanding introduction to a key element in electronic instrumentation. 582997-5 Pub. Pr., \$27.95 Club Pr., \$22.95

ANTENNA ENGINEERING HANDBOOK, 2/e. Edited by R. C. Johnson and H. Jasik, with contributions by 57 recognized authorities. 1,408 pp., 946 illus. This widely acclaimed Handbook gives you the guidance you need to solve problems in antenna design and application. It provides detailed information on physical fundamentals, patterns, structures, and design techniques for practical modern antennas. 322/910 Pub. Pr., \$95.00 Club Pr., \$62.50

INTRODUCTION TO RADAR SYSTEMS. By M. I. Skolnik. 2nd Ed., 698 pp., 244 illus. Covering every radar fundamental and all important changes, this EE text exposes you fully to the systems themselves—and to their applications! Topics include radar equation, CW and frequency-modulated radar, MTI, pulse-doppler, tracking radar, receivers, displays, duplexers, noise, and more. 579/091 Pub. Pr., \$43.00 Club Pr., \$32.25

MICROPROCESSOR APPLICATIONS HANDBOOK. Editor-in-Chief, D. F. Stout. 472 pp., 284 illus. At last—a reference guide to microprocessor applications to help you make your systems timely, versatile, and cost-effective. 617/988 Pub. Pr., \$41.95 Club Pr., \$31.45

MICROPROCESSOR AND MICRO-COMPUTER DATA DIGEST. By W. H. Buchsbaum and G. Weissenberg. 336 pp., 93 block diagrams, 106 pin configurations. If you work with electronic devices that use microprocessor or microcomputer integrated circuits, this much-needed book contains all the detailed technical data for every microprocessor IC that is currently listed as a "standard," off-the-shelf item. 582835-9 Pub. Pr., \$29.95 Club Pr., \$22.50

HANDBOOK OF ELECTRIC POWER CALCULATIONS. Edited by A. Seidman, H. Mahrous and T. G. Hicks. 448 pp., 300 illus. Here are 285 tested and proven procedures for handling the electric power problems most frequently encountered in actual practice. You'll find ingenious, time-saving ways to calculate fuel costs, motor efficiency, and power output. 560/617 Pub. Pr., \$41.50 Club Pr., \$31.50



New members!
Any one of these great
professional books
for only **\$2.89**
as a premium with your
1st selection!

Spectacular values up to **\$95.00**

HANDBOOK OF PRACTICAL ELECTRICAL DESIGN. By J. F. McPartland. 416 pp., 300 illus. This volume provides a step-by-step explanation of designing electrical systems for industrial, commercial, and residential applications. Packed with helpful tips for saving time and complying with code requirements from branch circuits to wiring size. 456/95X Pub. Pr., \$40.95 Club Pr., \$27.50

DIGITAL LOGIC DESIGN. By B. Holdsworth. 338 pp., 192 illus. All of the recent advances in digital design techniques are presented here in depth. It's both a text covering basic concepts and a practical guide to design techniques for combinational, clock-driven, and event-driven circuits. 582852-9 Pub. Pr., \$39.95 Club Pr., \$27.50

ELECTRONIC COMMUNICATIONS SYSTEMS. By W. D. Stanley. 566 pp., illus. Emphasizing the signal-processing functions of modulation and demodulation operation, this book presents the essentials of electronic communications in a logical, step-by-step sequence. 582834-0 Pub. Pr., \$25.95 Club Pr., \$20.95

MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL. By J. Markus. 1,264 pp., 3,666 circuit diagrams. Complete with values of components and suggestions for revisions—plus the original source of each circuit in case you want additional performance or construction details. 404/461 Pub. Pr., \$76.95 Club Pr., \$57.95

ELECTRONICS ENGINEERS' HANDBOOK, 2/e. Edited by D. G. Fink & D. Christiansen. 2,272 pp., 2,189 illus. This updated and enlarged edition covers all the latest knowledge in the field, including new advances in integrated circuits, pulsed and logic circuits, laser technology, telecommunications, and much more. 209/812 Pub. Pr., \$83.50 Club Pr., \$63.95

DIGITAL CIRCUITS AND MICRO-PROCESSORS. By H. Taub. 608 pp., heavily illus. This fast-paced, carefully written guide gives you thorough explanations of all the basic principles of digital systems and logic design—plus a solid introduction to microprocessors and microprocessor-based designs. 629/455 Pub. Pr., \$37.00 Club Pr., \$28.75

RADIO HANDBOOK. By W. Orr. 22nd Ed., 1,136 pp., more than 1,300 illus. The latest edition of what is universally regarded as the best liked and most useful communications reference in the industry. It's a handy "course" in communications, a fact-packed reference, and a how-to guide—all in a single book! 582442-6 Pub. Pr., \$21.95 Club Pr., \$17.95

INTRODUCTION TO MICROWAVE ELECTRONICS. By T.C. Edwards. 76 pp., illus., softbound. Eliminating unnecessary theory and mathematics, this book provides you with a lucid overview of microwave engineering and the devices and circuits being used today. Helpful even if you have only limited experience with microwave electronics. 583030-2 Pub. Pr., \$14.95 Club Pr., \$10.95

PRACTICAL DIGITAL DESIGN USING ICs, 2/e. By J. D. Greenfield. 717 pp., illus. This revised and expanded Second Edition of a popular guide shows how to get the most out of a wide range of popular integrated circuits. What's more, it contains the specialized know-how today's designer needs to interface ICs with microprocessors. 582853-7 Pub. Pr., \$25.95 Club Pr., \$19.95

ENGINEERING NETWORK ANALYSIS. By G. H. Hostetter. 912 pp., 372 illus. Emphasizing real-world applications, this comprehensive book covers the full range of analytical techniques for everything from source-resistor networks to switched networks. Brings you fully up to date on all the latest developments. 582966-5 Pub. Pr., \$35.50 Club Pr., \$27.95

STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 11/e. By D. G. Fink and H. Beaty. 2,448 pp., 1,414 illus. Today's most widely used source of electrical engineering information and data serves you as no other single work when you need detailed, timely, and reliable facts. 209/74X Pub. Pr., \$79.95 Club Pr., \$62.95

MICROWAVE SEMICONDUCTOR CIRCUIT DESIGN. By W.A. Davis. 416 pp., heavily illus. Provides in-depth coverage on microwave circuit analysis, passive microwave components, impedance transformers and circuits, broadband directional couplers, mechanical realization of selected transmission lines, CAD, CAM and CAT, characteristics of amplifiers and oscillators, noise, statistical thermodynamics and PN junction theory.

583044-2 Pub. Pr., \$47.50 Club Pr., \$35.50

INTRODUCTION TO RADIO FREQUENCY DESIGN. By W. H. Hayward. 383 pp., illus. This comprehensive volume prepares you to actually design HF, VHF, and UHF equipment and enables you to follow much of the current literature. Structured equation sets make it easy to write programs for small computers or calculators.

582748-4 Pub. Pr., \$29.95 Club Pr., \$24.75

MCGRAW-HILL ENCYCLOPEDIA OF ELECTRONICS AND COMPUTERS. By S. P. Parker, Editor-in-Chief. 960 pp., 1,266 illus., oversized 8 1/2 x 11 format. It's a single-volume library that covers the entire world of electronics from Edison's pioneering work in electricity right up to optical fiber communications, control systems, lasers, radar, TV receivers, artificial intelligence, and computer storage technology.

454/876 Pub. Pr., \$67.50 Club Pr., \$43.95

ELECTRONICS ENGINEERING FOR PROFESSIONAL ENGINEERS' EXAMINATIONS. By C. R. Hafer. 336 pp., more than 200 illus. Actually two books in one—a quick preparation manual to help you pass your P.E. exams on the first try and a rich source of practical electronics engineering information and know-how.

254/303 Pub. Pr., \$32.50 Club Pr., \$25.50

MCGRAW-HILL CONCISE ENCYCLOPEDIA OF SCIENCE AND TECHNOLOGY. Editor-in-Chief S. P. Parker and the Staff of the McGraw-Hill Encyclopedia of Science and Technology. 2,065 pp., 1,600 illus. This volume serves every need for understanding today's science and technology. Written by over 3,000 of the world's topmost experts, including 19 Nobel Prize winners, it covers 75 disciplines from Acoustics to Zoology. A 30,000-entry index and cross-references throughout make it a snap to find the information you're looking for.

454/825 Pub. Pr., \$95.00 Club Pr., \$66.50

COMPUTER METHODS FOR CIRCUIT ANALYSIS AND DESIGN. By J. Vlach and K. Singhal. 656 pp., 148 illus. Computational methods have become an integral part of circuit analysis and design. And a solid understanding of the basics of computer-aided design is a must for engineers who want to achieve their career objectives. This self-teaching book provides that know-how in a logical, easy-to-follow presentation.

582855-3 Pub. Pr., \$42.50 Club Pr., \$33.95

ELECTRONIC NOISE. By A. Ambrózy. 281 pp., illus. The data you'll find here will help you understand and cope with noise in all types of circuits. Covers noise parameters of linear networks, measurement techniques, effects of nonlinear transfer characteristics, and more.

011/249 Pub. Pr., \$44.50 Club Pr., \$34.25

Be sure to consider these important titles as well!

FIBEROPTIC & LASER HANDBOOK. By E. Safford. 583104-X Pub. Pr., \$21.95 Club Pr., \$16.50

VLSI SYSTEM DESIGN. By S. Muroga. 582823-5 Pub. Pr., \$34.95 Club Pr., \$26.50

MICROPROCESSOR SUPPORT CHIPS: Theory, Design, and Applications. By T. J. Byers. 095/183 Pub. Pr., \$39.50 Club Pr., \$31.00

ENGINEERING FORMULAS, 4/e. By K. Gieck. 232/199 Pub. Pr., \$18.95 Club Pr., \$14.50

ELECTRONICS CIRCUITS NOTEBOOK. Edited by S. Weber. 192/448 Pub. Pr., \$35.50 Club Pr., \$27.50

ANALYSIS AND DESIGN OF DIGITAL INTEGRATED CIRCUITS. By D. A. Hodges and H. G. Jackson. 291/535 Pub. Pr., \$36.95 Club Pr., \$30.25


HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN. By D. E. Stout & M. Kaufman. 617/97X Pub. Pr., \$42.50 Club Pr., \$31.25

ENGINEERING MATHEMATICS HANDBOOK, 2/e. By J. J. Tuma. 654/298 Pub. Pr., \$36.50 Club Pr., \$28.95

DIGITAL COMMUNICATIONS. By J. Proakis. 509/271 Pub. Pr., \$42.95 Club Pr., \$31.50

SIGNALS AND SYSTEMS. By A. Oppenheim, A. Willsky, and I. Young. 582674-7 Pub. Pr., \$36.95 Club Pr., \$28.95

 MAINTAINING AND REPAIRING VIDEOTAPE RECORDERS. By R. L. Goodman. 582895-2 Pub. Pr., \$15.45 Club Pr., \$12.50



Why YOU should join now!

- **BEST AND NEWEST BOOKS IN YOUR FIELD** — Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.
- **BIG SAVINGS** — Build your library and save money too! Savings ranging up to 30% or more off publishers' list prices — usually 20% to 25%.

BONUS BOOKS—You will immediately begin to participate in our Bonus Book Plan that allows you savings up to 70% off the publishers' prices of many professional and general interest books!

- **CONVENIENCE** — 12-14 times a year (about once every 3-4 weeks) you receive the Club Bulletin FREE. It fully describes the Main Selection and Alternate Selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing — it will be shipped automatically. If you want an Alternate Selection — or no book at all — you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want, you may return it for credit at the Club's expense.

As a Club member you agree only to the purchase of three books (including your first selection) during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the first selection plus two additional books.

Other McGraw-Hill Book Clubs:
 Architects' Book Club • Byte Book Club • Chemical Engineers' Book Club
 • Civil Engineers' Book Club • Mechanical Engineers' Book Club

For more information, write to:
 McGraw-Hill Book Clubs, P.O. Box 582, Hightstown, New Jersey 08520

MAIL THIS COUPON TODAY

McGraw-Hill Book Clubs
Electronics and Control Engineers'
Book Club®
 P.O. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the two books indicated, billing me for the \$2.89 premium and my first selection at the discounted member's price, plus local tax, shipping, and handling charges. I agree to purchase a minimum of two additional books during my first year of membership as outlined under the Club plan described in this ad. A shipping and handling charge is added to all shipments.

Write Code No. of
\$2.89 selection here

Write Code No. of
first selection here

Signature _____

Name _____

Address/Apt. # _____

City _____

State _____ Zip _____

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members.

E33731

BUILD THIS

If you've been wondering if you can obtain IBM compatibility for a reasonable price, the answer is that you can. We'll show you how.

ELLIOTT S. KANTER

FOR BETTER OR FOR WORSE, THE IBM PC HAS BECOME THE *DE FACTO* standard personal computer. Of course, like all computers, the PC has its shortcomings. But its most serious problem is its expense. There is a way around that problem, however, and **Radio-Electronics** will show you that way. We'll show you how you can put together a PC-compatible computer using parts available from HiTech International. We'll explain how the computer works, and we'll review its performance.

HiTech International, whose computer we'll be assembling, is a supplier of IBM PC XT-compatible motherboards (system boards) and other accessories. The best part about the HiTech computer is that even a novice at electronics construction can assemble his own computer at considerably less cost than IBM's offering.

PC Compatible Computer

 


TABLE 1
IBM PC XT SPECIFICATIONS

Microprocessor:	Intel 8088 (4.77 MHz) with socket for addition of an 8087 math co-processor.
Memory:	ROM: 40K, includes BASIC interpreter. RAM: Either 128K or 256K onboard, expandable up to 640 KB with a memory-expansion card
Keyboard:	83-keys with 10 function keys, numeric/cursor keypad, adjustable typing angle, and detachable 6-foot coiled cable
Mass Storage:	10 MB fixed/hard disk, 360 KB double-sided/double density 5¼-inch disk drive
Expansion:	Eight expansion slots
Software:	Diagnostics, <i>Microsoft</i> cassette BASIC interpreter in ROM
Operating System:	PC DOS 2.1 (with advanced disk BASIC)
Size:	5½ × 20 × 16 inches
Weight:	32 pounds
Cost:	\$3895
Warranty:	90 Days.

TABLE 2.
BASIC IBM PC XT

Part No.	Item	Price
8529254	PC XT motherboard with 128K RAM	\$750.00
8529247	130-watt power supply	\$390.00
8529161	Base Assy (case bottom)	\$ 86.00
852963	Bezel Assy (case front)	\$ 41.50
8529209	Top Cover (case)	\$ 50.50
	Keyboard assembly (complete)	\$270.00
	64K memory modules (2 required)	\$200.00(2)
	TOTAL:	\$1788.00

 


FIG. 1—A BLOCK DIAGRAM of the IBM PC XT shows the “musts” for a personal/business computer. The HiTech PC also has the same block diagram.

Many of HiTech's customers are service centers who buy the system or motherboard to use as running spares for PC XT's brought in for repair. The boards are the same size as IBM's, and—with the exception of the lack of BASIC in ROM—have the same form and function as that of the PC XT board. The basic

IBM PC XT can not tell the difference between an IBM board or a HiTech board. And, unless you run the *Advanced Diagnostics Program Diskette* from IBM, neither will you. The discernible difference between the two boards appears as an error message which translates to "Hey, there's no BASIC in the ROM..."

Building by subassembly

In this article, we won't show you how to put together a computer piece-by-piece. (For example, the motherboard is regarded as a single component.) Instead, we'll show you how to build it subassembly-by-subassembly. We'll build the system in stages so that it can be expanded when the need for more functions makes it necessary (or when the cash flow permits). But we're getting a little bit ahead of ourselves. Let's talk more about the IBM PC before we talk about how to assemble a PC-compatible computer.

A brief history of the PC

For many years, the terms "personal computer" and "PC" have been applied to small, limited-use microcomputers which, because of their limited power, have been relegated to home rather than business use. That changed when computer-giant IBM unleashed a small multi-function microcomputer that has become the *de facto* definition for PC. Some three years ago, the IBM PC was introduced to the marketplace and the public's perception of computers changed. More computers were found in small and large offices and in the home. While there were already a number of "business-quality" microcomputers or PC's available, the magic letters IBM tended to make them more acceptable.

There were many other fine companies producing computers. But when the sales figures for any given period are compared, it's obvious that, by numbers alone, IBM was literally taking over the market. Even so, the new entry to the scene was not without its detractors. The most common complaint was (and still is) about the keyboard. The company that pioneered a standard in typewriter keyboards with the *Selectric* really missed the boat with the PC. Some keys are located in illogical positions, and the feel is not comfortable (although you can get used to it). Others complained that IBM could have gone with a more advanced microprocessor, and that the machine was too slow. Despite those, and other, complaints, the sales of PC's continued.

In the business world, if a product sells it's a success! And success breeds imitation and—as the PC imitations came to be known—clones. The buzz words "IBM compatible" became a company's ticket to bigger sales. Many manufacturers did

TABLE 3.
BASIC PC XT HITECH INTERNATIONAL

PC XT motherboard with 128K RAM	\$525.00
Power supply, 130 watts	\$175.00
Case (complete)	\$150.00
Keyboard (complete)	\$150.00
RAM Each 64K 2 required(3)	\$ 50.00
Total:	\$1050.00

TABLE 4
HITECH PC XT SPECIFICATIONS

Microprocessor:	Intel 8088 (4.77 MHz) with socket for addition of an 8087 math co-processor.
Memory:	ROM: 8K implemented (can be expanded by user to 40K) RAM: Either 128K or 256K onboard, expandable up to 640K with a memory-expansion card
Keyboard:	Enhanced Key Tronic 5150 PC. 83-keys with 10 function keys, numeric/cursor keypad, adjustable typing angle and detachable 6-foot coiled cable
Mass Storage:	10 MB fixed/hard disk, 360 KB double sided/double density 5¼-inch disk drive
Expansion:	Eight expansion slots
Software:	Diagnostics, supports DISK BASIC
Operating System:	PC DOS 2.1 (with advanced disk BASIC)
Size:	5½ × 20 × 16 inches
Weight	32 pounds
Cost:	\$2,454.00
Warranty:	1 Year.

TABLE 5
HITECH PC XT + PARTS LIST

Part No.	Description	Price
RE-PCB W/IC	Motherboard with 128K RAM	\$525.00
RE-PS-130	130-watt power supply	175.00
RE-ROM	BIOS ROM	35.00
RE-CASE	Case (complete)	150.00
RE-5150	enhanced keyboard	150.00
RE-MON/DIS	RGB video card	175.00
RE-DISK DR.	Teac 360K disk drive	125.00
RE-CTRL-A	Disk controller/parallel port	175.00
RE-HARD DISK	10 megabyte drive with controller	650.00
RE-YAD	Y Adapter (to attach two drives)	5.00
Total:		2165.00

everything and anything they could to make their offering the same in form and function as the IBM PC. A few companies made such perfect duplicates that they found themselves in legal difficulties with IBM. Others modified their product and qualified their "compatibility" by stating it would "...run *most* of the vast library of business applications packages." That approach was perhaps the most prudent for the company which did not want to earn the attention of the lawyers in residence at IBM. There even were a few computers that *did* achieve compatibility without paying the price of legal hassles and the like. The system from HiTech International, which we are examining in this article, is one of them.

While achieving compatibility is important for the computer company, the bottom line is: Can the average small-business person afford the end product? While the IBM PC appeared on the surface to offer quite a "bang for the buck," closer examination revealed that the options necessary to make the computer a viable tool raised the price upward significantly. Naturally, those companies making "clones" were quick to point that out.

The display card, and other absolutely necessary "options" cost extra, as did sufficient memory, mass storage, printer outputs, etc.

Early in the game, IBM noted the limitations of their original PC and offered first an upgrade of disk drives to dual density, double sided—effectively doubling the available storage capacity on each drive. That wasn't enough. The industry was getting storage-hungry and demanded more and more storage, causing both IBM to turn to a hard-disk drive (often called a "Winchester"), which could bring the mass-storage capacity up to 10 megabytes in the same space as a floppy.

As the consumer was becoming memory-hungry, the computer was rapidly becoming power-poor. The PC's power supply was not capable of supplying the demands that the hard disk placed on it. So IBM was forced to offer a hard-disk storage expansion option together with a heftier supply. But that wasn't all bad; the expansion also added extra I/O slots. (The PC's five slots would be fully populated even in a minimal configuration.) The bad part about the expansion unit was that it

cost almost \$3000.

IBM finally determined what the customer wanted and needed: adequate memory, and more mass storage. Thus, the PC XT was introduced. The letters "XT" were chosen to give the feeling that the computer really had something "extra." (But is it really extra, or is it the minimal configuration that the PC should have been sold in from the start?)

A real computer

The basics "musts" for a personal/business computer are shown in Fig. 1, a block diagram of the motherboard or system board of the IBM PC XT. A listing of the basic specifications of the PC XT is shown in Table 1.

In that PC XT, three of the eight expansion slots are occupied by asynchronous communications, floppy-disk drive and fixed-disk adapter cards. The price shown (\$3895) includes those cards, and 256K RAM. The operating system, PC-DOS 2.10 is optional, and sells for \$65.00. The price shown in Table 1 does *not* include any graphics or video-output card.

No matter how you might look at it, when you take into account the operating system, display adapter card, and printer port, it will cost you in the neighborhood of \$5000 before you have a meaningful computer. That kind of price makes a lot of people wonder just what they're paying for. Is it a premium for the IBM logo, or is it the real value or cost of the computer (known in the trades as MOL or manufacturing overhead and labor). Well, in order to answer that question, let's see what it would cost to put together a basic IBM PC using IBM parts. Then we'll do the same using parts from HiTech.



FIG. 2—THE KEY TRONIC keyboard features a more comfortable feel and layout.

 


FIG. 3—THE BASIC INTERNAL ARRANGEMENT of the HiTech PC. Note that the 8 slots will accept full-size boards—an advantage over the IBM machine.

 


FIG. 4—THE HITECH MOTHERBOARD and some of the features you'll have to be familiar with.

Table 2 shows some pricing data from IBM's Part's Center. (When quoted those prices we were told that "...these prices are firm for today only and may change at any time...") Reduced to its basic building-block level (system board, case, power supply, and keyboard assembly) we see that we could put together a PC with 128K RAM but no disk drives for just under \$1800. (Note that parts numbers are listed shown in Table 2 with the exception of the Keyboard, which is made up of many separate items—at the manufacturing stage—and will be lumped together with the total cost.)

What would be the cost for the same system using parts from HiTech? Are there any real savings and are there any differences? Table 3 shows the prices for

HiTech's basic PC. As you can see, the price is about \$1050—a saving of about \$700. What do you lose? IBM BASIC, which is contained in ROM in the PC. But disk BASIC is supported.

Do you get anything extra? We should note that the keyboard that's furnished by HiTech is the Key Tronic model 5150, shown in Fig. 2. It's fully IBM-compatible but features a "corrected" keyboard layout with a feel unlike the IBM Selectric typewriter.

Now that we've looked at the savings you can hope for with the basic model, let's look at a more fully equipped model. Table 4 lists the specifications for HiTech's version of the XT, which you can compare to Table 1. We should note that two of the eight expansion slots are

occupied by a combination printer/floppy-drive controller and the hard-disk controller. In a similar configuration, an IBM PC XT would have two long and one short expansion slots filled. We should also note that the HiTech expansion slots will accommodate eight full-sized adapter boards as opposed to the IBM's capacity for 5 long and 3 short boards. The price shown does not include a video or graphics adapter card. We should also note that the price shown is for a user-assembled system.

As with the IBM, the operating system (PC-DOS 2.10) is optional and has a suggested retail price of \$65.00. If the standard IBM PC DOS Version 2.10 is used the system will not support BASICA. If the COMPAQ PC DOS Version 2.10 is used, all disk BASIC functions will be supported.

Building the Computer

Now that we've introduced you to the HiTech PC-compatible, it's time to put it together. Assembling your system really is easy and anyone can do it. HiTech seems to have set a standard for simplicity of assembly. The only tool you'll need is a common 1/4-inch flat-bladed screwdriver. And you'll need only about one hour. So we'll assume that if you can turn a screw, you will build your own PC-compatible computer.

Before we go any further, we should point out that a bare board is available from HiTech for \$95. So if you really want to assemble your computer piece-by-piece, you can. Whether you can really save any money depends on how well you can shop for bargains on IC's, connectors, etc. Be advised, however, that because HiTech cannot control how you put your board together, they cannot issue any warranty for a bare board.

 


FIG. 5—THE PROPER SETTING of the configuration switch for our system.

So, assuming that you'll start with a ready-assembled mother board, let's run down the features and components your computer will have:

- Systemboard with 128K RAM
- Single 360KB floppy disk drive
- 10 megabyte hard-disk drive
- 130-watt power supply
- Key Tronic 5150 keyboard
- Parallel printer port
- Applicable controller cards
- Color graphics/monochrome display adapter

continued on page 82




Know Before you Buy

Here are some things to think about before you buy that TVRO system.

BOB COOPER, JR.*
SATELLITE TV EDITOR

Part 2 AS WE SAW LAST TIME, THE LEVEL OF PICTURE quality is determined by two factors. Two of those are the size of the dish, and the sensitivity and gain of the LNA.

Finally, the third factor is receiver IF bandwidth, a parameter that has a direct bearing on the quality of the pictures you receive. Take a look at Fig. 2-a. It shows how the energy of a typical satellite TV signal is concentrated. Note that the majority (about 90%) of the energy is concentrated in the center portion of the signal. As a result, the signal strength in that region is high enough to override the natural noise level. (Noise is caused by a variety of sources including atmospheric conditions, local and space interference, sunspots, etc. As a result, for a signal to be

 

 


FIG. 2—WIDE VERSUS NARROW BANDWIDTH. While most video information is concentrated in the center portion of the signal (see a), luminance and color detail information is found at the signal edges, as is the majority of the noise. Using a narrow bandwidth IF (see b) allows most of that noise to be cut-off, but at the expense of the color detail and luminance. Using a wide bandwidth IF (see c) allows all of the picture information to be processed, but will also provide a noisier picture.

useable, it must override that noise "level.") But at the outer edges of the signal, the concentration of energy is much lower and the noise is no longer completely overridden. Because of that, about 90% of the noise in a signal is found at the edges of that signal.

It is of course possible to design a receiver with either a narrow or a wide IF bandwidth. With a narrow bandwidth, as shown in Fig. 2-b, the band edges are cut-off, allowing only the stronger central portion of the signal to pass. With a wide bandwidth, as shown in Fig. 2-c, all of the signal, as well as all of the noise is allowed to pass.

Now, with 90% of the picture information contained in the central portion of the signal, it would seem logical to go the narrow bandwidth route to obtain as noise-free a signal as possible. There is one major flaw to that, however.

That flaw is that two important parts of the picture information are contained in that ten percent of the signal that is thrown away. Those are the depth-of-field of the color and the high resolution detail in the black and white. To retain all of the color depth and all of the luminance (black and white) detail, you need a to go the wide bandwidth route.

If the satellite signal is good and strong, you can afford to select a wider bandwidth since the sheer strength of the signal will allow the receiver to display a high quality, noise-free picture even with that wider bandwidth. On the other hand, if the signal is weak (because of your having chosen a smaller-than-recommended dish, because of your location, or both), you may need to sacrifice color and detail to get a useable picture.

Receiver data sheets specify IF bandwidth. Some go for the narrow end, a few go for the wide end. Most hang out in the middle, with bandwidths between 24 and 26 MHz.

One last point before we move on. If your installation includes a projection TV, you may not have a real choice as far as bandwidth is concerned. That's because those sets "blow up" the image significantly. What was a small blemish on a 12-inch screen (and perhaps not visible to the

naked eye) becomes a glitch or glob on a four- or six-foot screen. Worse than that, when you take a picture designed to be viewed on a 19-inch tube and blow it up to projection-TV size, the scanning lines themselves becomes visible. And when your satellite receiver has lost the depth-of-color and the luminance detail because of a narrow receiver bandwidth, the picture becomes fuzzy and indistinct; it simply loses its ability to be a pleasing, well defined video image.

So when the installation includes such a set, the best advice is to stick with a dish that's large enough to allow you to use a receiver with a wide bandwidth. That will help make sure that when the picture gets enlarged for display, you don't end up with a fuzzy image that always seems to be slightly out of focus.

Audio considerations

Satellite television "broadcasting" is not broadcasting at all. It was never intended to be a system to transmit individual programs to individual homes; it sort of wound up that way because people got together and starting building equipment that would receive the satellite signals.

Satellite television is simply a relay system, using a single repeater station in-the-sky to relay uplinked microwave signals to stations around the country. Consequently, unlike regular TV, AM, or FM broadcasting, no regulatory agency has ever prescribed technical standards to which every satellite program relay must adhere (aside from rules governing interference to other users).

As you might expect in such an environment, there are a number of different audio formats currently in use (currently 16, though it is expected to grow to as many as 26 within a year). And the audio that is relayed is not limited to just the video signal's audio channel (or channels in the case of stereo). Each transponder has numerous audio subcarriers that carry a wealth of subsidiary services.

Which leads us to our next question: Are you interested in the program audio for television only, or do you also want the non-television audio services?

Program audio (the audio that accom-

panies the video signal) is normally transmitted on a specific subcarrier frequency between 5 and 8 MHz; for example, 6.8 MHz. A TVRO receiver has a tuning knob that allows continuous tuning of the subcarrier frequencies. As a point of information, around 80% of the program audio subcarriers are on 6.8 MHz, another 10% are on 6.2 MHz and the balance are scattered between 5 and 8 MHz.

You might expect that the program audio on the various satellites and transponders would follow a more-or-less uniform format. Unfortunately, that is not the case. For instance, consider audio bandwidth. Because there are no FCC or even industry standards to follow, the programmers have been free to choose almost any bandwidth that suits their needs.

That has put the satellite receiver designer in a bind. That's because while most program audio is transmitted with an FM (deviation) bandwidth of around 250 kHz, some are far greater. The Nashville Network and The Disney Channel, for example, have bandwidths that are closer to 500 kHz. To get around that, most receivers give you two selectable audio bandwidths, labeled narrow and wide.

If the receiver you use does not have an appropriate bandwidth for the audio signal you wish to receive, it is obvious that the reception will not be satisfactory. When you tune in an audio subcarrier that is wider than the receiver's bandwidth, the audio sounds muddy and indistinct. When you tune in subcarrier that is narrower, on the other hand, the audio sounds scratchy or noisy. Therefore, you want to select a receiver that has an appropriate range of bandwidths for the services that you are interested in receiving. We'll return to some tests you can conduct to determine that shortly.

So far we have been concerned with program audio. It is possible for a transponder to transmit not only its own program audio, but also a considerable number of non-TV-program related audio (see Fig. 3-a). The WGN transponder (F3R, TR3), for example, has more than a dozen subcarriers that carry material that has nothing to do with the television. Some of those are data signals, while others are music broadcast services intended for use by AM and FM radio stations. Satellite Music Network, as an example, uses several subcarriers on the WGN transponder to carry an adult contemporary music service, a country and western music service, and an MOR (Middle Of the Road) music service. Each of those services is transmitted in stereo (see Fig 3-b).

And stereo brings in a some further complications.

We've already mentioned that there are many different systems used to transmit monoaural audio. There are, as you might by now have guessed, also different tech-

 


FIG. 3—A TYPICAL TRANSPONDER SIGNAL consists of the video signal, a guard band, and a number of audio subcarriers (see a). The audio subcarriers for F3R, transponder 3 (WGN) is shown in b.

niques used to transmit stereo sound.

When the left audio is transmitted on one channel and the right audio is transmitted on another channel, we have what we call discrete stereo. To receive discrete stereo, the receiver designer has to build into the TVRO system two separate audio subcarrier tuners; one of which the user tunes to a designated subcarrier frequency (such as 5.58 MHz) and the other of which is tuned to another separate subcarrier frequency (such as 5.76 MHz.). One audio channel is found on one of the subcarriers, the other channel is found on the second subcarrier. The system connects to the in-home stereo system simply by connecting the right output of the TVRO receiver audio to the right input on the stereo, and so on.

Not all stereo is transmitted in that format. Some are transmitted in a matrix format. There are still two separate signals, but each involves mixing the left and right channels in a L + R, L - R format. It still requires a pair of subcarriers. One might be on 5.80 MHz and the other on 6.80 MHz, for example. With that system, the user tunes one of his subcarrier tuners to 5.80 MHz, and the other to 6.80 MHz, and inside the TVRO receiver, matrix decoder circuits separate the right and left signals so they can once again be fed to a home stereo system.

Now some buying tips.

Your first concern is that the receiver that interests you will be compatible with the level of audio services you desire. Regardless of whether you want stereo or not, you do want clean program audio. It may be difficult to ascertain what is clean

and crisp if you are trying to listen to a two-inch speaker crammed into the side of a TV set. So ask to have the audio fed through a good sound system.

Now, how good is the audio system? Here are some benchmarks.

- Tune in transponder 6 on F3R (SPN/Satellite Program Network). Place the receiver in the narrow position and look for the next-to-highest subcarrier (7.695 MHz); it will be a "comedy channel" (famous comedians doing comedy routines). See if the audio is noisy. That service uses a very narrow bandwidth, and if the narrow position provides clean, crisp sound here, then the receiver should do a good job with all narrow-bandwidth signals.

- Tune in transponder 4 or 24 on Galaxy 1 (The Disney Channel). If the receiver is stereo capable, set it for mono, and select a wide bandwidth. Now tune in the audio at 6.8 MHz. Check to see if the audio is "muddy" sounding. That audio channel uses a very wide bandwidth and if the audio is crisp and not muted, that receiver should have no problem with most wide bandwidth audio signals.

Perhaps more so than the video sections, the audio sections vary widely in performance between different receiver models and brands. There is a possible alternate solution if you fall in love with a receiver that has great video but not all of the audio features you would like (not all receiver designers have hopped on the "tune-every-audio service" bandwagon yet).

Stand-alone audio subcarrier tuners are available from a number of sources.

Those allow you to treat the audio independent of the video. Again they, like the TVRO receivers with built-in audio tuning controls, should be compared as we previously suggested, since the mere fact that it is a stand-alone audio subcarrier tuner is no guarantee that the designer has allowed for the proper blend of audio bandwidths in use.

Avoiding hype

When home TVRO systems first came into the marketplace, all dishes were large, all dishes moved by hand (if at all), and everything cost a great deal of money. Today, fully 70% of the LNA's, 60% of the receiver's, 20% of the motor drives, and 10% of the dishes are created outside of North America. And the percentage of products being manufactured off shore has been getting larger by the month.

Panasonic and Uniden have been recent non-U.S. entrants into the marketplace. Numerous U.S. firms, although still branding their products as "U.S.-made," now are having assembly done in Korea, Taiwan, Hong Kong, or even Mexico. Even Europe is in the North American TVRO act (Luxor from Sweden). With nearly 500,000 home systems sold during 1984 and up to 750,000 home systems forecast for 1985, the market has become large enough to attract many of the better known volume producers.

It is, however, a marketplace that exists almost exclusively within North America and the surrounding areas (where US and Canadian satellites can be received). That is not likely to change in the foreseeable future since North America utilizes certain satellite frequencies and those satellites provide certain services that exist no place else in the world in the same format.

If you are reading this overseas, the first bit of hype to avoid is that you can buy a satellite dish and watch HBO in Ghana, Singapore, etc. The world of international satellite reception is an entirely different subject from that addressed here, and the \$500 to \$8000 systems we have discussed won't even dent the requirements you will face outside of North America or the Caribbean.

The next bit of hype to avoid deals with signal scrambling. The present industry exists to some extent because with a home



STAND ALONE audio subcarrier tuners allow you to treat the audio separately from the video.

 


FIG. 4—THE DISH'S SIZE directly affects its beamwidth. As is shown here, the smaller diameter the dish, the larger the beamwidth. That can prove to be a problem for small diameter dishes if two-degree spacing is used. In that case, signals from adjacent satellites can be a source of interference.

TVRO you can tune in satellite program feeds from services such as HBO and Showtime. For many years those services have been open, or available to anyone with a TVRO. And for many years, there have been rumors and there has been speculation that some (or all) of those services will scramble.

Naturally if a substantial quantity of those 90 or so real TV channels did scramble, the desirability of owning a TVRO might change.

As you read this, at least HBO and Cinemax are virtually ready to turn on scrambling equipment. Showtime and The Movie Channel have announced they will also scramble. So, does that spell the end of TVRO?

Not at all. The programmers, if and when they scramble, are doing so because the home TVRO market is now reaching a point where the programmers can anticipate some new, additional revenues from TVRO's. They want to do business with TVRO system owners and after they scramble, there is every reason to expect that they will make their services available to you for a reasonable monthly fee; not unlike cable TV charges for the same services. So the hype that all signals will scramble (four out of 90 is hardly all) and TVRO's will be useless is just propaganda from ill-informed reporters.

The final bit of hype to avoid deals with

super-small systems using dishes in the four foot to less-than-seven foot category. We already know that small dishes have less gain, and even in Kansas (where signals are generally strongest) people still prefer 10-foot dishes. They also will have problems dealing with two-degree spacing. Let's see more about that.

Satellites, as we have seen, stretch across the sky in a belt over the equator. Each satellite is assigned an orbital slot by some agency (such as the FCC in the U.S.). The satellite stays within 35 miles of that slot at all times; if it wanders, its orbit is corrected via telemetry. That is important because if a satellite were to wander considerably, it would be difficult to track with a satellite dish, and its signals could interfere with those from an adjacent satellite.

In fact, it is because they are sufficiently apart in the sky that the whole system works at all, since they do use the same channels and we depend upon the directivity of our dish to look only at a single satellite at a time. That directivity is called the dish's beamwidth, and that beamwidth depends greatly on the diameter of the dish—the larger the dish's physical size, the narrower or smaller that beamwidth (see Fig. 4). So, small dishes have broad beamwidths and big dishes have narrow beamwidths.

Now to our problem. The FCC wants to

cram as many satellites into that portion of the sky set aside (by international agreement) for U.S. (and Canada/Mexico) use as possible. They want to move the satellites closer together, without causing interference between satellites to the users on the ground. At the present time, U.S. satellites are spaced 2.5 to 4 degrees apart in the Clark Orbit belt. The majority of the present satellites are at least 3 degrees from their neighbors, but the FCC warns us that within the next five years or so, they want to make all satellites uniformly 2 degrees apart.

The catch for small dish owners is that those dishes under 8 to 10 feet in diameter have no proven ability to still function properly when satellites get down to 2 degree spacing. And smaller dishes, 6 feet in size and down, will almost surely have very real problems. With those dishes, when you are pointed at the desired satellite, signals from other satellites on both sides, two degrees away, will certainly cause some amount of interference. Your satellite receiver, seeing both the desired signal and the non-desired signals will simply treat the non-desired signals as interference or noise. The bottom line will be less-than-perfect reception.

To be sure that your dish will still be useable when 2-degree spacing becomes the norm, our advice is to get a guarantee. Most responsible dish manufacturers will certify to you, in writing through the dealer, that their dish will function with two-degree satellite spacing.

Warranties and guarantees

Finally, we leave you with this observation. Early TVRO products were only as good as the local dealer's ability to cope with failures and to respond to the customer/user's plea for assistance. But, times are changing.


Well over 50% of all electronic units and perhaps an even greater percentage of dishes now carry manufacturer warranties. A 12-month original equipment manufacturer promise of performance or replacement statement is pretty standard these days, and some extend to two years and more.

Your bill of sale should make direct reference to the warranty/guarantee coverage and if the original equipment manufacturer provides his own printed statement, that document should become a part of your records—just in case.

The TVRO product area has become far more sophisticated, in both technology and business experience at the dealer level, in just the last 12 months. The industry is a rising star that many expect to continue to grow rapidly for the next five years or more. These may no longer be the pioneering days of yesteryear, but there is still plenty of excitement and challenge in finding the right equipment package for your own home.

R-E

Installing your TVRO

 

BOB COOPER, JR.* SATELLITE TV EDITOR

Take the guesswork out of TVRO installation with this step-by-step guide.

Part 2 LAST TIME, WE BEGAN to outline a model TVRO system. Let's continue by looking at one of the most obvious parts of a TVRO—the dish.

Assembly details vary from dish to dish. We are going to give you some guidelines; but out of necessity, they will be generic rather than specific. When assembling your own dish, follow the instructions supplied with the unit.

Most dishes assemble upside down, and work should be done on a flat surface. All pieces should fit and all bolts should slide through without your having to tug at parts, pry with heavy wedges, or (heaven forbid!) drill new holes for bolts. If you find something does not fit (i.e. holes do not line up), stop and stand back. Before you attack the stuck part with a pry bar or drill, see if perhaps you have misaligned some previously installed part that, in turn, results in the new part not aligning properly.

All name-brand dishes are now "gang drilled," which means that all of the holes are drilled at one time and in one opera-

tion. Workman error (misdrilling one hole) is virtually a thing of the past. Before you curse the manufacturer's quality control, check your own!

When assembling the dish superstructure, or in the case of fiberglass or solid metal surface dishes, don't wrench tighten any bolts until all pieces in the "pie" are in place. There is always a small amount of adjustment room in connecting segments together and if you start taking up that adjustment room by wrench tightening before you have all of the pieces in place, you may adjust yourself right out of the tolerances required to slide the last piece into place.

When you do tighten up the bolts with wrenches, follow a pattern. Do the inside (closest to the center or hub) bolts first, for example, and do the bolts opposite one another (across the hub or center) working around the dish (i.e. 12 o'clock and then 6 o'clock, 3 o'clock and then 9 o'clock, and so on). When all inner bolts are tight, then start over with the same pattern on the outer rings of bolts.


When the dish is completed, carefully

turn it over so that it faces up. That lets you sight across the dish from the near side to the far side to see if the two align precisely. Now move 90 degrees around the dish and sight across it again. If any of the sides appears to be out of alignment, there is a potential warp in the framework holding the dish. Find out why and fix it, because a warped dish will not work properly.

If your dish is of the screen-mesh variety, don't hesitate to use lots and lots of clips (attaching the mesh to the under support pieces). The clips do more than assure that the screen mesh won't blow away; they force the mesh down to the undercarriage and therein ensure that the surface will follow as closely as possible the desired parabolic curve.

Clips are seldom "fun" to install, and the tendency is to shortcut the job and install just enough to get by. That is a bad mistake, as performance of a screen-mesh dish depends upon forcing the surface into a near-parabolic curve; and that only happens when the mesh actually adapts to the parabolic curved undercarriage-support

*PUBLISHER, CSD MAGAZINE

 

USE PLENTY of clips! In many designs, the mesh surface adheres to supportive under structure only when lashed down with clips. If you use too few clips, the system will not perform to specifications.

pieces. Take an extra hour to put in lots and lots of clips and you will be properly rewarded with first-class pictures.

Get plenty of help to lift the dish onto the mount. If the dish gets away from you and falls, it will hit on an edge and bend or warp; probably permanently. If that happens, you'll be best off starting all over again.

The dish mount should include instructions for setting something called declination offset for your locale. That is a special adjustment, usually built into the rear of the arm protruding back from or away from the rear of the dish. It is very important if you want your dish to track the Clarke Orbit belt properly. You will need an inclinometer to set that offset adjustment. Most dish manuals have a chart that lists the declination offset amount for various states or areas.

The feed is that device that mounts on a pole out in front of the antenna. Its job is to gather the reflected signal and pass it on to the rest of the TVRO system. It needs to be adjusted properly if your system is to work. Some feeds allow only one adjust-



FEED-SUPPORT ARM places the feed and LNA (or LNB/LNC) at the focal point of the dish. The feed arm adjusts in and out to ensure precise setting for maximum signal.

ment by the installer; others allow several.

The most basic adjustment is setting the distance away from the dish. The dish manual will tell you the focal length, and that is the distance measured from the center plate of the dish, at the hub, to the edge of the feed that is nearest to the center of the dish. Use a rigid tape measure and slide the adjustable feed pole or pipe to reach that distance.

Another adjustment is the side-to-side centering. That, if available or required with your dish, ensures that the feed is looking squarely at the center of the dish, and therefore all around the dish surface equally.

If you want to make sure that the feed is properly centered (left and right, up and down), take a roll of string or long metal tape measure and measure the distance from the edge of the feed front to the rim of the dish at several points. The dish should be equal distance from the rim to the feed edge all the way around. Otherwise, the dish is warped and/or is somehow off center.

Tracking the dish

There are numerous techniques for locating your first satellite with your dish; once that's done, assuming everything is working properly, the dish should automatically track through the remaining satellites in the Clarke Orbit belt. The technique we would like to share with you is among the oldest, but it works very well.

Start by making sure your declination (offset) is properly adjusted. Now, using the chart you prepared that shows the elevation and azimuth headings for your location to the various satellites, select a satellite that is fairly low to your west, such as G1, F3R, or D4.

Take the elevation heading (15.1 degrees for F3R from Albany, New York for example) and hand-adjust the antenna's elevation (using the motor drive control if you have one) so that an inclinometer laid against the flat back on the dish reads 15 degrees. Now you have the dish set for one satellite's elevation.

Next, turn on the monitor or TV set (this assumes, of course, all of the electronics is now hooked up—we'll talk more about that later) and set the receiver to either scan (if a scanning feature is available) or a strong signal (such as transponder 7 on F3R, which is ESPN). Slowly rotate the dish on its pipe-stand mount toward the expected azimuth heading for F3R (246 degrees in Albany). With the dish already set at the proper elevation, you will "run across" F3R as you come up on the 246 degree heading. Stop there and temporarily lock down the bolts that tighten the dish-mount collar to the pipe-stand mount.

Now operate **only** the motor control or hand crank, and move the dish east. Place

the receiver in scan so that the receiver is changing channels automatically as the dish moves. As the dish's azimuth heading changes, the polar-mount mechanism will also cause the dish elevation to change, raising the dish higher and higher as it tracks to the east. That allows it to track the arc of the Clarke Satellite belt. (We have been assuming all along that you are using a polar mount; other types are available, but they are very difficult to adjust when moving from satellite to satellite.) Along the way, you will note flashes of signal as the dish tracks first past one satellite, then another. Stop when the dish is aimed at F4; transponder 7 (National Christian Network) on that satellite is also strong in most areas.

Now, adjust only the dish's mechanical elevation setting for best picture; do not touch the azimuth adjustment (i.e. don't spin the dish on the pipe mount by loosening the collar to pipe bolts). When you have peaked for best signal, operate the motor drive or hand crank and return to F3R.

Once you are back to that satellite, if the picture is no longer as good as it was when you first found it, adjust only the azimuth by carefully loosening the collar to pipe set bolts and nudging the antenna first one way and then the other. When you have the picture peaked, re-tighten the bolts in the following manner.

- Make each bolt finger tight.
- While watching the receiver signal-level meter (or if none is available, the TV screen, although that's a poor second choice), take a wrench and make one quarter turn on each of the collar tightening bolts in succession. Do not tighten one all the way and then move on to the next, since by doing so, you will slip or slide the collar on the pipe.
- Repeat the sequence, a quarter turn at a time, until all bolts are tight. Do not over-tighten; those bolts typically will break off if you use more than moderate wrench pressure.

Return to F4R and double check that it is still peaked. If necessary, re-touch its signal level by carefully adjusting the elevation adjustment. (If adjustment is needed, it is usually caused by an ill-threaded rod or turnbuckle.)

The feed system

The information on centering the feed aside, there is one adjustment required on the feed proper. That is the skew adjustment. Modern satellites (all but Westar 3 are modern by today's standards) transmit 24 channels of possible service. Twelve of those channels are transmitted using vertical polarization, and 12 using horizontal polarization. Polarization, of course, is the technique that makes it possible to cram 24 channels of programming into the frequency space allocated to 12. But that's not our concern here. (For more



ELEVATION is set on this antenna with turnbuckles.

information on that topic see "All About Satellite TV," in the June 1984 issue of **Radio-Electronics**.) Instead, we'll concentrate simply on how you install and properly adjust the feed.

The feed installs on a plate of some sort at the end of the feed arm or bracket. As we mentioned earlier, the length of that feed arm can be adjusted so that the feed is properly located. In addition, however, the arm (or in some cases, only the plate that the feed is mounted on) rotates. Let's see how that rotation is used to make the skew adjustment.

First of all, install the feed on the plate using the hardware provided. Adjust its distance to the center of the dish as described earlier. Once the system is operating on at least one satellite, tune in a signal. Note, using one of the many satellite TV guides (sometimes, one of those is even included with your dish) whether the transponder you are viewing is horizontally or vertically polarized. Going back to our old friend, F3R, transponder 7, we find that it is vertically polarized (on that satellite, odd-numbered transponders are vertically polarized; even-numbered ones horizontally polarized). Set the polarization control in your system for vertical. Examine the signal displayed on the monitor. Then switch to transponder 8, and re-examine the signal. If automatic polarization switching is built into receiver, the act of changing transponders should also have changed the polarization of the feed and you should have a good picture. If your receiver does not have automatic switching, you will have to set the polarity, via the appropriate control, for horizontal.

Unless you are extremely lucky, there is bound to be some evidence of the transponder 7 signal present. That may in-

clude drifting vertical lines, or even two video signals (the one from transponder 8 and a weaker one from transponder 7). If present, we obviously need to remove any sign of the vertically polarized transponder 7 signal. (If you have a receiver with automatic polarity switching, the first step is to temporarily disconnect the polarity control lines between the receiver and the LNB—simply unplug them from the back of the receiver.) To do that, mechanically rotate the feed support arm a touch until any signs of the adjacent transponder disappear. Now, switch back to transponder 7, but *leave the polarity control set for horizontal*. Once again, rotate the feed, if necessary, to make all signs of the vertically polarized transponder 7 signal disappear. Once that's done, tighten the bolts that lock the feed-support arm in place.

The electronics

Everything we have discussed up to this point applies to any type of TVRO system you might install. The rules are the same for LNA/downconverter, LNB, or LNC systems. The type of system you select will, however, affect what follows.

As we feel that block downconversion (BDC) offers some significant advantages, such as the ability to have multiple receivers without restricting the choice of viewing to a single transponder, we will outline a system that uses that technology. A BDC system consists of the following:

- Some form of signal amplification at the feed (LNA, LNB).
- Some form of frequency downconversion. If you use an LNA, you will need a separate block downconverter. If you use an LNB, the downconverter and LNA are in a single package.
- Cabling from the LNA/downconverter or LNB to the receiver
- Signal splitters that will allow you to route the satellite signals to multiple receivers (if your system calls for that).

The job of the block downconverter is to convert the satellite's 3.7- to 4.2 GHz signals to some lower band of frequencies. Among other things, that allows the connection between the dish and the receiver to be made using common coax, rather than special high-frequency (and very high cost) cable. The output frequencies of a block downconverter varies by manufacturer, and range from 270- to-770-MHz to 1140-to-1640-MHz, but all have one thing in common: They all use a 500-MHz band of frequencies, such as 450 to 950 MHz. That is because, in the block downconversion systems, all signals in the 500-MHz input band ($4.2 \text{ GHz} - 3.7 \text{ GHz} = .5 \text{ GHz} = 500 \text{ MHz}$) are output to the receiver. Thus, the output band is a faithful reproduction of the input band, only lower in frequency.

Even though the output of the downconverter is much lower in frequency than the input, it is still high enough for line

loss to become a significant problem, especially at the high end of the range of output-frequency bands used. The trick, then, is to ensure that each receiver in the home system receives adequate signal strength from the block downconverter. That factor must be considered when planning out your system. Also, in a multiple-receiver setup, the individual receiver locations should be isolated from one another to ensure that there is no unwanted interaction between those units.

Neither problem is really anything unique to satellite TV. They've all been faced and solved by CATV and MATV operators.

There is, however, an important difference. In setting up a home distribution system for satellite TV, we cannot simply march into our local parts supplier (such as Radio Shack) or a local CATV supply house, and purchase the components we need. That's because the frequencies used in satellite TV are generally higher than those used for cable or broadcast TV. Thus, since the signal splitters, taps, and so on, generally available from the above mentioned sources, are designed for use at lower frequencies, they will work poorly, or not at all, for our application. Fortunately, appropriate equipment, intended specifically for satellite-TV applications, is made by several manufacturers, and should be available from your installer or dealer.

Loss and gain

Receivers in a satellite system are categorized as masters and slaves. The difference is that the master receiver, which should be located where there is the most TV traffic, controls certain functions for the entire system, such as satellite selection and polarization selection.

Power for the LNB (or LNA and block downconverter) comes from the master receiver and is usually supplied via the same coaxial cable that carries the output from the downconverter indoors.

In satellite TV "lingo" the downconverter is labeled the *headend*, or more simply, the point where the signals originate. The downconverter has some output level, specified in dBmV, where 0 dBmV is 1 millivolt (measured across a 75-ohm coaxial cable). A typical signal level from a block downconverter is +10 dBmV.

That +10dBmV signal has to be shared between each of the receiver locations. (The typical satellite receiver requires a minimum input signal level of 0 dBmV.) There are two approaches to that. For larger systems, a tapped trunk approach, similar to that used by cable companies is the best route to go. For a relatively small system (4 or fewer receiver locations), as shown in Fig. 4, the splitter approach is recommended, since it makes slightly better use of the available signal levels. In

Fig. 4, we show a system with two receiver locations on the ground floor, and two receiver locations on the second floor. The connection from the downconverter to the house is made using a single length of RG-6/U. At the entry to the house, we have a two-way splitter; between the downconverter and the splitter we also have a line amplifier, but let's ignore that for now. The splitter splits the signal into two "legs". One of those legs, as we said before, feeds the two downstairs receivers. To do that, the signal is fed to a second two-way splitter. One output from that splitter feeds the master receiver, while the other goes to the first-floor slave. (Note that the control signals and power are fed from the master receiver to the LNA/downconverter.) Meanwhile, the second leg is once again fed to a two-way splitter whose outputs are used to feed two upstairs slave receivers.

While we've just outlined what looks to be a very efficient small distribution system, can we be sure that it will work as intended? To answer that, we have to keep some points in mind.

- The downconverter output is approximately +10dBmV (though that can vary, so check the manufacturer's specifications for your unit).
- The minimum acceptable input level at each receiver is 0dBmV.

From the above, it appears we can sustain about 10dB of loss before we run into problems. That loss will come from two sources: the splitters and the cable. Turning first to the splitters, there are two between each receiver and the downconverter. The typical two-way splitter has 4.0dB of "loss." (Actually, only about 1 dB is really lost, the balance of the 4 dB is simply the signal being split into two parts.) So before we even consider cable losses, we have 8dB of loss. Now, what about those cable losses?

The cable losses will be considerable. Just how much will depend upon what frequencies are output by the downconverter. Remember that various receiver manufacturers offer different output-frequency ranges. And the top end or highest frequency in the range will have the greatest loss. Table 3 shows the typical losses for RG-6/U and RG-59/U coax at various typical "high-end" frequencies.

Note that the values given in Table 3 are only typical, and will vary (sometimes greatly) with the grade and manufacturer. It is important to understand that neither RG-6/U nor RG-59/U are really intended for use much above 900 MHz (try to locate manufacturer specifications above 900 MHz and you will quickly agree!) so the cheaper grades of RG-59/U "TV-hook-up cable" sold prepackaged by many of the national chain stores are apt to suffer far greater losses (per 100 feet) than what is quoted here. Our best advice is to stick to quality cables from manufacturers who

 


FIG. 4—A FOUR-RECEIVER SYSTEM. Use of the line amplifier ensures that signal levels will be sufficient to overcome any line loss or the loss caused by the splitters.

TABLE 3—CABLE LOSS

Top end frequency	Cable type	Loss per 100-feet
770 MHz	RG-6/U	6.0 dB
770 MHz	RG-59/U	7.5 dB
950 MHz	RG-6/U	7.0 dB
950 MHz	RG-59/U	8.8 dB
1450 MHz	RG-6/U	9.5 dB
1450 MHz	RG-59/U	11.0 dB
1640 MHz	RG-6/U	10.1 dB
1640 MHz	RG-59/U	12.0 dB

will supply you with guaranteed loss-per-100 foot characteristics.

So, if we have lost 8dB of signal in our two splitters—and we can only lose 10 dB before we have a signal-level problem, it would appear we have 2dB left to lose in the cable. If our system uses a downconverter with an IF output of 950–1450, that means that we only can use about 21 feet of RG-6/U cable (total) for our hookup if we are to have satisfactory results at the high end of the band.

It is unlikely that we can reach all four sets in this system with no more than 21 feet of cable between the downconverter and the most distant TV receiver location. The solution is to use an amplifier.

As with the splitters we looked at earlier, line amplifiers intended for cable service often do not operate well at the frequencies output by satellite-TV downconverters, especially the higher frequencies. Fortunately there are a number of manufacturers that offer equipment specially intended for satellite-TV service.

Satellite-TV amplifiers typically have gains of 20dB, with a slope of 2 or 3 dB. For those unfamiliar with it, let's explain what is meant by slope. Remember that

cable losses increase with frequency. A length of RG-6/U, for example, may have 9.5dB of loss at 1450 MHz, but it will have only 7.0dB of loss at 950 MHz. That's a 2.5dB differential, and the object of our system is to maintain not only a minimum of 0dBmV to each receiver, but to also attempt to keep the level "balanced" (i.e. the same) at the input to each receiver and on each channel. A "sloped amplifier" has 2 to 3 dB more gain at 1450 MHz than it does at 950 MHz. That sloped gain acts to compensate for the expected additional cable losses at the higher frequencies.

In summary, many of the original problems of TVRO reception have been eliminated by newer equipment designs. Everything about TVRO equipment has become more consumer/user "friendly" in the past 18 months, and the industry is rapidly approaching a "mature" design level from which innovation will switch to product efficiencies rather than product features. Most equipment now arrives on your doorstep with reasonably adequate installation instruction manuals, and most equipment now carries at least a one-year OEM warranty. **R-E**

BUILD THIS

Digital Tach/Dwell Meter

Tune up your car for peak performance with this easy-to-build digital dwell/tachometer.

DAVID DEMERS

HAVE YOU BEEN SHYING AWAY FROM TUNING up your car because of the difficulty of making such measurements as dwell angle and engine rpm? If so, your car may not be running at its best. And even though gasoline prices have come down in recent months, you can still waste a tremendous amount of money by driving a car that is improperly tuned up.

Tuning up your car does not have to be difficult. You can start by building this digital dwell/tachometer that will make measuring your engine's idle speed and dwell angle nothing short of simple.

Handheld dwell/tachometers have been available at a reasonable cost for some time now. But those devices use analog meter movements. The meter we'll build uses a digital readout. It's not only more accurate; it's easier to use because there's no meter scale to interpret and no parallax error to worry about. That's important when you're crouching under the hood.

The tach/dwell meter

Those of you who are not familiar with the operation of your car may be wondering what a dwell/tachometer is used for. Well, the combination tachometer and dwell meter is one of the most common and useful test instruments for engine maintenance. As its name suggests, it measures two important parameters: engine speed (in revolutions per minute or rpm's) and the dwell angle (in degrees) by monitoring the voltage across the breaker points.

For those of you unfamiliar with how a car's ignition system works, we'll give a simplified explanation of the dwell angle. In a standard ignition system, the spark plugs fire when the breaker points open and interrupt the current flowing in the ignition coil. That causes the coil's magnetic field to collapse, producing the high voltage necessary in the coil's secondary to fire the plugs. The breaker points are

opened by a cam in the distributor. The angle through which the distributor rotates with the points closed is the dwell angle. An electronic ignition operates differently, but with the same results.

The waveform of the voltage across the breaker points is shown in Fig. 1. The ringing at the leading edge of the pulses is due to the collapsing magnetic field of the coil. The number of the pulses in a given unit of time is directly related to the rpm of the engine.

The meter we will build can measure engine speed in two ranges: TACH 2 or RPM $\times 10$ has a range of 0-999 and TACH 1 or RPM $\times 100$ has a range of 0-9999 rpm. The dwell meter has a range of 0-99.9 degrees to check the setting of the breaker points (or the corresponding circuits of an electronic ignition).

 


FIG. 1—TYPICAL VOLTAGE WAVEFORM of breaker points.



Measuring engine rpm

The schematic of the tach/dwell meter is shown in Fig. 2. The heart of the circuit is IC2, a 4046 micropower phase-locked loop or PLL. The incoming signals are fed to the PLL after being buffered by IC1-a and its associated components. The frequency of the incoming signal is multiplied by either 90, 60, or 45, depending on the setting of the CYLINDER SELECT switch, S2. That switch selects the proper output from counters IC3 and IC4, which are set to divide the output frequency of the PLL by those amounts, and then send the divided output back to the comparator to the PLL to keep it "locked on" to the input signal.

The PHASE PULSES output at pin 4 of IC2, the 4046 PLL, then go through an AND gate IC5-d (which only passes the signals if the PLL is locked on to an input signal, preventing stray readings), and then to the input of IC6.

When in the TACH mode, IC6—a 14553 3-decade, multiplexed-output counter—counts the number of pulses present at pin 12, during the timing interval generated by IC8 and the associated circuitry of IC1-b. Because of the varied multiplication rate for the different cylinder selections (90, 60, and 45 for 4, 6, and 8 cylinders,

 


FIG. 2—DWELL/TACHOMETER SCHEMATIC. As shown, the meter is set for 4 cylinders, low tach range. Because the TL092 op-amp that the author used is very hard to find, you might want to substitute National Semiconductor's LM358 for IC1.

 


FIG. 3—THE AUTHOR'S PROTOTYPE shown with the cover removed. Note that the display is simply glued to the front panel.

respectively), the time interval is always constant at 1/3 of a second. That is adjusted with R9, a 500K potentiometer; it is the only adjustment in the circuit.

In the high-tach (TACH 1 or $\times 100$) range of 0-9990 rpm, the output of IC2 (the 4046 PLL) is routed by switches S1-a and S3 through IC7, a divide-by-ten counter, which increases the count range tenfold. In the low tach (TACH 2 or $\times 10$) range of 0-999 rpm, that counter is bypassed.

Measuring dwell angle

In the DWELL mode, the operation of the circuit is a little trickier. The maximum dwell (which is measured in degrees) is determined by the number of cylinders. For a four-cylinder engine, the maximum dwell is 90 degrees, for a six-cylinder, 60, and for an eight-cylinder, 45 degrees. You will recall that those maximums are also the amounts by which the frequency of the incoming signal is being multiplied. The multiplied signal is applied to pin 12 of IC6, the three-digit counter.

In order to measure the dwell, it is necessary to count only during the time that

 


FIG. 4—PARTS PLACEMENT PATTERN for the dwell/tachometer. The PC board pattern is shown in our new "PC Service" department.

 


FIG. 5—THE OFF-BOARD CONNECTIONS are shown in this separate diagram.

the points are closed. Thus, if the points were almost always closed, the reading would approach the value of the multiplication factor of the input signal, which is the maximum reading possible. A signal from IC1-a is applied to the DISABLE pin of IC6 (pin 11), which halts the count when the point voltage is high (when the points are open).

The reading's accuracy is increased by averaging the count over ten cycles. That is accomplished by using IC7 to divide the output of IC1-a by ten. The output of IC7 is fed to the DISABLE pin of IC6.

Building the dwell/tachometer

Construction of the unit, which is shown in Fig. 3, is relatively easy if you are familiar with printed circuit board techniques. A suitable pattern appears in our special "PC Service" section on page 67. Using that pattern, you can directly etch the board from the magazine page! An etched board is also available from the source mentioned in the Parts List.

A parts-placement diagram is shown in Fig. 4. The circuit is simple enough so that it can be built using breadboard or wire-wrap techniques, if you are careful.

PARTS LIST

All resistors are 1/4 watt, 5% unless otherwise indicated

R1, R24, R25, R26—1000 ohms
 R2, R3, R6, R11—10,000 ohms
 R4, R7, R8—100,000 ohms
 R5—1800 ohms
 R9—500,000 ohms potentiometer
 R10—15,000 ohms
 R12, R16—R23—470 ohms
 R13—220,000 ohms
 R14—62,000 ohms
 R15—150 ohms

Capacitors:

C1, C2, C9—.001 μ F ceramic disc
 C3—470 pF ceramic disc
 C4—15 μ F, 16 volts, tantalum
 C5, C7, C8—.1 μ F ceramic disc
 C6—1 μ F, 16 volts, electrolytic
 C10, C11—10 μ F, 16 volts electrolytic

Semiconductors

D1, D2—9.1 volt Zener
 D3, D4, D5—1N914
 LED1—standard red LED
 Q1, Q2, Q3—2N3906
 Q4—2N3904
 IC1—TL092 op-amp
 IC2—4046 micropower PLL
 IC3—4017 decade counter
 IC4—4518 dual BCD up counter
 IC5—4081 quad AND gate
 IC6—14553 three-digit BCD counter
 IC7—4518 dual BCD up counter
 IC8—7555 low power timer
 IC9—4511 BCD-to-seven segment latch/decoder/driver

Other Components

DISP—NSB7881 4 digit, common-cathode, multiplexed display (National)
 S1—four pole, 2-position
 S2—one pole, 3-position
 S3—SPDT toggle

Miscellaneous:

PC board, IC sockets, switch knobs, etc.

A printed-circuit board is available from E²VSI, PO Box 72100, Roselle, IL 60172, for \$15.00 postpaid.

If you do use a PC board, mount the IC sockets first, followed by the resistors, capacitors, and other components. Then the eight jumpers may be added. Next, you have to wire the off-board components such as the display and the switches. Because there are so many off-board connections, a separate off-board diagram is shown in Fig. 5. The display wiring should be relatively easy as long as you follow the schematic and parts-placement diagrams. Just make sure that you keep the wires to the proper length for your cabinet. In wiring the switches, everything is straightforward except that the pole of S2 has two points on the board to be connected to. One is at pin 2 of IC5, the other at pin 3 of IC2.

continued on page 82

HOW TO

Servicing Cordless Telephones

A cordless telephone, like any other piece of electronic equipment, is bound to break down sooner or later. This article will show you how to troubleshoot and repair the problem.

CHRISTOPHER KITE

Part 3 THIS MONTH, WE TURN our attention to troubleshooting the base unit. Figure 2, a block diagram of a cordless phone, has been repeated to aid in our discussions.

Usually the base-unit receiver consists of several stages; an RF amplifier, first IF (first mixer, local oscillator, and IF filter), and second IF stage (second mixer, local oscillator, IF filter, and detector). First, check the local oscillators for activity; if they fail to oscillate, they are defective

and are probably the cause of the problem. After the local oscillators have been verified as operational, check the output of each stage. An RF probe connected to a multimeter is a convenient method of making those measurements.

The next step is to check that the pilot-signal detector is detecting the signal and causing the telephone to go off-hook. If the pilot signal (guardtone) is being detected, a signal should be sent to the relay driver to cause the telephone to go off-

hook. If the pilot signal is not being detected, vary the frequency of the guardtone signal to make sure that the pilot-signal detector is not set up to receive a different frequency guardtone. If the pilot-signal detector detects a different frequency from the one that was originally selected, adjust the pilot-signal detector in the portable to detect the pilot signal being produced by the pilot-signal generator in the base unit (see Fig. 9). Though it is possible to do that the other way



around, the results are usually less satisfactory.

If the pilot-signal detector is operating, the problem is either in the relay driver or the relay. Check that the output of the relay driver is sending a signal to the relay to cause it to switch to an off-hook state. If it is, the relay is defective. If it isn't, the relay driver is defective.

Dialing problems

If a pulse-dial cordless telephone fails to produce any digits at the dialed number decoder, the dialing IC is probably defective. Most pulse-dial cordless telephones have a dialing IC that turns the pilot signal generator on and off. That causes the base unit to switch on and off-hook and pulses the telephone line. Because all the other circuits were operational in the previous test, the dialing IC is essentially the only component that could be defective. That can be verified by checking dial pulsing in the portable unit with an oscilloscope.

If incorrect digits appear at the decoder, the base-unit relay is probably defective. Even though the relay operated properly for the ring test and dial-tone test, it is possible that it is causing the cordless telephone to dial the wrong digits. If the relay spring loses some of its tension or the relay becomes "sticky," the duty cycle of the pulses is changed and telephone company equipment sees the wrong digits. Replacing the relay will solve that dialing problem.

As with pulse-dial cordless telephones, the components that could possibly cause tone-dialing failure are very limited. The first step is to check the output of the crystal used in generating the DTMF tones. Use an oscilloscope to insure that the crystal is oscillating. If the crystal is oscillating, you should check the output of dialing IC. If the crystal is not operating, it should be replaced.

The dialing IC should output the proper tone (frequency) pairs for each digit. If it doesn't, it should be replaced. If both the dialing IC and crystal are operating, then

TABLE 2—DTMF FREQUENCIES

Digit or Symbol	Frequencies (Hz)
1	697 & 1209
2	697 & 1336
3	697 & 1477
4	770 & 1209
5	770 & 1336
6	770 & 1477
7	852 & 1209
8	852 & 1336
9	852 & 1477
0	941 & 1336
.	941 & 1209
#	941 & 1477

 


FIG. 2—HOW A CORDLESS TELEPHONE WORKS. A block diagram of a portable unit is shown in a, while the block diagram of the base unit is shown in b.

 


FIG. 9—IF THE PILOT SIGNAL generated by the portable can not be detected by the base, the detector circuits in the base are the ones that should be adjusted.

there must be attenuation somewhere in the signal path that is causing the tone level to be so low that it cannot be recognized. Table 2 shows the proper frequencies for the tone pairs for each digit.

If the portable unit proves to be operating properly, the problem is in the base unit. The two most common problems are distortion caused by the detector circuit, or improper tone-level adjustment. Mea-

sure the level of the dialing tones with an AC voltmeter. If the tones do not produce an amplitude of at least 0.25 volt, the problem is probably caused by an improper level adjustment. Check the service manual for your cordless telephone and find the level-adjustment potentiometer. Adjust it for correct tone level. If the level is correct, the problem is most likely distortion caused by the detector circuit. Connect an oscilloscope to the output of a demodulator circuit and check the signal for distortion. If distortion is present, the detector circuits in the cordless telephone are defective.

Poor voice level

The first step in troubleshooting why the voice level is insufficient is to check the portable unit. Use an audio generator to inject an audio tone into the microphone circuit of the portable unit. Trace the signal through the circuitry with an AC voltmeter. Check that there is a signal being fed to the audio-amp-and-gate. The audio-amp-and-gate should feed the amplified voice signal to the transmitter were

it is used to modulate the carrier signal. If the voice signal is being fed to the transmitter, but the demodulated RF signal has no audio present, there is probably a broken connection between the audio-amp-and-gate and the transmitter.

If the portable unit is operating properly, the next step is to check the base unit. At the base unit, the receiver demodulates the RF carrier and outputs the guardtone and voice-audio signals. The low-pass filter should output the voice audio and feed it to the hybrid transformer. The hybrid transformer should feed the signal out to the telephone line and back to the transmitter (the level of the signal fed to the telephone line should be much higher than the level of the signal fed to the transmitter) where it is sent to the portable unit as sidetone. Any problem must lie in the low-pass filter, the hybrid transformer, or the connection between the two because all other components involved have previously been tested.

Low sidetone level

Because the sidetone is fed to the portable unit from the base unit, the only likely cause of very low or nonexistent sidetone would be the failure of the hybrid transformer in the base unit. Because all other circuits involved have been tested previously, that is the only problem with sidetone that we are likely to see. Check the modulation level of the base transmitter with voice or audio tones applied. Less than 3-kHz deviation at normal voice peak-level indicates a problem in the hybrid transformer.

Poor voice quality

If the voice quality of the cordless telephone proves to be unacceptable, the problem could lie in either the portable or base unit. Connect an oscilloscope to the telephone line simulator. Inject a low-distortion sinewave at the portable-unit microphone. If distortion is evident on the scope, use the oscilloscope to examine the audio circuits of the portable-unit microphone circuit, and the base-unit receiver discriminator and audio circuit. If no distortion is present at the telephone line simulator, check the hybrid transformer in the base unit's transmitter, then the discriminator and speaker circuits of the portable unit's receiver.

Troubleshooting poor performance

When we talk about a cordless telephone performing poorly, we are usually referring to range problems. There are several things to consider when trying to diagnose range problems. Many of us think only of RF power when we try to correct a range problem, but there are, in fact, several reasons that the range of a cordless telephone might not be up to specifications. Just as low RF-power might affect range, receiver sensitivity

could also be the cause. An additional cause might be an offset ring-signal frequency. Range is also affected by the amount of shielding in the building and the effectiveness of the AC wiring as a 1.7-MHz antenna. Also to be considered is the fact that poor range could be caused by the base-unit transmitter, portable-unit transmitter, base-unit receiver, or portable-unit receiver (or any combination).

The most common problems causing reduced range are low RF-power and low receiver-sensitivity. Fortunately, those are also the easiest parameters to check.

When we tested the cordless telephone for ringing and dial tone, we measured the relative RF-power. As stated then, level readings for transmitters should be around 4 volts for most cordless telephones (some of the short range telephones have much lower output voltages, check the service manual for the telephone you are servicing). If the output voltage is not up to specifications, adjust the output of the weak transmitter.

Testing the sensitivity of a cordless telephone receiver is like testing the sensitivity of any radio receiver. Experience with similar type cordless telephones will quickly establish normal reference levels for each type. If the receiver does not operate acceptably, we must go through the receiver section and check for transistors that are not amplifying sufficiently or unwanted attenuation. Usually the problem will be caused by a defective transistor. If that is the case, replacing the transistor should cure the problem.

The ring signal can become offset and affect the range of the cordless telephone. It is important that the ring-signal frequency match the frequency of the ring-signal detector. Use a frequency counter connected to a demodulator circuit to measure the ring-signal frequency error of the base unit's transmitter. If the frequency is off just a slight amount, it could cause the range of the cordless telephone to become dramatically shorter. Ring-signal frequency error can also cause other operational difficulties and the ring-signal generator should be adjusted whenever an error is noticed.

Testing digitally-coded phones

When testing digitally-coded telephones, it is important that you consult the service manual for the telephone under test. Digital-coding techniques vary greatly from one manufacturer to another and even from one model to another.

Some digitally-coded telephones establish a "handshake" before voice communication is possible. With one popular scheme, the 1's and 0's of the digital code are created by shifting the RF carrier between two frequencies. The digital code is decoded by the base unit's receiver, which turns on the base unit's transmitter and encoder, and sends a code back to the

portable unit. Lastly, the portable unit's receiver decodes the returned digital message and completes the handshake by shutting off the encoder and enabling the voice circuits. The problem with troubleshooting that closed-loop system is that almost any problem, either RF or digital, will prevent the handshake from being completed. When the handshake is not completed after a few tries, the system shuts down, preventing RF testing.

With such phones, it is best to bypass the digital code (using jumper connections that are listed in the cordless telephone service manual) and test the base unit without the use of the coding. That permits testing of the RF and audio functions. Generally, if the unit works when the code is bypassed, the coding or decoding circuitry is faulty. Several things must be kept in mind when testing with that method, however. Some digitally-coded phones use no guardtone or ring signal; they send a digital code for ringing and a digital code to signal the base unit to go off-hook. That means that causing the portable unit to ring without using the base unit is very difficult. The rest of the circuitry can be tested however; if all is OK, the problem lies in the ring circuits.

Fortunately, most portable-unit transmitters can be activated and checked just by setting the portable unit to TALK. Usually it will be possible to view the digital code on an oscilloscope connected to a demodulator circuit. Most manufacturers seem to use a scheme that involves generating the digital code at the beginning of transmission. When using an oscilloscope, you probably won't be able to decipher the code. However, you can verify that the digital code is actually modulating the carrier. Chances are, if a code is being transmitted, the encoding circuits are OK. That means that the fault is probably in the decoding portion.

It is also possible with some units to use the portable unit to capture the base unit then turn off the power on the portable unit and maintain the link to the base unit with an RF generator. Use the power switch, rather than returning on-hook, so that the disconnect code is not sent.

Some cordless telephones have built-in systems for testing the phone. One such method involves setting all the digital-code selection switches to the ON position. That disables certain signals or tones that are generated for calling the user's attention to a problem.

Another method of testing the base-unit transmitter (if jumper connections are not listed in the service manual) is to activate the base unit's transmitter by applying a ring voltage to the telephone line. If the base unit's transmitter is operating and generating a ring code, the portable unit's receiver can be checked by monitoring the discriminator output or the CODE IN input to the digital encoder/decoder IC. **R-E**

ULTRASONIC PEST-REPELLERS


ROBERT F. SCOTT

OVER THE YEARS, THERE HAVE BEEN many articles published that proclaimed that ultrasonics, either in the form of pulses or a sweep signal, can be used as an effective insect and rodent repellent. I've always been skeptical of such claims and placed them in the same category with those electronic devices claimed to prevent swallows from nesting on the courthouse roof and prevent pigeons from defiling the Stonewall Jackson statue on the town square. Nevertheless, I filed those articles away for investigation sometime in the future.

Last summer, my hunting and fishing club took possession of a farmhouse that had been abruptly abandoned about a year ago. The house was absolutely overrun with mice and roaches that were bold enough to scamper about in full daylight. We were at a loss as to how to get rid of them.

Ultrasonic pest repellents had begun to appear in mail-order advertising and our club president suggested that we try one. Those devices, according to the literature, generate a signal that sweeps over a frequency range of approximately 22 kHz to 65 kHz, develop sound pressures ranging from 115 to 152 dB, and repel pests in areas of 2500 to 3500 square feet. Power consumption is typically 2 to 4 watts. Prices range from \$30.00 to \$70.00, plus shipping.

At first, I scoffed at the suggestion that we purchase an ultrasonic pest repeller, but agreed to try one since they were available for a 30-day trial and full refund. The \$30.00 model was available from several sources under names that include Pest Control, Pest-Elim 1500, and Westronix. We ordered one and it came within a few days. It was shipped in a plain unmarked carton and we were surprised to find that it did not carry a trade name or model number. We installed it in the clubhouse. Within two weeks, mice and roaches were nowhere to be seen—even when lights were suddenly turned on in a dark room. Now, we consider the clubhouse completely free of pests. Not a sign of them; even in the darkest corners and crannies.

 

The claims made for those ultrasonic pest repellents seem fantastic at first glance—but they really work. In this article, we'll find out what makes those devices "tick".

Now that the pest repeller had done its work, I began to speculate on its circuit. An early article on the use of ultrasonics in insect and rodent control ("Electronic Pest Control", by Lyman Greenlee, *Popular Electronics*, July 1972) indicated that the repeller needed a power amplifier de-

livering 16–20 watts in the ultrasonic region and special high-power tweeters. Certainly that little plastic box didn't contain a 20-watt power amplifier or high-power tweeters. Also, a 16–20-watt power amplifier drawing only 4 watts from a supply would be about as close to "per-

 


FIG. 1—SCHEMATIC DIAGRAM of a popular ultrasonic pest repeller. Despite its simplicity, the device was remarkable effective.

 


FIG. 2—THIS PEST REPELLER, of French design, is built around a CD4011 quad NAND gate. The schematic diagram is shown in a; a block diagram of the IC is shown in b.

 


FIG. 3—THIS CIRCUIT IS ideal for experimenting with ultrasonic signals. It can supply either a pulsed or continuous output.

petual motion" as one can come. Thus, I couldn't wait to pry open the repeller's $6\frac{1}{4} \times 4\frac{1}{4} \times 1\frac{1}{4}$ -inch plastic case and see what made it "tick".

Figure 1 is the circuit of the device we tested. We were quite surprised to find that the circuit was simply a 555 timer IC connected as a squarewave generator. Its base frequency is approximately 45 kHz, as determined by the values of R1, R2, and C1.

The 45-kHz "carrier" is frequency modulated by a modified trapezoidal voltage waveform applied to pin 5 of the 555 timer. That modulating voltage is developed by a network consisting of C2, R3, and R4 connected across one leg of the bridge rectifier. A check with an oscilloscope showed a sweep of approximately 20 kHz on each side of the base

frequency. That sweep of from 25 kHz to 65 kHz is surprisingly close to the 22–65-kHz range specified in the ads. The speaker is a 2 inch piezoelectric tweeter.

How the French do it

The circuit in Fig. 2 is a pest repeller described in the French electronics magazine, *Le Haut Parleur*. In the article, the author claims that frequencies in the range of 20 to 40 kHz cause highly uncomfortable cavities to form in brain fluids and blood vessels of mice and insects, causing them to beat a hasty retreat. Radiated power levels can be as low as $\frac{1}{3}$ watt.

Looking more closely at the circuit, a quad two-input NAND gate is connected as multivibrator operating at around 40 kHz. With the minimum of filtering used in the power supply, a residual 120-Hz sawtooth

on the line from the power supply modulates the ultrasonic frequency. Two Darlington-connected NPN transistors provide some power amplification and drive for the speaker.

Circuit for experimenters

If you want to experiment with the effects of continuous or pulsed high-frequency signals, the circuit in Fig. 3 is ideal; it can provide either a continuous or pulsed output. It was developed by Signetics and described in *Electronic Products Magazine*.

Looking at the circuit, one 555 timer, IC2, generates the ultrasonic squarewave at a recommended 20 kHz. That signal can be supplied continuously or pulsed on and off by a second 555, IC1.

Experimenting with frequency and duty cycle is easy. Duty cycle is the "on" time compared to the total period, and can be set from slightly above 50% to almost 100%. In the astable multivibrator circuit, the duty cycle is set by the timing resistors, R_{T1} and R_{T2} , and is equal to $R_{T1} + (R_{T2}/R_{T1}) + 2R_{T2}$.

The on time is close to 100% when R_{T1} is chosen to be as small as practical while limiting the current through the discharge transistor to the maximum specified in the data sheet. (The discharge transistor, which is on-board the 555, is an open-collector NPN device with the collector going to pin 7 and the emitter to ground at pin 1. The maximum current through it varies with different manufacturers so you should check the maker's data sheet to be sure.)

If you want a duty cycle of less than 50%, connect a general-purpose silicon diode such as the 1N914 across R_{T2} with its anode at pin 7 and cathode at pin 6. That effectively shorts R_{T2} while timing capacitor C_T is charging, and the duty cycle is now $(R_{T2}/R_{T1}) + R_{T2}$ and it can be varied from around 0 to nearly 100%. The frequency of the squarewave generator can be found from $1.44/C_T(R_{T1} + 2R_{T2})$, where resistance is in megohms and capacitance in microfarads.

If you want to vary the duty cycle of the oscillator while keeping the frequency constant, use the basic circuit shown in Fig. 4.

In that circuit, a single potentiometer is used for the two timing resistors. In that scheme, it is possible to set the value of one of the two "timing resistors" to zero. As that is undesirable, two resistors, R1 and R2, have been added to set minimum values for those timing resistors.

Use the basic circuit shown in Fig. 5 when you want to vary frequency while keeping the duty cycle constant at approximately 50%. The variable element used in that circuit, R_{T-a} and R_{T-b} , is a two-gang linear potentiometer. Note that the value of the two variable elements are

continued on page 82

DESIGNING WITH DIGITAL IC'S

This month, we'll see how to interface TTL and CMOS devices to each other, and to other circuitry.

JOSEPH J. CARR

Part 4 BY DEFINITION, THE inputs and outputs of a "family" of logic IC's can be interconnected without the need for additional interfacing circuitry. For instance, Fig. 1 shows the output stage of one TTL IC and the input stage of another. A TTL input is a current source consisting of the emitter of an input transistor. One standard TTL input ("fan-in" of 1) sources 1.8 milliamperes of current at +2.4 to +5.0 volts. A TTL output sinks current. Normally, a TTL output will sink ten TTL inputs (i.e. 18 mA), although some TTL-compatible microprocessor output lines have a fan-out of only 1 or 2 rather than 10.

Few problems are encountered when interfacing IC's of the same family, but certain rules must be followed and/or techniques used when either interfacing IC's of different families (or sub-families!), or interfacing devices such as lamps, relays, solenoids, or motors. In this article, we will deal with some of those rules and techniques.

Interfacing logic IC's

There are times when we will want to interface logic devices with ones from other families. Figures 2 and 3 show several ways that that could be done.

In Fig. 2-a we see how any TTL output can be interfaced to any CMOS input. Recall that a TTL output is a current sink, while a CMOS input offers a very high impedance. Therefore, we must provide a current source from the +V supply to satisfy the TTL output. Resistor R1 serves as the current source in Fig. 2-a; its value is scaled to limit the current to approx-

imately one TTL load when the TTL output is low. For CMOS devices operated from a +12-volt-DC power supply, a 10K resistor (R1) is used.

Figure 2-b shows a PMOS device used to drive a TTL input. In that case, we have a 6800-ohm pull-up resistor between the PMOS output and the -12-volt DC power supply, and a 1000-ohm resistor in series with the TTL input. The latter resistor is used to protect the TTL input stage when the output from the PMOS device goes negative.

The circuit of Fig. 3-a is similar to the one shown in Fig. 2-a, with the exception that the CMOS device is operated from the same +5-volt DC power supply that serves the TTL devices. Note that a 2000- to 3000-ohm pull-up resistor is sufficient here.

Figures 3-b, 3-c, and 3-d show methods of interfacing CMOS outputs to TTL inputs. The 74Lxx and 74LSxx TTL devices have substantially lower drive requirements than regular TTL. We can therefore, drive one 74Lxx or 74LSxx TTL input from a standard CMOS output (Fig. 3-b). Only the 4001 and 4002 CMOS IC's (see Fig. 3-c) are capable of driving a standard 54xx/74xx TTL input.

There are two CMOS 4000-series devices (Fig. 3-d) that are designed to drive TTL devices under the right circumstances; those are the 4049 and 4050. If those devices are operating from a standard TTL DC power supply (i.e. +V = 5-volts DC, -V = 0-volt DC), then they can be directly interfaced with up to two 74xx, 74Lxx and/or 74LSxx devices. In some cases, you will find them capable of

 


FIG. 1—THE INPUT AND OUTPUT STAGES of a TTL IC are shown here. As is indicated, no special interfacing circuitry is needed when going from the output of one TTL device to the input of another.

 


FIG. 2—INTERFACING DIFFERENT LOGIC families. Here, the methods used to interface a TTL output to a CMOS input (a) and a PMOS output to a TTL input (b) are shown.

driving three or four 74Lxx or 74LSxx devices, but that falls into the category of "getting away with something."

Figure 4 shows a method for interfacing CMOS devices to LED's. The CMOS output functions as a switch in both cases. Also in both cases, there are current-limiting resistors in series with the LED, so that both the LED and the CMOS device are protected when the LED is turned on. Both NAND gates are wired as inverters, so

 


FIG. 3—MORE INTERFACING TECHNIQUES. Here, various ways of interfacing TTL and CMOS circuitry is shown.

 


FIG. 4—THIS CIRCUIT SHOWS HOW a CMOS gate, configured as an inverter, can be used to control an LED indicator.

they will produce a low output when the input is high, and a high output when the input is low.

In the circuit, LED1 is wired to be on (i.e. lighted) when the input to gate IC1 is high. The output of IC1 will be low in that case, so that point A is essentially grounded. Current then flows through the LED and it is turned on. Alternately, when the input is low, point A is high, so both sides of the LED see approximately the same voltage. Under that condition, no current will flow in the LED, so it is off.

One problem with that type of circuit is that if the difference between the supply

voltage and the voltage at point A is great enough, then LED1 may turn on dimly when it is supposed to be off. A higher-value series resistor may solve the problem.

Looking at the other part of the circuit, LED2 is designed to turn on when the input to the circuit is low. There, the LED and its current-limiting resistor are connected between the output of IC2 and ground. When the input is high, the output of IC2 is low, so both sides of the LED are at ground and the LED is off. When the input is low, on the other hand, the IC2 output is high, and current flows through the LED to ground, lighting it.

Interfacing LED's with TTL devices requires use of an open-collector device. Perhaps the most common of those are the hex inverters (the 7406, 7407, 7416, and 7417). Those IC's each contain six independent inverters with open-collector outputs. Figure 5 shows an LED indicator connected to the output of an open-collector TTL inverter. Figure 6 shows the same circuit, this time also showing the output transistor of the inverter.

Since the IC we are dealing with in Figs. 5 and 6 is an inverter, its output will be low when the input is high, and high when the input is low. Thus point A in Fig 6 will be grounded (i.e. low) when the input is high, and close to +V if the input is low. When point A is low, current flows through the LED and it is turned on. If the voltage at A is close to +V, then no current will flow and the LED is off.

If the above-mentioned inverters are

 


FIG. 5—THIS CIRCUIT SHOWS HOW a TTL inverter can be interfaced to an LED.

 


FIG. 6—WHEN THE INPUT TO THE INVERTER is high, the voltage at point A will be close to ground, causing current to flow through the LED, lighting it.

 


FIG. 7—WHEN THE INVERTER'S OUTPUT is high, the transistor conducts, causing current to flow through the lamp, lighting it.

 


FIG. 8—A MORE COMMON METHOD of interfacing a TTL inverter with a lamp is shown here.

used, then an LED may be operated from voltages greater than +5-volts DC. Scale the value of R1 according to Ohm's law to limit current in the LED to a safe value. For example, if a 20 mA (0.020-amp) LED is operated from a +12-volt power supply, the resistor should equal $R = V/I = 12/0.020 = 600$ ohms. Thus, for that application, a 600-ohm or larger resistor is used. Note that 680 ohms is the closest standard value, and will suffice. As to the power rating of the resistor, it should be greater than $V \times I$, or 0.24 watts in this case, with a margin for tolerance. Here, a 0.5-watt unit should be used (a 0.25-watt unit does not give enough margin).

Two methods that can be used to interface an incandescent lamp are shown in Figs. 7 and 8. Even the smallest grain-of-wheat bulb draws more current than a TTL open-collector output can handle, so an external transistor (Q1) is used to handle the load. The TTL inverter controls the base of the transistor, thus also controlling the lamp. The transistor selected must have sufficient collector current, collector voltage, and collector power-dissipation ratings for the lamp being controlled. In addition, the beta must be high enough to saturate the transistor given the collector current and the drive capability of the inverter.

In Fig. 7, we see a regular TTL inverter driving an NPN transistor "lamp switch." An NPN transistor will conduct when the base is more positive than the emitter. In this circuit, therefore, the transistor conducts and turns on the lamp when the TTL output is high. Keep in mind that TTL outputs are not designed to supply current, so the base current for Q1

that's available in this mode is limited.

A more common circuit is shown in Fig. 8. Here we use a PNP transistor as the lamp switch. Such a transistor will conduct when the base is more negative than the emitter. The inverter is an open-collector type, so it will ground the base of Q1 when the output is low. Under that condition, the emitter is at +V and the base is close to ground, so the transistor conducts. When the output is high, however, the transistor is open-circuited, so resistor R1 keeps the base at essentially the same voltage as the emitter. Under that condition, the transistor does not conduct and the lamp is off.

Interfacing relays

Relays and solenoids can present special interfacing problems for digital electronics. Relays are electromechanical switches that are used to control high voltages and/or high currents. A relay consists of a coil electromagnet that activates a set of switch contacts. A solenoid is a device used to move or actuate mechanical objects. It consists of a hollow coil in which a movable core is placed. When current flows in the coil, a magnetic field is created that suddenly draws the core into the coil.

 


FIG. 9—AN OPEN-COLLECTOR TTL INVERTER can be used to directly control a relay or a solenoid if the device's current requirements are low enough.

Figure 9 shows a method for interfacing relays and solenoids to digital circuits. The relay/solenoid coil is connected as the load between +V and the output of an open-collector TTL device. When the TTL output is low, current flows through the coil and it is energized. Since the relay/solenoid is actuated when the TTL output is low, a high input to the inverter is required to actuate the relay/solenoid.

A diode, D1, is placed in parallel with relay coil in Fig. 9 to solve a special interfacing problem: "inductive kick." When an inductor is energized (current passes through the coil), a magnetic field builds up around the coil. If the flow of current is suddenly interrupted, the collapsing field creates a high-voltage spike that can damage electronic components. In digital circuits, the pulse from that inductive kick can upset circuit operation even when it does not destroy the components. Placing

 


FIG. 10—FOR RELAYS WITH CURRENT requirements that exceed 30–40 mA, this interfacing circuit can be used. Diode D1 is used to keep the level of any inductive spikes to less than 0.7-volt.

 


FIG. 11—THE USE OF A DARLINGTON PAIR allows a TTL inverter to control a relay or solenoid with very high current requirements.

the diode in the circuit as shown will clip any spikes to 0.7-volt.

The above method is only appropriate for use with relays that have current requirements of 30–40 mA, or less, and as such compatible with the capability of open-collector TTL devices. Two alternate methods of interfacing a relay or solenoid with higher current requirements are shown in Figs. 10 and 11.

Figure 10 uses a single transistor (Q1) to act as an electronic switch to control the relay or solenoid. The collector-emitter path of Q1 is in series with the coil, so the relay/solenoid will become energized when Q1 is turned on. That situation occurs when the base of Q1 (an NPN transistor) is more positive than the emitter. Since the base of Q1 is connected to a TTL output, the relay or solenoid is energized when the output is high. In some cases, a pull-up resistor is used between the TTL output and +V.

As in the previous case, a diode "spike suppressor" shunts the coil. A 1000-volt (PIV), 1-amp, 1N4007 diode is suitable for that application.

The value of resistor R1 depends upon the gain of Q1 (beta) and the required

collector current. In most +5-volt DC circuits, 2700 ohms is used for all but the lowest-gain transistors.

The circuit of Fig. 11 is used for solenoids and high-current relays. Transistors Q1 and Q2 form a Darlington pair. That circuit provides very high beta gain, as the overall beta is the product of the beta's of the two transistors.

Interfacing the 555

The 555 is an IC timer that has achieved widespread popularity. It can be used to output either a single pulse or a string of pulses. Its output (pin 3 when the device is housed in its usual 8-pin DIP) is capable of sinking or sourcing up to 200 mA of current.

Figure 12 shows a simple method for interfacing LED's, lamps, or relays, providing that they have current requirements of less than 200 mA. This circuit is "left-handed" in that the relay, LED, or lamp is energized when the 555's pin 3 output is low.

 


FIG. 12—AN LED, LAMP, OR RELAY (as shown), with a current requirement of less than 200 mA, can be interfaced directly with a 555 timer.

 


FIG. 13—A 555 TIMER CAN BE ACCIDENTALLY retriggered if noise is applied to its output terminal. To prevent that from happening, up to three diodes can be connected in series with the output, as shown.

Sometimes, a 555 is accidentally retriggered by circuit noise applied to the output terminal. Such noise is especially likely when inductive loads such as relay coils are driven. If that is a problem, then up to three 1N4000-series silicon diodes can be connected in series as shown in Fig. 13 to isolate the output of the 555.

In the next installment in this series, we will turn our attention to one of the building blocks of digital circuits, the basic flip-flop. At that time, we will discuss basic flip-flops, including the reset-set (RS) flip-flop, clocked RS flip-flop, and the master-slave flip-flop. R-E

ROBOTICS



MARK J. ROBILLARD
ROBOTICS EDITOR

Getting started in robotics

THE WORD "ROBOT" CONJURES UP many different images in people's minds; everything from Hollywood's lovable creations to the monstrous machines that many once believed would someday take over the Earth. Regardless of what you think of them, they are everywhere today. For instance, your car was probably assembled and inspected for defects on a robotic assembly line.

Even so, the number of problems found in new cars tells a lot about the state of robotics technology. Robots are prone to make many mistakes; after all, look at who created them! However, those system miscalculations are not the same misjudgments of which man is so often guilty. They are, instead, problems that arise due to the limitations of the technologies involved. Today, the field of robotics is where personal computers were in the mid-1970's.

Our purpose

In this column, we'll try to keep you up to date on the latest happenings in robotics field. We'll also cover several technical topics and look at numerous robotic devices that you can build. You'll receive instructions on building a robotics laboratory, an intelligent platform, and an ultrasonic vision system.

We'll include indepth product reviews of the various robots. And you'll have the opportunity to read about those products before you see them anywhere else. And since the field is still in its infancy, believe it or not, you can make a significant contribution through personal research. As a reader of **Radio-Electronics**, you are used to



FIG. 1

participating in new technologies. For example, the first construction details for a personal computer appeared in these pages.

Personal robots

About two and a half years ago, personal robots came to the attention of consumers through the introduction of RB Robot Corp.'s (14618 W. 6th Ave., Golden, Colorado) small cylindrical rover, the *RB-5X*. That microprocessor-based unit could directly execute BASIC programs entered by the user from a remote terminal. Several design changes have occurred since its introduction, including the addition of an ultrasonic range finder and a somewhat articulated arm.

Shortly thereafter, U.S. Heath Co. (Benton Harbor, MI 49022) introduced its *HERO-1* (see Fig. 1). Both the Heath and RB products showed that there was considerable interest in building and experimenting with intelligent vehicles.

Some time after *HERO* and *RB-5X* made their debut, a new company headed up by Atari's founder, Nolan Bushnell, introduced the *TOPO* robot. That unit was much taller, with a more human-like appearance; but its limited capabilities and non-existent third-party support kept it from reaching its full potential. Today, Heath's *HERO* is said to be leading in sales, with a rumored 8000 machines in existence. However, the field is constantly widening.

Industrial robotics

Although the public views the robotic production line as merely a collection of mechanized arms, the industry is having a love affair with those mechanical marvels. Assembly-line robots are usually supplied materials via a system of intelligent, roving, driverless vehicles. Those vehicles are built using a combination of technologies, including mechanical engineering, electronics engineering, and computer science.

From those fields come the design of the various robot parts. For example, mechanical engineering provides the body structure, the wheeled mechanics, and the arm linkages. Electronics engineering contributes the control circuitry and various sensory devices needed to help make the robot system interact with its environment.

The sensors include sonic distance-measuring systems, tactile sensors for finger tips, wheel-position feedback sensors based on optoelectronic or Hall-effect technologies, etc. Computer sci-

continued on page 70

PC SERVICE

As anyone who has ever tried knows, one of the most difficult tasks in building one of the many construction projects featured in **Radio-Electronics** is making the PC board using just the foil pattern provided in the article. True, all sorts of kits and things are sold to let you lift a foil pattern from a magazine page. But, while some of them do work, most of them don't. What usually happens is that you wind up copying the artwork by hand.

Well, we're doing something about it.

We've moved all the foil patterns to a new section of the magazine. They'll be printed by themselves, full sized, with nothing on the back side of the page. What that means for you, is that the printed page can be used directly to produce PC boards!

Actually the method you'll need to use to etch directly from printed artwork is a little bit different from the one you're probably used to using to produce PC boards, but we've done some testing and it works!

In order to produce a board directly from the magazine page, you first need to do a little bit of work on the foil pattern. The first thing to do is remove the page from the magazine and carefully inspect it either under a good light or on a light table. As a matter of fact you should really do both of those since each one will show up different kinds of imperfections in the artwork. What you're looking for are breaks in the traces, bridges between traces, and in general, all the kinds of things you look for in the final etched board. You can clean up the published artwork the same way you clean up your own artwork. Drafting tape and graphic aids can fix incomplete traces and doughnuts, and you can use a hobby knife to get rid of bridges and dirt.


Once you're satisfied that the artwork is clean, take a little bit of mineral oil and carefully wipe it across the back of the artwork. Don't get any on the front side of the paper (the side with the pattern) because you'll contaminate the sensitized

surface of the copper blank. (If you *do* contaminate it, you won't notice anything when you make the exposure, but when you develop the board, the oil can act just like resist and keep the developer from dissolving the unwanted resist on the board.

After the oil has "dried" a bit—patting with a paper towel will help speed the process—place the pattern front side down on the sensitized copper blank, and make the exposure.

The mineral oil is optional, but it does do two things for you. It makes the paper much more translucent and it makes the foil pattern appear darker. A successful exposure depends on having as much contrast as possible in the exposure mask and that's exactly what the mineral oil does.

 Even though the mineral-oil treated paper is translucent, it's still not anywhere as clear as lithographic film (which is what's normally used in producing PC



PC SERVICE

boards). That means that you're going to have use a longer exposure time than you are probably used to.

We can't tell you exactly how long to make the exposure time, because we don't have any idea what kind of light source you use. A simple rule of thumb is to figure that there's a 50 percent increase in exposure time over lithographic film. But that doesn't necessarily mean you'll need a 50 percent increase. If you're used to taping up a pattern on mylar sheets,

you'll find that rubbing the paper with mineral oil makes it just about as translucent as mylar.

Note that sensitizers vary as well. Mineral oil isn't as transparent to ultraviolet light as it is to other parts of the spectrum. If your sensitizer wants to see ultraviolet, you may find using mineral oil to be more trouble than it's worth.

You'll have to experiment to find the best method to use with the chemicals you're familiar with. And once you find it,

stick with it. Don't forget the "three C's" of making PC boards—care, cleanliness, and consistency.

Finally, we would like to here how you make out using our method. Write and tell us of your success, and failures, and what techniques work best for you. Address your letters to:

Radio-Electronics
Department PCB
200 Park Avenue South
New York, NY 10003

DESIGNER'S NOTEBOOK



ROBERT GROSSBLATT

Do-it-yourself test instruments

THE MORE EXPERIENCED YOU BECOME in electronics design, the more you depend on test equipment. While there are commercially available devices designed to test just about any kind of parameter you can think of, many designers wind up building their own test instruments to do quick-and-dirty tests on the breadboard. And the simpler the parameter, the more likely the test instrument used will be something home-grown.

If you're dealing with digital design, things like logic probes and pulse stretchers are more likely to be products of your own imagination. Logic probes are easily built. At the most basic level, all that's needed is an LED and a resistor. You can, of course, add "bells and whistles" like high and low tone generators, but the simplest circuit will do the job just as well.

Pulse stretchers are more complex to design, although a perfectly workable one can be built from a handful of parts. Which parts you use is up to you. Once you understand the theory, translating it into practice is simple. Pulse stretchers are really two-part circuits.

Pulse stretcher circuits

Figure 1 shows a basic pulse stretcher circuit. The first half is an input section that detects the pulse and triggers the second half of the circuit, a pulse generator. The factors to keep in mind when designing such circuits are the same ones you should consider in the design of any other circuit: The circuit should not affect the unit under test; its input impedance should be at least 1 megohm; it should operate over a wide voltage range, and it should be able to draw power from the unit under test.

The circuit in Fig. 1 is a good example of a simple pulse stretcher that meets all the criteria we've listed. It can be assembled from leftover parts in your circuit.

The input section is a single inverter, IC1-a. When a positive pulse appears at its input, an equivalent negative pulse is generated at its output. That discharges the capacitor through the diode, D1, and causes the output of the second inverter to go high. The inverter at the input reverts to its original state as soon as the input pulse ends, but D1 prevents the

capacitor from charging up again through the input. The capacitor has to charge through the resistor in a time equal to the familiar formula $T = RC$.

You should recognize the second half of the circuit as a one-shot. If you so desired, you could even eliminate the second inverter and drive the LED directly from the input section. However, the output section of the pulse stretcher follows the same calculations: $T = RC$.

You can also use a 555 as a pulse stretcher...just set it up as a one-shot and you're in business. But you may find the inverter version shown here a bit handier, since there's always a spare logic gate or two left on the breadboard. In any event, once you understand the theory, it's easy to put together a pulse stretcher.

You've probably noticed that the circuit is set to detect *only* positive pulses applied to its input. Detecting negative pulses is just as easy. Two ways of accomplishing that are by adding another inverter to the input section, or by reversing the resistor and capacitor connections. If you go the latter route, remember to flip the diode around and tie the LED anode to +V instead of ground.

A full-blown pulse detector would be able to detect pulses of either polarity, and the output pulse should give some indication of the width of the input pulse you're detecting. Designing a circuit that does all that isn't really difficult; you can easily do it yourself. And if there's enough interest, I'll do it here.

R-E

 


FIG. 1

ROBOTICS

continued from page 66

ence provides the software to control and use all the sensors to effectively control the wheels and appendages.

Almost any intelligent system can qualify for the term robot. What's meant by "intelligent system" is a fully integrated mechanical/electronic machine that has the ability to perform a seemingly intelligent task. An example of that is the increased use of automatic machine-vision systems that manufactures are using to detect subtle flaws in the workmanship of the mechanical arms.

Such vision systems use lots of electronics and some pretty sophisticated software routines to imitate the eye of a trained inspector. Those systems are slower than their typical human counterparts, but the precision achieved far surpasses that of the human inspector. And their overall output is constant.

The industrial future

Industrial robots have been around for several years, although the technology is considered to be in its infancy. While some manufacturing processes are automated, several thousand other tasks remain mostly manual operations. And although many universities and several corporations are involved in the study of robotic systems, there's still plenty of research not being done.

The price range for a typical arm system can be in tens of thousands of dollars. One factor that keeps costs high has to do with the power that's required to do the work. It's not easy to design powerful mechanized muscles.

Recent advances in what is called "light industrial" robots (those with limited capability) have driven the cost down. But, those robots were never intended for home use.

But what should a home robot do? That's a question that has been around even before the personal-robotics field emerged. And it's just one of the questions that we'll answer in the coming months. **R-E**




SUBSCRIPTION TV MANUAL. This information packed book details the methods used by subscription TV companies to scramble and descramble video signals. Covers the Sinewave, Gated Pulse, SSAVI system, and the methods used by most cable companies. Includes circuit schematics, theory, and trouble shooting hints. **Only \$12.95 plus \$2.00** first class P&H. **ELEPHANT ELECTRONICS INC., (formally Random Access) Box 41770-R, Phoenix, AZ 85080**
CIRCLE 120 ON FREE INFORMATION CARD



FREE CATALOG OF HARD-TO-FIND TOOLS is packed with more than 2000 quality items. Your single source for precision tools used by electronic technicians, engineers, instrument mechanics, schools, laboratories and government agencies. Also contains Jensen's line of more than 40 tool kits. Send for your free copy today! **JENSEN TOOLS INC., 7815 46th St., Phoenix, AZ 85040. (602) 968-6231.**

CIRCLE 115 ON FREE INFORMATION CARD

 


THE MOST EXCITING KIT YOU WILL EVER BUILD The model WAT-50 miniature FM transmitter uses a 4-stage circuit NOT to be confused with a simple wireless microphone. Up to 1 mile range. So sensitive, it will pick-up a whisper 50 feet away! Use with any FM radio. Complete kit only **\$29.95** tax incl. **FREE SHIPPING. DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 241-2827.**

CIRCLE 127 ON FREE INFORMATION CARD



APPLIANCE REPAIR HANDBOOKS—13 volumes by service experts, easy-to-understand diagrams, illustrations. For major appliances (air conditioners, refrigerators, washers, dryers, microwaves, etc.), elec. housewares, personal-care appliances. Basics of solid state, setting up shop, test instruments. **\$2.65 to \$5.90 each.** Free brochure. **APPLIANCE SERVICE, PO Box 789, Lombard, IL 60148. 1-(312) 932-9550.**

CIRCLE 84 ON FREE INFORMATION CARD

 

CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$650 per each insertion.
- Reaches 225,016 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call **212-777-6400** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS. RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.

Radio-Electronics mini-ADS




TEST COMPONENTS IN CIRCUIT, POWER OFF WITH THE NEW HUNTRON® TRACKER® 2000. Revolutionary Huntron Trackers find shorts, opens, leakage and bonding problems in analog, digital and hybrid components. Test capacitors, logic circuits, op amps, transistors and more. An excellent troubleshooting tool that finds the faults scopes, DMM's and logic analyzers miss. Tracker prices start at \$995.00 For nearest distributor, call 1-800-426-9265. **HUNTRON INSTRUMENTS, INC.**, 15123 Highway 99 North Lynnwood, WA 98037. **CIRCLE 272 ON FREE INFORMATION CARD**




ZENITH SSAVI DESCRAMBLERS only \$169; GATED PULSE & SINEWAVE decoders \$199 each. Reconditioned. Original equipment for UHF chs. 23,27,31, 48,50,51,54,57,60,67,68 etc. Quantity discounts. Surplus Cable TV equipment: Jerrold SB-3, Oak N-12, Zenith Z-Tac, Hamlin 1200, etc. Catalog \$1. 10 days satisfaction guarantee & 90 day warranty. **AIS SATELLITE, P.O. Box 1226-E, Dublin, PA 18917.** 1-800-643-2001 or 215-249-9411. **CIRCLE 260 ON FREE INFORMATION CARD**



 
R & D SHEET METAL WORKER new multi-purpose machine now with 6" male dies and removable female dies. A complete R&D in-house shop at 1/3rd the cost. Over (1500) worldwide industrial/government/educational. Call today—**TELEX 4996168 POC NPT, PACIFIC ONE CORP., STEK542513 Superior Ave., Newport Bch., CA 92663.** (714) 645-5962. **CIRCLE 118 ON FREE INFORMATION CARD**



 MAKE NOISE-FREE RECORDINGS. The P-522 Tape Noise Reduction uses 2:1 companding to increase headroom while reducing tape hiss for a 30 dB improvement over normal recording. The kit (P-522-NR) is only \$79 and the assembled (P-522-NRA) \$139. **PHOENIX SYSTEMS, INC-RE, P.O. Box 338-b, Stone Mountain, Ga. 30086** or call (404) 934-9626. M/C & VISA welcome. **CIRCLE 69 ON FREE INFORMATION CARD**



MODEL 502 PRECISION PANAPRESS. Less than 6 pounds, standing only 7 inches high, this hand arbor press exerts pressure up to a quarter-ton. **Panapress** is ideal for pressing bearings, sleeves or collars, forming and assembling small parts, punching, riveting, broaching, staking and dozens of other operations. Only \$65.95. See your dealer or contact: **PANAVISE PRODUCTS INC., 2850 East 29th Street, Long Beach, CA 90806.** (213) 595-7621. **CIRCLE 256 ON FREE INFORMATION CARD**

 

SATELLITE TELEVISION RECEIVER SEMIKIT with dual conversion downconverter. Features infrared remote control tuning, AFC, SAW filter, RF or video output, stereo output, Polorator controls, LED channel & tuning indicators. Install six factory assembled circuit boards to complete. **Semikit \$300.00**. Completed downconverter add \$100. Completed receiver and downconverter add \$150. **JAMES WALTER SATELLITE RECEIVER, 2697 Nickel, San Pablo, CA 94806.** Tel 415-724-0587. **CIRCLE 124 ON FREE INFORMATION CARD**



ELECTRO IMPORTING CO. CATALOG. This reprint of the historic 176-page catalog No. 20 gives you an accurate look at the state of electronics in 1918. Contains everything from a Zinc Spark Gap to a 1000-Mile Receiving Outfit. You can get your own copy of this modern antique, profusely illustrated, for only \$4.95 plus \$1.00 P&H. Order yours from **R-E BOOKSTORE, Radio-Electronics, 200 Park Avenue South, New York, NY 10003.**



THE WIRELESS TELEPHONE TRANSMITTER model WTT-20 is only the size of a dime, yet transmits both sides of a telephone conversation with crystal clarity. Completely automatic Uses power from the telephone line itself. Never needs a battery! Up to ¼ mile range. Use with any FM radio. Complete kit only \$29.95. Tax included. **FREE SHIPPING. DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507.** (914) 241-2827. **CIRCLE 127 ON FREE INFORMATION CARD**



CALIFORNIA-DC REGULATED SWITCHING POWER SUPPLY +5v dc @ 5 amp + 12v dc @ 2.8 amp + 12v dc @ 2 amp -12v dc @ .5 amp 115-230v ac input, fused. EMI filtered. Removable DC Power Harness and Schematics included. 7.4" x 6.2" x 1.7" ht. Visa/MC/M.O./check; when clears. \$37.50 ea. (Free shipping in U.S.) 1-800-327-7182/305-830-8886. **POWER PLUS, 130 Baywood Ave., Longwood, FL 32750.** (Call for quantity price). **CIRCLE 125 ON FREE INFORMATION CARD**

DRAWING BOARD




ROBERT GROSSBLATT

Putting the 5101 to work

THERE'S A KIND OF NATURAL LAW GOVERNING the development of new electronic equipment. As the revision numbers on the boards go up, the amount of power drawn by the unit goes down. Something that starts life needing 86% of the output of the TVA usually winds up, a couple of revisions later, one tenth the size and running on barometric pressure!

Much of that progress is due to more efficient design, custom IC's, and microprocessors. But the major factor is the continuing evolution of CMOS technology.

 The 5101 was an early entry into the low-power CMOS market. When it first appeared, most designers were knocked out of their socks by its low-power charac-



0 = 0000	4 = 0100	8 = 1000	C = 1100
1 = 0001	5 = 0101	9 = 1001	D = 1101
2 = 0010	6 = 0110	A = 1010	E = 1110
3 = 0011	7 = 0111	B = 1011	F = 1111

FIG. 3

teristics, and its guarantee to retain data at a low-power figure. Although technology has gone beyond the 5101, knowing how to use its low-power feature is still important.

Memory control

Although the data sheet for the 5101 gives the impression that using its standby feature is as easy as putting the right voltage on pin 17, there's a bit more to it than that. To be sure that your data doesn't disappear in the standby mode, there are four hard-and-fast rules that must be followed closely and in a certain order:

- The IC has to be locked in the read mode.
- The address lines have to be stabilized.
- All inputs and outputs must be turned off.
- The transition to standby power has to be glitch-free.

Locking the IC in the read mode is important, but often overlooked. Remember that you can write to the 5101 when R/\bar{W} is brought low. That line is also brought low when system power is disconnected. But if another line stays active for any time after that,

a phony-baloney write is generated. That means that the next time the circuit is powered up, you'll find some of the data overwritten.

There are two ways we can guard against that. One way is to lock the operation of pin 19, CHIP ENABLE, to the power-down procedure. The other way is to directly control the R/\bar{W} pin, and synchronize it to the transition to standby.

Control synchronization

If you lock the device in read by directly controlling the R/\bar{W} pin, the address lines must remain unchanged. However, the more traditional way is to completely disable the IC. Then, what's going on with the address bus is irrelevant.

The same thing applies to the I/O. Disabling the entire IC, naturally, disconnects the IC from the I/O bus. However, if things are done differently, you'll have to design a circuit that first disconnects the memory from system I/O. The outputs are no problem since the 5101 has a separate control (pin 18) to three-state the output. But a buffer arrangement of some type is needed for the inputs.

The last rule, and the last opera-

 


FIG. 1

 


FIG. 2

COMPUTER DIGEST

VOL. 2 NO. 7

July 1985

NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS

OPTICAL CHARACTER RECOGNITION

Keeping Up With The State Of The Art



A
GERNSBACK
PUBLICATION

YOU CAN ADD A HARD DISK

It May Not Be As Difficult As You Thought

WRITE PROTECT NOTCH BYPASS

Now You Can Use Both Sides Of A Disk


ZORBA

PORTABLE COMPUTER

THE EXPERTS' CHOICE

FEATURES:

 - 9" GREEN OR AMBER CRT
- 19 INDEPENDENT 55 PROGRAMMABLE FUNCTION KEYS
- TWO 400K DSDD DRIVES
- 64K BYTES 200 NS RAM
- C BASIC COMPILER
- IEEE 488 BUS MASTER PORT
- 24.6 LBS
- CPM 2.2 OPERATING SYSTEM
- M80 (L80, LIB80, CREF80)
- SOURCE CODE OF THE BIOS PLUS UTILITIES
- DATA COMMUNICATIONS SETUP PACKAGE
- SERIAL & PARALLEL PRINTER PORT
- DATA COMMUNICATION PORT



OPTIONS:

- 16 BIT 256K RAM UPGRADE (8088 CPU) \$600.00
- 800K DSQD 96TPI DRIVES \$200.00
- COMPOSITE VIDEO OUTPUT \$100.00
- SOFT VINYL CASE \$25.00
- TUTOR KIT; \$15.00 (CPM, WORDSTAR, CALCSTAR)
- SCHEMATIC SET \$10.00
- 10MB HARD DISK DRIVE

VISA/MC

BUNDLED WITH
WORDSTAR, MAIL MERG, SPELLSTAR,
DATA STAR, REPORTSTAR, CALCSTAR

\$849.00

W/O Bundle

DEALER INQUIRIES INVITED

\$1049.00

With Bundle

General Specifications

ZORBA is the lowest cost full featured portable computer. This light weight computer is ruggedly packaged in a convenient carrying case. The case surrounds a strong inner chassis which further protects the Z80A based computer with its two double sided double density disk 400K drives, large easy to read 9" display screen and well designed detachable keyboard.

ZORBA uses CP/M, the industry standard operating system, which means that a wide range of existing software is readily available to the user.

The ZORBA users manual covers operation of the unit, all supplied software and all interface and internal information. A system diskette is supplied with all system files and utilities. A second diskette contains the sources for all ZORBA software including BIOS, SETUP, FORMAT, and PATCH.

Keyboard

Keyboard communicates serially with CPU Detachable with 2 foot coiled cord 95 keys in standard QWERTY format 13 Key Numeric pad Independent Caps Lock and Shift Lock 55 Software programmable function keys All keys auto-repeat after 1 second delay All Standard cursor and terminal control keys

Disk System

Controller: WD1793
Drives: 5.25 Double Sided, Double Density, 400K 48 TPI

Built-in disk interchange formats: Xerox 820 (SD, DD), Kaycomp (DD), DEC VT-180 (SD), Osborne (SD) and IBM-PC (eg. CPM/86) and Televideo 802 (Read/Write and Format compatibility) (Expandable to 61 Formats)

Specifications

General Mechanical and Electrical

Width -17.5 inches (44.45 cm)
Height - 9.0 inches (22.86 cm)
Depth -16.0 inches (40.64 cm)
Weight -24.6 pounds (11.1 Kg)
Power -80-130 VAC or 190-245 VAC 50/60 Hz 170 watts max

Display

Display Tube: 9" diagonal, Green or Amber High resolution display circuitry 60 Hz refresh rate

Display Format:

25 lines x 80 columns
5x7 Character Font with full descenders
128 ASCII Characters
8x9 32 Characters Graphic Font
2K Memory Mapped Display Buffer

CPU Board

Z80A CPU running at 4 Mhz with no wait states 64K bytes of 200 ns RAM (58K after CP/M loaded) 16K bytes of EPROM (2732) can be switched in and out by software 12K available for user EPROMS 8275 CRT controller, DMA driven 1793 Floppy disk controller, SMC data separator Bipolar proms configure 10 addresses Fully structured interrupts prioritized by bipolar proms

Interfaces

- Full asynchronous RS232 port with modem control. Baud rates and data translation and protocol programmable
- Full asynchronous full duplex RS232 port with hardware handshake (for printers). Baud rates and protocol programmable. (Serial Printer Port)
- One 8 Bit parallel port with independent strobe and ready lines. Supports Centronics interface with an available adaptor cable.
- IEEE 488 Bus Master Port (ie: General Purpose Instrumentation Bus) not Software Supported.
- 21 Standard Software Programmable Baud Rates: 45.5 to 19,200 BPS



GEMINI ELECTRONICS, INC.

130 Baywood Avenue, Longwood, Florida 32750
305-830-8886 800-327-7182

CONTENTS

Vol. 2 No. 7

July 1985

8 Optical Character Recognition

The technology has come a long way, as you'll learn in this state-of-the-art report. OCR units are able to save a lot of time and work.

Mark Stern

12 Write-Protect Notch Bypass

You won't have to cut or punch slots or holes any longer. This simple circuit does it all electronically. **Noel Nyman**

14 Adding A Hardisk Driver

This step-by-step explanation makes it all simple. Even if you have no plans to do this in the near future, you will want to learn what's involved—and what the benefits are. **Herb Friedman**

4 Editorial


Language: Words can be important

5 Letters


5 Computer Products

7 Software Review

Dysan Interogator

 

Page 8

 

Page 14

ON THE COVER

Optical Character Recognition (OCR) has come a long way since its inception. We now see a form of it in daily use at grocery checkouts with Uniform Price Codes. Our cover shows the Desk-Top unit from DEST, Inc. See page 8.

NEXT MONTH

DIGITIZING TABLETS

Inputting without a keyboard isn't new but technological changes have been making it better.

CASSETTE-TO-CASSETTE INTERFACE

This simple construction project will take the drudgery out of tape copying for you.

DELUXING THE RADIO SHACK COLOR COMPUTER

Making your low-cost unit perform like a top-dollar investment.



EDITORIAL

Language: A tool for communication.

■ There's an old saying among writers, "Write to *express* not to *impress*." One of the first things that technical writers learn, is that the first time you use a new technical term, you explain it. If you aren't communicating, no matter how well-written the piece may be, it's worthless.

We who are involved with computers are often guilty of the same kind of sin. We know what we mean, we know what we want to say, but we sometimes forget who it is that we're talking to. And if we use words, terms or expressions that our listeners do not understand, we are not communicating.

These "special words" that are indigenous to a specific field, are called "jargon." And they exist in every trade there is. Among the practitioners of that trade, the words are well understood, but to an outsider, they might as well be a complex foreign language.

While they form a sort of "spoken shorthand" to people within a given field, they only serve to confuse those who are neophytes. If you're out to impress people with your knowledge, you can sprinkle jargon into everything you say and when you see the utter confusion on their faces, you can mentally pat yourself on the back and remind yourself about how positively *brilliant* you are!

But rest assured that there are others—many others—who know a good deal more about computers than you do, and are capable of leaving you confused as well.

How much better to make certain that what you say is understood by everybody present. For one thing, it's only polite. For another, you'll be communicating. And if you really have something to say, it will be understood and appreciated by all. Those who are truly secure in their own knowledge don't feel that they have to impress anybody.

So of course, they make a much better impression!



Byron G. Wels
Editor

COMPUTER DIGEST

Hugo Gernsback (1884-1967)
founder

M. Harvey Gernsback,
editor-in-chief

Larry Steckler, CET, publisher

Art Kleiman, editorial director

Byron G. Wels, editor

Brian C. Fenton, technical editor

Carl Laron, associate editor

Robert A. Young, assistant editor

Ruby M. Yee, production manager

Robert A. W. Lowndes,
production associate

Dianne Osias,
production assistant

Karen Tucker, production assistant

Jacqueline P. Weaver,
circulation director

Arline R. Fishman,
advertising coordinator

Gernsback Publications, Inc.
200 Park Ave. South
New York, NY 10003
Chairman of the Board:
M. Harvey Gernsback
President: Larry Steckler

ADVERTISING SALES 212-777-6400

Larry Steckler
Publisher

EAST/SOUTHEAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
212-777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
Radio-Electronics
540 Frontage Road—Suite 325
Northfield, Illinois 60093
312-446-1444

PACIFIC COAST Mountain States

Marvin Green
Radio-Electronics
15335 Morrison St., Suite 227,
Sherman Oaks, CA 91403
818-986-2001

ComputerDigest is published monthly as an insert in Radio-Electronics magazine by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Second-Class Postage Paid at New York, N.Y. and additional mailing offices. Copyright © 1985 Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

LETTERS

Out Of Warranty

After I hit the necessary break-in mileage on my car, I finally got to floor the accelerator and see what it could do. Now, finally, my computer has passed the warranty date. Does this mean that at last I can open 'er up and start modifying some of the innards without having to worry?—Tony Richards, Corpus Christi, TX.

It's not the same thing at all, Tony. Up until that warranty point, should anything have gone wrong, you could have brought your computer back for factory service—provided you had not opened it up. Now that the date has passed, anything that goes wrong, either with or without your help, is on your own shoulders and pocketbook. Good luck.

Glitch!

In the April, 1985 Issue of **ComputerDigest** there appear to be some mistakes in the program for "Resonant Circuit Design." One error was corrected by changing

line 420 as follows:

420
T = SQR((Z*((9*D) + (10*G)))/D)
was published.

420
T = SQR((Z*((9*D) + (10*G)))/D/D)
is correct.

Also, line 100 should end with a quotation mark (") like line 90, and in line 140 the semicolon after CLS should be a colon. There should be a space between GOTO and 90. In line 220, delete the comma. And while line 450 is not wrong, I would recommend a space between the first quote-mark and the word IS.

After making these changes, the program ran quite well.—Jack Ivers, Westwood, MA.

Thank you Jack. We've received a few calls and letters on that one, and your information certainly helped. We really appreciate it.

Dear Abie?

My girl friend left me for another guy who is loaded with money, and I can't get her out of my mind.

What can I do?—Ken Harwood, Hilo, HI.

Ken, I think you must have written TWO letters and put them in the wrong envelopes. I'm really curious to see how "Dear Abie" answers the one intended for us!

Computer Operator?

What exactly constitutes a "computer operator?" Granted, the guy who can write his own software and run it is a computer operator. But if this is true, how about the man who buys ready-to-use software and just runs it on his home computer? Isn't he an "operator?" What started all this was a friend who just bought a new car with a computer control in it, and now he's telling everybody he's a computer operator.—Frank Spevins, New York, NY.

It seems to be a matter of degree Frank. But be tolerant. If this makes him happy, go along with it. It doesn't hurt anything, does it?

COMPUTER PRODUCTS

For more details use the free information card inside the back cover

SCHEMATIC DESIGNER SYSTEM, the DASH-2, is designed for engineers using the IBM PC/XT or AT, adding a new coordinated set of enhanced, mouse-driven editing features.

DASH-2 capabilities include:

Tag and drag, which enables the user to pick a symbol, a drawing area, or alphanumeric field and drag the targeted selection across the screen while maintaining connections.

Snap, which allows the user, when drawing a circuit connection, to position the cursor in the vicinity of a pin, "snapping" the connection in place. In the snap mode, when the cursor is inside a symbol cell, a pin cursor appears on the closest pin. The pin cursor jumps from pin to pin as the



CIRCLE 21 ON FREE INFORMATION CARD

cursor is moved to locate the desired contact pin.

Area definition, using mouse, whereby the mouse is used to locate any two opposite corners of the desired area. The area boundary is displayed in "real time."

The DASH-2 add-on package (model D2-MAP-PC) for the IBM PC is priced at \$5,980, with the complete DASH-2 system (model D2-545-PC), including the IBM PC and printer, selling for \$9,980. DASH-2 for the IBM XT (model D2-MAP-XT) is priced at \$6,280, add-on-package, and \$12,980 for the complete system (model D2-SYS-XT).—FutureNet Corporation, 6709 Independence Ave., Canoga Park, CA 91303-2997.

VIDEO DISPLAY TERMINAL, the model ADM 12plus, is a smart editing terminal useful for word-processing, financial spreadsheets, and other specialized applications. The block mode terminal is compatible with the Tele-

video 925, 950, 912, and 920 terminals, and the Lear Siegler ADM 2, ADM 12, and the ADM 31.



CIRCLE 22 ON FREE INFORMATION CARD

The terminal features programmable cursor keys for word-processing programs such as WordStar, a variable-format display memory, variable-speed vertical and horizontal scrolling. The model ADM 12plus provides two pages of 80/132-column by 24-line display memory (plus 25th status line), or a choice of wide and long page-memory configurations. A four-page memory option is also available to double the standard memory formats and add a 158-column by 48-line "Super Page" display-memory format.

The model ADM 12plus is priced at \$745.00.—Lear Siegler, Inc./Data Products Division, 901 East Ball Road, Anaheim, CA 91805.

SPEECH SYNTHESIZER, the Voice Master for the Commodore 64, the Apple II, II+, and IIe (shown), is three products in one: a speech synthesizer, voice-recognition system, and music machine.



CIRCLE 23 ON FREE INFORMATION CARD

The Voice Master speaks clearly in your own voice, in any language, and with any accent. It is basically a digital tape recorder. To record speech, the user uses the command LEARN and speaks into the microphone what he or she wants the computer to say. To play back, the SPEAK command is used. Up to 64 different words, phrases, or other sounds can be in memory at one time, and entire vocabularies can be stored and loaded from disk.

To use the speech-recognition feature, the user stores the words or

phrases to be recognized, using the RECOGNIZE command. Voice commands can be used to change letter keys to cursor keys and control cursor speed with voice pitch -- faster and easier than using a mouse or joystick. Other applications include voice-activated padlocks, telephone dialers, and aids for the physically handicapped.

To use the voice harp, the user can compose and perform music in real time by humming or whistling. The user's voice or whistle pitch will write the notes—including duration and rests.

The Voice Master for the Commodore 64 (specify disk or tape) is priced at \$89.95; for the Apple II, II+, or IIe, the price is \$119.95. The Sound Master only, with demo disk and 32-page manual, is available for \$39.95.—Covox, Inc., 675-D Conger Street, Eugene, OR 97402.

EDUCATIONAL GAME, *Torpedo Run*, is a simulation which presents eight historical World War II submarine missions in which the player sub confronts enemy surface vessels in the same sequence as actually occurred.



CIRCLE 24 ON FREE INFORMATION CARD

Players can compare their performances against that of the U.S. sub in those historic naval engagements.

Torpedo Run puts the player in the role of captain of a diesel electric submarine operating in the South Pacific. The player is challenged to develop good judgment, strategy decisions, and battle tactics. Constant on-screen display monitors such variables as speed, heading, depth, and remaining power and torpedo supply, and provide immediate data on enemy vessels. Enemy surface patrols drop depth charges. Increasing speed for underwater maneuvering risks depletion of electrical power. Surfacing to recharge batteries opens sub to attack.

It is interesting to speculate on how the actual submarine commanders might do with this game could they reenact the original missions.

Torpedo Run has a suggested retail price of \$39.95.—Brainpower, Inc.,

24009 Ventura Blvd., Calabasas, CA 91302.




CIRCLE 25 ON FREE INFORMATION CARD

LANGUAGE SERIES, *LINKWORD*, is available for all models of the Atari computer, as well as for the Commodore 64. The four programs in the series consist of Spanish, French, German, and Italian. *LINKWORD* uses a system based on imagery, linking foreign words to acoustically similar English words to provide an easy-to-remember visual association. Using both the computer program and the audio cassette, the student can expect to learn a basic 400-word vocabulary, plus grammar and pronunciation in about 10 hours. The suggested retail price of *LINKWORD* is \$24.95 for each language.—Artworx Software Company, Inc., 150 Main Street, Fairport, NY 14450.

EXTENDER BOARD, the model 3690-20, has test points for all 86 bus lines adjacent to the card connector for fast troubleshooting. Each line is marked for convenient identification.

The 9.00-inch long by 9.75-inch wide board is fabricated of 0.0625-inch thick FR4 epoxy-glass laminate, clad with two-ounce copper-plated bus lines. Bus lines are protected by a thick solder-mask coating to prevent short circuits during testing.

 Card-edge-connector contacts have a 10-micro-inch gold flashing over nickel plating, while receptacle con-



CIRCLE 26 ON FREE INFORMATION CARD

tacts incorporate 30-micro-inch gold inlays. The model 3690-20 is priced at \$50.70.—Vector Electronic Company, 12460 Gladstone Avenue, Sylmar, CA 91342.

SOFTWARE REVIEW

Dysan's "Interrogator."

■ A floppy disk drive is a precision device. Everything, from the rotational speed of the floppy disk—called the "Spindle Speed"—to the tolerances of the mechanism that positions the read/write head is measured in minute increments, and everything must come together with the same relationships each time the drive is used. Whether it's the first access, the tenth or the ten-thousandth, the read/write head must take exactly the same position(s) every time.

Insignificant variations in the speed of the disk or positioning of the read/write head can prevent a drive from reading disk files written earlier in the year, or files written by the computer at the next desk. It's the reason why disk files written by your office PC won't read on your home PCjr, and vice versa.

To insure that any drive can read the disks written by any other drive, floppy disk drives must be maintained within a narrow range of tolerance limits. Variations from these tolerances are termed *misalignment*.

Unfortunately, ordinary misalignment read/write problems which can be rectified by a moderately-priced alignment usually appear to the non-technical user as a computer malfunction or as a glitched disk, and many a dollar has been wasted on phantom computer repairs, just as many a perfectly good disk has been glitched attempting to "repair" or "recover" from a non-existent glitch. Yet all these problems and hassles can be easily eliminated in less than a minute by using a software package called *Interrogator* to evaluate a PC's disk drives.

Interrogator, which is produced by Dysan, the same company that manufactures high quality disks and the special test disks used by disk drive manufacturers and service technicians, consists of two 5¼ inch disks and an instruction manual. One disk contains a self-booting, menu-driven control program, the other disk is Dysan's Digital Diagnostic Disk (called a DDD), the same test disk used by disk manufacturers and service technicians. Together, they can evaluate the floppy drives of an IBM PC, XT or PC Portable, and can uncover potential disk drive problems before they begin to seriously affect writing and reading of the disk files.

To use *Interrogator* you simply load the self-booting control program and then replace the control program disk with the DDD disk. The DDD, which runs under control of the menu driven software, contains several test functions for such things as the spindle speed, alignment and positioning of the read/write head, and actual reading of test writes. Since most of the checks

and tests are intended for the service technician they are run as individual tests and the results are displayed graphically in a form understood by technicians, or by someone with an idea of how a disk drive works. For the layman there is a menu selection called *Auto Sequence Tests* that automatically steps the drive through the tests, displaying the test results in layman's rather than technical terms, also indicating by a single phrase whether the drive has passed or failed the tests (whether the drive is within predetermined tolerance limits). Any test result that does not fall within the range of the preset tolerance limits is highlighted so the user knows what test has failed.

The screen displays of the *Auto Sequence Tests* for each drive can be printed for side-by-side comparisons or for future reference. *Interrogator* even permits the user to type a short comment at the bottom of each display prior to printing.

At each step of the test selection and printing the user responds directly to on-screen prompts using only the function keys. It takes no technical skill, knowledge or even experience with a computer to use *Interrogator*.

The documentation works on two levels. It covers the layman's tests and what they represent, then progresses through an easily-understood discussion of a disk drive's parameters, and finally covers the use and interpretation of the technician-oriented checks.

A menu driven PROGRAM SETUP allows the user to change the default conditions of the disk drive's track-seek time, head-settle time, read/write retries, and the total sides tested: the *Auto* sequence tolerance limits: the program parameters (monochrome or color and sound on or off): and to create backup disks with user-determined setup values and parameters. As initially supplied, *Interrogator* is configured for a monochrome monitor, and while the color display is most decorative, it serves no functional purpose. Similarly, while it might appear there is some need to change the tolerance limits, the average user would have no reason to do so. While it's possible a disk-service technician might have some reason to change the tolerance limits, they are best left as they are. Although the use of *Interrogator* almost insures the compatibility of disk files between several IBM personal computers, it is also surprisingly effective at detecting the cause of intermittent read and write failures. For example, the computer on which this review was written has had a recent problem with intermittent reads and writes from the B: drive.

Interrogator disclosed that the drive was sluggish and out of tolerance when the computer was first turned on, but after several disk operations—what is called "exercising the drive"—the drive "pulled in." Knowing what was wrong, by exercising the B: drive until *Interrogator* showed all parameters to be within the accepted tolerance range, it was possible to avoid defective reads and writes until the computer could be freed for overhaul of the disk drives. Considering that the *Auto* mode runs a complete check in nominally 20 seconds, one could not ask for a more convenient way to check the system. —Dysan Corp., 5201 Patrick Henry Drive, Santa Clara, CA 95050. ◀▶

OPTICAL CHARACTER RECOGNITION

There are other ways to input than the keyboard—easier ways.

MARC STERN

■ If there's one thing you learn when you buy a microcomputer, it's this: the keyboard is a great input device, but sometimes you'll wish it were better. You usually realize this when you find a fantastic program which must be laboriously entered line-by-line from the keyboard.

Relief at hand

The need for alternative input methods is strong and the market points this out. At the moment, you can find digital pen tablets and bar code readers, as well as keyboards available for data input. Each offers its own advantages and, its drawbacks.

The bar code reader can accept input from Universal Product Code strips, but can't recognize handprinted or written data. Which brings us to an input alternative that can save you hours at the keyboard, the optical character recognition device.

The OCR

These can range from simple wand-like instruments that you draw across a typed or printed line, to sophisticated standalone devices which will read many typestyles and increase the versatility of any small-computer system. In fact, the key difference between the wand and the larger device is that the wand can recognize far fewer typestyles.

One of the most sophisticated units on the market—perhaps the most sophisticated—is manufactured by DEST Corp. of Milpitas, CA. DEST is one of the leaders in optical character recognition technology (OCR) and it offers this functionality in its WorkLess Station.

Looking like a standard office copying machine, the compact DEST device works automatically; recognizes over 100 characters from at least 10 typestyles, and inserts formatting codes for word processing programs. (See Fig. 1)

Shrinking technology

If you've been involved with computers for more than a couple of years, you've probably run across OCR readers. Typically, they were big units, standing as much



as three or more feet tall. That has changed.

For example, there's an OCR device made by Oberon which looks like a secretary's copying stand. It holds a piece of paper and you move the OCR head across the line of type. Then, there's the WorkLess Station, which occupies the desk space of a microcomputer system. That the manufacturers have

 


FIG. 1—THE DEST WORKLESS STATION is an example of today's advanced OCR technology. It is capable of recognizing about 10 typefaces, which cover the majority of typestyles used commercially. Because of this, it can accept a wide variety of printed input.

been able to achieve these size reductions is due to very large-scale integration technology which has taken the functions once handled by many computer boards and has put those functions on integrated circuit chips.

Further, these devices are smarter. In today's desktop, microprocessor-driven OCR device a 2,048-element linear photodiode array can recognize almost any typeface used commercially. This contrasts with older OCR devices which were limited to specially designed "computer" typefaces—Courier 10 and 12.

(In a recent test, in fact, a DEST unit recognized a typeface which it wasn't supposed to be able to recognize. The specifications on this unit, in fact, seem conservative. Although the company claims it will recognize 10 or so typefaces, chances are it will recognize many more.)

Intelligent character recognition

Now that we've established that OCR is a vital input technology, it's interesting to see how a typical system works.

For starters, this system is driven by an eight-bit microprocessor (MPU) unit—DEST uses an 8085. The MPU controls the entire device.

Take a look at Fig. 2 and you'll see—in block form—how the system works. The photodiode array sends its information to a video unit, which digitizes the input and which, in turn, sends it to a control unit and on to the isolation unit where the MPU is housed. The isolation unit is connected to an optional format unit, which takes the raw, digitized output and formats it into word-processor-compatible text output. It also sends the formatted data to the host computer system. If a character isn't recognized immediately, recognition, correlator and typestyle extender modules are brought into play.

In essence, that's the entire system, but, it's a good idea to explore its operation in detail so you'll have a better idea of how OCR technology works.

When the system operator first inserts a sheet of printed material into the OCR unit, it is scanned by a lamp which illuminates a mirror and lens and focuses the line on the photodiode array. The array receives a focused, one-pixel high reflection and each diode detects the amount of light corresponding to one pixel. The diodes turn this information into a series of voltages representing the data and these analog signals

usually contains the MPU, as well as a DMA controller. The rest of the circuitry contains serial to parallel conversion logic; 32K of read-only memory-based (ROM) character isolation routines; 32K of RAM, and a universal synchronous-asynchronous receiver/transmitter (USART) to communicate with the host computer system.

(The last feature makes this device system independent. It can be used with any small-computer system on the market that employs an RS-232C serial communications interface. Further, it can be immediately interfaced with that system, rather than requiring special interface cards or configuration routines. You can see the value of a universal type of input device.)

In operation, the isolation module of a typical OCR device isolates each character on a background frame. Some systems use a 24 by 32 pixel frame, which gives the system enough character definition to work with.

 


FIG. 2—PRINTED INPUT IS DIRECTED from a mirror to an array module which turns the pixel-high scan lines into their analog equivalents. From there, it is processed by a video board and sent through a controller module to the isolation module. The isolation module filters input and directs the digitized character flow to the recognition module and correlator board. These are the essential pieces of the OCR picture, although some units add optional format and extended typestyle modules.

are sent to the video module, where each pixel is digitized. (See Fig. 3)

That digitization determines whether the pixel is black or white and the information—similar to the image digitization in a facsimile machine—is sent through the control module to the isolation module where the image is stored in the unit's random access memory.

The isolation module is the heart of the unit. It

 


FIG. 3—USING A 2,048-ELEMENT linear photodiode array, an advanced OCR unit creates a series of one-pixel scan lines. The diode array detects the light. Each character occupies a 24 × 32 pixel matrix.

This type of definition is also great enough to compensate for skewed or bowed lines, close or touching characters or underlines.

When the system is finished isolating the particular character, it is sent to the recognition module, which, in conjunction with the correlator module, compares the characters to those stored in ROM. The recognition module contains RAM to store the still-unknown character and it contains a ROM-based recognition routine for the character identification. When the text is identified, it is sent to the computer in page form, using the RS-232C port. A format module can set this information up for a specific word-processing program if it is commanded to.

Character recognition

The heart of today's OCR device is the typestyle recognition routine stored in ROM. This can be permanent ROM or erasable programmable read-only memory (EPROM).

In general, these routines are generic and are capable of recognizing a wide variety of typefaces from many manufacturers. (See Fig. 4.) There are some limited OCR systems which require typeface-specific ROM for the device to work correctly, but today's sophisticated devices are capable of recognizing a great range. For example, the DEST system can recognize about 10 generic typestyles, which cover about 95 percent of the typefaces used today.

The typical advanced OCR system today uses a character-recognition system that is as much a filter as it

filtering out any speck that is smaller than the dot on an i. The filtering action also normalizes any letter stroke abnormalities.

The character-recognition routine is actually a matrix-type matching algorithm, a system such as that employed by DEST matches unknown characters with those stored in ROM templates. And, if the system fails to achieve a good match, the character is rejected until the best known-to-unknown character match is achieved. Interestingly, the program algorithm also has the capability of dealing with a duplicate match situation. If an unknown letter falls best not only under one A template in the program's memory, but that it also fits under another A category. In this situation, the algorithm determines which is the better fit and recognizes that letter.

But if the system still can't determine what letter a character is supposed to represent, the algorithm has a fail-safe built in, a context resolution system which it uses to distinguish among characters of similar shape.

For example, with some typefaces the digit 1 and the letter "l" and the digit 0 and letter "O" are almost indistinguishable.

In this situation, the program takes advantage of artificial intelligence techniques and resorts to deduction. Look at the price \$35.10 and the word still. In each case, there are characters that just can't be identified on the basis of their shape -- 0, "O", 1, "l."

Like someone using deduction in the numeric example, the program sees there is a 5 in the immediate vicinity and makes the determination that it is working with a number. It doesn't look at the decimal, but relies on positional information, instead. Since it does, it determines that a one and zero follow the decimal point. Likewise, using positional information, the algorithm sees an "i" before the two "ls" in still and therefore determines it is a word.

If the algorithm still can't determine a letter after all the filtering, the microprocessor in the system issues a reject-character code and sends it to the computer where it appears in the text. Since the algorithm recognizes most letters, it is easy for the computer user to search through and replace those characters with a word-processor's global search command.

Fortunately the occurrence of rejected letters is fairly rare. Statistics show they occur about once in 2000 characters. Further, those characters which might slip through the cracks in the recognition algorithm and which might turn up as incorrect letters are even more rare, on the order of once in 20,000 to 30,000 characters.

Special cases

Today's advanced OCR has a feature that earlier systems lacked, the ability to recognize an extended character set. For example, earlier and more limited systems usually can recognize 80 to 90 characters at a maximum. However, today's advanced system can recognize 100 or more.

Today's OCR device can now be used by the microcomputer user and it will be a welcomed addition, indeed. ◀◀▶▶

 


FIG. 4—THE CHARACTER-RECOGNITION ALGORITHMS in an advanced OCR device, such as that made by DEST, is generic. This means it is capable of recognizing a wide variety of typestyles from various manufacturers.

is a character-identifier. The algorithm used for character recognition also accommodates such things as ink splatter, copier specks and stroke-width variations. In this mode, it acts as a filter to take extraneous "noise" out of the picture. For example, let's say you are attempting to read a document loaded with copier specks. The device's programming makes allowance by

Electronics Paperback Books



SECRETS OF THE COMMODORE 64 \$5.00. Masses of useful info and programming tips not found in any user's manual.



INTRO TO PROGRAMMING THE ATARI 600/800 XL \$5.00. Perfect complement to the Atari user's manual. Even shows how to use animated graphics.




COMPUTER TECHNOLOGY EXPLAINED \$5.00. Explanations for computer terms often encountered. A dictionary for computer lingo.



INTRO TO Z-80 MACHINE CODE \$5.75. Speed up your programs. They may be harder to write, but it's worth learning how. Some demo programs are included.



 WHITE'S RADIO LOG \$5.95. Up-to-date directory of North American AM, FM, & TV stations. Includes section on world-wide shortwave stations.



25 SIMPLE AMATEUR BAND ANTENNAS \$5.00. All kinds of antennas for all kinds of amateur radio reception.



25 SIMPLE AMATEUR BAND ANTENNAS \$5.00. All kinds of antennas for all kinds of amateur radio reception.



25 SIMPLE AMATEUR BAND ANTENNAS \$5.00. All kinds of antennas for all kinds of amateur radio reception.



25 SIMPLE AMATEUR BAND ANTENNAS \$5.00. All kinds of antennas for all kinds of amateur radio reception.



25 SIMPLE AMATEUR BAND ANTENNAS \$5.00. All kinds of antennas for all kinds of amateur radio reception.



25 SIMPLE AMATEUR BAND ANTENNAS \$5.00. All kinds of antennas for all kinds of amateur radio reception.

Quality Paperbacks



LONG DISTANCE TV DXING \$5.00. A practical and authoritative introduction to this unusual aspect of electronics.



HOW TO DESIGN ELECTRONIC PROJECTS \$5.75. How to use standard circuit elements to make custom electronic projects.



HOW TO GET YOUR ELECTRONIC PROJECTS WORKING \$5.00. How to find the faults in your projects, repair them and get them working.



DESIGN & MAKE YOUR OWN PCB BOARDS \$5.75. Everything you need to know before you make printed-circuit boards for your projects.



INTERNATIONAL DIODE EQUIVALENTS \$5.75. Helps find replacements for rectifier diodes, triacs, thyristors, photo diodes and display diodes.



INTERNATIONAL TRANSISTOR EQUIVALENTS \$7.50. Locates possible substitutes for a popular user-oriented selection of modern transistors. Japanese, European and American types.




PRACTICAL ELECTRONIC BUILDING BLOCKS. Book 1 \$5.75. Build the blocks and then combine them to form almost any custom project of your choice.



PRACTICAL ELECTRONIC BUILDING BLOCKS. Book 2 \$5.75. Amplifiers of all kinds to add to the circuits from Book 1 of this series.



 THE SIMPLE ELECTRONIC CIRCUIT. Book 1 \$5.75. Elements of Electronics. Fundamental electronics theory.



ALTERNATING CURRENT THEORY. Book 2 \$5.75. Elements of Electronics. Needed for comprehension of speech, music, radio, TV and more.



SEMICONDUCTOR THEORY. Book 3 \$5.75. Elements of Electronics. Leads into transistors and other semiconductor devices.

Affordable Prices



SEMICONDUCTOR THEORY. Book 3 \$5.75. Elements of Electronics. Leads into transistors and other semiconductor devices.



HOW TO USE OP AMPS \$5.75. A source book of circuits and a reference book for design calculations.



ELECTRONIC SYNTHESIZER PROJECTS \$4.50. How to assemble the elements of a synthesizer and then put them all together.



ELECTRONIC TIMER PROJECTS \$5.00. Timing circuits to fit just about every application. Required for every experimenter.



SINGLE IC PROJECTS \$4.25. All projects in this book are based on one IC and are simple to construct. Great way to get started with ICs.



POPULAR ELECTRONIC PROJECTS \$4.75. A collection of a wide range of electronic projects and circuits for the experimenter.



IC PROJECTS FOR BEGINNERS \$5.00. Written especially for the less experienced experimenter. Complete parts layouts and wiring diagrams.



555 PROJECTS \$5.00. So useful that this IC has an unparalleled reputation. Here's a book full of useful applications.



POPULAR ELECTRONIC CIRCUITS. Book 1 \$5.75. More circuits for hobbyists. Audio, radio, test, music, household and more.



POPULAR ELECTRONIC CIRCUITS. Book 2 \$5.75. More circuits for hobbyists. Audio, radio, test, music, household and more.




POPULAR ELECTRONIC CIRCUITS. Book 3 \$5.75. More circuits for hobbyists. Audio, radio, test, music, household and more.

CHECK OFF THE BOOKS YOU WANT

BOOKS LISTED BELOW ARE 25% OFF REGULAR CATALOG PRICE



STEREO QUADRAPHONY HANDBOOK \$2.25

 

AUDIO ENTHUSIASTS HANDBOOK \$2.60



SOLID STATE NOVELTY CIRCUITS \$2.60




BUILD HI-FI AUDIO ACCESSORIES \$2.60



28 TESTED TRANSISTOR PROJECTS \$3.18



50 PROJECTS USING CA3130 \$3.35

 


PRACTICAL INTRODUCTION TO DIGITAL IC'S \$3.18



FIRST BOOK OF PRACTICAL PROJECTS \$2.80



MAJOR SOLID STATE HI-FI PROJECTS \$2.25

 

50 CIRCUITS USING DIODES \$2.80



IC LM3900 PROJECTS \$3.55



50 CIRCUITS USING 7400 IC'S \$3.35



50 SIMPLE LED CIRCUITS \$3.18



FIRST BOOK OF TRANSISTOR EQUIVALENTS \$2.80



ELECTRONIC PROJECTS FOR BEGINNERS \$3.75



50 FET TRANSISTOR PROJECTS \$3.35



BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS \$3.75



ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST \$3.75

THE MORE YOU BUY.....THE MORE YOU SAVE.....THE MORE YOU BUY.....

SPECIAL CLEARANCE SALE OFFER ENDS AUGUST 15, 1985

ELECTRONIC TECHNOLOGY TODAY INC.

P.O. Box 240, Massapequa Park, NY 11762-0240

Name _____

Address _____

City _____ State _____ Zip _____

*Canadian Shipping

Number of books ordered

Total Price of Books \$ _____

Sales Tax (NY State Residents) \$ _____

*Shipping in U.S. only (\$1.00 1st two books, 40c ea additional) \$ _____

TOTAL ENCLOSED \$ _____

WRITE- PROTECT NOTCH BY-PASS

*You paid for both sides of your disks.
Here's how to use both sides.*

NOEL NYMAN

■ If you own a single-sided floppy disk drive, you may have read that the opposite side of your diskettes can also be used to store data and programs. During manufacturing, all disks are tested for data recording integrity on both sides. Those not meeting manufacturer's standards on one side are packaged as single-sided disks.

Using the uncertified "backside" of disks isn't recommended for valuable data or for disks that will be read frequently. When you flip a disk over, the cleaning material inside the jacket may release particles of dust and oxide to the disk surface and corrupt your read/write head. Dual-sided drive owners don't have this problem: their disks turn in one direction only. However, many computer owners use this technique for archival or back-up disks which are read infrequently.

To write on a disk, the write-protect notch must be uncovered. On a single-sided disk, there is no write-protect notch for the back. Special punches are available that will cut a neat, square notch. Most users prefer to use a conductor's punch or a scissors. Using any of those methods may damage the disk jacket or warp the disk itself.


How it works

Here's how to modify your drive to electronically bypass the write-protect circuitry. We'll use the Commodore 1541 disk drive in our example, but the same idea should be adaptable to Atari drives or any other disk drive that doesn't use the small timing hole near the disk's center.

In most disk drives, the write-protect notch is sensed optically. An LED is mounted opposite a phototransistor with the write-protect notch lined up between them when the disk is inserted. If the notch is uncovered, the light from the LED causes the phototransistor to conduct.

On the Commodore 1541, this brings the write-protect line low (ground potential or near zero volts) and signals the drive circuitry that the disk can be written to.

 If a write-protect tab is in place, or there is no notch on the jacket, the light path is blocked and the



SMALL CIRCUIT BOARD with IC, switch and resistor all in place illustrates the simplicity of this circuit. It allows you to write to both sides of the disk with no need for punching holes.

transistor does not conduct. This leaves the write-protect line high on the 1541 and the drive will not write to the disk.

To bypass the circuit, hold the write-protect line low by shunting the phototransistor with a resistor. This is easy in most drives since the phototransistor is mounted on the drive mechanism and the leads from it plug into the circuit board. No changes are required on the circuit board itself.

Be careful!

You may want to wait until the warranty expires before attempting any modification. If possible, obtain a schematic of your drive from a dealer or repair service. The drive circuits use CMOS chips which can be damaged by improper handling. Use normal CMOS precautions when working around the circuit board.

First unplug all cables, then remove the top cover from the Commodore 1541 by loosening the four mounting screws accessed through holes in the bottom cover. Remove the metal shield that covers the circuit board. Two screws on the left side secure the shield.

Look for the largest plug, labelled "P6" on most boards. It is a 15-pin plug but only a few wires are connected. Counting from the back of the drive, locate pins 12 and 13. These are the wires coming from the

 


FIG. 1—IN ITS SIMPLEST FORM, the schematic above uses only a switch and resistor.

phototransistor.

To make sure you have the right wires, carefully bare the insulation near the plug and connect a voltmeter or logic probe to them. Pin 13 is the negative or ground side. Plug in the power cord and turn on the drive. Be careful not to touch the circuit board while the power cord is connected. The voltmeter should read near zero volts.

Put a disk part-way into the drive so the write-

protect area is blocked. The voltage should increase to almost three volts, a TTL logic one or high. If you get these readings, you have the proper wires.

Figure 1 is a diagram for installing a switch and resistor to bypass the phototransistor. A 2K resistor (R1) worked on the drives we tested, but you may have to try values between 1K and 2K to get reliable operation. Do not simply short the two wires together, as this might damage the phototransistor or other circuit components. If you mount the resistor directly to the switch, no separate circuit board or stand-offs will be required to hold it.

Additional circuitry

Although this simple modification will allow you to write to the uncertified side of the disk without punching notches in it, we recommend the circuit shown in Figure 2. This will flash the green "Power On" LED whenever the write-protect bypass switch is turned on.

We used the LM3909 (IC1) because it provides a bright LED flash at low voltage. This lets us use the 2 volts available at the green LED's plug directly with no

 


FIG. 2—MORE ELABORATE CIRCUIT is still not complicated, but accomplishes a great deal more. Resistor R1 might have to be changed. See text.

changes on the drive circuit board. Cut the red and black wires going to the green LED and connect them as shown in the schematic. You may want to use plugs and sockets to connect the circuit to the drive so you can remove it if you need to have your drive serviced.

Any double-pole, double-throw switch will work, but select one that will fit into the case past the drive chassis before you start punching holes. The switch we used is a miniature toggle that can be located almost anywhere. A slide switch might have been more compact, but would have required additional holes. The circuit board we used fits nicely in front of the "short" circuit board used in the newer 1541 drives and can be bolted to the unused circuit board mounting tab.

Once the switch and LED flasher are in place, test by trying to SAVE a program to a disk with a covered write-protect notch. With the switch in the on position,

the green LED should flash and the program will SAVE to the disk.

Avoid confusion

You should turn the switch on only when you SAVE to or format a disk with no notch. If the switch is left on, your drive can get very confused and give you strange errors. To illustrate this, turn the write-protect switch off, put a disk with an uncovered notch in the drive, and type the following in direct mode (Commodore only):

```
OPEN2,8,2,"X,S,W"
```

This tells the drive that we're about to write information to a sequential file we've called "X." The red LED should come on and stay on, indicating that a data channel is open to the drive. Now remove the disk from the drive. The red LED will go out. The drive "knows" that you've removed the disk and that the data

PARTS LIST

- IC1—LM3909 LED Flasher
- R1—2000 ohm, ¼ watt resistor
- C1—470µF Electrolytic Capacitor
- S1—SPDT Toggle Switch
- S2—DPDT Toggle Switch
- Circuit board, plugs and mounting hardware

channel shouldn't be held open.

Type: CLOSE2

To get rid of the open file in the computer, then try the same experiment with the write-protect switch on. This time, the red LED does *not* go out! The disk drive uses the high-to-low transition of the write-protect line as the back of the disk crosses the light path to tell that you've removed a disk. With the write-protect switch on, this line is held low and the drive doesn't see any change. If you change disks in this way, you will have difficulty LOADING files on the first try. More important, if you SAVE to the second disk, you may overwrite important data or programs because the drive will use the Block Availability Map of the previous disk.

Properly used, the write-protect switch will give you access to the back of your disks without the need for expensive punches or danger of damage. It also gives you a measure of security since there's no telltale notch to indicate that anything has been recorded on the back.

Using the electronic circuits shown here, you can write to the back of the disk at your own volition; you'll find this a great convenience if you haven't had this facility before. It effectively doubles the capacity of your disks.

However, it's always a good idea to mark or number your disks so you'll know which disks are written on both sides, and what information is contained on the backs. A separate sheet or ledger can be maintained as a menu so you can quickly and easily locate the information you require at any given time. You might also want to carefully clip one corner of the disk envelope so you can easily tap out any collection of oxides and/or debris that might accumulate in the envelope and possibly foul your heads. ◀▶

ADDING A HARD DISK DRIVE

Here's how to add that hard disk drive you've always wanted.

HERB FRIEDMAN

■As software for personal computers gets more complex, programs require greater storage capacity for the program and related data. Even the two-sided disk is hard-pressed to hold a complete program; the PC-DOS version of *WordStar* and its spelling checker, *CorrectStar* can't fit on one disk: They require two disks, and become a pain to run from conventional floppy disk drives.

The easiest, most cost-effective way to increase storage capacity for an IBM and some IBM-compatible personal computers is to retrofit the PC with a hard disk drive having at least 10 megabyte capacity. Although the hardware for 10MB of storage can cost you anywhere from a shade under \$800 to the price of a used car, higher cost equipment doesn't always make the system better: It often just makes it more expensive. (While hard disk systems of 15, 20 and even 30MB are available, their cost and capacity are often beyond what's needed by the average technician, so we'll restrict our comments to the 10MB equipment.)

Three kinds of installation

There are three ways to add a hard disk drive to a PC: 1) *Internally*—the hard disk drive replaces the computer's floppy B: drive; 2) *Externally*—the hard drive is in an external cabinet with its own power supply and the PC retains both of its floppy disk drives; 3) *Expansion-External*—the external hard disk unit also

has expansion slots for accessory adapters such as Asynchronous Communications and Parallel Printer Adapters.

As you might surmise, the least expensive hard disk retrofit is a straight internal replacement, while the most expensive is the expansion-external because it's going to have much of the same hardware as the original computer.

At the minimum you will need the hard disk drive and a hard disk controller, which is an adapter card that plugs into the computer, or the expansion unit. Although the hard disk drive and controller is the rock-bottom minimum configuration, the controller requires its own "long" expansion slot, which means the minimum PC configuration requires a floppy disk controller, a hard disk controller, and at least a monochrome or color monitor card: That's three slots out of a maximum of five before you add any other adapters. A multi-function card and an internal modem will fill the computer.

The internal hard disk drive

An internal hard disk drive replaces the computer's floppy B: drive. The capacity of a PC's 63 watt power supply is no longer a primary consideration when substituting a hard disk for a floppy because the new half-height hard disk drives, such as the "Qubie" (See Fig. 1) uses about the same power as the full-size floppy disk drive for which the PC was originally designed. A straight swap of a hard for a floppy drive does not require a heavier power supply even if the computer's expansion slots are fully loaded. But, a hard disk runs continuously—it does not cycle on and off like a floppy drive—so there is always a minimum power drain. If the computer is also equipped with a memory expansion adapter, extra serial ports, and an internal modem—another user of moderate continuous power—the 63 watts from a PC's power supply might be barely adequate for reliable operation.

The power supply let's you know if there's an overload condition by turning itself off. If your PC's power supply can't accommodate the extra continuous load of a hard disk, the least-expensive way to provide extra power capacity is through an auxiliary power

 


FIG. 1—MOST RETROFIT HALF-HEIGHT hard disk drives come with a full size front panel so the drive can directly replace a full size floppy disk drive.

 


FIG. 2—TO INSTALL THE HARD DISK simply unplug the cables from the floppy B: drive, remove the two screws that secure the drive and slide the floppy drive out of the cabinet, replacing it with the half-height hard disk.

supply for the hard disk drive that piggybacks on the rear apron. Qubie', and several other suppliers of hard disk units, sell "piggyback" power supplies specifically designed for retrofit hard disk drives. While you could just as easily replace the PC's power supply with a 130 watt unit, the piggyback supply is all you need, and it's about half the cost of a 130 watt retrofit or replacement power supply. (See Fig. 2.)

The external hard disk drive.

Although internal hard disks are relatively inexpensive and convenient to install—the hardware simply plugs together—they are often more trouble than they're worth because you lose the floppy B: drive (unless you also replace the A: drive with two half-height floppy drives, in which case the overall cost is going to get out of hand). The problems caused by loss of the B: drive can often prove insurmountable because much software is specifically intended for a data disk on drive B:, or works between drives A: and B: and won't run from a hard disk. Also, if you leave your computer connected to a telephone line for remote access via a modem, you leave the files on your hard disk exposed to unauthorized use: Someone can easily issue a **FORMAT** command and erase the hard disk's files.

All such problems are avoided by using an external hard disk unit, which can be nothing more than the

 


FIG. 3—IF YOU WANT AN EXTERNAL hard disk the drive can be installed in a conventional enclosure/power supply such as used for floppy drives.

same drive used for the internal installation, but in a separate cabinet with its own power supply (See Fig. 3). The connections are generally the same ribbon cables used for internal hard disks, only now they are passed from the hard disk controller, out the back of the computer, into the external hard disk cabinet. Normally, the cabinet and power supply for an external drive adds anywhere from \$200 to \$300 to the cost of the hard disk unit. You could do the same thing by using a conventional \$45 floppy disk cabinet/power supply from Software Support, Inc. (One Edgell Road, Framingham, MA 01701).

Although an external hard disk still requires a hard disk controller in the PC, you don't have to remove the B: drive, and more important, you can turn off the hard

disk by turning off its external power supply. (On boot-up the PC's POST (Power On Self Test) automatically determines if the hard disk is available.) If you now leave the PC connected on-line to the telephone only the A: and B: drives can be accessed; it's as if the hard disk doesn't exist at all. If you need to allow on-line access to some hard disk files, copy them to a floppy disk before putting the computer on-line.

 


FIG. 4—IBM's EXPANSION UNIT comes with a new BIOS ROM (on the conductive foam) and a removal tool which is used to extract the existing pre-March 1983 ROM.

External-expansion.

Unless your budget can afford replacing your present floppy disk controller with one of the combination floppy/hard disk controller adapters, you must give up one more expansion slot, leaving a maximum of three for everything else including the monitor. If you require greater expansion capacity the best option is a device called an *Expansion Unit*, which contains a power supply, one or two hard disk drives, the hard disk's controller, a *Receiver Card*, and up to five open expansion slots. Let's explain the *Receiver Card*. Some sort of "communications system" system is required to exchange signals between the computer and the expansion unit. This is accomplished through an *Extender Card*—a "transmitter"—in one of the PC's expansion slots, and a *Receiver Card* in the expansion unit: A multi-conductor cable interconnects the two.

 


FIG. 5—The expansion unit contains its own power supply, the controller, a Receiver Card, and one hard disk. An empty compartment (on the left) is provided for a second hard disk drive.

The "communications circuit" permits some of the PC's adapters, such as Asynchronous Communication Adapters, Parallel Printer Adapters, a Prototype Card, a Game Control Adapter, and the Hard Disk Controller to be moved to the expansion unit. The Monochrome Display/Printer Adapter, memory expansion adapters and the floppy disk controller can not be moved to an expansion unit (unless the expansion unit provides DMA—Direct Memory Addressing) See Fig. 4.

Although there are several hard disk expansion units in the marketplace, the best value will prove to be the IBM Expansion unit shown in Figure 5, because it comes in a complete kit that even includes a ROM module and a special IC tool.

Auto boot.

In order to access memory options of more than 544K and an Expansion Unit—to boot directly to a hard disk rather than Drive A.—an IBM PC requires a "late" BIOS ROM: the ROM installed in all PCs manufactured after March 1983. (The date of manufacture is attached to a cloth tag usually placed over the internal speaker wires.) If you purchase the IBM Expansion Unit the ROM is supplied in the kit along with a special tool used to remove the original ROM. (If you don't need the ROM you don't use it.) If you purchase a non-IBM Expansion Unit you don't get the ROM; instead, you usually get a software package containing a utility that allows the early model computer—usually called the PC-1—to recognize the hard disk after it boots from a floppy. Alternately, you could purchase an IBM ROM upgrade kit (under \$30) so the PC-1 boots directly from the hard disk.

Unfortunately, as many users have learned the hard way, IBM has undocumented and proprietary features in their BIOS: If you want a guarantee that most future software will work both the new ROM and a fully PC-DOS 2.x IB—compatible hard disk expansion unit is suggested. For maximum convenience, a hard disk unit should permit the computer to boot directly from the hard disk without need for utility software.

Programming the hard disk

If you use an IBM hard disk, or a fully IBM-compatible hard disk such as the Qubie', it will be automatically programmed as the next higher drive as determined by the computer's internal floppy drive selector switches: DIP switch sections SW1-7 and SW-8. If the DIP sections are programmed for two floppy drives—drives A: and B:—an IBM-compatible hard disk is automatically programmed as Drive C.; a second hard disk is automatically programmed as drive D:. If you want to use two RAMdisks (disk emulators) they will be drives C: and D:, and most RAMdisk software requires that DIP sections SW-7 and SW-8 be configured for four disk drives: two floppy and two RAMdisk; hence, the hard disk(s) will be automatically programmed as drive E: (and drive F:). While it really doesn't make any difference whether the hard disk is recognized as C: or E: (or anything else), some applications software which is intended for use on either a floppy or a hard disk specifically looks for the hard disk as drive C:. If your

computer's DIP sections program the hard disk as drive E: the software will never locate the disk files.

IBM has built some very cute "tricks" into the POST which tells you a lot about the condition of the hard disk. If the hard disk is internal—if it's part of the PC—the POST automatically recognizes it as device 1801. If there are any problems with the installation the numerals 1801 will appear in the upper left corner of the screen at power up. If no numerals show the drive is most likely functioning correctly. External hard disks are automatically recognized as device 1701. The nice part about auto-recognition is that if you forget to turn on the external hard disk's power supply POST indicates a 1701 error on the screen, reminding you to turn on the hard disk and reboot. (you must reboot for the computer to recognize a change in device configuration.) On the other hand, if you want your hard disk turned off the 1701 display let's you know for certain that it's off. (See Fig. 6.)



FIG. 6—THE COMPUTER CONNECTS to the Expansion Unit through a somewhat bulky connecting cable. The Expansion Unit can be disconnected by simply "pulling the plug."

If you install an internal hard disk retrofit and have any thoughts of eventually making it external make certain you have a BACKUP of everything on the hard disk because moving a hard disk into a new magnetic field—such as the power transformer of an external power supply—can glitch one or more tracks, sectors, or files. After you complete the external installation check both the DOS and your files for proper operation. If anything appears to have been glitched don't waste time trying to get it to work. Simply reformat the disk (which erases all data) and RESTORE the files from your BACKUPS; then avoid moving the hard disk unit because they are not as shock-resistant as the hard disk drives used for portable computers; shock and vibration can cause the head(s) to slam into the disk, damaging the magnetic surface and the recorded data. If you must move a hard disk unit, avoid the possibility of damage to the magnetic surface(s) by first *parking* the heads by running the *RELOCATION* program which is on the IBM DIAGNOSTICS that was supplied with your computer. The relocation program can be accessed as item No. 3 from the menu, or run the SHIPDISK.COM program on the diagnostics disk directly from PC-DOS. ◀▶

tion to be done, is to make sure that the switch-over to standby is completely glitch-free. No matter how well you design the rest of the procedure, if there's much bouncing at the +v pin at shutdown, you're sure to foul up the data stored in the memory.

Now that we have an idea of what must be done to use the standby feature of the IC, let's put it to practical use in the circuit we've been designing. The best way to set things up is to lock the operation of the **STANDBY** control, pin 17, to the **CHIP ENABLE**, pin 19. If we do that and sync them properly, as shown in Fig. 1, we'll be sure that the IC is put to sleep properly, and that the timing is correct. You'll note that an automatic back-up battery supply is shown separated from the rest of the circuit by dashed lines. It simply kicks in automatically when there is a power failure.

Note also that pin 17 and pin 19 are controlled by the same line on the data bus and are separated from each other by a spare inverter. (The inverter is one leftover from previous columns in this series.) If you look over the truth table of the 5101 (which appeared in the April "Drawing Board"), you'll see exactly what's going on.

As long as the line feeding the memory is kept low, the entire IC is enabled. That low also causes the inverter to output a high to pin 17, taking the IC out of the standby mode. A low sensed at pin 17 puts the IC to sleep. But that inverter does more than let us lock the operation of both control pins together.

Remember that we're concerned with both the state of those pins, and the order in which things happen. If we don't sync things properly, the IC will go to sleep, but the data will probably glitch. The propagation delay of the inverter makes sure that that part of the power down operation happens in the right order.

When a high is applied to pin 19, the entire IC is disabled. And later, after a propagation delay, the standby mode is chosen. That means we have to modify the schematic of the circuit we've been building over the last few months. By tying the operation of pins 17

and 19 together, we need only three of the lines coming out of IC6-b.

The last thing to consider in our demonstration circuit is what to do about the display. Unfortunately, standard display drivers are going to be somewhat inadequate. Unless you use oddball IC's, display drivers do really weird things when presented with straight binary data. Everything is fine as long as you stick to BCD. But if the most-significant bit is high, the display will usually be useless.

For our purposes, the easiest thing to do (as Fig. 2 shows) is to just hang LED's off the outputs. You can do the same thing on the outputs of the latches. That gives you a way to see what's happening on the address and data bus while keeping an eye on the state of the memory's control pins. (I'm the first to admit that that's a less-than-ideal solution.)

Getting standard display drivers like the 4511 or 7448 to deliver meaningful information when presented with straight binary is a tricky business.

Therefore, it's time to start another contest. The rules are really simple; I'm looking for the simplest, most elegant way to design a display driver circuit to produce displays like those shown in Fig. 3. It goes without saying that the winner will have the circuit published in **Radio-Electronics**. R-E

No previous experience necessary

LEARN PROGRAMMING



Master computers in your own home at your own pace in your spare time. Learn even before you decide on a computer.

BE YOUR OWN COMPUTER EXPERT

Programming is the best way to learn to use computers, and we can show you the best—and most economical—way to learn programming!

Send today for your free information package. No obligation. No salesman will call.

HALIX INSTITUTE
CENTER FOR COMPUTER EDUCATION DEPT. 497
1543 W. OLYMPIC, #226
LOS ANGELES, CA 90015-3894

YES! Send me free information on how I can learn about computers and programming at home!

Name _____
Address _____
City _____ State/Zip _____

Be an FCC LICENSED

ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Computers, Radar, Avonics and more! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School
This proven course is easy, fast and low cost! **GUARANTEED PASS** - You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90
P.O. Box 2223, San Francisco, CA 94126


Please rush **FREE** details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

SUPER LONG PLAY TAPE RECORDERS

10 Hour Model — \$95.00*
14 Hour Model — \$159.00*

 Modified Panasonic Slimline, high quality, AC-DC Recorders provide 5 or 7 continuous hours of quality recording & playback on each side of cassette for a total of 10 or 14 hours depending on model. Built-in features include • Voice level control • Digital counter, etc. TDK DC 180 Cassette Furnished.



PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up. **\$24.50***
FCC APPROVED



VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike. **\$24.95***
*Add for ship & hdg. Phone Adapter & Vox \$1.50 ea. Recorders \$4.00 ea. Cal. Res. add tax. Mail order, VISA, MIC, COD's OK. Money Back Guarantee. Qty. disc. avail. Dealer Inquiries invited. Free data.
AMC SALES INC. Dept. A 9335 Lubec St., Box 928, Downey, CA 90421 (213) 869-8519



CIRCLE 108 ON FREE INFORMATION CARD

10-to-1 ratio of R1 and R2, most of the line voltage is dropped across R1.

With the phone on the hook, the voltage appearing at pin 6 is about 4.5 volts, but when the phone is lifted from its cradle that value drops to about 1 volt. When that happens, IC1 outputs a high that follows two paths.

In the first of those paths, that high is fed to IC2-c (1/2 of a 4050 buffer) to provide sufficient drive to turn on (VMOS) transistor Q1. With that transistor turned on, LMP1 lights showing that a receiver is off the hook.

In the other path, the signal is fed to IC2-a, which outputs a high that causes capacitor C2 to charge. When C2 is charged, it triggers IC4-a (1/4 of a quad NAND Schmitt trigger) into conduction. The low output of IC4-a toggles JK flip-flop IC3, which then triggers the 7555 (CMOS) timer, IC5. The output of IC4-a is also fed to pin 11, RESET, of IC6 enabling it.

The timer produces a 1-Hz squarewave output that is fed to

IC4-d (pin 6), and to IC6 through IC4-c. Now IC6 begins to count, and after about 2048 seconds (or 34 minutes), pin 14 of IC6 goes high. That high is fed to IC4-d, causing its output to go low, which in turn causes the piezoelectric buzzer, PB1, to sound. The circuit is designed so that the buzzer continues sounding until either the phone is hung up, or the circuit is reset by pressing switch S1.

The circuit is powered by a 15-volt, 300-mA supply; and, since

the circuit is made of mostly CMOS IC's, power consumption in the standby mode is low. In operation, the lamp draws most of the power. If you want to reduce power consumption even more, the lamp may be replaced with an LED, allowing a power supply with a lower output to be used.

A word of caution: *Do not* earth-ground the circuit. Also, be sure that the power supply is isolated from the AC line.—William Stamile

Learn micro-processing with the new MICRO-PROFESSOR 1P



Students, engineers or technicians—upgrade your micro-processing skills with the new Micro-Professor 1P.

The MPF-1P features:

- complete software support
- more built-in memory
- improved keyboard
- larger display

Three tutorial guides help cover all capabilities. The ideal training tool! MPF-1P will deliver you into the growing world of micro-processing. Invest now!

Plus—FREE GIFT Only **\$179.95**

Check this box for FREE Z-80 Microprocessor Programming and Interfacing textbook when you order within 7 days. \$12.95 value. (Include \$5.00 postage & handling)

ETRONIX

Dept. RE0685
14803 N.E. 40th
Redmond, WA 98052

For immediate action call TOLL FREE:

1-800-426-1044

Full money back guarantee.



Radio-Electronics REPRINT BOOKSTORE

- | | | | |
|--|---------|--|---------------|
| <input type="checkbox"/> Build Your Own Satellite TV Receiver | \$7.00 | <input type="checkbox"/> Special Projects (Spring 1981) | \$4.50 |
| <input type="checkbox"/> 8-Ball Satellite TV Antenna | \$5.00 | <input type="checkbox"/> Special Projects #4 (Summer 1982) | \$4.50 |
| <input type="checkbox"/> Build Your Own Robot | \$12.00 | <input type="checkbox"/> Special Projects #5 (Winter 1983) | \$4.00 |
| <input type="checkbox"/> TV Descrambler (January, February 1981) | \$3.00 | <input type="checkbox"/> Special Projects #6 (Spring 1983) | \$4.00 |
| <input type="checkbox"/> Radio-Electronics back issues (1984) | \$3.00 | <input type="checkbox"/> Special Projects #7 (Summer 83) NOT AVAILABLE | |
| <input type="checkbox"/> Radio-Electronics back issues (1983) | \$3.50 | <input type="checkbox"/> Special Projects #8 (Fall 83) | NOT AVAILABLE |
| (January, February, May 1983 not available) | | <input type="checkbox"/> Special Projects #10 (Spring 84) | \$4.00 |
| Write in issues desired | | <input type="checkbox"/> Radio-Electronics Annual 1983 | \$3.50 |
| <input type="checkbox"/> Radio-Electronics back issues (1982) | \$3.50 | <input type="checkbox"/> Radio-Electronics Annual 1984 | \$2.50 |
| Write in issues desired | | <input type="checkbox"/> How to Make PC Boards | \$2.00 |
| <input type="checkbox"/> Radio-Electronics back issues (1981) | \$4.00 | <input type="checkbox"/> All About Kits | \$2.00 |
| (Jan., Feb., March, Dec. 1981 not available) | | <input type="checkbox"/> Modern Electrics (Vol. 1. #1 | \$2.25 |
| Write in issues desired | | April 1908) | |
| <input type="checkbox"/> Etch your own PC boards | \$3.00 | <input type="checkbox"/> Electro Importing Co. Catalog | \$4.95 |
| <input type="checkbox"/> Hands On Electronics #1 | \$3.00 | (1918) (176 pp) | |
| <input type="checkbox"/> RE Annual '85 | \$2.50 | <input type="checkbox"/> Low Frequency Receiving Techniques | \$6.00 |
| <input type="checkbox"/> VCR Repairs | \$3.00 | Building and using VLF Antennas | |
| <input type="checkbox"/> IBM Typewriter to | | <input type="checkbox"/> New ideas - 42 circuits for experimenters | \$3.75 |
| Computer Interface | \$3.00 | | |

To order any of the items indicated above, check off the ones you want. Complete the order form below, include your payment, check or money order (DO NOT SEND CASH), and mail to Radio-Electronics, Reprint Department, 200 Park Ave. South, New York, NY 10003. Please allow 4-6 weeks for delivery.

If you need a copy of an article that is in an issue we indicate is unavailable you can order it directly from us. We charge 50¢ per page. Indicate the issue (month & year), pages and article desired. Include payment in full, plus shipping and handling charge.

ARTICLE _____

PAGES _____

MONTH _____

YEAR _____

TOTAL PAGES _____

@50¢ each

TOTAL PRICE _____

MAIL TO: Radio-Electronics

Reprint Department, 200 Park Ave. South, New York, NY 10003

All payments must be in U.S. funds

Total price of order	\$ _____
Sales Tax (New York State Residents only)	\$ _____
Shipping & Handling (U.S. & Canada only) (Includes FIRST CLASS POSTAGE) \$1.00 per item	\$ _____
All other countries (\$2.00 per item, sea mail)	\$ _____
(\$4.00 per item, air mail)	\$ _____

Total Enclosed

Name _____

Address _____

City _____ State _____ Zip _____

STATE OF SOLID STATE

A new series of CMOS counters

COUNTERS ARE AMONG THE MOST useful digital-logic circuits. They can receive uniform pulses (representing units to be counted) and develop a voltage that is proportional to the number of pulses input. That makes them useful for such applications as measuring time, period, or frequency.

LSI Computer Systems has introduced a new series of complementary CMOS divider IC's (a divider, of course, is a counter that produces an output for every n^{th} input pulse, instead of for every input pulse). The five new devices, which have been dubbed the RED series, and their functions are: RED 5/6, divide by 5 or 6; RED 50/60, divide by 50 or 60; RED 100/120, divide by 100 or 120; RED 300/360, divide by 300 or 360, and RED 3000/3600, divide by 3000 or 3600.

The counters are used as time-base generators operating from either 50- or 60-Hz line frequencies. They produce outputs ranging from 10 pulses per second (RED 5/6) to 1 pulse per minute (RED 3000/3600), depending on the particular IC.

The devices feature low power dissipation and high noise immunity and can operate from supplies

 


FIG. 1

 


FIG. 2

of from +5 to +15 volts. The output is low-power TTL compatible when the IC is operated from a +5-volt supply. The clock input can accept a 50 or 60 Hz sinewave directly thanks to the inclusion of an onboard pulse shaper. The output is in squarewave form, except for the RED 5/6 when used in the divide by 5 mode. Inputs, in addition to the clock input, include 50-/60-Hz division select, input enable, and reset. All of the inputs are protected.

Figure 1 is a pinout of the RED series counters. The devices are identical in all but one respect—the number of Johnson-type decade counters used in the output. For instance the RED 5/6 uses a single counter, while the RED 50/60 uses two counters. Figure 2 shows the counter-timing diagram. Note that the counting will always be proper if, as at points A through E, the reset and enable signals are allowed to switch only when the input clock is low.

The counter advances by one count on each negative transition of the input clock, as long as the ENABLE is high and RESET is low. When ENABLE is low, the input clock pulses are inhibited and the counter is held in the state it was in prior

to switching. A high reset signal clears the counter to zero. A low on the DIVISION SELECT pin causes a divide by 6, 60, 120, 360, or 3600, depending on the counter being used. A high on the DIVISION SELECT pin causes a divide by 5, 50, 100, 300, or 3000.

The units are priced as follows: RED 5/6 and RED 50/60 devices, \$1.65; RED 100/120, RED 300/360, and RED 3000/3600 are \$1.95, each in lots of 1 to 24. For orders of less than \$25.00, add \$5.00 for shipping and handling. For the RED series data sheet, contact—LSI Computer Systems, Inc., 1235 Walt Whitman Rd., Melville, NY 11747

New low-dropout regulator


A positive voltage regulator that can source output-current up to 1.5 amperes with an input/output differential of typically 0.65 volt is now available from National Semiconductor. The latest addition their line of regulators, the LM2940CT-5.0, features an output current in excess of 1 amp that, along with the low dropout voltage, makes it useful in applications where the input voltage is kept at a level within a volt or two of the output.

The device is a plug-in replace-



ROBERT F. SCOTT,
SEMICONDUCTOR EDITOR

 **SOME OF THE
GREATEST
THINGS IN
AMERICA
NEVER CHANGE.**



SOME DO.



Now paying 10.94%.

U.S. Savings Bonds now pay like money market accounts! At the current rate—10.94%—you could double your money in less than seven years. Just hold Bonds for five years and you get the new higher variable rates. Plus, you get a guaranteed return. That's the kind of change anyone can appreciate.

But some of the best things about Bonds haven't changed. Savings Bonds are still as safe as ever. They're still exempt from state and local income taxes. And since Bonds cost as little as \$25, they're as affordable as ever. What's more, Bonds remain a great way to keep our country strong.

You can purchase Bonds almost anywhere. At neighborhood banks, savings and loans and credit unions. Or easier still, right through the Payroll Savings Plan where you work.

For your free booklet, write: "50 Q&A," U.S. Savings Bonds Division, Washington, DC 20226.

U.S. SAVINGS BONDS
Paying Better Than Ever

Variable rates apply to Bonds purchased on and after 11/1/82 and held at least 5 years. Bonds purchased before 11/1/82 earn variable rates when held beyond 10/31/87. Bonds held less than 5 years earn lower interest.

ment for similar NPN-type regulators and is pin-for-pin compatible with the LM340. Its guaranteed accuracy is $\pm 3\%$ at 25°C . The LM2940CT-5.0 is ideal for use in battery-powered applications and in automotive applications where large transient voltages, such as ± 45 volts, can be expected.

Its features include internal short-circuit current limiting, thermal-overload protection, low quiescent current, reverse-battery protection, and a trimmed output voltage. Other voltage options are soon to be made available. Housed in a TO-220 package, the LM2940CT-5.0 sells for \$0.95 in lots of 100 or more.—National Semiconductor Corp., 2900 Semiconductor Drive, Santa Clara, CA 95051.

CMOS and TMOS technologies combined

The SMARTpower II device is a Motorola innovation that combines the best qualities of high-speed CMOS logic and high-current TMOS vertical power structuring into a single IC.

The MPC2005 can handle up to 15 amperes of continuous anode current, but is also capable of discharging capacitors with peak currents to 150 amps. When voltages exceed 6.2 volts or the junction temperature rises above 125°C , the device trips and removes the voltage from the system.

The MPC2005 can protect voltage-sensitive systems and memories on 5-volt buses from over-voltage transients and extreme temperatures that can damage the system. The device dissipates extremely low amounts of power in the off state, hence, it can be used to protect temperature sensitive devices since its junction temperature is essentially the same as that of the case.

The device includes a pin that can be used to set the trip-point to a level other than the pre-set 6.2 volts. A capacitor can be connected to the pin to change the delay time of the trip voltage. A single MPC2005 can replace three resistors, an SCR, and an IC. Priced at \$4.50 in lots of 100 and up, it is available from Motorola Semiconductor Products, P.O. Box 20912, Phoenix, AZ 85036. R-E

McIntosh®

Get all the newest and latest information on McIntosh stereo equipment from McIntosh Laboratory.

XL 1 Speakers



MR 500 Tuner
MC 502 Amplifier
C 504 Preamplifier



C 33 Stereo Preamplifier



MC 2255 Stereo Power Amplifier

Send For Your Stereo Information

McIntosh Laboratory Inc. RE
East Side Station P.O. Box 96
Binghamton, N.Y. 13904-0096

Name _____

Address _____

City _____ State _____

Zip _____

Phone Area Code _____

CIRCLE 67 ON FREE INFORMATION CARD

ANTIQUE RADIO



RICHARD D. FITCH

Servicing your antique radio

TO MANY OF YOU WHO HAVE GROWN up in this age of transistors and integrated circuits, the vacuum tube is a total stranger. And even some of us "older guys," have forgotten much about that old friend. But if you expect to get your antique radio working, you have to know a little something about the "antiques" inside it. In this month's column, we'll show you how to check tubes, and give you some other pointers to help you get your old radio back into action.

Testing tubes

Back in the early days of radio, any good radio repairmen kept a complete stock of tubes in his repair kit. To complement his tube assortment, the repairmen usually carried a tube tester, much like the ones shown in Fig. 1. Such units could test about 100 tubes of various size and pin configurations. The tester came with a tube chart on a single card that told the user how to set the various switches to test different tube types.

When restoring old radios, a tube tester is a handy instrument to have around, but it isn't absolutely necessary. Continuity checks can be used to see whether

 


FIG. 2

the tubes are usable. Such a test can tell you if the tube should be discarded, but not necessarily if it is good, and certainly not whether it's weak.

Checking the continuity of old radio tubes can be done with an ohmmeter or simple continuity tester. Before you start removing the tubes, however, check to see if there is a tube-placement diagram either inside the cabinet or beneath it. A diagram can at least cut down on the problems that you are likely to encounter. If no placement diagram is found, you can make your own as you remove the tubes.

A word of caution: Make sure that the set is turned off and unplugged before removing any chassis component (the reason for that is obvious). Test all or as many components as you can with your ohmmeter or continuity tester.

Figure 2 shows some of the most popular vacuum-tube pin configurations. The pins shown in bold are the filament pins.

Using your ohmmeter, check for continuity of the tube filament. If there is continuity between the two filament pins, that portion of the tube is probably OK. Then check to see that there is infinite resistance (no continuity) between the other pins (elements). If continuity exists between two tube elements, or between a filament and an element, the tube is shorted, therefore it should be discarded. A shorted tube can knock out several other components.

There are, of course, components other than tubes in an old radio. Most of those, such as resistors, capacitors, and transformers, you are familiar with—they function just like their mod-



FIG. 1

ern day counterparts. Their appearance, though, may be slightly different.

One of those differences in appearance should be noted here. Modern resistors use the banded color-coding scheme that we are all familiar with. Older units do not use banding, but they do make use of the same coding scheme. On those older units, the main body-color represents the first digit, the color of the tip of the resistor is the second digit, and the multiplier is signified by the color of a dot or band at the middle of the unit.

Also, the leads on older tubular electrolytic capacitors used a color-code, of sorts. In those, the black lead was usually negative, while the colored lead was positive.

Beginning in the early 1930's, some manufacturers have followed a standardized wiring color code. If applicable, that information might be found on the parts-location diagram. Be aware, however, that colors fade with time, and any repairs in the intervening years may have led to different-color wiring being used. Thus, the knowing the wiring color code used in your set is likely not to be a great help, and it could be a hindrance (due to fading, those "tan" or "brown" wires may very well have started out being wires of a quite different color).

Troubleshooting the audio

Dust, corrosion, dampness, and time take their toll on old radios, and any one of those factors can cause your radio to fail to operate satisfactorily.

Operational antique radios have a wonderful tone that's quite unlike that of any of today's sets. If the volume in your set is OK, but the sound is horrible, all is not lost; it is often possible to restore your radio's good sound quality.

Hum is probably the most common problem found in the audio of old radios. It is most often caused by age and non-use. While an audible hum is present in all old sets, it should not be loud enough to be heard when the set is tuned to a station. An audible hum doesn't necessarily mean that

there's a serious problem.

Scratchy sounds, during tuning, can almost always be traced to the plates of the tuning capacitor. The wafer-thin plates should mesh, but never touch. Dust can build up between the plates and cause distortion. Clean between the plates with a brush or vacuum cleaner.

Bent plates or foreign objects between the plates (paper clips, coins, etc.) are common problems in old radios that have been lying idle for many years. Corrosion on the trimmers can cause distortion or off-frequency problems.

Distortion in superheterodyne radios can often be traced to the IF transformers. Corrosion or damaged mica in the trimmers can upset the frequency and send assorted noises through the loudspeaker. Make sure that the metal transformer-shielding is firmly attached to the chassis.

Sometimes you'll hear a crackling sound coming through the loudspeaker, which may be due to arcing in the IF. To find out if that's what is happening, just turn off the lights, "crank" up the set, and look down the little hole on top of the IF shield. If you see sparks, you've found the trouble.

All the parts in the speaker assembly play an important part in the quality of the sound produced by old radios, including the diameter of the speaker cone. Torn speaker cones—a common occurrence to old radios—can be repaired with speaker cement. Of course, you can use tape to temporarily patch the cone, but tape can dry out and peel off, or cause distortion.

An off-center voice coil can cause a scratching noise whether the set is being turned on or off. The coil can be checked by lightly pressing the cone to see if its movement is smooth. If not, the speaker is probably damaged. That may have been caused by warping due to dampness, or by the speaker being dropped. On some early sets, the "spider" (the flat, springy object that holds the apex of the speaker's cone) can be adjusted to compensate for poor-quality sound. If there are no adjustments possible, then the speaker must be replaced. R-E

IF YOU OWN A CABLE TV DESCRAMBLER

THE NEW FEDERAL LAW
EFFECTIVE DEC 29, 1984
APPLIES TO YOU.
BEFORE YOU FALL FOR
"MISLEADING" ADVERTISING
GET THE FACTS!!!


SEND \$9.95 IN CHECK OR
MONEY ORDER TO:

CONSUMER CABLE PRODUCTS
794 FRANKLIN AVE.
FRANKLIN LAKES, NJ 07417

PROTECT YOURSELF
THIS IS INFORMATION
YOU CANNOT AFFORD
TO BE WITHOUT.

mail service only

ELECTRONIC COMPONENTS

 

MANUFACTURERS OF QUALITY ELECTRONIC COMPONENTS

- BATTERY CLIPS & HOLDERS
- CABLE SETS • CONNECTORS • CAPACITORS
- DISPLAYS • LEDs • FUSES • JACKS & PLUGS
- KNOBS • LAMPS • POTENTIOMETERS
- RF COILS • RELAYS • RESISTORS
- SWITCHES • SEMICONDUCTORS • SPEAKERS
- TEST EQUIPMENT • TRANSFORMERS • TOOLS
- WIRE & CABLE

OVER 15,000 DIFFERENT ITEMS IN STOCK!

- Sales and Order Desk
Open from 8:00a.m. (PST)
- TERMS: C.O.D., Visa,
MasterCharge
(Open Accounts Available)
- Phone and Mail
Orders Welcome
- Catalogs Mailed
Outside USA
Send \$2.00

MOUSER ELECTRONICS
11433 WOODSIDE AVE. SANTEE, CA 92071
PHONE (619) 449-2222 TWX 910-331-1175

CIRCLE 117 ON FREE INFORMATION CARD

SERVICE CLINIC

Testing capacitors

HOW MANY TIMES HAVE YOU WISHED that you had a good capacitor tester, but talked yourself out of buying one, figuring that it isn't needed often enough to justify the expense? Well, the fact is, if you have a scope on your workbench, you *have* the best capacitor checker there is at your disposal!

A scope, like the one in Fig. 1, can instantly tell you whether any capacitor in the set that you are working on is doing its job. And it doesn't matter whether the unit is a 4000 μ F electrolytic or a teeny-weeny ceramic capacitor.

 


FIG. 1

How, you may ask, do you use a scope to test capacitors? Easy! With the scope's vertical gain-control set for greatest sensitivity, touch the probe tip to the hot terminal of the capacitor and observe the scope trace. Most of the time you can use the standard low-capacitance probe to do that test, though there are times when a demodulator probe can be used to good advantage.

Checking capacitors

To test capacitors using a scope, you must first know what job the unit was put in the circuit to do. In TV sets, generally speaking, ca-

pacitors fall into three basic groupings—bypass, coupling, and filter.

Bypass capacitors are used to filter out the AC component of a signal. Such capacitors are always grounded at one end. But, what about filters?—they too are grounded at one end. Well, you might say that a filter capacitor is nothing more than an over-sized bypass capacitor. Filter capacitors are used to remove the hum and RF from a circuit by passing those signals to ground.

Coupling (or blocking) capacitors are usually found in circuits where both AC and DC voltages are present, or where some component of the input signal must be kept from the following stage. A good example of where a coupling capacitor might be used is in multi-stage amplifiers. In such applications, the capacitor is placed between the individual stages to block DC or some other undesirable component of the signal voltage, while passing only the AC or desired signal.

One thing to keep in mind is that no matter what the capacitor's function, you'll be looking for the absence or presence of a signal. If the capacitor is a bypass, for example, there should be no AC signal on the hot lead (the end connected to positive). If you see anything at the positive terminal other than a nice straight line, you've found a problem. On the other hand, if the unit is used as a coupler, there should be signals at both ends of the capacitor.

An undesired signal on the hot end of a bypass means that the unit is open. If you see any signal, bridge the old capacitor with an-



JACK DARR

other known to be good, and watch the scope to see if the signal disappears. If it does, the test is conclusive; the bypass is open.

Defective bypass capacitors can cause such problems as feedback, oscillation, streaks and wriggles on the screen, and many others too numerous to mention. And since (as we've already said) a filter is just a big bypass capacitor, the same testing method can be used to catch problems that we often fail to associate with filter capacitors. Unlike bypasses, however, filters usually do pass some ripple voltage; the amount of that ripple is usually shown on the schematic and is almost never more than 1.5-volts P-P.

Filter capacitors do a lot of the RF bypassing in the B+ return circuit. If the capacitor develops a high power-factor, it ceases to be a good RF bypass. Such problems do not always show up when using a standard capacitor tester to check the component, unless your tester has a power-factor test. However, a scope catches it every time—just look for signals (RF, IF, or even audio) on the hot end of the component.

Such signals can cause a feedback loop, which then leads to a myriad of different problems, like those mentioned. A high-power factor means that the AC series resistance of the capacitor has gone up, and that is where the problems come in. Now, instead of shunting (passing to ground) the undesired signal, the signal is blocked from ground by the increased resistance. However, if there is no perceptible signal on the hot side of the capacitor, even at the highest

gain level of your scope, the capacitor is OK.

There will be times when the problem is not really in the capacitor itself. For example, some time ago, I worked on a set in which the IF was oscillating. I checked the screen bypass capacitor on the second IF, and found signals on the screen grid. Figuring that that was the problem, I replaced the 0.05 μ F screen bypass capacitor. But after putting in the new unit, there still was oscillation.

My next thought was that it must be a bad ground connection. (The ground lead of the original bypass went all the way around the socket, to a solder lug on the other side.) While poking around with a small screwdriver, the oscillation stopped. I had accidentally grounded the lead of the capacitor right at the end of the case.

The long ground lead evidently had enough inductance at 45 MHz to cause the oscillation. Grounding it right at the end of the case did the "trick." The original capacitor was perfectly good. The only thing I couldn't figure out was how the set had worked fine for so long (it was by no means new).

So, remember: The next time you get a TV set with mysterious wriggles or beats in the picture, reach for your scope. It's a great time saver, so use it! R-E

SERVICE QUESTIONS

REPLACEMENT NOT AVAILABLE

In one of your "Service Clinic" articles, it was mentioned that subbing a V.S. 23JS6 replacement tube for a Toshiba brand is not advisable in sets that use 280 volts on the cathode. But since I couldn't get a Toshiba tube, I put in a V.S. replacement anyway. However, it blew out within three months. Any ideas?—M.G., Maywood, NJ

My thought is to remove the filament connections to 23JS6 tube, and in place of those connections, put a 40-ohm, 15-watt resistor (so much for keeping the series-filament string intact). Then replace the 23JS6 tube with a 6JS6, heated from a separate 6.3-volt AC, filament transformer. The cathode

will have less tendency to break down with no ground return.

SHADED RASTER

The Sears set that I've been working on has a black bar running down the left side of the screen. I've tried replacing the blanking diode, but that hasn't helped. Adjusting the brightness and contrast controls, moves the bar. I'm sending you my voltage readings to look over; hopefully you can see something that I've missed.—R.G., Quebec, Canada

The voltages that stick out like a sore thumb are those at the collectors of the three color outputs—they're too low! Capacitor C251 (a 200-volt filter), if open, will lower the 200-volt supply and also cause a shaded raster (which is what I think you have).

Now as to your question about replacing the blanking diodes: Whenever working around the horizontal frequency, it's important to use fast-acting diodes, such as the GE511. R-E

im

The Professional Test Equipment Source

The Instrument Mart

295 Community Drive, Great Neck, New York 11021
(516) 487-7430 Outside N.Y. (800) 645-6535

Sales, Service, Rental/Leasing Programs
... and Pre-Owned Test Equipment also Available


R_x

For *Profitable Video Camera Service*

Fix no. 101

Instrument Mart gives you the professional equipment and know-how to do the job!

 ...Like the Leader Sync/Test Generator, Vectorscope and Waveform Monitor. Used by Sony, Panasonic, Zenith and many more for factory authorized in-warranty service. Available at very competitive prices.



Call today, toll-free, 800-645-6535

plus FREE

Video Cameras: Theory and Servicing

with any purchase of \$1,000. Just mention this ad. A 260 page book with over 300 illustrations and photos. A practical "how-to" approach to video camera service for the VCR serviceman. Written in simple language by one of the industry's most respected experts. An outstanding value that will remain in your shop as the in-house expert long after the salesman leaves.

Dispense as written.

M.D. The Instrument Mart

PHILIPS

FLUKE

LEADER Instruments Corp

Tektronix

KEITHLEY

HITACHI

BECKMAN

Simpson

Polaroid

WATSON

ASSOCIATED RESEARCH, INC.

DATA PRECISION

HAMEG

POWER DESIGNS

YEW

WESTON

SOLTEC CORPORATION

... and Pre-Owned Test Equipment also Available

Fix no. 101

Call today, toll-free, 800-645-6535

PEST REPELLERS

continued from page 62

 


FIG. 4—IF YOU WISH TO VARY the duty cycle while keeping the frequency constant, replace the timing resistors with a single potentiometer.

 


FIG. 5—IF YOU WISH TO VARY the frequency, but keep the duty constant, at about 50%, the 555 circuit can be modified as shown.

equal at all times.

Returning to our basic circuit, the power amplifier, IC3, may be any convenient type with response reaching into the ultrasonic region. You might consider using a low-power IC amplifier such as the Sprague ULN3705 or 3784B, or the National LM380, LM383, or LM384.

The output transducer may be an inexpensive tweeter. Piezoelectric types should be given special preference. You'll find several appropriate transducers listed in the catalogs put out by many of the mail-order firms advertising on the back pages of this magazine.

When experimenting with ultrasonic frequencies, be aware that if the frequency is too close to the audible range, the signal may be annoying, and possibly painful, to house pets and some people—particularly girls and young women. Due to the nature of ultrasonics, those effected may not be aware of the source of this discomfort. So, be alert to the condition of those around you when you are experimenting. **R-E**

TACH/DWELL METER

continued from page 57

Finally, the three input leads may be installed. Ideally, they should be color-coded, to aid in their identification. Use a red lead for the connection to +12 volts and use a black lead for the connection to ground. Use a white lead for the signal input from the points.

Because you are probably going to be using the meter in a rough environment, be careful with your construction practices. For example, use strain reliefs for the power and signal-input wires, and mount the switches in easy-to-get-at locations. After you calibrate the instrument, use a dab of fingernail polish to hold the potentiometer in place.

Calibration and operation

To calibrate the meter, a squarewave generator with an output of at least 10 volts peak-to-peak is needed. It should be set to 100 Hz and the signal fed to the input of the meter. The meter should be set at the eight cylinder, high-tach (rpm x 100) range. Adjust R9 until a readout of 1500 is obtained. Check the settings of the other cylinder settings. The six-cylinder setting should produce a reading of 2000, and the four-cylinder setting should produce a reading of 3000 rpm.

To check the low-tach range (rpm x 10) set the generator to 30 Hz. The readings should now be: 450, 600, and 900 for the eight-, six-, and four-cylinder settings, respectively. No calibration of the Dwell function is necessary.

You're now ready to use your meter the next time you want to tune up your car. Consult the owner's manual or shop manual for your car (or the information sticker under the hood) for the specifications for your car and the proper way to adjust the points and engine rpm. Then just connect the red lead to the positive battery terminal, the black lead to ground, and the input lead to the output of the breaker points (or, where applicable, the output of the electronic ignition system). **R-E**



"Brilliant, Master but is it a marketable application of VLSI technology?"

HITECH IBM PC/XT

continued from page 46

The system we'll describe uses several multi-function adapter cards. That will allow us to leave open 5 of the 8 expansion slots. From a standpoint of comparison, the IBM PC XT without the addition of any monitor or display adapter card(s) already has 3 of the available 8 slots in use. The addition of the color graphics and monochrome display adapter cards will increase the load to an additional 2 slots leaving only 3 available slots for any accessories and expansions you might have in mind. The suggested parts listing and cost for the system is described in Table 5.

Note that our computer uses a parallel printer port rather than the RS-232C port present on the IBM PC XT. That doesn't mean that you have to. We made that choice because we already had a parallel printer on hand, and because we were using a plug-in modem card. But the combination floppy-disk controller/printer-port board is available in either configuration. One of the advantages of putting your own computer together is that you can control the selection and actual configuration of options for it.

Figure 3 shows the basic internal arrangement of the case. The case is of all metal construction with the needed brackets for mounting the drive(s) welded into position. The areas reserved for both the floppy drive(s) and the hard disk drive are supplied with pop-out plastic panel covers (front) which will be removed as the respective drives are installed.

The first phase of construction will deal with the motherboard as shown in Fig. 4. During these steps we will:

- Configure DIP Switch SW1
- Locate and install the ROM
- Locate the power input connector
- Locate the RAM area and expand to 256K if desired.
- Locate power connector JP1

Position the board on your work surface with the expansion slots facing up and to your left. We will be setting configuration DIP Switch located near U20 on the PC board. Because of the possible variations in physical appearance of this switch, refer to Fig. 5 for guidance as to switch positions and settings. Your switch may or may not have the ON position marked. If it does not, ON will be in the position of the arrow. A ball-point pen might be useful in setting this switch.

We'll tell you how to assemble and configure your computer next time. But before we go, let's mention that the parts listed in Table 5 can be obtained from: HiTech International, Dept. RE, 1180 Milraloma Way, Suite M, Sunnyvale, CA 94086. (408) 738-0601. **R-E**

MARKET CENTER

PLANS AND KITS

CATALOG: Hobby, radio broadcasting, CB, lowfrets. Transmitters, linears, active antennas, converters, scramblers, bugging devices, more! **PANAXIS**, Box 130-F7, Paradise, CA 95969.

DESCRAMBLER plans. New design decodes gated sync suppressed signals—newest pilotless method. Circuit boards, most parts from Radio

Shack. Detailed theory, drawings, schematics, instructions \$14.95 plus \$2.00 shipping. **DIRIJO CORP.**, Box 212, Lowell, NC 28098.

1000 plus commercial equip. schematics for sale in 30 areas including CATV, videogame, radar detector, burglar alarm. Send S.A.S.E. with your field of interest for category list and specific items in your field. **BOMARC SERVICES**, Box 1113, Casper, Wyoming 82602.

CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

Radio-Electronics Classified Ads, 200 Park Avenue South, N.Y., N.Y. 10003

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$20.00.

() Plans/Kits () Business Opportunities () For Sale
() Education/Instruction () Wanted () Satellite Television

Special Category: \$20.00

PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$37.50)
16 (\$40.00)	17 (\$42.50)	18 (\$45.00)	19 (\$47.50)	20 (\$50.00)
21 (\$52.50)	22 (\$55.00)	23 (\$57.50)	24 (\$60.00)	25 (\$62.50)
26 (\$65.00)	27 (\$67.50)	28 (\$70.00)	29 (\$72.50)	30 (\$75.00)
31 (\$77.50)	32 (\$88.00)	33 (\$82.50)	34 (\$85.00)	35 (\$87.50)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted.):

Card Number

Expiration Date

Signature

IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.

CLASSIFIED COMMERCIAL RATE: (for firms or individuals offering commercial products or services) \$2.50 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS.** 5% discount for same ad in 6 issues; 10% discount for same ad in 12 issues within one year; if prepaid. **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$2.00 per word, prepaid....no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) **50¢ per word additional (20% premium).** Entire ad in boldface, **add 20% premium** to total price. **TINT SCREEN BEHIND ENTIRE AD:** add 25% premium to total price. **TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD:** add 45% premium to total price. **EXPANDED TYPE AD:** \$3.75 per word prepaid. All other items same as for STANDARD COMMERCIAL RATE. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD:** add 25% premium to total price. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD:** add 45% premium to total price. **DISPLAY ADS:** 1" x 2 1/4"—\$270.00; 2" x 2 1/4"—\$540.00; 3" x 2 1/4"—\$810.00. **General Information:** Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 15th of the third month preceding the date of the issue. (i.e., August issue copy must be received by May 15th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding working day.

CABLE-TV Converters: Jerrold products include "new Jerrold Tri-Mode", SB-3, Hamlin, Oak VN-12, M-35-B, Zenith, and more. UHF Deluxe II kits. (Quantity discounts) 60 day warranty. Repairs of cable converters. For fast service C.O.D. orders accepted. Send S.A.S.E. (60 cents postage), or call for info. 1 (312) 637-4408. **HIGGINS ELECTRONICS**, 5143 W. Diversey, Chicago, IL 60639. No Illinois orders accepted.

KITS! Sound effects generator, capacitance meter, C64 drum machine, stereo scratch filter, and more. Semi-assembled and tested. Free literature. **GRAYCO**, 1024 Lancer, San Jose, CA 95129.

LEARN by building functional reed relays and proximity switches. Design your own burglar alarm system, etc. Send for our free price list. **ALLREED**, 138 5th Ave., Suite 160, Pelham, NY 10803.

NEW antenna invention. Delivers extremely great performance on all HF and VHF bands. Perfect for Ham, CB—or for monitoring police, fire, and short-wave. Also extremely effective for VHF television and AM/FM radio. Total parts cost less than \$10.00, and are easily obtainable. For complete construction manual send only \$20.00, postpaid to: **R. CHRISTIE**, 215-28 Spencer Ave., Queens Village, NY 11427.

CONVERT AM/FM pocket radios to receive short-wave, FM 2-meter Ham, police, aircraft. For more info send S.A.S.E. to **HOWARD BAILEY**, 115 Manor Place, Santa Cruz, CA 95060.

CB MODIFICATIONS

Increase channels, range, privacy! We specialize in frequency expanders, speech processors, FM converters, PLL & slider tricks, how-to books, plans, kits. Expert mail-in repairs & conversions. 16-page catalog \$2.

CBC INTERNATIONAL, P.O. BOX 31500RE, PHOENIX, AZ 85046 (602) 996-8700

COMMODORE kits, C-64, VIC-20. **Eprom programmer:** programs 2732, 2764, 27128, etc., \$79.90/kit, \$99.00/A&T. **Speech Synthesizer:** Includes extensive vocabulary or create your own \$44.90/kit, \$54.90/A&T. Kits include all hardware, software, P.C. boards, documentation. Specify machine and tape or disk. **H&H ELECTRONICS**, P.O. Box 50111, Tulsa, OK 74150.

QUALITY printed-circuit boards. 15 cents sq-in.. Free drilling. Quantity discounts, **INTERNATIONAL ENTERPRISE**, 6452 Hazel Circle, Simi Valley, CA 93063.

EXPERIMENTERS! 40KV from any ignition coil using our solid state driver kit, \$24.95. Catalog \$1.00. **NESTRONICS**, P.O. Box 611, Tobyhanna, PA 18466.

DESCRAMBLER plans. Gated sync suppressed signal. Newest design, **everything** Radio Shack. Complete drawing-theory, parts list, PC layout, instructions. Send \$15.00, **HENRY PRICE**, P.O. Box 835, Leland, NC 28451.



REMOVES VOCALS FROM RECORDS!

Now You can sing with the world's best bands! The Thompson Vocal Eliminator can remove most or virtually all of a lead vocal from a standard stereo record and leave the background!

Write or call for a free brochure and demo record.

LT Sound, Dept. R-1, P.O. Box 338, Stone Mountain, GA 30086 (404) 493-1258

Quality Microwave TV Antennas

Multi-Channel 1.9 to 2.7 GHz
40dB Gain True Parabolic 20 Inch Dish
Complete System \$84.95 (Shipping incl.)
Dealerships, Qty. Pricing, Replacement Parts

Phillips-Tech Electronics
P.O. Box 34772 • Phoenix, AZ 85067
(602) 947-7700 (\$3.00 Credit all phone orders!)

LIFETIME WARRANTY MasterCard • Visa • COO's

ATTENTION ELECTRONIC TECHNICIANS

Highly Effective Home Study BSEE Degree Program for Experienced Electronic Technicians
Our New Advanced Placement Program grants Credit for previous Schooling & Professional Experience. Advance Rapidly! Our 40th Year FREE DESCRIPTIVE LITERATURE!

Cook's Institute of Electronics Engineering
P.O. BOX 20345, JACKSON, MS 39209

LEARN how to use a computer. Train at home in spare time! No previous experience needed! Learn computer programming, computer applications and operations...even computer games. Use hundreds of programs already available or learn to write your own. Experts explain everything in easy-to-understand language with step-by-step directions. Call for free facts! 1-800-862-6262, extension 56, or write **ICS COMPUTER SCHOOL**, Dept. DEC65, Scranton, PA 18515.

BUSINESS OPPORTUNITIES

MECHANICALLY inclined individuals desiring ownership of small electronics manufacturing business—without investment. Write: **BUSINESSES**, 92-R, Brighton 11th, Brooklyn, NY 11235.

YOUR own radio station! AM, FM, cable. Home operation possible. **BROADCASTING**, Box 130-F7, Paradise, CA 95969.

BIG PROFITS ELECTRONIC ASSEMBLY BUSINESS

Start home, spare time. Investment knowledge or experience unnecessary. **BIG DEMAND** assembling electronic devices. Sales handled by professionals. Unusual business opportunity.

FREE: Complete illustrated literature
BARTA, RE-O Box 248
Walnut Creek, Calif. 94597

WANTED

INVENTIONS, ideas, new products wanted! Industry presentation/national exposition. Call free (1-800) 528-6050. Arizona, (1-800) 352-0458. X831.

ELECTRONIC assembly business requires additional contracts and new products. Very competitive due to low labor cost and large export incentives. **GOMAR**, A.A. 26, Manizales, Columbia, S.A.

REEL-TO-REEL TAPES

AMPEX professional series open reel tape, 1800- or 2400-feet on 7-inch reels, used once. Case of 40, \$45.00. 10½ × 3600 feet and cassettes available. MasterCard/Visa. **VALTECH ELECTRONICS**, Box 6-RE, Richboro, PA 18954 (215) 322-4866.

INVENTORS!

CAN you profit from your idea? Call us today regarding the marketing of your invention, or write for your free information package. Over a decade of service. **AMERICAN INVENTORS CORPORATION**, 82 Broad Street, Dept. RE, Westfield, MA 01086, (413) 568-3753. (Not an answering service.) Offices nationwide.

DO-IT-YOURSELF TV REPAIR

NEW!...Repair any TV...Easy. Anyone can do it. Write, **RESEARCH**, Rt. 3, Box 601 BR, Colville, WA 99114.

EPROM PROGRAMMING

HOBBYISTS: Pretested **EPROM's** sold with your programming installed. Program listing provided. Fast service. Write or call: **ROMULUS MICRO-CONTROL**, Box 8669, Rockville, MD 20856, (301) 540-8863.

Don't let your lungs go to pot.

Smoking marijuana is a lot more dangerous than you think. And a lot less cool.

AMERICAN LUNG ASSOCIATION
The Christmas Seal People®

Space contributed by the publisher as a public service

EDUCATION & INSTRUCTION

F.C.C. Commercial General Radiotelephone License. Electronics home study. Fast, inexpensive! "Free" details. **COMMAND**, D-167, Box 2223, San Francisco, CA 94126.

MASTERCARD AND VISA are now accepted for payment of your advertising. Simply complete the form on the first page of the Market Center and we will bill.

"INCREASE YOUR MEMORY WITH 64K DRAM MEMORY CHIPS"

Return this ad for your complimentary catalog

SPECIAL OF THE MONTH

Computer chips

4116 16K 150 NS \$.95
4164 64K 150 NS \$ 2.15
41256 256K 150 NS \$14.60

CALL FOR QUANTITY PRICING

Books • Breadboard & Accessories • Capacitors • Chemicals • Connectors • Crystals • Plugs & Jacks • Enclosures • Fans • Filters • Fuses • Heat Shrink Tubing • Heat Sinks • Kits • Knobs • Peripherals • Probes • Opto • PCB Products • Potentiometers • Power Supplies • Relays • Resistors • Cable Assemblies Sockets

Active

YOUR ELECTRONIC COMPONENT CENTER
MAIL ORDERS
PROCESSED WITHIN 24 HRS

SELF SERVE STORES

US
WESTBOROUGH MASS. (617) 366-9684
BELLEVUE WASH. (206) 881-8191

CANADA
MONTREAL (514) 731-7441
DOWNSVIEW (416) 630-0400
OTTAWA (613) 728-7900
EDMONTON (403) 438-5888
TORONTO (416) 977-7692
VANCOUVER (604) 438-3321
CALGARY (403) 295-5300

U.S. 1-800-361-5884
U.S. 1-800-343-0874

REPLACEMENT FOR

ECG®/GE®/SK®

TRIPLERS Min 3 Pc/Type	OUTPUT TRANSISTORS 5 Pc Min 100 Min
500A/GE527/SK3304..... 9.95	165/SK3115/GE38..... 2.25 1.95
523/GE528/SK3306..... 9.95	238/GE37/SK3710..... 2.25 1.95
526A/GE521/SK3306..... 9.95	283/SK3467..... 2.75 2.25
528/SK3906..... 12.75	25D1341P/1500V/7A..... 2.25 1.90
529/GE529/SK3307..... 11.80	

AUDIO POWER	RECTIFIER DIODES
10 Pc Min 100 Pc Min	100 Pc Min 1000 Pc Min
152/SK3893 .30 .24	125 1000V/2.5A .07 .05
153/SK3274 .30 .24	156 1000V/5A .18 .14
196/SK3054 .49 .44	506 Damper-Hi Volt Fast Recovery .29 .22
197/SK3083 .59 .54	
291/SK3440 .49 .44	
292/SK3441 .49 .44	

SPECIAL OF THE MONTH

375/SK9118 44¢ 10 Pc Min 39¢ 100 Pc Min.
712 TV Sound/IF FM/DET/ 75¢ 10 Pc Min 60¢ 100 Pc Min.

SUPER SAVINGS

10 MIN	100 MIN	10 MIN	100 MIN	10 MIN	100 MIN
85..... .21 .18	159..... .16 .11	189..... .50 .45			
102A..... .35 .29	160..... .88 .77	190..... .59 .50			
108..... .18 .14	161..... .65 .50	191..... .65 .55			
123A..... .18 .14	162A..... 2.25 1.95	198..... .65 .53			
123AP..... .13 .09	163A..... 2.35 1.99	199..... .18 .12			
128..... .38 .33	171..... .49 .39	234..... .19 .13			
129..... .38 .33	184..... .38 .30	287..... .29 .22			
130..... .59 .53	185..... .38 .30	288..... .29 .22			
154..... .75 .65	187..... .48 .40	376..... .55 .49			
157..... .49 .39	188..... .50 .45	398..... .59 .49			

FOR A COMPLETE LIST CALL OR WRITE—C.O.D. Orders Welcome (Min. Order \$25)

DIGITRON ELECTRONICS
110 HILLSIDE AVENUE, SPRINGFIELD, NEW JERSEY 07081
Toll Free 1-800-528-4928 In NJ 201-379-9016 Telex 138441
PRICES SUBJECT TO CHANGE WITHOUT NOTICE. OFFER GOOD WHILE SUPPLY LASTS.
ECG is a Trade Mark of Philips ECG.
Digitron Electronics is not associated in any way with Philips ECG.

WE HAVE QUALITY PARTS, DISCOUNT PRICES AND FAST SHIPPING!

TRANSFORMERS

120 volt primaries




5.6 VOLTS @ 750 MA	\$3.00
6 VOLTS @ 150 MA	\$1.25
12 VCT @ 200 MA	\$2.00
18 V. @ 650 MA	\$3.50
18 VOLTS @ 1 AMP	\$4.50
24 VOLTS @ 250 MA	\$2.50
24 VCT @ 1 AMP	\$4.50

LINE CORDS

TWO WIRE
6' 18ga TWO WIRE
3 FOR \$1.00

THREE WIRE
8 FOOT 18ga THREE WIRE
\$2.00 EACH

MIKE CONNECTOR

 


5 CONDUCTOR IN-LINE PLUG AND CHASSIS MOUNT JACK. TWIST LOCK STYLE. SAME AS SWITCHCRAFT 12CL5M. \$2.50 PER SET

7 CONDUCTOR RIBBON CABLE



SPECTRA-STRIP RED MARKER STRIP. 28 GA STRANDED WIRE. \$5.00 PER ROLL (100 FT.)

REVERBERATION UNIT

 

ACCUTRONICS COIL SPRING TYPE UNITS. USED IN ELECTRONIC ORGANS TO PROVIDE ACOUSTIC DELAY SOUND EFFECTS. INPUT IMPEDANCE 8 OHMS, OUTPUT IMPEDANCE 2250 OHMS. 4 1/2" x 16 1/2" x 1 1/2"

\$7.50 EACH

WALL TRANSFORMER

ALL ARE 115 VAC PLUG IN




4 VDC @ 70 MA	\$2.00
6 VAC @ 500 MA	\$3.50
6 VDC @ 750 MA	\$6.50
9 VDC @ 500 MA	\$5.00
9 VAC @ 1 AMP	\$3.00
12.5 VAC @ 265 MA	\$2.50
17 VAC @ 500 MA	\$4.00
24 VAC @ 250 MA	\$3.00

MULTI-SWITCHES

3 STATION NON-INTERLOCKING
3 - 2PDT SWITCHES. EACH OPERATES INDEPENDENTLY.
1 1/4" BETWEEN MOUNTING CENTERS.
\$1.75 EACH

METER

0 - 15 V.D.C.

 

THIS 2-1/4" SQUARE METER MEASURES 0-15 VDC. \$4.50 EACH

2K 10 TURN

MULTI-TURN POT SPECTROL #MOD 534-7161
\$5.00 EACH

SOUND AND VIDEO MODULATOR FOR T.I. COMPUTER



T.I. # UM1381-1. DESIGNED FOR USE WITH T.I. COMPUTERS. CAN BE USED WITH VIDEO SOURCES. BUILT-IN A/B SWITCH. CHANNEL 3 OR 4 SELECTION SWITCH. OPERATES ON 12 VDC. HOOK UP DIAGRAM INCLUDED.
\$10.00 EACH

SPRING LEVER TERMINALS

TWO COLOR CODED TERMINALS ON A STURDY 2 3/4" x 3 3/4" BAKELITE PLATE. GREAT FOR SPEAKER ENCLOSURES OR POWER SUPPLIES.
\$1.00 EACH 10 FOR \$9.00



5 STATION INTERLOCKING

MADE BY ALPS. 3 - 2PDT AND 2 - 6PDT SWITCHES ON FULLY INTERLOCKING ASSEMBLY. 3/4" BETWEEN MOUNTING CENTERS.
\$2.50 EACH



SUB-MINIATURE D TYPE CONNECTOR



SOLDER TYPE SUB-MINIATURE CONNECTORS USED FOR COMPUTER HOOK UPS.
DB-15 PLUG \$2.75
DB-15 SOCKET \$4.00
DB-15 HOOD \$1.50
DB-25 PLUG \$2.75
DB-25 SOCKET \$3.50
DB-25 HOOD \$1.25

ROTARY SWITCH

1 POLE 6 POSITION
1 1/4" DIA x 1 1/2" HIGH
75¢ EACH
10 FOR \$6.00



48 KEY ASSEMBLY FOR T.I. COMPUTER



NEW TEXAS INSTRUMENTS KEYBOARD. UNENCODED. 48 S.P.S.T. MECHANICAL SWITCHES. TERMINATES TO 15 PIN CONNECTOR. SOLID METAL FRAME 4" x 9".
\$6.50 EACH 2 FOR \$11.00

TI SWITCHING POWER SUPPLY

TI # 1053214-2
COMPACT, WELL-REGULATED SWITCHING POWER SUPPLY DESIGNED TO POWER TEXAS INSTRUMENTS COMPUTER EQUIPMENT.
INPUT: 14VAC-25 VAC AT 1A
OUTPUT: +12VDC AT 350MA
+ 5VDC AT 1.2A
- 5VDC AT 200MA
SIZE: 4 1/4" x 4 1/4" x 1 1/4" \$5.00 EACH



"PARALLEL" PRINTER CONNECTOR



SOLDER STYLE 36 PIN MALE USED ON "PARALLEL" DATA CABLES.
\$5.50 EACH

PUSHBUTTON POWER SWITCH



DOUBLE POLE POWER SWITCH PUSH-ON, PUSH-OFF.
\$1.00 EACH

EDGE CONNECTORS

ALL ARE .156" SPACING

10 PIN EDGE CONNECTOR
TRW #50-10-A-20 \$2.00 EACH

120V INDICATOR



NEON INDICATOR. RATED 120 V 1/3 W. MOUNTS IN 5/16" HOLE... RED LENS.
75¢ EACH
10 FOR \$7.00
100 FOR \$65.00

FREE! → SEND FOR **NEW 1985** 48 PAGE CATALOG ← **FREE!**

13.8 VOLT REGULATED POWER SUPPLY

THESE ARE SOLID STATE FULLY REGULATED 13.8 VDC POWER SUPPLIES. ALL FEATURE 100% SOLID STATE CONSTRUCTION, FUSE PROTECTION, L.E.D. POWER INDICATOR.
2 AMP CONSTANT, 4 AMP SURGE.
UL LISTED \$18.00 EACH



RELAYS

SOLID STATE RELAY
HEINEMANN ELECTRIC #101-5A-140-5 AMP CONTROL: 3-32VDC LOAD: 140WAC 5 AMPS SIZE: 2" X 1 1/4" X 4" HIGH
\$5.00 EACH 10 FOR \$45.00



COMPUTER GRADE CAPACITORS



2,000 mfd. 200 VDC 13/4" DIA. x 5" HIGH \$2.00
3,600 mfd. 40 VDC 13/8" DIA. x 3 3/4" HIGH \$1.00
6,400 mfd. 60 VDC 13/8" DIA. x 4 1/4" HIGH \$2.50
31,000 mfd. 15 VDC 13/4" DIA. x 4" HIGH \$2.50
72,000 mfd. 15 VDC 2" DIA. x 4 3/8" HIGH \$3.50
185,000 mfd. 6 VDC 2 1/2" DIA. x 4 1/2" HIGH \$1.50
CLAMPS TO FIT CAPACITORS 50¢ ea.

SLIDE POTS


100K linear taper 2" LONG 1 5/8" TRAVEL 75¢ EACH
500K linear taper 2 7/8" LONG 1 3/4" TRAVEL 75¢ EACH
DUAL 100K audio taper 3 1/2" LONG 2 1/2" TRAVEL \$1.50 EACH



L.E.D.'S STANDARD JUMBO DIFFUSED

RED 10 FOR \$1.50
GREEN 10 FOR \$2.00
YELLOW 10 FOR \$2.00

 FLASHER LED 5 VOLT OPERATION RED JUMBO SIZE \$1.00 EACH
BI POLAR LED 2 FOR \$1.70



DC CONVERTER



DESIGNED TO PROVIDE A STEADY ±5 VDC @ 240 MA FROM A BATTERY SUPPLY OF 3.5 TO 6.25 V.
2 1/16" X 1 1/16" X 1 1/16" HIGH. \$1.50 EACH

1N4148 SPECIAL

45" SPACING P.C. LEADS
1000 FOR \$10.00
10,000 FOR \$85.00



MINIATURE 6 VDC RELAY



SUPER SMALL SPDT RELAY. GOLD COBALT CONTACTS.
RATED 1 AMP AT 30 VDC; HIGHLY SENSITIVE. TTL DIRECT DRIVE POSSIBLE. OPERATES FROM 4.3 TO 6 V. COIL RES. 220 OHM.
1 3/16" x 13/32" x 7/16" AROMAT # RSD-6V
\$1.50 EACH 10 FOR \$13.50


CRYSTALS

CASE STYLE HC33/U
COLORBURST 3579.545 KC
2 MHZ \$3.50 EACH \$1.00 EACH




METAL OXIDE VARISTOR

 POPULAR GE # 130LA10A VARISTOR. 5/8" DIAMETER. \$1.25 EACH



LED HOLDERS

 
TWO PIECE HOLDER FOR JUMBO LED 10 FOR 65¢ 200 FOR \$10.00
CLEAR CLIPLITE HOLDER MAKE LED A FANCY INDICATOR. CLEAR. 4 FOR \$1.00



TRANSISTORS

2N706	4 FOR \$1.00
2N2222A	3 FOR \$1.00
PN2222	4 FOR \$1.00
2N2904	3 FOR \$1.00
2N2905	3 FOR \$1.00
2N2907	3 FOR \$1.00

KEY ASSEMBLY 5 KEY

 

\$1.00 EACH
CONTAINS 5 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 3 3/4" LONG

6 KEY
\$1.25 EACH
CONTAINS 6 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 4 1/4" LONG.

13 VDC RELAY



CONTACT: S.P.N.C. 10 AMP @ 120 VAC ENERGIZE COIL TO OPEN CONTACT...
COIL: 13 VDC 650 OHMS SPECIAL PRICE \$1.00 EACH

MINIATURE TOGGLE SWITCHES

ALL ARE RATED 5 AMPS @ 125 VAC

S.P.D.T. (on-on)
P.C. STYLE. NON-THREADED BUSHING. 75¢ EACH 10 FOR \$7.00

S.P.D.T. (on-off-on)
SOLDER LUG TERMINALS. \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00

S.P.D.T. (on-on)
P.C. LUGS. THREADED BUSHING. \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00

D.P.D.T. (on-on)
SOLDER LUG TERMINALS. \$2.00 EACH 10 FOR \$19.00 100 FOR \$180.00




3 1/2" SPEAKER



8 OHM IMPEDANCE, FULL RANGE SPEAKER. 8 OZ MAGNET. 4" DIAGONAL MOUNTING CENTERS.
\$2.50 EACH
10 FOR \$20.00

8" P.A. SPEAKERS

 

C.T.S. MODEL 883079 \$5.00 EACH
8 OHMS COIL
3.0 OZ FERRITE MAGNET CASE OF TYPICAL RESPONSE RANGE: 8 SPEAKERS 100 - 10,000 HZ. \$32.00
POWER RATING 15 WATTS MAX.
DRILLED TO MOUNT LINE MATCHING TRANSFORMERS.

4 PDT RELAY



14 pin style
3 amp contacts
24 volt d.c. or 120 volt a.c. coil
Used but fully tested \$1.70 EACH
specify coil voltage
LARGE QUANTITIES AVAILABLE
SOCKETS FOR RELAY 50¢ each

SOLID STATE BUZZER



STAR #SMB-06L. 6VDC. TTL COMPATIBLE. \$1.00 EACH 10 FOR \$9.00

ALL ELECTRONICS CORP.

TOLL FREE ORDERS ONLY 1-800-826-5432 (ORDER ONLY) (IN CALIFORNIA: 1-800-258-6666) ALASKA, HAWAII, OR INFORMATION (213) 380-8000

905 S. VERMONT AVE. P.O. BOX 20406 LOS ANGELES, CA 90006
6228 SEPULVEDA BLVD. VAN NUYS, CA 91411

QUANTITIES LIMITED MINIMUM ORDER \$10.00 USA: \$3.00 SHIPPING FOREIGN ORDERS INCLUDE SUFFICIENT SHIPPING CALIF RES ADD 6.12 NO C.O.D.

SECOND LOCATION!

JULY 1985 85

Power Problems?

AEGIS™ Power Conditioning Equipment... THE SOLUTION! Protects Computers & High-tech Equipment From Damaging Voltage Surges, Lost Data, & Costly Down Time.

SURGES! SPKES! RFVEMR! BLACKOUTS! BROWNOUTS!

SPIKE-SPIKER®
Transient Voltage Surge & Spike Suppressors & Noise Filters • Eleven Models—All Models Rated 120V, 15A
Priced From \$29.95

LINE-SAVER™
Standby Uninterruptible & Emergency Power Systems. Self-Contained Batteries, Compact Design, Completely Automatic.
Priced From \$495.00

Call or write for free literature.
Dealer inquiries invited.

INSTANT ORDER LINE
800-524-0400
TWX 501-651-2101
IN PENNA. 215-837-0700

KALO®
6584 Ruch Rd., Dept. re
Bethlehem, PA 18017
MADE IN USA

FOR SALE

CABLE-TV Secrets—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers list included. \$8.95. **CABLE FACTS**, Box 711-R, Pataskala, OH 43062.

RESISTORS ¼W, ½W 5% C.F. 3 cents. 1% metal-films, custom wirewounds, capacitors and other components. **JR INDUSTRIES**, 5834-H Swancreek, Toledo, OH 43614.

FREE catalog featuring scanner accessories, carrier/subcarrier detectors, voice scramblers, unusual kits. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520.

THE Intelligence Library—Restricted technical information & books on **electronic surveillance, surveillance-device schematics, lock-picking, investigation, weapons, identification documents, covert sciences**, etc. The best selection available. **Free brochures**. **MENTOR**, (Dept. Z), 135-53 No. Blvd., Flushing, NY 11354.

WHOLESALE MATV/CATV equipments, antenna, accessories, cartridges, radios, speakers, cables. (718) 897-0509, **D&W**, 68-12 110 Street, Flushing, NY 11375.

TI-99/4A software/hardware bargains. Hard-to-find items. Huge selection. Fast service. Free catalog. **DYNA**, Box 690, Hicksville, NY 11801.

TUBES, new, unused. Send self-addressed, stamped envelope for list. **FALA ELECTRONICS**, Box 1376-2, Milwaukee, WI 53201.

FREE Automotive Security Catalog. Largest selection available. Do-it-yourself pagers, alarms, hood/locks, glass detectors. Allow 4 weeks for delivery, or for rush send \$1.00. **AUTOMOTIVE SECURITY EQUIPMENT COMPANY**, Dept. 1, P.O. Box 382, Plainville, NY 11803.

INDIVIDUAL photofact folders. No. 1 to no. 1400, \$3.00 postpaid. **LBT**, 414 Chestnut Lane, East Meadow, NY 11554.

DESCRAMBLERS for downconverters. High gain. Send \$2.00. **RB ELECTRONICS**, P.O. Box 643, Kalamazoo, MI 49005.

TOKO coil set (four) \$8.00. **BFQ85 substitute transistor** \$2.00. **JIM RHODES, INC.**, 1025 Ransome Lane, Kingsport, TN 37660.

ELECTRONICS catalog. Over 4,500 items. Parts & components. Everything needed by the hobbyist or technician. \$2.00 postage & handling (States only), refundable with first \$15.00 order. **T & M ELECTRONICS**, Dept. R, 472 East Main Street, Patchogue, NY 11772, (516) 289-2520.

CABLE CONVERTERS & DESCRAMBLERS
HAMLIN OAK JERROLD
SCIENTIFIC SYLVANIA ZENITH
ALL TYPES OF CABLE TV EQUIPMENT
MICROWAVE ANTENNAS & ACCESSORIES
— FREE ILLUSTRATED BROCHURE —
— CALL OR WRITE —
H.M.R. SALES
221 E. CAMELBACK #1
PHOENIX, AZ 85012
(602) 993-0398

WRITE FOR
McGEE'S
SPEAKER & ELECTRONICS CATALOG
1001 BARGAINS IN SPEAKERS
toll free 1-800-346-2433 for ordering only.
1901 MCGEE STREET KANSAS CITY, MO. 64108

WANTED: Cash for old tubes, speakers, amplifiers. Western Electric, RCA, Cunningham, McIntosh, Marantz, Quad, Tannoy, JBL, Altec, Dynaco, Leak, (713) 728-4343. **MAURY**, 11122 Atwell, Houston, TX 77096.

PC-2 & Sharp PC-1500 owners: floppy disk emulator for your cassette files. **A/MP**, Box 78533, L.A., CA 90016.

SCIENTIFIC Atlanta cable systems. New CM-04 descrambler. Receive all channels. Send \$2.00. **ADVANCED TECHNOLOGY SYSTEMS**, Box 316, Auburn, MA 01501. (617) 832-2339.

TUBES, hard-to-find. Send self-addressed stamped envelope for list. **AUDIO VIDEO STOP**, 7477 Village Parkway, Dublin, CA 94568.

CABLE- and Subscription-TV secret manual. Build your own descramblers, converters—HBO, Showtime, Movie Channel, UHF. Latest theory, schematics, instructions, suppliers list. Send \$8.95 to: **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

FREE catalog. Electronic, electrical, parts, tools, controls, switches, relays, tech books, manuals. **JS CHRISTIANSON, INC.**, 120 Oser Ave., Hauppauge, NY 11788.

CIRCUIT boards: your artwork, quick delivery, reasonable. **ATLAS CIRCUITS**, Dept. A, P.O. Box 892, Lincolnton, NC 28092. (704) 735-3943.

FREE Pay-TV reception. "How-To" book. HBO, Showtime, Cinemax, \$5.00. **DIPTRONICS**, Box 80, (E7), Lake Hiawatha, NJ 07034.

★ ★ ★ ★ ★ ★ ★ ★ **WM. B. ALLEN'S** ★ ★ ★ ★ ★ ★ ★ ★

HOLIDAY FLUKE BONANZA

70 SERIES ANALOG/DIGITAL	
73.....	\$ 75
75.....	\$ 88
77.....	\$115
8020B SERIES 3 ½ DIGIT DMM	
8020B.....	\$174
8021B.....	\$139
8022B.....	\$135
8024B.....	\$217
8026B.....	\$174
4 ½ DIGIT DMM	
8060A.....	\$305
8062A.....	\$257
DIGITAL COUNTERS	
1900A (80MHz).....	\$358
1910A (125MHz).....	\$497
1911A (250 MHz).....	\$589
1912A (520MHz).....	\$719

REDEEM YOUR SPECIAL FLUKE REVIEW 80TK \$25-OFF COUPON AT WM. B. ALLEN

20 SERIES Analog/Digital
FLUKE 25 \$200
FLUKE 27 \$226

SPECIAL INTRODUCTORY PRICES ON 80TK TEMPERATURE ACCESSORY

SAVE NOW ON THE FIRST CHOICE OF PROFESSIONALS WORLDWIDE

CALL TOLL FREE
800 535-9593
LOUISIANA TOLL FREE 800 462-9520

TOTAL ELECTRONICS CENTER • OVER 70,000 ITEMS IN STOCK
WM. B. ALLEN SUPPLY CO. INC.
ALLEN SQUARE
300 BLOCK NORTH RAMPART STREET, NEW ORLEANS, LOUISIANA 70112

MCM ELECTRONICS

WE HAVE WHAT YOU NEED AT
THE PRICES YOU WANT!

CALL TOLL FREE
1-800-543-4330

(IN OHIO 1-800-762-4315)

(IN HAWAII OR ALASKA 1-800-858-1849)




TENMA®

DROP PROOF DIGITAL MULTIMETER

■ DC input impedance 10M ohm
■ Shock-mounted LCD display
■ Overload protection ■ Auto
polarity ■ Backed by our 1-year
limited warranty ■ For more
specifications see MCM catalog
#10, page 122

#72-057 **\$29⁹⁵**
each

 


TENMA®

15 MHz DUAL TRACE BATTERY OPERATED OSCILLOSCOPE

■ Two High Quality 10:1 Probes
included ■ Backed by our 2-year Limited
Warranty ■ Internal rechargeable batteries
provide 2 hours of continuous operation
without the need for any outside power
source. ■ For specifications see MCM
Catalog #10, page 121

#72-335 **\$489⁹⁵**

 


TENMA®

3 1/2 DIGIT LDC MULTIMETER

■ DC input impedance 10M ohm
■ Diode and HFE transistor tests
■ Overload protection ■ Auto
polarity ■ Backed by our 1-year
limited warranty ■ For more
specifications see MCM catalog
#10, page 122.

#72-050 **\$36⁸⁰**
\$39.80 (1-9) (10-up)

 

TENMA®

35 MHz DUAL TRACE OSCILLOSCOPE

■ Two High Quality 10:1 probes included
■ Backed by our 2-year limited warranty
■ For specifications see MCM catalog
#10, page 121

#72-330 **\$569⁰⁰**




TENMA®

DIGITAL CAPACITANCE METER

■ Measures capacitors from 0.1pF
to 1999mFd ■ Accuracy 0.5%
typical ■ Fuse protected
■ Checks capacitors in and out
of circuit ■ Backed by our 1-year
limited warranty ■ For more
specifications see MCM catalog
#10, page 122

#72-040 **\$54⁹⁵**
\$59.80 each (2-up)

 

TENMA®

20 MHz DUAL TRACE OSCILLOSCOPE

■ Two High Quality 10:1 probes included
■ Backed by our 2-year limited warranty
■ For specifications see MCM catalog
#10, page 121

#72-320 **\$389⁹⁵**

VCR BATTERY PACK


■ Fits many RCA and Panasonic
portable VCR's ■ Replaces RCA
battery #149722 and Panasonic
#LCR1812 ■ 12V, 1.9 Ah ■ Size: 7/8" (L)
x 1" (W) x 2 3/8" (H)


 
#29-260 **\$26⁸⁰**
\$27.95 (1-9) (10-up)

VCR LAMPS TAPE SENSING LAMP


■ Replaces: RCA #149389, Magnavox and Panasonic
#XAMV0019, Philco and Sylvania #07-28817-303


 
#25-235 **80¢**
95¢ (1-9) 85¢ (10-99) (100-up)

TAPE SENSING LAMP

■ Replaces: RCA #144075, Panasonic
#XAMQ27P150W, Philco and Sylvania #07-28777-433



#25-245 **85¢**
\$1.20 (1-9) \$1.05 (10-99) (100-up)

BE SURE TO CALL FOR YOUR FREE

132
PAGE
CATALOG!
OVER
5,000
ITEMS!



We have the Largest
Selection of Original
Japanese Semiconductors
in the Country!

We Also Have... a full line of test equipment,
computer accessories, telephone accessories,
speakers, television parts, flybacks, yokes, switches,
fuses, lamps, capacitors, resistors, cartridges, styli,
wire, CATV equipment, and many more. **Over 5,000
items AT THE LOWEST PRICES AROUND!**

Terms:



- \$10 minimum order. \$1.00 charge for orders
under \$10.
- \$20 minimum charge card order.
- Orders shipped UPS C.O.D.
- Most orders shipped within 24 hours.
- Sales office open 8:30 am to 7:00 pm. Saturdays
10:00 am to 3 pm. EST.
- For prepaid orders add \$2.75 for shipping and
handling.
- Should shipping & handling charges exceed \$2.75,
the balance due will be sent C.O.D.



MCM
ELECTRONICS
858 East Congress Park Drive
Centerville, Ohio 45459
513-434-0031

SOURCE NO. RE-11

Your ad could be selling merchandise for you in this space. The price is a remarkable \$250. To place your order, call any Radio-Electronics salesman: Stan Levitan (212) 777-6400, Marvin Green (818) 986-2001, Ralph Bergen (312) 446-1444.

TUNABLE notch filters, brochure, \$1.00. **D.K. VIDEO**, Box 63/6025, Margate, FL 33063. (305) 752-9202.

SECURE your home with our sound activated switch. Easy to build. Turns lights and/or radio on at any attempted break-in and off when it's safe. For plans and parts list send \$5.00 to **J.R. ELECTRONICS**, P.O. Box 99A, Marietta, GA 30061.

ASSORTMENT #102—Toko coils (1) 144LY-120K, (1) E520HN-3000023 and (2) BKAN-K5552AXX transformers, (1) BFQ85 Sub., and (1) AC adapter only \$15.00. For fast free shipping, use MasterCard/VISA and call toll free 1-800-821-5226, ext. 426 (orders only) or write **JIM RHODES, INC.**, 1025 Ransome Lane, Kingsport, TN 37660.

TUBES: "Oldies", latest. Supplies, components, schematics. Send S.A.S.E. for catalog. **STEINMETZ**, 7519 Maplewood, RE, Hammond, IN 46324.

AMAZING profits in your own electronics manufacturing business! Thousands waiting to sell your products!!! Free details. **BROWN**, Box 51-R7, Tecumseh, MI 49286.

WE make PC boards and sell components. Turn around 1 day or 3 weeks. **ET PROD**, Box 86172, St. Pete, FL 33738, (813) 397-6421.

CABLE-TV Source Book—a complete listing of suppliers for hard-to-find converters, descramblers, technical information, schematics and much, much more. Full refund if not satisfied. Send \$4.95 to **CABLE**, Box 12505-R, Columbus, OH 43212.

TUBES — OVER 2000 TYPES! DISCOUNT PRICES



Parts, supplies, and literature for tube type radios, including early and hard-to-find tubes.

Send \$1.00 for 24 page wholesale catalog.
ANTIQUE ELECTRONIC SUPPLY
1725 W. University • Tempe, Arizona 85281 • (602) 894-9503

NEW...Convert any portable television into a giant five foot picture screen. Guaranteed. Only \$24.50.
QUEEN ENTERPRISES, P.O. Box 159, Toronto, Ontario M6M 4Z2.

FREE catalog 99-cent kits—audio, video, TV, computer parts. **ALLKIT**, 434 W. 4th St., West Islip, N.Y. 11795.

VIDEO and **TVRO** buffs—Proc-amp board regenerates sync and gives total control over video/sync ratio. \$42.00. Kit—\$32.00. DA-4 board has one video input and provides four buffered outputs. \$37.00. Kit—\$27.00. **GRIFFIN ENTERPRISES**, Box 6104, Sumter, SC 29150-6104.

DESCRAMBER cable/over-the-air programs—kits \$97.95. Plans \$9.95—details \$1.00. **MINUTE**, Box 531, Westchester Station, Bronx, NY 10461.

COMMODORE 64 new 6" digit program helps pick lottery numbers. **Program Database**, find your programs fast, \$29.95 each. M.O. only. **RONALD O'DOMSKI**, 1107 Powderhorn Dr., Newark, DE 19713.

THE BEST PLACE TO BUY, SELL or TRADE NEW and USED EQUIPMENT
NUTS & VOLTS MAGAZINE
BOX 1111-E • PLACENTIA, CA 92670
(714) 632-7721
Join Thousands of Readers Nationwide Every Month
ONE YEAR U.S. SUBSCRIPTIONS
\$10.00 - 3rd Class • \$15.00 - 1st Class
\$35.00 - Lifetime - 3rd Class

NUTS & VOLTS
HAM GEAR COMPUTERS SOFTWARE SCANNERS • OPTICS TEST EQUIPMENT MICROWAVE AUDIO VISUAL NEW PRODUCTS COMPONENTS • KITS ANTENNA PROJECT PUBLICATIONS PLANS • SERVICES

SPEAKER builders—A complete guide to speaker design methods, construction techniques, technical specifications, suppliers. 20 quality computer designed stereo speakers, \$5.00. **TIM SEQUIN**, RE, 3959 Castle Dr., Bay City, MI 48706.

PREWAR, postwar tubes, rider volumes, Sam's Photofacts ARs, TSMs, CBs, unit sales, S.A.S.E. **TWORCK**, 22001 Dorion, St. Clair Shores, MI 48082.

TECHNICA 140/channel cable converter fully remote and video unit only \$149.00, **Jerrold** LCC58 converter only \$79.00, **Jerrold** DRZ450 converter 90/channel auto tuning only \$89.00. All units carry full manufacturer's warranty, specials while they last. For catalogue send \$3.00. Thanks. **REDCOAT ELECTRONICS**, P.O. Box 28504, Jamaica, NY 11428. (718) 459-5088.

SCANNERS

JOIN 30,000 other scanner owners in the nation's largest not-for-profit association of scanner owners. Bi-monthly publication with tech tips, fascinating true stories, news of new listening adventures. Plus member benefit package including car rental discounts, no-extra-cost insurance coverage, free classified ad service, and more. Send just \$9.75 for 10-month trial membership to: **SCANNER ASSOCIATION OF NORTH AMERICA**, 240-A Fencil Lane, Hillside, IL 60162.

CABLE TV FILTER "CYLINDERS"

SUPER powered notch filters. Equivalent of cable company "cylinders". Eliminate undesirable signals. Any channel 2 through 8; 14(A) through 22(I). (Please specify.) Send \$20.00 each. **Money back guarantee.** Quantity discounts, **CATV**, Box 17621, Plantation, FL 33318.

ALL SALES SUBJECT TO THE TERMS OF OUR 90 DAY LIMITED WARRANTY. FREE COPY UPON REQUEST.


SOLAR CELL SPECIAL: 4 In. Diameter Rated .45 VDC At 1.2 Amps Or Better. Brand New Units, Cosmetic Seconds, But Perfect Electrically. \$3.99 6/\$20.

THE NEW ZRT-80 CRT TERMINAL BOARD!

A LOW COST Z-80 BASED SINGLE BOARD THAT ONLY NEEDS AN ASCII KEYBOARD, POWER SUPPLY, AND VIDEO MONITOR TO MAKE A COMPLETE CRT TERMINAL. USE AS A COMPUTER CONSOLE, OR WITH A MODEM FOR USE WITH ANY OF THE PHONE-LINE COMPUTER SERVICES.

FEATURES:

- Uses a Z80A and 6845 CRT Controller for powerful video capabilities.
- RS232 at 16 BAUD Rates from 75 to 19,200.
- 24 x 80 standard format (60 Hz).
- Optional formats from 24 x 80 (50 Hz) to 64 lines x 96 characters (60 Hz).
- Higher density formats require up to 3 additional 2K x 8 6116 RAMS.
- Uses N.S. INS 8250 BAUD Rate Gen. and USART combo IC.
- 3 Terminal Emulation Modes which are Dip Switch selectable. These include the LSI-ADM3A, the Heath H-19, and the Beehive.
- Composite or Split Video.
- Any polarity of video or sync.
- Inverse Video Capability.
- Small Size: 6.5 x 9 Inches.
- Upper & lower case with descenders.
- 7 x 9 Character Matrix.
- Requires Par. ASCII keyboard.

 

BLANK PCB WITH 2716 CHAR. ROM, 2732 MON. ROM

\$4995

SOURCE DISKETTE - ADD \$10
SET OF 2 CRYSTALS - ADD \$7.50

\$9995 (COMPLETE KIT, # ZRT-80, 2K VIDEO RAM)

Digital Research Computers

P.O. BOX 461565 • GARLAND, TEXAS 75046 • (214) 225-2309

Call or write for a free catalog on Z-80 or 6809 Single Board Computers, SS-50 Boards, and other S-100 products.

TERMS: Add \$3.00 postage. We pay balance. Orders under \$15 add 75¢ handling. No C.O.D. We accept Visa and MasterCard. Texas Res. add 5-1/8% Tax. Foreign orders (except Canada) add 20% P & H. Orders over \$50 add 85¢ for insurance.

508 Central Ave.
Westfield, N.J. 07090
(201) 654-6008

UHF-TV PREAMP
(As featured in Radio Electronics March/May articles, 1982)
This inexpensive antenna mounted preamp can add more than 25 dB of gain to your system. Lots of satisfied customers and repeat orders for this high quality kit, which includes all component parts. PC BD, Case, Power Supply and Balun \$34.50 Assembled Version \$57.50

COILS FOR RADIO ELEC FEB 84 TV PROJECT, TOKO #1 (L1, L2, L3, L12UM) & L-21 (0.1UH) COMPLETE SET OF ALL 4 COILS..... 8.50
MC1350 - PRIME (HOT)..... 20/1.00
BFG-85 TRANSISTOR..... 1.50
DISC CAPS .001UF..... 20/1.00
74123 - PRIME (NAT)..... 2/1.00
470UF 25V (RADIAL)..... 2/1.00
470UF 10V (AXIAL)..... 4/1.00
2N3904..... 10/1.00
1N914..... 40/1.00
5P DIP NICAL..... 2/1.00
5.1V ZENER DIODES..... 5/1.00
VOLTAGE REGULATOR (PP3ME TO 220) 7812, 7812, 7905, 7912 - MIX OR MATCH..... 3/1.00
VOLTAGE REGULATOR SPECIAL-UNMARKED TO 220 MAY INCLUDE POSITIVE/NEG & ADJUST 15/1.00
*BLOB VOLTAGE REGULATOR (DM104)..... 20/1.00
PH222A (PLASTIC)..... 20/1.00
2N5308..... 20/1.00
555 TIMERS - PRIME (TI)..... 4/1.00
741J OF AMPHIBIOUS DIP HI REL Pkg1..... 4/1.00
JUMBO RED LED'S-DIFFUSED LENS, PRIME (TI) NO COSMETIC DEFECTS, ALL 100K..... 15/1.00
100/86.00, 1,000/857.50
LED MOUNTING CLIPS/RINGS..... 15/1.00
8 PIN IC SOCKETS..... 15/1.00
28 PIN IC SOCKETS..... 10/1.00
TEXAS INST #44A KEYBOARD - INC/DATA FOR PINS MADE WHEN EACH KEY DEPRESSED... 4.95
CLOC/MODULE - CRYSTAL CONTROLLED, GREEN DISPLAY/12VDC/TIME SET SWITCHES/DATA-4.95
DIP SWITCH - 12 POSITION..... 2/1.00
DIP SWITCH - 8 POSITION..... 4/1.00
DIP SWITCH - 3 POSITION..... 10/1.00
ROTARY SWITCH 3 POSITION, SA 123V 3/1.00
GIANT ALPHA NUMERIC DISPLAY - 1 1/2" X 2 1/4" 7X5 (35) TOTAL RED LED MATRIX, 0/DATA - 4.95
11 LED BAR GRAPH DISPLAY - 2 3/4" LONG, RECT LED'S SPECIFY RED, GRN, AMB/DATA... 2.49
TAPPED TRANSFORMER (7A) 7.5, 9, 15, 18V - 80.95
WALL PLUG TRANSFORMER - 24V 525MA..... 1.25
TRANSFORMER (6.25V, 1.2A)..... 1.25
5.600UF 25V COMP GRADE 2 5/8" x 1 1/2" 3/1.00

FREE **Antenna**

FREE THE ANTIENA WITH EVERY PURCHASE OF ANY OF THE FOLLOWING PROFESSIONAL INSTALLATION KITS

#4845 - FREE ANTENNA - 65 FEET OF PREMIUM SHIELDED COAXIAL CABLE, 2 FT COAXIAL CABLE PATCH CORD WITH "F" CONNECTORS, 2 FT 500 OHM TWIN LEAD, 2 PCS INSTALLER'S NYLON WALL FEED "HURU'S", 2 PCS NYLON CABLE TIES, 300 TO 75 OHM BALUN, 300 OHM TERMINAL, "F" CONNECTOR, "U" BOLT AND ALL MOUNTING HARDWARE..... 89.95 - 92.25 SHIPPING

#4124 - FREE ANTENNA/WALL-CEILING MOUNT FOR SUPER EASY INDOOR INSTALLATION, 25 FT PREMIUM SHIELDED COAXIAL CABLE, ALL PATCH CORDS, TIES/BALUN/CONNECTORS, ETC (SAME AS ABOVE) - SPECIAL WALL/CEILING MOUNTING HARDWARE..... 88.95 - 93.25 SHIPPING

#4846 - FREE ANTENNA/SPECIALLY DESIGNED POLE/HARDWARE FOR EXTRA EASY INDOOR USE - 25 FT PREMIUM SHIELDED COAXIAL CABLE, ALL COBDS, TIES/BALUN/CONNECTORS, ETC (SAME AS ABOVE)..... 88.95 - 92.25 SHIPPING

470UF 25V (RADIAL)..... 20/1.00
470UF 10V (AXIAL) (MICRO)..... 10/1.00
.1UF 50V MONOLITHICS..... 20/1.00
.22UF 50V MONOLITHICS..... 20/1.00
POTS - 1 MEG, LINEAR TAPER..... 5/1.00
MOTION DETECTOR BOARDS-#2 EACH..... 7/10.00
MOTION DETECTOR IC'S (ULN2231/82, 20/810 BLACK, PLASTIC PROJECT BOX FOR ABOVE-1.95
EXTENSIVE CONSTRUCTION ARTICLE FOR DET.#1, 1,000 PC RESISTOR ASS'T (130 VALUES)/2W-#3
ZENER DIODES - 20V 1W..... 30/1.00
ZENER DIODES - 13V 1W GLASS..... 30/1.00
1N4007'S..... 20/1.00
ZENITH IV REPLACEMENT IC SPECIAL \$1 EACH
221-42, 221-43, 221-45, 221-48, 221-49, 221-79, 221-87, 221-96, 221-104, 221-105, 221-106
28C112/TOSHIBA - HORIZ. OUTPUT..... 1.95
CHIP CAPS - SET OF 4, 2 EACH 2.763-3p-1.00
MINIATURE BEAR MOTOR (AURORA)..... 2/1.00
ZENER DIODES - 13V 1W GLASS..... 30/1.00
RF CHOKES - 1.8UH, 8.2UH, 12UH, 22UH, 10/1.00

MICRO-CONTROLLER BOARD (KIT/\$119.50)

Terms: MICRO-MART accepts Visa, MC and telephone C.O.D's. Minimum order \$10.00. Shipping—U.S. orders, \$2.00. Canada and other countries \$3.50 (includes ins.). Shipping rate adjusted where applicable. NJ residents add 6% sales tax.

MICRO-MART • 508 CENTRAL AVE., WESTFIELD, NJ 07090 • (201) 654-6008

RAMSEY

THE FIRST NAME IN ELECTRONIC TEST GEAR




20 MHz DUAL TRACE OSCILLOSCOPE

Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features include a component testing circuit for resistor, capacitor, digital circuit and diode testing. • TV video sync filter • wide bandwidth & high sensitivity • internal graticule • front panel trace rotator • Z axis • high sensitivity x-y mode • regulated power supply • built-in calibrator • rock solid triggering

\$39995*

high quality hook on probes included

 *USA—Add \$10.00 per unit for postage, overseas orders add 15% of total order for insured surface mail.



NEW

45 MHz DUAL SWEEP OSCILLOSCOPE

The Ramsey 625 is a dual time base, delayed sweep unit that includes a built-in signal delay line to permit clear viewing during very short rise times of high frequency waveforms. Other features include: variable trigger holdoff • 20 calibrated sweep time ranges from 0.5 μ s/div to 0.2 μ s/div • fully adjustable sweep time • X5 sweep magnification • five trigger sources; CH1, CH2, LINE EXternal and Internal (V mode) • front panel x-y operation, Z axis input • sum difference of CH1, and CH2 waveforms displayed as single trace • sweep gate and sweep output • auto focus • single sweep

\$79995*

high quality hook on probes included

*Same as unit to left.



RAMSEY D-1100 VOM MULTITESTER

Compact and reliable, designed to service a wide variety of equipment. Features include • mirror back scale • double-jeweled precision moving coil • double overload protection • an ideal low cost unit for the beginner or as a spare back-up unit.


\$1995 test leads and battery included



NEW RAMSEY 1200 VOM MULTITESTER

Check transistors, diodes and LEDs with this professional quality meter. Other features include: decibel scale • 20K volt metering system • 3 1/2" mirrored scale • polarity switch • 20 measuring ranges • safety probes • high impact plastic case

\$2495 test leads and battery included

 

RAMSEY D-3100 DIGITAL MULTIMETER

Reliable, accurate digital measurements at an amazingly low cost • in-line color coded push buttons, speeds range selection • abs plastic tilt stand • recessed input jacks • overload protection on all ranges • 3 1/2 digit LCD display with auto zero, auto polarity & low BAT. indicator

\$4995 test leads and battery included




CT-70 7 DIGIT 525 MHz COUNTER

Lab quality at a breakthrough price. Features • 3 frequency ranges each with pre amp • dual selectable gate times • gate activity indicator • 50mV @ 150 MHz typical sensitivity • wide frequency range • 1 ppm accuracy

\$11995 wired includes AC adapter

CT-70 kit \$99.95
BP-4 nicad pack 8.95

 


CT-90 9 DIGIT 600 MHz COUNTER

The most versatile for less than \$300. Features 3 selectable gate times • 9 digits • gate indicator • display hold • 25mV @ 150 MHz typical sensitivity • 10 MHz timebase for WWV calibration • 1 ppm accuracy

\$14995 wired includes AC adapter

 CT-90 kit \$129.95
OV-1 0.1 PPM oven timebase 59.95
BP-4 nicad pack 8.95




CT-125 9 DIGIT 1.2 GHz COUNTER

A 9 digit counter that will outperform units costing hundreds more. • gate indicator • 24mV @ 150 MHz typical sensitivity • 9 digit display • 1 ppm accuracy • display hold • dual inputs with preamps

\$16995 wired includes AC adapter

BP-4 nicad pack 8.95

 

CT-50 8 DIGIT 600 MHz COUNTER

A versatile lab bench counter with optional receive frequency adapter, which turns the CT-50 into a digital readout for most any receiver • 25 mV @ 150 MHz typical sensitivity • 8 digit display • 1 ppm accuracy

\$16995 wired

CT-50 kit \$139.95
RA-1 receiver adapter kit 14.95



DM-700 DIGITAL MULTIMETER

Professional quality at a hobbyist price. Features include 26 different ranges and 5 functions • 3 1/2 digit, 1/2 inch LED display • automatic decimal placement • automatic polarity

\$11995 wired includes AC adapter

DM-700 kit \$99.95
MP-1 probe set 4.95



PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies UP in frequency • great for PL tone measurements • multiplies by 10 or 100 • 0.01 Hz resolution & built-in signal preamp/conditioner

\$4995 wired

PS-2 kit \$39.95



PR-2 COUNTER PREAMP

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for shifting RF • ideal receiver/TV preamp

\$4495 wired includes AC adapter

PR-2 kit \$34.95



PS-1B 600 MHz PRESCALER

Extends the range of your present counter to 600 MHz • 2 stage preamp • divide by 10 circuitry • sensitivity: 25mV @ 150 MHz • BNC connectors • drives any counter

\$5995 wired includes AC adapter

PS-1B kit \$49.95

ACCESSORIES FOR RAMSEY COUNTERS

Telescopic whip antenna—BNC plug \$ 8.95
High impedance probe, light loading 16.95
Low pass probe, audio use 16.95
Direct probe, general purpose use 13.95
Tilt bail, for CT-70, 90, 125 3.95



PHONE ORDERS CALL
716-586-3950

TELEX 466735 RAMSEY CI

TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased, return in original form for refund • add 6% for shipping and insurance to a maximum of \$10.00 • overseas add 15% for surface mail • COD add \$2.50 (COD in USA only) • orders under \$15.00 add \$1.50 • NY residents add 7% sales tax • 90 day parts warranty on all kits • 1 year parts & labor warranty on all wired units.



RAMSEY ELECTRONICS, INC.
2575 Baird Rd.
Penfield, N.Y. 14626

CIRCLE 70 ON FREE INFORMATION CARD

JULY 1985

91

Commodore Accessories

RS232 Adapter for VIC-20 and Commodore 64

The JE232CM allows connection of standard serial RS232 printers, modems, etc. to your VIC-20 and C-64. A 4-pole switch allows the inversion of the 4 control lines. Complete installation and operation instructions included.

- Plugs into User Port
- Provides Standard RS232 signal levels
- Uses 6 signals (Transmit, Receive, Clear to Send, Request to Send, Data Terminal Ready, Data Set Ready)

JE232CM \$39.95

VOICE SYNTHESIZER FOR APPLE AND COMMODORE

Reduced Pricing!

Over 250 word vocabulary - affixes allow the formation of more than 500 words • Built-in amplifier, speaker, volume control, and audio jack • Recreates a clear, natural male voice • Plug-in user ready with documentation and sample software • Case size: 7 1/4" L x 3 1/4" W x 1-3/8" H

Part No. Description Price
JE520CM For Commodore 64 & VIC-20 \$ 99.95
JE520AP For Apple II, II+, and IIe \$119.95

Computer Memory Expansion Kits

IBM PC, PC XT and Compatibles

Most of the popular Memory Boards (e.g. Quadram™ Expansion Boards) allow you to add an additional 64K, 128K, 192K or 256K. The IBM4K Kit will populate these boards in 64K byte increments. The Kit is simple to install - just insert the 9 - 64K RAM chips in the provided sockets and set the 2 groups of switches. Complete conversion documentation included.

IBM64K (Nine 200ns 64K RAMs)..... \$19.95

IBM PC AT

Each kit comes complete with nine 128K dynamic RAMs and documentation for conversion.

IBM128K (Nine 250ns 128K RAMs).... \$174.95

APPLE IIe

Extended 80-Column/64K RAM Card. Expands memory by 64K to give 128K when used with programs like VisiCalc™. Fully assembled and tested.

JE864..... \$79.95

TRS-80 MODEL I, III

Each Kit comes complete with eight MM5290 (JPD416/416) 16K Dynamic RAMs and documentation for conversion. Model I: 16K equipped with Expansion Interface can be expanded to 48K with 2 Kits. Model III: Can be expanded from 16K to 48K using 2 Kits. Each Kit will expand computer by 16K increments.

TRS-16K3 200ns (Model III)..... \$6.29
TRS-16K4 250ns (Model I)..... \$5.49

TRS-80 MODEL IV & 4P

Easy to install Kit comes complete with 8 ea. 4164N-20 (200ns) 64K Dynamic RAMs and conversion documentation. Converts TRS-80 Model IV computers from 16K to 64K. Also expands Model 4P from 64K to 128K.

TRS-64K-2..... \$17.95
 (Converts the Model IV from 16K to 64K or will expand the Model 4P from 64K to 128K)

TRS-64K2PAL (Model IV only)..... \$38.95
 (8 - 4164's with PAL Chip to expand from 64K to 128K)

TRS-80 COLOR AND COLOR II

Easy to install Kit comes complete with 8 ea. 4164N-20 (200ns) 64K Dynamic RAMs and documentation for conversion. Converts TRS-80 Color Computers with D, E, ET, F and NC circuit boards to 32K. Also converts TRS-80 Color Computer II to 64K. Flex DOS or OS-9 required to utilize full 64K RAM on all computers.

TRS-64K-2..... \$17.95

INDUSTRIES

PROTECT YOURSELF.. DATASHIELD® Surge Protector

Eliminates voltage spikes and L-N-R noise before it can damage your equipment or cause data loss. 6-mo. warranty. Power dissipation (100 microsecond): 2,000,000 watts

MODEL	DESCRIPTION	PRICE
MODEL 75	4 Sockets, On/Off Switch.....	\$49.95
MODEL 85	6 Sock., Super Filters, On/Off Switch.....	\$59.95
MODEL 100	6 Sock., Super Filters, Low Volt. Alarm.....	\$69.95
MODEL 110AMS	6 Sockets, Super Filters, Auto. Master Switch.....	\$99.95

DATASHIELD® Back-Up Power Source

Protect your computer from black-outs, brown-outs, power surges and line noise. PTT's PC200 is designed for PCs with floppy disk memory, the XT300 for hard disk memory and the AT300 for multi-user systems. A typical compatible PC for each of these standbys will be supported for 15 to 25 minutes after power is lost. Weight (PC200: 24 lbs.) - (XT300: 37.5 lbs.) - (AT300: 53 lbs.) - (AT600: 83 lbs.)

PC200 (200 Watt Rating).....	\$299.95
XT300 (300 Watt Rating).....	\$399.95
AT300 (500 Watt Rating).....	\$499.95
AT600 (800 Watt Rating).....	\$799.95

***** SUMMER SPECIALS *****

PROMETHEUS

Intelligent 300/1200 Baud Telephone Modem with Real Time Clock/Calendar

The ProModem™ is a Bell 212A (300/1200 baud) intelligent stand-alone modem. Full featured expandable modem. Standard features include Auto Answer and Auto Dial, Help Commands, Programmable Intelligent Dialing, Touch Tone™ and Pulse Dialing & More. Hayes command set compatible plus an additional extended command set. Shown w/alphanumeric display option.

Part No.	Description	Price
PM1200	RS-232 Stand Alone Unit.....	\$319.95
PM1200A	Apple II, II+ and IIe Internal Unit.....	\$299.95
PM1200B	IBM PC and Compatible Internal Unit.....	\$239.95
PM1200BS	IBM PC & Compatible Internal Unit w/Mite Software.....	\$274.95
MAC PAC	Macintosh Package.....	\$369.95

(Includes PM1200, Cable, and ProCom-M Software)

OPTIONS FOR ProModem 1200

PM-COM (ProCom Communication Software).....	\$79.95
PM-OP (Options Processor).....	\$79.95
PMO-16K (Options Processor Memory - 16K).....	\$ 4.50
PMO-32K (Options Processor Memory - 32K).....	\$ 9.00
PMO-64K (Options Processor Memory - 64K).....	\$18.00
PM-ALP (Alphanumeric Display).....	\$79.95

PM-Special (Includes Options Processor, 64K Memory and Alphanumeric Display)..... \$169.95

KEYBOARDS

Mitsumi 54-Key Unencoded All-Purpose Keyboard

SPST keyswitches • 20 pin ribbon cable connection • Low profile keys • Features: cursor controls, control, caps (lock), function, enter and shift keys • Color (keycaps): grey • Wt.: 1 lb. • Pinout included

KB54..... \$14.95

82-Key ASCII Cherry Keyboard

7-bit parallel ASCII • 11-key numeric keypad • Cursor keypad • SPST mechanical keyswitches • 4 illuminated keys • 26-pin header connector • Color, white • Size: 18" L x 6 1/4" W x 1 1/4" H • Spec included

KB8201..... (1700 avail.)... \$29.95

Apple Keyboard and Case for Apple II and II+

Keyboard: 68 keys • 15-key keypad • Direct connection with 16-pin ribbon connector • 26 special functions • Size: 14 1/2" L x 5 1/2" W x 1 1/4" H

Case: Accommodates KB-A68 • Pop-up lid for easy access • Fits power supply and motherboard too • Size: 15 1/4" W x 18 1/2" D x 4 1/4" H

Part No.	Description	Price
KB-EA1	Apple Keyboard and Case (pictured above).....	\$134.95
KB-A68	68-Key Apple Keyboard only.....	\$ 79.95
EAEC-1	Expanded Apple Enclosure Case only.....	\$ 59.95

POWER SUPPLIES

Power/Mate Corp. REGULATED POWER SUPPLY

Input: 105-125/210-250 VAC at 47-63 Hz • Line regulation: ±0.05% • Three mounting surfaces • Overvoltage protection • UL recognized • CSA certified

Part No.	Output	Protection	Size	Weight	Price
EMAS/6B	5V@3A/6V@2.5A	4 1/4" L x 4" W x 2 1/4" H	2 lbs.	\$29.95	
EMAS/6C	5V@6A/6V@5A	5 1/4" L x 4 1/4" W x 2 1/4" H	4 lbs.	\$39.95	

KEPCO/TDK 4-OUTPUT SWITCHING POWER SUPPLY

Ideal for disk drive needs of CRT terminals, microcomputers and video games • Input: 115/230VAC, 50/60Hz • Output: +5V @ 5 Amp, +12V @ 1.5 Amp, -12V @ 2 Amp, -12V @ 0.5 Amp • UL recognized • CSA certified • Size: 7 1/4" L x 6-3/16" W x 1 1/4" H • Weight: 2 lbs.

MRM 174KF..... \$49.95

Switching Power Supply for APPLE II, II+ & IIe™

Can drive four floppy disk drives and up to eight expansion cards • Short circuit and overload protection • Fits inside Apple computer • Fully regulated +5V @ 5A, +12V @ 1.5A, -5V @ .5A, -12V @ .5A • Direct plug-in power cord included • Size: 9 1/4" L x 3 1/2" W x 2 1/4" H • Weight: 2 lbs.

KHP4007 (SPS-109)..... \$59.95

4-CHANNEL SWITCHING POWER SUPPLY

Microprocessor, mini-computer, terminal, medical equipment and process control applications • Input: 90-130VAC, 47-400Hz • Output: +5VDC @ 5A, -5VDC @ 1A, +12VDC @ 1A, -12VDC @ 1A • Line regulation: ±0.2% • Ripple: 30mV p-p • Load regulation: ±1% • Overcurrent protection • Adj: 5V main output • 10% • Size: 8 1/4" L x 1 1/4" W x 4-15/16" H • Weight: 1 1/2 lbs.

FCS-604A..... \$69.95

IBM PCXT EQUIVALENT 130 WATT POWER SUPPLY. UPGRADE YOUR PC!

Input: 100V-130V/200V-260V selectable @ 47 to 63Hz • Output: +5VDC @ 15A, -5VDC @ 0.5A, +12VDC @ 4.2A, -12VDC @ 0.5A • Plug compatible connectors • Fits into IBM PC • Weight: 6 lbs.

IBM-PS..... \$159.95

\$10 Minimum Order - U.S. Funds Only CA Residents: Add 6% Sales Tax Spec Sheets - 30¢ each Shipping: Add \$5 plus \$1.50 Insurance Send \$1 Postage for FREE 1985 Jameco Catalog Prices Subject to Change Send stamped, self-addressed envelope to receive a Monthly Sales Flyer - FREE!

MasterCard **Jameco** ELECTRONICS **VISA**

1355 SHOREWAY ROAD, BELMONT, CA 94002
 7/85 PHONE ORDERS WELCOME - (415) 592-8097 - Telex: 176043

Apple Accessories

5 1/4" APPLE™ Direct Plug-In Compatible Disk Drive and Controller Card

The ADD-514 Disk Drive uses Shugart SA390 mechanics - 143K formatted storage - 35 tracks • Compatible with Apple Controller & ACC-1 Controller • The drive comes complete with connector and cable - just plug into your disk controller card • Size: 6" L x 3 1/4" W x 8-9/16" D • Weight: 4 1/2 lbs.

ADD-514 (Disk Drive)..... \$149.95
ACC-1 (Controller Card)..... \$ 49.95

More Apple Compatible Add-Ons...

APF-1 (Cooling Fan with surge protection).....	\$39.95
KHP4007 (Switching Power Supply).....	\$59.95
JE614 (Numeric/Aux. Keypad for IIe).....	\$49.95
KB-A68 (Keyboard w/Keypad for II & II+).....	\$79.95
MON-12G (12" Green Monitor w/swivel stand).....	\$79.95
JE864 (80 Col. - 64K RAM for IIe).....	\$79.95
ADD-12 (5 1/4" Half-Height Disk Drive).....	\$159.95

ADDITIONAL APPLE™ ADD-ONS AVAILABLE

ARC-16K (16K RAM Card for Apple II & II+)..... \$39.95
AEB-2 (EPROM Burner for Apple II, II+ & IIe)..... \$69.95
 Allows copy of standard EPROMs 2716, 2732, 2764

A80-C (80-Column Card w/Soft Switch)..... \$74.95
ADD-IIc (5 1/4" Half-Ht. Disk Drive for Apple IIc)..... \$169.95

DISK DRIVES

Documentation Included Best Buys!

MP1518 (MPI 5 1/4" SS full-ht.).....	\$ 89.95
RFD480 (Remex 5 1/4" DS full-ht.).....	\$ 99.95
TM100-2 (Tandon 5 1/4" DS full-ht.).....	\$159.95
FD55B (Teac 5 1/4" DS half-ht.).....	\$139.95
SA455 (Shugart 5 1/4" DS half-ht.).....	\$139.95
FDD100-8 (Siemens 8" SS full-ht.).....	\$119.95
PKC-5 (5 1/4" Power Cable Kit).....	\$ 29.95
PKC-8 (8" Power Cable Kit).....	\$ 39.95

UV-EPROM Eraser

8 Chips - 21 Minutes

1 Chip - 15 Minutes

Erases all EPROMs. Erases up to 8 chips within 21 minutes (1 chip in 15 minutes). Maintains constant exposure distance of one inch. Special conductive foam liner eliminates static build-up. Built-in safety lock to prevent UV exposure. Compact - only 9.00" L x 3.70" W x 2.60" H. Complete with holding tray for 8 chips.

DE-4 UV-EPROM Eraser..... \$74.95
UVS-11EL Replacement Bulb..... \$16.95

JE664 EPROM PROGRAMMER

See Our New IBM Communications Program!

24 & 28 PIN PACKAGES

8K to 64K EPROMs

REQUIRES NO ADDITIONAL SYSTEMS FOR OPERATION

Programs and validates EPROMs • Checks for properly erased EPROMs • Emulates PROMs or EPROMs • Loads data in RAM by keyboard • Changes data in RAM by keyboard • Loads RAM from an EPROM • 64K RAMs can be used for external microprocessor development • Compares EPROMs for content differences • Copies EPROMs • Input: 115VAC @ 60Hz • Assembled and tested • Size: 15 1/4" L x 8 1/4" W x 3 1/4" H • Wt. 5 1/2 lbs. • 2716 Module included

JE664-A EPROM Programmer..... \$995.00

JE665-RS232C INTERFACE OPTION - This option implements computer access to the JE664-A RAM, allowing computer to manipulate, store, and transfer EPROM data to and from the JE664. Sample program listing is supplied in MBASIC for CP/M computers. Documentation provided to adapt the software to other computers with an RS232C port. Specs: 9600 Baud, 8-bit word, odd parity with 2 stop bits • Assembled and tested • 2716 Module included

JE664-ARS EPROM Programmer..... \$1195.00
 w/JE665 Option

JE664-ARS COMMUNICATION PROGRAM

For IBM-PC or XT and Compatibles

Fast compiled BASIC program • Easy to use, menu-driven • Print hard-copies of EPROM data • View data in HEX and ASCII **NEW!** The JE664-ARS Communication Program was written for quick interfacing between the JE664-ARS EPROM Programmer and the IBM-PC computer and compatibles. Menu-driven program allows user to Load and Save EPROM data to and from the computer or floppy disk. Data entered by the computer can be viewed in Hex & ASCII formats. Printed hard-copies are also displayed in both formats. Program is ideal for keeping archives of master EPROMs on disk. The program is compatible for all EPROMs tested with the JE664. Computer requirements: IBM-PC, XT (or eq.) with at least 128K RAM and one serial port. Optional: One parallel port for printer.

JE664-ARS-CP..... \$49.95
JE664-CP CABLE..... \$29.95

JUMPER (Personality) MODULES - Jumper (Personality) Modules for 8K, 16K, 32K, and 64K EPROMs. Please specify EPROM and manufacturer. **JUMPER (Personality) MODULE..... \$14.95 each**

For cable accessories, there's no place like Sone.



1. **JERROLD RSX WIRED REMOTE*** This 36 Channel Remote features: fine tuning control-20 foot cord-90 day warranty.
2. **JERROLD JRX WIRED REMOTE*** This 36 Channel Remote features: 20 foot cord-fine tuning control-90 day warranty.
3. **JERROLD RSC WIRED REMOTE*** This 30 Channel Remote's features include: 20 foot cord-fine tuning control-90 day warranty.
4. **EAGLE EVSC-2000 REMOTE CABLE TV CONVERTER** You can choose from up to 60 cable TV Channels with this powerful unit. Other features include: last channel recall-favorite channel scan-remote control.
5. **DW-63K ELECTRONIC VIDEO SELECTOR** This sophisticated video selector allows you to connect up to 6 different inputs and 3 outputs. Features include: LED monitor display-soft touch keyboard.
6. **VIEWSTAR VSS-1000 REMOTE TV CONVERTER WITH VOLUME CONTROL** Expand the excitement of cable TV viewing with this 67 Channel unit. Features include: fine tuning control-last channel recall-remote control.
7. **CABLE TV BLOCK CONVERTER** Program your VCR to record one channel while you watch another. This unit also restores control functions and fine tunes for offset channels.
8. **CHANNEL SCAN WIRELESS REMOTE CONTROL** A fully assembled, easy to install remote control for your TV. Features include: channel changer and illuminated channel indicator.
9. **DW-42K ELECTRONIC VIDEO SELECTOR** This unit can handle up to 4 different inputs and 2 outputs. Features include: LED display monitor-soft touch keyboard.

* Factory Refurbished

**Now You Can Record Boxing on ESPN at 8 P.M.,
Your Favorite Sitcom on Network at 10 and the Late Movie on HBO —
All Without Ever Going Home to Change Channels.**

Introducing CableMaster

CableMaster features a special time-control capability that allows you to record any combination of channels unattended — up to 8 events, two weeks in advance.

There's no special installation needed, and no new connection necessary to your cable equipment or VCR. All you do is plug the CableMaster into an electrical outlet, plug in the special



CableMaster

"Personality Module" that's coded for the descrambler used by your cable company, and the CableMaster is ready to record your favorite programs.

Special Features Include: • 14 day, 8 event timer • Quartz Clock • Automatic Sequencing of Programmed Events

Only \$149.

Check method of payment <input type="checkbox"/> VISA <input type="checkbox"/> MASTERCARD <input type="checkbox"/> C.O.D. (Cash)	Quantity Prices	1 piece	3 pieces	10 pieces	Total
Credit card number _____ Expiration date _____	1. Jerrold RSX	\$44	\$40	\$35	\$
Signature _____ Name _____	2. Jerrold JRX	\$49	\$44	\$39	\$
Address _____	3. Jerrold RSC	\$39	\$35	\$30	\$
City _____ State _____ Zip _____	4. Eagle EVSC	\$99	\$89	\$79	\$
For CableMaster, please list the descrambler used by your Cable Company _____	5. DW-63K	\$69	—	\$52	\$
	6. Viewstar	\$119	\$109	\$99	\$
	7. Block	\$19	\$15	\$11	\$
	8. Channel Scan	\$49	\$44	\$39	\$
	9. DW-42K	\$45	—	\$39	\$
	10. CableMaster	\$149	—	\$145	\$

For larger quantities or catalog, please call or write.

Sone Associates • 5 Broadway - Suite 201 • Troy, N.Y. 12180 • (518) 274-0608

MASTERCARD AND VISA are now accepted for payment of your advertising. Simply complete the form on the first page of the Market Center and we will bill.

FCC LICENSE TRAINING

EARN \$600.00+ week! Get your "F.C.C. General Radiotelephone License." Electronics home study. Fast, inexpensive! "Free" details. **COMMAND**, D-168, Box 2223, San Francisco, CA 94126.

GRAPHIC EQUALIZERS, ETC.

NOISE eliminators, expanders, power meters, others. Twelve-24 bands/channel equalizers from \$89.00. Kit see **R-E 5-6/78, 2/80, 3-4/81**. Catalog: **SSS**, 856R Lynnrose, Santa Rosa, CA 95404. (707) 546-3895.

EMPLOYEES APPRECIATE THE PAYROLL SAVINGS PLAN. JUST ASK THE PEOPLE AT E-SYSTEMS.

"Bonds are a good liquid investment, and if I don't use them, they continue to earn interest."

—L.A. Fulcher



"I save them, but when I want something extra, I know they're there. They're great for emergencies."

—Jose Acosta



U.S. Savings Bonds now offer higher, variable interest rates and a guaranteed return. Your employees will appreciate that. They'll also appreciate your giving them the easiest, surest way to save.

For more information, write to: Steven R. Mead, Executive Director, U.S. Savings Bonds Division, Department of the Treasury, Washington, DC 20226.



U.S. SAVINGS BONDS
Paying Better Than Ever

A public service of this publication.

LOW

Video to Video Cable Set

Own a video cassette? Want to dub tapes? You must have one of these amazing cable sets. Doesn't matter what type...VHS, Beta, U-matic...Philips... this suits any to any! Comes with 2 metres audio/video cable with phono adaptors to suit UHF (PL259), BNC, 6.5mm, 5 pin DIN and 6 pin DIN. Every video enthusiast should have one! Cat. W-1287

HUGE SAVINGS \$9.95

\$4.95/325' roll

LIGHT DUTY SPEAKER CABLE

Ideal cable for use with Hi Fi systems for speaker connections or with intercoms. Twin plastic insulated conductors, insulation marked with a trace to keep speakers correctly polarised. Cat W-2010

DICK SMITH'S FUNWAY INTO ELECTRONICS GIFT PACK

Contains the famous introductory Funway Into Electronics Vol 1 which starts off from the very basics of electronics and shows you how to make 20 different projects, including: Transistor Tester, Beer Powered Radio, Light/Dark Indicator, Electronic Siren, Radio Receivers, Music Maker and many more. Book and all components included.

ONLY \$24.95

NO SOLDERING REQUIRED



Cat K-2605

"PROTECT YOUR CAR" CAR ALARM

Sophisticated yet simple. Uses a triggering technique which will sense a voltage drop anywhere in the electrical system, making it less prone to false alarms.

\$34.95 Cat L-5090

HIGH TECH - EASY TO INSTALL



CURRENT SENSING



Cat K-3439 \$89.95

500MHz DIGITAL FREQUENCY COUNTER

Uses latest IC technology, especially designed for ease of construction and reliability

GAMMA™ FOR APPLE® IC COMPUTERS

- Media: Standard 5.25" single sided floppy diskette
- Track Density: 48 lpi
- Tracks/Diskette: 40
- Sectors/Track: 16
- Bytes/Sector: 256
- Capacity: 160K bytes
- Disk Rotation Speed: 300 rpm
- Track to track access time: less than 12msec

LIST PRICE \$199
ONLY \$129

- Low cost
- Precise band positioner
- Track00 sensor design eliminates recalibrate noise
- Reliable data read/write
- 12 msec track to track access time
- 160K bytes storage capacity



Cat X-7505

APPLE® is a registered trademark of Apple Computer Inc. GAMMA™ is a registered trademark of Video Technology Ltd.

KIT


- Includes high quality instrument case
- 7 segment display
- 3 frequency ranges: 0-10MHz, 0-50 MHz, 10-500MHz (with optional pre-sealer)
- high accuracy

PRE-SEALER

Cat K-3432

\$22.50

 ORDER HOT LINE
TOLL FREE 1-800-DEAL DSE
3325 373
CALL NOW



HUGE 1 AMP OUTPUT

HIGH OUTPUT SOLAR PANEL \$149

Cat Z-4845

Calling all boat owners, amateur operators, technicians and anyone else who's had to keep a 12V battery charged in out-of-the-way place.

- 2 x 10V @ 500mA (20V @ 500mA @ 10V @ 1A)
- Diode Protected

EVERYTHING FOR THE ELECTRONICS ENTHUSIAST



**132 PAGES
PACKED WITH
ELECTRONIC
GOODIES AT
INCREDIBLY LOW
PRICES!**

**THAT'S THE 1985
DICK SMITH ELECTRONICS
CATALOG**

CIRCLE 95 ON FREE INFORMATION CARD



**NEW SWISS MADE
1 GHz Frequency Counter**

We have been fortunate enough to make this exclusive direct buy. Compare the price of this state-of-the-art unit with older models.
Cat Q-1315 **\$249⁰⁰**

**IDC CONNECTORS
NO SOLDER
'D' TYPE
25 pin 'D' Plug**

Cat P-2693 \$5.49 ea
10 up \$4.80 ea

25 way 'D' Socket

Cat P-2694 \$5.95 ea
10 up \$5.50 ea

36 way Centronics Connectors

57.30360 Plug
Solder tail w/cover
Cat P-2680 \$2.95 ea
10 up \$2.50 ea

57.40360 Socket
Solder tail
Cat P-2681 \$5.95 ea
10 up \$5.50 ea



50 Watt Amp Module

Ideal for home stereo systems. An economical solution for those who want to update their old system without a huge outlay of money. ● Input sensitivity is 500mV ● Supplied with exclusive instruction booklet ● rugged fiberglass PCB ● easy assembly. Heatsink bracket is supplied but heatsink itself is extra.
Cat K-3440 **\$14⁹⁵**

100 Watt Amp Module

● 100 watts RMS; 5kHz at 100dB signal to noise ratio. ● the ultimate in simplicity; even the power transistors mount on the PCB. ● PCB heatsink bracket is supplied ● Has on-board fuse protection ● input sensitivity: 1V ● Use with K-3468 power supply. Ideal for the home constructor or technician who wants to 'roll his own' amplifier system for the home or professional use.
Cat K-3442 **\$19⁹⁵**

IDC COMPUTER CABLE

We buy this cable by the mile direct from the manufacturer to get the lowest possible price so check our prices before you buy.

Type	Cat No.	Price
26 way	W-2750	46¢/ft
34 way	W-2752	60¢/ft
40 way	W-2754	72¢/ft
50 way	W-2756	89¢/ft

**At last! 'No leak' Rechargeable
BATTERIES
12V 3Ah
Gel Cell**

**OFFER EXPIRES
END JUNE**

Designed especially for 'trickle charge' circuits such as burglar alarms and emergency supplies. Sealed to prevent leaks and mess.

Cat S-3315 12V 1.2Ah \$7.95 ea
10 up \$6.95 ea WILL BE \$9.95

Cat S-3320 12V 3Ah \$13.95 ea
10 up \$12.95 ea WILL BE \$17.95



**AMAZING
VALUE**



**PLAYMASTER
MOSFET
AMPLIFIER
KIT**

\$149⁰⁰

Build this handsome Mosfet Integrated Stereo Amplifier yourself and impress your friends. Just look at these features for such a low price:

- LED indicated input ● loudness control ● muting control
 - integral speaker protection ● full speaker switching facility
 - stereo/mono switching ● tape monitor switch ● FULL 45 watts per channel output ● frequency response 30Hz-20kHz
- Cat K-3515 Full instruction supplied with kit



**AMAZINGLY
LOW PRICE!
CAN'T READ
OUR AD?**



\$6⁵⁰


\$2 off for any customer who has difficulty reading this ad.

2 1/2" double glass lens, stamp/coin viewer - excellent for inspecting hair-line cracks in PCB's.
Cat Y-0500

**19" RACK
MOUNTING CASE**

Professional quality black instrument case fits standard 19" racks, overall they're 16.75" x 9.8" x 5.5".

Cat H-2481 **\$29.95**
10 up \$26.95 ea

 

**QUALITY
NI-CAD
Rechargeable
Batteries**

From **\$1.49** ea
(10 up price of AA)



**OPENING
SPECIAL**

Ni-Cads work out much cheaper in the long run, especially if you buy them from Dick Smith Electronics.

Type	Cat No.	Price each
AA	S-3300	1.99
AAA	S-3305	1.95
C	S-3301	2.95
D	S-3003	2.95

**INSTRUMENT
CASE**

A superb case for all 'instrument' type projects, and many other besides. Case splits apart for ease of working, comes complete with 4 moulded feet and assembly screws. Amazingly versatile allowing for various PCB mounting positions, front & rear panel are moulded plastic for ease of working (they can be replaced with aluminium panel if required). Size approx. 8" x 6 1/2" x 2 1/2"
Cat H-2505



Normally \$9.95
\$4.95 if you buy
by the end of
June

VALUE!

MAIL ORDER CENTER AND SHOWROOM:

390 Convention Way, Redwood City CA 94063
PO Box 2249, Redwood City CA 94063
Telephone: (415) 368 8844
Order Hotline: (415) 368 1066
Californian residents add 6 1/2%
HANDLING - ALL ORDERS \$4.00
PLUS SHIPPING
INSIDE USA 5% OF ORDER TOTAL
(MIN \$1.50)
OUTSIDE USA 10% OF ORDER
TOTAL (MIN \$3.00)

RE1

**OFFER EXPIRES
END JUNE**

**MAIL THIS COUPON TODAY WITH \$2 & \$1 SHIPPING
AND WE'LL SEND YOU A CATALOG AS SOON AS THEY
ARE PRINTED IN JUNE** \$2 COUPON IN CATALOG REDEEMS YOUR COST
WITH YOUR FIRST ORDER

Name _____ Address _____
City _____ State _____ Zip _____

**DICK SMITH
ELECTRONICS**

INCORPORATED IN THE STATE OF CALIFORNIA

OVER 60 STORES IN 3 COUNTRIES

cable TV

DESCRAMBLER PARTS

We stock the exact parts and PC Board for Radio Electronic's February Article on building your own Cable TV Descrambler.

- #701 PARTS PACKAGE \$29.95**
Includes all the original resistors, capacitors, diodes, transistors, integrated circuits, coils and IF transformers (BKAN-K552AAX).
- #702 PC BOARD \$12.95**
Original etched & drilled silk-screened PC Board used in the article.
- #704 AC ADAPTOR \$12.95**
(14 volts DC @ 285MA)
- Both #701 & #702 \$39.00**

FREE!! Reprint of Radio Electronics Article on Building Your Own Cable TV Descrambler with any purchase.

Add \$4.00 Postage & Handling

TOLL FREE

1-800-227 8529 (Orders Only)
1-617-339-5372 (Information)

J & W ELECTRONICS, INC.

P.O. Box 800
Mansfield, MA 02048

CIRCLE 65 ON FREE INFORMATION CARD

DON'T BLAME THE SOFTWARE!

Our Isolators eliminate equipment interaction, clean up interference, curb damaging power line spikes and lightning bursts.



ISO-1 ISOLATOR

3 isolated sockets; quality spike suppression; basic protection. . \$81.95

ISO-3 SUPER-ISOLATOR

3 dual isolated sockets; suppressor; commercial protection. \$122.95

ISO-17 MAGNUM ISOLATOR

4 quad isolated sockets; suppressor; laboratory grade protection. . \$213.95

ESP Electronic Specialists, Inc.
171 S. Main, Natick, MA 01780 (617) 655-1532
Toll Free Order Desk 1-800-225-4876
MasterCard, VISA, American Express

CIRCLE 60 ON FREE INFORMATION CARD

THE BEST PRICES

5 1/4" DISKS AS LOW AS 77¢

Excellent quality, 1 year replacement warranty. With sleeve and label.
#UD10 DS/DD 10/80/40
#UD20 DS/DD 10/10/80/50
#UD30 DS/DD built 100/878
#UD30 DS/DD built 100/899

RECTIFIER SALE!

type	description	sale
INS24	2SA 200P1V	12/81
INS210R	2SA 200P1V	4/81
INS194R	30A 200P1V	3/81
INS207	1A 100P1V	5/81
6ABR	6A 50V BRIDGE	2/81

MINI-FANS \$4

RFI tested, muffin-type. 4.5" sq. 110V, #MUFFIN

RFS IC's: Removed from sockets of unused boards, tested, guaranteed, full spec. Partial list, send for full list!

74LS00	.15	74LS197	.70	7804A-RTD	2.45	6116	5.50
74LS02	.15	74LS241	.75	LX301	.28	6505	8.50
74LS04	.15	74LS244	.75	LX308	.81	6508	8.50
74LS05	.15	74LS247	.75	LM317T	1.50	6532	8.00
74LS08	.19	74LS248	1.10	LX318	1.90	6900	2.50
74LS10	.25	74LS251	.45	LX319	1.50	6902	2.50
74LS14	.25	74LS253	.45	LX324	.50	6909	6.95
74LS20	.19	74LS257	.45	LX348	.85	6910	2.50
74LS22	.25	74LS259	1.70	LX351	.85	6921	7.25
74LS27	.29	74LS266	.35	LF356	.99	69445	11.75
74LS28	.29	74LS273	.30	LX393	.60	6950	7.25
74LS32	.40	74LS280	.40	P18	.48	8008	1.00
74LS37	.25	74LS298	.65	NE525	.45	8048	12.50
74LS42	.40	74LS303	1.90	LX356	.60	8080A	1.65
74LS51	.20	74LS363	1.35	NE564	1.50	8095A	4.00
74LS74	.30	74LS368	.35	LX367	.75	8096	17.00
74LS75	.30	74LS373	.35	LX721	.25	8268	17.00
74LS76	.30	74LS374	.30	LM741N/H	.20	8237A	19.95
74LS93	.50	74LS375	.40	LX717	.60	8237	2.50
74LS98	.40	74LS377	.75	9300C	12.60	8233	2.20
74LS99	.40	74LS393	.90	AYS-1013A	3.00	8257	3.50
74LS107	.30	74LS395	1.20	MC1458	.40	8259	5.50
74LS123	.45	EPROMS		1489	.40	8273	12.50
74LS138	.40	1702A	.60	F01735	17.00	8283	7.50
74LS145	.39	2708	.99	COM2017	2.00	8284A	4.75
74LS153	.45	2716(CV)	.99	2101	.45	8289	17.00
74LS154	.90	TMS2516	.99	2102	.45	8289	19.95
74LS155	.40	TMS2716	.99	2103	.45	8325	18.50
74LS158	.40	TMS2720	3.00	2112	1.80	8325	18.50
74LS160	.60	TMS2822	3.00	2114	.60	8748	18.50
74LS161	.45	2724(CV)	3.50	2118	2.60	8749	18.50
74LS163	.40	TMS2764	3.50	2147	1.85	8751	18.50
74LS164	.35	2712B	19.95	2148	4.50	8752A	18.50
74LS173	.45	OTHER ICs		LX390	1.68	75451	.25
74LS174	.40	8798	.70	KE3600PRD	7.50	75454	.25
74LS191	.70	8798	.70	4116	.30	75492	.75
74LS192	.70	Z80-CPU	2.00	4118	3.50		
74LS193	.70	Z80-CPU	3.00	4164-150	1.88		
74LS195	.55	Z80-DMA	7.50	AMS012	.22		

HOW TO ORDER: Order by phone or mail, pay by MC, Visa, Amex, COB, check, min order \$17. Include 1 cent tax for shipping, bal refunded. **GUARANTEED SATISFACTION OR YOUR MONEY BACK** within 30 days of receipt. SEND FOR FREE FILTER! (free removed from equipment)

UNITECH (800)343-0472

IN MASS: (617)UNI-TECH
20R HURLEY ST. CAMBRIDGE, MA 02141

CIRCLE 262 ON FREE INFORMATION CARD

ACTIVE RECEIVING ANTENNA

Gives excellent reception, 50 KHz to 30 MHz.

New MFJ-1024 Active Receiving Antenna mounts outdoors away from electrical noise for maximum signal.

Gives excellent reception of 50 KHz to 30 MHz signals. Equivalent to wire hundreds of feet long. Use any SWL, MW, BCB, VLF or Ham receiver.

High dynamic range RF amplifier. 54 in. whip. 50 foot coax. 20 dB attenuator prevents receiver overload. Switch between two receivers. Select auxiliary or active antenna. Gain control. "ON" LED. Remote unit, 3x2x4 in. Control, 6x2x5 in. 12 VDC or 110 VAC with optional adapter, MFJ-1312, \$9.95.

\$129.95
(+\$4.00 shipping)

Order from MFJ and try it. If not delighted, return within 30 days for refund (less shipping). One year unconditional guarantee.

Order today. Call TOLL FREE 800-647-1800. Charge VISA, MC. Or mail check, money order. Write for free catalog. Over 100 products.

CALL TOLL FREE 800-647-1800

Call 601-323-5869 in Miss., outside continental USA, tech/order/repair info. TELEX 53-4590.

MFJ ENTERPRISES, INCORPORATED

Box 494, Mississippi State, MS 39762

CIRCLE 105 ON FREE INFORMATION CARD

AMAZING DEVICES

PERSONAL DEFENSE AND PROPERTY PROTECTION UTILIZE SPACE AGE TECHNOLOGY. CAUTION THESE DEVICES CAN BE HAZARDOUS AND MAY SOON BE ILLEGAL.

- POCKET PAIN FIELD GENERATOR — IPG50**
Assembled \$64.50
IPG5 Plans \$8.00 IPG5K Kit/Plans \$44.50
- PHASOR PAIN FIELD CROWD CONTROLLER — PPF10**
Assembled \$250.00
PPF1 Plans \$15.00 PPF1K Kit/Plans \$175.00
- BLASTER** - Provides a plasma discharge capable of puncturing a can. Produces a 100,000 WATT PULSE.
ASSEMBLED \$89.50
- BLS10** PLANS \$10.00 BLS1K KIT/PLANS \$69.50
- PLASMA STUN GUN** - Very intimidating and effective 5 to 10 feet 100,000 VOLTS
ASSEMBLED \$99.50
ITM10 PLANS \$10.00 ITM1K KIT/PLANS \$69.50

RUBY LASER RAY GUN — Intense visible red beam burns and welds hardest of metals. **MAY BE HAZARDOUS.**

RUB3All Parts Available for Completing Device \$15.00
CARBON DIOXIDE BURNING, CUTTING LASER — Produces a continuous beam of high energy. **MAY BE HAZARDOUS.**

LC5. All Parts Available for Completing Device. \$15.00
VISIBLE LASER LIGHT GUN — produces intense red beam for sighting, spotting, etc. Hand held complete.

LGU3. Plans. \$10.00 (Kit & Assembled Units Available)
IR PULSED LASER RIFLE — Produces 15-30 watt infra-red pulses at 200-2000 per sec.

LRG3. All Parts & Diodes Available \$10.00
BEGINNERS LOW POWER VISIBLE LASER — Choice of red, yellow, green — provides an excellent source of monochromatic light.

LHC2 Plans \$5.00 **LHC2K** Kit \$34.50

SNOOPER PHONE — Allows user to call his premises and listen in without phone ever ringing.

SNP20 Assembled \$89.50
SNP2 Plans \$9.00 **SNP2K** Plans/Kit \$59.50

LONG RANGE WIRELESS MIKE — Miniature device clearly transmits well over one mile. Super sensitive, powerful.


MFT1 Plans \$7.00 **MFT1K** Plans/Kit \$49.50
WIRELESS TELEPHONE TRANSMITTER — Transmits both sides of phone conversation over one mile, shuts off automatically.

VWPM5 Plans \$8.00 **VWPM5K** Plans/Kit \$39.50
TALK & TELL AUTOMATIC TELEPHONE RECORDING DEVICE — Great for monitoring telephone use.

TAT20 Assembled \$24.50
TAT2 Plans \$5.00 **TAT2K** Plans/Kit \$14.50

Our phone is open for orders anytime. Technicians are available 9-11 a.m., Mon-Thurs for those needing assistance or information. Send \$1.00 for catalog of hundreds more similar devices. Send check, cash, MO, Visa, MC. COD to: **INFORMATION UNLIMITED**
DEPT RB, P.O. Box 716, Amherst, N.H. 03031 Tel: 603-673-4730

CIRCLE 72 ON FREE INFORMATION CARD

 

Let's close the book on forest fires.

Ad Council A Public Service of This Magazine & The Advertising Council



NEW LIQUIDATING GAVILAN COMPUTER CALL FOR GAVILAN 8/16 LINE COMPUTERS

See Below - GAVILAN SPECIALS

**IF YOU DON'T
SEE IT HERE
CALL TOLL FREE**

Corporate Buyers ...
Call For Volume Quotes!

MAIL ORDER PRICING ONLY

64K
UPGRADE
\$24.95

SINCE 1976

1985
CATALOG
Send \$1.00

APPLE COMPATIBLE PERIPHERALS

ALI-CPM 3.0 PLUS CARD	\$299.00
CODEX 16K RAM CARD	39.95
CODEX PAR. PRINTER CARD	49.95
CODEX 80 COL. EXT. 64K CARD	99.95
15 MB PK400 IO (I/O)	139.95
KENNINGTON SYSTEM SAVER	69.95
KENNINGTON PC SAVER	39.95
KRAFT JOYSTICK	36.95
MOT. SPEED DEMON	249.95
MICROSOFT 2.50 SOFTCARD	247.95
GRAPPLER PLUS	99.95
BUFFED GRAPPLER	\$189.95
GRAPPLER SUPER	SALE \$119.95
VIDEO 7 RGB IN. I/O	189.95
APPLE II SERIAL CABLE	36.95
APPLE II KEYBOARD	49.95
APPLE II POWER SUPPLY	59.95
APPLE II DISK CONTROLLER	49.95
APPLE II SPEECH SYSTEM	99.95
APPLE II COOLING FAN SYSTEM	49.95
TITAN ACCELERATOR II CARD	449.95
WOZZARD 80 COLUMN CARD	SALE 99.00

FARADAY IBM PC'S

CPU Board w/4K MS-DOS Compatible
\$299.95

IBM PC HARDWARE

AST "COMBOPLUS" 64K	\$199.00
HIGH "MAXIMIZER" 64K	249.95
BIOS/DISK CONTROLLER	249.95
BARDISK DISK CONTROLLER	249.95
10 MB INTERNAL HARD DISK	895.00
10 MB EXTERNAL HARD DISK	605.00
10 MB INTERNAL HARD DISK	849.00
15 MB EXTERNAL HARD DISK	1049.00
90 WATT BOOSTER SUPPLY	149.95
120 WATT IBM SUPPLY	159.95
PC COMPATIBLE KEYBOARD	99.00
IBM PC CHASSIS	129.95
PLANTRONICS "COLORPLUS"	389.95
10 MB INT. TAP. STREAMER	499.00
PERYST MONO CARD	199.00
PARADISE MONO/COLOR	409.00
HERCULES MONO CARD	369.95

ROCKWELL AIM

6502 Single Board Computer
\$249.00

S-100 SALE ITEMS

KEYTRONIC 5150/51	158.00/199.00
MOUSE SYSTEMS MOUSE W/5W	149.95
QUADBOARD W/RAK	263.00
TECMAR GRAPHICS MASTER	499.00
TECMAR CAPTAIN 64K	319.00
CURTIS PC PEDESTAL	39.00
POS or C/JUNCTION ADAPTOR	49.00
TILT and SWIVEL STAND	21.00
SYSTEM STAND	21.00
EXTENSION CABLE IBM MONO	38.00
KEYBOARD EXTENSION CABLE	20.00
SURGE SUPPRESSORS:	
DIAMOND (LEMON)	39.00
PSB or C/JUNCTION	49.00
SAPPHIRE (PEACH)	59.00
RUBY (ORANGE)	69.00
CODEX 384K MULTICARD w/OK	169.00

INTERNAL STD-BUS BOARDS

ISB3100 280 CPU	\$200	\$99.95
ISB3101 280 Univ. CPU	200	99.95
ISB3110 8086 CPU	200	79.95
ISB3216 16K CMOS RAM	610	99.95
ISB3218 16K 8088 RAM	200	39.95
ISB3220 16K CMOS RAM	750	119.95
ISB3330 280 PIO (I/O)	210	49.95
ISB3331 Universal PIO	210	49.95
ISB3340 Cpu Opt. Input	300	149.95
ISB3400 Floppy Controller	215	79.95
ISB3410 SASI (DMA) W/Int. Interf.	255	99.95
ISB3500 Trap	215	99.95
ISB3510 Cpu-to-IO Input	270	119.95
ISB3520 SPST Relay	150	99.95
ISB3521 DPDT Relay	190	99.95
ISB3600 Arithmetic	375	179.95
ISB3610 EPROM Programmer	300	79.95
ISB3700 Sync/Async	245	69.95
ISB3711 Univ. Sync/Async	245	69.95
ISB3720 REMOADS	215	149.95
ISB3830 12 Bi. A/D	720	269.95

MONITORS

AMDEK 3000 (GREEN)	\$139.95
AMDEK 300A (AMBER)	149.95
AMDEK 310A (IBM AMBER)	169.95
CALL FOR COLOR & NEW MODELS	
PGS M-12 (IBM COLOR)	69.95
PGS SF-12 (H-RES)	59.95
PGS M-12 (IBM GREEN)	198.95
PGS DOUBLE BOARD	227.00
TAXAN 420 (H-RES IBM)	89.95
ZENITH 122A/123G	89.95
ZENITH ZVM3131/35	Call
SANYO 6500 (MED RES)	279.00
SANYO 7500 (H-RES)	379.00
SANYO (LOOKALIKE) 12" AMBER SALE	74.95

MODEMS

BIZCOMP - PC INTELLIMODEM (INT)	\$349.95
HAYES SMARTMODEM (EXT)	469.95
HAYES SMARTMODEM 1200B (INT)	399.95
HAYES SMARTMODEM 300 (EXT)	299.95
MICROMODEM APPLE II	49.95
PROMETHEUS 1200 (MACINTOSH)	459.95
PROMETHEUS 1200 (PC)	369.95
NOVATION ACCESS 2-3	199.95
CAT COMMUNICATIONS SYSTEM	419.95
APPLE COMP. LOW COST MODEM (300) 49.95	

HARD DISKS

SEAGATE ST506 (5MB)	\$269.00
SEAGATE ST149 (15MB)	449.00
SEAGATE ST104B/GT212	449.00
CALL FOR 15, 25MB	
ROCKWELL 10, 15, 22MB	Call
SHUGART SA604 (5MB)	149.95
SYQUEST REMOVABLE	Call

CALL FOR QUOTE ON HIGHER CAPACITY HARD DRIVES!

SUPER SAVER SHUGART SA604 HARD DISK

5Mb \$129.95

NEW FACTORY Qty 119.95
DIRECT Qty 109.95

DISK DRIVES

SHUGART 8" DISK DRIVES	\$269.95
SIEMENS FD010-8	129.95
SIEMENS FD200-8 DS/D0	195.00
MITS M2894	143.95
MITS M2896 1/4H	143.95
TANDON 848E 1/4H	369.95
QUCO 242 1/4H	369.95

DRIVE CABINETS

5" CASE POWER SUPPLY	\$69.95
5" DUAL 1/4H. W/POWER SUPPLY	79.95
5" DUAL CASE W/POWER SUPPLY	279.95
8" THINLINE DUAL W/POWER SUPPLY	199.95
5" HARD DISK W/POWER SUPPLY	199.95
5" 1/4 HIGH HARD DISK	199.95

APPLE DISK DRIVES

APPLE II COMPATIBLE	\$174.95
APPLE II COMPATIBLE w/ HIGH	164.95
MICRODISK APPLE II DRIVE	219.95
APPLE II w/ APPLE II CAPTOR	199.95
APPLE II DISK CONTROLLER	49.95

NOTICE TO DEALERS - We Will Pay Top Dollar For Your Excess Inventory

6800

68000	\$48.95	68010	\$ 2.85	68050	\$ 3.25
68000A	99.95	68020	4.75	68060	6.65
68001	2.90	68021	1.90	68060	7.90
68002	7.75	68028	14.50	68075	6.75
68003	18.95	68040	12.75	68080	2.20
68009E	14.50	68045	14.95		

6500

6502	\$4.50	6504	\$6.75	6522	\$6.75
6502A	6.00	6507	9.75	6522	9.50
6502B	9.50	6520	4.25	6551	11.50

8000

8035	\$ 5.75	8214	\$ 3.75	8259	\$ 6.75
8000	6.75	8219	6.95	8271	69.95
8080A	2.95	8224	2.20	8275	26.95
8085A	4.90	8226	1.96	8279	6.75
8085B	9.95	8228	3.40	8282	6.25
8095	24.50	8237	14.75	8283	6.25
8097	129.95	8237.5	18.95	8284	5.50
8088	29.50	8238	4.25	8286	6.45
8089	88.95	8239	6.50	8287	6.75
8155	6.75	8206	10.50	8288	14.45
8156	6.75	8251	4.25	8289	44.95
8185	26.95	8251A	6.95	8292	15.95
8202	33.95	8253	6.75	87	37.95
8203	3.25	8255	4.25	8748	24.60
8205	3.25	8255A	6.95	8749	24.60
8212	9.95	8257	5.75	8755A	34.95

Z-80

Z80-CPU	2.95	4.35	9.50
Z80-CTC	3.75	4.75	12.25
Z80-DART	11.25	12.25	15.00
Z80-DMA	12.95	11.95	17.95
Z80-DPO	2.95	4.25	12.50
Z80-SIOB	11.25	12.25	15.00
Z80-SIOA	11.95	12.75	15.00
Z80-SIOB	11.95	12.75	36.95
Z80-SIOA	11.95	12.75	

DISK CONTROLLERS

Z8030 34.95	Z8001 53.95	Z8132 33.95
Z8030 34.95	Z8002 34.95	Z8071 37.95

CRT CONTROLLERS

6845 84.95	8225 58.50	8359 139.50
6845 84.95	8226 39.95	8360 39.95
6847 11.50	8207 17.95	8545 14.95
46505 14.70	5037 21.95	8502 19.95
69047 24.50	NEC2220 Graphics	36.95

TRANSISTORS/DIODES

PN2222A 7/51.00	2N3904 11/51.00
PN2399A 5/1.00	2N3906 11/11.00
PN2918 3/1.00	2N2904 2/1.00
2N2219A 4/5	2N2906 2/1.00
2N2905 4/5	2N2907 2/1.00
2N2907 2/5	1N4148 2/51.00
2N3055 6/9	1N751 5/1.00
2N3638 4/1.00	1N4002 12/1.00
2N3638 4/1.00	1N4004 10/1.00
2N3772 1/5	1N4007 2/5

OPTO ISOLATORS

MCT-2	1.50	4N33	5.89
MCT-6	1.99	4N35	1.25
4N35	1.25	4N37	1.25
MCA-255	1.69	4N38	98
4N26	1.50	TL117	78
4N27	85	4N29	49.95
4N28	69	4N25	5/1.00

LED LAMPS

Jumbo Red	\$ 0.99	100
Jumbo Green	17	15
Jumbo Yellow	17	15
Mini Size Red	10	10.09
Mini Size Green	10	10.09
Mini Size Yellow	19	16

EDGE CONNECTORS

S-100 ST	1.99	100
S-100 HW	33.95	33.25
S-100 WW	4.75	4.10
44 Pin ST	2.75	2.60
44 Pin HW	6.50	6.10
72 Pin ST	6.75	6.30
72 Pin HW	7.25	6.95

D-SUBMINIATURE

DB25S Female	53.10	28
DB25P Male	2.40	2.29
Hood \$1.25	Mfg HW \$ 99	
DE37S Female	59.95	75
DE37P Male	5.25	5.10
Hood \$1.75	Mfg HW \$ 99	
DO50S Female	58.95	65.65
DO50P Male	6.00	5.75
Hood \$3.25	Mfg HW \$ 99	

GAVILAN SPECIALS

8 or 16 LINE COMPUTERS	Call
16 LINE BY LCD DISPLAY	\$79.95
S LINE BY 80 LCD DISPLAY	39.95
THERMAL PRINTER MICROMAN	14.95
GAVILAN/IBM KEYBOARDS	14.95
8 1/2 x 11 THERMAL PAPER (500 sheet)	2.99
12V Ni-CAD BATTERY-PAN/AL	14.95
20 MHz CRYSTAL OSCILLATOR	3.95

SUPER SAVER IBM PC'S

Comp. DOS/IO Disk Drive
\$89.95

HI-TECH SPECIALS AMD7910

300 BAUD MODEM IC
\$29.95

DATA ACQUISITION

ADC0808 \$14.95	ADC0817 \$9.75	1408L6 \$1.95
ADC0809 3.00	DAC0808 2.95	1408L8 5.60
DAC0806 1.90	DAC0808 2.85	DAC100 7.95
ADC0809 4.45	DAC1002 7.95	DAC08 7.95
ADC0816 14.25	DAC1052 5.95	DAC01 6.95
AD7523-AN 1.99	LF398N 1.99	LF1301IN 2.95


LINEAR

LM108AH \$3.95	NE990 \$2.45	LM3509 98
LM3090 99	NE992 2.70	LM3314 \$2.95
LM3011 35	LM709H 95	LM3915 2.95
LM304H 189	LM709H 1.90	LM3916 2.95
LM3059 95	LM710 68	MC4004 3.75
LM3068 4.75	LM711 75	MC4044 3.50
LM3070 40	LM715 3.95	RC4131 3.75
LM3080 35	LM723H 35	RC4136 1.19
LM3100 1.05	LM723H 75	RC4153 3.75
LM3112 1.75	LM737 98	CA3023 2.75
LM3124 1.45	LM742N 1.85	CA3039 1.25
LM3181 1.55	LM741H 40	CA3059 2.85
LM319N 1.19	LM741N 29	CA3060 2.85
LM3200 95	LM750H 2.95	RC4136 1.19
LM324N 55	LM748 55	CA3080 1.10
LM3399 95	LM1014 1.15	CA3081 1.60
LM340 (see YF8)	LM3503 1.90	CA3082 1.60
LM348N 1.45	LM747C 2.35	CA3083 1.55
LM358C 65	MC1330 1.65	CA3088 8.00
LM359 1.75	MC1349 1.85	CA3089 2.95
LM3609 2.95	MC1350 3.45	CA3096 3.45
LM370N 4.95	MC1358 1.65	CA3130 3.50
LM373N 3.95	MC1372 6.75	CA3140 1.60
LM376N 3.75	LM1414 1.55	CA3146 1.79
LM377N 1.90	LM2901 3.75	TL072CP 1.90
LM3800 65	LM1800 2.35	LM13090 1.25

Radio Shack Parts Place®

The Store for Builders. Over 1000 Items in Stock!

 The Shack® Has the Factory-Fresh ICs You Need



Speech Synthesizer. SPO256-AL2. Now you can teach your microcomputer to talk! This MOS LSI device uses a program stored in its built-in 16K ROM to synthesize natural sounding speech. Easy to interface with most computers. 28-pin DIP with detailed data. Requires external components available at Radio Shack, not incl. #276-1784 .. **12.95**

LM567 PLL/Tone Detector. Ideal for Touch-Tone, remote control and communications decoding. Operates from 0.01 Hz to 500 kHz. Low-cost external components set center frequency, bandwidth, output delay. 8-pin DIP with data. #276-1721 .. **1.99**

Low-Power Op Amps. Silicone-gate CMOS. Very low power drain. Ideal for battery-powered circuits.


Type	DIP	Cat. No.	Each
TLC271 (Single)	8-pin	276-1748	1.59
TLC272 (Dual)	8-pin	276-1749	2.19
TLC274 (Quad)	14-pin	276-1750	2.99

LM386. Low-voltage amplifier for 8-ohm loads requires minimum support parts—ideal for projects and replacement use in battery-powered devices. 400 mW output. 4 to 12 VDC. 8-pin DIP. #276-1731 .. **1.09**

1/4-Watt, 5% Resistors

39¢


Pkg. of 5

 

Ohms	Cat. No.
10	271-1301
100	271-1311
150	271-1312
220	271-1313
270	271-1314
330	271-1315
470	271-1317
1k	271-1321
1.8k	271-1324
2.2k	271-1325
3.3k	271-1328
4.7k	271-1330
6.8k	271-1333

Ohms	Cat. No.
10k	271-1335
15k	271-1337
22k	271-1339
27k	271-1340
33k	271-1341
47k	271-1342
68k	271-1345
100k	271-1347
220k	271-1350
470k	271-1354
1 meg	271-1356
10 meg	271-1365

Pre-Drilled PC Boards and Accessories

 

(1) **Multi-Purpose Plug-In Board.** Poly-glass material withstands circuit changes. 4 1/2 x 4" with 1/16" grids. Fits 44-pin socket. #276-152 .. **2.99**

(2) **3-Voltage Source Board.** Above with 3 buses. Ideal for op-amps. #276-154 .. **2.99**

(3) **44-Position Socket.** For above. #276-1551 .. **2.99**

(4) **Grid Board.** 2200 solder-ringed holes on .100 x .100 centers for DIP ICs, sockets. Indexed to help you identify component pin outs. 4 1/2 x 6 5/8". #276-147 .. **2.99**

(5) **16-Position DIP Header.** You can mount resistors, capacitors, jumpers and more in this header that fits 16-pin DIP sockets. With cover. #276-1980 .. **1.69**

Electronics Textbook

NEW! 795



Basic Electronics Technology. The "hows" and "whys" of modern electronics presented in plain language. Learn how semiconductors work as amplifiers, oscillators, in power supplies, radio/TV, and computers. Illustrated. 464 pages. #62-1394

Developed by Texas Instruments Learning Center

4000-Series CMOS ICs

With Pin-Out and Specs



Type	Cat. No.	Each
4001	276-2401	.99
4011	276-2411	.99
4013	276-2413	1.19
4017	276-2417	1.49
4049	276-2449	1.19
4066	276-2466	1.19

Solid-State Sound Makers



Electronic Chime. Familiar "ding-dong" sound. Operates on 1 1/2 VDC at 30 mA. 4 3/4" leads. #273-067 .. **6.95**

Piezo Pulsing Buzzer. Selectable continuous or pulsing mode. Only 10 mA at 12 VDC. Fits 1 1/16" dia. hole. #273-068 .. **6.95**

Submini Toggle Switches

Low **189**
As

10 amps at 125 VAC. Each includes 4 colored handle covers. 1/2 x 7/16 x 1/2". Mount in 1/4" holes.

Type	Cat. No.	Each
SPST	275-324	1.89
SPDT	275-326	1.99
SPDT Center-Off	275-325	2.19



TTL Digital ICs

With Pin-Out and Specs



Type	Cat. No.	Each
7400	276-1801	.89
7404	276-1802	.99
7408	276-1822	1.29
7447	276-1805	1.69
7490	276-1808	1.19

Heavy-Duty AC Line Filter

SALE! Reg. 7.95 577

Rated 250 VAC at 5 Amps, 50/60 Hz



Keeps RF interference from being conducted into equipment (or from equipment) through the AC power line. Ideal for computers, transceivers. 2 3/8" mounting centers. U.L. recognized. #273-103

Sale! TV RF Modulator

30% Off
Reg. 9.95 **695**



UM1285-8. Accepts video and sound from computers, satellite receivers, TV cameras, projects. Selectable channel 3 or 4 output. Requires 6 VDC, a shielded enclosure and a few low-cost external components to build a complete system. With pin-out and data. #277-221

SPECIAL PURCHASE Continuity Tester Chassis



Circuit continuity produces a warbling tone. Can be the heart of a moisture alarm, capacitor/diode checker or ???. Use your imagination! Requires 9V battery. #277-1014 .. **1.95**

Compact 25-Range Folding Multimeter

2995

Detented Hinge With Hold Positions at 90, 120, 150 And 180°



"Big-meter" features include fuse and surge-absorber protection, 4" three-color mirrored meter with automatic shunt protection (when case is closed). 20,000 ohms per volt DC sensitivity. DC volts: 0 to 1200, 7 ranges. AC volts: 0 to 1200, 5 ranges. DC current to 300 mA, 4 ranges. Resistance to 2 megohms. 7 1/4 x 4 5/16 x 1 1/4" when open. With leads and manual. Requires "AA" battery. #22-211 .. **29.95**


Radio Shack®
A DIVISION OF TANDY CORPORATION

Prices apply at participating Radio Shack stores and dealers

UNBELIEVABLE PRICES!

MODEM \$69⁹⁵

FOR APPLE OR IBM

 

SPECIFY IBM OR APPLE WHEN ORDERING

INCLUDES ASCII PRO-EZ™ MENU DRIVEN SOFTWARE
(AT LEAST A \$100 VALUE IN ITSELF!)


- * FCC APPROVED
- * BELL SYSTEM 103 COMPATIBLE
- * 300 BAUD
- * AUTO-DIAL/AUTO-ANSWER
- * DIRECT CONNECT
- * INCLUDES AC ADAPTOR

TAXAN MODEL 415

RGB

VISION III
MONITOR

 ORIGINALLY
MADE FOR
ACORN COMPUTER
SAME SPECS AS
THE TAXAN 420



- * 18 Mhz BANDWIDTH
- * 640 x 262 PIXEL RESOLUTION
- * 16 COLORS
WITH INTENSITY CONTROL
- * 12" BLACK MATRIX
- * IBM AND LOTUS COMPATIBLE

\$299⁹⁵

RGB MONITOR CABLE FOR IBM \$15.95

IBM COMPATIBLE INTERFACE CARDS

MADE IN THE USA BY INTERSIL SYSTEMS

COLOR/GRAPHICS

- * SUPPORTS COMPOSITE
OR RGB MONITOR
- * OPERATES IN ALPHANUMERIC
OR ALL-POINTS-ADDRESSABLE
GRAPHICS MODE
- * SUPPORTS 16 COLORS
- * CONTAINS LIGHT PEN INTERFACE

\$129⁹⁵

MONOCHROME DISPLAY ADAPTOR

- * 720 x 350 PIXEL SCREEN
(80 CHARACTERS x 25 LINES)
- * CHARACTER ATTRIBUTES:
BLINK, UNDERLINE, REVERSE
VIDEO, INTENSIFIED
- * STANDARD TTL OUTPUT

\$149⁹⁵

CIRCLE 273 ON FREE INFORMATION CARD

JDR Microdevices

1224 S. Bascom Avenue, San Jose, CA 95128

800-538-5000 • 800-662-6279 (CA) • (408) 995-5430

FAX (408) 275-8415 • Telex 171-110

© Copyright 1985 JDR Microdevices

RETAIL STORE - 1256 S. BASCOM AVENUE
HOURS: M-W-F, 9-5 TU-TH, 9-9 SAT, 10-3

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING

TERMS: Minimum order \$10.00. For shipping and handling include \$2.50 for UPS Ground and \$3.50 for UPS Air. Orders over 1 lb. and foreign orders may require additional shipping charges - please contact our sales department for the amount. CA. residents must include 6% sales tax. Bay Area and LA residents include 6 1/2%. All merchandise is warranted for 90 days unless otherwise stated. Prices are subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturer. All merchandise subject to prior sale.

PARTIAL LISTING ONLY- PLEASE CALL OR WRITE FOR FREE CATALOG.

STATIC RAMS

2112	256x4 (450ns)	2.99
2114	1024x4 (450ns)	8/9.95
2114-25	1024x4 (250ns)	8/10.95
2114L-4	1024x4 (450ns)(LP)	8/12.95
2114L-3	1024x4 (300ns)(LP)	8/13.45
2114L-2	1024x4 (200ns)(LP)	8/13.95
TMM2016-200	2048x8 (200ns)	3.25
TMM2016-150	2048x8 (150ns)	3.75
TMM2016-100	2048x8 (100ns)	4.75
HM6116-4	2048x8 (200ns)(cmos)	3.69
HM6116-3	2048x8 (150ns)(cmos)	3.95
HM6116LP-4	2048x8 (200ns)(cmos)(LP)	3.95
HM6116LP-3	2048x8 (150ns)(cmos)(LP)	4.25
HM6264P-15	8192x8 (150ns)(cmos)(LP)	10.25

LP = Low Power

DYNAMIC RAMS

4116-250	16384x1 (250ns)	8/6.95
4116-200	16384x1 (200ns)	8/8.95
4116-150	16384x1 (150ns)	8/10.95
4164-200	65536x1 (200ns)(5v)	9/14.95
4164-150	65536x1 (150ns)(5v)	9/16.95
TMS4164	65536x1 (150ns)(5v)	7.95

5v = Single 5 Volt Supply

EPROMS

2708	1024x8 (450ns)	3.95
2716	2048x8 (450ns)(5v)	3.95
2716-1	2048x8 (350ns)(5v)	4.95
TMS2532	4096x8 (450ns)(5v)	4.95
2732	4096x8 (450ns)(5v)	4.25
2732A-4	4096x8 (400ns)(5v)(21vPGM)	4.95
2732A-35	4096x8 (350ns)(5v)(21vPGM)	4.95
2732A	4096x8 (250ns)(5v)(21vPGM)	6.95
2732A-2	4096x8 (200ns)(5v)(21vPGM)	10.95
2764	8192x8 (450ns)(5v)	4.95
2764-250	8192x8 (250ns)(5v)	5.25
2764-200	8192x8 (200ns)(5v)	8.95
27128	16384x8 (250ns)(5v)	7.95
27256	32768x8 (250ns)(5v)	19.95

5v = Single 5 Volt Supply
21vPGM = Program at 21 Volts

**SPECTRONICS CORPORATION
EPROM ERASERS**

	Timer	Chip Capacity	Intensity (uW/Cm ²)	
PE-14		9	8,000	83.00
PE-14T	X	9	8,000	119.00
PE-24T	X	9	9,600	175.00

8000

8035	5.95
8039	5.95
8080	3.95
8085	4.95
8085A-2	11.95
8087-3	129.00
8087-6	119.00
8088	19.95
8155	6.95
8155-2	7.95
8156	6.95
8748	24.95
8755	24.95

8200

8203	39.95
8205	3.50
8212	1.80
8216	1.75
8228	3.49
8237-5	15.95
8243	4.45
8250	10.95
8251A	4.49
8253	6.95
8253-5	7.95
8255	4.49
8255-5	5.25
8259	6.90
8259-5	7.50
8272	19.95
8275	29.95
8279	6.95
8282	6.50
8284	5.50
8286	6.50
8288	14.95

Z80

Z80-CPU	2.49
Z80-CTC	2.95
Z80-PIO	2.95
Z80-SIO/0	9.95

4.0 Mhz

Z80A-CPU	2.49
Z80A-CTC	3.95
Z80A-DART	8.95
Z80A-PIO	3.95
Z80A-SIO/0	10.95

6.0 Mhz

Z80B-CPU	8.95
----------	------

6500

6502	4.95
6520	2.95
6522	5.49
6532	9.95
6551	9.95
6502A	5.95
6522A	9.95
6551A	11.95

6800

68000-8	39.95
6800	2.95
6802	7.95
6809	8.95
6809E	8.95
6821	2.95
6845	12.95
6850	3.25
6883	22.95

DISK CONTR

1771	15.95
1791	23.95
1793	23.95
UPD765	19.95

INTERFACE

8T26	1.59
8T72	1.98
DM8131	2.95
DP8304	2.29

CLOCK CHIPS

MM5314	4.95
MM5369	1.95
MM58167	8.95
MSM5832	3.95

DATA ACQ

ADC0804	3.49
ADC0809	4.49
ADC0817	9.95
DAC0808	2.95
MC1408L8	2.95

SOUND CHIPS

76477	3.95
76488	5.95
AY3-8910	12.95
SSI263	39.95

74LS00

74LS00	.24	74LS157	.65
74LS01	.25	74LS158	.59
74LS02	.25	74LS160	.69
74LS03	.25	74LS161	.65
74LS04	.24	74LS163	.65
74LS05	.25	74LS164	.69
74LS08	.28	74LS165	.95
74LS09	.29	74LS166	1.95
74LS10	.25	74LS169	1.75
74LS11	.35	74LS173	.69
74LS12	.35	74LS174	.55
74LS13	.45	74LS191	.89
74LS14	.59	74LS192	.79
74LS20	.25	74LS193	.79
74LS21	.29	74LS194	.69
74LS26	.29	74LS195	.69
74LS27	.29	74LS197	.79
74LS32	.29	74LS221	.89
74LS33	.55	74LS240	.95
74LS37	.35	74LS241	.99
74LS38	.35	74LS242	.99
74LS40	.25	74LS243	.99
74LS42	.49	74LS244	1.29
74LS47	.75	74LS245	1.49
74LS51	.25	74LS251	.59
74LS73	.39	74LS253	.59
74LS74	.35	74LS257	.59
74LS75	.39	74LS258	.59
74LS76	.39	74LS259	2.75
74LS85	.69	74LS260	.59
74LS86	.39	74LS266	.55
74LS90	.55	74LS279	.49
74LS92	.55	74LS280	1.98
74LS93	.55	74LS283	.69
74LS107	.39	74LS290	.89
74LS109	.39	74LS293	.89
74LS112	.39	74LS299	1.75
74LS122	.45	74LS323	3.50
74LS123	.79	74LS365	.49
74LS124	2.90	74LS367	.45
74LS125	.49	74LS368	.45
74LS126	.49	74LS373	1.39
74LS132	.59	74LS374	1.39
74LS136	.39	74LS377	1.39
74LS138	.55	74LS390	1.19
74LS139	.55	74LS393	1.19
74LS145	1.20	74LS640	2.20
74LS148	1.35	74LS645	2.20
74LS151	.55	74LS670	1.49
74LS153	.55	74LS682	3.20
74LS154	1.90	74LS688	2.40
74LS155	.69	81LS95	1.49
74LS156	.69	25LS2521	2.80

7400

7400	.19	7492	.50
7401	.19	7493	.35
7402	.19	74100	1.75
7403	.19	74107	.30
7404	.19	74116	1.55
7405	.25	74121	.29
7406	.29	74122	.45
7407	.29	74123	.49
7408	.24	74125	.45
7409	.19	74126	.45
7410	.19	74132	.45
7411	.25	74145	.60
7413	.35	74148	1.20
7414	.49	74150	1.35
7416	.25	74151	.55
7417	.25	74153	.55
7420	.19	74154	1.25
7421	.35	74155	.75
7425	.29	74157	.55
7427	.29	74159	1.65
7430	.19	74161	.69
7432	.29	74163	.69
7437	.29	74164	.85
7438	.29	74165	.85
7442	.49	74166	1.00
7445	.69	74173	.75
7447	.69	74174	.89
7448	.69	74175	.89
7473	.34	74185	2.00
7474	.33	74192	.79
7475	.45	74193	.79
7476	.35	74194	.85
7483	.50	74259	2.25
7485	.59	74367	.65
7489	2.15	74368	.65
7490	.35	74393	1.35

74S00

74S00	.32
74S02	.35
74S04	.35
74S05	.35
74S08	.35
74S10	.35
74S11	.35
74S20	.35
74S32	.40
74S37	.88
74S74	.50
74S86	.50
74S112	.50
74S124	2.75
74S132	1.24
74S133	.45
74S138	.85
74S139	.85
74S140	.55
74S151	.95
74S153	.95
74S157	.95
74S158	.95
74S161	1.95
74S163	1.95
74S174	.95
74S175	.95
74S240	2.20
74S241	2.20
74S242	2.20
74S280	1.95
74S287	1.90
74S288	1.90
74S373	2.45
74S374	2.45
74S471	4.95

★★★★HIGH-TECH★★★★

8087-6 \$119.00

- * 4.87 MHz VERSION
- OF 8087 MATH COPROCESSOR
- * IBM-PC COMPATIBLE
- * RUNS TURBO PROGRAMS AS MUCH AS 100 TIMES FASTER THAN 8088 ALONE

★★★★SPOTLIGHT★★★★

CRYSTALS

32.768Khz	1.95
1.0Mhz	3.95
1.8432	3.95
2.0	2.95
2.4576	2.95
3.579545	2.95
4.0	2.95
5.0	2.95
5.0688	2.95
6.0	2.95
6.144	2.95
8.0	2.95
10.0	2.95
10.738635	2.95
14.31818	2.95
15.0	2.95
16.0	2.95
17.430	2.95
18.432	2.95
20.0	2.95

UARTS

AY5-1013	3.95
AY3-1015	6.95
TR1602	3.95
2651	8.95
IM6402	7.95

BIT-RATE GENERATORS

BR1941	11.95
4702	12.95
COM8116	10.95
14411	11.95

MISC.

3242	7.95
MC3470	4.95
MC3487	2.95
AY5-3600 PRO	11.95
HD46505SP	15.95
CRT5027	19.95

LINEAR

TL084	2.19	NE564	2.95
LM301	.34	LM565	.99
LM307	.45	LM566	1.49
LM308	.69	NE592	.98
LM309K	1.25	LM733	.98
LM310	1.75	LM741	.35
LM311	.64	LM747	.69
LM317T	1.19	LM1310	1.49
LM317K	3.95	MC1330	1.69
LM318	1.49	MC1372	6.95
LM323K	4.95	LM1458	.59
LM324	.59	LM1488	.69
LM331	3.95	LM1489	.69
LM334	1.19	LM1496	.85
LM335	1.40	LM1800	2.37
LM336	1.75	LM1812	8.25
LM337T	1.95	LM1889	1.95
LM338K	3.95	ULN2003	1.29
LM339	.99	XR2206	3.75
LM348	.99	XR2211	5.25
LM350K			

PARTIAL LISTING ONLY- PLEASE CALL OR WRITE FOR FREE CATALOG.

**CAPACITORS
ELECTROLYTIC
RADIAL AXIAL**

47uf	50v .14	10	50v .16
10	50v .15	22	16v .14
47	35v .18	47	50v .20
100	16v .18	100	15v .20
220	35v .20	150	25v .25

50v MONOLITHIC

.01uf	.14	.1	.18
.047	.15	.47	.25

50v DISC

10pf	.05	470	.05
22	.05	560	.05
25	.05	680	.05
27	.05	820	.05
33	.05	.001uf	.05
47	.05	.0015	.05
56	.05	.0022	.05
68	.05	.005	.05
82	.05	.01	.07
100	.05	.02	.07
220	.05	.05	.07
330	.05	.1	.12

BYPASS CAPS

.01uf disc	50v	100/6.00
.1uf disc	12v	100/8.00
.01uf mono	50v	100/12.00
.1uf mono	50v	100/15.00

IC SOCKETS

1-99	100
8 pin ST	.13 .11
14 pin ST	.15 .12
16 pin ST	.17 .13
18 pin ST	.20 .18
20 pin ST	.29 .27
22 pin ST	.30 .27
24 pin ST	.30 .27
28 pin ST	.40 .32
40 pin ST	.49 .39
64 pin ST	4.25 call
ST-SOLDERTAIL	
8 pin WW	.59 .49
14 pin WW	.69 .52
16 pin WW	.69 .58
18 pin WW	.99 .90
20 pin WW	1.09 .98
22 pin WW	1.39 1.28
24 pin WW	1.49 1.35
28 pin WW	1.69 1.49
40 pin WW	1.99 1.80
WW-WIREWRAP	
16 pin ZIF	4.95 call
24 pin ZIF	5.95 call
28 pin ZIF	6.95 call
ZIF-TEXTOL (Zero Insertion Force)	

**ACCESSORIES & PERIPHERALS
FOR IBM**

MAXIMIZER Memory Multifunction	259.95
HAYES SMARTMODEM 1200B	419.95
130W POWER SUPPLY	159.95
TEAC FD-55B 1/2 Ht. Disk Drive, DS/DD	119.95
MPI-B52 5 1/4" FDD, DS/DD	109.95
PROTOTYPE CARD	27.95
PROTOTYPE CARD With Decoding	29.95

FOR APPLE

JDR 16K RAM CARD	39.95
EPROM PROGRAMMER RP525	79.95
PRINTMAX Parallel printer interface	49.95
BAL-500 1/2 Ht. Disk Drive, Teac Mechanism	159.95
BAL-525 1/2 Ht. Disk Drive, Alps Mechanism	139.95
MITAC AD-1 Full Height, Shugart Mechanism	149.95
DISK CONTROLLER CARD	49.95
VIEWMAX-80 80 Column For Apple II-	159.95
VIEWMAX-80e 80 Column For Apple IIe	129.95
THUNDERCLOCK Official PRODOS Clock	129.95
KRAFT JOYSTICK	39.95
60W POWER SUPPLY	49.95

MISCELLANEOUS

ZENITH ZVM-123 15 MHz Green Monitor	105.00
NEC JB1201M 20 MHz Green Monitor	169.00
BMC BM-AU9191U Comp. 13" Color Monitor	279.00
BMC BX-80 PRINTER	199.95
NASHUA DISKETTES SS/SD Box of 10	19.95
VERBATIM DATALIFE DISKETTES DS/DD	34.95
DISKETTE FILE Holds 70 Diskettes	9.95

BARGAIN HUNTERS CORNER

DYNAMIC RAMS

4164 200ns \$.99 ea.
100 PIECE MINIMUM

41256 150ns \$5.99 ea.
27 PIECE MINIMUM

SPECIALS END 7/31/85

SWITCHING POWER SUPPLIES

P3-ASTEC	P3-3
MODEL AA 12110	ASTEC AA11190
+12V @ 2A	+5V @ 4A
-12V @ .1A	+12V @ 2.5A
+5V @ 2.5A or	-5V @ .25A
5A if 12V not used	-12V @ .30A
19.95	39.95

5 1/4" DISK DRIVES

TANDON TM100-2	DS/DD	159.95
SHUGART SA400L	SS/DD	199.95
MPI B52	DS/DD	109.95
TEAC FD55B 1/2 Ht.	DS/DD	129.95
TEAC FD55F 1/2 Ht.	DS/Quad	139.95

8" DISK DRIVES

SIEMENS FD200-8	DS/DD	180.00
SIEMENS FD100-8	SS/DD	129.00

BEST SELLING IDC CONN.

RIBBON HEADER SOCKETS			
IDS 20	2.25	IDS 40	1.99
IDS 26	1.39	IDS 50	2.25
IDS 34	1.59		
RIBBON EDGE CARDS			
IDE 20	2.25	IDE 40	3.80
IDE 26	2.65	IDE 50	3.95
IDE 34	2.75		

**LIGHT EMITTING DIODES
JUMBO DISPLAYS**

	1-99	100-up	MAN-72 CA .3"	.99
RED	.10	.09	MAN-74 CC .3"	.99
GREEN	.18	.15	FND-500 CC .5"	1.49
YELLOW	.18	.15	FND-507 CA .5"	1.49

D-SUBMINIATURE

DESCRIPTION	ORDER BY	CONTACTS				
		9	15	25	37	
SOLDER CUPS	MALE	DBxxP	1.19	1.59	1.90	2.85
	FEMALE	DBxxS	1.50	1.85	2.25	3.90
RT. ANGLE	MALE	DBxxPR	1.65	2.20	3.00	4.83
PC SOLDER	FEMALE	DBxxSR	2.18	3.03	3.00	6.19
IDC	MALE	IDBxxP	2.95	3.90	4.75	6.95
RIBBON CABLE	FEMALE	IDBxxS	3.25	4.29	5.25	7.95
HOODS	BLACK	HOOD-B	---	---	.99	---
	GREY	HOOD-xx	.89	.99	.99	1.09

MOUNTING HARDWARE-\$1.00
ORDERING INSTRUCTIONS: INSERT # OF PINS INTO "xx"

9000

9334	2.50
9368	3.95
9602	1.50

INTERSIL

ICL7107	12.95
ICL7660	2.95
ICL8038	3.95

DIP SWITCHES

4 position	.85
6 position	.90
7 position	.95
8 position	.95

TRANSISTORS

2N2222	.25	PN2907	.13
PN2222	.10	2N3055	.79
2N2905	.50	2N3904	.10
2N2907	.25	2N3906	.10

DISCRETE

1N751	5.1v zener	.25
1N759	12.0v zener	.25
1N4148	(1N914) switching	25/1.00
1N4004	400PIV rectifier	10/1.00
KBP02	200PIV 1.5a bridge	.45
4N33	OPTO-ISOLATOR	1.75

RIBBON CABLE

CONTACTS	SINGLE COLOR		COLOR CODED	
	1'	10'	1'	10'
25	.45	4.00	1.32	11.80
34	.61	5.40	1.65	14.50
50	.89	7.50	2.50	22.00

36 PIN CENTRONICS

CEN36 MALE SOLDER CUP	7.95
IDCEN36 MALE RIBBON CABLE	8.95
IDCEN36F FEMALE RIBBON CABLE	8.95

**VOLTAGE
REGULATORS**

7805T	.75	7915T	.85
78M05C	.35	7805K	1.39
7808T	.75	78H05K	9.95
7812T	.75	7812K	1.39
7815T	.75	7912K	1.49
7824T	.85	78L05	.69
7905T	.85	79L05	.79
7912T	.85	79L12	.79

C, T=TO-220, K=TO-3, L=TO-92

CMOS

4001	.25	4027	.45	4066	.39	4538	1.95
4002	.25	4028	.69	4069	.29	4543	1.19
4011	.25	4029	.79	4070	.35	4553	5.79
4012	.25	4040	.75	4071	.29	4584	.75
4013	.38	4042	.69	4081	.29	74C00	.35
4015	.39	4046	.85	4082	.29	74C04	.35
4016	.39	4047	.95	4093	.49	74C14	.59
4017	.69	4049	.35	4503	.65	74C74	.65
4018	.79	4050	.35	4511	.85	74C906	.95
4020	.75	4051	.79	4518	.89	74C922	4.49
4023	.29	4053	.79	4520	.79	74C923	4.95
4024	.65	4060	.89	4528	1.19	74C926	7.95



ORDER TOLL FREE
800-538-5000 **800-662-6279 (CA)**



Copyright 1985 JDR Microdevices

CIRCLE 113 ON FREE INFORMATION CARD

JULY 1985

SPARTAN Electronics Inc



CALL
(516) 499-9500
MAIL
6094 Jericho Tpke.
Commack, N.Y. 11725

CTC9R Philips Remote Cable Converter

• Micro computer technology • Quartz controlled 10's lock in picture & prevent drift • 60 channel selections • Programmable time on & off • 24 hour LED digital clock • Favorite channel memory & recall plus scan • Wireless hand held "infra-red" transmitter system • Automatic line tune • Adaptable to any brand television • One year warranty service.

\$129.95

Jerrold 58 Channel Wireless Remote Converter \$84.95

Replacement Transmitter Wireless/Hand-held w/on/off/Fine Tuning \$29.95

Zenith data systems \$2249.00

Go Beyond IBM Compatibility... Reach for Total Performance Zenith's Z-150PC!

Memory—320K RAM expandable to 640KB
Disks—Dual 5¼" Floppies (720KB total)
Video—RGB/Composite monochrome (80char x 25lines)
I/O—1-Series port/1-Parallel Printer Port
Keyboard—Detached/Shift lock & Numeric lock indicators

RS232 TRANSMISSION LINE TESTER

Features: *All 25 Signal lines accessible *Dual Color: Red/Green

Accessories: 1 Cable 10' male to Female Extension Jumper Set: 6 Straight 1 T-Jumper

Vinyl Case
Call for quantity prices. **\$169.95**

POCKET TECHNOLOGY INC.
10 MHz LogicScope 136

10 MHz Real Time Bandwidth
50-100 NS Glitch Catcher
True Dual Traces
Two 200 Element LED Displays
50-100 Bit Waveform Memories
3 Input Channels (A, B, T)
9 Volt Battery AC Operation
Light Weight, Hand Held
Audio Functions

SCALL IN STOCK

The Next Logical Step in Test Instrumentation

The LogicScope 136 combines the function of Logic Analyzer and Oscilloscope Technology and weighs only 1.25 pounds!

BEFORE YOU PAY \$\$ FOR A TELEPHONE SERVICE CALL, TEST IT YOURSELF

Telephone Line Analyze Model #1042 **BK PRECISION**

— Tests telephone line functions that affect telephone operation
— Verifies line and ring voltage levels
— Checks condition of telephone line from central office to user's telephone jack
— Verifies telephone line polarity that can affect polarity sensitive telephones

\$19.95

PROFESSIONAL TELEPHONE PRODUCT TESTER

Features: **MODEL 1045**

- Provides basic operation tests for corded and cordless telephones, answering machines, and automatic dialers
- Checks telephone line cords and handsets cords for continuity, shorts and intermittents
- Verifies number dialed and redialled for pulse or touch-tone telephones
- Provides low and normal level ring test sequence
- Verifies that voice and DTMF (Dual Tone Multiple Frequency) levels are above minimum required level

\$335.95

- Can be used by the consumer without the aid of a salesperson—an easy-to-follow instruction card is provided with the tester
- Can be used by the salesperson to demonstrate operation and features of telephone products and to screen returns before making an exchange

Dealers Welcome
Visa MC BAC Amex All above prices include 4% cash discount. G.O.D. money order, check Add for shipping

Volume Discounts

Min. Order \$25.00	Shipping	to 75.00	\$2.50
International shipping Add 1	76.00 to 250.00		\$4.50
Prices subject to change without notice	251.00 to 500.00		\$6.00
COD 2.00 Extra	501.00 to 750.00		\$8.50
Add 1 shipping for monitors	751.00 to 1000.00		\$12.00
	Over 1000.00		\$12.50

(516) 499-9500 Mon Th Tu W F Sa
TEL EX: 551-427 SPARTAN 9-8 9-6 9:30-5

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page		Page
260	A.I.S. Satellite	71	NRI
108	AMC Sales	73	NTS
76	AP Products	27	265 OK Industries
—	Active Electronics	84	118 Pacific One
—	Advance Electronics	7	90 Paia
106	Advanced Computer Products	99	256 Panavise
107	All Electronics	85	68,264 Philips ECG
72	Amazing Devices	98	69 Phoenix System
84	Appliance Service	70	101 Pomona Electronics
77	B&K Precision	36	125 Power Plus
98	Beckman Instruments	26	126 RAG Electronics
—	CIE	28-31	78 Radio Shack
—	Command Productions	73	70 Ramsey
79	Communications Electronics	2	— Research Service Lab
—	Consumer Cable Products	79	— RE Bookstore
95	Dick Smith Electronics	96, 97	253 Saratoga Electronics
263	Dalbani	42	270 Sone
127	Deco Industries	70, 71	75 Spartan Electronics
271	Deltax Dynamic	35	— Tektronix
267	Diehl Engineering	23	262 Unitech
82	Digi-Key	95	257 Wavetek
—	Digital Research Computers	90	103 Wm B Allen
57	Digitron	84	
110	Dokay	87	
60	Electronic Specialists	98	
—	ETT	CD11	
120	Elephant Electronics	70	
111	Etronix	75	
100	Firestik II	33	
259	Fluke Manufacturing	5	
—	Fordham Radio	13, 17, CV4	
264	Gemini Electronics	CD2	
62	Global Specialties	32	
—	Grantham College of Engineering	1	
—	Halix Instruments	73	
268, 269	HW Sams	16, 34	
86	Heath	22	
272	Huntron	71	
63	Instrument Mart	81	
114	Jameco	92, 93	
273, 113	JDR Microdevices	101, 102, 103	
115	Jensen	70	
65	J&W	98	
124	James Walter Satellite Rec.	71	
254, 255	Kikusui	33, 35	
266	Kepro Circuit Systems	33	
—	McGraw Hill Book Club	38-41	
87	MCM Audio	89	
105	MFJ	98	
67	McIntosh Labs	77	
261	Micro-Mart	90	
117	Mouser	79	

Gernsback Publications, Inc.
200 Park Ave. South
New York, NY 10003
(212) 777-6400
Chairman of the Board:
M. Harvey Gernsback
President: Larry Steckler

ADVERTISING SALES 212-777-6400

Larry Steckler
publisher
Arline Fishman
advertising coordinator
Shelli Weinman
advertising associate
Lisa Strassman
credit manager
Donna Sala
credit associate
Naomi Matten
advertising assistant

Sales Offices

EAST/SOUTHEAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
718-428-6037, 212-777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
Radio-Electronics
540 Frontage Road—Suite 325
Northfield, IL 60093
312-446-1444

PACIFIC COAST/ Mountain States

Marvin Green
Radio-Electronics
15335 Morrison St.—Suite 227
Sherman Oaks, CA 91403
818-986-2001

Matter of fact, our book will show you more banana plug and jack combinations and variations than you can shake a stick at. Regular or miniature, patch cord and cable assembly combinations; you name it and the chances are we'll have it.

And now that you have an idea of our depth and variety you should also be aware that the banana plugs and jacks we design and manufacture are considered by electronic design engineers to be right at the top. No question.

A superior product? You know you've got

that. And you should know, also, that we make sure you receive fast service and specified quantity through your favorite electronic parts distributor.

After all, we wrote the book.

And it's free. Our products are described and illustrated in our


1985 general catalog. Just call (714) 623-3463 or 623-6751. Or, write to us at ITT Pomona Electronics, a division of ITT Corporation, 1500 E. Ninth St., Pomona, Ca 91769.

ITT

Pomona Electronics

CIRCLE 101 ON FREE INFORMATION CARD

 Pomona wrote the book on banana plugs and jacks. Don't miss it.



PERFORMANCE

SCOPE HAND-HELD DIGITAL CAPACITANCE and MULTIMETERS

- 0.5% DC Accuracy
- Highest Quality
- Highest Performance
- Lowest Prices

THE ULTIMATE TEST



Model DCM-602
\$79⁹⁵

3 1/2 Digit Capacitance Meter
8 ranges with full scale values to 2000 uF
FEATURES • Broad test range - 1 pF to 2000 uF • LSI circuit provides high reliability and durability • Lower power consumption • Crystal time base
• Protected from charged capacitors
• Frequency range - 800 Hz to 8 Hz



Model DVM-634
\$48⁷⁵

7 functions, 32 ranges.
Transistor measurement included.

3 1/2 Digit Multimeters

FEATURES • DC Voltage 100 uV - 1000 V • AC Voltage 100 uV - 750 V • AC/DC Current 200 uA - 10 Amps • Resistance 20 Megohms • Capacitance (DVM 636/638) 1 pF - 20 uF • Overload Protection • Auto-decimal LCD readout • Polarity indication • 3000 hour battery life with 9V transistor battery • Low battery indication



Model DVM-638
\$79⁹⁵

11 functions, 38 ranges.
Includes logic level detector, audible visual continuity, capacitance and conductance measurement.



Model DVM-636
\$62⁷⁵

8 functions, 37 ranges.
Capacitance measurement included.

ASK FOR FREE CATALOG.

Money orders, checks accepted. C.O.D.'s require 25% deposit.



Fordham

260 Motor Parkway, Hauppauge, NY 11788

Toll Free
800-645-9518
In NY State 800-832-1446

Service and Shipping Charge Schedule

FOR ORDERS	ADD
\$25-250	\$4.50
\$251-500	\$6.50
\$501-750	\$8.50
\$751-1,000	\$12.50
\$1,001 and up	\$15.00