

# Radio — HOW TO SERVICE COMPACT-DISC PLAYERS

\$1.95 NOV. 1985  
IN CANADA \$2.50

# Electronics®

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE

## BUILD R-E's VIDEO TITLER

Now you can superimpose text and graphics directly on video images!

## ELECTROMAGNETIC INTERFERENCE

How EMI is caused and how you can fight it.

## ALL ABOUT AUDIO COMPANDERS


How you can use companders to improve your hi-fi.

## REMOTE CONTROL

Two IC's make it easy to build a full-function system.

## DIGITAL IC's

How to use counters in your designs.

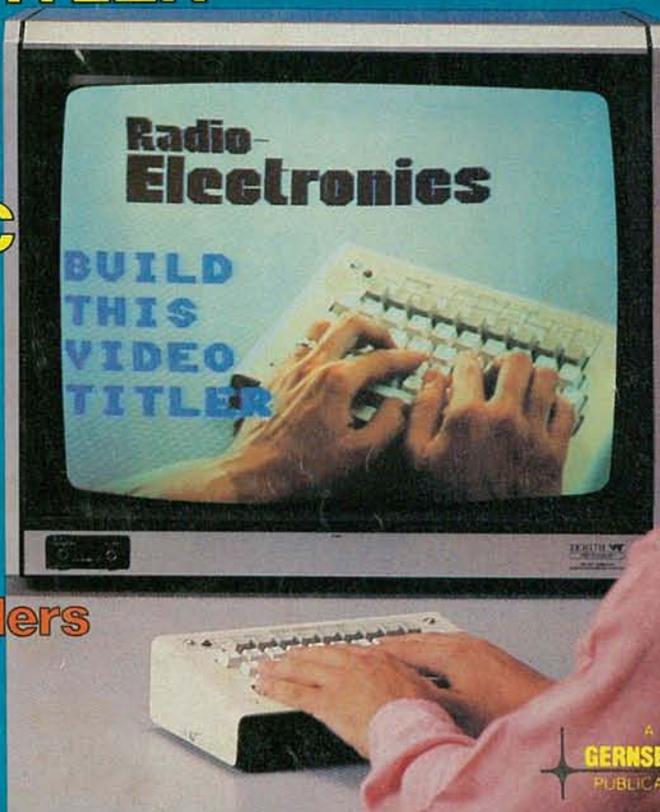

A  
**GERNSBACK**  
PUBLICATION


## BUILD THIS PULSE GENERATOR

It's a versatile and low-cost addition to your testbench.

### PLUS:

- ★ **COMPUTER DIGEST** ★ Equipment Reports
- ★ State-Of-Solid-State ★ Robotics
- ★ Designer's Notebook

# You can't judge a scope by its cover.

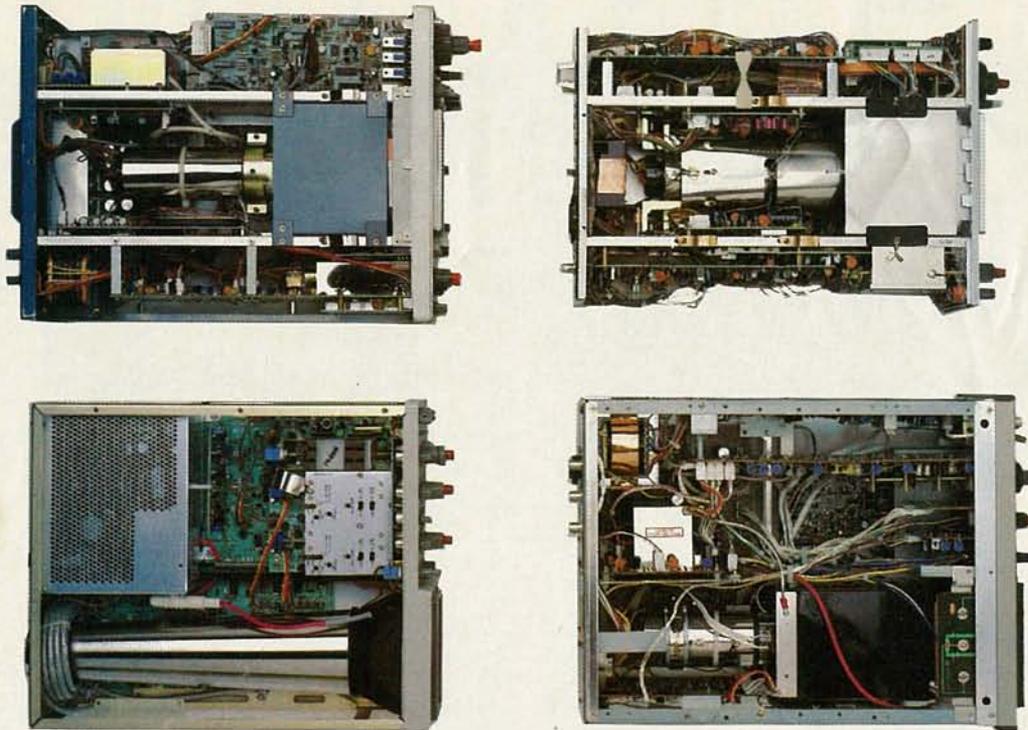

**When you look at our simplified, practical internal design, you see why the Tek 2200 Series delivers unparalleled high performance and reliability in the field.** You get quality that's unmistakably Tektronix in scopes so advanced, they cost you less to buy and own.

Through an innovative new concept in scope design we reduced the number of mechanical parts by 65%. Reduced cabling by 90%. Virtually eliminated board electrical connectors. And eliminated the need for a cooling fan.

**The result: a scope with designed-in simplicity that increases reliability as it cuts downtime and repair costs.** All of which means outstanding value in

a compact, lightweight package that your service technicians will appreciate.

Plus, you get a selection of performance to precisely match your needs. There are the 60 MHz single time base delay 2213A at \$1275\* and the 60 MHz dual time base 2215A at \$1525\*. And at 100 MHz, the dual time base 2235 at \$1750\* and the 2236 with an integrated counter/timer/multimeter at \$2650\*.

**The industry's first three-year warranty† is testimony to 2200 Series dependability.** Adding value to value are a variety of optional service plans that can economically extend this coverage to five years.

Consider what you're paying

now in downtime, in service, in back-up scopes. On the bottom line, a Tek 2200 Series scope will save you money, time and trouble now and in the years to come.

**Contact your Tek Sales Engineer for a demo today. Or call 1-800-426-2200, Ext. 201.**

In Oregon, call collect: (503) 627-9000, Ext. 201.



**Tektronix**<sup>®</sup>  
COMMITTED TO EXCELLENCE

\*Prices F.O.B. Beaverton, Oregon  
†3-year warranty includes CRT and applies to 2200 family oscilloscopes purchased after 1/1/83. Scopes are UL listed, CSA and VDE approved.

# NOVEMBER '85

**Radio-  
Electronics**  
Electronics publishers since 1908

Vol. 56 No. 11

- BUILD THIS**
- 45 **VIDEO TITLER**  
Now you can spice up your home video productions by superimposing characters and graphics onto video signals. **Jack Flack**
  - 57 **VERSATILE PULSE GENERATOR**  
You can build this full-featured pulse generator for your electronics workbench. **Joseph Gianelli**
  - 77 **PC SERVICE**  
Use the direct-etch foil patterns to make your own PC boards!

## RADIO

- 98 **COMMUNICATIONS CORNER**  
Communications in the computer age. **Herb Friedman**
- 102 **ANTIQUA RADIOS**  
Tubes aren't always easy to come by. **Richard D. Fitch**

## VIDEO

- 6 **VIDEO NEWS**  
A review of the fast-changing video scene. **David Lachenbruch**
- 106 **SERVICE CLINIC**  
Servicing with a function generator. **Jack Darr**
- 107 **SERVICE QUESTIONS**  
Answers to your service questions.

## COMPUTERS

- Following page 106
- COMPUTER DIGEST**  
RAM-disks, modems, and more!

## EQUIPMENT REPORTS

- 24 **Canon Typestar 6**
- 30 **Fluke 80TK Thermocouple Converter**

## DEPARTMENTS

- 138 **Advertising and Sales Offices**
- 138 **Advertising Index**
- 139 **Free Information Card**
- 15 **Letters**
- 114 **Market Center**
- 38 **New Products**
- 4 **What's News**

- TECHNOLOGY**
- 10 **SATELLITE TV**  
Trends in TVRO ownership. **Bob Cooper, Jr.**
  - 60 **REPAIRING COMPACT DISC PLAYERS**  
Compact-disc players have their own set of unique problems to be serviced. **John D. Lenk**
  - 71 **MEDICAL USES OF ELECTRIC SHOCK**  
Electric shock isn't always damaging; it can sometimes save your life! **Ray Fish, Ph.D., M.D.**
  - 80 **GLOSSARY OF COMMONLY USED SATELLITE-TV TERMS**  
A guide to TVRO jargon.
  - 89 **ROBOTICS**  
Ultrasonic eyes. **Mark J. Robillard**

## CIRCUITS AND COMPONENTS

- 8 **NEW IDEAS**  
Commodore cassette interface.
- 50 **ELECTROMAGNETIC INTERFERENCE**  
A look at some of the causes of EMI and at some ways to fight it. **Michael F. Violette**
- 64 **A VERSATILE REMOTE CONTROLLER**  
Part 2. Two IC's make it easy to build a 256-function remote control. **J. Daniel Gifford**
- 67 **ALL ABOUT AUDIO COMPANDING**  
How companders work, and how they can improve your hi-fi system. **Tom Pask**
- 75 **DESIGNING WITH DIGITAL IC's**  
Part 7. All about counters. **Joseph Carr**
- 84 **DESIGNER'S NOTEBOOK**  
A keyboard encoder promised months ago in the Drawing Board. **Robert Grossblatt**
- 92 **DRAWING BOARD**  
Hexadecimal display circuits. **Robert Grossblatt**
- 94 **STATE OF SOLID STATE**  
Surface-mount technology. **Robert F. Scott**

Radio-Electronics, (ISSN 0033-7862) Vol. 56 No. 11 issued Sept. 10, 1985. Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Second-Class Postage paid at New York, NY and additional mailing offices. Second-Class mail registration No. 9242 authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$15.97, Canada \$20.97, all other countries \$23.47. Subscription orders payable in US funds only, international postal money order or check drawn on a U.S.A. bank. Single copies \$1.95. © 1985 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

# COVER 1



The video titler shown on our cover is not just a standard video titler. This one lets you superimpose characters and graphics directly on a video image. Any other titler on the market will let you add characters—but at the expense of the video image. The screen shown on the Zenith CV-2562 25-inch monitor is an actual photograph. The letters and the R-E logo were superimposed onto the image from a Magnavox *Lolite* video camera.

If you want to add more than just titles to your videotapes, you can use your IBM PC, TRS-80 Color Computer, Apple II, or Commodore 64 to access the titler's video-image generator. That will allow you to superimpose complex graphics or even real-time animation over an external signal. For more on this exciting build-it-yourself project, turn to page 45.

# NEXT MONTH

THE DECEMBER ISSUE IS  
ON SALE NOVEMBER 5

## WHAT'S NEW IN IC TECHNOLOGY

Two special articles look at the year's advances in both analog and digital IC's.

## BUILD A VIDEO TITLER

We continue with details on the circuit and construction.

## BUILD A HOME SECURITY SYSTEM

It works like an expensive commercial system, but it's easy-to-build and it's inexpensive.

## HOW TO DESIGN WITH DIGITAL IC's

All about digital counters.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in RADIO-ELECTRONICS may relate to or be covered by U.S. patents, RADIO-ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

## Radio-Electronics

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback, editor-in-chief

Larry Steckler, EHF, CET, publisher

### EDITORIAL DEPARTMENT

Art Kleiman, editor

Brian C. Fenton,  
technical editor

Carl Laron, WB2SLR,  
associate editor

Jeffrey K. Holtzman,  
assistant technical editor

Robert A. Young, assistant editor

Julian S. Martin, editorial associate

Byron G. Wels, editorial associate

Jack Darr, CET, service editor

Robert F. Scott,  
semiconductor editor

Herb Friedman,  
communications editor

Bob Cooper, Jr. satellite-TV editor

Robert Grossblatt, circuits editor

David Lachenbruch,  
contributing editor

Richard D. Fitch,  
contributing editor

Mark J. Robillard, robotics editor

Bess Isaacson, editorial assistant

### PRODUCTION DEPARTMENT

Ruby M. Yee, production manager

Robert A. W. Lowndes,  
editorial production

Andre Duzant, technical illustrator

Karen Tucker, advertising production

Geoffrey S. Weil, production traffic

### CIRCULATION DEPARTMENT

Jacqueline P. Cheeseboro,  
circulation director

Rita Sabalis,  
assistant circulation director

Jacqueline Allen, circulation assistant

Radio-Electronics is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Microfilm & Microfiche editions are available. Contact circulation department for details.

Advertising Sales Offices listed  
on page 138.



# NEW!

# uniden®

# Bearcat®



## Scanners

Communications Electronics™, the world's largest distributor of radio scanners, introduces new scanners and scanner accessories from J.I.L., Regency and also Uniden/Bearcat. Chances are the police, fire and weather emergencies you'll read about in tomorrow's paper are coming through on a scanner today.

**NEW! Regency® MX7000-K**  
List price \$699.95/CE price \$429.00/SPECIAL  
**10-Band, 20 Channel • Crystalless • AC/DC**  
Frequency range: 25-550 MHz. continuous coverage and 800 MHz. to 1.2 GHz. continuous coverage  
In addition to normal scanner listening, the MX7000 offers CB, VHF, and UHF TV audio, FM Broadcast, all aircraft bands (civil and military), 800 MHz communications, cellular telephone, and when connected to a printer or CRT, satellite weather pictures.

**NEW! Regency® MX5000-K**  
List price \$599.95/CE price \$329.00/SPECIAL  
**Multi-Band, 20 Channel • No-crystal scanner**  
**Search • Lockout • Priority • AC/DC**  
**Selectable AM-FM modes • LCD display**  
**World's first continuous coverage scanner**  
Frequency range: 25-550 MHz. continuous coverage.  
Never before have so many features come in such a small package. The Regency MX5000 mobile or home scanner has continuous coverage from 25 to 550 MHz. That means you can hear CB, Television audio, FM broadcast stations, all aircraft bands including military and the normal scanner bands, all on your choice of 20 programmable channels.

**NEW! Regency® MX4000-K**  
List price \$629.95/CE price \$299.00/SPECIAL  
**Multi-Band, 20 Channel • No-crystal scanner**  
**Search • Lockout • Priority • AC/DC**  
**Selectable AM-FM modes • LCD display**  
Bands: 30-50, 118-136, 144-174, 440-512, 800-950 MHz.  
The Regency MX4000 is gives coverage in the standard VHF and UHF ranges with the important addition of the 800 MHz. and aircraft bands. It features keyboard entry, multifunction liquid crystal display and variable search increments.

**NEW! Regency® Z60-K**  
List price \$379.95/CE price \$216.00/SPECIAL  
**8-Band, 60 Channel • No-crystal scanner**  
Bands: 30-50, 88-108, 118-136, 144-174, 440-512 MHz.  
Cover your choice of over 15,000 frequencies on 60 channels at the touch of your finger.

## NEW! JIL SX-400-K

List price \$799.95/CE price \$469.00/SPECIAL  
**Multi-Band, 20 Channel • No-crystal Scanner**  
**Search • Lockout • Priority • AC/DC**  
Frequency range: 26-520 MHz. continuous coverage.  
With optionally equipped RF converters 150KHz-3.7 GHz.  
The JIL SX-400 synthesized scanner is designed for commercial and professional monitor users that demand features not found in ordinary scanners. The SX-400 will cover from 150 KHz to 3.7 GHz. with RF converters. Order the following RF converters for your SX-400 scanner. **RF-1030-K** at \$259.00 each for frequency range 150 KHz. - 30 MHz. USB, LSB, CW and AM. (CW filter required for CW signal reception); **RF-5080-K** at \$199.00 each for 500-800 MHz.; **RF-8014-K** at \$199.00 each for 800 MHz-1.4 GHz. Be sure to also order **ACB-300-K** at \$99.00 each which is an antenna control box for connection of the RF converters. The **RC-4000-K** data interface at \$259.00 each gives you control of the SX-400 scanner and RF converters through a computer. Add \$3.00 shipping for each RF converter, data interface or antenna control box. If you need further information on the JIL scanners, contact JIL directly at 213-926-6727 or write JIL at 17120 Edwards Road, Cerritos, California 90701 U.S.A.

## SPECIAL! JIL SX-200-K

List price \$499.95/CE special price \$159.00  
**Multi-Band - 16 Channel • No-Crystal Scanner**  
Frequency range 26-88, 108-180, 380-514 MHz.  
The JIL SX-200 scanner tunes military, F.B.I., Space Satellites, Police and Fire, Drug Enforcement Agencies, Defense Department, Aeronautical AM band, Aero Navigation Band, Fish & Game, Immigration, Paramedics, Amateur Radio, Justice Department, State Department, plus other thousands of radio frequencies most other scanners can't pick up. The SX-200 has selectable AM/FM receiver circuits, tri-squelch squelch settings - signal, audio and signal & audio, outboard AC power supply - DC at 12 volts built-in, quartz clock - bright vacuum fluorescent blue readouts and dimmer, dual level search speeds, tri-level scan delay switches, 16 memory channels in two channels banks, receive fine tune (RT) ± 2KHz., dual level RF gain settings - 20 db pad, AGC test points for optional signal strength meters.

## Regency® HX1000-K

List price \$329.95/CE price \$209.00  
**6-Band, 30 Channel • No Crystal scanner**  
**Search • Lockout • Priority • Scan delay**  
**Sidelit liquid crystal display • Digital Clock**  
Frequency range: 30-50, 144-174, 440-512 MHz.  
The new handheld Regency HX1000 scanner is fully keyboard-programmable for the ultimate in versatility. You can scan up to 30 channels at the same time. When you activate the priority control, you automatically override all other calls to listen to your favorite frequency. The LCD display is even sidelit for night use. Order **MA-256-K** rapid charge drop-in battery charger for \$79.00 plus \$3.00 shipping/handling. Includes wall charger, carrying case, belt clip, flexible antenna and nicad battery. Order now.

## NEW! Bearcat® 100XL-K

List price \$349.95/CE price \$229.00  
**9-Band, 16 Channel • Priority • Scan Delay**  
**Search • Limit • Hold • Lockout • AC/DC**  
Frequency range: 30-50, 118-174, 406-512 MHz.  
The world's first no-crystal handheld scanner now has a LCD channel display with backlight for low light use and aircraft band coverage at the same low price. Size is 1 3/4" x 7 1/2" x 2 1/4". The Bearcat 100XL has wide frequency coverage that includes all public service bands (Low, High, UHF and "T" bands), the AM aircraft band, the 2-meter and 70 cm. amateur bands, plus military and federal government frequencies. Wow...what a scanner!  
Included in our low CE price is a sturdy carrying case, earphone, battery charger/AC adapter, six AA ni-cad batteries and flexible antenna. Order your scanner now.

## NEW! Regency® HX2000-K

**The World's First 800 MHz. Handheld Scanner**  
List price \$569.95/CE price \$359.00  
**7-Band, 20 Channel • No-crystal scanner**  
**Priority control • Search/Scan • AC/DC**  
**Sidelit liquid crystal display • Memory backup**  
Bands: 118-136, 144-174, 440-512, 800-950 MHz.  
The HX2000 scanner operates on 120V AC or 6 VDC. Scans 15 channels per second. Size 3" x 7" x 1 1/2". Includes wall charger, carrying case, belt clip, flexible antenna and nicad batteries. Selectable AM/FM modes.

## NEW! Bearcat® 800XLT-K

List price \$499.95/CE price \$329.00  
**12-Band, 40 Channel • No-crystal scanner**  
**Priority control • Search/Scan • AC/DC**  
Bands: 29-54, 118-174, 406-512, 806-912 MHz.  
The Uniden 800XLT receives 40 channels in two banks. Scans 15 channels per second. Size 9 1/4" x 4 1/2" x 12 1/2".

### OTHER RADIOS AND ACCESSORIES

Panasonic RF-2600-K Shortwave receiver.....	\$179.00
Panasonic RF-B300-K Shortwave receiver.....	\$195.00
RD95-K Uniden Remote mount Radar Detector.....	\$139.00
RD55-K Uniden Visor mount Radar Detector.....	\$119.00
BC 20/20-K Bearcat 40 channel scanner.....	\$274.00
BC 210XW-K Bearcat 20 channel scanner.....	\$219.00
BC-WA-K Bearcat Weather Alert™.....	\$39.00
DX1000-K Bearcat shortwave receiver.....	\$459.00
PC22-K Uniden remote mount CB transceiver.....	\$99.00
PC55-K Uniden mobile mount CB transceiver.....	\$59.00
Z10-K Regency 10 channel scanner.....	\$139.00
Z30-K Regency 30 channel scanner.....	\$154.00
Z45-K Regency 45 channel scanner.....	\$179.00
R1060-K Regency 10 channel scanner.....	\$98.95
MX3000-K Regency 30 channel scanner.....	\$189.00
C403-K Regency 4 channel scanner.....	\$69.00
R106-K Regency 10 channel scanner.....	\$99.00
RH250B-K Regency 10 channel VHF transceiver.....	\$329.00
RU150B-K Regency 10 channel UHF transceiver.....	\$449.00
RPH410-K 10 ch. handheld no-crystal transceiver.....	\$399.00
BC10-K Battery charger for Regency RPH410.....	\$79.00
MA256-K Drop-in charger for HX1000 scanner.....	\$79.95
MA257-K Cigarette lighter cord for HX1000.....	\$19.95
MA917-K Ni-Cad battery pack for HX1000.....	\$24.95
EC10-K Programming tool for Regency RPH410.....	\$20.00
SMRH250-K Service man. for Regency RH250.....	\$20.00
SMRU150-K Service man. for Regency RU150.....	\$20.00
SMRPH410-K Service man. for Regency RPH410.....	\$20.00
SMMX7000-K Svc. man. for MX7000 & MX5000.....	\$20.00
SMMX3000-K Service man. for Regency MX3000.....	\$20.00
B-4-K 1.2 V AAA Ni-Cad batteries (set of four).....	\$9.00
A-135C-K Crystal certificate.....	\$3.00
FB-E-K Frequency Directory for Eastern U.S.A.....	\$12.00
FB-W-K Frequency Directory for Western U.S.A.....	\$12.00
TSG-K "Top Secret" Registry of U.S. Govt. Freq.....	\$15.00
TIC-K Techniques for Intercepting Comm.....	\$15.00
RRF-K Railroad frequency directory.....	\$10.00
CIE-K Covert Intelligence. Elect. Eavesdropping.....	\$15.00
AB0-K Magnet mount mobile scanner antenna.....	\$35.00
A70-K Base station scanner antenna.....	\$35.00
USAMM-K Mag mount VHF/UHF ant. w/ 12' cable.....	\$39.95
USAK-K 3/4" hole mount VHF/UHF ant. w/ 17' cable.....	\$35.95
USATLM-K Trunk lip mount VHF/UHF antenna.....	\$35.95

### BUY WITH CONFIDENCE


To get the fastest delivery from CE of any scanner, send or phone your order directly to our Scanner Distribution Center™. Michigan residents please add 4% sales tax or supply your tax I.D. number. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. All sales are subject to availability, acceptance and verification. All sales on accessories are final. Prices, terms and specifications are subject to change without notice. All prices are in U.S. dollars. Out of stock items will be placed on backorder automatically unless CE is instructed differently. A \$5.00 additional handling fee will be charged for all orders with a merchandise total under \$50.00. Shipments are F.O.B. Ann Arbor, Michigan. No COD's. Most products that we sell have a manufacturer's warranty. Free copies of warranties on these products are available prior to purchase by writing to CE. Non-certified checks require bank clearance.

**Mail orders to:** Communications Electronics™, Box 1045, Ann Arbor, Michigan 48106 U.S.A. Add \$7.00 per scanner for U.P.S. ground shipping and handling in the continental U.S.A. For Canada, Puerto Rico, Hawaii, Alaska, or APO/FPO delivery, shipping charges are a three times continental U.S. rates. If you have a Visa or Master Card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-USA-SCAN. In Canada, order toll-free by calling 800-221-3475. Telex CE anytime, dial 810-223-2422. If you are outside the U.S. or in Michigan dial 313-973-8888. Order today.

Scanner Distribution Center™ and CE logos are trademarks of Communications Electronics Inc.  
† Bearcat is a registered trademark of Uniden Corporation.  
‡ Regency is a federally registered trademark of Regency Electronics Inc. AD #090385-K

Copyright © 1985 Communications Electronics

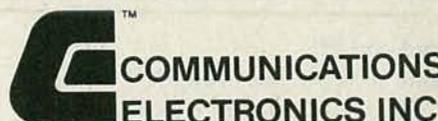For credit card orders call  
**1-800-USA-SCAN**




**Consumer Products Division**  
P.O. Box 1045 □ Ann Arbor, Michigan 48106-1045 U.S.A.  
Call 800-USA-SCAN or outside U.S.A. 313-973-8888



CIRCLE 79 ON FREE INFORMATION CARD

# WHAT'S NEWS
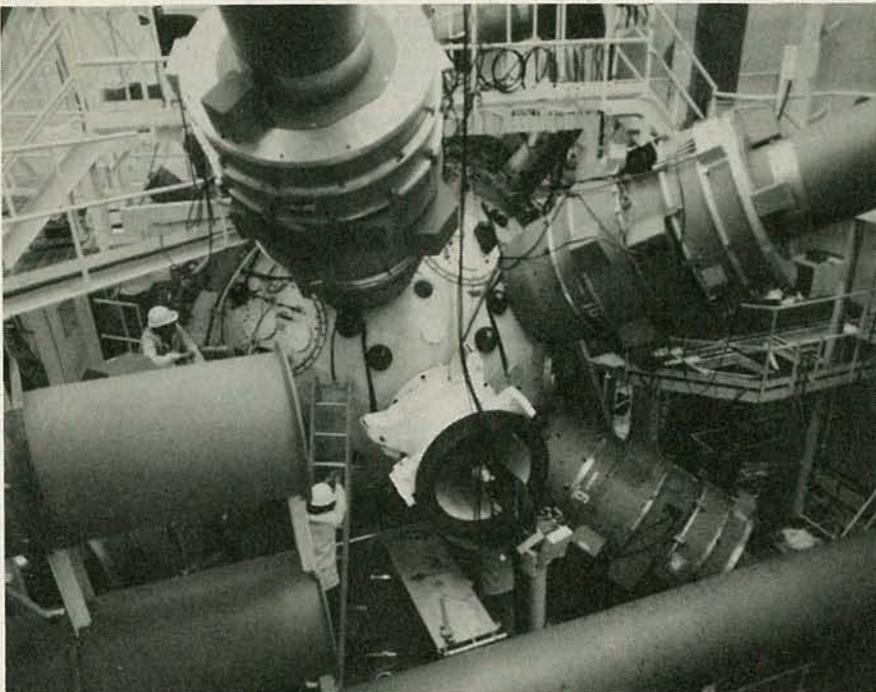
## World's biggest laser is six stories high



**TARGET CHAMBER OF NOVA, WORLD'S LARGEST LASER.** The 16-foot-diameter evacuated sphere is shown with some of the lens systems that focus laser beams on a small pellet at its center to produce fusion reactions. The size of the equipment may be judged from the two technicians working on it. The spaceframe holding it and its associated equipment is six stories high. The immediate use of Nova is as a laboratory tool for studying weapons physics. In the long term it is hoped that it will be a tool to help scientists to develop nuclear fusion as a safe, economical, and inexhaustible source of power.

Nova, the world's largest laser, was dedicated this past spring at the Lawrence Livermore Laboratory of the University of California. It will be used as a laboratory tool for studying nuclear physics, and for experiments intended to help scientists in their long-term quest for practical nuclear fusion.

Housed in a four-room building—one room is more than 200 feet long and another is six stories high—it is not only the world's biggest laser, but also the world's largest optical instrument, with more than 300 square meters of optical surfaces.

Nova uses a fantastically power-

ful capacitor bank to store 40 million joules of electrical energy at 20,000 volts to operate almost 6,000 xenon flashlamps. When the laser is fired, it produces a pulse of infrared light that is divided into ten pulses that are passed through 150 laser amplifiers toward the target. Those amplifiers—neodymium glass rods and discs—release their energy as the laser pulses pass through them.

Large mirrors steer the ten pulses toward the target vacuum chamber, a 16-foot diameter hollow aluminum sphere containing a fuel pellet. When the combined pulse is focused on it, for 30 to 50 trillionths of a second the pellet is subjected to a force 200 times greater than the power produced by the entire electrical generating capacity of the United States.

The high intensity laser pulses heat the fuel pellet, causing its outer shell to boil off and rocket outward. The reaction drives the remaining pellet wall inward, compressing the center of the pellet to a density and temperature comparable to that of the center of the sun.

Nova will thus be able to produce conditions under which atomic fusion can take place. That can provide more light on the theories of what is called inertial confinement fusion, and may be a step toward a practical technology for producing power from nuclear fusion.

## Ford and JBL unite to make auto sound

JBL Inc. and the Electrical and Electronics Division of Ford Motor Co. have launched a five-year program to develop high-perfor-

mance automotive sound systems for Ford's cars and light trucks. Details of the program have been agreed on and engineers are already at work on the first phases of the plan, said a Ford spokesman.

According to a recent survey by *Billboard Magazine*, JBL is the leading supplier of professional loudspeakers to North American recording studios and to international concert touring groups. **R-E**


# RAG

## ELECTRONICS, INC.

New and Used Electronic Test Equipment  
Sales • Service • Rental • Leasing


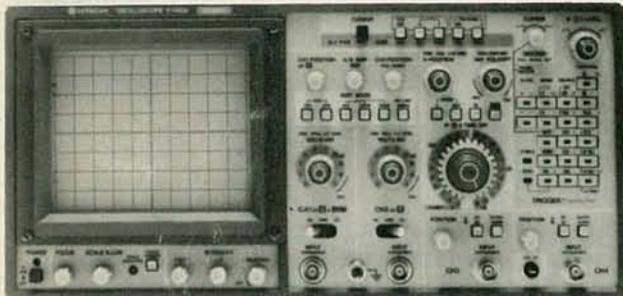
### V1100A DC to 100 MHz Portable Readout Oscilloscope




#### FEATURES

- Character display of set-up information on CRT (VOLTS/DIV, TIME/DIV, CAL or UNCAL, Delay Time, Trigger source, etc.)
- Cursor read-out function eliminates conventional calculation procedures (V,  $\Delta V$ ,  $\Delta V\%$ ,  $\Delta T$ ,  $1/\Delta T$ ,  $\Delta T\%$ , phase).
- Digital measuring function displays, DC voltage, AC voltage, and Frequency.
- Comment display function allows user's comments to be displayed on the CRT such as date and measurement data. Excellent for photo documentation.
- 4 channel, 8 trace, DC to 100 MHz, High sensitivity 1 mV/Div, Delayed sweep, Full TV triggering, Alternate triggering.

List Price \$2,490.00      **Sale Price \$2,250.00**


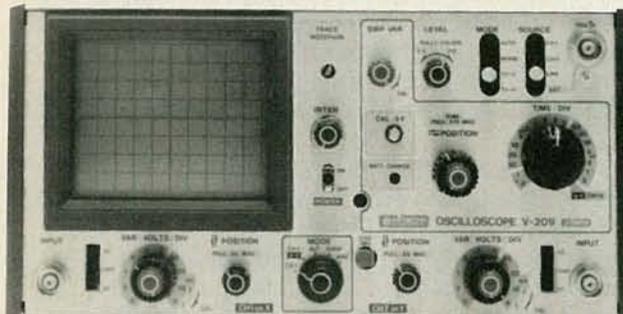
### V-209 DC to 20 MHz Mini-Portable Dual-Trace Oscilloscope



- A three-way power supply takes the V-209 anywhere, anytime for speedy field measurements.
- High sensitivity (1 mV/div at 10MHz) and fast sweep times (50ns/div) make the V-209 a valuable tool in R&D as well as servicing in a wide variety of applications including computers and video equipment.
- A Built-in TV sync separation circuit with easily selectable TV-V and TV-H modes ensures stable observation of both vertical and horizontal TV signal waveforms.
- An auto focus feature maintains constant trace without the necessity of troublesome manual focus adjustments.
- The V-209 is just what it claims to be—a powerful field service tool in a compact, lightweight package.

List Price \$945.00      **Sale Price \$708.00**



### Portable Oscilloscopes



Model V-422 shown

CIRCLE 126 ON FREE INFORMATION CARD

#### MODEL V-212

**\$461.00**

DC to 20 MHz, 1 mV/div, Dual Trace. Features 6" Rectangular CRT (w/two X10 probes).

#### MODEL V-422

**\$694.00**

DC to 40 MHz, 1 mV/div, Dual Trace, D.C. offset for DMM Output, Vertical Mode Trigger 6" CRT (w/two X10 probes).

#### MODEL V-1050F

**\$1,276.00**

DC to 100 MHz, .5 mV/div, Quad Trace, Delayed Sweep. Full TV Triggering, Alternate time base (w/two X10 probes).

Full 2 year parts and labor warranties on the above scopes.

HITACHI GSA CONTRACT NUMBER GS00S57322

CALL US TOLL FREE  
**1-800-732-3457**  
IN CALIFORNIA TOLL FREE  
**1-800-272-4225**

- Master Charge
- VISA ■ COD
- Money Order
- Check



ADD FOR SHIPPING AND INSURANCE	
\$0 to \$250.00	\$4.50
\$251.00 to \$600.00	\$6.50
\$501.00 to \$750.00	\$8.50
\$751.00 to \$1000.00	\$12.50
over \$1000.00	\$15.00

Prices subject to change without notice.

RAG ELECTRONICS, INC. / 21418 Parthenia Street / Canoga Park, CA 91304 / 1-818-998-6500

# VIDEO NEWS



**DAVID LACHENBRUCH**  
CONTRIBUTING EDITOR

● **RCA's Preview.** RCA gave the industry an advance peek at two of its "products of the future" recently at its laboratories in Princeton. The first product, to be introduced "as soon as possible," is a home satellite receiver component for the company's *Dimensia* audio-video system. The receiver can pick up both C- and Ku-band signals, and has a built-in descrambler designed for the M/A-Com encoding system adopted by HBO and Cinemax.

The other "product of the future" is a digital TV set, built around three basic IC's, containing its own frame memory. The receiver converts the incoming standard interlaced signal, with 60 262.5-line fields per second, to a progressive-scan non-interlaced one with 60 complete 525-line frames per second. The resulting picture showed no line structure or jitter. RCA said that a consumer-priced frame memory would need to be developed before the set could be marketed, but that one wouldn't be available until about 1990.

● **"High Quality" VHS.** The VHS group has decided not to follow Beta's lead in developing "super VCR's" with high-band color—at least not at this time—because of compatibility problems. Instead, VHS manufacturers are introducing an improvement called "High Quality," which uses signal processing to enhance the picture without sacrificing compatibility. Among the picture enhancements are a system called "video-noise reduction," which uses recursive comb filtering, and an increase in white clip level, which results in sharper image edges. JVC, which is given credit for developing the improvements, probably will feature them first, but they're expected to be used eventually by all members of the VHS camp.

● **VCR's to be Made Here.** Matsushita, the world's largest manufacturer of VCR's, has become the first company to announce the establishment of a factory to manufacture videocassette recorders in the United States. Sanyo has since followed, saying that it would also set up a VCR plant here. Hitachi, Toshiba, Sharp, and Sony have also said that they are looking into setting up plants here. Matsushita's

announcement came as the Japanese sought to relieve the top-heavy imbalance of trade with the United States. VCR's now constitute Japan's biggest electronics export to the U.S.—worth more than \$3.3 billion last year. No consumer VCR's currently are made in this country; all are imported, largely from Japan, with Korea recently getting into the act. The new Japanese-owned VCR plants here are expected to be little more than assembly operations at first; more complete manufacturing operations will come later as U.S.-made parts and components become available.

Meanwhile, Philips has announced that it is setting up a joint venture with a Korean firm to manufacture NTSC VCR's in Korea. They will be sold domestically in Korea and exported to countries that use the NTSC standard, including the U.S. Philips' U.S. affiliate, North American Philips, currently buys VCR's exclusively from Matsushita for its three brands—Magnavox, Sylvania, and Philco. The new Video Corporation of Korea, owned by Philips (70%) and Dongwon Electronics (30%) is scheduled to start up about a year from now and eventually supply VCR's for North American Philips' three U.S. brands.

● **Video Vignettes.** A portable projection TV system with built-in VHS recorder, audio cassette player, and PA system has been introduced by Display Sciences Inc., New York, at \$3,995.

Mitsubishi has now introduced the first model with a 35-inch direct-view picture tube (**Radio-Electronics**, March 1985) and priced it at a suggested list of \$3,200.

Videocassette players—that is, playback-only devices—seem like a good idea in view of the success of prerecorded software, and they're already being offered by such companies as Emerson, GE, Daewoo, Gold Star, Lloyd's, Magnavox, Quasar, and Panasonic. But few of those companies expect them to be very popular, except for the rental market. The reason: There's very little saving in eliminating the record function, thus the VCP's cost about the same as low-priced VCR's by the time they reach the marketplace.

**R-E**

# More quality accessories for more DMMs than anyone else in the world.

Fluke has over thirty ways to expand the horizons of your DMM — even if your existing DMM is made by someone else.

Take our new, low-priced 80i-400 current clamp, for example. It's one of five different accessories offered by Fluke to let you take safer, more accurate current measurements in high energy circuits.

Or consider our universal temperature accessories. They convert your DMM into a thermometer for air, surface, and non-corrosive liquid temperature measurements.

Fluke also offers a variety of probes to measure high voltage and probes for high frequency ac measurements. Plus a complete selection of test leads, battery eliminators, carrying cases, and more.

It's the largest selection of DMM accessories available in the world.

So why spend a lot of money on new equipment, when all you may really need are new accessories.

To get the whole story, ask for a copy of our complete DMM accessories booklet. It's yours for free by contacting your local Fluke Distributor, or by calling toll-free **1-800-426-0361**.

FROM THE WORLD LEADER IN DIGITAL MULTIMETERS.



**FLUKE**®

IN THE U.S. AND NON-EUROPEAN COUNTRIES: John Fluke Mfg. Co., Inc. P.O. Box C9990, M/S 250C, Everett, WA 98206. Sales (206) 356-5400. Other (206) 347-6100  
EUROPEAN HEADQUARTERS: Fluke (Holland) B.V., P.O. Box 2269, 5600 CG Eindhoven, The Netherlands. (040) 458045. TLX: 51846  
© Copyright 1985 John Fluke Mfg. Co., Inc. All rights reserved. Ad No. 4703-8020

CIRCLE 254 ON FREE INFORMATION CARD

# NEW IDEAS

## Commodore-64/VIC-20 cassette interface

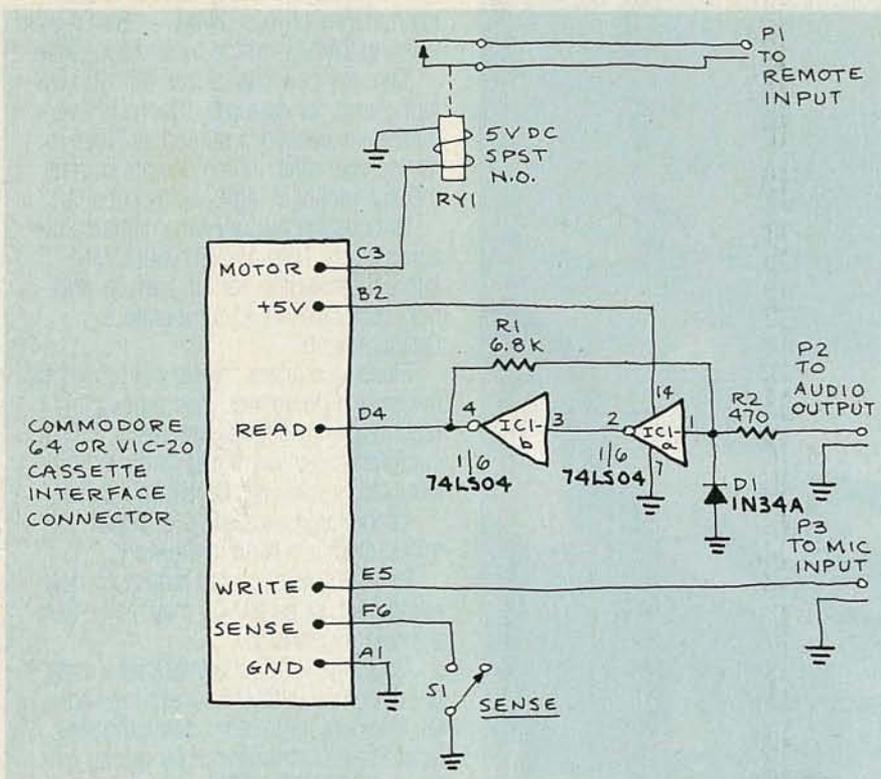


FIG. 1

THE CASSETTE RECORDERS THAT Commodore sells for use with the Commodore-64 and VIC-20 personal computers are expensive, even though they're not much different from standard audio recorders. Why are the Commodore *Datasette* recorders special? The Commodore CASSETTE WRITE output is a squarewave whose duty cycle is varied to transmit data.

Unfortunately, when you try to record that squarewave on audio tape, what you end up with looks more like a sinewave than a squarewave. When you play the tape back and try to load programs or data, the computer doesn't recognize the signals. However, the circuit presented here will turn the recorded signal back into one that the Commodore computers can

use. With it, you'll be able to use almost any recorder for data storage.

### Circuit operation

As shown in Fig. 1, audio output from a cassette recorder is fed through the limiting network composed of resistor R2 and diode D1. The resistor limits the peak voltage fed to IC1-a, and the diode ensures that voltages less than zero are not fed to the IC. Inverters IC1-a and IC1-b, together with resistor R1, form what is called a Schmitt trigger, which "squares up" the analog signals from the recorder so that they're acceptable to the computer.

As shown, a 74LS04 was used for the inverters, but you could easily

*continued on page 111*

### NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

All published entries, upon publication, will earn \$25. In addition, for U.S. residents only, Panavise will donate their model 333—The Rapid Assembly Circuit Board Holder, having a retail price of \$39.95. It features an eight-position rotating adjustment, indexing at 45-degree increments, and six positive lock positions in the vertical plane, giving you a full ten-inch height adjustment for comfortable working.



I agree to the above terms, and grant **Radio-Electronics** Magazine the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material has not been previously published.

Title of Idea \_\_\_\_\_

Signature \_\_\_\_\_

Print Name \_\_\_\_\_

Date \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Mail your idea along with this coupon to: **New Ideas Radio-Electronics,**  
200 Park Ave. South,  
New York, NY 10003

# PERFORMANCE

THAT IS OUT OF THIS WORLD...



**\$389<sup>00</sup>**

**MODEL 2000 20MHz  
DUAL TRACE**

**\$549<sup>00</sup>**

**MODEL 3500 35MHz  
DUAL TRACE DELAYED SWEEP**

## ...AT A DOWN TO EARTH PRICE

At last! Truly affordable test equipment with no compromise in design, and features you would expect to find only on oscilloscopes costing hundreds of dollars more! JDR Instruments presents two, new, high-performance models backed by a two year warranty and technical support which is only a phone call away. Perfect for the technician or advanced hobbyist, both models feature Dual Trace capability and a variety of operating and triggering modes, including CH-B Subtract and X-Y operation.

MODEL 2000 has a 20 MHz bandwidth and 20 calibrated sweeps ranging from .2s to .2 $\mu$ s. A convenient built-in component tester provides additional diagnostic power.



INCLUDES TWO HIGH QUALITY  
1x, 10x TEST PROBES

MODEL 3500 features a 35 MHz bandwidth and exceptional 1mV/DIV sensitivity. Delayed sweep and variable holdoff allow stable viewing of complex waveforms.

CIRCLE 113 ON FREE INFORMATION CARD

**ORDER TOLL FREE**  
**800-538-5000**  
**800-662-6279 (CA)**



**JDR INSTRUMENTS**  
1224 South Bascom Avenue  
San Jose, California 95128 (408) 995-5430

# SATELLITE TV



**BOB COOPER, JR.\***  
SATELLITE TV EDITOR

## TVRO ownership—present and future.

TWO THOUSAND TVRO OWNERS HAVE provided the home-satellite industry with its first in-depth profile of TVRO users. Many beliefs and assumptions fell by the wayside when the 150-page, *1985 TVRO Market Profile* was completed. Here are some of the findings.

The majority of TVRO owners (72%) do not live in cities, but 26.5% do have access to cable service. Of those who can subscribe to cable, 23% do, but 49% have discontinued their cable service.

For the last six months animosity between TVRO and cable has been increasing. Several cable firms have begun large-scale advertising in which they advise potential purchasers not to buy a TVRO because of the possibility that, when satellite signals scramble, TVRO owners will be left with nothing to view.

Ownership of TVRO systems has been growing tremendously for the past few years: 30% of TVRO owners purchased their systems in 1983, and 59% purchased their systems in 1984. Approximately one third of all TVRO buyers made their purchase after seeing a TVRO in operation at a friend's or neighbor's home; 25% bought after seeing a TVRO demonstrated by a dealer; and 22% bought because they wanted a greater choice of programming and felt that cable was too expensive, or simply unavailable.

When asked to give their reasons for buying a TVRO, 61% said their primary reason was to have access to a wider variety of programming. Significantly, 59% of those buying had access to a

\*publisher of CSD magazine

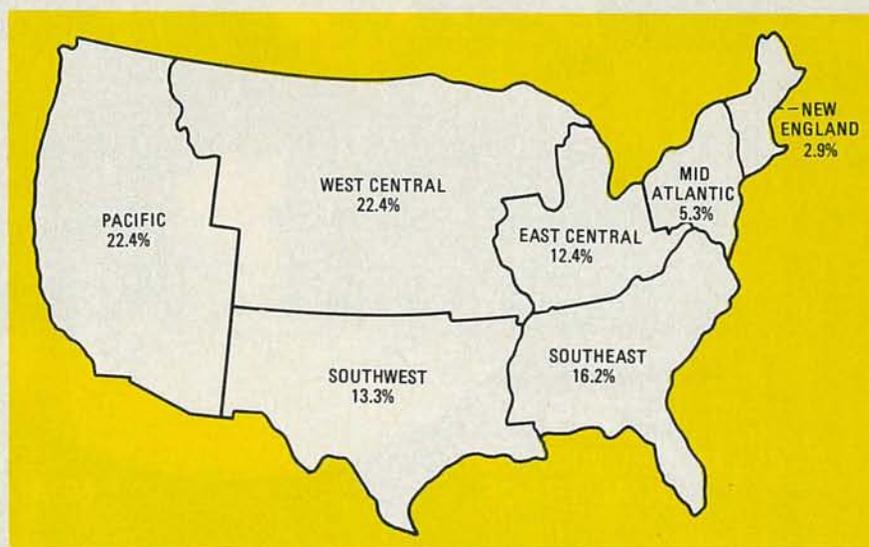


FIG. 1

many as 4 off-air (terrestrial) television channels, indicating that they live in areas where regular TV programming is not high quality.

Eighty percent of TVRO owners also own more than one TV set, 39% own a VCR, and 21% own a personal computer. VCR ownership and personal-computer ownership is markedly higher than the national average, which indicates the "upscale demographics" of TVRO ownership. Eighty-eight percent have a high school education or better, and 52% earn at least \$30,000 per year.

Although the largest market segment (39%) is between 35 and 49 years of age and still has children at home, a large percentage (21%) are over 60 years of age, and are either retired or semi-retired.

### Geographic distribution

As shown in Fig. 1, the study found that 47% of all system owners live in either the Pacific or

the West-Central regions of the United States. New England has the lowest percentage of TVRO owners (3%), while the mid-Atlantic region claims little over 5%. Those numbers would seem to support the thesis that TVRO is largely a rural—or at least western—phenomenon. But other evidence indicates that where buyers live, as well as who they are, is changing rapidly.

TVRO owners tend to spend many hours watching TV. The national average is in the vicinity of 37 hours per week, but the study found that 54% of TVRO users watched their satellite systems more than 40 hours per week, and that 18.4% use their systems more than 59 hours per week—almost 8.5 hours per day!

It is interesting to note that there is a high degree of user satisfaction with TVRO: 62.6% said they were "very satisfied" with their system, and only 1.6% reported they were



# PRINTER BARGAIN

*We guarantee that you'll never find a bargain as sensational as the letter-quality daisy wheel printer you see in this advertisement.*

*We covered up the name of the printer so as not to embarrass the manufacturer.*

**I realize that what you are about to read may seem incredible. I can understand. But occasionally there are indeed bargains and opportunities that only come once in a lifetime. I'm convinced that this is one of them.**

*By Joseph Sugarman, President*

The letter-quality printer you see above has a suggested retail price of \$1795. It prints bidirectionally at 40 characters per second using a daisy wheel print element, comes with a parallel interface and prints a 13.6 inch line.

A similar printer might be found at some discount computer dealers for as low as \$1000. And at that price it is indeed a bargain.

## AUTOMATIC FEATURES

If we'd offer it to you at \$499—a unit that we could be selling for \$1795 and that would be a bargain at \$1000—you'd probably think that there was a catch. But guess again. As unusual a bargain as this may appear, and despite all its quality features, this printer can be yours for the incredible low price of only \$499—below wholesale, below dealer cost and without question, the lowest priced high-speed letter-quality printer sold today.

JS&A bought out an entire warehouse full of these printers, promised that we would not display the name on the unit, in our photo, mention the name in our ad nor reveal the name over the phone to avoid embarrassing the manufacturer or his dealers.

I'm so convinced that this is one of the greatest values I've ever offered, I am making a bet and a commitment. First, the commitment. I'm giving you 30 days to test it out. If it's not the best printer value in the country, return it for a full refund including your \$25 postage.

Finally, I'll bet that you'll immediately recognize the name of the billion dollar company whose name is on the product or you don't deserve to own a computer. The company is a successful computer company whose products you may even now own. They'll back the product with service through its 90-day limited warranty and for years to come with hundreds of national factory service centers throughout the United States.

## EXCEPTIONAL VALUE

The printer is not an outdated model with old technology but a brand new unit with the latest electronics and the most advanced technology. For example, there's an automatic print pressure control which automatically varies the printing pressure according to the shape of the

character. This single feature produces an incredibly clean impression while prolonging the life of the daisy wheel. But there's more.

An aluminum diecast integral-constructed frame gives the printer a solid home for its advanced electronics. And with a weight of 30 pounds, you know there's built-in commercial-quality construction. The controls include: 'line feed' which advances the carriage by one line, 'page advance' which advances the document to the next page when using continuous form paper and a 'set page' button that tells the printer where the start of the form is located. A lighted condition panel tells you the printer status with red and green LEDs. You can use single sheets or continuous form fan-fold paper and with the 'paper out sensor' the printer detects the last sheet of the fan fold paper and automatically stops. And the printer has a 2K buffer memory.

There are also features that give you enormous printing flexibility. You can underscore words, double print each character which creates a bold look or you can use shadow print which moves the print head 1/120th of an inch between strikes. With the proper daisy wheel you can also set the printer for proportional printing which gives your documents a professional—almost printed look.

## SELF-TEST MODE

There's a self-test mode which lets you print out all the characters on your daisy wheel continually until you stop. And the system uses standard Diablo daisy wheels and ribbons which you can get from JS&A or any computer store.

With the Pica pitch, you can print up to 136 columns and with the Elite pitch, up to 163. The 15.5" carriage will take a print area of 13.6 inches. It measures 6 x 16 x 24", comes with a 10-pitch daisy wheel, one ribbon and complete instructions. The unit has provisions for a tractor feed and a sheet feeder which can be purchased locally or at a discount from JS&A.

You can select either 10, 12 or 15 for the print pitch or even use the 10-pitch daisy wheel supplied with the unit at the 12-pitch setting for large and tight letter spacing. There are dip switches which let you customize each printer to any computer with a parallel printer interface. Setting recommendations are supplied for IBM, Apple and other popular computers.

What happened? How can JS&A obtain and then sell these printers—products that are brand new with the latest state-of-the-art technology and from a major manufacturer at a price that at first is hard to believe? Quite frankly, it wasn't easy.

With our low overhead we can efficiently sell

these units in tremendous quantities without the high markups that many stores must have to make a profit. And we can do this on a mass-market national scale. Since many manufacturers know this and know that we could quickly move tremendous amounts of merchandise without upsetting many of the retailers (because we keep the name of the manufacturer confidential) they are willing to let us buy their product direct, often at foreign, export prices.

We'll be happy to supply companies with several printers for their computer departments to upgrade their printing speed and quality. There is no limit to the number you can order although we only have a few thousand available so we reserve the right to return your order should we run out.

## ACT QUICKLY

There are bargains available that are indeed too good to be true and often end up to be much less than you expected. But here's an example that is not only too good to be true but that we guarantee you'll find better than you expected. Order one at no obligation, today.

Simply send your check or money order using the order numbers shown in parentheses (IL residents add 7% sales tax) plus \$25 for postage and handling for each printer ordered. Credit card buyers call toll-free number below. Send your order to: JS&A Special Printer Bargain Offer at the address below.

Printer (6087) . . . . .	<b>\$499</b>
Tractor Feed (6084) . . . . .	<b>189</b>
Sheet Feeder (6088) . . . . .	<b>239</b>
3-Pack Ribbons (6089) . . . . .	<b>15</b>
Daisy Wheels: (List supplied with unit)	
<b>Cables/Interfaces (includes everything you need to connect to your computer:</b>	
IBM & Compatibles (25 pin) (6076) . . . . .	<b>39</b>
Apple II +/e (6099) . . . . .	<b>69</b>
Apple IIc (7011) . . . . .	<b>69</b>
Commodore VIC-20 C-64 & C-128 (7002) . . . . .	<b>69</b>
Atari 400/600/600XL/800/800XL (7003) . . . . .	<b>69</b>
Visual 1050 (7004) . . . . .	<b>39</b>
All Other Computers with Standard Parallel Printer Port (36 Pin) (7009) . . . . .	<b>39</b>

**JS&A PRODUCTS**  
THAT THINK®

One JS&A Plaza, Dept RE  
Northbrook, IL 60062 (312) 564-7000  
**ORDERS ONLY: 800 228-5000**  
**QUESTIONS ONLY: (316) 264-1109**  
IL residents add 7% sales tax. ©JS&A Group, Inc., 1985

"very satisfied" with their system, and only 1.6% reported they were "very dissatisfied" with it. A different attitude emerged from TVRO owners (26.5%) with access to cable TV service; 69.7% of them said they were "not pleased" with the quality of the local cable service.

The popularity of satellite reception was not surprising. Motorized dish movers are more often part of a system than not, these days, so most users buying systems now

have the ability to scan the Clarke orbit belt and lock in on virtually any U.S. or Canadian satellite in operation. That gives TVRO owners a lot to choose from. More than 88% of our sample reported that they tune in the Hughes Galaxy satellite, 83.8% tune in RCA's F3R, and 54.9% tune in RCA's F4, all at a rate of at least three times per week.

Network service, available on satellite in the form of intra-network feeds intended to be re-

#### TVRO dealer "Starter Kit" available

Bob Cooper's *CSD Magazine* has arranged with a number of TVRO equipment suppliers to provide a single-package of material that will help introduce you to the world of TVRO dealership. A short booklet written by Bob Cooper describes the start-up pitfalls to be avoided by any would-be TVRO dealer, in addition, product data and pricing sheets from prominent suppliers in the field are included. That package of material is free of charge and is supplied to firms or individuals in the electronics service business as an introduction to the 1984/85 world of selling TVRO systems retail.

You may obtain your *TVRO Dealer Starter Kit* free of charge by writing on company letterhead, or by enclosing a business card with your request. Address your inquiries to: *TVRO STARTER KIT*, P.O. Box 100858, Fort Lauderdale, FL 33310. That kit *not* available to individuals not involved in some form of electronics sales and service.

## SATELLITE TV/

### The First Five Years!



**THE MOST COMPLETE** report on the mushrooming home 'TVRO' industry ever compiled, written as only the 'father of TVRO' could have prepared. More than **1000 pages** (!) tracing the complete story of home TVRO, lavishly illustrated with equipment photos, schematic diagrams, equipment analysis reports. **Bob Cooper**, the first private individual to own and operate a TVRO (1976) has collected and polished hundreds of individual reports into a unique 'collector's edition' which clearly explains the TVRO phenomenon in North America. From Coop's first 20 foot 'monster' dish to the present day 5 foot 'C-band' TVROs, the fascinating growth of TVRO equipment and its legal status unfolds for you.

**THIS TWO VOLUME SET** totaling more than 1,000 pages is available for the first time to readers of **Radio-Electronics** at special discount pricing. **Originally sold** at \$100 per two-volume set, a limited supply is now available **ONLY** through this advertisement. **PLUS**, you will also receive a special extraordinary bonus; the 200 page (+) **October 1984** edition of **CSD/Coop's Satellite Digest**. This very special edition of CSD is a best-seller in the TVRO industry, with the most comprehensive collection of TVRO facts and figures ever compiled. Combined with the 1,000 page 'CSD ANTHOLOGY' report, you have instant reference to **everything** you will ever need to know about the state of the home TVRO industry. It is **MUST** reading for every person in, or thinking about 'getting into,' **any** segment of the home TVRO world.

broadcast by local stations, drew viewing percentages of about 30-35%, CBS satellite feeds being the most popular. Significantly, of the non-premium (non-pay) satellite services available, Ted Turner's WTBS outranked all others, and actually surpassed the popularity of satellite feeds from ABC and NBC.

#### What's being watched

Movies are clearly the most popular type of programming (66.2%), although people who have owned TVRO system for three years or more are less enchanted with movies than new owners are (dropping to 57% most popular).

Movies, of course, make up the overwhelming majority of the programming on such premium services as HBO and Showtime. In view of that, and in view of the above mentioned popularity of movies, care should be taken in drawing conclusions from the figures that follow.

HBO had been viewed during the 24 hours preceding our survey by 54.4% of all those responding to it, Cinemax by 49.2%, and Showtime by 46.3%.

Sports programming was the second most popular type of programming: all-sports ESPN pulled 28.9% of all viewers. However, sports programming is widely *continued on page 111*



— SEND CSD ANTHOLOGY/2 Vols. + CSD Bonus.  
— SEND CSD October '84 Special Issue **ONLY**.

NAME \_\_\_\_\_ COMPANY \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Payment: \$60 US funds (Anthology + Bonus), \$15 US funds CSD Oct. **ONLY**; payable "CSD ANTHOLOGY."  
Shipping charges prepaid. Enter order to: **CSD Anthology**, Radio-Electronics Magazine, 200 Park Av. S., New York, NY 10003; or call 305-771-0505 for credit card orders **ONLY**.

# You may not be able to solve the world's problems. But at least you can listen.



## The Panasonic Command Series™. With double superheterodyne tuning, you'll hear the world loud and clear.

Now it's easy to listen in on the world's hot spots. With the Panasonic RF-B600 Command Series FM/LW/MW/SW receiver.

Its advanced microcomputer-controlled tuner lets you preset up to nine different frequencies. And reach them at the touch of a button. Or, press the appropriate buttons and tune in any desired frequency with direct-access digital tuning. It'll lock right in to every signal with a PLL quartz-synthesized tuner. Once tuned in, the Panasonic double superheterodyne system helps deliver a clean, consistent signal.

There's even built-in auto-tuning to let you scan the shortwave band automatically, as well as manually. All this means you can tune in Berlin, pick up Paris, or locate London in an instant. Without dialing all over the band.

Both the RF-B600 and the RF-B300 are packed with features and built to go anywhere.

The Panasonic Command Series offers something for everyone. With equipment sophisticated enough to impress the most avid enthusiast, and automatic features that get you where you want to be. Fast.

There's a whole world out there that's waiting to be heard. Tune in to it with the Panasonic Command Series.



Batteries not included.

CIRCLE 280 ON FREE INFORMATION CARD


**Panasonic**<sup>®</sup>  
just slightly ahead of our time.™

**MEASURE FOR MEASURE  
THE BEST.**

Beckman Industrial 60MHz and 100MHz oscilloscopes are advanced designed for greater performance and ease of use. They offer more control, more versatility and more features than other models. And they are backed by a nationwide network of factory authorized service centers. Compare and you'll agree. Nothing measures up to Beckman Industrial oscilloscopes.

- 1mV/DIV Sensitivity
- 3 Channel, 8 Trace
- Dual Time Base
- Delayed Sweep

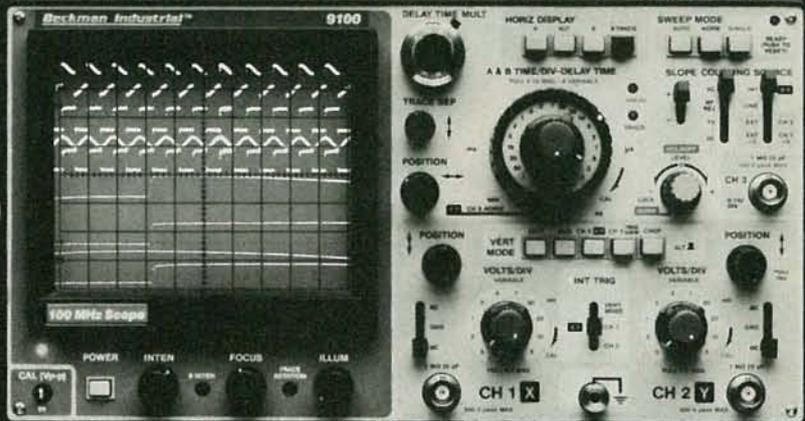Check out Beckman Industrial Models 9060 and 9100 oscilloscopes. At your local Beckman Industrial distributor.



Our UC10 Universal Counter gives you more of each. It measures frequency up to 100MHz...and gives you a variety of capabilities including frequency ratio, period, time interval and unit counting.

- Beeper/LED Function Indicators
- 20mV Input Sensitivity
- High/Low Ranges

**UC10 Universal Counter . . . . . \$319.95\***

You get the same advantages with our FG2 2MHz Function Generator.

- Sine, Square, Triangle and TTL Outputs
- Unique 5:1 Duty Cycle Control
- Wide 1000:1 VCF Sweep Range
- 50 OHM Output Impedance

**FG2 Function Generator . . . . . \$199.95\***

Great features, performance and value are always as close as your local Beckman Industrial distributor.

**FEATURES. PERFORMANCE. VALUE.**



Beckman Industrial Corporation, Instrumentation Products Division, A Subsidiary of Emerson Electric Co., 630 Puente St., Brea, CA 92621, (714) 671-4800.

\*Suggested list price.

CIRCLE 98 ON FREE INFORMATION CARD

# LETTERS

## WRITE TO:

LETTERS  
Radio-Electronics  
200 Park Ave South  
New York, NY 10003

### PC SERVICE

Your July 1985 article, "PC Service", was very interesting, especially since we make one of those kits you refer to: the ER-4 Photo Etch set. It's one that works. Its principle is patented. It's been sold to engineers and experimenters, and accepted in industry, for years.

But I'm writing for another reason. In your article, you recommend using the printed page as a poor man's film positive. That may work with some positive resists, but there are a few ways in which you can improve results.

1. You should publish the mirror image of the pattern that is to be reproduced. The pattern can then be placed directly against the sensitized board and exposed. If you continue to print a "right-reading" image, the blank paper side *must* be placed against the sensitized PC board. The printed image is separated from the foil board by the paper thickness, and your paper substrate will cause considerable light diffusion around and under the "black" areas. That causes thin circuit traces to break up or completely wash away.

2. You use a clay-coated paper in **Radio-Electronics**. Frequently, UV brighteners are added to the clay to make the paper look whiter. They absorb UV and retransmit the energy at longer wavelengths. What you now have seems to be OK. If you ever change paper, you'd better check things out again!

3. You should warn your readers that the system will work *only* with positive etch resist boards. It may seem obvious, but plenty of people will try it with negative resist—and waste a board.

4. Your comment about mineral

oil is well-taken; yet, it's essential to transparentize the paper to minimize diffusion and to shorten exposure times. A good approach is to use a clear gloss acrylic spray. Here, it's best that the coating resins be *all* acrylic. Alkyds and nitrocellulose are often used as modifiers and they absorb some UV. I experimented with DATAKOAT gloss No. 04177 as a transparentizer and the results follow.

I coated both sides of page 67 from your July 1985 issue with two very wet coats of DATAKOAT. That was to ensure complete penetration of the paper by the clear acrylic resin. The page was hung on clothespins to dry.

I then taped the coated paper and an uncoated page with blank-paper areas to a north-facing window. I used a Gossen Pilot exposure meter held against the unprinted area of each sheet of paper to measure the comparative light transmission. With the ASA index set at 100, my results were:

uncoated 1/250sec @ f/3.8;

coated 1/250sec @ f/2.8.

Those values can be reduced to relative light-transmission ratios as follows:

The ratio of light intensity to corresponding to *f*/stop value varies as the inverse square of the *f* value, or

$E = k/f^2$  where *k* is a constant; so

$E_1 = k/(3.8)^2$  or  $k = E_1(3.8)^2$  (1)

and

$E_2 = k/(2.8)^2$  or  $k = E_2(2.8)^2$  (2).


Combining (1) and (2) and rearranging gives:

$E_2/E_1 = (3.8/2.8)^2$

$E_2/E_1 = 1.84$  or an **84% improvement** in light transmission. DATAKOAT Gloss No. 04177 is available from many electronics parts distributors. Other 100% acrylic

(Continued on page 20)
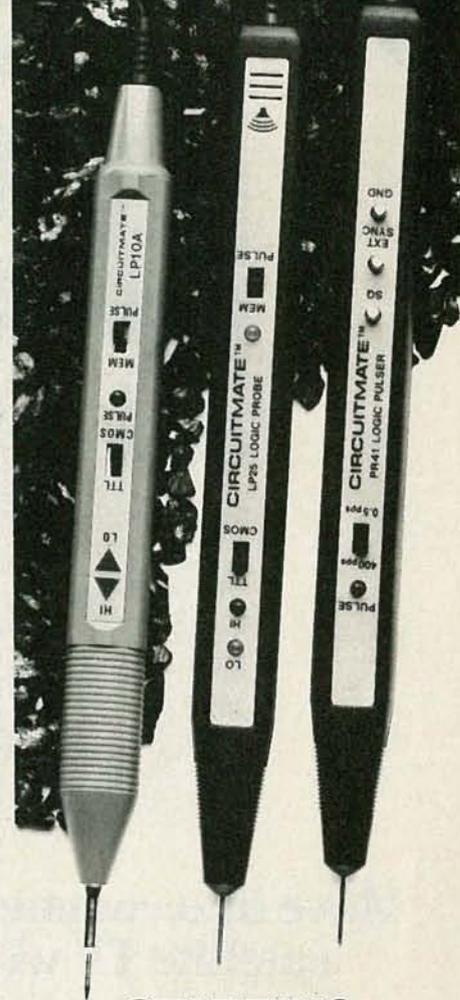
## WE'VE GOT THE LOWEST PRICED PROBES ON THE CIRCUIT.



## STARTING AT \$16.95\*

Compare these features.

**LP10A Logic Probe:**

- 30nS pulses to 17MHz
- Pen-like design

**LP25 Logic Probe:**

- 30nS pulses to 25MHz
- Beeper/LED logic indicators

**PR41 Logic Pulser:**

- 0.5/400Hz pulse rate
- 100mA, 10 $\mu$ S pulses

Beckman Industrial Corporation, Instrumentation Products Division, A Subsidiary of Emerson Electric Co., 630 Puente St., Brea, CA 92621, (714) 671-4800  
\*Suggested list price.

**Beckman Industrial™**

© 1985 Beckman Industrial Corporation

CIRCLE 251 ON FREE INFORMATION CARD

NOVEMBER 1985

15

**NEW!**

# Satellite Communications Training from NRI!



**Move into commercial satellite communications and home satellite TV with NRI's latest training breakthrough!**

---

**Explore Every Aspect of Satellite Transmission and Reception As You Assemble, Install, and Train With the Complete TVRO System Included in Your Course**

---

Back in 1964, great excitement surrounded the launching of Syncom 2, the true forerunner of today's satellites. But not even the most hopeful of scientists believed that in less than 25 years, communications satellites would have such a tremendous impact on the professional and personal lives of millions of people around the globe.

Today, thanks to the rapid development of satellite technology, a call to Paris is as clear and as easy to make as a call to your next door neighbor . . . executives from multi-national corporations and even small businesses use video conferencing to "meet" without leaving their offices . . . simultaneously a billion people witness a single event (a soccer game, an inauguration, a benefit rock concert) . . . global weather maps transmitted from satellites allow meteorologists to forecast weather trends weeks

in advance . . . and scientists now explore and investigate the mysteries of outer space without leaving their labs.

And, not surprisingly, these amazing applications of satellite technology have opened up exciting new opportunities for the technician trained to install, maintain, troubleshoot and repair satellite communications equipment.

---

**Home Satellite TV Is Just at the Start of Its Explosive Future**

---


You've seen them in suburban backyards and alongside country farmhouses. Home satellite TV systems are springing up all across the country.

Already there are over a million TVRO (Television Receive-Only) systems in place in the U.S. alone, and experts predict that by 1990, a remarkable 60% of U.S. homes will have a satellite dish. Contributing to the field's phenomenal growth are the support of the FCC and Congress, steady improvement in product quality, the development of smaller dishes, and a growing consumer enthusiasm for satellite TV.

---

## New Jobs, New Careers for the Trained Technician

---

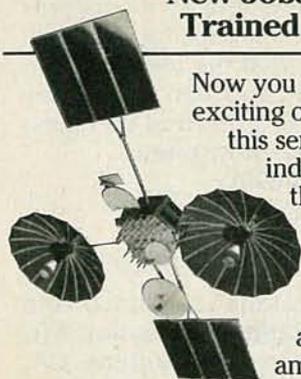

Now you can take advantage of the exciting opportunities opening up in this service- and support-intensive industry. NRI's new breakthrough training prepares you to fill the increasing need for technicians to install, adjust, and repair earth station equipment, such as dishes, antennas, receivers, and amplifiers.

As an NRI-trained technician, you can concentrate your efforts on consumer-oriented TVRO equipment. Or you can use your NRI training to build a career servicing larger commercial or military equipment used both to transmit and receive voice, data, and video signals. You'll also find opportunities in sales and system consulting, a role some expect to increase tenfold within the next five years on both the corporate and consumer levels.

---

## NRI Brings Satellite Technology Down to Earth

---

Only NRI has the resources and the skills necessary to transform today's most sophisticated technology into understandable, step-by-step training.

NRI's new course in Satellite Communications gets you in on the ground floor of this booming technology. You are thoroughly trained in the necessary basic electronics, fundamental communications principles, and television transmission and operation.

Using the remarkable NRI Discovery Lab<sup>®</sup>, you demonstrate first-hand many important points covered in your lessons. You perform critical tests and measurements with your digital multimeter. And, using your NRI Antenna Applications and Design Lab, you assemble and test various types of antennas and matching sections.

Then you concentrate on both commercial and consumer satellite earth station equipment, putting theory to practice as you assemble and install the 5' parabolic dish antenna system included in your course.

---

## Your Home Satellite TV System Brings Theory to Life!

---

The Wilson TVRO system included in your course comes complete with 5' parabolic dish antenna system, low-noise amplifier (LNA), down converter, receiver, low-loss coaxial cable, and even a permanent polar mount.

By training with an actual TVRO system, you'll come to understand the function and operation of a satellite earth station—knowledge that you can apply to both consumer and commercial equipment. And once you have completed your TVRO system, you'll have access to the best television entertainment available—direct from the satellite to your home.



---

## At-Home Training the Uniquely Successful NRI Way

---

It's hands-on training, at home... designed around the latest state-of-the-art electronic equipment you work with as part of your training. You start from scratch and "discover by doing" all the way up to the level of a fully qualified professional. You conduct key experiments... perform vital tests... install your own system... and you do it at the pace that suits you best.

But, most important to your success, you don't do it alone. Built into your NRI training is the enormous experience of our development specialists and instructors, whose long-proven training skills and personal guidance come to you on a one-to-one basis. They are always available for consultation and help.



---

## Make Your Move Into the Future Today! Send for Your FREE NRI Catalog

---

Only NRI can train you at home for an exciting and rewarding career as a satellite communications technician. The knowledge and know-how you gain from your NRI training provide you with the soundest possible foundation for further growth with the industry. But now is the time to act. Return the post-paid card to us today. You will receive your 100-page catalog free. It's filled with all the details you'll want to know about our training methods and materials and our more than 70 years of successful

innovation in at-home, hands-on career training—the kind of experience that enables NRI to provide the most effective training possible to prepare you for today's, and tomorrow's, high-tech opportunities. (If the card is missing, write to us at the address below.)



**NRI** SCHOOL OF ELECTRONICS

McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue, NW  
Washington, DC 20016

We'll give you tomorrow.



## LETTERS

continued from page 15

gloss sprays should give comparable results, but additional coats may be required.

BARRY DAVID BROWN,  
President,  
The Datak Corporation,  
Sparks, NE.

Thanks for your informative letter. We should point out one thing, though: The PC-board image printed on the page is not a right-reading one. The dimensions read right, but the pattern is flopped to minimize diffusion. We hope to hear from others on their experiences as well.—Editor

### MANUAL NEEDED

I need a service manual for a Fisher, model 1434, 4-channel/stereo receiver. I am willing to pay a reasonable sum for a schematic and parts list. That material is not available from the Fisher Radio Corp., or from Sams Photofact. Thank you very much.  
CHARLES D. PRATER  
Edna, KY 41419

### ELECTRONIC TESTING OF AUTOS

I have been a reader of **Radio-Electronics** for the last eight years and have seen the radical changes that it has gone through. It is the last of a breed of consumer-experimenter-technical-amateur electronics magazines.

I would like to see some articles devoted to electronic testing of autos, such as special scopes for electronic-ignition type cars without points. I would also like to see some articles devoted to higher-band video recording, such as is coming out in Beta machines, as well as editing machines with flying erase heads.

Keep up the good work, and don't go the way of all the computer-based competition.

BERNARD H. WEISS  
Edison, NJ

We have good news for you! An article, "Automotive Electronic Troubleshooting," by Herbert Freidman, will appear in Issue Number 6 of our sister publica-

tion, **Hands-On Electronics**, which is due to go on sale October 15, 1985—Editor.

### ELECTRICAL SAFETY

I just finished reading Earl "Doc" Savage's "Hobby Corner," in the May 1985 **Radio-Electronics**—and after reading the section about the Headphone Adapter, I was horrified. Shame on you, "Doc!" I know you know better—but you forgot something.

The circuits you show are perfectly OK, but you left out the most important part: *electrical safety*. I'm sure you're aware that most new equipment—especially TV sets that have been built over the last three to four years—are *hot chassis*. Therefore, hooking any external wires or exposed equipment to anything in that set will create an extreme shock hazard, or even death under the right conditions.

Of course, the correct way to make those installations is first to wire a 1-to-1 isolation transformer between the set and the speaker. That will eliminate the shock hazard, as well as give some overload protection to the output circuits. Then the headphone jack can be hooked up in the manner that you show. Most manufacturers use that same system.

AL LAMER, CET  
Keizer, OR

### THE e-Z BOARD

I am delighted at the review of our product, the *e-Z board*, which appeared in the "Equipment Reports" section, July 1985 issue of **Radio-Electronics**.

A further item of possible interest to you is that we are using a mylar label with an excellent adhesive backing to identify the bus signals on the *e-Z Board*. For some reason, it probably appears that we have glued two strips of ordinary paper, as your review indicates. We realized that a cup of coffee is frequently at hand when someone is breadboarding, and we wanted the label to be stainproof, as it were. So, in designing the label, we asked the manufacturer to make sure that the identification is printed onto a

mylar backing, and an insulator is placed over the backing. That will also ensure that the identification is permanent and won't fade away in time, or as a result of being exposed to the atmosphere.

RAHIM SABADIA  
Yorba Linda, CA

### COMMODORE MONITOR

In the "Letters" section of the June 1985 **Radio-Electronics**, Mr. Charles Matlin, Bell Gardens, CA, says that he is looking for a schematic and a block diagram of the Commodore 1702 color monitor.

In reviewing my copy of *Sams Photofact Annual Index 1985* (Howard W. Sams & Co., Inc., PO Box 7092, Indianapolis, IN 46206), page 11, I find that there is available, as of January 1985, tentative computerfact schedule production of repair data for the Commodore 1701 monitor.

Sams may be able to provide that data Mr. Matlin needs for his Commodore 1702. He should write or call Sams (800-428 SAMS) for information.

DENNIS DERRY  
Niceville, FL

### AGREES WITH ROBERT GROSSBLATT


I am writing this letter to express agreement with comments made by Robert Grossblatt in his article, "Understanding Memory IC's" (**Radio-Electronics**, February 1985).

I have a 15-year-old son, Saul, who spends much of his free time glued to his TRS-80 computer. He listened to me as I began to read Mr. Grossblatt's article, aloud. The obvious point being made in the introductory paragraph was how brainwashed we are that we all need computers. I quote the article: "People are buying them like umbrellas in a rainstorm, whether they need them or not. In what has to be a classic case of consumer brainwashing, the public has been convinced that the list of life's basic necessities now includes a 64K memory. Well, it just ain't so!" At that point, my son asked: "Well, then, how much memory do we need?"

Consumer brainwashing? I must agree—how right you are!

BARRY KELNER,  
Manalapan, NJ

R-E

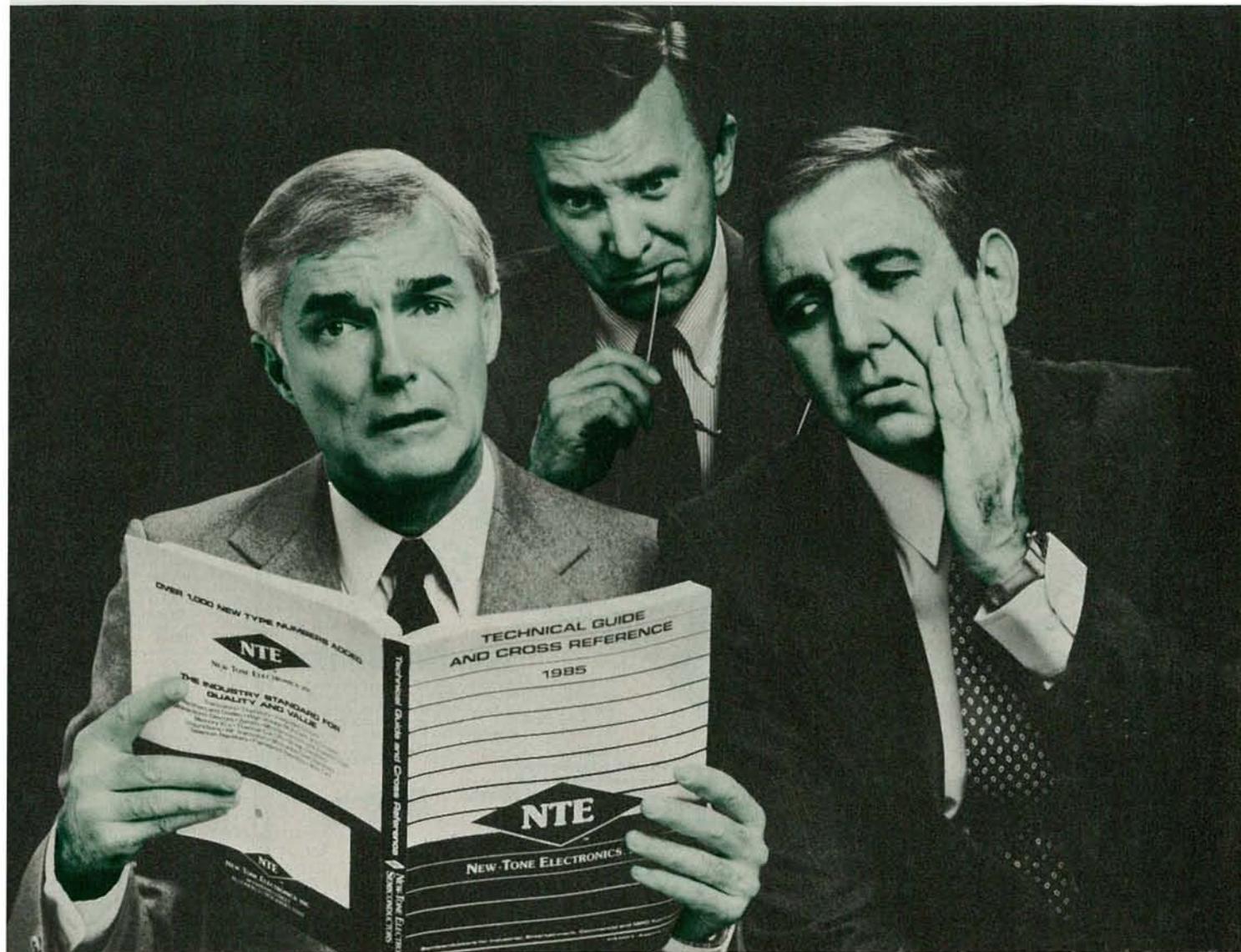

# WE'RE TURNING THE COMPETITION GREEN WITH ENVY.

NTE is the red hot success story of the electronics industry and the big boys are green with envy. They don't like the fact that we've built our reputation on giving you more of what you're looking for in a replacement part. More quality. More reliability. And, more parts to choose from. That's why more and more technicians across the country are picking the package with the green NTE diamond on the front.

NTE parts are extensively tested on state-of-the-art equipment during every phase of production to ensure top performance — performance that's backed by the industry's only two year warranty.

What's more, NTE uses a special computer controlled inventory system, so when you replace or design with NTE, you can be sure that the part you need is on your distributor's shelf. Our new 1985/86 Technical Guide and Cross-Reference manual, which has over 3,100 NTE types cross-referenced to over 220,000 industry part numbers, is now available.

Why settle for our competitor's parts when you get more quality and service with NTE? Look for NTE's replacement parts in the bright green polybags and cartons at your distributor today.

Don't forget to ask about our new Flameproof Resistors and Wire Ties, too!



**NTE ELECTRONICS, INC.**

44 FARRAND STREET, BLOOMFIELD, NEW JERSEY 07003

CIRCLE 289 ON FREE INFORMATION CARD

# ONE OFF OR VALUE PACK - YOU CHOOSE!

**DISK SMITH VALUE PACK**

**PREMIUM LED PACK**  
 top quality matched for brightness and color. Standard 0.2" size - at this price you can afford to use premium LED's on all your projects! You get: sixty red, twenty green, ten yellow and ten orange.  
 Cat Z-3015 **\$12.95**  
**WORTH OVER \$18!**

**DISK SMITH VALUE PACK**

**GREENCAP PACK**  
 Every green cap is as used in a number of circuits. 100 volt rating, too - and the values are selected from .001uF to 0.22uF (60 caps in all).  
 Cat R-7010 **\$6.95**  
**GREAT VALUE!**

**DISK SMITH VALUE PACK**

**ELECTROLYTIC PACK**  
 55 top quality single ended (pcb mounting) Range from 2.2uF to 470uF, voltages from 10 to 25.  
 Cat R-7030 **\$5.95**  
**WORTH OVER \$11!**

**DISK SMITH VALUE PACK**

**CERAMIC PACK**  
 Quality ceramic caps in a specially selected pack. Voltages from 50V - some as high as 500V.  
 Cat R-7050 **\$2.95**  
**WORTH OVER \$6!**

**INSTALL & SAVE!** YOUR OWN PRO QUALITY SECURITY SYSTEM BASED ON **The Dick Smith Security Center**

This is the type of alarm system the professional installers could charge you \$500 - \$1000 for...and more! Suitable for homes, offices...you name it! With six individual sectors all fully controllable for instant or delayed alarm, each able to isolate and each triggerable by a huge range of sensors.

- Features:**
- ★ Resistive loop sensing suits both n/o & n/c alarm sensors will trigger alarm.
  - ★ Any sector can be isolated while the rest of the alarm remains on.
  - ★ Six different sectors, all with LED indication to show sector status.
  - ★ Includes fire detector provision.

**GREAT VALUE** Cat L-5100 **\$149.00**

**Membrane Keyboard Kit** **NOW IN STOCK!**

New! New! We found these little beauties at a recent trade show and did a deal on the spot with the suppliers so we could squeeze them into the catalog. We thought you'd like them as they can be used for just about any application from design to finished project. Switching is normally open, momentary contact push button type. Easy to assemble.

**SPECIFICATIONS**

- ★ Circuit resistance: less than 150 ohms
- ★ Contact rating: DC 24V max 5mA max
- ★ Open Circuit Resistance: 100 MEG minimum
- ★ Contact material: carbon in sides
- Life time: tested to one 3 million operations at 24V DC 5mA

4 key Cat K-3605 **\$4.95**  
 12 key Cat K-3607 **\$6.95**  
 16 key Cat K-3609 **\$8.95**  
 80 key Cat K-3611 **VALUE**

**Metal Film Resistor Pack**

Our 1% metal film resistors are even better value when bought by the pack! Use metal films in all your projects - at this price!

Cat R-7015 **\$11.95**  
**WORTH \$24!**

**OUR TOP SELLER!**

**19" Rack Mounting Case**

Quality black instrument case fits standard 19" racks over all they're 16.75" x 9.8" x 5.5". Supplied flat assembly takes just a couple of minutes. Heavy gauge (0.12) front panel, top and bottom pre-punched for ventilation.

Cat Q-1440 **\$29.95**  
**GREAT VALUE**

**E-24 Metal Film 1% Resistor Pack**

Superb pack of low noise 1% metal films to our range: in the full E-24 series. Consists of 300 pieces covering 60 values between 11 ohms and 910 kohms.

Cat R-7020 **\$11.95**  
**WORTH \$24!**

**Resistor Pack**

60 values specially chosen by the computer. Quality 5% types - huge savings on normal prices.

Cat R-7010 **\$5.95**  
**WORTH \$15!**

**Power Diode Pack**

Over fifty of the most used power diodes and SCR's. You get: 10 each 1N4002, 1N4004, 1N4007 1A diodes, 10 each 1N5404 & 1N5408 3A diodes, two W04 1.5A 400V bridges, three C106Y1 and two C122E general purpose SCR's.

Cat Z-3010 **\$9.95**  
**WORTH OVER \$12!**

**Signal Diode Pack**

A selection of the types of diodes we all use for projects - Contains five OA90, fifteen OA91/DSOA91, five OA95, five OA47 germanium diodes, and a huge seventy 1N914 silicon diodes.

Cat Z-3000 **\$7.95**  
**WORTH OVER \$9!**

**17 YEARS MAIL ORDER EXPERIENCE**

**Wet Walkie?**

Anyone who owns a Walkie-type stereo knows the hassles: get them wet and they tend to stop. Solve the problem with this water resistant carry bag.

Cat A-4010 **ONLY \$6.95**

**AMAZING PRICE BREAKTHROUGH!**

For a quality **LCD MULTIMETER**

Beautifully made. We believe this multimeter must be the best value available in America.

**SPECIFICATIONS**

- DC Voltage - 1-2-200-100 volts.
- AC Voltage - 0-200-500- volts (RMS)
- DC Current - 0-2-20-200 mA
- Resistance - 0-2K-20K-200K2 MEG Ohms

200 hour battery life, Full overload protection and diode check function.

Cat Q-1440 **\$29.95**

**IS YOUR PHONE TAPPED?**

**Tap Trap**

Using the TAP TRAP, you can quickly and easily check your phone line for on-premises series and parallel bugs and wiretaps. You can also check your telephone for the most common types of hookswitch bypasses which can turn it into a room monitor.

**ONLY \$95.00**

Cat F-1007

**PRICE TECHNOLOGY BREAKTHROUGH**

**Pocket TV**

State of the art technology. Fits in the palm of your hand. The world's smallest black and white TV features 2" LCD screen and operates on 2" AA" batteries (included). Weighs only 7 oz. Auto tuning locks in each channel: receives UHF and VHF channels.

Cat Y-8525 **\$99.00**

**BOOKS**

**Fiberoptics**  
 Everthing the hobbyist needs to know about fiberoptics. Fundamentals, hardware, and applications, with practical projects to provide hands-on experience.  
 Cat B3800 **\$9.95**

**How To Build Your Own Self-Programming Robot**  
 Explains what a robot is and isn't, how robots work, how machine intelligence operates, how microprocessors are used, and everything else you need to know.  
 Cat B-1802 **\$9.95**

**222 Weekend Electronic Projects**  
 A treasury of more than 200 practical, proven electronics projects that can be built in only a few hours time from inexpensive, readily accessible components.  
 Cat B-3640 **\$14.95**

**The Radio Control Hobbyist's Handbook**  
 Jam-packed with information on radio-controlled airplanes, helicopters, model rocketry, and robotics. A must for any one who wants to tackle radio control modeling.  
 Cat B-3636 **\$18.95**

**ORDER TOLL FREE 1-800-332-5373**

Dear Enthusiast,

Have you ever wanted just ONE resistor but had to buy a pack of five? At Dick Smith Electronics we don't agree with that and we don't offer fancy over-packaged blister packs. We'll sell you one of any component and at our normal low prices (please compare!).

Want to buy in quantity? Our "no frills" value packs offer even further savings off our low one-off prices. Whatever you decide, our aim is to offer the products you want in what quantities you want and at prices you like. We're always ready to listen to you and if you have any comments about our prices or products we'd like to hear them. Thanks for your support.

Ike Bain


## YOU INSTALL & SAVE! Deluxe Car Alarm

These days your car needs protection from car thieves, not just kids out for a joyride. Door and ignition locks are simply not enough. You need an alarm that will warn of all conceivable methods of entry and have its own back-up in case of tampering.
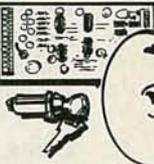
### FEATURES:

- ★ Two delayed and six instant alarm inputs
- ★ Delayed entry and exit times (10s each)
- ★ Provision for auxiliary battery
- ★ Siren output (in case vehicle horn is disabled)
- ★ Flashing dash lamp, internal key operated on/off etc.

Cheap insurance for your vehicle!  
Cat K-3252 ★ ★



ONLY \$59.95

GREAT VALUE

SEE OUR FUN WAY 2 KITS FEATURED IN OCT NOV ISSUE 'HANDS ON'

## TOP CHIPS - COMPARE OUR PRICES!

CAT NO.	DESCRIPTION	EA.
-6144	TL 555 CP CMOS Timer IC	69¢
-6145	DS 555/NE 555 Timer IC	34¢
-6382	LM 741 OP Amp 8 pm DIL	35¢

YOU REAP THE BENEFIT!

SATELLITE TV KIT LATEST NEWS: PROTOTYPE IN CALIFORNIA AND WORKING FANTASTICALLY AWAITING FIRST SHIPMENT.

## SEE YOUR MUSK.

The Dick Smith Musicolor Mk IV

What's better than a color organ and a chaser? The Musicolor MkIV - it combines both! Four chase patterns plus auto chase and reverse chase AND four channel color organ with built-in microphone (no connection to speakers necessary!) means you're ready to stage a light show!



ONLY \$99.95  
Cat K-3143 ★ ★ ★

## Power Supply

Full PCB and component kit for one K-3442 or two K-3440 modules. Supplied complete with speaker relay and Zener regulated plus 6 minus 15V pre-amp rails. Special assembly instructions supplied. Cat K-3438 ★

VALUE AT \$14.95  
GREAT VALUE

## 50 Watt Amp Module Kit

Same design simplicity as the 100 watt module but cheaper because of lower power. And there's added economy as two units can be run from the one K-3438 power supply. An economical solution for those who want to update their old system without a huge outlay of money. Cat K-3440

FOR ONLY \$14.95

## HIGH POWER!

## 100 Watt Amp Module Kit

100 watts RMS 100dB signal to noise ratio at 5kHz: The ultimate in simplicity: even the power transistors mount on the one PCB heatsink bracket is supplied, and the heavy duty fiberglass PCB has a silkscreened overlay to make the construction even easier! Has on-board fuse protection. Input sensitivity: 1V. Cat K-3442 ★ ★

FOR ONLY \$19.95

## NEW COAX-SEAL

- ★ Stays Flexible At Any Temperature
- ★ Insures Low SWR
- ★ Forms and Seals Over Odd Shaped and Difficult COAX Fittings
- ★ Fast-Easy Seal for All Antenna Connections
- ★ Non-Contaminating
- ★ Non-Conductive

\$2.49


DICK SMITH #1 FOR KITS

## TOP SELLING BREADBOARDS

No more birds nests. Now you can build up those incredible technology breakthroughs easily and simply with these breadboards. No soldering required - component leads simply push into holes (accepts most component lengths of tinned components can have short lengths of tinned copper wire soldered to them) Spacing of the holes is designed to accept standard DIP packages. And if one board isn't enough, add more... as many as you need, they stay together too.

Mini 3" x 2.4" Cat P-4614 \$4.95  
Midi 7" x 2.7" Cat P-4615 \$9.95  
Maxi 8" x 6" Cat P-4616 \$19.95

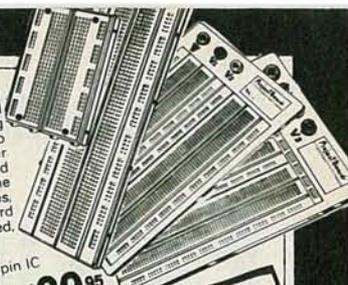Super 27 x 14 pin IC capacity Cat P-4617 \$29.95



## LEARN ABOUT IC'S DICK SMITH'S FUN WAY VOL 3 into Electronics



Another 100 pages of fun: that's Fun Way Volume 3. It's the logical progression for those who have worked through Fun Way Vol 1 and 2. It's for the more advanced hobbyist because Fun Way Volume 3 projects are all based on integrated circuits. There are ten projects in a number of forms - so there are virtually as many individual projects in Fun Way 3 as there are in the other two books. And because the Fun Way 3 projects are more complex, they are dealt with in more detail. More explanation, more construction details - so you learn much more with Fun Way 3. Cat B-2610 \$6.95

## AND BUILD THESE EXCITING PROJECTS!

### Cricket

Here's a ton of fun! Hide the cricket: when the lights go out it starts chirping. Turn the lights on or make a noise and it stops. Makes it so hard to find! It really is infuriating! Cat K-2663 \$9.95

### Minder

C'mon, Guvnor - leave the auto alone. That's the Fun line that it is looking after! It's actually doing much more - makes a great 'lights on' warning and 'door open' warning as well as a pseudo burglar alarm Cat K-2660 \$7.95

### Two-up

Australia's 'national game' has finally been converted to electronics. And you don't have to find any King George pennies! Simulates the throw, the spin and the final result. Come in spinner! Cat K-2661 \$9.95

### Lil' Pokey

You'll have a ball with this one - and you don't risk losing a single cent! A digital project which not only shows how the one armed bandit works - it teaches you how logic circuits work, too. Cat K-2662 \$19.95

### Mini Stereo Amp

Want an amplifier for your 'walkie' stereo or radio? Don't be tied to phones: use this project and listen in comfort! Or you can build this into a mini PA amplifier. Cat K-2667 \$14.95

### Mini Color Organ

Your very own disco colour organ - but ours is battery operated - so it's much safer than mains devices! Connect it to your radio, cassette or stereo for a real lightshow! Cat K-2664 \$12.95

### Binary Bingo



A great school project: it's a fun game - but even more it demonstrates binary numbers very well. And they're the basis of all computers! It seems pretty simple to play... but try it! Cat K-2668 \$19.95

### Mini Synth

It's a real beauty, this one: a real 'live' musical synthesiser - and it's live because it uses YOU as the note generator! You get an amazing range of control over the sound. Cat K-2669 \$19.95



### 1 Light and Sound

What versatility! It's really 6 projects in one: you just build the form you want - a LED flasher, a mini strobe flasher, police siren, motor boat sound effects, continuity tester and Morse Code practice oscillator. Cat K-2665 \$8.95

## EVERYTHING FOR THE ELECTRONICS ENTHUSIAST

# DICK SMITH ELECTRONICS

INCORPORATED IN THE STATE OF CALIFORNIA

STORES AT:  
BERKELEY: 2474 Shattuck Ave., Ph:(415) 486 0755  
REDWOOD CITY: 390 Convention Way, Ph:(415) 368 8844  
SAN JOSE: 4980 Stevens Creek Blvd, Ph:(408) 241 2266  
STORE HOURS: San Jose & Berkeley 10 AM - 6PM EVERYDAY  
Redwood City 10AM - 6PM Mon - Sat; 12-5PM Sunday  
MAIL ORDERS: PO Box 8021, Redwood City, CA 94063  
HEAD OFFICE: 390 Convention Way, Redwood City, CA 94063


HANDLING - ALL ORDERS \$1.00 PLUS SHIPPING  
INSIDE USA 5% OF ORDER TOTAL (MIN \$1.50)  
OUTSIDE USA 10% OF ORDER TOTAL (MIN \$3.00)

★ ★ ★ ★ ★ MAIL THIS COUPON TODAY WITH JUST \$1 FOR SHIPPING AND WE'LL SEND OUR FREE 132 PAGE COLOR CATALOG ★ ★ ★ ★ ★  
\$2 COUPON IN CATALOG MORE THAN REDEEMS YOUR COST WITH YOUR FIRST ORDER  
Name... Address... City... State... Zip...  
WHERE THE ELECTRONICS ENTHUSIAST IS #1

# EQUIPMENT REPORTS
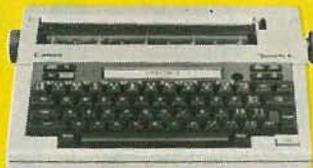
## Canon Tpestar 6

This typewriter includes some of the most powerful features of both typewriters and computers.



CIRCLE 5 ON FREE INFORMATION CARD

character LCD (Liquid Crystal Display), a full-travel keyboard, and has a set of operating commands that allow it to function like an expensive word-processor.

### Using the Tpestar 6

The Tpestar 6 has several modes of operation, selected by use of the MODE key. In the *character* mode, characters are printed one-by-one as they are entered at the keyboard. In the *line* mode, a whole line is entered before it is printed. That gives you a chance to correct mistakes before

THERE'S AN INTERESTING PHENOMENON going on in the portable typewriter market: the traditional portable typewriter is merging with today's portable computer,

and the combination frequently provides some of the best features of both. For example, the Canon Tpestar 6 features a high-density dot-matrix printhead, a 28-

FAST (over 11 mHz CIK) (Intel 8052 AH Basic - Based)

## UL BASIC CONTROLLER

WITH ON-BOARD EPROM/E<sup>2</sup>PROM PROGRAMMER

MLC-1 ONLY \$188<sup>87</sup>

Assembled & Tested. Store many programs on up to 32K on board EPROM.

### SINGLE BOARD FEATURES:

The board itself is a breakthrough in controller power, simplicity and price. The user can be writing and running programs in Basic, even storing them on EPROM/E<sup>2</sup>PROM's within minutes of initial hookup. Applications - Real time intelligent security systems, auto-test equipment, home and industrial environmental control, robotics, . . . . We think you'll really enjoy using our product.

### HARDWARE FEATURES: 8052 BASIC

RS232 Serial port with auto baudrate detection at virtually any baud rate; Serial printer port output available; 48 I/O lines (six-8 bit ports); PWM output; Real time Clock (5m Sec. resolution); Fast 11.0592 mHz clock rate; Up to 16Kx8 on board RAM

EPROM Programmer: Programs 2716, 2732, 2764, 27128, 27256; On board regulator for programming voltages (selectable). Comes with 8Kx8 of RAM and 8Kx8 of EPROM; Additional RAM and EPROM AVAILABLE (call for prices).


### SOFTWARE FEATURES: Fast Full Basic Interpreter (Not "Tiny Basic")

BCD floating pt. math; Hex to Decimal, Decimal to Hex conversion; Exponential number handling; ±.9999999E - 127 to ±1E+127; All Basic routines can be called by assembly language programs; Basic can call user assembly language subroutines; Basic or assembly handling of interrupts; Single command transfer of RAM program to EPROM/E<sup>2</sup>PROM any of which can be transferred back to RAM with a single command. Single step Basic Commands to control 6-8 bit I/O ports, as well as internal and external memory. Can execute EPROM program on power up if desired without use of a terminal.

Requirements: Dumb terminal (stand-alone after programming) + 5V @ 1A, ±12V @ .1A, +30V @ .1A
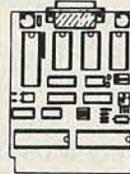
### TERMS:

Mastercharge and Visa accepted (add4%) C.O.D. orders add \*3%. Wisconsin residents add 5% sales tax. Personal checks must clear before shipping. S & H add \*4% per board. All orders refused or returned are subject to a 10% restocking fee. Prices and specifications subject to change without notice.



**NEW**

IN POWER & SIMPLICITY!

### ACCESSORY PERIPHERALS:

AD12-1	12 bit A/D with 8 channel input mux; with on board precision ref.	\$132 <sup>00</sup>
AD6-8	8 bit-8 channel A/D Board; AD 7581 Based; 86us conv. rate.	\$117 <sup>00</sup>
DA12-1	12 bit D/A Board 8 channel output mux; (500ns conv. before mux)	\$96 <sup>00</sup>
DA6-8	8 channel 8 bit D/A (8 independent channels); (dual AD7226's)	\$164 <sup>00</sup>
DA8-4	4 channel version	\$128 <sup>00</sup>
AC-8	Isolated 8 channel AC Solid State Relay Board	
	each channel 12A 600V with output transient protection and fused outputs.	\$179 <sup>00</sup>
DC-8	Isolated 8 channel DC Power Switching Board	
	each channel 8A 200V with protection diodes and fused outputs. (8 channel with common GND)	\$158 <sup>00</sup>
DC-8A	Same as above only with 8 channels 8 separate grounds.	\$209 <sup>00</sup>
ME-1	Memory Expansion Board Expands total memory to 64K RAM/ROM	
	AND 32K of EPROM Add \$9 <sup>00</sup> each for 8Kx8 ram (up to 6)	\$64 <sup>00</sup>
MB-1	Mother Board	
	Can chain up to eight MB-1's to control up to 255 peripherals. 100 pin edge card connectors add \$8 <sup>00</sup> each.	\$49 <sup>00</sup>

### HOBBY KITS:

HK-8052	8052AH-Basic chip, 11.0592 mHz crystal Intel Basic manual and application notes	\$74 <sup>00</sup>
HK-MLC-BD	MLC-1 P.C. Board, Micro Linear Kit Ass'y Manual and Micro Linear Application notes.	\$47 <sup>00</sup>

### MICRO LINEAR CONTROLS

4900 Memco Lane  
Racine, WI 53404 - 1099



Orders only call TOLL-FREE 1-800-222-2298  
for technical information call (414)-639-1105  
Call for OEM and Quantity Pricing.



FREE WATTS OUTSIDE WI  
**1-800-222-2298**

ACCEPTED  
ADD 4%

# VIDEO ACCESSORIES

■ Highest quality ■ Highest performance ■ Lowest prices

## bp VIDEO-CINE CONVERTER

The BP Video-Cine Converter is an optical device that allows the easy transfer of slides, 8mm or 16mm movie film to VCR tape. The Video-Cine Converter's precision optics put the image from your movie or slide projector on a high-contrast, rear projection screen. Your video camera shoots that image, can color-correct faded pictures, add narration to other sound. Can be used with any video camera or slide projector. If your video camera lacks close-up capability, you will need a macro lens attachment.



MODEL V-1701 **\$36<sup>95</sup>**

Macro Lens Attachment  
Model 0314 **\$14<sup>95</sup>**

# FOR ULTIMATE VIEWING

### TEKNIKA WIRELESS REMOTE CONTROL TV TUNER & CABLE CONVERTER WITH VOLUME CONTROL

Model 6510  
**\$169<sup>95</sup>**



Wireless remote control with volume for cable TV, VHF-UHF antenna systems upgrades any TV to 140 channel capability.

- Works with any TV set
- Quick, easy installation
- Off-air and cable compatible
- Quartz frequency synthesizer tuning
- Direct access/memory scan selector
- Ultra-compact, hand-held wireless remote control

### bp 61 CHANNEL WIRELESS REMOTE CONTROL

Model V7661 **\$79<sup>95</sup>**



Wireless remote control on/off, channel selection and fine tuning.

- Works with any TV
- 61 channel capability
- Microcomputer controlled PLL operation
- Converter panel controllable for channel up, down, on/off, fine tuning
- LED display
- Compatible with CATV systems.

### bp STABILIZER/IMAGE ENHANCER/RF CONVERTER/VIDEO FADER/2-WAY DISTRIBUTION AMPLIFIER

Model V1880 **\$99<sup>95</sup>**




Hook-up cable kit  
**\$11.75**

The most versatile, all-in-one video processor. Can be used as a video guard remover for video tapes, enhancer, video to RF converter, professional video fade in and out and a dual output distribution amplifier.

### bp VIDEO SWITCH

Model V4804 **\$49<sup>95</sup>**

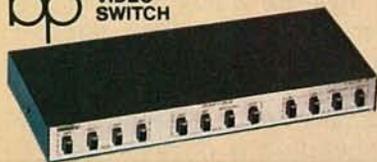

Record a pay channel while viewing a standard channel. You can also connect an antenna/cable, VCR, video disc player, home computer and video game.

### bp VIDEO TAPE REWINDER

Model V7777 VHS **\$49<sup>95</sup>**

Model V7778 BETA **\$49<sup>95</sup>**



Reduce wear and tear of your VCR heads with the AC powered circuit protected rewinders, LED power-on indicators.

Charge it with VISA/MASTERCARD. Phone orders accepted.

# Fordham

Toll Free

In NY State 800-832-1446

260 Motor Parkway, Hauppauge, NY 11788

#### Service and Shipping Charge Schedule

FOR ORDERS	ADD
\$25-250 .....	\$4.50
\$251-500 .....	\$6.50
\$501-750 .....	\$8.50
\$751-1,000 .....	\$12.50
\$1,001 and up .....	\$15.00

NOVEMBER 1985

# TOOL DISPOSAL NOTICE

Over 130  
High Quality  
Guaranteed  
Tools!!

## ATTACHE TOOL KITS

- Your choice of leatherette wood case or lightweight aluminum case (pictured)
- Plus a fantastic assortment of over 130 quality tools professionals need and use every day
- Features heavy duty removable tool boards, keyed dual locks & additional storage compartment
- Ideal for computer, copy machine, alarm & electronics technicians

AS LOW AS  
\$169<sup>00</sup> Tools and Case Included!!

FREE DELIVERY

Compare at \$350.00 to \$500.00 elsewhere.

### TOOL SET INCLUDES

- |                                     |                                     |
|-------------------------------------|-------------------------------------|
| (2) Alignment tools                 | Oiler                               |
| (3) Burnishers                      | Penlight                            |
| Decimal/metric conversion wheel     | 4-1/2" diagonal cutting plier       |
| 7 blade feeler gauge                | 5-1/4" diagonal cutting plier       |
| Ball pein hammer 4 oz.              | 10" groove joint plier              |
| Handle, Driver Blades (4-5/8") Red  | 5-1/4" long nose plier              |
| Handle, Driver Blades (4-5/8") Blue | 6-1/2" long nose plier & cutter     |
| (9) Hex driver blades               | External retaining ring pliers      |
| (8) Metric hex key wrenches         | Internal retaining ring pliers      |
| Icepick/scribe                      | 3/32" center punch                  |
| Case key                            | 1/16" pin punch                     |
| Key chain with 4-way screwdriver    | 6" stainless rule                   |
| Electricians knife                  | Scissors (sharp, sharp)             |
| Inspection mirror                   | Offset ratchet screwdriver          |
| Multi-tester with probes & fuse     | #0x2-1/2" phillips clip screwdriver |
| (9) Nut driver blades               | Hemostat                            |

### FREE MULTI-TESTER!!

- |                                   |                              |
|-----------------------------------|------------------------------|
| #1x3" phillips screwdriver        | Solder sucker                |
| #2 phillips screwdriver/stubby    | Solder iron holder           |
| #2x4" phillips screwdriver        | (110/120 V, 30/35W)          |
| 3/32"x2" slotted clip screwdriver | Spring tool, pull            |
| 1/8" x 4" slotted screwdriver     | Spring tools, push           |
| 1/8" x 8" slotted screwdriver     | 21 Pc. 1/4" drive socket set |
| 3/16" x 3" slotted screwdriver    | 1/4" drive fingertip ratchet |
| 1/4" slotted screwdriver-stubby   | (8) Retaining plier tips     |
| 1/4" x 4" slotted screwdriver     | Reverse action tweezers      |
| 5/16" x 6" slotted screwdriver    | Wire crimper/stripper        |
| (7) Jewelers screwdrivers         | Wire stripper/cutter         |
| Phillips & slotted screwdriver    | 6" adjustable wrench         |
| Solder Aid, Fork and hook         | 8" adjustable wrench         |
| Solder brush                      | (8) Ignition wrenches        |
| Solder removal braid              |                              |
| Solder in pull tube               |                              |

For orders of 5 or more sets call Toll Free ☎ 800-423-2567 for quantity discount prices!!

Qty.	Lot No.	Item	Unit Price	Amount
	64986	Leatherette Wood Case	\$50.00	
	62286	Aluminum Case	\$65.00	
	494-186	130 Pc. Tool Set	\$129.00	
	392-186	Wood Case & Tools	\$169.00	
	390-186	Aluminum Case & Tools	\$189.00	
Subtotal				
Sales Tax for CA & KY Residents				
Total				

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Phone ( ) \_\_\_\_\_ Zip \_\_\_\_\_

Signature \_\_\_\_\_

Check or money order enclosed

M/C  Visa Expiration date \_\_\_\_\_

Acct. No. \_\_\_\_\_

## HARBOR FREIGHT SALVAGE CO.

3491 Mission Oaks, Blvd., P.O. Box 6015  
Dept. T986, Camarillo, CA 93011-6015

PHONE TOLL FREE 800-423-2567

committing them to paper. Finally, the *memory* mode allows you to enter and edit data in the *Typestar 6's* 2000-character memory.

That memory may be divided into as many as 26 different buffers of arbitrary length, each of which may be edited and printed separately. To edit a buffer, you press the **TEXT** key, a letter from A to Z (representing the desired buffer), and the **CODE** key. At that point you may use the **DELETE** key, **LEFT** and **RIGHT** arrow keys, and the **RELOCATE** key to clean up your text. The **RELOCATE** key moves the cursor to the beginning or end of the current buffer on alternate key-strokes. The arrow keys move the cursor one character at a time in the appropriate direction, and the **DELETE** key deletes the character at the current cursor position.

A collection agency, for example, might make use of that memory to store a set of messages to be used in printing form letters. The contents of each message would vary depending on how long an account had been overdue. To print a letter, the typist would manually type the name and address block, then choose the appropriate buffer, as done for editing, and then press the **TEXT PRINT** key. Finally, a signature line would be typed in manually.

One nice thing about the keyboard is that the **SHIFT LOCK** key has a small red indicator that lights up when that key has been depressed. There are separate keys for setting left and right margins, keys for setting and clearing tab stops, a margin release key, a **REPEAT** key, and the **KB** (keyboard) key, which allows you to choose between several different foreign language character sets.

### The printer

The *Typestar 6* has a thermal-transfer printer that uses special miniature ribbon cartridges. The thermal process ensures that operation is fairly quiet. As a matter of fact, operation is noisiest when the printhead returns to the left side of the page after printing a line. The whirring sound emitted when that happens seems loud because there is so little noise otherwise!

It is interesting that the *Typestar*

Canon		Typestar 6												
OVERALL														
PRICE														
EASE OF USE														
INSTRUCTION MANUAL														
PRICE/VALUE														
		1	2	3	4	5	6	7	8	9	10			
		Poor		Fair			Good			Excellent				

6 uses a much higher density printhead than is common with even the best of today's dot-matrix printers. A 24 x 9 matrix is about the highest density available on current printers, but the *Typestar 6* uses a 32 x 26 matrix, which yields characters almost indistinguishable from those formed by daisy-wheel or ball printers.

In addition, you may choose from among five different type-faces. The *Typestar 6* comes with Courier 10 built in, but has a slot on the left side of the machine that will accept one ROM (Read Only Memory) cartridge containing an alternate character set. At the present time you may choose from Courier 12, Cubic PS, America PS, and Courier Italic 10, each of which retails for about \$30.

### Word-processing functions

So far, the *Typestar 6* might not sound much different from a standard memory typewriter. Its word-processing functions are what distinguish it. For example, it can center a line of text between the current margins, or between tabs, at the touch of a key. You can specify that your text come out left justified (with a ragged right margin), right justified (with a ragged left margin), or fully justified (both margins even). In addition to setting the usual tabs and margins, the *Typestar 6* handles decimal tabs, allowing you to align columns of numbers easily.

Other parameters you can specify include line spacing, automatic underlining, double-width printing, and automatically underlined double-width printing. You can set the *Typestar 6* up to return the carriage and feed the paper only when you press the RETURN key. Or you can let the *Typestar 6* return (Continued on page 30)

BK PRECISION

FLUKE



ELECTRONICS, INC.

New and Used Electronic Test Equipment  
Sales • Service • Rental • Leasing

CIRCLE 257 ON FREE INFORMATION CARD

## ok Soldering & Desoldering Tools

### DESOLDERING STATIONS



SA-150 Variable Temp. \$364.00  
SA-100 Fixed Temp \$309.00

Compact, lightweight desoldering station with self-contained, high volume vacuum pump and variable heat control. Powerful enough for most difficult thru-hole and multi-layer applications. Features pistol-grip handpiece, trigger-actuated operation, no-clog, straight flow design, easy collector cleaning and handy, built-in tool holder. Easily disassembled for service. Supplied with a .039" conical tip, tip-cleaning pin and spare filters.

### SOLDERING STATION



SA-3-115 \$84.00

Special tip-mounted sensor and sophisticated control circuitry. Temperature stability within 5% over the range of 100°C to 500°C (200°F to 930°F). For 115 VAC. 50/60 Hz operation; 230 VAC model also available. Lighted power and heater indicators, proportional temperature control and temperature indication meter, iron holder and tip cleaning sponge standard. Rugged, compact enclosure. Supplied with special 24 volt, 48 watt, low-leakage iron and SAT-3-01 (1/32 inch) conical tip.


\$29.90

### WB-104-1 WISHBOARD

- 3 bus strips
- 2 sockets
- 3 binding posts
- Mounted on a 5.9" x 8.7" Aluminum ground plate
- 18 14-pin DIP capacity


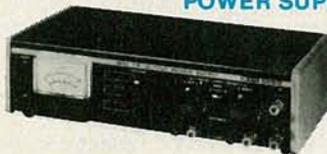
### BK PRECISION TRIPLE OUTPUT POWER SUPPLY



MODEL 1650 \$319.00

- Functions as three separate supplies
- Exclusive tracking circuit
- Fixed output 5 VDC, 5A
- Two 0 to 25 VDC outputs at 0.5A
- Fully automatic, current-limited overload protection
- + and - terminals of each output are fully isolated, in all modes
- All three outputs may be connected in series or parallel for higher voltage or current

### WP-707A Dual Output



\$369.00

- Two DC power supplies, 0-25 V, 0-2 A full load each, or in series to provide 0-50 VDC.
- Two digital voltmeters with range of 99.9 VDC. May be used to measure DC source voltage or current (switch selectable).
- Load regulation .075% max. over full range.
- Ripple 5mV peak to peak max.
- Automatic short circuit shut down (current limiting)

LICATEK DC POWER SUPPLY \$135.00

MODEL 30-3/0-30 VDC/0-3A



LP-1 \$19.95

### DIGITAL LOGIC PROBE

- Use to 50 ns, 10 MHz
- Circuit powered, portable
- Compatible with most logic families

CALL US TOLL FREE

1-800-732-3457

IN CALIFORNIA TOLL FREE

1-800-272-4225

	ADD FOR SHIPPING AND INSURANCE
Master Charge	\$0 to \$250.00 \$4.50
VISA COD	\$251.00 to \$600.00 \$6.50
Money Order	\$601.00 to \$750.00 \$8.50
Check	\$751.00 to \$1000.00 \$12.50
	over \$1000.00 \$15.00

Prices subject to change without notice.

RAG ELECTRONICS, INC. / 21418 Parthenia Street / Canoga Park, CA 91304 / 1-818-998-6500

HITACHI Hitachi Denshi, Ltd.

IWATSU

LEADER Instruments Corporation

POWER DESIGNS


# RAG

## ELECTRONICS, INC.

New and Used Electronic Test Equipment  
Sales • Service • Rental • Leasing

**LEADER**  
Instruments Corporation


### SPECIAL SALE ON LEADER SCOPES

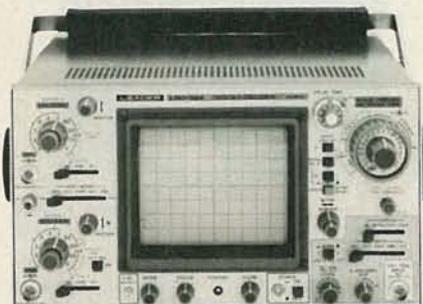

#### LBO 524L DC to 40 MHz

The LBO-524L is designed to meet a broad range of applications in design, testing and servicing of both analog and digital circuits and equipment. Its large 8x10 cm PDA CRT provides sharp, bright displays even at highest sweep rates. Comprehensive triggering controls including holdoff, alternate triggering and delayed sweep triggered functions permit stable displays for even the most complex signals. With 0.5 millivolt sensitivity, extremely low-level signals can easily be observed. A channel 1 output is available on the rear panel to drive other less sensitive instruments such as a frequency counter with an input level as low as 500 microvolts. The dual time base permits accurate observation and time interval measurements of complex waveforms.

**\$749.00**

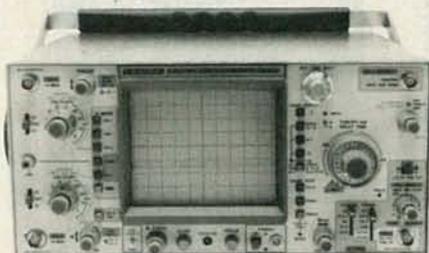


#### LBO-516 DC to 100 MHz

The LBO-516 is an economical 100-MHz, 3-channel, alternate time base oscilloscope. It has all of the important features that are expected in a 100-MHz oscilloscope such as full front panel operation, alternate triggering for simultaneous view of asynchronous signals and independent or simultaneous display of main and delayed time bases. The bright 20-kV PDA CRT and 0.5mV sensitivity permit sharp, bright displays of even those normally tough to see critical signals.

Eight trace capability is possible by displaying main and delayed versions of CH-1, CH-2, CH-3, and CH-1+CH-2. Also included are comprehensive triggering facilities with video sync separators, variable trigger holdoff, excellent trigger sensitivity and more.

**\$1195.00**

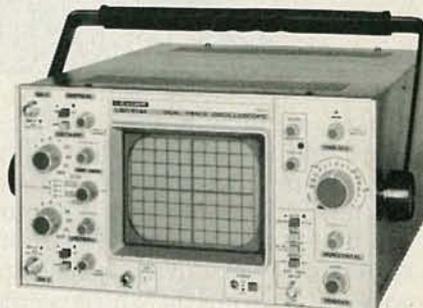

#### LBO-514A DC to 15 MHz

The LBO-514A is a compact 5-inch oscilloscope that offers maximum performance at low cost. Equipped with both vertical and horizontal magnifiers, it has 1-mV sensitivity with X5 magnification and a maximum sweep speed of 0.1 us/cm (0.2 s/cm to 0.5 usec in 18 calibrated steps plus X5 magnification). The LBO-514A provides both chop and alternate dual trace displays.

**\$447.00**

Ask about Leader's Video and RF Generators

LOGICAL

### SHOOTER LOW-COST EPROM BLASTER



- Ideal for Hobbyists or Light Usage
- 128K RAM Buffer
- Build-In RS-232 Port
- Completely Assembled & Tested
- Programs 2716 through 27256
- Fast Intelligent Algorithm
- Works with Any Computer or Dumb Terminal
- Stand-Alone Mode. Copies and Verifies
- Upload/Download in Intel/Motorola/Binary Formats
- 90 Day Warrantee Parts & Labor

**\$395.00**



#### INDUSTRIAL MODEL WITH TIMER MODEL T8/2T

**\$97.50**

- Erases 15 EPROMs in 20-30 Minutes
- Rugged 60 Minute Auto Shut-Off Timer and Safety Interlock
- 5" x 8" Tray with Indicator
- Conductive Pad
- Attractive Steel Enclosure

#### MODEL T8/1

**\$49.95**

This is a Low Cost Unit Designed in a Two Part Plastic Case. This unit erases as many as 8 EPROMs in 15-20 minutes.

CALL US TOLL FREE

**1-800-732-3457**  
IN CALIFORNIA TOLL FREE  
**1-800-272-4225**

CIRCLE 258 ON FREE INFORMATION CARD

RAG ELECTRONICS, INC. / 21418 Parthenia Street/Canoga Park, CA 91304 / 1-818-998-6500

- Master Charge
- VISA ■ COD
- Money Order
- Check



ADD FOR SHIPPING AND INSURANCE	
\$0 to \$250.00	\$4.50
\$251.00 to \$600.00	\$6.50
\$601.00 to \$750.00	\$8.50
\$751.00 to \$1000.00	\$12.50
over \$1000.00	\$15.00

Prices subject to change without notice.

# GIANT 15th ANNIVERSARY SALE!

## FLUKE DMM Accessories



**801-600 AC Current Probe**  
+1000 transformer. Features large jaw opening for industrial use.  
Accuracy:  $\pm 3\%$   
Range: 1A to 600A 30 Hz to 1 kHz  
Jaw Opening: 2 inches (50 mm)

**\$89.00**



**Y8100 DC/AC Current Probe**  
Uses Hall-effect to measure dc or ac current without electrical contact. Battery powered. Two ranges, 20A and 200A  
Accuracy:  $\pm 2\%$  of range (dc to 200 Hz)  
Range: to 200A and 1 kHz  
Jaw Opening: 0.75 inch (19 mm)

**\$197.00**



**85 RF Probe**  
Accuracy:  $\pm 0.5$  dB above 0.5V  
Range: 100 kHz to 500 MHz  
Input Level: 0.25V to 30V rms

**\$76.50**



**Fluke's 80TK** plug-in thermocouple accessory converts virtually any DMM with standard banana plug inputs in a convenient, easy to use temperature measuring device.

**\$52.00**

**80TK SPECIFICATIONS**  
Temperature Measurement Range  
-50 to 1000°C  
-58 to 1832°F  
Battery Life: 1600 Hours (9V)



**80K-40 High Voltage Probe**  
(+1000 resistive divider).  
Accuracy:  $\pm 2\%$ , 20 kV to 30 kV  
Range: to 40,000V dc or peak ac (60 Hz)

**\$72.00**

## LEADER Instruments Corporation

### Audio Sine/Square Wave Generator

- Distortion from  $< 0.05\%$
- 10 Hz to 1 MHz
- 3V 600 $\Omega$



**LAG-120B**  
**\$259.95**



## BK PRECISION FUNCTION GENERATOR

**MODEL 3010**

**\$189.00**

- Sine, square and triangle output
- Variable and fixed TTL outputs
- 0.1 Hz to 1 MHz in six ranges
- Typical distortion under 0.5% from 1 Hz to 100 kHz
- Variable DC offset
- VCO input for sweep tests



## MULTI-FUNCTION COUNTER

**MODEL WD-755**

**\$248.00**

- 5 Hz to 125 MHz
- 8 Digit LED Display
- Period Measurement 5 Hz to 2 MHz
- Totalizes to 99,999,999 Plus Overflow
- Frequency Ratio Mode
- Time Interval Mode
- Switchable Attenuator & Low Pass Filter



## ESCORT DMM's & Capacitance Meter



**MODEL EDM 1116A** **\$89.00**

- 0.5 basic DC accuracy
- AC/DC 200mV, 2V, 200V, 1000V
- AC/DC 2mA, 20mA, 200mA, 10A
- 200 $\Omega$ , 2k $\Omega$ , 200k $\Omega$ , 2M $\Omega$ , 20M $\Omega$
- 2nF, 20nF, 200nF, 2 $\mu$ F, 20 $\mu$ F
- Diode Testing
- hFe Testing
- Audible Continuity Testing



**4 1/2-Digit Multimeter**  
**MODEL EDM 1346A** **\$189.00**

- Audible Continuity Testing
  - Diode Testing
  - Data Hold
- DC Voltage: 200mV-1000V  $\pm(0.05\%rdg + 3dgt)$   
AC Voltage: (True RMS - 200 mV-200V @45Hz-1KHz  $\pm(0.75\%rdg + 10dgt)$   
DC Current: 2A-10A  $\pm(0.75\%rdg + 3dgt)$   
AC Current: (True RMS / 20mA - 200mA @45Hz-400Hz  $\pm(0.75\%rdg + 10dgt)$   
Resistance: 2K $\Omega$ -200K $\Omega$   $\pm(0.1\%rdg + 3dgt)$   
Frequency: 20KHz-200KHz  $\pm(0.5\%rdg + 3dgt)$

## ESCORT



**3 1/2-Digit Capacitance Meter**  
Range: 200PF - 20mF

**MODEL EDC110A** **\$89.00**

- Accuracy:  
20PF-20uF  $\pm(0.5\%rdg + 1dgt + 0.5PF)$   
200uF  $\pm(1.0\%rdg + 1dgt)$   
2000uF-20mF  $\pm(2.0\%rdg + 1dgt)$

CIRCLE 258 ON FREE INFORMATION CARD

the carriage for you automatically when you approach the end of a line. How do you know when you're nearing the end of the line? The *Typestar 6* allows you to set the column at which an alarm bell sounds. Further, the *Typestar 6* has the capability of doing hyphenation. With that feature enabled, as you approach the end of a line and press the hyphen key, the typewriter will automatically print the hyphen and move to the next line.

As capable as it is, the *Typestar 6* does have a few drawbacks. First, it is slow. An experienced typist can easily run several lines ahead of the printhead; and while the microprocessor is taking care of its printing chores, the display is updated very slowly.

Another drawback is the type of paper that must be used. Although you can use inexpensive bond paper for general typing, if you would like high-quality work, then you must use special paper available from Canon that takes advantage of the *Typestar 6's* special thermal-transfer printing process.

You should also be aware that the miniature ribbon cartridges the *Typestar 6* uses are good for only about 20 pages before printing starts to fade. On the other hand, the ribbons are quite inexpensive—about \$2.00.

It would be nice if the unit could be used as a computer printer. (After all, its 26 × 34-dot-matrix printhead is capable of producing nicer output than just about any printer in its price class.) Unfortunately, as no computer interface has been provided, that is not easily done.

The documentation is very good. It is written in clear, readable language, and is printed on high-quality stock. It quickly takes you through the basic operation of the typewriter, and gives you a good understanding of how to use and get the most from its many advanced capabilities.

The Canon *Typestar 6* retails for \$299.95; for more information on that product contact Canon USA, One Canon Plaza, Lake Success, NY, 11042. **R-E**

## Fluke 80TK Thermocouple Converter

Use your DMM to measure temperature.



CIRCLE 6 ON FREE INFORMATION CARD

A PRECISION DIGITAL THERMOMETER IS a vital addition to any laboratory. But even around the house, there are a great many instances when it would be useful to know a temperature with a fair degree of precision (such as when you are

## ChannelPlus™

INTERCONNECT VIDEO WITHOUT SWITCHES

ChannelPlus actually adds new channels right to your existing antenna or cable wires. Take each of your video sources; VCRs, satellite dish, video disk, computer, color or black and white camera, video game, etc. and connect them to ChannelPlus.

If you are adding:


one video source—  
use model H1V—**\$129.95**  
two video sources—  
use model H2V—**\$199.95**

As seen in  
**POPULAR SCIENCE**  
and **VIDEO MAGAZINE.**



one video & one pay TV—  
use model HRV—**\$239.95**  
three video sources—  
use model H3V—**\$269.95**

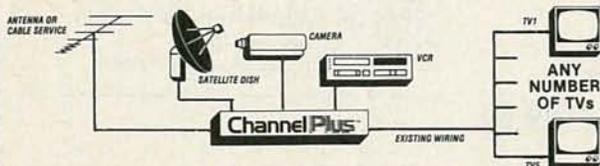Video source picture quality is often improved because ChannelPlus uses the direct video and audio outputs. Use the channel 3 or 4 output from pay TV sources.



*Yours  
Truly*

Please charge my  Visa  Mastercard

Expiration Date \_\_\_\_\_

Signature \_\_\_\_\_

Card Number \_\_\_\_\_

1484 North Kraemer Blvd., Suite 382  
Placentia, CA 92670 • 714-680-0645

CIRCLE 262 ON FREE INFORMATION CARD



## UNGAR® Electronic Soldering System

- Electronic Control
- 24 Volt at the Handle

This versatile soldering system can be tailored to fit most job requirements. The variable temperature range of the 9900 system is 450°F to 850°F. The power base can utilize either a micro-sized or macro-sized iron. The system's versatility is easy to use.

SEND NOW FOR YOUR FREE COPY OF  
THE NEW JENKS ELECTRONICS CATALOG!

Please send the indicated materials:

- Ungar soldering station with power base and micro-size iron (model 9910) **\$87.00**
- Ungar soldering station with power base and macro-size iron (model 9920) **\$93.00**
- Ungar soldering station with power base, micro-size and macro-size irons **\$124.94**
- FREE WS JENKS ELECTRONICS CATALOG

Check/Money Order  MasterCard  VISA  American Express

Card No. \_\_\_\_\_ Exp. \_\_\_\_\_

Signature \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

VA residents add 4% tax; DC residents add 6% tax; MD residents add 5% tax

**w.s. JENKS & Son**



Toll-Free Order Line  
**1-800-638-6405**

2024 West Virginia Ave. NE  
Washington DC 20002

CIRCLE 66 ON FREE INFORMATION CARD

checking your stove, refrigerator, or heating system.) However, a precision digital thermometer can cost in excess of a few hundred dollars. That's quite a sum to pay when you consider that if you own a DMM, you already own a much of the circuitry in such a thermometer.

Fluke (PO Box C9090, Everett, WA 98206) has recently introduced a low-cost alternative. It is the 80TK thermocouple converter. That device takes the output of a K-type thermocouple and converts it so that it can be fed to a standard hand-held or bench-type DMM. (If you are unfamiliar with thermocouples, see "Making Measurements Electronically" in the May 1984 issue of **Radio-Electronics**. That article includes information on thermocouples, their ratings, and how they are used.)

### The 80TK

The 80TK converts the output of a k-type thermocouple into a 1-millivolt-per-degree signal that can be input directly to a DMM. The temperature can be read from the DMM's display, with a resolution as high as 0.1 degree. Of course, the level of resolution will depend on the voltage scale that the meter is set on (of course, higher temperatures will require use of a higher scale).

Temperatures can be measured in either degrees Celsius or Fahrenheit. The temperature scale is switch-selectable from the front of the converter. As that is the only control on the unit, the same switch is used to turn the 80TK on and off.

Using the converter is very simple. The unit is plugged into a DMM, and, in turn, a thermocouple is plugged into the converter. The converter and DMM are turned on, the thermocouple is exposed to whatever it is you want to measure, and the temperature is displayed on the DMM's read-out.

The converter itself is lightweight, weighing in at just 4.5 ounces. Its overall length, including the banana-plug outputs, is just 4 5/8 inches. The banana plugs are spaced 3/4 inches apart, so the unit can be plugged directly into any DMM that adheres to that

BK PRECISION

FLUKE

**RAG**

**ELECTRONICS, INC.**

New and Used Electronic Test Equipment  
Sales • Service • Rental • Leasing

CIRCLE 259 ON FREE INFORMATION CARD

**HITACHI**  
Hitachi Denshi, Ltd.

## CCTV Cameras & Monitors



MODEL KP-120

Meet the new generation of TV cameras that brim with useful features, thanks to the MOS solid-state imaging devices.

- Compact size and light weight
- Long life and high reliability
- Extreme low-light handling capabilities
- No geometric distortion
- Reduced lag and no sticking
- Excellent immunity to vibration and shock
- No effects of magnetic fields
- Sensitive to near-infrared

### MODEL KP-120 Camera Head

Lenses available

**\$775.00**



MODEL HV-720

- Owing to the use of an automatic sensitivity adjusting circuit, the only necessary camera operation is focusing
- A white suppressor circuit ensures faithful reproduction on the video monitor, even for subjects with strong contrast.
- Camera mounting screws are provided at the top and bottom of the camera, facilitating mounting of the camera.
- Switchover to external synchronization takes place automatically when an external drive signal is input, hence no switch operation is necessary.\*
- Synchronizing System: Line-lock 2:1 interlace.
- Pick-up tube: Vidicon tube.
- Includes 16mm f1.6 lens

MODEL HV-720

**\$144.00**

\*MODEL HV-730

**\$199.00**

### B&W MONITORS



VM-900A	9"/500 line/video loop	<b>\$126.00</b>
VM-910	9"/500 line/video loop/ DC restoration/rack mountable	<b>\$164.00</b>
VM-906	9"/700 line/video loop/ DC restoration/rack mountable	<b>\$210.00</b>
VM-129	12"/700 line/video loop/ DC restoration	<b>\$276.00</b>
VM-173	17"/700 line/video loop/ DC restoration	<b>\$312.00</b>

## RAG Used Equipment Sale List

Manufacturer	Model	Description	Price
Hewlett Packard	141T/8552B	Display Storage W/8555A Plug-In	\$13,500.00
Hewlett Packard	141T/8552B	Display Storage W/8554B Plug-In	11,000.00
Hewlett Packard	141T/8552B	Display Storage W/8553B Plug-In	9,500.00
Tektronix	465B	Oscilloscope	2,100.00
Tektronix	2445	Oscilloscope	3,000.00
Tektronix	2215	Oscilloscope	1,300.00
Hewlett Packard	8640B	Signal Generator Option 001 & 003	9,000.00
Hewlett Packard	6268A	Power Supply	1,000.00
Hewlett Packard	8614A	Signal Generator	3,000.00
Hewlett Packard	100CD	Oscillator	250.00
AUL Instruments	ME 30/U	Milliterized HP 400 E	200.00
Hewlett Packard	606B	Signal Generator	1,000.00
Hewlett Packard	608E/F	Signal Generator	1,500.00
Hewlett Packard	1740A	Oscilloscope	1,500.00
Hewlett Packard	334A	Distortion Analyzer	1,300.00

Above equipment sold with 120 day warrantee parts and labor

CALL US TOLL FREE

**1-800-732-3457**

IN CALIFORNIA TOLL FREE

**1-800-272-4225**

Master Charge  
VISA • COD  
Money Order  
Check



ADD FOR SHIPPING AND INSURANCE  
\$0 to \$250.00 ..... \$4.50  
\$251.00 to \$600.00 ..... \$6.50  
\$601.00 to \$750.00 ..... \$8.50  
\$751.00 to \$1000.00 ..... \$12.50  
over \$1000.00 ..... \$15.00

Prices subject to change without notice.

RAG ELECTRONICS, INC. / 21418 Parthenia Street / Canoga Park, CA 91304 / 1-818-998-6500

**HITACHI**  
Hitachi Denshi, Ltd.

**IWATSU**

**LEADER**  
Instruments Corporation

**POWER  
DESIGNS**

# Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Computers, Radar, Avionics and more! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School**  
This proven course is easy, fast and low cost! **GUARANTEED PASS** - You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

**COMMAND PRODUCTIONS**  
FCC LICENSE TRAINING, Dept. 90  
P.O. Box 2223, San Francisco, CA 94126  
Please rush FREE details immediately!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

**OUR 20 YRS.**

of manufacturing quality crystals for the industry, military services, radio amateur and citizens band and experimenters

**IS YOUR ASSURANCE OF STABILITY**



**JAN CRYSTALS**  
Call or Write  
**JAN CRYSTALS**  
P.O. Box 06017  
Fort Myers  
FL 33906-6017  
(813) 936-2397

Since 1965

VISA MasterCard

spacing for its v and COMMON inputs (as most DMM's do).

The 80TK is powered by a nine-volt battery. Estimated battery life is claimed to be 1600 hours by the manufacturer.

Fluke		80TK												
OVERALL PRICE														
EASE OF USE														
INSTRUCTION MANUAL														
PRICE/VALUE														
		1	2	3	4	5	6	7	8	9	10			
		Poor		Fair		Good		Excellent						

### Thermocouples

The unit is supplied with a general-purpose bead thermocouple probe. That probe has a measurement range of  $-40^{\circ}\text{C}$  to  $+260^{\circ}\text{C}$  ( $-40^{\circ}\text{F}$  to  $+500^{\circ}\text{F}$ ). In addition Fluke offers an optional immersion probe for liquids or gels and a surface probe for direct contact

with the surface being measured. All of the Fluke probes attach to the converter via a mini thermocouple connector (sub-miniature K plug). The unit can also be used with probes from other manufacturers that use similar thermocouple connectors.

The converter's specified temperature measurement range is  $-50$  to  $+1000^{\circ}\text{C}$  ( $-58$  to  $+1832^{\circ}\text{F}$ ). Accuracy, provided that the converter is kept within its ambient temperature range ( $0$  to  $50^{\circ}\text{C}$ ), varies between  $0.5\% \pm 2^{\circ}\text{C}$  ( $0.5\% \pm 3.6^{\circ}\text{F}$ ) and  $2.5\% \pm 2^{\circ}\text{C}$  ( $2.5\% \pm 3.6^{\circ}\text{F}$ ), depending on the temperature being measured.

Note that those specifications refer only to the converter itself. They do not include the error introduced by either the thermocouple or the DMM.

The documentation supplied with the unit is brief, but to the point. It does a good job of describing how to use the unit effectively. Maintenance, testing, and calibration information is also provided, as is a schematic diagram and parts list.

While the unit does not have the accuracy of some of the more expensive laboratory models, it should prove more than accurate enough for most applications. The 80TK thermocouple converter carries a one-year warranty, and sells for \$59.00. **R-E**

## Radio-Electronics

is happy to announce a new column to serve our readers. If you have a question regarding any area of electronics, ask us! We'll do our best to find an answer to your question or, at least, suggest where you might find one. Send your questions to:

**Ask Radio-Electronics**  
200 Park Avenue South  
New York, NY 10003



"It looks as if his horizontal hold needs some adjustng."

INCLUDING  
800 MHz COVERAGE!

# Regency hand held scanners

*bring you all the action...  
wherever you are!*



HX1000



HX2000



HX750



HX650

When you need to hear the action from wherever you are, Regency delivers. Our portable scanners keep you in touch with the local news. Whether it's bank hold ups, three alarm fires, weather, business, marine radio, or aircraft calls, Regency portables bring you the on the scene action. While it's happening from where it's happening . . . in your neighborhood.

## PROGRAMMABILITY WITH A CHOICE

Regency offers you two new exciting keyboard programmable hand held scanners. First there's the HX2000 20 channel, no crystal scanner. It offers UHF and VHF ranges with the important addition of 800 MHz and aircraft frequencies. And with features like search and scan, priority, liquid crystal display, and selectable search

increments, the HX2000 is a sure winner.

If you don't need the extended coverage, there's the HX1000. It let's you cover your choice of over 15,000 frequencies on 30 channels at the touch of your finger. No crystals are necessary. Six band coverage, search and scan, priority control, and a liquid crystal display with special programming messages and clock are all part of the package. And with the sealed rubber keyboard and die-cast aluminum chassis, the HX1000 is the most rugged and durable hand held on the market.

## CRYSTAL-CLEAR

If you don't need all the features of programmables, but you want the convenience of portability, we've got you covered. Our two crystal controlled hand held scanners, the HX650 and HX750, offer

six channels, individual channel lock outs, LED channel indicators, step control, two antennas and an adaptor/charger. Both cover VHF high and low, UHF and "T" public service bands, with the HX750 offering the additional coverage of VHF aircraft band.

## DECIDE FOR YOURSELF

Your Regency Scanner dealer would be happy to give you a free demonstration of these and other new Regency Scanners. Stop in today. Or, write Regency Electronics, 7707 Records St., Indpls., IN 46226.

  
**ELECTRONICS, INC.**  
7707 Records Street  
Indianapolis, IN 46226

CIRCLE 278 ON FREE INFORMATION CARD

# IF YOU WANT TO GET INTO YOU HAVE TO GET INTO

## Learn PC Servicing By Building Your Own NTS/HEATH HS-15 Desk-Top Computer, Circuit-By-Circuit

### NTS Intrinsic Home Training Takes You Below The Surface

NTS gets you right down into the heart of computer circuitry. You learn how microprocessors function, how they are designed, how they operate and are used to solve problems. Your program includes a wide variety of tests and projects, as you assemble your PC. You experience the excitement of seeing your own skills grow, the security of knowing you really understand what makes a computer tick.

### A Career in PC Servicing

The world of computers is constantly expanding. Applications have spread from business to manufacturing, from industry to medical and scientific fields. Computer-aided design, engineering, and production have revolutionized drafting, graphics, and prototyping. Computer sales figures point to a continuing need for service technicians as well as installation and maintenance specialists. The type of training you receive will largely determine your ability to take advantage of these opportunities .... and nothing beats the practical, down-to-earth training you get from NTS.

### The NTS/HEATH 16-Bit HS-151

This desk-top PC is the most powerful and versatile ever offered in any home training program. Check the advanced features listed below:

1. 128 KB RAM user memory on board, expandable to 640 KB
2. 16-bit 8088 Microprocessor accepts advanced software, speeds word processing; also allows selection from the huge library of IBM software.
3. 5.25-inch floppy disk drive, double density, IBM formatted, stores up to 360 KB. (Expandable to dual disk drive, and optional 10.5 MB hard-disk drive.)
4. MS-DOS operating system, IBM compatibility, make a wide choice of software programs available.
5. Four open IBM-compatible slots provide for future expansion, printer, modem, etc. Will accept most peripheral boards designed for IBM-PC.
6. Two video outputs for color or monochrome display monitor. Your NTS course includes a high resolution monitor displaying 80 characters by 25 lines, or graphics.
7. Editing capabilities help you insert or delete characters and lines, erase, jump or smooth scroll, etc.

Your NTS training course will teach you to program on this outstanding PC, using lessons, texts, and diagrams to make full use of its capabilities. Catalog contains complete details.

**IBM  
Compatible**




*Learning circuitry through the construction of this equipment offers practical training for which there is no substitute. Test equipment is included.*

*Field servicing is interesting and rewarding. Technicians may work for a service company, manufacturer, or major users.*

*The NTS/HEATH HS-151 PC completed, includes monitor and full-function keyboard with calculator style keypad, and typewriter format.*




# NTS TO PC SERVICING A MICROCOMPUTER

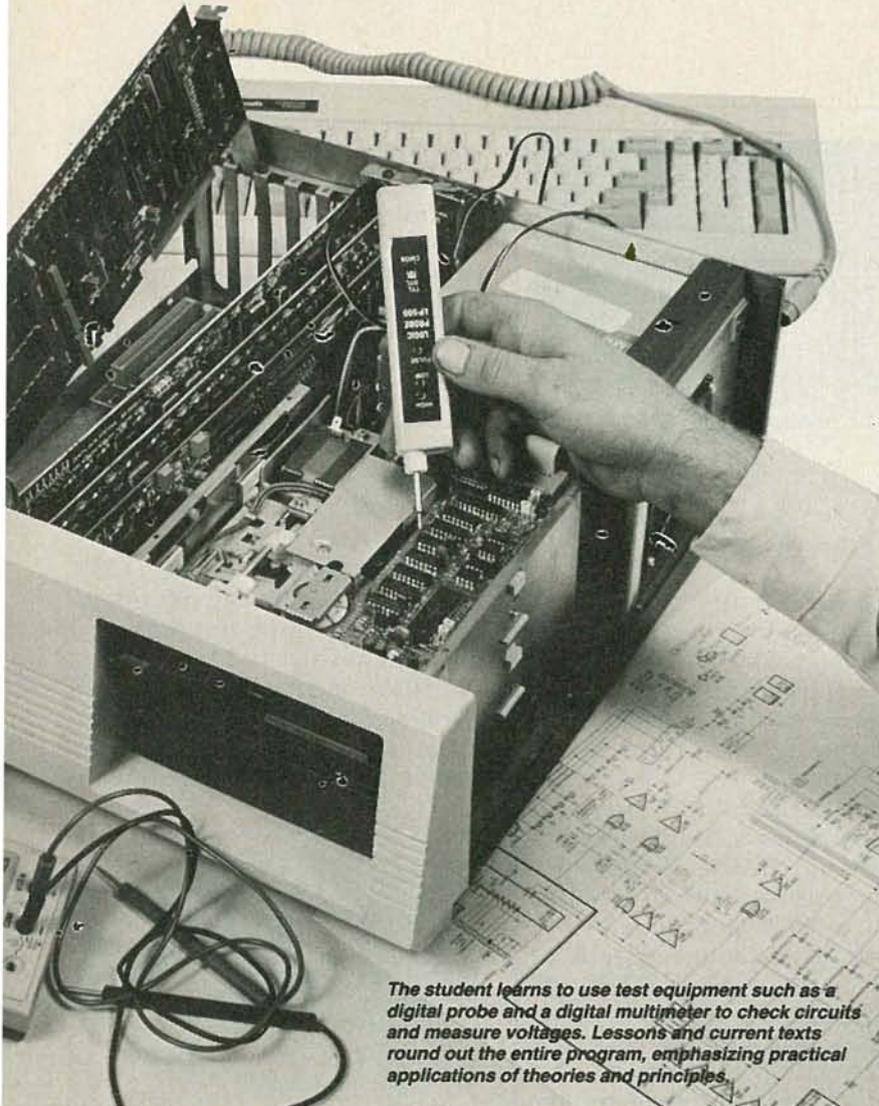

*The student learns to use test equipment such as a digital probe and a digital multimeter to check circuits and measure voltages. Lessons and current texts round out the entire program, emphasizing practical applications of theories and principles.*

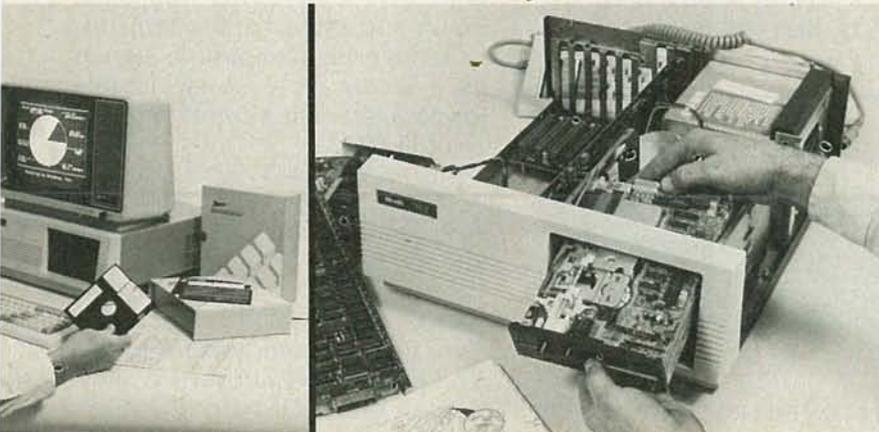*Installing the disk-drive in the PC is one of the final stages in the assembly of the microcomputer. Learning the use of test equipment to check circuits is an integral part of the training which, with field experience, develops invaluable career skills.*



## NTS COURSES COVER MANY AREAS OF SPECIALIZATION IN ELECTRONICS:

**Robotics:** Build the NTS/HEATH Hero 1 Robot as you learn robotic programming. Robot is complete with arm and gripper, voice synthesizer. Robotics is becoming increasingly important in industry as almost daily news features attest.

**Video Technology:** Build one of the most advanced Color TV sets in America as you learn circuit diagnostics, and the use of digital test instruments. Course covers color TV, video tape recorders, computer fundamentals, solid-state devices.

**Industrial and Microprocessor Technology** covers circuit analysis, microprocessors and automation applications, lasers, and basic industrial robotics.

**TV & Radio Servicing** is a specialized course offering an excellent foundation in the use and application of both analog and digital test equipment as applied to the TV servicing field. Learn circuits, adjustments, trouble-shooting, and servicing of Color and monochrome monitors.

**Digital Electronics** offers the student the opportunity to get involved with computer concepts, computer technology fundamentals, and digital equipment by training on the NTS Compu-Trainer.

**Basic Electronics** is a course designed for those wishing to have an over-view of electronics in many of its aspects including radio receivers, solid state devices, and electronic components.

NTS Intronic training programs include a variety of superb equipment, most of which is classified as field-type, making the training practical and career oriented. Texts and lessons have been tested in our Resident School in Los Angeles to assure home study students their courses of training are easy to understand. NTS, now in its 80th. year, continues to be at the leading edge in Electronics home training.

\* IBM is a trademark of International Business Machines Corp.

\* MS is a trademark of Microsoft Corp.

If card is missing, simply write to the address shown below stating the course you are interested in. A FREE color catalog with all details will be sent to you by return mail.


**NTS NATIONAL  
TECHNICAL  
SCHOOLS**

TECHNICAL TRADE TRAINING SINCE 1905  
Resident and Home-Study Schools

4000 So. Figueroa St., Los Angeles, CA 90037

NOVEMBER 1985

# NEW PRODUCTS

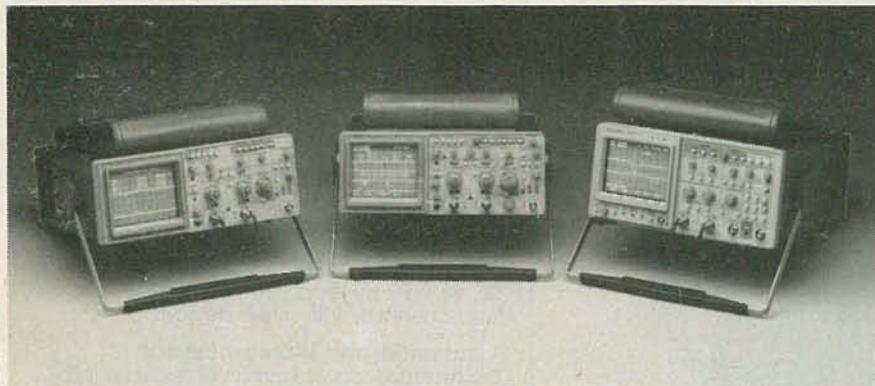

CIRCLE 21 ON FREE INFORMATION CARD

**DIGITAL STORAGE OSCILLOSCOPES**, models 2220, 2230 and 2430 offer high speed in portable packages. The top-of-the-line model 2430 has a digitizing speed of 100 million samples per second, a bandwidth of 150 MHz, and can catch glitches as narrow as 2 nsec. The 2430 has two CCD's (Charge Coupled Devices) for simultaneous dual-channel signal acquisition. Its extensive trigger capabilities include time- and event-delay, combination, variable hold-off, auto-level, etc.


A special patented feature, "save-on-delta," allows the 2430 to compare incoming waveforms with a previously stored reference, and save the incoming wave if it differs from the reference. That makes the unit ideal for "babysitting" applications. The 2430 can store as many as six waveforms

after power is removed. The 2430 comes standard with a GPIB interface, through which it may be programmed. The unit may also be programmed using menus selected through five front-panel pushbuttons.

Models 2230 and 2220 offer similar capabilities at lesser speeds: 100 MHz and 60 MHz, respectively. Both models offer digitizing speeds of 20 million samples per second, glitch-capture speeds of 100 nsec, and optional GPIB and RS232C interface modules.

Models 2240 and 2230 allow the user to position cursors on the screen to read out delta-time, inverse of delta-time (frequency) and delta-volts. The 2240 lists for \$8900; the 2230 lists for \$5150; and the 2220 lists for \$4150.—**Tektronix, Inc.**, P. O. Box 500, Beaverton, OR 97077.

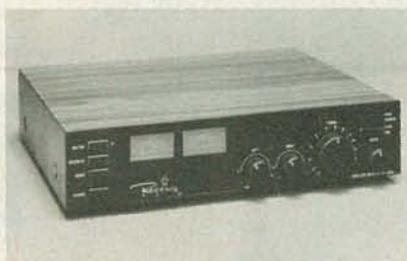**STEREO SATELLITE RECEIVER**, the model SR3500, uses a block down-converter instead of the usual single conversion type. The block system ensures a clean, crisp picture, and allows the user to install a multiple-receiver system. The unit can also receive stereo broadcasts in either the discrete or matrix mode.



CIRCLE 22 ON FREE INFORMATION CARD

Other features include signal strength and tuning meters, built-in Chaparral Polarotor 1 polarity control, channel 2 or 3 RF modulator, and a contemporary design with simulated woodgrain cabinet. An A/B switch, compatible with the Regency SR5000 block system, is also available for dual feed installations. The model SR3500 is priced at \$599.95.—**Regency Electronics, Inc.**, 7707 Records Street, Indianapolis, IN 46226-9989.

**MULTI-COUNTER**, model WD-757, is capable of frequency, period, totalize, ratio, and time-interval measurements. It achieves  $\pm 0.003\%$  accuracy and  $\pm .002\%$  stability tolerance through a combination of CMOS, TTL, low-power Schottky, and LSI tech-



CIRCLE 23 ON FREE INFORMATION CARD

nology. It is equipped with three inputs and a switchable attenuator to reduce high-amplitude signals by a factor of 10. A switchable lowpass filter has a cutoff frequency of 10 MHz.

The model WD-757 has a suggested list price of \$479.00—**VIZ Test Equipment**, 335 East Price Street, Philadelphia, PA 19144.

**PROBE**, model IR-10, is a non-contact, infrared temperature probe. The model IR-10 converts a Simpson (or other) DMM or VOM to a


# ADVANCE ELECTRONICS

IS PROUD TO ANNOUNCE

**Beckman Industrial™ EASY B.O.B. SERIES**

OF PORTABLE

## Break Out Boxes

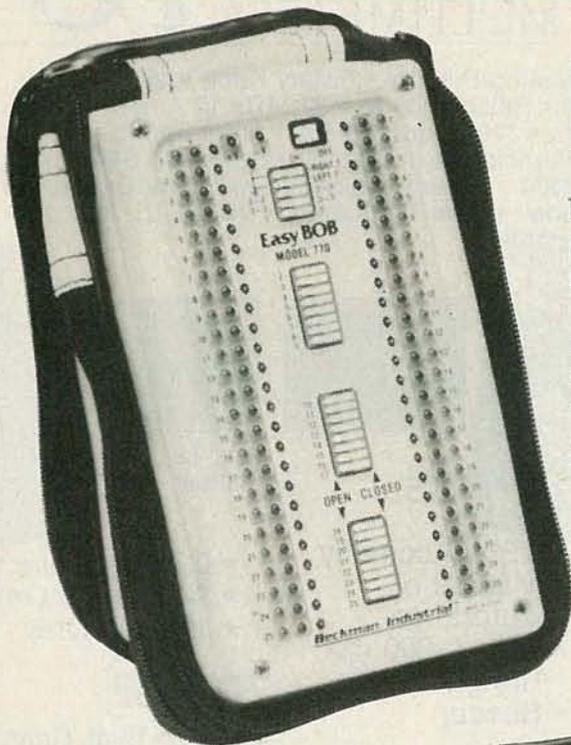

**EASY B.O.B.**  
Model 750, 770  
Breakout Box, RS 232C

**FEATURES:**

- Full RS 232C Breakout
- Line Powered (750) (not shown) or Self-Powered (770) (shown)
- 50 Pairs of Red and Green LED's
- Control Signal Simulation
- 2/3 Swap Switch
- Convenient Dual-Gender Connectors
- Cable Test Feature

*The Ultimate in Interface Testing—  
Four State signal status of all lines at  
a glance, null modem and loopback  
testing at the flip of a switch, dual  
gender connectors, switchable  
ground line, cable test feature,  
choice of powered (Model 770) or  
unpowered (Model 750) and more!*

### EASY CABLETESTER

Model 715  
RS 232C



**FEATURES:**

- Quickly Identifies Cable Wiring
- Scan and Single Step Test
- Convenient Dual-Gender Connectors
- Fits in the Palm of Your Hand
- Optional Remote Indicator for Analyzing Installed Cables (Model 716)
- No External Power Required
- Open, Continuity and Bridging Light Indicators

### EASY B.O.B.

Model 730  
Breakout Box, RS 232C

**FEATURES:**

- Full RS 232C Breakout
- Self-powered
- Sensitive, High Impedance Circuitry
- Dual Pulse Trap
- Control Signal Simulation
- Convenient Dual-Gender Connectors
- 49 Probe Points

**CALL FOR  
PRICES!**



TOLL FREE HOT LINE  
**800-223-0474**

212-730-7030

26 WEST 46th STREET, NEW YORK, N.Y. 10036

THE TEST EQUIPMENT SPECIALISTS

**ADVANCE  
ELECTRONICS**



PHILIPS



WESTON



Non-Linear Systems



LEADER



- 77**
- 0.3% Accuracy
  - Manual or Autorange
  - 10A + mA Range
  - Beeper
  - "Touch-Hold" Function

Sale (with holster)  
**\$11995**

**WE CARRY A FULL LINE OF FLUKE MULTI-METERS. IN STOCK NOW**

SALES ENDS NOV. 85

# FLUKE 70 SERIES MULTIMETERS

- Analog Display • Rotary Knob • Volts AC & DC • Resistance to • 32 MΩ • 10 Amps • Diode Test • 3200 Counts • Fast Autoranging • Function Annunciators in Display • Power-Up Self Test • 2000+ Hour Battery Life w/ Power Down "Sleep Mode" • New Test Leads • VDE & UL Approval



SALE  
**\$8995**

**75**

- 0.5% Accuracy
- Manual or Autorange
- 10A + 300 mA Range
- Beeper



SALE  
**\$7995**

and free C70 holster **73**

- 0.7% Accuracy
- Autorange Only
- 10 Amp Only



**4 1/2 DIGIT MULTIMETERS**

**\$349 00**

MODEL 8060A



- Frequency measurements to 200KHz
- dB measurements
- Basic dc accuracy 0.4%; 10 μV, 10 nA and 10 mΩ sensitivity
- Relative measurements
- True RMS
- High-speed Beeper



**BREAKS THE PRICE BARRIER**


**WITH THESE HIGH PERFORMANCE OSCILLOSCOPES**

**100 MHz Dual Trace/ Dual Time Base**

- 1 mV/div sensitivity
- 23 calibrated sweeps
- Rectangular CRT with internal graticule and scale illumination
- Signal Delay Line

**\$995**

Does not include probes (\$60.00 a pair when purchased with scope)

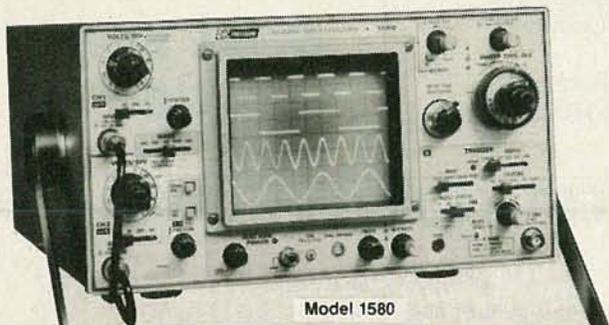

Model 1580

**QUANTITIES ARE LIMITED**



**100 MHz Dual Time Base SCOPE**

MODEL 1590



**\$1395 00**

PRICE DOES NOT INCLUDE PROBES

- 1mV/division sensitivity to 70 MHz
- 500 μV/division cascade sensitivity
- Four-input operation provides trigger view on 4 separate inputs
- Alternate time base operation
- Switching power supply delivers best efficiency and regulation at lowest weight



**INDUSTRIAL TRANSISTOR TESTER**

**\$21995**

MODEL 520B



- Now with HI/LO Drive
- Works in-circuit when others won't
- Identifies all three transistor leads
- Random lead connection
- Audibly and visually indicates GOOD transistor



**CAPACITANCE METERS**  
**\$20995**

MODEL 830

- Automatically measures capacitance from 0.1pF to 200mF
- 0.1pF resolution
- 0.2% basic accuracy
- 3 1/2 digit LCD display



**\$16995**

MODEL 820

- Resolves to 0.1pF
- 4 digit easy-to-read LED display
- Fuse protected against charged capacitors
- Overrange Indication

# BECKMAN'S CIRCUITMATE® ALL UNDER \$100

AVAILABLE NOW...



**\$64.95**

Circuitmate DM 20—  
3½-digit, pocket-size  
multimeter; 0.8% Vdc  
accuracy, diode test,  
hFE test, conductance,  
10 amps AC and DC  
ranges, auto-polarity,  
auto-zero, auto-  
decimal



**\$69.95**

Circuitmate DM 40 —  
3½-digit multimeter;  
0.8% Vdc accuracy,  
diode test, auto-  
polarity, auto-zero,  
auto-decimal



**\$89.95**

Circuitmate DM 45 —  
3½-digit multimeter;  
0.5% Vdc accuracy,  
diode test, continuity  
beeper, 10 amps AC  
and DC ranges, auto-  
zero, auto-polarity,  
auto-decimal



**\$79.95**

Circuitmate DM-25—  
3½ digit, pocket-size  
multimeter; 0.5% Vac  
accuracy, diode test,  
capacitance, continuity  
beeper, conductance,  
10 amps AC and DC  
ranges, auto-polarity,  
auto-zero, auto-  
decimal

**SUPER REBATES  
ON B&K SCOPES  
CALL NOW**



The DM73 is the smallest digital multimeter on the market. Its probe-style design makes it ideal for taking measurements in hard-to-reach test areas.

**SALE  
\$59.95**

- Small Size
- Complete Autoranging
- "Touch Hold"
- Audible continuity checking



**\$76.95**

The DM 77 gives you the convenience of autoranging plus 10 amps ac/dc measurement capability. You simply select the function you want, and the DM 77 automatically sets the required range.

...Quality and Performance  
Beckman and 4½ Digits...




MODEL 4410

True RMS

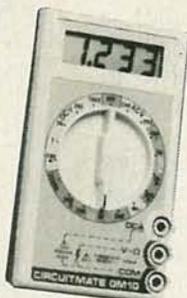**\$239.00**

AVAILABLE NOW!

BECKMAN does it again...a true RMS 4½ DMM w/1 year calibrated cycle at a 3½ digit price.



**NEW**  
Beckman  
Circuit-mate  
DM10

**\$39.95**

in stock now  
Model DM 10B  
with Beeper \$49.95



POWER SUPPLIES



**\$319.95**

MODEL  
1601

- Isolated 0-50VDC, continuously variable; 0-2A in four ranges
- Fully automatic shutdown, adjustable current limit
- Perfect for solid state servicing



**\$339.95**

MODEL 1650

- Functions as three separate supplies
- Exclusive tracking circuit
- Fixed output 5VDC, 5A
- Two 0 to 25VDC outputs at 0.5A
- Fully automatic, current-limited overload protection



MODEL  
3010

FUNCTION GENERATORS

**\$199.95**

- Sine, square and triangle output
- Variable and fixed TTL outputs
- 0.1 Hz to 1MHz in six ranges
- Push button range and function selection
- Typical sine wave distortion under 0.5% from 1 Hz to 100kHz

MODEL **\$329.95**  
3020

SWEEP FUNCTION

- Four instruments in one package — sweep generator, function generator, pulse generator, tone-burst generator
- Covers 0.02Hz-2MHz
- 1000:1 tuning range
- Low-distortion high-accuracy outputs



TOLL FREE HOT LINE

**800-223-0474**

212-730-7030

26 WEST 46th STREET, NEW YORK, N.Y. 10036

THE TEST EQUIPMENT SPECIALISTS

**ADVANCE  
ELECTRONICS**

# NOW, a mini-scope with the features most wanted by field engineers!



B&K-PRECISION MODEL 1420 \$825

This 15MHz dual-trace mini-scope was designed by B&K-PRECISION engineers to respond to the special needs of field engineers... a mini-scope with lab-scope features.

It easily fits into a standard attache case with plenty of storage room for a DMM, tools and accessories. The 1420 can be powered from the AC line, 10-16VDC or an optional internal battery pack.

The rugged 1420 features dual-trace operation and an honest 15MHz response, with useful response beyond 20MHz. An efficient rectangular CRT displays waveforms with good readability under all field service conditions.

There is no sacrifice of features or performance for compact size. The 1420 has 18 sweep ranges from 1  $\mu$ S/div. to 0.5S/div. in a 1-2-5 sequence; variable between ranges. Sweep magnification is X10, extending the maximum sweep rate to 100nS/div. For use with computer terminals or video circuits, a video sync separator is built in. Automatic selection of chop and alternate sweep modes is provided, as is front-panel X-Y operation.

The Model 1420 measures only 4.5 X 8.5 X 12", weighs 7.75 lbs., with batteries and comes with two 10:1 probes.

For complete specifications contact your local distributor or call B&K-PRECISION.

**BK PRECISION**  
**DYNASCAN**  
**CORPORATION**

6460 West Cortland Street  
Chicago, Illinois 60635 • 312/889-9087  
International Sales, 6460 W. Cortland St., Chicago, IL 60635  
Canadian Sales: Atlas Electronics, Ontario  
South and Central American Sales,  
Empire Exporters, Plainville, NY 11803

CIRCLE 77 ON FREE INFORMATION CARD

direct reading, non-contact temperature tester. It can be used to measure the temperature of hazardous materials, fragile objects, live circuits, rough or uneven surfaces, or moving objects. It does not affect the temperature of the object under test.



CIRCLE 24 ON FREE INFORMATION CARD

Probe size is 1.4 inches in diameter X 5.4 inches long, with a 36-inch (uncoiled) cord. The electronic control unit is 2.5 X 1.2 X 4.5-inches. A single 9-volt alkaline battery provides up to 6 months of typical (>100 hours continuous) operation. The model IR-10 is priced at \$395.00.—Simpson Electric Company, 853 Dundee Ave., Elgin, IL 60120.

**AM/FM CASSETTE PLAYERS,** CAR 335, CAR 362, and CAR 372 (shown) are auto-reverse, AM/FM stereo cassette players.

The analog CAR 335 features auto-reverse, a fader, preamp outputs, night illumination, metal tape equalization, auto eject, a DIN-size chassis, and an output of four watts per channel with no more than 1% THD. It is priced at \$149.95.

Both the CAR 362 and the CAR 372 feature a liquid-crystal display with a clock, digital AM/FM tuners with six AM and six FM station



CIRCLE 25 ON FREE INFORMATION CARD


memories, auto-reverse, fader, night illumination, auto seek, pre-amp outputs, metal tape equalization, automatic pinch roller retraction, locking fast forward and rewind, power-antenna leads, and a DIN chassis size.

The CAR 3562 has a single tone control and an output of four watts per channel, with no more than 1% THD. It is priced at \$239.95.

The CAR 372 features, as well, Dolby noise reduction, separate bass and treble controls, and an output of 10 watts per channel with no more than 1% THD. It is priced at \$299.95.

Marantz also offers a mobile power amplifier, model SA402, featuring an output of 40 watts per channel at 10% THD and 30 watts per channel at 1% THD, high and low level inputs, adjustable gain controls, integral heat-sink cooling, and remote on/off sensing. It is priced at \$99.95.—Marantz, 20525 Nordhoff St., Chatsworth, CA 91311.

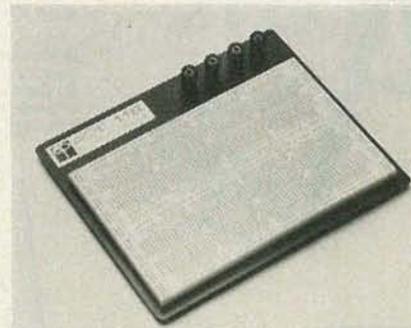**SOLDERLESS BREADBOARD,** the ACE 118, features four binding posts, something usually found on much larger boards. The four standard five-way posts, attached to the base plate, make convenient connections to power supplies, signal generators, or other external equipment.



CIRCLE 26 ON FREE INFORMATION CARD

The ACE 118 has 1280 terminal tie points. Up to 18 14-pin DIPS or 16 16-pin DIPS can be used on the breadboard. Included are 544 distribution tie points, which can be used to offer such functions as voltage and ground buses, reset and clock lines, etc. The ACE 118 accepts all DIP sizes, as well as a wide variety of discreet components. It has a suggested retail

*continued on page 112*

# FREE high tech catalog



Most Accurate Clock uses NBS atomic clock signal to keep "perfect" UTS time.



"Smart" metal locator homes-in on precious metals, disregards junk.



Build IBM-PC compatible Heathkit computer and save, or buy assembled.



Computerized weather station "remembers" weather to aid in forecasting.




Robotics technology comes to life in building HERO™ I and teaching it movement, speech, and manipulation.



World's first low-cost hand-held, microprocessor-controlled Real Time Spectrum Analyzer.



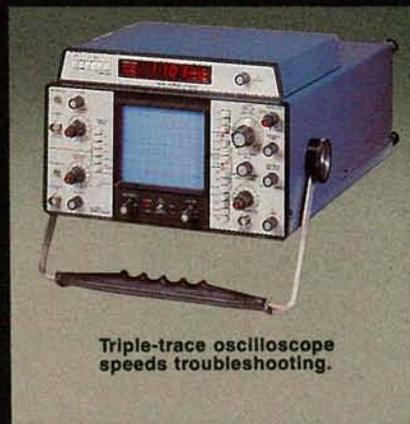"Universal" terminal interfaces computer, ham station for RTTY.



Triple-trace oscilloscope speeds troubleshooting.



Learn computers, programming with Micro-processor Trainer and Course.



HW-5400, one of the finest multi-purpose ham rigs, in affordable kit form.

More than just a catalog, a trustworthy guide to what's new in electronics and computers.

News about important product innovations is packed into every page of the quarterly, full-color Heathkit catalog. Ever since radio became electronics, the illustrated Heathkit Catalog has been a guide to new and exciting kit products for people like you to build. Enjoy and learn from them, while saving money in the process. What sets the Heathkit catalog apart is its range of high quality products and accurate information to help make your buying decisions easy.

All you have to do is fill out the coupon to get your copy

**Heathkit®**  
Heath  
Company

Heath Company  
Dept. 020-354  
Benton Harbor, Michigan 49022

YES! Please send me a copy of the all-new FREE Heathkit Catalog.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

CL-775B Zip \_\_\_\_\_



# Super Disk™ Diskettes

## Now...Diskettes you can swear by, not swear at.

Lucky for you, the diskette buyer, there are many diskette brands to choose from. Some brands are good, some not as good, and some you wouldn't think of trusting with even one byte of your valuable data. Sadly, some manufacturers have put their profit motive ahead of creating quality products. This has resulted in an abundance of low quality but rather expensive diskettes in the marketplace.

### A NEW COMPANY WAS NEEDED AND STARTED

Fortunately, other people in the diskette industry recognized that making ultra-high quality diskettes required the best and newest manufacturing equipment as well as the best people to operate this equipment. Since most manufacturers seemed satisfied to give you only the everyday quality now available, an assemblage of quality conscious individuals decided to start a new company to give you a new and better diskette. They called this product the *Super Disk* diskette, and you're going to love them. Now you have a product you can swear by, not swear at.

### HOW THEY MADE THE BEST DISKETTES EVEN BETTER

The management of *Super Disk* diskettes then hired all the top brains in the diskette industry to make the *Super Disk* product. Then these top bananas (sometimes called floppy freaks) created a new standard of diskette quality and reliability. To learn the "manufacturing secrets" of the top diskette makers, they've also hired the remaining "magnetic media moguls" from competitors around the world. Then all these world class, top-dollar engineers, physicists, research scientists and production experts (if they've missed you, send in your resume to *Super Disk*) were given one directive...to pool all their manufacturing know-how and create a new, better diskette.

### HOW SUPER DISK DISKETTES ARE MANUFACTURED

The *Super Disk* crew then assembled the newest, totally quality monitored, automated production line in the industry. Since the manufacturing equipment at *Super Disk* is new, it's easy for *Super Disk* to consistently make better diskettes. You can always be assured of ultra-tight tolerances and superb dependability when you use *Super Disk* diskettes. If all this manufacturing mumbo-jumbo doesn't impress you, we're sure that at least one of these other benefits from using *Super Disk* diskettes will:

- 1. TOTAL SURFACE TESTING** - For maximum reliability, and to lessen the likelihood of disk errors, all diskettes must be totally surface tested. At *Super Disk*, each diskette is 100% surface tested. *Super Disk* is so picky in their testing, they even test the tracks that are in between the regular tracks.
- 2. COMPLETE LINE OF PRODUCTS** - For a diskette to be useful to you and your computer, it must be compatible physically. *Super Disk* has an entire line of 5 1/4-inch diskettes for your computer.
- 3. SPECIALLY LUBRICATED DISK** - *Super Disk* uses a special oxide lubricant which is added to the base media in the production of their diskettes. This gives you a better disk drive head to media contact and longer head and disk life.
- 4. HIGH TEMPERATURE/LOW-MARRING JACKET** - A unique high temperature and low-marring vinyl jacket allows use of their product where other diskettes won't work. This special jacket is more rigid than other diskettes and helps eliminate dust on the jacket.
- 5. REINFORCED HUB RINGS** - Standard on all *Super Disk* mini-disks, to strengthen the center hub hole. This increases the life of the disk to save you money and increase overall diskette reliability.
- 6. DISK DURABILITY** - *Super Disk* diskettes will beat all industry standards for reliability since they will give you more than 75% of the original signal amplitude remaining even after an average (Weibul B-50) of 30 million passes. They are compatible with all industry specifications as established by ANSI, ECMA, ISO, IBM and JIS.
- 7. CUSTOMER ORIENTED PACKAGING** - All *Super Disk* disks are packaged 10 disks to a carton and 10 cartons to a case. The economy bulk pack is packaged 100 disks to a case without envelopes or labels.
- 8. LIFETIME WARRANTY** - If all else fails, remember, all disks made by *Super Disk* Inc., have a lifetime warranty. If any *Super Disk* diskette fails to meet factory specifications, *Super Disk* Inc. will replace them under the terms of the *Super Disk* warranty.
- 9. SUPERB VALUE** - With *Super Disk's* automated production line, high-quality, error-free disks are yours without the high cost.

## Order toll free 800-USA-DISK

### NOW...NAME BRAND QUALITY AT SUPER CE PRICES

Now, you can buy *Super Disk* brand diskettes directly from Communications Electronics at prices less than "unbranded" generic diskettes. Your data is valuable, so why take chances using a diskette that could be so unreliable that the manufacturer refuses to put their name on it. To save you even more, we also offer *Super Disk* bulk product where 100 diskettes are packed in the same box without envelopes or labels. Since we save packaging costs, these savings are passed on to you. Diskette envelopes are also available from us. These super strong and tear resistant Tyvek® envelopes are only \$15.00 per 100 pack or \$160.00 per 2,000 pack. Use order # TE-5 and specify quantity of 5 1/4" diskette envelopes.

### QUANTITY DISCOUNTS AVAILABLE

Our diskettes are packed 10 disks to a carton and 10 cartons to a case. The economy bulk pack is packaged 100 disks to a case without envelopes or labels. Please order only in increments of 100 units for quantity 100 pricing. With the exception of bulk pack, we are also willing to accommodate your smaller orders. Quantities less than 100 units are available in increments of 10 units at a 20% surcharge above our 100 unit price. **Quantity discounts** are also available. Order 200 or more disks at the same time and deduct 1%; 300 or more saves you 2%; 400 or more saves 3%; 500 or more saves 4%; 1,000 or more saves 5%; 2,000 or more saves 6%; 3,000 or more saves 7%; 5,000 or more saves 8%; 7,500 or more saves 9% and 10,000 or more disks earns you a 10% discount off our super low quantity 100 price. Almost all our diskettes are immediately available from *Super Disk*. Our efficient warehouse facilities are equipped to help us get you the quality product you need, when you need it.

#### SAVE ON SUPER DISK™ DISKETTES

Product Description	Part #	Super Disk 100 price per disc (\$)
5 1/4" SSSD Soft Sector w/Hub Ring	6431-ZJ	0.74
5 1/4" Same as above, but bulk pack w/o envelope	6437-ZJ	0.54
5 1/4" SSDD Soft Sector w/Hub Ring	6481-ZJ	0.84
5 1/4" Same as above, but bulk pack w/o envelope	6487-ZJ	0.64
5 1/4" DSDD Soft Sector w/Hub Ring	6491-ZJ	0.94
5 1/4" Same as above, but bulk pack w/o envelope	6497-ZJ	0.74
5 1/4" DSQD Soft Sector w/Hub Ring (96 TPI)	6501-ZJ	1.49

SSSD = Single Sided Single Density; SSDD = Single Sided Double Density; DSDD = Double Sided Double Density; DSQD = Double Sided Quad Density. TPI = Tracks per inch.

### BUY YOUR DISKETTES FROM CE WITH CONFIDENCE

To get the fastest delivery of your diskettes, phone your order directly to our order desk and charge it to your credit card. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. For maximum savings, your order should be prepaid. All sales are subject to availability, acceptance and verification. All sales are final. All prices are in U.S. dollars. Prices, terms and specifications are subject to change without notice. A \$5.00 additional handling fee will be charged for all orders with a merchandise total under \$50.00. All shipments are F.O.B. CE warehouse in Ann Arbor, Michigan. COD terms are available, in U.S. UPS areas for \$5.00 extra, and are payable with cash or certified check. Michigan residents add 4% sales tax.

For shipping charges add \$6.00 per 100 diskettes and/or any fraction of 100 5 1/4-inch diskettes for U.P.S. ground shipping and handling in the continental U.S. For 1,000 or more disks shipped to the continental U.S., shipping charges are \$3.00 per hundred diskettes. UPS 2nd day air rates are three times continental U.S. rates. For Canada, Puerto Rico, Hawaii, Alaska, or APO/FPO delivery, shipping is three times the continental U.S. rate.

**Mail orders to:** Communications Electronics Inc., Box 1045, Ann Arbor, Michigan 48106-1045 U.S.A. If you have a Visa or Master Card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-USA-DISK. In Canada, order toll-free by calling 800-CA1-DISK. If you are outside the U.S. or in Michigan dial 313-973-8888. Telex anytime 810-223-2422. Order your *Super Disk* diskettes now.

Copyright © 1985 Communications Electronics Inc.

Ad #080185-ZJ



quantity 10,000

# less than 49¢ a disk

# BUILD THIS

# VIDEO TITLER

*Now you can superimpose  
titles and computer graphics  
on video images!*

JACK FLACK

HAVE YOU EVER WANTED TO ADD TITLES TO SOME OF YOUR VCR RECORDINGS? WHILE THERE ARE MANY titlers commercially available that let you liven up your video presentations by adding characters, they do so at the expense of the video image. But the titler we'll describe will change all that. It lets you *superimpose* characters directly on the video image from a VCR, video camera, videodisk player, or even an over-the-air broadcast!

If characters aren't enough for your needs, the titler can be interfaced with a home computer such as the IBM PC, TRS-80 Color Computer, Commodore 64, or Apple II to allow you to superimpose computer-generated graphics or even real-time animation on a standard video signal.

Even with the current "video boom," a device such as this has not been available commercially to the home video enthusiast—until now. Why not? After all, the networks and even local television stations have had expensive computer-based character generators for over 10 years.

Unlike audio, video signals are very complex; they must contain synchronizing, color, detail, and other information necessary to generate a television picture. And to superimpose one video image on top of another, both signals must be synchronized. The difficulty in doing that—because there are no LSI IC's available to do it—is apparently what has kept a product like our titler off the market...until now.

The video titler uses



Motorola's 6809 microprocessor and Texas Instruments' TMS9128 VDP (Video Display Processor). The VDP performs most of the functions needed to generate computer images. It provides: refresh for 16K dynamic video RAM's, asynchronous bi-directional data transfer to internal registers and video RAM, 256×192-pixel resolution, 16 colors, up to 32 separate movable objects called sprites, and—most important for superimposition—the ability to be synchronized (gen-locked) with an external video signal.

Before we go any further in our description of how the video titler works, we should review some of the fundamentals of video and television.

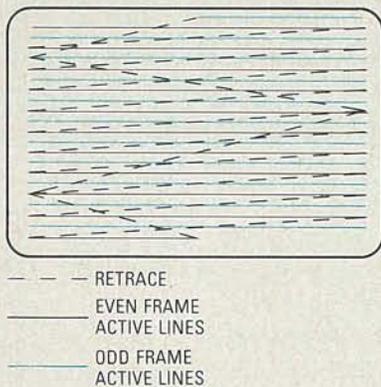


FIG. 1—THE NTSC VIDEO FIELD consists of two frames, which combine for a total of 525 horizontal lines.

### Background on video

The standards for television in the U.S. were adopted during the 1940's for black-and-white TV and enhanced in the early 1950's to provide for color. The group of industry representatives responsible for these standards was the National Television Systems Committee (NTSC).

The NTSC standards call for a *raster* (which is the pattern of scanning lines on a TV picture tube when no signal is being received) of 525 horizontal lines. The raster *frame* of 525 lines consists of 2 *fields*, usually referred to as the odd and even fields. Each field therefore consists of 262.5 horizontal lines. See Fig. 1.

To generate the frame, all the odd lines from the top of the screen to the bottom are scanned first (making up the odd field). Then the beam is returned to the top of the screen, and the even lines are then scanned from the top to the bottom (making up the even field). The process of "weaving together" the odd and even fields to form a raster is called *interlacing*.

Each field is scanned in 1/60 second, so each complete frame is repeated at a rate of 30 frames per second.

The reason that interlaced scanning was chosen by the NTSC is that it helps to eliminate flicker by producing a relatively smooth transition between fields. You can sometimes observe flicker, which is the

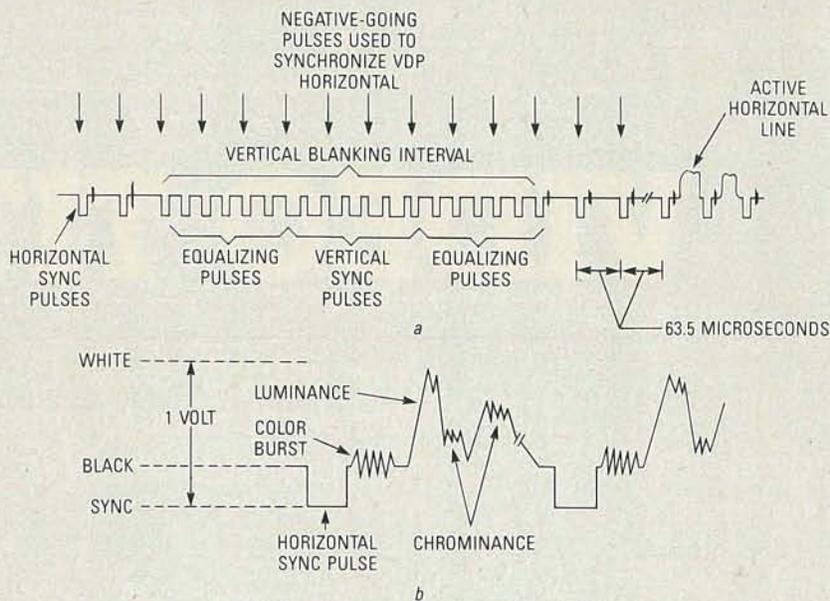


FIG. 2—THE NTSC COMPOSITE VIDEO SIGNAL contains several timing components. For superimposition it's important that the video titler's output be synchronized with them. The vertical blanking pulse is shown in a, and the horizontal sync pulse is shown in b.

slight shifting up and down of images on the screen, with large white-on-black characters (or other high-contrast images). Flicker, which can make it difficult to read characters, especially small characters, is the primary reason computer designers chose not to use 30 frame-per-second interlacing. Home computers usually operate with 262 horizontal lines in each field. The beam then traces the same path 60 times per second. This approach eliminates flicker; however, it also reduces the vertical resolution to one half of the resolution of 525 line interlaced images.

### Composite video

The NTSC composite-video signal that is used to transmit television picture information was also standardized in the 1940's and 1950's. (It is also sometimes referred to as RS-170). Although the polarity and peak-to-peak voltage of the composite video signal is not mentioned in the standard, the other parts of the waveform are fixed. Fortunately, the VCR and video camera industry have standardized the polarity and peak-to-peak voltage of the composite video signals as negative-going sync and 1 volt peak-to-peak amplitude (AC) into a 75-ohm impedance. Make sure that any device you use with the video titler follows those standards!

Figure 2 shows the composite video signal. The signal contains timing components and picture-definition components. For superimposing, the timing components from the titler's video signal (the *vertical sync*, *horizontal sync* and *colorburst*) must be synchronized with those of the external video signal.

**The horizontal sync** and blanking pulses keep the TV receiver's horizontal scanning in step with that at the transmit-

ter, and cut off the picture tube during horizontal retrace. The duration of one horizontal line is 63.5  $\mu$ s, and the blanking pulse interval lasts for about 10  $\mu$ s. Thus, the active video portion of one horizontal line that is actually seen lasts for 53.5  $\mu$ s.

The horizontal sync pulses are about 5 microseconds wide and ride on the blanking pulse pedestal. The colorburst ride on the *back porch* of the horizontal blanking pulse.

**The vertical sync** and blanking pulse must be provided between each field to ensure that vertical retrace begins at the proper time, and to hide the visual effect of the retrace. The pulse occurs at the end of each field, and lasts until vertical retrace has ended. Each vertical blanking interval lasts for between 13 and 21 horizontal lines. (Thus for each frame, 26 to 42 horizontal lines are lost to vertical blanking.)

There are three types of pulses riding on the vertical blanking pulse: equalizing, vertical-sync, and horizontal sync pulses. (A colorburst is inserted after each horizontal sync pulse for color signals.)

Note the waveform of the vertical sync in Fig. 2. Remember that vertical sync occurs after 262.5 horizontal lines. In order to maintain horizontal synchronization during the vertical sync, *vertical serrations* are inserted inbetween the vertical sync pulses and occur at twice the horizontal frequency. The equalizing pulses before and after the vertical sync also occur at twice the horizontal frequency. You will later see that all negative edges of the equalizing pulses, vertical serrations, and horizontal sync pulses are used to synchronize the video titler's horizontal frequency.

**The colorburst** is the heart of the

color-reproduction process. Although this precise 3.579545-MHz (referred to as 3.58 MHz) burst appears only for a few microseconds during the back porch of the horizontal sync, it is used to generate a continuous 3.58 MHz sinewave. This sinewave's frequency and phase is re-established every active horizontal line (except during the vertical blanking period). The way in which the colorburst is used in the generation of colors will be discussed later. For now, it's sufficient to say that the video titler must synchronize its color clock to the external colorburst.

Otherwise, images generated by the titler will appear in a rainbow of random colors.

**The luminance** represents the black-and-white picture detail. It basically is the brightness or degree of white present in each picture element, without regard to the color.

**The chrominance** is the color information of the video signal. The chrominance signal carries the hue and saturation information. Figure 3 illustrates how the chrominance information is encoded and decoded.

The chrominance signal is compared to the chroma subcarrier, which is internally generated by the TV set using the colorburst as a reference sample. Differences in phase result in different hues. The relative amplitude of the chrominance with respect to the chroma subcarrier determines the saturation of the color. A chrominance signal with a small amplitude will result in a pastel color. On the other hand, a large amplitude will result in deep saturated colors.

#### How the video titler works

Now that we have a basic understanding of the standard video signal, let's look at how the video titler can superimpose its video image over an external NTSC composite video signal. Certain conditions must be met before the two signals can be mixed. The vertical, horizontal and color clocks must be synchronized and the amplitude and DC level must be matched.

The heart of the video titler is Texas Instruments' TMS9128 VDP. The VDP operates with a 10.738635-MHz clock (which is 3 times the color subcarrier frequency of 3.58 MHz), from which all of the other internal clocks are derived. The pixel clock is 5.4 MHz (10.7/2), which means that each pixel is approximately 186 nanoseconds wide. The pixel clock is divided by 342 to generate horizontal sync.

The VDP provides for vertical and horizontal synchronization to an external composite video signal through a 3 level RESET/SYNC input. System reset occurs when that input is brought low (less than 0.8 volts). For normal operation, the SYNC/RESET input is held at 5 volts. When it exceeds 9 volts for greater than 7 microseconds, the VDP resets its internal video counters.

That would seem to mean that all we need is a positive-going external sync-signal applied to the RESET/SYNC input, operating between 5 and greater than 9 volts, to synchronize the VDP's internal vertical and horizontal counters with the external signal. Unfortunately, that's not exactly true. Texas Instruments chose not to use the NTSC standard for its sync pulses, and that results in problems with the external reset mechanism.

The VDP resets its horizontal clocks on the leading edge of the pixel clock. If you use some simple math you find that the NTSC horizontal sync occurs about every 63.556 microseconds. That works out to 341.25 pixel clocks. The one-fourth pixel difference causes jagged edges to appear on the images being superimposed on the screen.

The TMS9128 VDP does not internally generate the 3.58 MHz chrominance information. To generate color, it uses color difference signals (R - Y and B - Y) in connection with an external chrominance modulator.

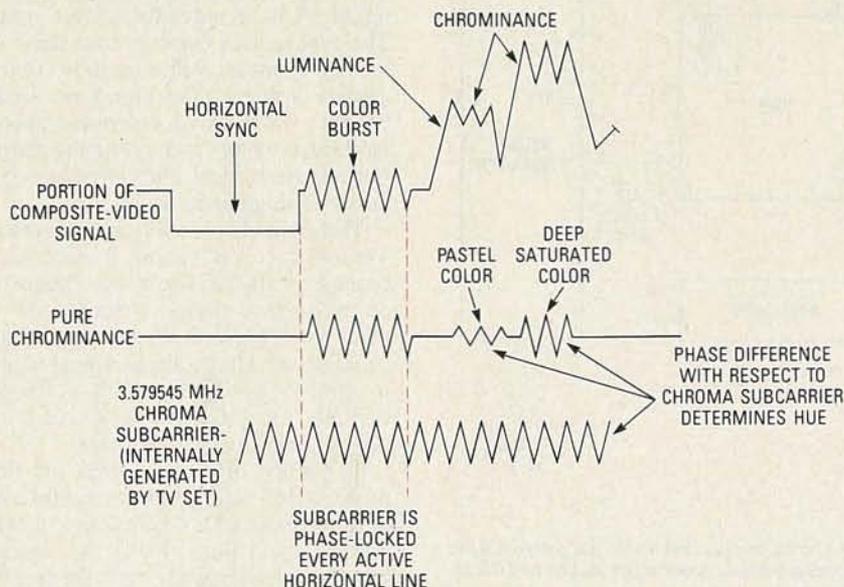


FIG. 3—THE CHROMINANCE SIGNAL AND CHROMA SUBCARRIER, which is generated by the TV set using the colorburst as a reference, are compared to each other. A phase change represents changes in hue.

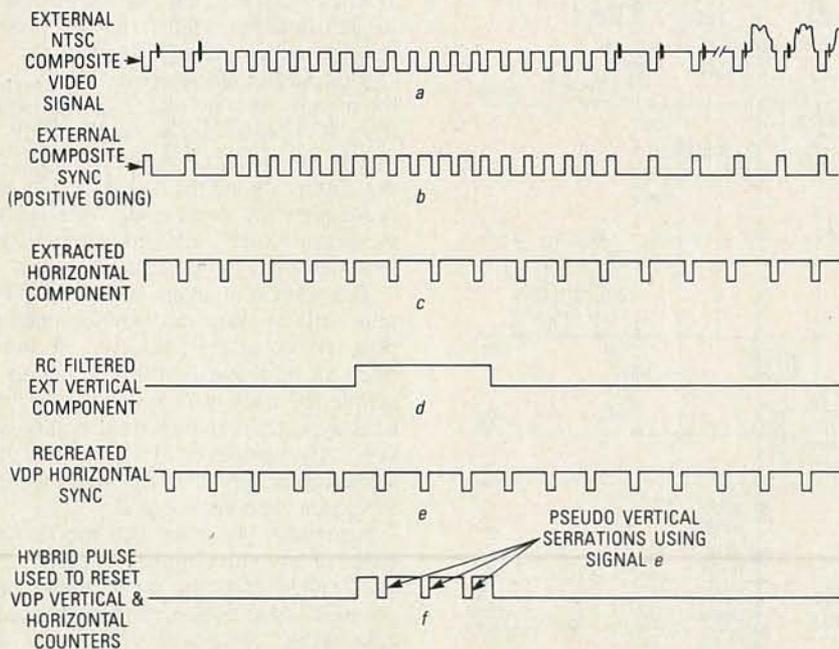


FIG. 4—TIMING SIGNALS USED TO SYNCHRONIZE THE VDP with external horizontal and vertical timing elements. Shown in a is the external composite-video signal, and in b, the external composite sync. In c, we see the extracted horizontal component. The vertical component is shown in d, and the recreated horizontal sync is shown in e. Finally, the hybrid pulse used to reset the VDP's horizontal and vertical counters is shown in f.

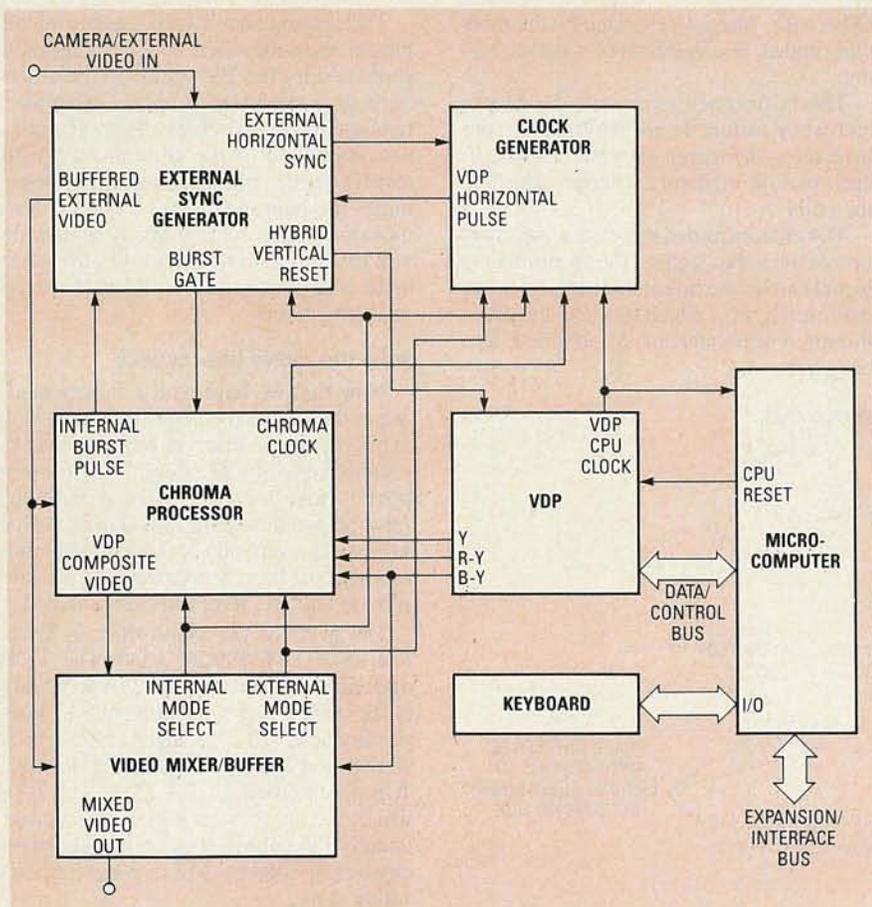


FIG. 5—THE BLOCK DIAGRAM OF THE VIDEO TITLER shows its main sections: the external sync generator, clock generator, video display processor, chroma processor, video mixer/buffer, and micro-computer. We'll discuss those sections in detail next month.

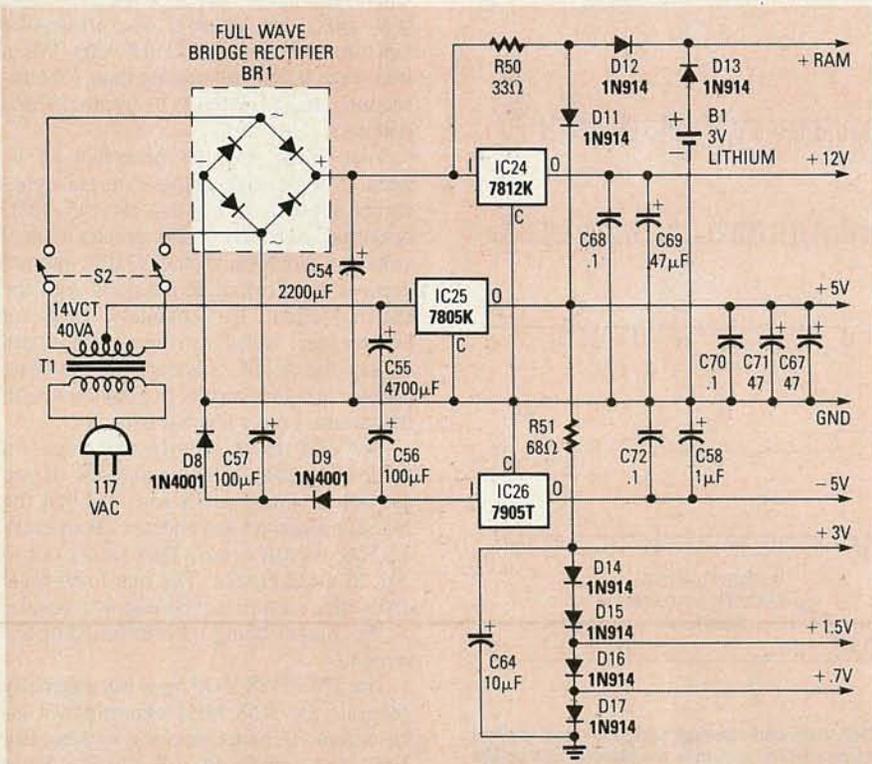


FIG. 6—THE POWER SUPPLY. While the titler operates mainly on +5 volts, the supply also provides the operating voltage for an external video camera.

The TMS9128 can operate quite well at frequencies slightly higher or lower than 10.738635 MHz without affecting the color-generation process. With a standard NTSC horizontal line of 63.556 microseconds, a VDP pixel width of 185.8349 nanoseconds (63.556 divided by 342 pixels per line) will result in the VDP operating at the NTSC horizontal rate. This pixel width can be derived from a master clock of 10.762237 MHz. You'd think with this problem overcome we'd be all set. But not yet.

A second problem exists with the VDP's process of synchronizing to an external VCR or videodisc-player signal. The sync pulses coming from these devices are not as stable as those from a camera or direct video broadcast. That is because VCR's and videodisc players have servo motors controlling the generation of the vertical and horizontal sync pulses during playback.

That instability is referred to as "jitter." Vertical jitter is not as much of a concern because of the relatively slow frequency of the vertical timing element. On the other hand, horizontal jitter may actually be observed when a jittery signal is used to directly reset the VDP's horizontal counters. Once again, what is seen is jagged edges on the VDP's images.

The video titler overcomes the jitter problem by letting the horizontal sync track the external horizontal sync using a phase-locked loop (PLL) to "average out" the jitter. However, the VDP does not provide a separate horizontal output pulse and does not generate vertical serrations or equalizing pulses in its non-standard video signal. Therefore to obtain a horizontal sync during the vertical period, a pseudo horizontal pulse has to be constructed using available signals.

That pulse could be derived by dividing the master clock by 684. However, since the CPU CLOCK output on the VDP is merely the master clock divided by 3, we can further divide the signal by 228 and accomplish the same result. (Using that technique actually allowed us to use one less 4-bit binary counter in the circuit.)

The vertical counters within the VDP must still be reset in order to superimpose. By doing that, however, we introduce an additional problem. Using a simple RC filter, we can extract the vertical sync from the external composite sync. After proper level adjustment, that signal can be applied to the VDP's RESET/SYNC input. So far, so good.

Remember, however, that the leading edges of any pulse applied to the RESET/SYNC input resets the VDP's horizontal counters. Also remember that the standard NTSC composite video calls for 262.5 horizontal lines for each vertical sync pulse. This means that each successive external vertical sync pulse will also reset the VDP's horizontal counters

## PARTS LIST

### All resistors 1/4-watt, 5% unless otherwise noted.

RN1—10,000 ohms × 9 resistor network  
 R1, R16—10,000 ohms  
 R2—6800 ohms  
 R3—75 ohms  
 R4, R48—51,000 ohms  
 R5, R11, R12, R15, R25—R27, R35, R43, R49—1000 ohms  
 R6, R8, R30, R31, R39—4700 ohms  
 R7—3900 ohms  
 R9—5100 ohms, metal film, 1%  
 R10—4300 ohms, metal film, 1%  
 R13, R16, R18, R22, R24, R28, R33, R40—2200 ohms  
 R14, R23—680 ohms  
 R17, R36—120,000 ohms  
 R19, R20, R21—470 ohms  
 R29, R32—1000 ohms, PC-mount trimmer potentiometer  
 R34, R47—220 ohms  
 R37—1500 ohms  
 R38—5100 ohms  
 R41, R42—3300 ohms  
 R44, R45—820 ohms  
 R46—10,000 ohms, PC-mount trimmer potentiometer  
 R50—33 ohms  
 R51—68 ohms

### Capacitors

C1, C40—C42, C44, C64—10  $\mu$ F, 25 volts, electrolytic  
 C2, C3, C5, C9, C11, C14, C15, C16, C26, C33, C38, C39, C45, C47, C48, C49, C50, C51, C53, C60, C61, C62, C63, C68, C70, C72, C73—0.1  $\mu$ F ceramic disc  
 C4—0.01 Metallized film, 5%  
 C6—0.002  $\mu$ F ceramic disc  
 C7—0.005  $\mu$ F ceramic disc  
 C8—0.001  $\mu$ F ceramic disc  
 C10—47  $\mu$ F, 25 volts, electrolytic  
 C12, C27—5–30 pF PC-mount trimmer  
 C13, C28—12 pF, ceramic disc  
 C17—C19, C66—220 pF, ceramic disc  
 C20—150pF ceramic disc

C21—390 pF ceramic disc  
 C24, C30, C58—1  $\mu$ F, 25 volts, electrolytic  
 C35, C37—47 pF ceramic disc  
 C45—22  $\mu$ F, 10 volts, electrolytic  
 C46, C56, C57, C59—100  $\mu$ F, 25 volts, electrolytic  
 C52, C67, C69, C71—47  $\mu$ F, 16 volts, electrolytic  
 C54—2200  $\mu$ F, 25 volts, electrolytic  
 C55—4700  $\mu$ F, 16 volts, electrolytic  
 C65—33 pF, ceramic disc

### Semiconductors

IC1—LM339 quad comparator  
 IC2—74LS221 dual non-retriggerable one-shot  
 IC3—74LS05 hex inverter  
 IC4—MC4044 phase-frequency detector  
 IC5—MC4024 dual voltage-controlled multivibrator  
 IC6, IC7—74LS191 up/down binary counter  
 IC8, IC9, IC13—4066 quad analog switch  
 IC10—TMS9128 video display processor (Texas Instruments)  
 IC11, IC12—4416 16K × 4 dynamic RAM, 150 ns  
 IC14—CA3126 chroma processor (RCA)  
 IC15—74LS00 quad NAND gate  
 IC16—LM1889 TV video modulator (National)  
 IC17—LM361 high-speed comparator  
 IC18—74LS139 dual 1-of-4 decoder  
 IC19—2732 4K × 8 EPROM  
 IC20—6116 2K × 8 static RAM (or 2016)  
 IC21—74LS273 octal D-type flip-flop  
 IC22—74LS244 octal 3-state driver  
 IC23—MC6809 microprocessor  
 IC24—7812K regulator, +12-volts  
 IC25—7805K regulator, +5-volts  
 IC26—7905T regulator, -5-volts  
 D1, D3, D4, D5—D7, D11—D18—1N914  
 D2—1N751 Zener, 5.1 volts  
 D8, D9—1N4001 rectifier, 50 PIV  
 D10—not used  
 BR1—full-wave bridge rectifier, 6 amps

LED1—standard red LED  
 Q1, Q6—2N2222  
 Q2, Q3—2N3906  
 Q4, Q5—2N3904

### Other components

XTAL1—3.579545 MHz  
 L1—56  $\mu$ H  
 T1—14-volt secondary, center-tapped  
 J1—10-pin video camera jack  
 J2, J4—J6—PC-mount phono jack  
 J3—3/32 inch phone jack  
 S1—SPST PC-mount slide switch  
 S2—DPDT rocker switch, vertical PC mount

**Miscellaneous:** Lithium-battery holder and battery, 49-key keyboard, 16-conductor ribbon cable, enclosure, etc.

The following are available prepaid from Micro-Video-Technology, P.O. Box 76, Chattanooga, TN 37343: main PC board (silk screened, with gold fingers), \$40; Programmed EPROM, \$25; Custom keyboard (Cherry Electric), \$80; Custom enclosure, \$40; All switches, jacks, and connectors, \$30; 14 VCT wall transformer, \$30; TMS9128 VDP, \$30; partial kit (includes all the above), \$250. All orders add \$5 (\$13 outside U.S.) for shipping and handling.

The following is available from MFJ Enterprises, Inc., 921 Louisville Road, Starkville, MS 39759: Complete titler, assembled and tested with 1 year unconditional guarantee, \$599.95 plus \$6 shipping. (Return if not satisfied within 30 days for refund, less shipping.) Orders only (outside Mississippi) 1-800-647-1800. Information and Mississippi orders 601-323-5869. MasterCard and Visa accepted.

at a point that is one half horizontal line different from the previous frame.

In the meantime, the recreated VDP horizontal pulse is still tracking the external horizontal frequency. That would cause characters on the left of the screen to jump to the center and back to the left with each successive external vertical sync pulse!

In order to deal with that within the video titler, pseudo vertical serrations (inverted VDP horizontal sync pulses) were inserted into the vertical pulse used to reset the VDP. Those horizontal pulses are, in fact, the same recreated pulses used by the PLL. Figure 4 shows the signals used to synchronize the VDP with external horizontal and vertical timing elements.

As for the color synchronization of the titler, there are a number of chroma-processor integrated circuits designed specifically to generate a synchronous chroma subcarrier. The RCA CA3126 was se-

lected primarily because of its sinewave output, which provides relatively easy interface with the video titler's chroma modulator, National's LM1889.

The last design area of the titler worth mentioning here is the requirement for matched signal amplitude and DC level. Fortunately the video signal amplitude of the VDP is very close to the external signal being used and the DC level adjustment is handled by a simple diode clamp.

### The video titler circuit

Figure 5 is a block diagram of the video titler. The six main sections of the titler are: the external sync generator, clock generator, video display processor, chroma processor, video mixer/buffer, and microcomputer.

There is an additional section to the titler—the power supply—that isn't shown in the block diagram. Its schematic is, however, shown in Fig. 6. The power supply provides several separate DC volt-

ages: +12, +5, +3, +1.5, +.7, and -5.


The power supply obtains the necessary positive and negative voltages from a wall-mounted transformer.

The -5 volts is obtained by applying the 14-volt AC signal through C57 and clamping the most positive peak at zero using D8. Diode D9 serves as a half wave rectifier whose output is filtered by C56 before going to the -5 volt regulator (IC26).

Two positive voltages of about +8.5 and 17 are regulated to provide +12 and +5-volt supplies. Simple 3 terminal voltage regulators with TO3 cases (IC24 and IC25) were selected because of their heat sinking capacity.

That's all the circuit we have room to talk about this month. When we continue, we'll discuss other features of the power supply, and we'll present the rest of the circuit, along with foil patterns and construction details.

R-E

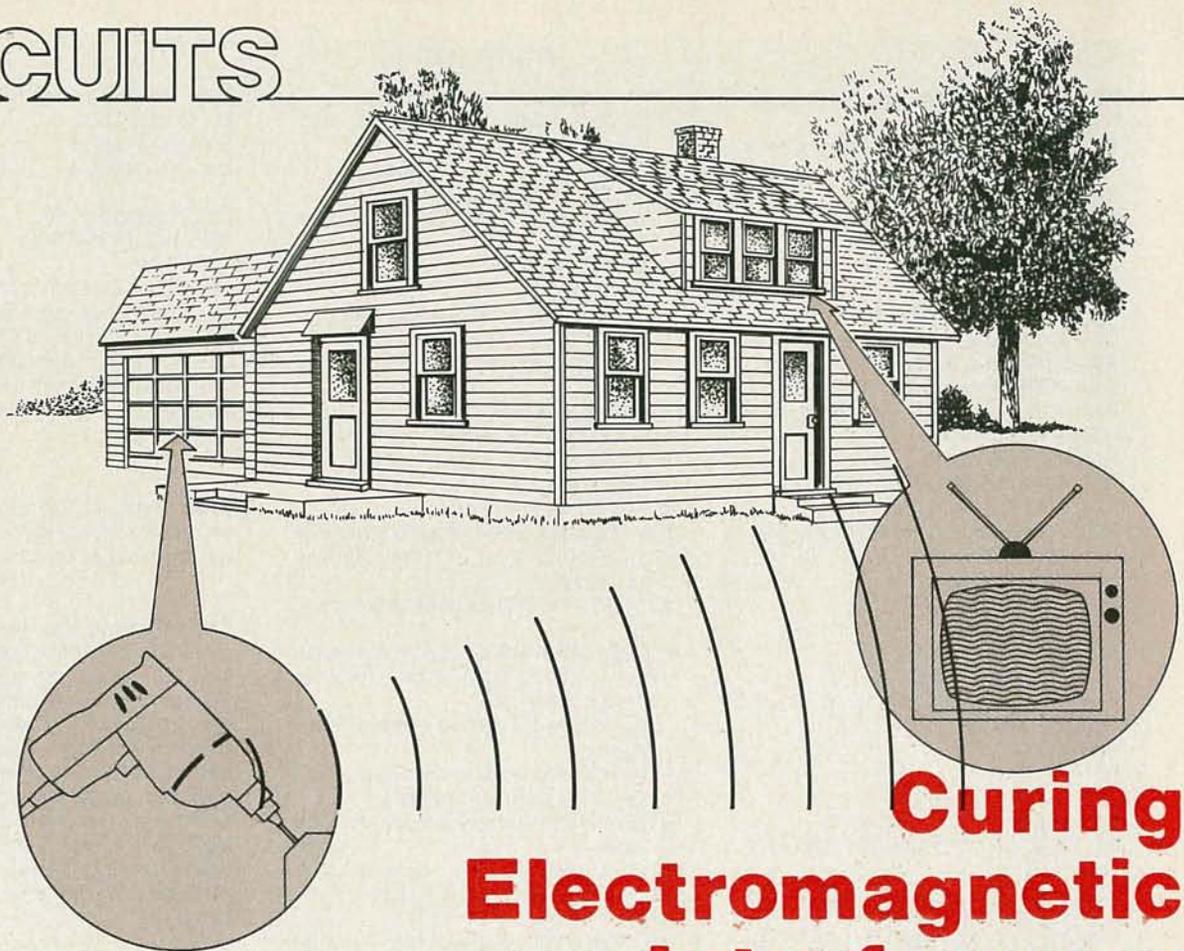

## Curing Electromagnetic Interference

MICHAEL F. VIOLETTE

*Learn all about the causes of electromagnetic interference, and what you can do to neutralize its effects.*

EACH AND EVERY ONE OF US HAS EXPERIENCED the effects of electromagnetic interference (EMI). For instance, that phenomenon is what causes static on your TV every time someone turns on another appliance. But EMI can have some far more serious consequences. For instance, the EMI generated by an electrostatic discharge ("shocks" caused by static electricity) can severely affect nearby computers. In dry weather, it is not uncommon for those mild shocks to cause a computer located on the other side of a fair sized room to "crash." The effects of EMI can even cause an otherwise sound device or circuit to fail to operate at all. And the effects of EMI can be dangerous, such as when the starting of a motor inadvertently triggers a nearby remotely controlled piece of industrial equipment.

The above mentioned effects of EMI, as well as many, many others are familiar to hobbyists, engineers, and users of electronic equipment. Sometimes EMI-caused problems have simple solutions. Such solutions might involve rerouting

some wires or adding a bypass capacitor to a circuit. Other times, a less-than-severe problem is simply tolerated. More troublesome cases are cured only after extensive trial-and-error attempts and a lot of wasted time.

This article is an introduction to a few of the most common causes of EMI and some of the remedies that can be used to combat EMI's effects. Our goal is to achieve "electromagnetic compatibility" (EMC). Electronic circuits and systems are said to have achieved EMC when they can operate within the same electrical and physical environment without any one circuit or system causing problems for another.

### Types of EMI

EMI can be loosely defined as an undesirable signal that affects the normal operation of equipment such that the equipment malfunctions, or the performance of the equipment is degraded in some manner. The phenomenon, its causes, and its cure have all become es-

pecially important as new technologies that use low voltage levels and high-density packaging have been developed. Such technologies are especially sensitive to EMI.

Just as electrical energy is moved from one place to another either by conduction (through wires) or radiation (through the atmosphere or space), EMI "reaches" its "victim" via radiation and/or conduction. For instance, consider the case of static on a television caused by someone using an electric hair dryer. If you look at the dryer motor while the dryer is in use, you can see electricity arcing between the motor's commutator and brushes. Those arcs are a source of both conducted and radiated broadband electric noise that can affect the normal operation of a TV set. By *broadband* we mean that the noise signal contains a wide variety of frequencies, including in most cases those that fall in the TV band (54-216 MHz VHF, 470-890 MHz UHF).

Figure 1 shows a situation that is found in millions of households—an electric

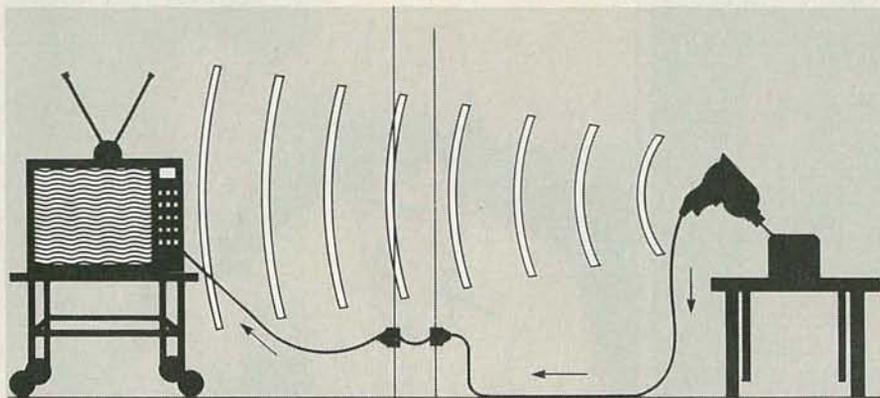


FIG. 1—A COMMON INTERFERENCE SITUATION. The electric drill generates EMI, which is coupled to the TV set via two separate paths.

drill in use in one room affecting the operation of a TV set in another. Note that though the drill and the TV set are physically separated, they are both fed from the same branch of the house's wiring. The signal generated by the arcing within the drill motor is conducted to the TV set via the line cords of the two devices and the house wiring. Once the signal reaches the TV set, it can be coupled into the set's circuitry (more on that in a moment) and processed as if it were a video signal. The result is displayed on the screen as static.

At the same time, the noise signal traveling through the line cord of the drill causes an electromagnetic field to form around that cord; that is, the line cord becomes a "transmitting antenna." The noise signal that is "broadcast" from that

antenna can then be picked up by the TV antenna and processed like any other signal.

Table 1 lists some typical sources of EMI, both man-made and natural. That list is not intended to be exhaustive, but only to give you an idea of the variety of those sources. Table 2 is a brief list of the types of equipment that are subject to electromagnetic interference.

Also, it is possible that the source and victim of the interference is the same piece of equipment. That "self-jamming" occurs when there are several different systems within the same piece of equipment and one of those systems is interfering with another.

### Coupling paths

We've already seen that for EMI to occur there must be a path between the source and the victim. That path is called a coupling path. Usually, the task of locating the coupling path or paths responsible for the transmission of the EMI is the most difficult aspect of solving the problem. That is the case, because there may be a number of paths contributing to the problem. Often, the EMI may persist even though you have eliminated one or more paths. The only solution in those cases is to keep searching until all coupling paths are found.

A further complication that multiple coupling paths presents is that it makes it difficult to determine if eliminating a suspected path has actually done any good. If two or more paths contribute equally to the problem, eliminating only one path may provide little apparent improvement.

In order to discuss the various ways in which EMI can couple from one system to another, it is necessary to define a few terms.

When dealing with conducted interference, there are two varieties that we are concerned with. The first variety is *differential-mode interference*. That is an in-

terference signal that appears between the input terminals of a circuit. The other variety of conducted interference is called *common-mode interference*. A common-mode interference signal appears between each input terminal and a third point; that third point is called the *common-mode reference*. That reference may be the equipment chassis, an earth ground, or some other point.

Let's look at those types of interference a little more closely. In Fig. 2-a we show a simple circuit consisting of a signal source,  $V_S$ , and a load,  $R_L$ . In Fig. 2-b we show what happens when differential-mode interference is introduced into the circuit by an outside source (more on that in a moment). As is shown, an interference voltage,  $V_D$ , appears between the two input terminals, an interference current,  $I_D$ , flows in the circuit. The result is noise at the load. If, for instance, the load is a logic gate in a computer, and the amplitude of  $V_D$  is sufficiently high, it is possible for the gate to incorrectly change states. It is possible that such an occurrence would alter the results of any com-

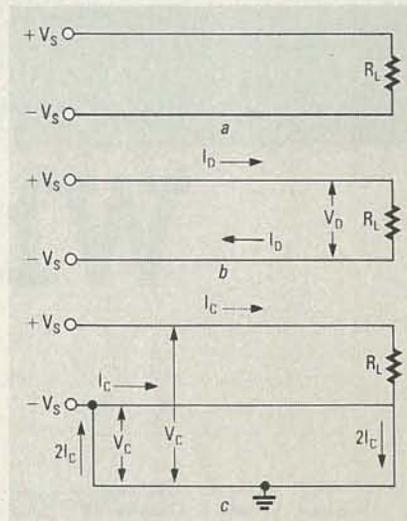


FIG. 2—TWO TYPES OF INTERFERENCE. In differential-mode interference (b) the noise voltage appears between the inputs of the circuit. In common mode interference (c) the noise voltage appears between each input and a third point called the common-mode reference.

putations being performed at the time—a rather undesirable situation.

Figure 2-c shows what happens when a *ground loop* is added to our circuit. Ground loops, which are undesirable current paths through a grounded body (such as a chassis), are usually caused by poor design or by the failure of a component. In the presence of an interference source, common-mode currents,  $I_C$ , and a common-mode voltage,  $V_C$  can appear, with the ground loop acting as the common-mode reference. The common-mode cur-

TABLE 1—SOURCES OF ELECTROMAGNETIC INTERFERENCE

#### Man-Made Sources



- RF transmitters
- Automotive Ignitions
- Electric motors
- Arc welders
- Computers
- Fluorescent lights
- Relays
- Neon signs
- High-voltage power lines
- Switches
- Dimmers

#### Natural Sources

- Electrostatic discharge
- Lightning

TABLE 2—VICTIMS OF ELECTROMAGNETIC INTERFERENCE

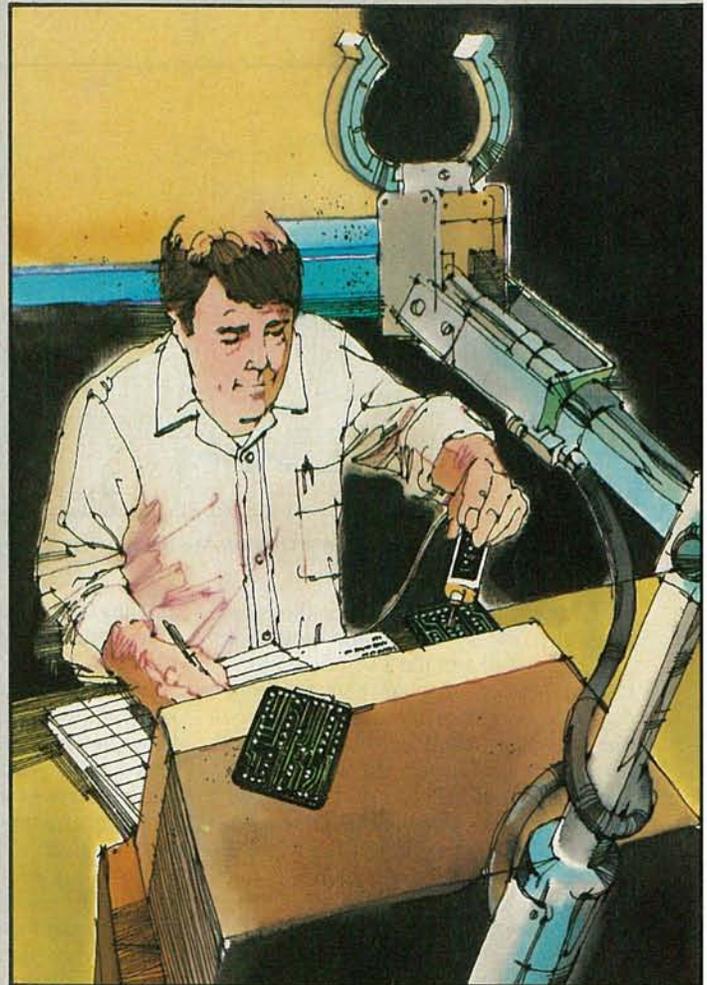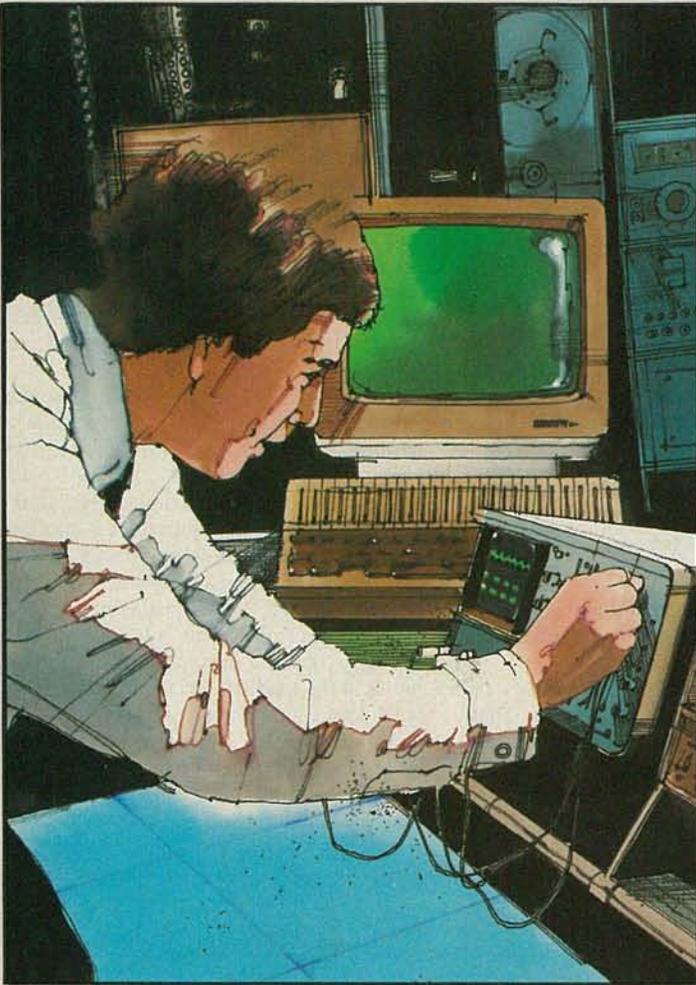- Computers
- Medical equipment
- TV's
- Radios
- Electronic control equipment
- Ordinance (explosives, etc)
- Telephone equipment



# What can you do Just about

## CIE can show you how.

Computer technology. Satellite communications. Cable television. Cellular radio. Digital electronics. Robotics. Just a few of the hottest career areas in electronics. The ones everybody is talking about. The ones that are changing the way we live, the way we do business, the way we entertain ourselves. The best way to start a career in any of them? By learning the basic electronics theory and principles of how they work from CIE.

## Join a leader.



Leading the world in specialized electronics training, CIE is the largest school of its kind with over 25,000 students at home and abroad. And with over 50 years of experience teaching electronics to thousands of men and women through proven

methods of independent study **without** classroom sessions.
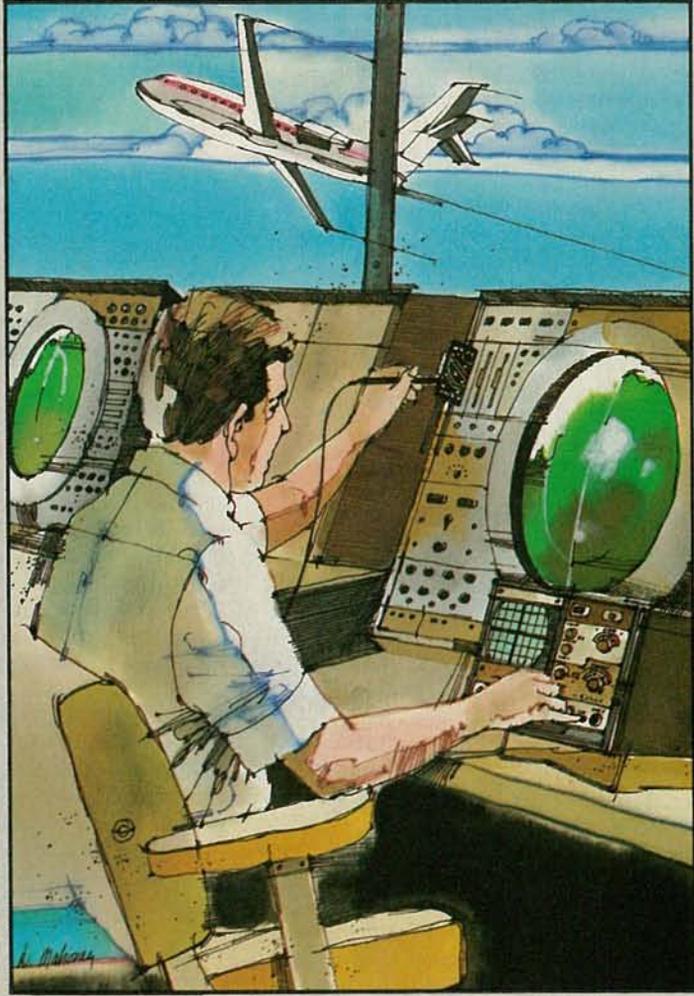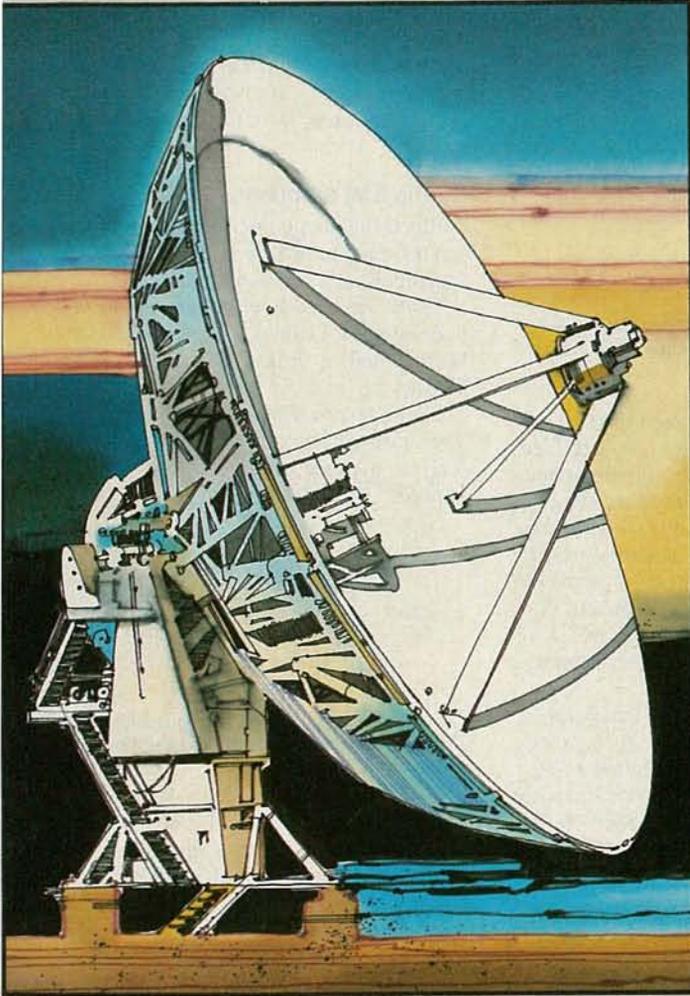
## Learn as much as you want, when you want.

Whether you're interested in learning new skills or upgrading old ones, earning a diploma or an A.A.S. degree, CIE can match your needs with courses and programs that let you start where you want, go as far as you want from a basic beginner course all the way to CIE's Associate in Applied Science Degree in Electronics – a comprehensive program that prepares you for advanced electronics careers.

Custom training  
equipment helps you learn.  
CIE believes in the importance of learning by



# with electronics? anything.

doing. So most of our courses include specialized training laboratories keyed to specific lessons for practical experience through teaching experiments. Our CIE Microprocessor, for example, comes fully assembled and ready to use to teach you how a computer CPU works through a series of experiments you perform on your own.

## Are you ready?

If you're ready to do something now about your future, there's no waiting to enroll with CIE. Get all the information you need to enroll simply by calling us toll-free at **1-800-321-2155** (in Ohio, 1-800-362-2105). Or mail in the handy reply coupon or card to Cleveland Institute of Electronics, 1776 East 17th Street, Cleveland, Ohio 44114.

**CIE** World Headquarters

Cleveland Institute of Electronics, Inc.  
1776 East 17th Street • Cleveland, Ohio 44114

- Please send me your CIE Off-Campus Studies Catalog, including details about the Associate Degree program. I understand there is no cost for the catalog and a CIE representative may call, but there is no obligation.

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. No. \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Age \_\_\_\_\_ Area Code/Phone No. \_\_\_\_\_/\_\_\_\_\_

Check box for G.I. Bill bulletin on Educational Benefits


- Veteran  Active Duty

**MAIL TODAY!**

RE21

rent flows on both input lines, and has the same instantaneous polarity and direction (the current and voltage are in phase), and returns through the common-mode reference. The common-mode voltage between each input and the common-mode reference is identical.

Coupling itself can take place in one of several ways. Some of those include field-to-cable coupling, cable-to-cable coupling,

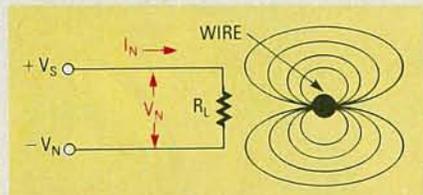


**FIG. 3—FIELD-TO-CABLE COUPLING.** If a circuit is placed within a time-varying electromagnetic field (such as that generated by a current carrying wire), the field will induce a current and voltage in that circuit.

ling, and common-impedance coupling. Let's look at those types of coupling one at a time.

The principle behind field-to-cable coupling is the same as that behind the receiving antenna. That is, when a conductor is placed in a time-varying electromagnetic field, a current is induced in that conductor. That is shown in Fig. 3. In that figure, we see a signal source,  $V_S$ , driving a load,  $R_L$ . Nearby there is a current carrying wire (or other conductor). Surrounding the wire is an electromagnetic field. The presence of the field causes the circuit to act as a loop antenna. As such, an interference current,  $I_N$ , and interference voltage,  $V_N$ , are induced in the circuit. The magnitude of the induced interference signal is roughly proportional to the frequency of the incoming field, the size of the loop, and the total impedance of the loop.

Cable-to-cable coupling occurs when two wires or cables are run close to one another. Because any two conducting bodies have capacitance between them, called stray capacitance, a time-varying signal in one wire can couple via that capacitance into the other wire. That is referred to as capacitive coupling. Another mechanism of cable-to-cable coupling is mutual inductance. Any wire carrying a time-varying current will develop a magnetic field around it. If a second conductor is placed near enough to that wire, that magnetic field will induce a similar current in the second conductor. That type of coupling is called inductive coupling. In cable-to-cable coupling, either or both of those mechanisms may be responsible for the existence of an interference condition.


Figure 4 shows how cable-to-cable coupling works. Figure 4-a shows two lengths of cable (or other conductors) that are running side-by-side. Though there is no

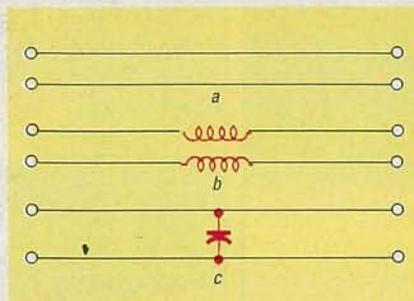

**FIG. 4—CABLE-TO-CABLE COUPLING** can occur via either inductive coupling (b) or capacitive coupling (c).

physical connection between the two cables, the properties we have just described make it possible for the signal on one cable to be coupled to the other. Mutual inductance, as shown in Fig. 4-b, makes the cables behave as if a poorly wound transformer were connected between them; stray capacitance, as shown in Fig. 4-c makes the two cables behave as if there were a coupling capacitor between them.

Either or both of the above-mentioned properties cause the cables to be electromagnetically coupled such that a time-varying signal present on one will cause a portion of that signal to appear on the other. The "efficiency" of the coupling

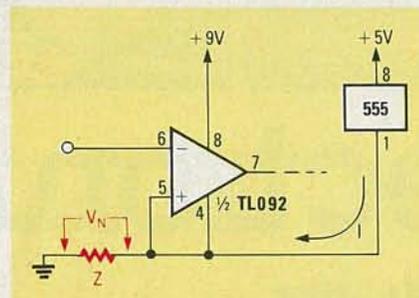

**FIG. 5—BECAUSE THE GROUND** return does not have an impedance of zero, the current from pin 1 of the 555 will cause a noise voltage to be generated. That voltage will appear in series with the input to the op-amp.

increases with frequency and inversely with the distance between the two cables. One example of cable-to-cable coupling is telephone "crosstalk," in which several phone conversations can be overheard at once. The term crosstalk is now commonly used to describe all types of cable-to-cable coupling. Sometimes it is also used to describe any type of induced interference, though such use is incorrect.

Common-mode impedance coupling occurs when two circuits share a common bus or wire. In Fig. 5 we show a circuit that is susceptible to that type of coupling. In that figure a TL092 op-amp and a 555 timer share a common return or ground. Since any conductor (including a PC-board trace) is not ideal, that ground will have a non-zero impedance,  $Z$ . Because of that, the current  $I$  from pin 1 of the 555


will cause a noise voltage,  $V_N$ , to develop; that voltage is equal to  $I \times Z$ . That noise voltage will appear in series with the input to the op-amp. If that voltage is of sufficient amplitude, a noise condition will result.

### Curing EMI problems

Electromagnetic interference problems can be cured in three ways: through filtering, shielding, and isolation.

Filters are used to eliminate conducted interference on cables and wires, and can be installed at either the source or the victim.

Figure 6 shows an AC power-line filter. The values of the components are not critical; as a guide, the capacitors can be between .01 and .001  $\mu\text{F}$ , and the induc-

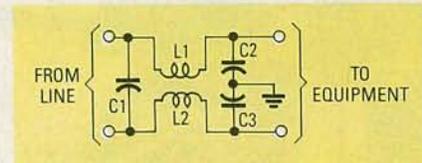

**FIG. 6—THIS AC LINE FILTER** is designed to eliminate both common-mode and differential mode interference currents.


tors are nominally 6.3  $\mu\text{H}$ . Let's see how that filter does its job. Capacitor C1 is designed to shunt any high-frequency differential-mode currents before they can enter the equipment to be protected. Capacitors C2 and C3 are included to shunt any common-mode currents to ground. The inductors, L1 and L2, are called common-mode chokes, and are placed in the circuit to impede any common-mode currents.

Shielding is used to reduce the amount of electromagnetic radiation reaching a sensitive circuit. Shields are made of metal and work on the principle that electromagnetic fields are reflected and/or attenuated by a metal surface. Different types of shielding are needed for different types of fields. Thus, the type of metal used in the shield and the shield's construction must be considered carefully if the shield is to function properly. The ideal shield has no holes or voids, and, in order to accommodate cooling vents, buttons, lamps, and access panels, special meshes and "EMI-hardened" components are needed.

Isolation is often the cure for many EMI problems. In general, high-voltage circuits and devices such as power supplies and motors need to be isolated from low-voltage analog and digital circuits.

To be most effective, the above points should be considered during the design of a circuit. If nothing else, such consideration may help eliminate some difficult troubleshooting. In the next part of this article, we'll look at how you can design electromagnetic compatibility into your projects. **R-E**

# BUILD THIS

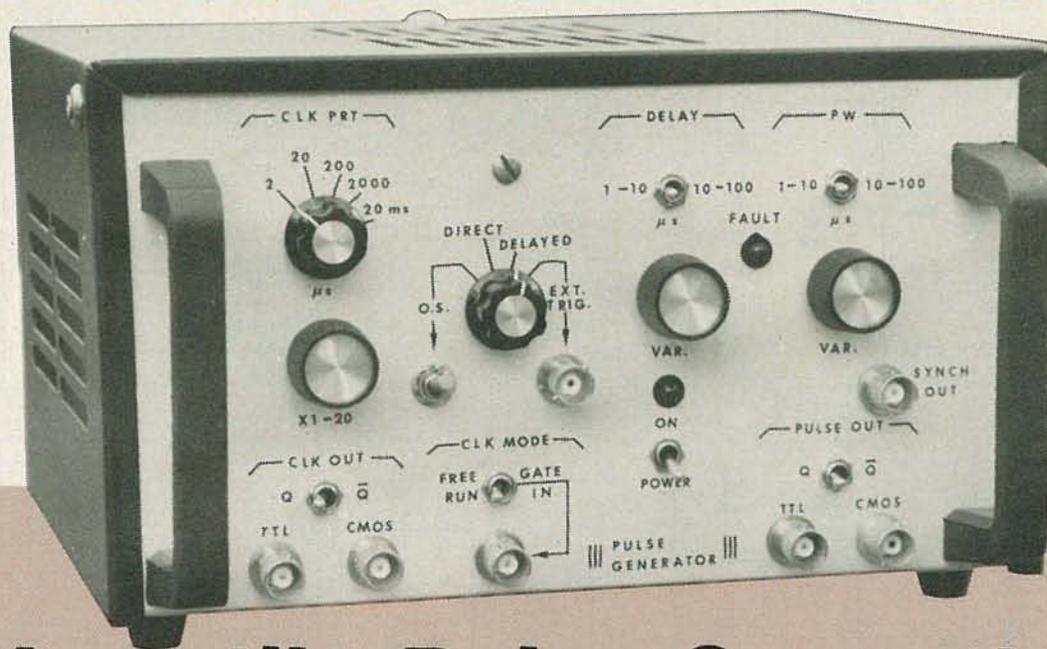

## Versatile Pulse Generator

*This full-featured pulse generator is so easy to build that you have no excuse for not adding it to your workbench!*

JOSEPH GIANELLI

PULSE GENERATORS ARE NOTORIOUSLY absent from many hobby-electronics test benches. That's not because hobbyists have no use for them. On the contrary: A pulse generator can be invaluable for testing, troubleshooting and experimenting with digital equipment. Unfortunately, commercial pulse generators are expensive.

We'll show you how to build a pulse generator that's not expensive; it should cost under \$80 if you use all new parts. If you have some of the parts on hand, especially the switches and cabinet, you'll be able to build it for much less. The generator features a free-running, square-wave clock output that may be gated, and it also features a pulse output that may be derived directly from the clock circuit, from an external trigger, or from an internal delay generator. In addition, there is a one-shot output that delivers one pulse of the selected width for each depression of a front-panel switch. The polarity of all outputs is selectable by the user.

One special feature of our generator is the inclusion of a fault-detection circuit that lights a front-panel indicator whenever the delay or pulse width is greater than the selected clock rate; output will also be disabled. Reducing either the pulse width or the delay time will ex-

tinguish the indicator and restore output.

Our generator is built entirely from CMOS circuits, so power requirements are extremely modest. In fact, battery operation is entirely feasible. A nine-volt alkaline battery should provide about 150 hours of operation. Complete specifications for the pulse generator are given in Table 1.

### Circuit description

Referring to Fig. 1, IC1 is a multivibrator used in the astable mode. Its oscillating frequency is determined by resistors R1 and R2, and one of capacitors C1-C5, as selected by the CLOCK RATE or CLK PRT (Pulse Repetition Time) switch S3. With CLK MODE switch S1 in the FREE RUN position, output will appear continuously at jacks J4 and J5; however, with S1 in the GATED position, output will be inhibited whenever pin 5 of IC1 is brought low. To restore output, a gate signal with a voltage exceeding  $\frac{1}{2} V_{CC}$  should be applied; for the present circuit, a seven-volt gate signal will suffice.

Sync-generator IC5-a, half of a 4098 dual monostable multivibrator, is also triggered by IC1's Q output. When S2 is in the DIRECT position, the sync-generator's output is fed directly to pulse-width generator IC3-b. The width of the pulse gen-

erated by IC3-b is determined by resistors R5 and R6 in combination with C10 or C11, as selected by the PW switch S6. The width of the pulse may vary from approximately  $1 \mu\text{S}$  to  $100 \mu\text{S}$ . Note that IC1 determines the repetition rate of the pulse generator; IC3-b determines the width of those pulses.

When S2 is in the DELAYED position, the sync generator drives IC5-b, the delay generator, which in turn drives IC3-b. The delay generator uses the same resistor and capacitor values as the pulse generator, so the delay may also vary from approximately  $1 \mu\text{S}$  to  $100 \mu\text{S}$ .

When S2 is in the EXT. TRIGGER position, the clock and delay generators are disconnected from the pulse generator circuit. In that mode, a pulse of the selected width is generated on the leading edge of each pulse applied to J6, TRIGGER INPUT. As with the clock-gating signal, the trigger pulse should have an amplitude exceeding  $\frac{1}{2} V_{CC}$ , again seven volts. The sync generator is driven by clock generator IC1, so the sync pulses appearing at J1 will not be synchronized to the external trigger.

When S2 is in the ONE-SHOT position, the clock and delay generators are again disconnected from the pulse-generator circuit. In that mode, a pulse of the se-

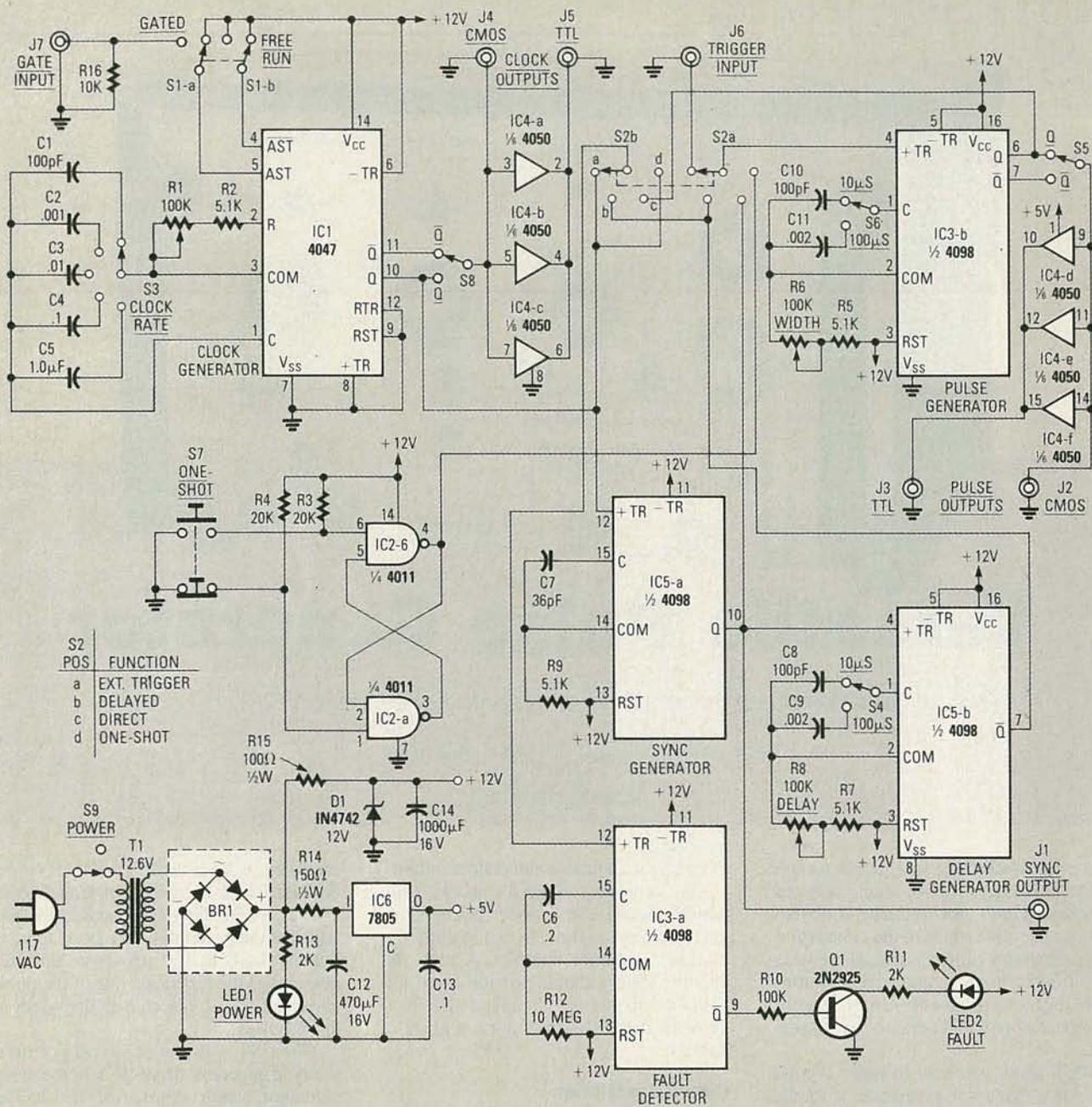


FIG. 1—SCHEMATIC DIAGRAM of the pulse generator. All CMOS components are used, making this a very-low-power device.

lected width is generated each time ONE-SHOT switch, S7, is depressed. Sync pulses are not synchronized to the one-shot output.

The clock output from IC1 and the pulse output from IC3-b are each fed through three 4050 non-inverting buffers wired in parallel. Doing that allows the pulse generator to drive six TTL loads. Separate jacks were used for the CMOS and TTL outputs in lieu of a switch in order to avoid accidentally overdriving TTL IC's with a high voltage. If you don't need to drive TTL circuits, IC4 may be eliminated, as well as the components associated with the five-volt power supply (R14, C12, C13 and IC6). On the other

hand, if you work solely with five-volt circuits (TTL or CMOS), the twelve-volt power supply (R15, D1 and C14) could be eliminated, and the entire circuit powered from the five-volt supply.

Switch S2-b connects FAULT detector IC3-a to the output signal selected by S2-a. IC3-a operates in the re-triggerable mode so that, as long as it is receiving trigger pulses, its  $\bar{Q}$  output will remain low, which will keep Q1, and hence LED2, turned off.

When S2 is in either the EXT. TRIGGER or the ONE-SHOT mode, IC3-a's TRIGGER input is connected to the Q output of the clock generator, IC1, so the fault detector will remain off. When S2 is in the DE-

LAYED mode, the fault detector's input is connected to the output of the delay generator, IC5-b, and when S2 is in the DIRECT mode, the fault detector's input is connected to the output of the pulse generator, IC3-b. In either case, fault detector LED2 will remain off as long as the delay time, or the pulse width, respectively, does not exceed the clock period.

Two NAND gates in IC2 are set up as a latch to debounce switch S7, and provide dependable triggering in the one-shot mode.

### Construction

The pulse generator may be built in any convenient manner, but a printed-circuit

TABLE 1—SPECIFICATIONS

One Shot	1 TO 100 $\mu$ s duration
Pulse Output	1 TO 100 $\mu$ s duration ( $\square$ and $\bar{\square}$ )
Pulse Delay	1 TO 100 $\mu$ s duration
Ext. Trigger	Active on rising edge
Sync. Output	12 volts, 1 $\mu$ s
Clock Output	2 $\mu$ s to 400 ms squarewave ( $\square$ and $\bar{\square}$ )
Gated Clock	variable burst
Outputs	TTL (5 Volt) AND CMOS (12 Volt)
Fault LED	Lights when pulse delay or width greater than pulse repetition rate.

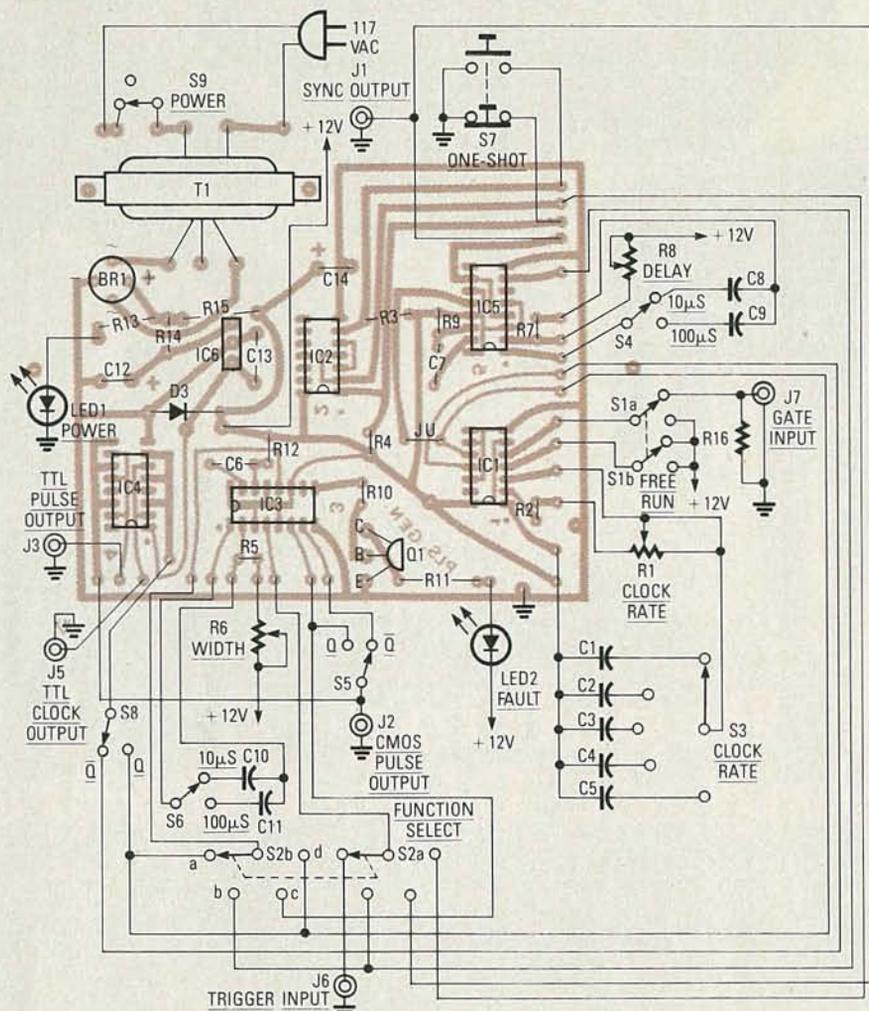


FIG. 2—COMPONENT-PLACEMENT DIAGRAM of the pulse generator. The lines going to +12 volts and ground actually go to a small terminal strip mounted on the front panel. Note that there is one jumper, to avoid using a double sided board.

board simplifies things considerably. Full-size PC artwork is shown in the "PC Service" section of this magazine; alternatively, you may purchase a pre-etched and drilled board; see the Parts List for information.

Whether you buy a PC board or make your own, inspect it carefully before mounting any components. If there are any shorted traces, carefully scrape between them with a sharp hobby knife.

When the board is up to snuff, you can start mounting components using the component-placement guide shown in Fig. 2. Mount components in a pro-

gression starting with those having the lowest profile: First mount the jumper, then add the resistors and diodes, then the IC sockets, and so on. After each group of a certain height has been inserted, turn the board over, making sure that the components remain flush, bend their leads slightly, then solder and clip those leads. After all components have been mounted, check the board carefully for solder bridges between adjacent pads and traces. Fix any problems that you find, but don't insert the IC's in their sockets yet. There's more wiring to do.

Now connect all the front-panel switch-

es, potentiometers and BNC jacks to the PC board, as shown in Fig. 2, with short lengths of insulated wire. Note that timing capacitors C1-C5 and C8-C11 mount directly to their associated switches, not on the PC board. The timing capacitors should be mica, metal polyester, or other high-quality types. Resistor R16 similarly mounts on front panel jack J6.

## PARTS LIST

All resistors 1/4-watt, 5% unless otherwise noted

- R1, R6, R8—100,000 ohms, linear potentiometer
- R2, R5, R7, R9—5100 ohms
- R3, R4—20,000 ohms
- R10—100,000 ohms
- R11, R13—2000 ohms
- R12—10 megohms
- R14—150 ohms, 1/2-watt
- R15—100 ohms, 1/2-watt
- R16—10,000 ohms

### Capacitors

- C1, C8, C10—100 pF, mica
- C2—0.001, metalized polyester
- C3—0.01  $\mu$ F, metalized polyester
- C4, C13—0.1  $\mu$ F, metalized polyester
- C5—1.0  $\mu$ F, metalized polyester
- C6—0.2  $\mu$ F, metalized polyester
- C7—36 pF, mica
- C9, C11—0.002, metalized polyester
- C12—470  $\mu$ F, 16 volts, electrolytic, radial leads
- C14—1000  $\mu$ F, 16 volts, electrolytic, radial leads

### Semiconductors

- IC1—4047 multivibrator
- IC2—4011 quad two-input NAND gate
- IC3, IC5—4098 dual multivibrator
- IC4—4050 noninverting hex buffer and TTL driver
- IC6—7805 5 volt regulator
- Q1—2N2925
- BR1—bridge rectifier 50 volts, 1.5 amps
- D1—IN4742 12V Zener
- LED1, LED2—standard red LED


### Other components

- J1—J7—BNC female connectors
- S1—DPDT, miniature toggle
- S2—2 pole, 4 position miniature rotary
- S3—1 pole, 5 position miniature rotary
- S4—S6, S8—SPDT, miniature toggle
- S7—SPDT, miniature momentary
- S9—SPST, miniature toggle
- T1—Transformer 12.6 volts, 0.12 amps, Radio Shack #273-1360

**Note:** An etched and drilled PC board is available from E<sup>2</sup>VSI, P.O. Box 72100, Roselle, IL 60172 for \$11.95 postpaid.

Check over your wiring, and if everything looks OK, apply 117 volts AC power to the pulse generator, and turn on switch S9. With a voltmeter verify that the power-supply voltages are correct, and that +12 volts appears at pin 14 of IC1, and pin 16 of IC2, IC3 and IC5. Also make sure that +5 volts are present at pin 14 of IC4. If everything checks out, remove power and insert the IC's.

continued on page 113

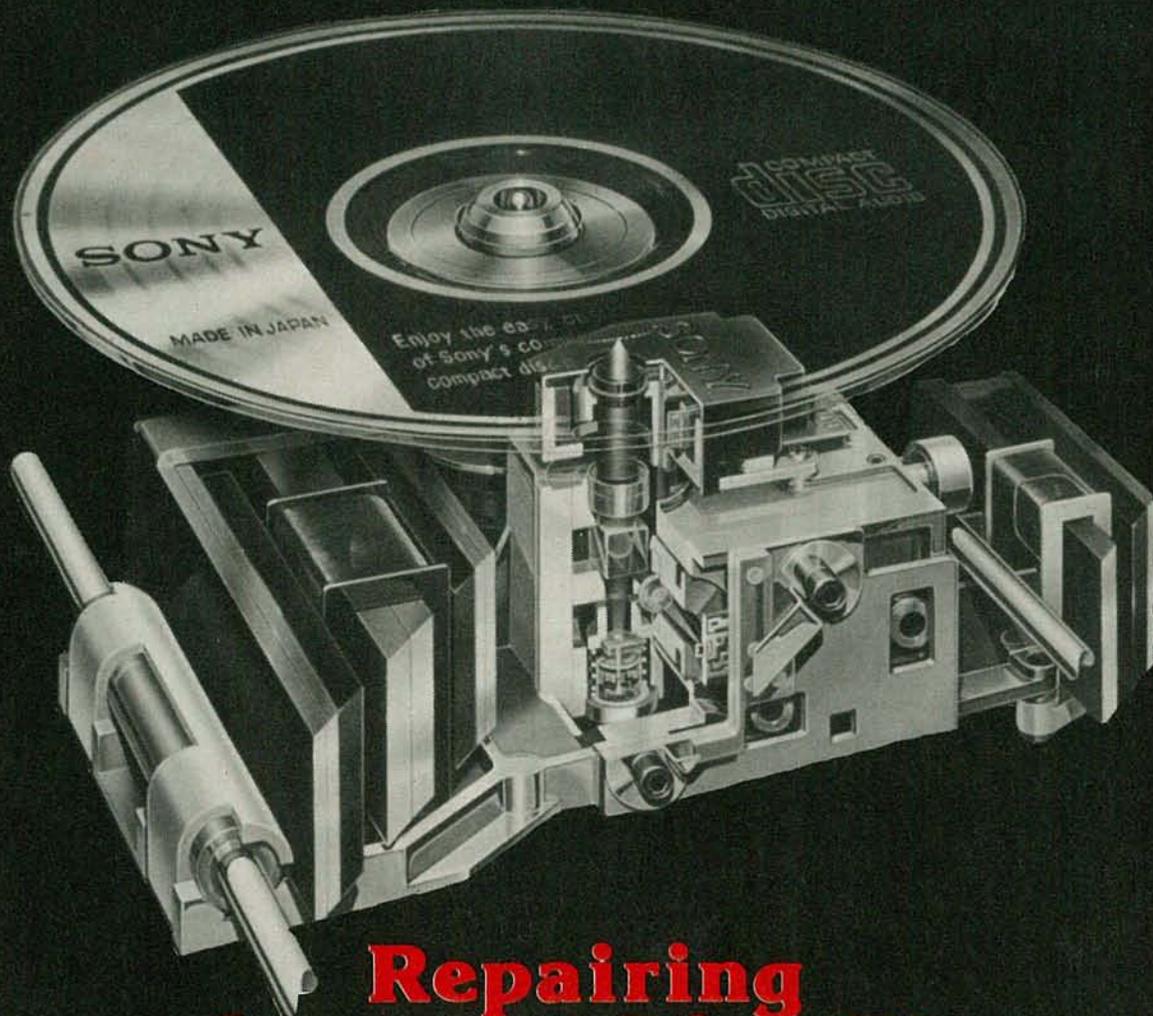

## Repairing Compact Disc Players

*Compact disc players are the most exciting development in audio in years. In this article we'll show you how those devices work, and how you can repair them when something goes wrong.*

JOHN D. LENK

COMPACT DISC (CD) SYSTEMS ARE SIMPLER than VCR's and videodisc players, but they are still complex devices that require topnotch troubleshooting skills if they are to be successfully serviced. But if you have had some experience troubleshooting and repairing video or audio equipment, there's no reason not to try your hand at CD servicing.

Servicing CD players is not difficult, if you follow the procedures outlined in the manuals. Unfortunately, most such manuals assume that you are familiar with how a CD player operates. Because of that, little in the way of theory or background is provided. That is a shortcoming that this article aims to eliminate. By the time we

are done, you will know the basics of CD-player operation, and repair.

### CD player basics.

In this article we will cover CD players designed to reproduce sound from digital compact discs (digital CD's). The compact disc itself is single-sided, 4.75 inches (120 mm) in diameter, and can be used to store about 60 minutes of program information (in stereo). Just as with phonograph records, the program information on a CD may be music, speech, or any other type of audio. But such discs are not to be confused with conventional analog LP records, or with the so-called "digital" LP's. While in the manufactur-

ing of digital LP's PCM (Pulse Code Modulation) is used to record the original performance (PCM is also the recording technique in CD), the signal that is put on the LP record and played back at home is analog. The CD's described here are not interchangeable (electrically or physically) with analog LP records, digital PCM records, or videodiscs (even though the operating principles of videodisc players are quite similar to those of CD players).

Let's see how a CD player works. Figure 1 is a block diagram of a typical CD player. First off, unlike a phonograph record, a CD is "played" from the underside. The pickup used is not the familiar me-

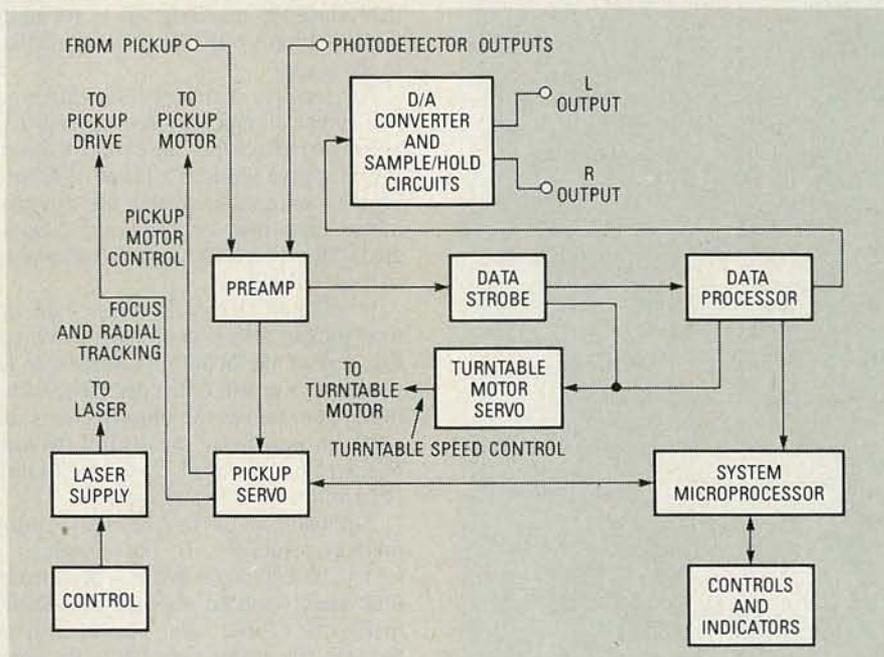


FIG. 1—BLOCK DIAGRAM of a typical CD player. The use of a microprocessor is what makes many convenience features possible.

chanical needle/stylus used in conventional phonographs, but rather an optical system that uses a light beam generated by a laser.

Another important difference is the manner in which information is recorded on a disc. The beginning of a CD "track" is near the center of the disc; as the program plays, the laser beam moves from the center of the disc to its outer edge. Also, rather than a groove, the information is recorded in the form of microscopic pits and flats. Those pits and flats are coded with music or other audio, as well as synchronization and identification information.

The light beam used in the CD optical pickup is focused on the CD surface by an objective lens. As the CD is played, the lens and beam are made to follow the track by a servo-operated pickup motor. The objective lens is part of a pickup assembly. There are two basic types of pickup assemblies, as shown in Fig. 2. In one, the optical system (including the objective lens) is mounted at the end of a rotating arm. The arm and lens are rotated (by the servo drive motor) so that the lens moves from disc center to edge. In the other configuration, the optical system is part of a slide assembly (also called the sled) that is motor driven.

While on the subject of motors, there is also a servo-operated turntable drive motor in all CD players (to spin the disc), and usually a loading motor (or possibly two) to insert and remove the disc from the player.

Although we have already pointed out that the method used in CD's to record

information differs from that used in conventional phonograph records, perhaps we should point out the significance of that difference. Phonograph records store information in a continuous groove cut into the surface of the disc. The storage technique is analog; that is, the amplitude or depth of the groove is a direct representation of the audio signal. A conventional phonograph reproduces the audio signal via a mechanical pickup, called a needle or stylus, that detects the shape of the groove and is in direct physical contact with the surface of the disc.

On the other hand, the audio signals stored on a CD are in a high-density digital format. Further, a CD player's pickup never comes into physical contact with the disc surface. The first point means that the signal recorded on the disc is an extremely accurate representation of the original audio signal. The second point means that the problem of deteriorating sound quality over time, caused by the record wear that is unavoidable with a mechanical pick-up system, is eliminated. Also, mechanical pickup systems themselves introduce noise, such as clicks and pops, during playback; such noise is not generated by the CD playback system.

The laser beam is generated by a small low-power semiconductor diode made of aluminum-gallium-arsenide (AlGaAs). The laser beam is focused on the surface of the disc by the objective lens. That lens focuses the beam into a spot slightly less than  $1 \mu\text{m}$  in diameter. Light is then reflected from the pits and flats back through the lens and optical system into infrared photodiodes. The signal from the

photodiodes is used to reproduce the digitally-recorded information.

The groove on an LP record contains two signals—the stereo sum- and difference-signals—that must be simultaneously read and reproduced by conventional turntable pickup systems. The CD carries left and right channel information separately, but interlaces it on a single track. The nature of the information—that is, whether it is left or right channel, changes at fixed intervals. The player is programmed to keep step with those changes and thus maintains a high degree of isolation between the two audio channels. Realistically, channel separation of better than 90 dB is possible.

Signals are recorded in PCM form. During the recording process, the audio is sampled 44,100 times per second, (over twice the usual 20-kHz audio range). The composition (frequency, level, etc.) of each separate signal sample is then converted into a 16-bit (place) binary number. That process involves quantization. That is, the maximum signal amplitude is divided up into  $2^{16}$  (65,536) gradations. The real level of the audio signal is then rounded to the nearest quantized value.

The use of the 16-bit system and the high sampling rate allows for an extremely accurate digital representation of the original analog signal. In theory, the dynamic range of the 16-bit system is almost 98 dB, although most CD manufacturers claim about a 90- to 95-dB dynamic range.

Figure 3-a shows a track of pits and flats. The length of the pits and flats determines the information contained on the track. The pits and flats can vary in length from about 1 to  $3 \mu\text{m}$ . That variation in length is used to convey the information in the signal. Since the pits reflect less light than the flats, the CD player's optical pickup can differentiate between the two. Figure 3-b shows the analog signal that is recovered from the track shown in Fig. 3-b.

### Optical pickup systems

Figure 4 shows the basic elements of the optical pickup (also called the optical readout) used by most slide-type CD players (the most popular type). The laser beam developed by the laser diode is applied to the reflective surface of the disc through an optical system (a series of lenses, prisms, gratings, and possibly mirrors). The beam is then reflected back through the optics to photodiode detectors (typically 6 diodes). The detector produces an output that corresponds to the audio stored on the disc, as well as tracking and focus signals.

In the system shown in Fig. 4 the disc spins in a horizontal plane. In many CD

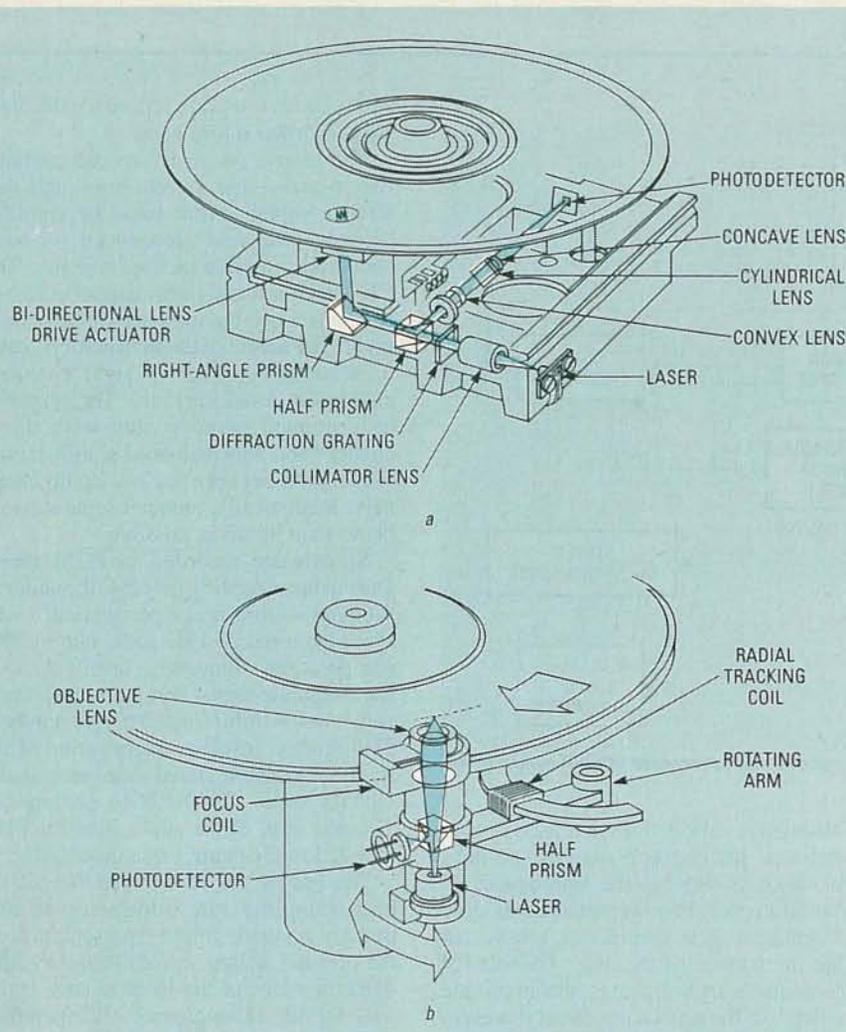


FIG. 2—CD PLAYER PICKUP SYSTEMS. Most CD players use either the slide (or sled) system shown in a or the rotating arm pickup shown in b.

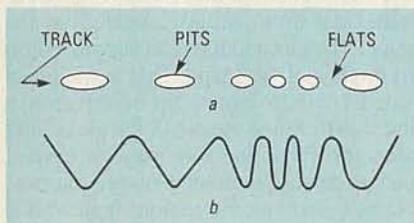


FIG. 3—THE LENGTHS OF the pits and flats (a) are used by the player to recover the original audio signal (b).

players, the disc spins vertically. Either way, it is essential that the laser beam follows the track of pits and flats as the optical pickup is drawn across the disc by the pickup motor, regardless of any possible disc eccentricity. That is called radial tracking, and usually involves a radial-tracking coil operated by a tracking servo to move the lens (and beam) as necessary.

The radial tracking system uses the 3-beam principle shown in Fig. 5. The 3-beam technique uses two sub-beams to detect tracking errors, and the main beam detects the audio signal. The sub-beams are produced by routing the laser beam through a glass diffraction grating, which

creates several images on the same object. The two sub-beams are located ahead of and behind the main beam. After being reflected by the disc, each beam is routed through the optical system to corresponding photodetector diodes. The error signal from the two sub-beams is converted into an electrical signal, and then fed to an error-signal amplifier.

As long as disc tracking is precise, the error-signal amplifier output is zero. However, if even the slightest radial-tracking error is detected, the input differential between the two error signals (right and left) produces an output. That output is fed to the radial-tracking servo and coil; those move the objective lens (at right angles to the track) as necessary to correct the position of the main beam.

In rotating-arm systems, the radial tracking coil moves the entire arm and pickup as necessary to restore proper tracking. In most slide-type systems, the radial tracking coil moves the optical system (lenses, etc.) in relation to the remainder of the pickup assembly to restore tracking. A few players use a third system in which the tracking coil operates a ro-

tary mirror placed between the laser and lens so that the beam is bent 90° when reflected by the mirror. The tracking signals cause the tracking coil to rotate the mirror (slightly) and direct the beam back to the track.

For service, it makes little difference which type of optical system is used since you must replace the entire pickup assembly as a package in the event of failure. Possible exceptions to that are the drive motor, drive belt, or a few gears. Optics are rarely replaceable, or even adjustable, in most CD players.

In addition to radial tracking, the optical pickup also provides for automatic focusing of the beam to compensate for vertical movement of the disc. The focusing system moves the objective lens (toward, or away from, the disc) if the laser beam is not focused precisely (within  $\pm 1\mu\text{m}$ ) on the pits and flats.

Automatic focus (or AF) uses the astigmatism principle. In the simplest of terms, the main laser beam is detected by four equally-spaced photodiodes, shown in Fig. 6. (Those same diodes also reproduce the audio signal.) If the main beam is properly focused, the beam spot is round, and all four diodes receive the same amount of light (and output signals of the same strength). If the beam is not properly focused, the beam spot is elliptical, and the four diodes receive different amounts of light (and produce different outputs). The outputs from the four diodes are summed by an error amplifier; the output of that amplifier is the focus error. That error (if any) is fed to a focus coil or actuator that moves the objective lens as necessary to correct the focus.

## Signal processing

The block diagram of Fig. 1 shows the sequence of signal processing within a typical CD. We will discuss each of those circuits later in this series. For now, let's quickly run through the sequence.

The photodiode output is very low, so it is first fed to a pre-amp where it is amplified. From there it is fed to a data strobe circuit that is used to differentiate between the logic-highs and logic-lows in the signal. The data strobe also extracts and separates the sync signals from the music and other audio. (Those sync signals are encoded along with the music at the time of disc manufacture; they make it possible for the CD player to reproduce audio at selected points on the disc track.)

The next stage is the data processor. That stage has many functions, including demodulation of the signal data, error detection and correction, and overall control of the signal processing circuit.

All CD player circuits include some provision for interleaving of signal data. When a CD is recorded, the music or other audio is interleaved before recording on the disc to provide error correction.

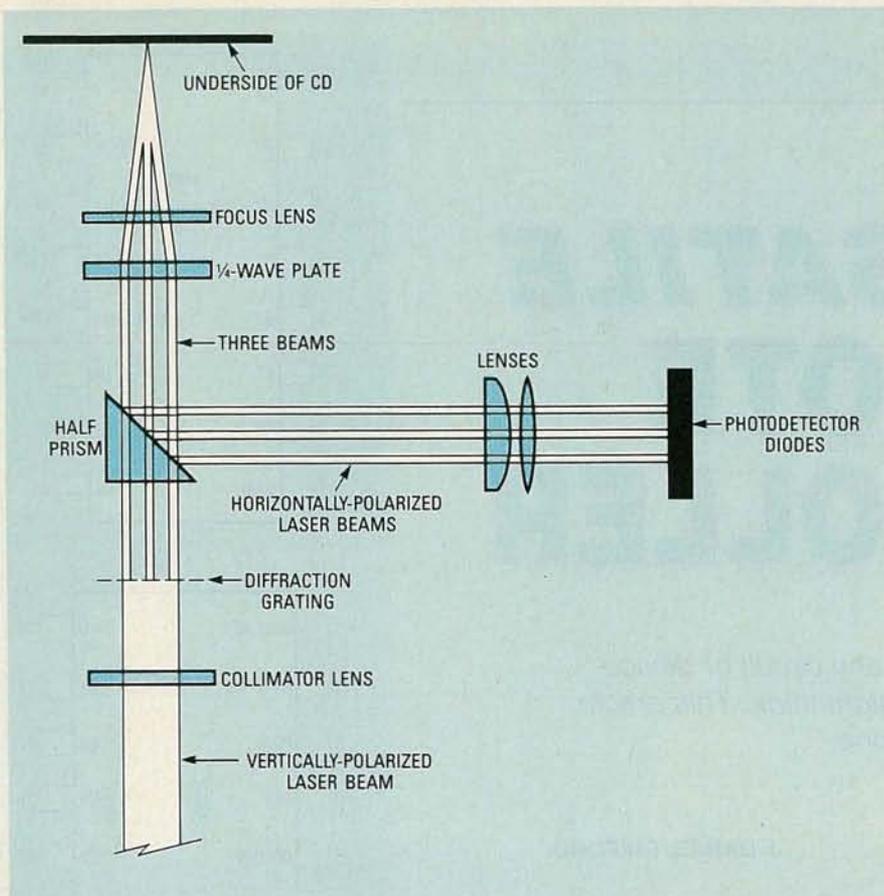


FIG. 4—BASIC ELEMENTS of a CD optical pickup system. In the system shown here the disc spins in a horizontal plane.

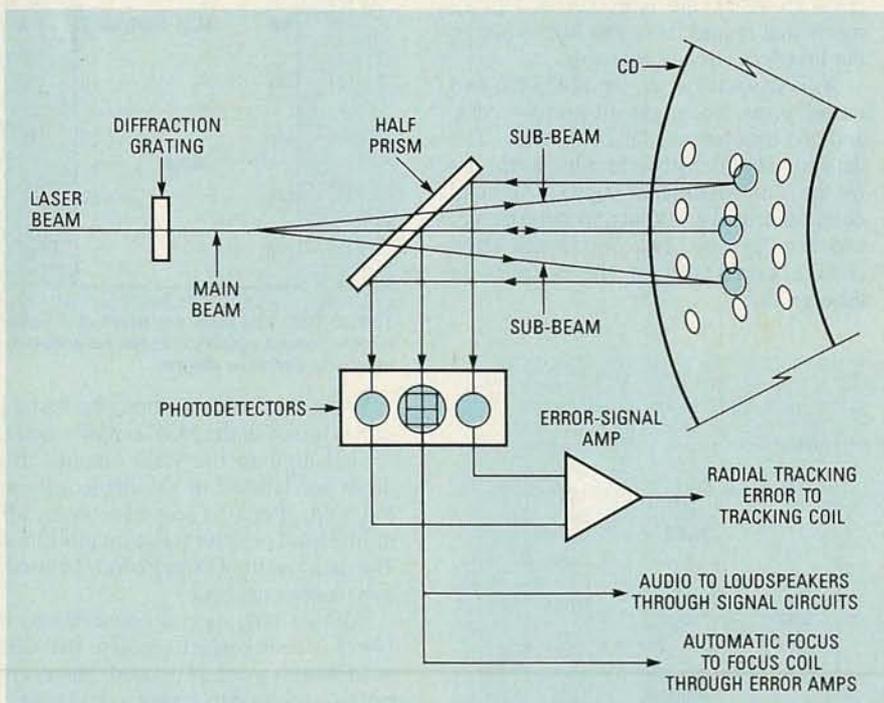


FIG. 5—A DIFFRACTION GRATING splits two sub-beams from the main laser beam. The sub-beams are used to make sure that the player is tracking properly.

The error correction method is called CIRC or Cross Interleaved Reed-Solomon Code, and involves both parity bits and

interleaving. We will not go into CIRC here since that topic is beyond the scope of this article. But you must have some

knowledge of interleaving to understand how a CD player works.

In the most basic of terms, interleaving involves dividing the audio to be recorded into a series of random sections, and then lining the sections in a new, fixed, order before recording. During playback, the

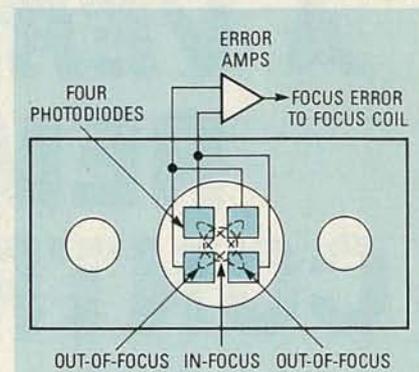


FIG. 6—FOUR PHOTODIODES are used to make sure that the beam is correctly focused.

sections are rearranged by the opposite process to recreate the original music or other signal. The playback arrangement processing is done by temporarily storing the data in RAM and then retrieving the data in the original order.

With interleaving, the effects of dropouts in the audio (from any cause) are greatly minimized. That is true if even a relatively large part of the signal is lost. That's because such a loss is distributed over various smaller gaps in the recreated, final, audio signal. It is a relatively simple task for the digital signal-processing circuitry to "fill in" a small section of missing information when the data on either side of the gap is present.

The D/A converter follows the signal-processing circuits. The D/A converter transforms the digital signal back into an analog signal. The converted analog signal is then restored to pure two-channel audio by a sample-and-hold (S/H) circuit, and applied to the left and right stereo outputs.

Before we move on, let's look a little more closely at the D/A converter. Earlier we mentioned that the original audio is converted to 16-bit digital form for recording on a CD. Such discs, however, can be played back with almost no loss in dynamic range on players that use 14-bit D/A converters. The advantage of the use of such a converter, as opposed to a 16-bit converter, is cost. Thus you will find that many consumer CD players make use of 14-bit D/A converters.

Before one attempts to repair a CD player, it would be helpful to know how that player is supposed to operate in the first place. In the next part of this article we'll see how the various features and functions found on a typical CD player normally operate.

R-E

## A VERSATILE REMOTE CONTROLLER

*Adding remote control to any circuit or device is not as hard as you might think. This article shows you how its done.*

J. DANIEL GIFFORD

**Part 2** LAST TIME WE BEGAN to look at the receiver half of our remote-control system. Let's continue that discussion now.

The output from either the ultrasonic or infrared pickup must be amplified before being input to the 14458. One suitable amplifier design is shown in Fig. 10. That circuit takes the signal from either type of pickup, amplifies and conditions it, and clips its amplitude between 0 and 5 volts, producing at its output an exact duplicate of the signal applied to the transmitting LED's or transducer. Other amplifier de-

signs could be used, as long as they have a high-impedance input and extremely high gain. However, the amplifier in Fig. 10 meets that requirement and uses some of the inverters already available.

As discussed earlier, the 14458 has two output ports, one eight-bit port for data, and one four-bit port for commands. The data port is actually two four-bit ports, one for the *Most Significant Digit* (MSD) and composed of the outputs M1 through M8, and one for the *Least Significant Digit* (LSD), composed of the outputs L1 through L8.


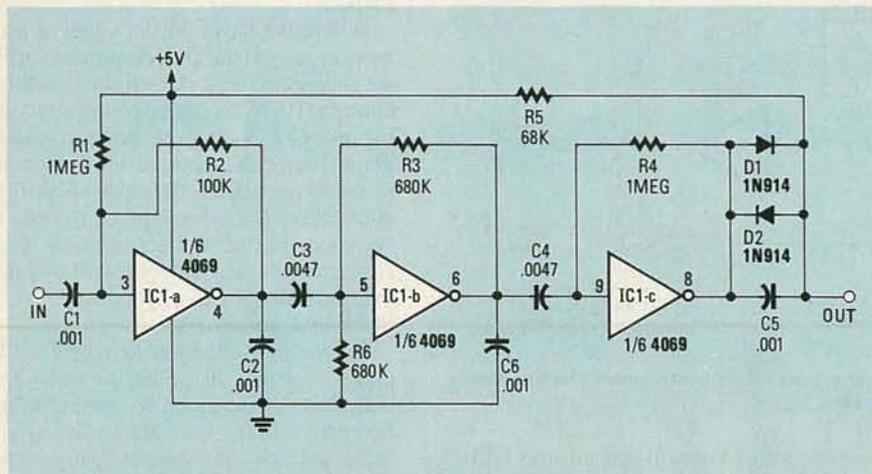
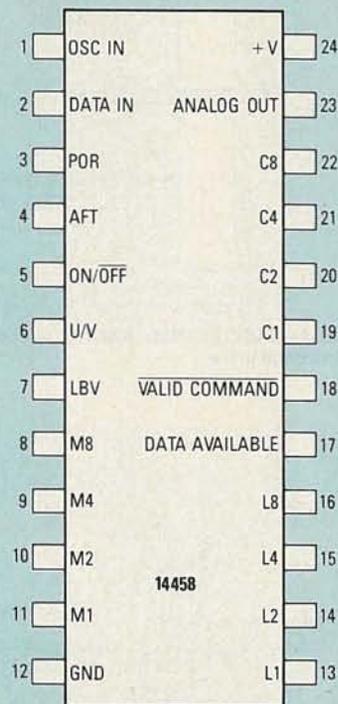


FIG. 10—THIS INPUT AMPLIFIER is ideal for use with the receiver. It can accept the output from either the infrared or ultrasonic pickup.

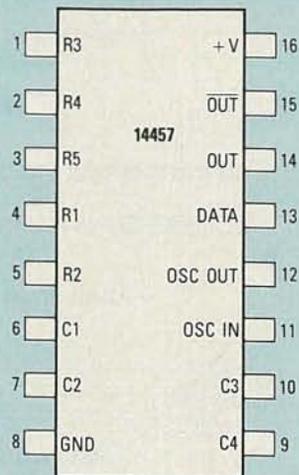

THESE TWO IC's form the heart of a versatile remote control system that can be added to almost any circuit or device.

When data is transmitted, the first digit sent is routed to the MSD outputs, and the second digit to the LSD outputs. Both digits are latched in simultaneously and followed, after a 0.1 second delay, by a 0.8 millisecond positive pulse on pin 17 (DA). The data and the DA pulse may be used in any manner necessary.

Without any special connections, the 14458 is configured to receive two digits as a full data word. If desired, the receiver can be converted to accept a single digit as a full data word by connecting pin 9 (M4) to +V and pin 6 (u/v) to ground. In single-digit mode, the first data digit transmitted will be latched into the LSD outputs and followed by the DA pulse.

The command transmission situation is

### Ordering Information

The following are available from Circuit Specialists, PO Box 3047, Scottsdale, AZ 85257: 14457/14458 transmitter/receiver pair, \$17.00 postpaid; 455-kHz ceramic resonator (Mallory CU455), \$8.50 each, postpaid.

Also, the following are available from Dick Smith Electronics, PO Box 8021, Redwood City, CA 94063; telephone number 800-332-5373: Photodiode (catalog number Z-1950), \$.60 plus shipping and handling; a matched pair (receive/transmit) of ultrasonic transducers (catalog numbers L-7050 and L-7052), \$2.95 each plus shipping and handling. Note that this supplier requires a \$10.00 minimum order.

somewhat more involved. If the function bit in the data stream is a 1, the four-bit code is identified as a command, and is routed to the command port. Once the digit is latched into the port, there is a 0.1-second delay and then a negative 0.8-millisecond pulse appears on the  $\overline{VC}$  output, pin 18. All 16 commands and the  $\overline{VC}$  pulse may be used as necessary; however, four of the commands are also internally decoded by the 14458 to control two specialized outputs.

When the key corresponding to command 09 or OFF is pressed, pin 5 on the 14458, ON/OFF, is driven low. That pin is also set low when the IC is powered up, and is driven high when any data word is transmitted. If the 14458's power supply remains uninterrupted, that pin can be used to turn the controlled device on and off. When the ON/OFF pin goes low or off, the rest of the 14458 goes into a standby mode, with commands being ignored until a data word is transmitted.

The other three commands decoded by the 14458 all control one output, pin 23,

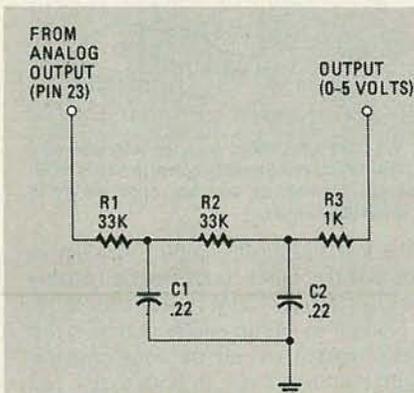


FIG. 11—THE LOW-PASS FILTER used to obtain a smooth DC signal from the ANALOG OUT output. An active filter and/or voltage follower can also be used.

ANALOG OUT. That output provides a variable voltage between 0 and 5, with a total of 64 steps between the two extremes. When the 14458 is powered up, the voltage is at 0. When the ANALOG UP KEY (command 07) is pressed, the voltage at the ANALOG OUT pin begins to step upwards at a rate of 10 steps per second, until the key is released or until the maximum of 5 volts is reached. The ANALOG DOWN key (command 06) operates in the opposite manner, stepping the voltage at the ANALOG OUT pin down at a rate of 10 steps/second until either the key is released or 0 volts is reached.

The MUTE key (command 08) when pressed once forces the ANALOG OUT voltage to 0, and when pressed again, returns it to its previous level. The ANALOG UP key will also return the voltage to its previous level and, if held down, continue to increase it.

The ANALOG OUT signal is pulse-width-modulated, and must be passed through a low-pass filter (Fig. 11) in order to obtain a smooth DC signal. If more than a few milliamps of output current are needed, an op-amp voltage follower should be added. The ANALOG OUT signal is intended to control a TV's volume, but can be used for any purpose.

There are two basic types of commands, toggle and continuous. The only difference between the two is that with the toggle type, the command is only sent once (with one  $\overline{VC}$  pulse) no matter how long the key is held down, while with the continuous type, the command is retransmitted (each time with a  $\overline{VC}$  pulse) every 0.1 seconds as long as the key is depressed. OFF and MUTE are examples of toggle-type commands; ANALOG UP and ANALOG DOWN are continuous types. There are twelve uncommitted commands, two of which are toggle-type and ten of which are continuous.

The 14458 also has three specialized outputs intended for TV control that are probably of little use otherwise. All three are controlled by the data sent to the data port.

Pins 6 (U/V) and 7 (LBV) are used to switch between tuners and bands in a TV set. When the data at the data port is between 14 and 83, the U/V pin will be high; it is low otherwise. If the data is between 02 and 06, the LBV will be low; it is high otherwise. When the data is between 7 and 13, both pins will be low.

The third specialized TV output is different in that it may have other uses. Pin 4 (AFT) is used to disable a TV's automatic fine tuning circuit briefly each time the channel is changed. Each time new data is entered into the data port, that output will

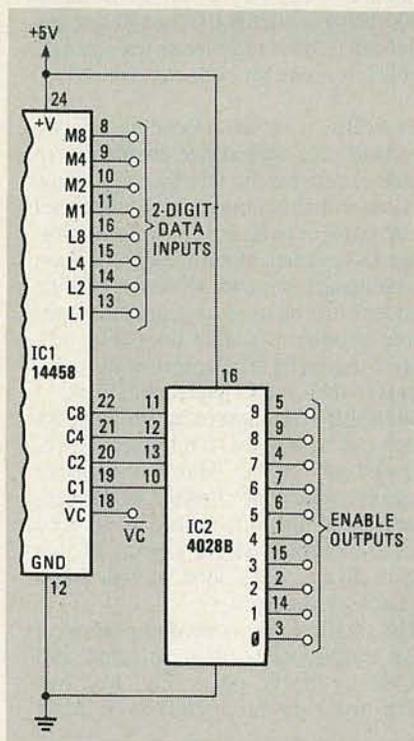


FIG. 12—THE OUTPUTS and decoding scheme for the receiver used in the 20- and 26-key systems. Each enable output is used to activate one output device.

drop low for 0.4 seconds. That could be used as an alternate to the DA pulse, or as a countering or resetting signal to it. The only problem is that four other commands (00, TOGGLE 1; 01, TOGGLE 2; 02, CONT 1; 03, CONT 2) also cause that pin to drop low, which could interfere with such reset functions.

### Decoding and interfacing

The most difficult part of using a remote-control system built with the 14457 and 14458 is interfacing the receiver to the system under control. Since the idea here is not to tell you how to build a specific sort of remote-controlled device, we will not discuss specific sorts of interfacing. Instead, let's look at a universal system that can be used to decode the 14458's commands to control functions remotely. It is up to you to provide the final link between these decoders and the device you want to control.

If the 10-key transmitter is used, no decoding is needed as none of the commands are accessible. The only step necessary would be to interface the data port (either one or two digits) to the security system or other device. Note that although no direct OFF control is possible with that configuration, the OFF output can be driven high by transmitting any data word. The OFF output (and the 14458) could be

reset by the controlled device by pulsing the POR input low.

With the 20- or 26- key transmitter, ten commands are available and must be decoded by external circuitry. Since the command codes fit the ten BCD digits (0000-1001), a 4028B BCD-to-10 line decoder can be used to generate ten separate enable lines, one for each command (Fig. 12).

Basically, what that decoding scheme does is use the appropriate enable line to enable or activate the interface circuit associated with the command, and then uses the  $\overline{VC}$  pulse or pulses to clock the circuit. If the 32-key transmitter is used, there are 16 commands, so a 4514B hex-to-16 line decoder must be used to generate the required number of enable lines (Fig. 13). Table 2 shows the relationship of the commands to their respective enable lines.

With that basic approach, an interface circuit can be devised to interface the enable and  $\overline{VC}$  lines to control the proper function on the controlled device. If necessary, more than one enable line can be used to control different aspects of one output device. Let's look at four basic interface circuit types.

The simplest type is used to generate a pulse output when it is selected and clocked by the  $\overline{VC}$  pulse (Fig. 14). Two 4001B NOR gates are used, one to invert

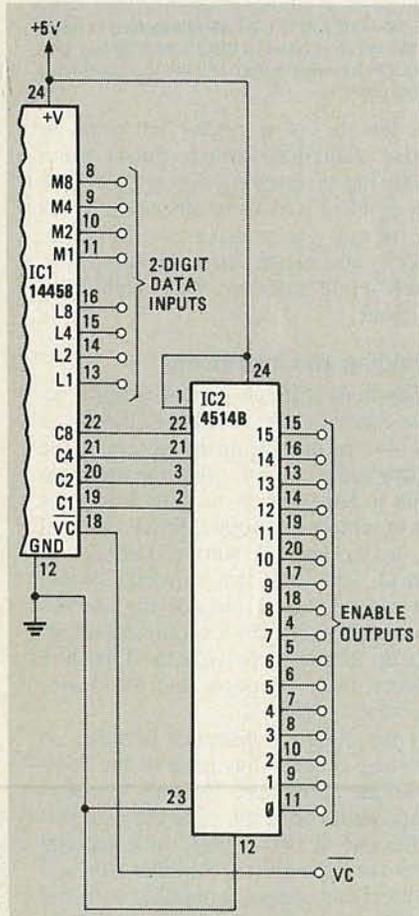


FIG. 13—THE OUTPUTS and decoding scheme for the 32 key system.

TABLE 2—ENABLE DECODER OUTPUTS

Output	Command
00	TOGGLE 1
01	TOGGLE 2
02	CONT 1
03	CONT 2
04	CONT 3
05	CONT 4
06	ANALOG DOWN*
07	ANALOG UP*
08	MUTE*
09	OFF*
10	CONT 5
11	CONT 6
12	CONT 7
13	CONT 8
14	CONT 9
15	CONT 10

\*also internally decoded by the 4458

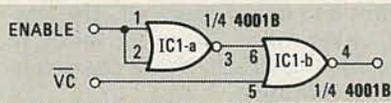


FIG. 14—THIS INTERFACE CIRCUIT outputs a pulse that can be used to control a device.

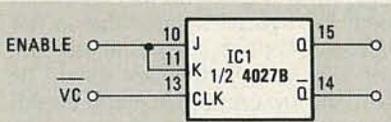


FIG. 15—THE ONE-BUTTON alternate-action interface circuit.

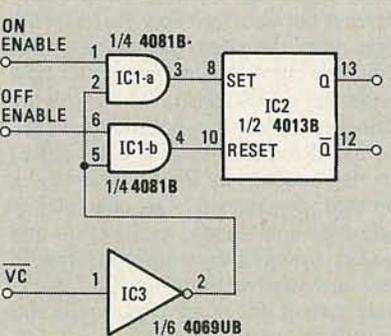


FIG. 16—THE TWO-BUTTON alternate-action interface circuit. Either a 4013B or 4027B type flip-flop may be used.

the enable line signal, and the other to act as a gate that will pass the  $\overline{VC}$  pulse (in inverted form) when the correct enable line is high. The pulse will be an exact mirror of the  $\overline{VC}$  pulse, 0.8 milliseconds wide, and positive in polarity. A third or gate could be added to re-invert the pulse's polarity, and if a longer pulse width is desired, a 4528B monostable or 555 timer can be added to the output.

The basic on-off type of control is a one-button alternate-action decoder (Fig. 15). A 4027B JK flip-flop has its J and K inputs tied together and to the correct enable line, and its CLK input tied to the  $\overline{VC}$

pin. If the enable line is low, a pulse on the  $\overline{VC}$  pin will have no effect on its outputs. If the enable line is high, the pulse will cause the outputs to change states. That type of output device should be used with a toggle-type command to keep it from changing states more than once per key press.

A more positive such control is a two-button alternate-action decoder (Fig. 16). Either a 4013B or a 4027B flip-flop may be used in that circuit, since only the SET and RESET inputs of either are used. One enable line is used, via a 4081B AND gate, to allow the  $\overline{VC}$  pulse to reach the SET input and drive the Q output high (and the Q output low, of course); another enable line and AND gate are used to similarly allow the  $\overline{VC}$  pulse to reach the RESET input and drive the Q output low. Note that the  $\overline{VC}$  signal is inverted in that circuit. The advantage of the two-button control is that it is impossible to mis-set the flip-flop if the correct button is pressed. Repeated pressing of a button or (in the case of a continuous command) repeated  $\overline{VC}$  pulses will have no effect on the output; only pressing the opposite button will alternate the outputs.


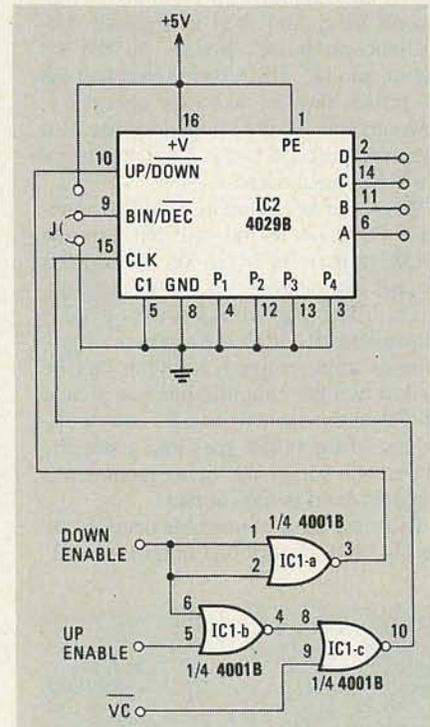


FIG. 17—THE UP/DOWN counter interface circuit. The 4029B can be set to count in either BCD or binary format, or can be replaced by a 4510B/4516B counter.

The last and most complex decoder is an up/down counter controlled by two enable lines (Fig. 17). One is used to activate the counter in the up-counting mode; the other is used to activate the counter in the down-counting mode. In both cases, the  $\overline{VC}$  pulse is used to clock the counter in the desired direction.

(Continued on page 113)

# Audio Comping

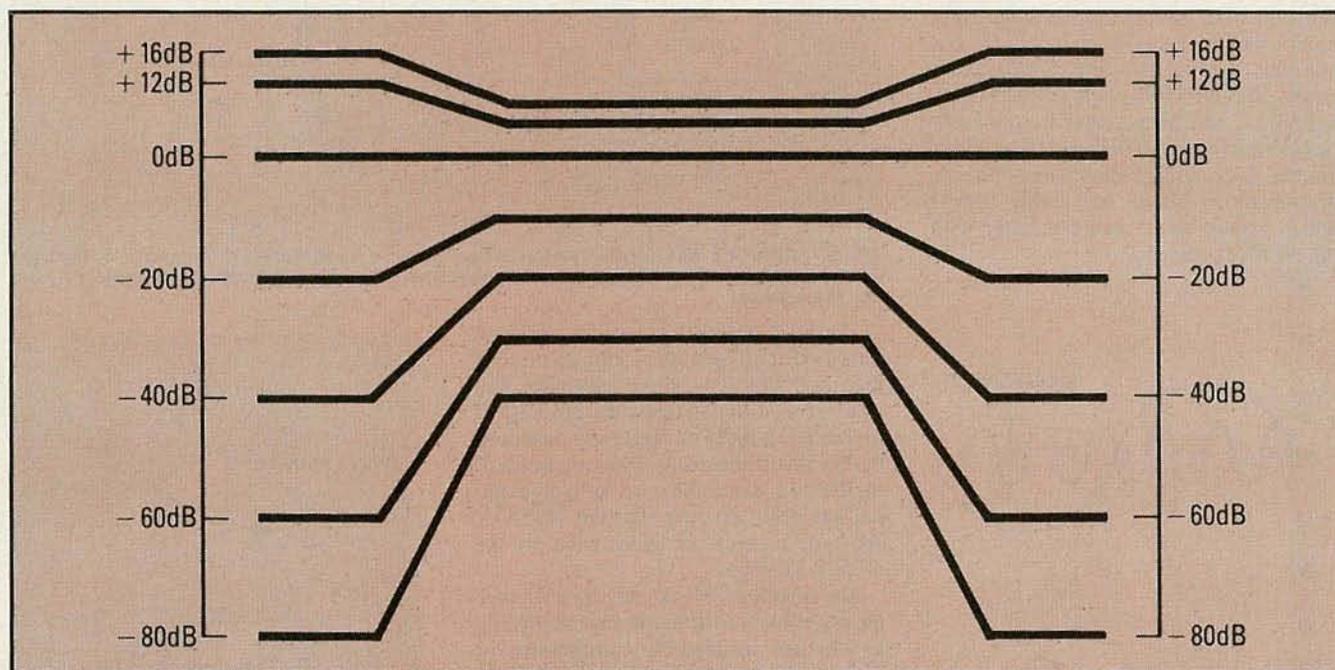

You can build a professional-quality compander for your hi-fi system using circuits designed around Signetics' NE570 compander IC.

TOM PASK

IF YOU'RE LOOKING FOR WAYS TO IMPROVE your hi-fi system, don't overlook companders. They can be used to reduce noise from your tape recordings and to bring back the dynamic range that is lost when recording and broadcast engineers compress their audio signals. Companders also are used in cordless telephones, speaker-phones, and wireless microphones, and as signal-level controllers in electronic organs, MODEM's, and mobile telephone equipment.

In this article we will explain the fundamental theory of companders, discuss basic applications, and we'll also present a circuit, complete with PC-board patterns, that you can use to experiment with the Signetics NE570 family of IC companders.

## Basic compander theory

The compander is a versatile, low-cost, dual-channel gain-control device primarily used for audio noise reduction. The word compander is actually a contraction of the two words *COMP*ressor and *EXP*ANDER, and they indicate the compander's complementary tasks: compressing and expanding the level of an audio signal, which could be music,

speech, or tone-encoded computer data. Signals are compressed before transmitting or recording so that all components of the signal are above the inherent noise level of the transmitting or recording medium, but below the saturation level of that medium. Signals then undergo complementary expansion at the receiving, or playback device to restore their natural dynamic range, and to improve the ratio of the signal to the noise that entered in the transmitting or recording medium.

For example, assume we have a 1000-Hz signal at a level of 2.5 volts P-P combined with a 6000-Hz signal at a level of 1.0 volt P-P. (See Fig. 1-a.) On an oscilloscope the 6000-Hz signal would seem to "ride" the 1000-Hz signal, but for clarity, we have shown them separately. The 0.5 volt P-P high-frequency noise signal is not part of the original signal; it's noise that's introduced in the recording or transmission medium: tape hiss, for example.

In Fig. 1-b we see what happens when an across-the-board gain of three is applied to those signals. The level of the 6000-Hz signal is greatly increased with respect to the noise signal, but the 1000 Hz signal is clipped, due to the 6-volt P-P

dynamic range of our example transmission channel.

That is clearly unacceptable, and Fig. 1-c shows the remedy. There the 1000-Hz signal is left as is, and the 6000-Hz signal is amplified by a factor of two. Now the signal-to-noise ratio of both input signals has been increased with no clipping. That is the essence of *compression*.

By contrast, *expansion* restores all components of a signal to their original levels. Feeding the signal represented in Fig. 1-c through an expander complementary to the compressor that produced that signal would result in the original signal shown in Fig. 1-a. The result is a clean, undistorted signal with a high signal-to-noise ratio and a dynamic range like that of the original signal.

## Companion components

The basic compander consists of a current-controlled variable-gain cell ( $\Delta$ -G), a full-wave averaging rectifier and voltage-to-current converter, (hereafter referred to as the rectifier), and an operational amplifier. The block diagram of the NE570, NE571 and SA571 is shown in Fig. 2-a; that of the NE572 is shown in Fig. 2-b. Note that although the figure shows only

one channel for each type of device, the IC's contain two identical, independent channels.

The NE570 and NE571 have quite similar operating characteristics, but those of the NE570 are somewhat better than those of the NE571, and include wider supply range, lower distortion, lower DC output shift, etc. The SA571 has the same electrical characteristics as the NE571, but operates over a different temperature range. The NE570/1 devices differ from the NE572 in that the latter has an additional buffer inserted between the rectifier and the  $\Delta$ -G cell that allows separate programming of attack and delay times, which cannot be set independently with the NE570/1 devices.

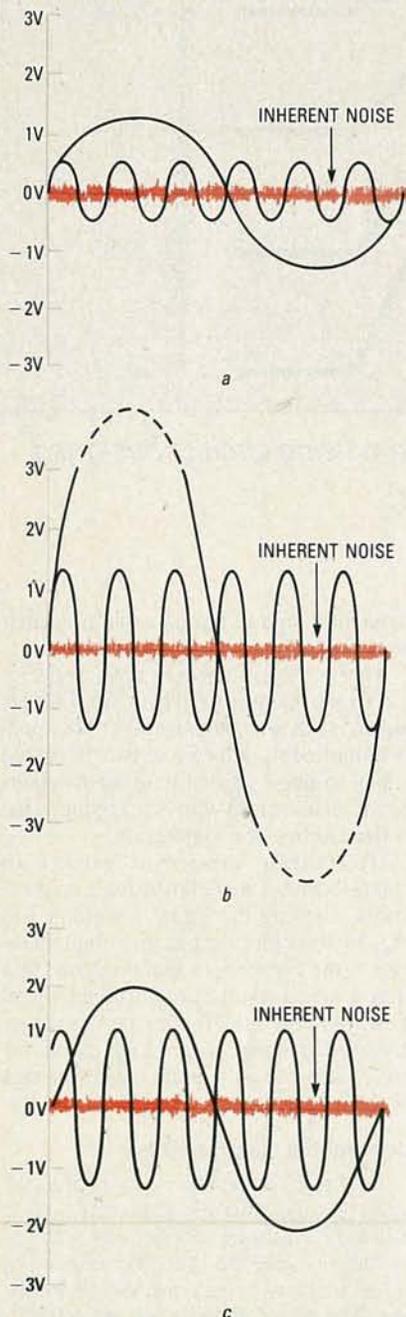


FIG. 1—BASIC COMPANDER ACTION is compared with straight amplification. The input signal (a) is amplified by a factor of three (b) and companded by a factor of two (c).

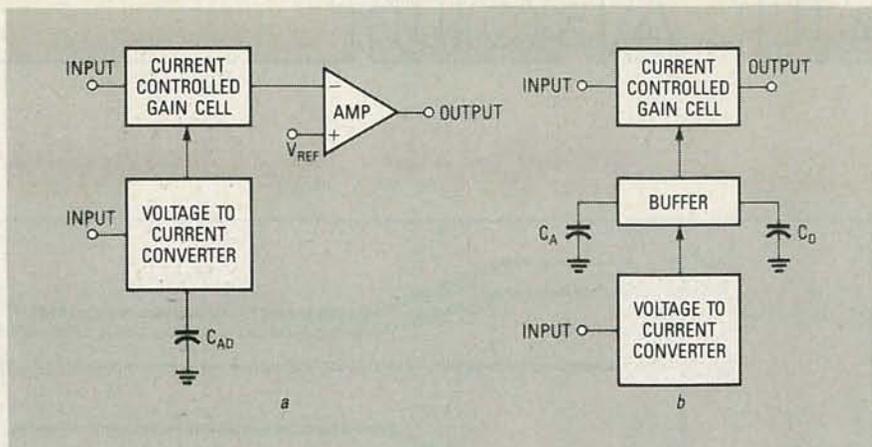


FIG. 2—SIGNETICS' NE570, NE571 and SA571 are shown in a, and the NE572 is shown in b. The latter has no output buffer, but allows attack and delay times to be set independently by capacitors  $C_A$  and  $C_D$ , respectively.

However, that buffer leaves no space on the chip for an output op-amp, so circuits requiring additional drive capability will need an additional outboard op-amp. If high fidelity audio or separately programmable attack and decay times are needed, the NE572 should be used with an external low-noise op-amp like the NE5534. We will restrict our discussion to the NE570/1 devices.

The functional blocks mentioned above are assembled in different ways according to whether we need the compression or the expansion function. But in either case, an operational amplifier provides the main signal path and output drive, and the rectifier converts the AC input voltage into a DC current that controls the gain of the op-amp.

### Compressor theory

As shown in Fig. 3-a, the compressor may be thought of as an op-amp with a variable feedback resistor,  $R_F$ . When the input signal increases above a preset crossover level (0 dB),  $R_F$  decreases in value, and that causes the gain to decrease. As the input signal decreases below the crossover level,  $R_F$  increases in value, and that causes the gain to increase. In fact, as shown in Fig. 3-b; the  $\Delta$ -G cell and rectifier are simply placed in the feedback loop of a standard inverting op-amp circuit and take the place of  $R_F$ . The equation for voltage gain in such a circuit is

$$A_v = -R_F/R_{IN}$$

Referring again to Fig. 3-b, the compressor's gain is described by this equation:

$$A_v = \sqrt{\frac{R_1 R_2 I_B}{2 R_{IN} V_{IN(avg)}}}$$

Resistors  $R_1$  and  $R_2$  are internal to the compander IC, and have values of 10K and 20K, respectively. The bias current  $I_B$  must be limited to 140 $\mu$ A, and  $V_{IN(avg)}$  equals  $0.9 \times V_{IN(rms)}$ .

### Sample compressor application

Since the compressor is a feedback

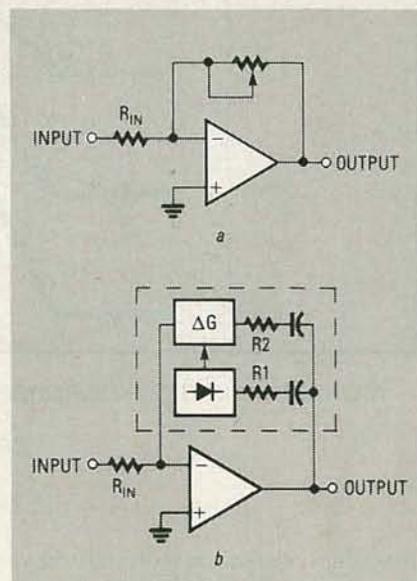


FIG. 3—THE BASIC COMPRESSOR may be thought of as an op-amp with a variable feedback resistor. The components in the dashed box (b) correspond to  $R_F$  in (a).

controlled system, its stability must be maintained for all input conditions. You must bias the DC level of the output pins at approximately half the supply voltage. If that isn't done, the positive or negative peaks may be clipped, causing distortion. To allow for maximum voltage swing, the op-amp is biased by resistors  $R_{DC}$  and  $R_4$  as shown in Fig. 4. The equation describing the output bias level is:

$$V_{OUT(DC)} = V_{REF} (1 + 2R_{DC}/R_4)$$

$V_{REF}$  is biased internally to a level of +1.8 volts.

Note that the value of  $C_{DC}$  must be large enough to shunt any AC flowing through that point to ground. Capacitors  $C_{F1}$  and  $C_{F2}$ , which should have fairly large values, are used in the  $\Delta$ -G and rectifier circuits to prevent DC bias currents from flowing between those circuits. The input capacitor,  $C_{IN}$ , is also used for AC coupling; it preserves the DC bias on the op-amp.

You must plan for the maximum output

## PARTS LIST

All resistors 1/4-watt, 5%

R1—33,000 ohms

R2—36,000 ohms

R3—12,000 ohms

### Capacitors

C1, C4, C5, C7, C8—2.2  $\mu$ F, 25 volts, tantalum

C2, C6, C12, C13—10  $\mu$ F, 35 volts, tantalum

C3, C11—200 pF

C9, C10—1.0  $\mu$ F, 35 volts, tantalum

### Semiconductors

IC1—NE570, NE571, or SA571

### Other components

S1—SPST, PC-mount

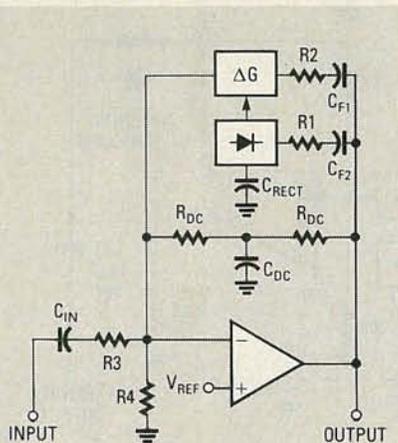


FIG. 4—THE BIASING NETWORK for the compressor. See the text for details on calculating the resistor and capacitor values.

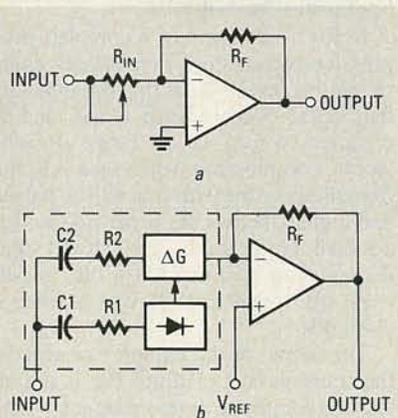


FIG. 5—THE BASIC EXPANDER may be thought of as an op-amp with a variable input resistor. The components in the dashed box (b) correspond to  $R_{IN}$  in (a).

voltage swing because the  $\Delta$ -G and rectifier cells can handle peaks of only 140  $\mu$ A and 300  $\mu$ A, respectively. Use the following formulas to determine the resistor values to use in order to remain below those levels.

$$R1 = (V_{OUT(peak)} / 300 \mu A) - 10,000$$

$$R2 = (V_{OUT(peak)} / 140 \mu A) - 20,000$$

Resistors R1 and R2 are reduced by

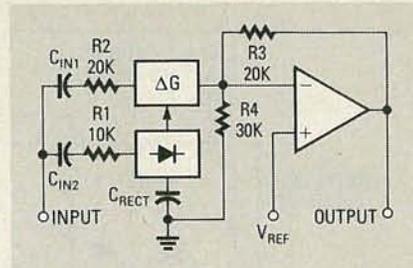


FIG. 6—THE BIASING NETWORK for the expander. See the text for details on calculating the resistor and capacitor values.

10,000 and 20,000 ohms, respectively, because the NE570/1 devices have internal protection resistors with those values.

Rectifier capacitor  $C_{RECT}$  controls the attack and decay times of the circuit. It will usually have a value between 1.0  $\mu$ F and 2.0  $\mu$ F. A 2.0  $\mu$ F capacitor gives an attack time of about 3 ms and a decay time of about 13 ms. Note that decreasing  $C_{RECT}$  to speed up the attack will cause distortion to increase.

Some applications may be especially sensitive to THD (Total Harmonic Distortion) or low-level tracking errors. Signetics' 1985 *Linear LSI Data and Applications Manual* discusses methods of reducing both. Also, some circuit layouts may cause low-level oscillation if the THD trim pin is left unconnected. That is cured by adding a 200 pF capacitor between that pin and ground.

For use in the real world, an input buffer amp may be necessary to match the input impedance of NE570/1 to that of the circuit driving it. In some applications "breathing," noise-pumping, or other strange sounds may occur; they can be reduced or eliminated with pre-emphasis circuitry.

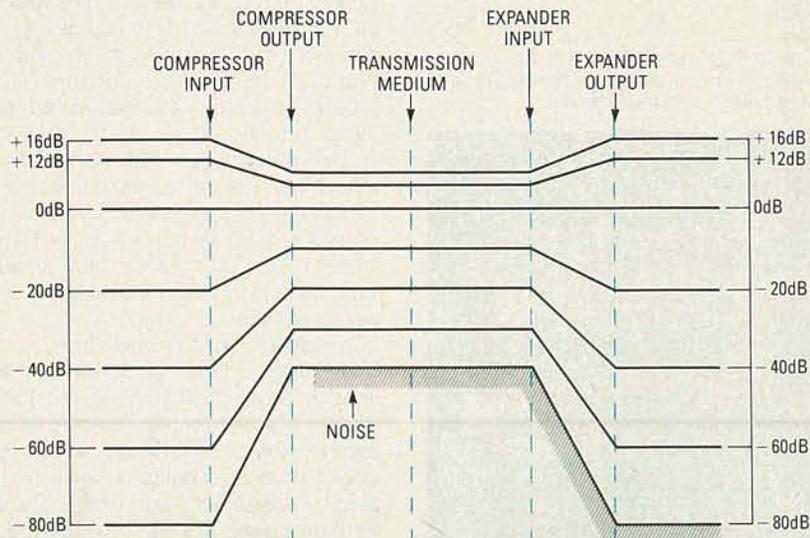


FIG. 7—SIGNAL LEVELS IN A COMPLETE COMPANDER SYSTEM. The compander works on a 2:1 compression ratio and a 1:2 expansion ratio. Noise inherent to the transmission medium is kept below the level of the weakest signal.

## Expander theory

The expander uses the same building blocks as the compressor, but in this configuration the  $\Delta$ -G cell is inserted before the inverting input of the op-amp, where it functions as a variable input resistance,  $R_{IN}$ , as shown in Fig. 5-a. When the input signal increases above a preset crossover level (0 dB), the variable resistor decreases in value, and that causes the gain to increase. As the input signal decreases below the crossover level, the variable resistor increases in value, and that causes the gain to decrease. The equation for voltage gain in such a circuit is still:

$$A_v = -R_F/R_{IN}$$

In fact, in the expander configuration,  $R_{IN}$  is replaced by the  $\Delta$ -G cell and the rectifier as shown in Fig. 5-b. Resistors R1 and R2 are still internal to the compander IC and have values of 10K and 20K, respectively;  $I_B$  must still be maintained below 140  $\mu$ A; so the gain equation for the expander is:

$$A_v = \frac{2 R_3 V_{IN(avg)}}{R_1 R_2 I_B}$$

## Sample expander application

As with the compressor application described above, care has to be taken with the expander to avoid clipping. The output should again be biased at one-half the supply voltage. The circuit shown in Fig. 6 is designed to operate from a six-volt power source, so the DC level of the output is biased at three volts.

When using a supply voltage higher than six volts, adjust the output bias level accordingly. To raise the DC output level, it is recommended that the value of R4 be decreased by connecting resistors in parallel with it. Changing R3 would affect the expander's AC gain, and thus would cause a mismatch in a companding sys-

tem. In other words, the expansion ratio would be different than the compression ratio. The DC bias of the output can be calculated using this equation:

$$V_{OUT} = V_{REF} (1 + R3/R4)$$

If  $R3 = 20K$ ,  $R4 = 30K$  and  $V_{REF} = 1.8$ , then  $V_{OUT} = 2.99$  volts.

The input and output coupling capacitors must be large valued. For lowest distortion, a separate capacitor should be

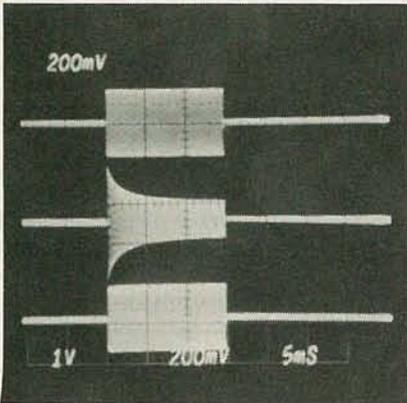


FIG. 8—THE 15 KHZ SIGNAL in the upper trace is fed through the compressor, whose output appears in the middle trace. That signal is restored to its original form, as shown in the lower trace, by the expander.

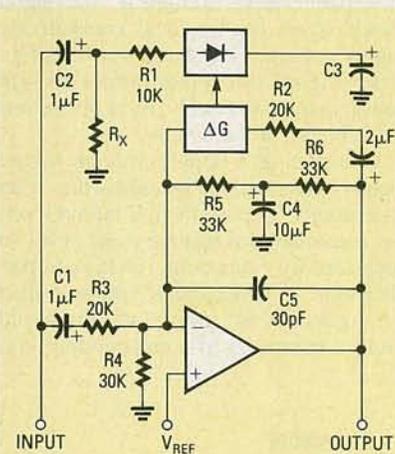


FIG. 9—THE COMPANDER USED AS AN ALC DEVICE. This circuit combines elements of both the compressor and the expander.

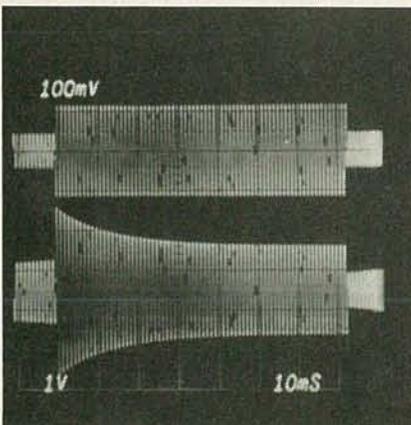


FIG. 10—ALC ACTION is shown here. The upper trace shows the input signal, and the lower trace shows it being processed by the ALC circuit.

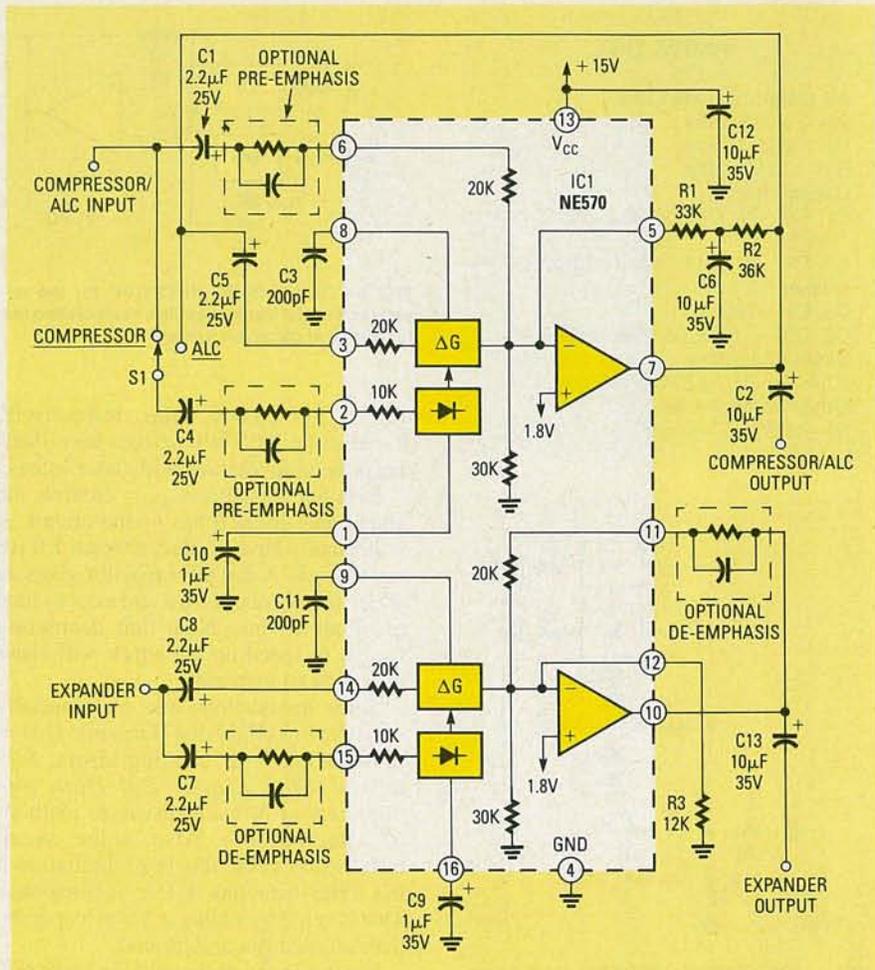


FIG. 11—A COMPANDER CIRCUIT you can build to experiment with compression, expansion and ALC. The pre- and de-emphasis networks may be replaced by jumpers if they are not needed.

placed in series with both the  $\Delta$ -G cell's input ( $C_{IN1}$ ) and the rectifier's input ( $C_{IN2}$ ).

If you anticipate an input signal greater than 2.8 volts peak, which corresponds to an input current of 140  $\mu$ A, then the value of R2 must be increased. If the input signal is greater than 3.0 volts peak, R1 will also have to be increased. As with the compressor, signal distortion can be avoided by limiting the compander's peak input currents.

The effects  $C_{RECT}$  has on attack and delay times, as well as distortion, are the same as in the compressor circuit, so start off with a value of 1  $\mu$ F to 2  $\mu$ F for  $C_{RECT}$ . In any case,  $C_{RECT}$  should have the same value in both circuits of a complete compander system.

An input buffer may again be necessary if the input impedance of the NE570/1 needs to be matched to that of the driving device. Also, de-emphasis would be necessary if the complementary compressor circuit used pre-emphasis, such as that used by high-fidelity tape decks. The distortion trim pin functions as in the compressor, and if not used, should be bypassed with a 200 pF capacitor to ground.

### Comping example

In Fig. 7 we see how a complete compression/expansion system affects signals of various levels. Note that the input signals occur over a 96 dB range, and are compressed to a 48 dB range. In other words, compression works on a 2:1 ratio. Signals above the 0 dB line will be halved, and signals below the 0 dB line will be doubled. For example, the +16 dB signal decreases to a value of +8 dB, and the -80 dB signal increases to a value of -40 dB.

The output of the compressor is fed to the transmission medium (be it the airwaves, telephone lines, magnetic tape, etc.) where a low-level noise signal is picked up. The signal is then fed to the expander where it is expanded from 48 dB to 96 dB, that is, at a 1:2 ratio. Here, signals above the 0 dB line are doubled, and signals below the 0 dB line are halved. For example, the +8 dB signal increases to a value of +16 dB, and the -40 dB signal decreases to a value of -80 dB. Note that the noise arising in the transmission medium is kept below the -80 dB level by companding.

The oscilloscope photo in Fig. 8 shows *continued on page 109*

ACCIDENTAL CONTACT WITH HIGH VOLTAGES or currents can often result in injury or even death. However, there are many instances when deliberate exposure to some type of electrical stimulation is an effective part of treatment for an illness or condition. In this article we are going to look at some of those instances.

## Electrical stimulation of the heart

In a healthy heart, muscle contractions are initiated and coordinated by a natural "pacemaker" and "conduction" system that is made up of special muscle cells. While many cells in the heart will electrically discharge, causing a contraction to occur, the pacemaker area of the heart contains cells that spontaneously discharge the fastest. After the pacemaker cells discharge, electrical signals travel throughout the atria (the top half of the heart). The atria are electrically insulated from the ventricles (the bottom half of the heart). The signal from the atria is conducted to the ventricles by a specialized collection of muscle fibers (the AV node and associated fibers) that cause a delay of about a tenth of a second. Thus, after the atria contract to push blood into the ventricles, there is a delay of about a tenth of a second before the ventricles receive the signal to contract. It is the ventricles that produce the real pumping action, giving a pulse that can be felt at the wrist and elsewhere.

When that normal pattern is disrupted, the heart is said to be in fibrillation. When fibrillation is brought on, due to extra pacemaker signals being generated or to an irritation of the heart, the beating of the heart muscle becomes uncoordinated. During fibrillation the exposed heart can

be seen to writhe like a bag of worms, rather than contracting in a useful manner. If the ventricles beat normally but there is atrial fibrillation, about 20% of the efficiency of the heart is lost because blood does not enter the ventricles as well as it should. In addition, the fibrillation sig-

and decreases the ventricular contraction rate (the effective heart rate).


Ventricular fibrillation, if not treated within minutes, is fatal. About 350,000 Americans die each year from disruptions in cardiac rhythm, usually ventricular fibrillation. Most of those electrical disturbances take place during or within a few days of a myocardial infarction (heart attack). Many of the people who die do so needlessly. Though the heart muscle has been damaged by a heart attack, if the electrical disturbance is corrected, the person might live for many more years.

One way to stop fibrillation of the atria and ventricles is to apply an electrical shock to the chest. That shock is administered via large paddles (as you've doubtless seen on TV or at the movies) using a machine called a defibrillator. When that electrical shock is applied, all muscle cells in the heart are depolarized, as if they had just discharged. The first cells to recover are those in the pacemaker area of the heart; they send signals to the conduction system, which causes organized contraction of the heart muscles.

Figure 1 shows an electrocardiogram of a patient in ventricular fibrillation. The region labeled A shows irregular, nonrepeating voltage fluctuations. A defibrillating shock of about 1,000 volts is applied at B. That causes the electrocardiogram amplifier to overload. For a period the electrocardiogram shows a signal with an elevated baseline, then the amplifier saturates again (C). After a few seconds the heart begins to beat slowly (D), though not in a normal manner.

A relatively small number of people have recurrent episodes of cardiac rhythm disturbances (arrhythmias) that are not as-

## Medical Uses of Electric Shock

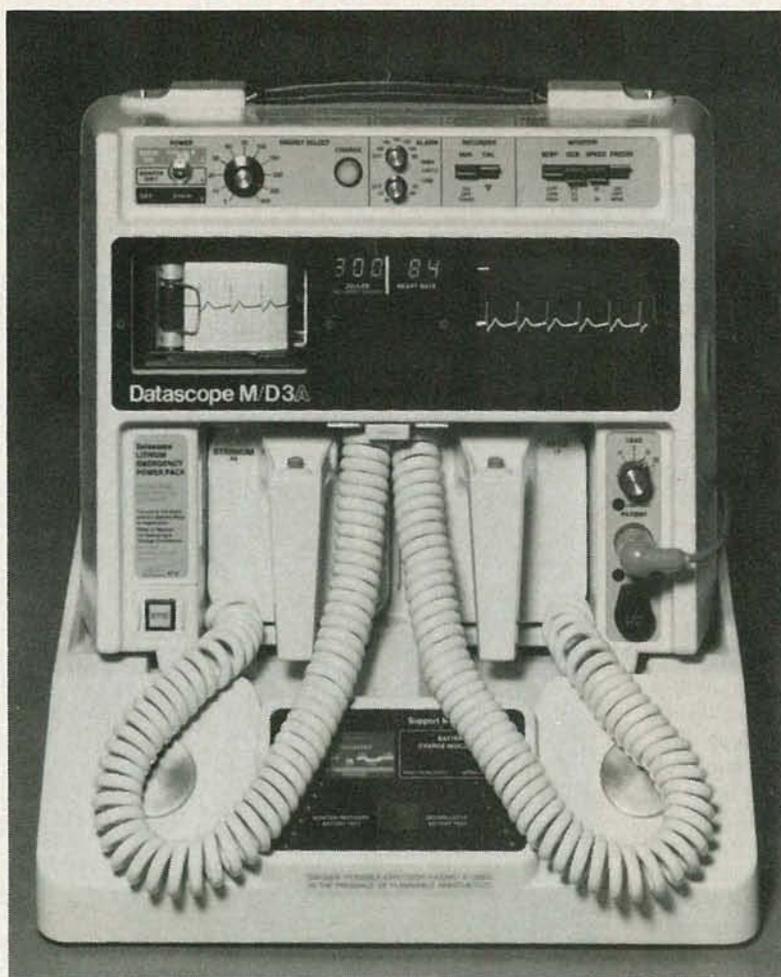

*Electrical stimulation of the body can be dangerous, but there are some instances where it can save a life.*

RAY FISH, Ph.D., M.D.

nals passing through the AV node usually stimulate the ventricles to contract at a rate of about 170 beats per minute, a condition not well tolerated by most individuals. While many people have atrial fibrillation which cannot be stopped, the rate of the beating of the ventricles can be controlled by medication that slows conduction of impulses through the AV node

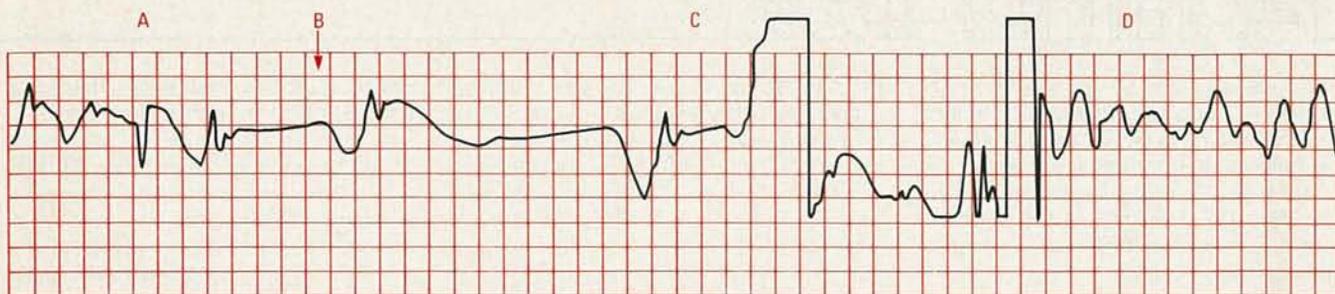


FIG. 1—ELECTROCARDIOGRAM of a patient with ventricular fibrillation. At point *b* defibrillation (the applying of a voltage) is performed. A heartbeat, although abnormal, slowly begins to appear after several seconds (*d*).



FIG. 2—THIS SLOW HEARTBEAT is the result of a heart attack. In order to restore the heartbeat to normal, a pacemaker had to be implanted. Differences in the waveform are due to the different locations of electrodes used to take the reading.

sociated with heart attacks. Many of those disturbances are corrected by electrical shock, or defibrillation. A few dozen people with recurrent potentially-lethal arrhythmias have been treated with surgically implanted defibrillators. When a fatal rhythm is recognized by such a unit, a shock of 30 joules is applied to the heart. That is less than the 300 joules usually applied when the defibrillation shock is administered externally. But then again, the power requirements are less because the shock is applied directly to the heart rather than to the chest wall.

In fibrillation there are too many signals or depolarizations occurring. With a slow or absent heart rate, there are too few depolarizations. Figure 2 shows an electrocardiogram from a patient who has suffered an acute heart attack. The beats are coming much too slowly, about one every 2 seconds. That gives a pulse rate of about 30 beats per minute. It was decided that a pacemaker was needed in that case because drugs would not increase the heart rate, and the patient was in shock. A temporary pacemaker, actually a specially built pulse generator in a small box, was connected to the heart by a catheter with wires built into it. The pacemaker catheter was inserted into a large vein under the clavicle (collar bone) and pushed forward until it reached the heart. (See Figs. 3 and 4.)

Usually when a pacemaker catheter is inserted, the positioning of the catheter is obtained using "fluoroscopy." That technique uses a continuous X-ray source and an image intensifier system that permits the physician to see a real-time image of the catheter working its way to the heart. Because veins branch and turn it is useful to be able to see where the catheter is

by the signal from the pacemaker, were seen in the patient's electrocardiogram. The presence of those spikes meant that the catheter was near the chest electrodes used to monitor the electrocardiogram. The catheter was further advanced until the small spikes were followed by heartbeats, as seen in Fig 5. That was electrical confirmation of the fact that the pacemaker had "captured" (was stimulating) the heart. Later, routine X-rays showed that the pacemaker was in a good location. Because of the type of heart at-

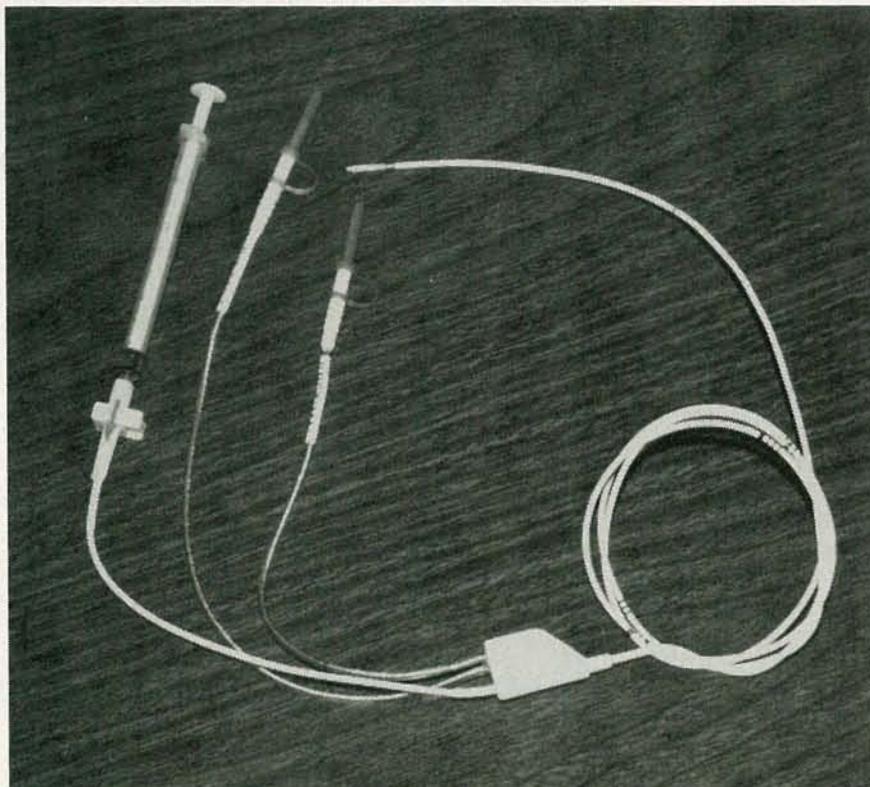


FIG. 3—A PACEMAKER CATHETER, such as the one shown here, is inserted into the body so that the electrodes at its end contact the heart muscle.

going and to twist or redirect it when needed.

Because the condition of the patient whose electrocardiogram is shown in Fig. 2 was so acutely poor, there was not time to set up the equipment or wait for the technicians who run it to come to the hospital. Thus the catheter was inserted "blindly." That is, the catheter was inserted in the vein via a large needle and pushed forward until small spikes, caused

tack, that pacemaker was only needed for a few days. In other cases a permanent pacemaker must be surgically implanted in the patient and connected to the heart.

There are several types of electronic pacemakers. An atrial pacemaker can be used if the atria are not contracting often enough, but the natural conduction between the atria and ventricles is normal. A ventricular pacemaker can be used to stimulate just the ventricles. The atria

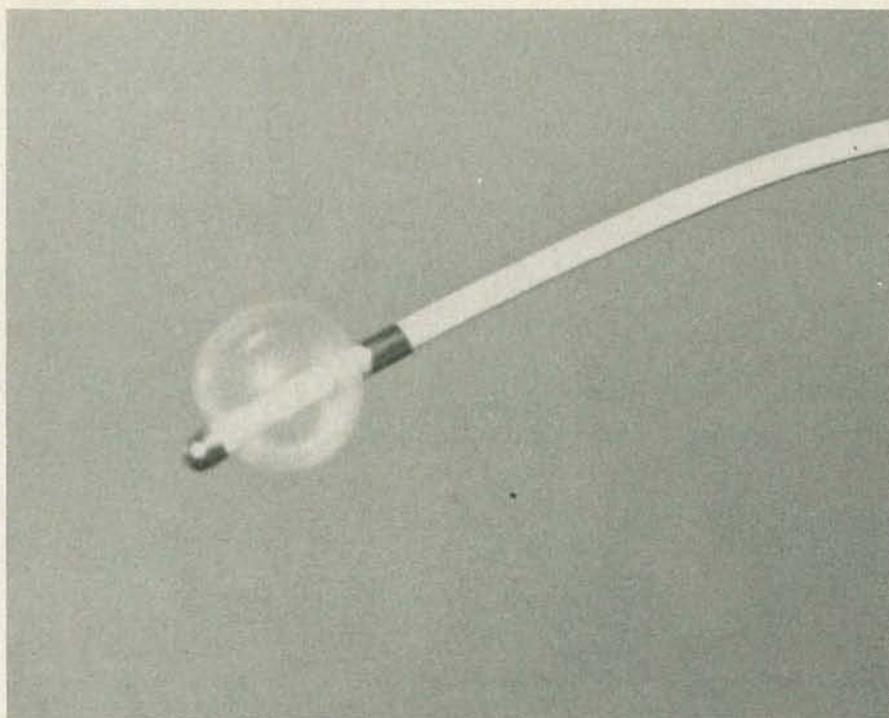


FIG. 4—IF THERE IS ANY CIRCULATION, a balloon at the end of the catheter is inflated so that the catheter tip will be carried to the heart by blood flow.

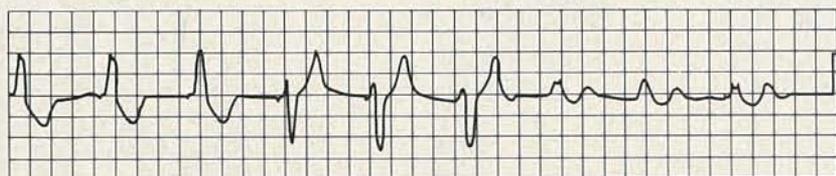


FIG. 5—SMALL SPIKES, which are the output signals from the pacemaker, are followed by heartbeats. This shows that the pacemaker has "captured" the heart.

may be stimulated by backward conduction through the AV node, but the resulting atrial contraction would be at the wrong time to do any good. A sequential pacemaker has two sets of wires: One stimulates or senses the signal from the atria; the second stimulates the ventricles after a delay that simulates the delay normally caused by the AV node. With a sequential pacemaker, the 20% boost in cardiac output provided by the atria is retained.

Different pacemakers operate in different manners. Some work only when needed; those are called *demand pacemakers*. The same wires that stimulate the heart are used to detect heart signals that are spontaneously present. Thus, if the heart is beating on its own, the pacemaker does not fire. If the heart rate gets below the minimum a patient could tolerate, the pacemaker fires.

Some pacemakers fire regardless of spontaneous heart activity. Those are called *asynchronous pacemakers*.

Instead of turning off when a heartbeat is detected, some pacemakers fire within milliseconds of each detected heartbeat (with a maximum rate of firing). In that way externally induced electrical signals

cannot trick the pacemaker into shutting off. Units that operate in that manner are called *stimulated pacemakers*.

External pacemakers have controls that allow the physician to program the stimulus current and heart rate. It is also possible to choose whether or not the pacemaker should be inhibited by spontaneous heart activity. With surgically implanted pacemakers that is not possible. To overcome that problem, remotely programmable pacemakers have been developed. The pacemaker contains a radio receiver that detects coded signals sent by a hand-held transmitter that looks something like a calculator or small computer. With such a unit, it is possible to control a wide variety of pacemaker parameters.

If a permanently implanted pacemaker is not functioning, troubleshooting can be difficult. However, there are some tests that can be done to help determine the cause of the problem.

Almost all demand pacemakers contain a magnetic reed switch. Placing a strong permanent magnet near the pacemaker will activate the switch and convert the pacemaker to an asynchronous mode of operation. As long as the magnet is held in place, the pacemaker will fire at a con-

stant rate regardless of the person's spontaneous heart rate. If a magnet is applied and no pacemaker spikes can be seen on the electrocardiogram, either the pulse generator or the electrode wire is defective.

If a pacemaker fails within weeks of being implanted, the problem is usually with the electrode wire. The wire may have dislodged, or the electrical resistance between the electrode and the heart tissue may have increased.

A failure after years of operation is most often due to weak batteries; placing a magnet over the pacemaker may give a relatively slow heartrate when batteries are weak.

When pacemaker spikes are seen on the electrocardiogram, but there is no capture of the heart, the problem might be with the patient or with electrode placement. A chest X-ray may show a break in the electrode wire. The X-ray can also indicate if the electrode has moved or perforated the wall of the heart. Listening to heart sounds may reveal a "pericardial rub" that indicates irritation of the lining of the outside of the heart; the patient may feel pain due to the electrode. If the electrode is in the proper location, loss of capture may be due to chemical imbalances in the patient's blood. Low levels of potassium or calcium can increase the amount of energy needed for electrical capture of the heart.

Further troubleshooting can be done if the pacemaker is a programmable type. Some such pacemakers allow measurements of lead impedance, sensitivity, and output energy.

### Stimulating the inner ear

Severe hearing loss can be partially corrected by a new kind of hearing aid, manufactured by 3M (St. Paul, MN), that electrically stimulates the inner ear. Unlike conventional hearing aids that amplify and filter sound, those new hearing aids perform a spectrum analysis and use the resulting signals to stimulate certain portions of the auditory nerve.

The human ear is shown in Fig. 6. Normally sound travels through the air to the eardrum. The eardrum vibrates and those vibrations are transferred to three small bones. Those bones in turn cause vibration of fluid in a snail-shaped structure called the cochlea. Sound causes a membrane, called the basilar membrane, in the cochlea to vibrate at various places. Which portion of the membrane vibrates depends on the frequency of the sound present. Specialized receptor cells along the membrane transmit signals to fibers of the auditory nerve. Thus the ear acts as a real time "spectrum analyzer" and transmits many parallel signals to the brain.

The portion of the basilar membrane that vibrates determines the pitch that is perceived. To a lesser extent the frequen-

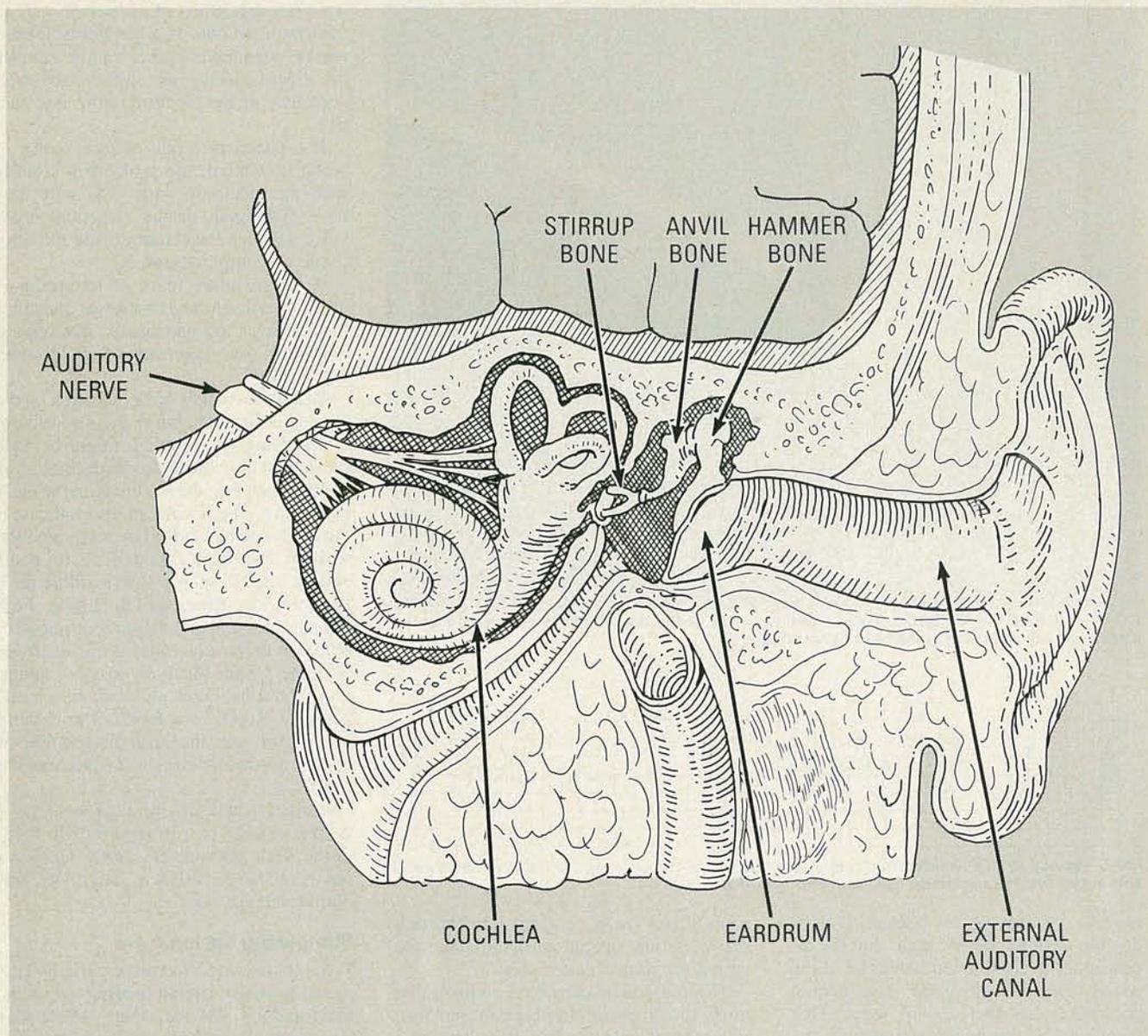


FIG. 6—THE MAJOR STRUCTURES of the human ear are shown here.

cy of stimulation of the basilar membrane as well as the location of the stimulation influences the perception of pitch; that is more important at lower frequencies.

Surgery and conventional hearing aids can correct many hearing problems that are caused by damage to the structures of the outer ear (ear canal) and the middle ear (the eardrum and three bones). But if the cochlea (inner ear) were damaged, there was little that could be done until recently. Clinical trials of cochlear implants began in 1972. Since then hundreds of people have had electrode arrays inserted into their inner ears.

The earliest cochlear implant, or prosthesis, used a single electrode. Such a device allows the user to recognize differences in a sound's intensity and duration, but allowed only low frequency sounds to be recognized. Single electrode devices allow users to recognize some en-

vironmental sounds and make lipreading easier.

Multiple channel cochlear implants contain spectrum analyzers and may have 16 electrodes. The stimulating voltage on each electrode is determined by the amplitude of sound in a certain frequency range. Information about the timing and amplitude of signals in various frequency ranges is preserved. Some users of multiple channel cochlear implants are able to understand speech in a limited manner. One study reported 70% recognition of vowels and 30% recognition of consonants without lipreading. Persons with cochlear implants can hear with sensitivity approaching normal. Although the sound is distorted, doorbells, car horns, and other sounds can be heard almost as well as by a person with normal hearing.

A typical cochlear prosthesis consists

of two electronic assemblies—one outside of the head, and one that is surgically implanted. The external electronics package detects sound, performs spectrum analysis, and transmits signals to the implanted electronics.

The surgically implanted internal electronics package detects the transmitted signals and converts them so that they can be perceived by the auditory nerve. Some systems use a rigid electrode that is inserted directly into the auditory nerve. More commonly, however, a flexible electrode array is inserted into the cochlea and made to lie along the basilar membrane, which is then made to vibrate by the electrodes in response to the transmitted signals. That vibration is detected by the auditory nerve as normal. Which frequencies cause which electrodes to vibrate can be varied to adjust for differences in perception from patient to patient.

R-E

## DESIGNING WITH DIGITAL IC'S

This month we learn about counter circuits and how they work.

JOSEPH J. CARR

**Part 7** BEFORE WE GET TO our topic for this month, let's clear up an error that appeared in our last installment (September 1985). Among the circuits that we looked at then was a shift register called a pseudo-random sequencer. Due to a mix-up, an incorrect schematic was shown for that circuit (Fig. 15 in that issue). The correct schematic is shown here in Fig. 1.

Actually, that circuit can serve as a good introduction to this month's topic—counters. Remember last time we said that the output of the pseudo-random sequencer only *appears* to be random. Instead its output repeats every  $2^n - 1$  times, where  $n$  is the number of stages in the circuit. Because of that, the shift register can be thought of as a counter.

A counter is defined as a sequential-state circuit. That is, it has  $n$  different states into which it can go, and it enters those states in a predetermined sequence. You can use a counter to divide an input signal frequency by  $n$ , or to produce a single output pulse for every  $n$  input pulses.

Let's stop for a moment and define a few terms that are used when talking about counters. The *modulo* of a counter refers to the number of different states that a counter sequences through. For instance, the modulo of a hexadecimal, or base-16 counter is 16. The modulo of a binary counter is two.

The *coding* of a counter tells us which

states it will pass through, and in what sequence. The coding is particularly important when the counter is *weighted*. In a weighted counter, each parallel output is used to represent a number of counts. To make that a little clearer, let's look at an example.

Figure 2 shows a base-16 counter consisting of four J-K flip-flop stages in series. The relationship between the signals at the four parallel outputs and the input is shown in Fig. 3. Studying that figure reveals that the outputs of that modulo-16 counter are weighted 1, 2, 4, and 8. That is  $Q_1 = 2^0$ ;  $Q_2 = 2^1$ ;  $Q_3 = 2^2$ , and  $Q_4 = 2^3$ . Thus, an output of 1010 represents a count of  $(1 \times 1) + (0 \times 2) + (1 \times 4) + (0 \times 8) = 1 + 0 + 4 + 0 = 5$ . A quick check of Fig. 3 will verify that that indeed is the output at T5. That type of weighting is called binary weighting.

A counter is said to be *decodable* if it is possible to continuously monitor the state of the count using relatively simple circuitry. Generally, for a counter to be decodable it should use a standard weighted code such as binary or BCD (more on BCD in a moment). The counter of Fig. 2 is decodable because the state of the count is always available at the parallel outputs.

A counter can also be *resettable* or *presettable*. A resettable counter is one that can be forced into an all-zeros state. In the counter of Fig. 2 that is done by tying the active-low CLR pins on the flip-flops together to form an active-low reset line.

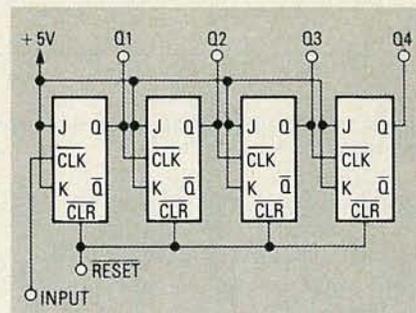


FIG. 2—A FOUR-STAGE ripple counter. The outputs of the counter are weighted 1, 2, 4, and 8.

Bringing that line low momentarily forces all the outputs to go low simultaneously.

A presettable counter is one that can be forced into a desired state. That is done by placing the desired state on a set of preset inputs called "jam" inputs. A pin called PRESET ENABLE, or something similar, controls the preset function.

The reset line can be used to form a decimal (or base-10) counter. In Fig. 4, a NAND gate has been added to our base-16 counter. That gate is placed there to detect the unique output state that follows the tenth count (i.e. both  $Q_2$  and  $Q_4$  are high simultaneously). When those two outputs are high, the output of the NAND gate goes low forcing the reset line, and in turn  $Q_1$ – $Q_4$ , low.

The outputs of that counter are still weighted 1248, but the output states run only from 0000 to 1001 (0 to 9 in base 10). That coding is called Binary Coded Decimal, or BCD.

Let's consider at a typical BCD counter, for instance the 7490. That TTL IC is designed as a bi-quinary counter; that is, it has divide-by-two and divide-by-five sections that are cascaded (pins 12 and 1 shorted) to form a divide-by-ten counter. The reset pins (2 and 3), which are normally strapped together in decimal operation, are active-high. Thus those pins are normally grounded. If it is necessary reset the counter to zero (0000<sub>2</sub>), then pins 2 and 3 are momentarily brought high. That will clear the flip-flops, thereby forcing the outputs to 0000<sub>2</sub>. Another set of terminals (6 & 7) resets the 7490 to 9<sub>10</sub> (1001<sub>2</sub>). The 7490 is now considered the classic decimal counter, although for certain applications other devices may prove to be a better choice.

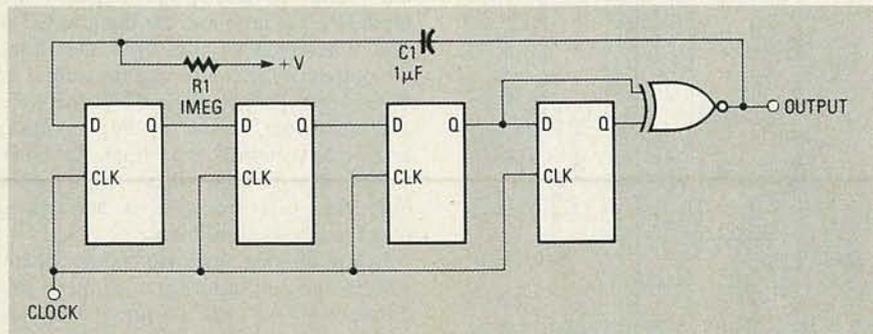


FIG. 1—A PSEUDO-RANDOM sequencer. Due to an error, the schematic shown in the Sept. issue for this circuit was incorrect. The correct circuit is shown here.

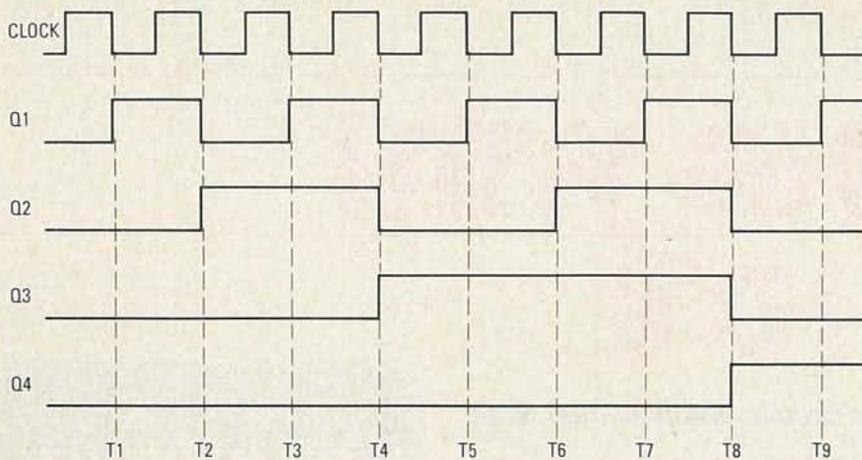


FIG. 3—THIS TIMING DIAGRAM shows the relationship between the clock signal and the signal at the four outputs for the circuit of Fig. 2.

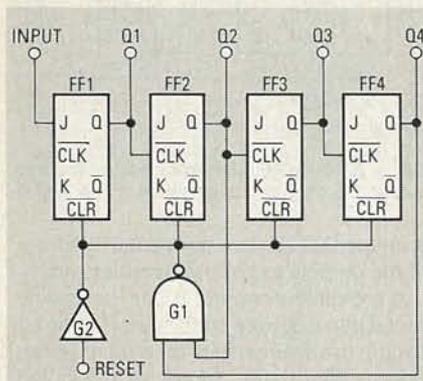


FIG. 4—A BINARY-CODED-DECIMAL counter. This counter resets after the count reaches 1001.

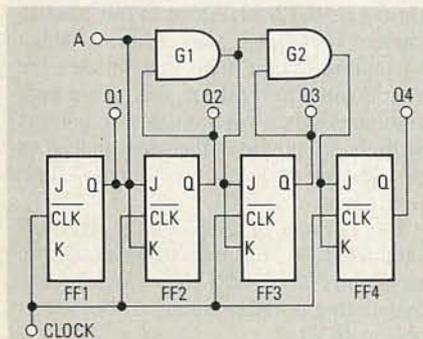


FIG. 5—IN A SYNCHRONOUS COUNTER all outputs change state simultaneously. This counter has two major advantages over the ripple counter—speed and freedom from glitches.

### Synchronous counters

Counters such as the hexadecimal (base-16) and decimal (base-10) circuits discussed thus far suffer from one major problem: speed. Those counters are called ripple counters because they are connected in cascade such that the output of one stage drives the clock input of the succeeding stage. Thus, a change in the input must ripple through the entire chain before it brings the outputs to their final state. In addition, propagation delays in the circuit can cause glitches to appear in the count.

Those problems are eliminated in a second type of counter, called a *synchronous* counter. In that type of counter, all of the counter stages are driven directly from a single input, and all outputs change simultaneously.

Figure 5 shows a synchronous counter circuit. The most obvious features of that circuit are the two AND gates and the fact that all four clock inputs are tied in parallel to form a common clock line. One of the AND gates is connected so that both Q1 and Q2 must be high before flip-flop FF3 changes state. In a similar manner, Q2 and Q3 must be high before FF4 changes state. When a pulse is received on the clock line, all flip-flops that are "scheduled" to change states do so simultaneously, no matter how many stages the counter has.

Some common TTL synchronous counters include the 74160 (BCD with direct clear input), 74161 (hexadecimal with direct clear input), 74162 (BCD), and 74163 (hexadecimal).

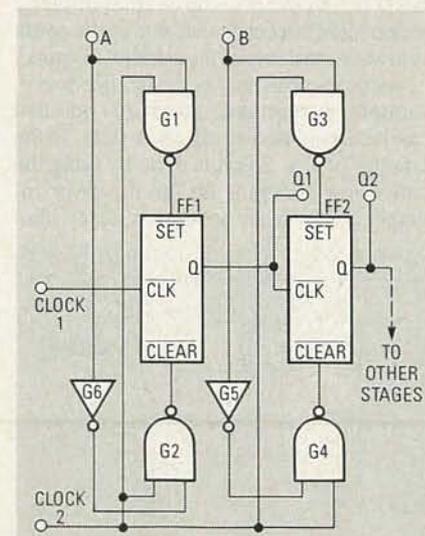


FIG. 6—THE COUNT'S STARTING POINT can be preset using jam inputs A and B. This type of counter is called a presettable counter.

### Preset counters

Most counters increment from 0000<sub>2</sub>. A preset counter is one that can be made to increment from another value. That is done by loading the value of the starting point into the counter via a set of jam inputs.

Figure 6 shows a portion of a preset counter circuit that uses the jam input method to preset the flip-flops of the counter. Although only two stages are shown here, the same technique is used in the succeeding stages.

The preset count value is applied to the jam inputs, labeled here as A and B. For sake of this discussion, let's consider only the A input (which drives FF1). The data at A is applied directly to one input of NAND gate G1, and through an inverter to one input of G2. The remaining inputs of G1 and G2 are connected together to form clock line number 2 (CLOCK2).

In order to understand the operation of CLOCK2 and the A jam input, let's review the rules governing a two-input NAND gate:

- If either input is low, then the output is high.
- Both inputs must be high for the output to be low.

The rules above tell us that CLOCK2 is active-high; let's see why. When CLOCK2 is low, both outputs G1 and G2 are kept high. The output of G1 controls the active-low SET input on FF1, while the output of G2 controls the active-low CLEAR input. Thus, a low on CLOCK2 keeps SET and CLEAR high, and therefore inactive.

Let's consider circuit action for two situations: when A is low and when A is high. The first situation implies that we are forcing the circuit's Q1 output low. Let's see if that is what happens.

If a low is applied to A, then the input to G1 is low, and the input to G2 is high (due to the inverter). When CLOCK2 goes high, the output of G1 is high (keeping SET inactive) and the output of G2 is low (activating CLEAR). Since CLEAR is now active, the flip-flop's output Q goes low. Therefore, Q1 is forced low whenever the A jam input is low and CLOCK2 is active, and that is how the circuit should operate.

Now let's see what happens when the input at A is high, which implies that we are forcing Q1 high. In that situation, the input to G1 is high and the input to G2 is low. When CLOCK2 goes high, therefore, the output of G1 is low, and the output of G2 is high. That renders CLEAR inactive, and SET active, so the flip-flop's output, and circuit output Q1 is high. In other words, if A is high when CLOCK2 goes high, then Q1 is forced high, and that is how the circuit should operate.

In a multi-stage cascade counter, there will be one jam input for each bit of the counter. All bits will be preset simultaneously when CLOCK2 goes high. After

(Continued on page 110)

# PC SERVICE

One of the most difficult tasks in building any construction project featured in **Radio-Electronics** is making the PC board using just the foil pattern provided with the article. Well, we're doing something about it.


We've moved all the foil patterns to this new section, where they're printed by themselves, full sized, with nothing on the back side of the page. What that means

for you is that the printed page can be used directly to produce PC boards!

In order to produce a board directly from the magazine page, remove the page and carefully inspect it under a strong light and/or on a light table. Look for breaks in the traces, bridges between traces, and, in general, all the kinds of things you look for in the final etched board. You can clean up the published artwork the same way


you clean up your own artwork. Drafting tape and graphic aids can fix incomplete traces and doughnuts, and you can use a hobby knife to get rid of bridges and dirt.

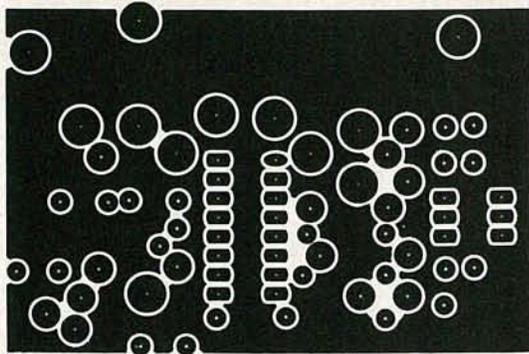An optional step, once you're satisfied that the artwork is clean, is to take a little bit of mineral oil and carefully wipe it across the back of the artwork. That helps make the paper translucent. Don't get any oil on the front side of the paper (the



← 2¾ INCHES →

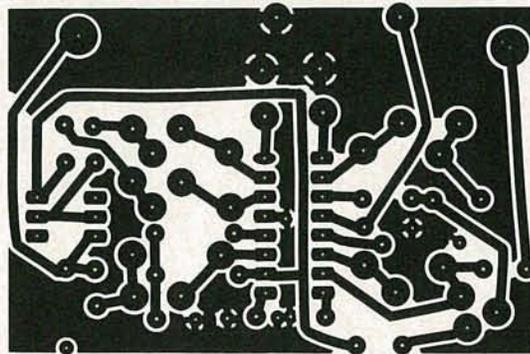COMPONENT SIDE for the audio compander PC board.



← 2¾ INCHES →

SOLDER SIDE for the audio compander PC board.

# PC SERVICE


side with the pattern) because you'll contaminate the sensitized surface of the copper blank. After the oil has "dried" a bit—patting with a paper towel will help speed up the process—place the pattern front side down on the sensitized copper blank, and make the exposure. You'll probably have to use a longer exposure time than you are used to.

We can't tell you exactly how long an

exposure time you will need because we don't know what kind of light source you use. As a starting point, figure that there's a 50 percent increase in exposure time over lithographic film. But you'll have to experiment to find the best method to use with your chemicals. And once you find it, stick with it. Don't forget the "three C's" of making PC boards—care, cleanliness, and consistency.

Finally, we would like to hear how you make out using our method. Write and tell us of your successes, and failures, and what techniques work best for you. Address your letters to:

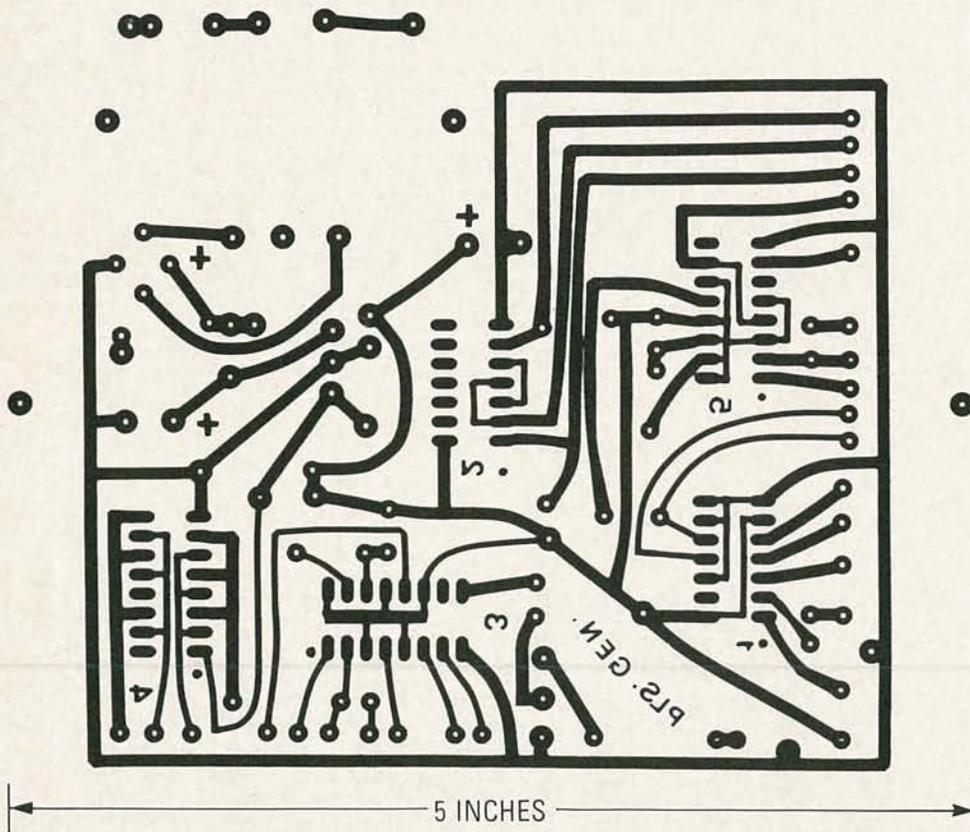**Radio-Electronics**  
Department PCB  
200 Park Avenue South  
New York, NY 10003



USE THIS FOIL PATTERN to make the PC board for the versatile pulse generator.

**United States  
Instrument Rentals, Inc.**



A U.S. Leasing Company

2988 Campus Drive  
San Mateo, CA 94403

Call for Special Prices and

**Free Catalog**  
**800-824-2873**



**Hitachi Denshi America, Ltd.**

**Beckman Industrial™**



**SCOPES**

**Iwatsu**

- All 14 models in stock
- 2-3 year warranties
- 20-250 MHz

Model 5702—\$ 535  
5705—\$ 899  
5710—\$1245  
5711—\$1695  
7506—\$ 749

**Hitachi**

- All 20 models in stock
- 2-3 year warranties
- 20-100 MHz

Model 222—\$ 599  
1050—\$1299  
509—\$1199  
VC 6041—\$5499  
422—\$ 699  
1100—\$2490  
650—\$ 930



Hitachi V-209

**SALE \$695**  
List \$945

**Hitachi V-209**

Portable Dual Trace Scope

- DC-20 MHz
- Battery Operated
- 3-Way Power Supply
- Lightweight
- High Sensitivity and Fast Sweep Timer

**DIGITAL MULTIMETERS**

**Beckman**

- All 300, HD, and circuitmate series
- All accessories in stock

HD100—\$169 320—\$179  
HD110—\$189 330—\$219  
HD130—\$239 350—\$229  
HD140—\$259 360—\$289  
300—\$120 4410—\$239  
310—\$145

**Fluke**

- Autorange • Analog display
- Touchhold function
- 0.3% accuracy • Heavy duty

Model 73—\$ 85 8010A—\$279  
75—\$ 99 8012A—\$359  
21—\$ 99 8020B—\$199  
23—\$145 8022B—\$154  
25—\$299 8024B—\$249  
27—\$259 8050A—\$389

**SALE \$114**  
List \$129

**Fluke 77**

Analog/Digital Multimeter



**COUNTERS—DIGITAL THERMOMETERS—PLOTTERS**

MANY MODELS AVAILABLE — CALL 800-824-2873

Example: **Fluke 1900 Counter** Sale \$389.50

*Battery and BCD Data Options Available*

**Used Test Equipment, too!—Over 3,000 Models Available at  
Huge Discounts with Warranties!**

- Quantity Discounts Available
- Dealers Welcome
- Freight and Tax extra
- Immediate Availability of Equipment

Call

**800-824-2873**

CIRCLE 261 ON FREE INFORMATION CARD

## GLOSSARY OF COMMONLY USED SATELLITE-TV TERMS

For those readers unfamiliar with satellite-TV terminology, we have included the following glossary of commonly used terms. You'll notice that satellite-TV technology has not only caused the development of "a language of its own." In many cases, existing words and phrases are given new meanings. In such cases, we will deal only with the definition related to satellite TV.

**Active component**—A device whose output is dependent on a source of power other than the input signal.

**Aperture**—The diameter of an antenna dish.

**Apogee**—The point in an elliptical satellite-orbit that is farthest from the earth's surface.

**Audio subcarrier**—Subcarriers of satellite video-signals that are modulated by audio. The frequency range can be from 5–8 MHz but is usually 6.2 or 6.8 MHz.

**Az/El mount**—A dish mount whose position is changed by two separate adjustments (in azimuth and elevation.)

**Azimuth**—The angular displacement of a dish in a horizontal plane with respect to true north (measured in a clockwise direction).

**Baseband**—The frequency band occupied by the modulating signal. For example, baseband-video signals occupy a band from 0 to 4.3 MHz.

**Block downconverter**—A device that converts an entire band (for example the 3.7–4.2 GHz C-band) down to a lower band of frequencies.

**Boresight point**—The area of maximum signal strength of a down-link signal. The center of the transponder "footprint."

**C band**—A band of downlink frequencies having a range from 3.7 GHz to 4.2 GHz. This band also includes uplink signal frequencies from 5.92 to 6.42 GHz.

**Cassegrain antenna**—An antenna that uses a subreflector at the focal point to reflect the received signals to a feed located at the dish's apex (center).

**CATV**—Abbreviation for Community Antenna TeleVision. Now generally used to mean cable TV.

**Channel**—A band of frequencies used for carrying video and/or audio signals, data, news, etc. Bandwidth depends on the amount of information to be transmitted. Channel frequencies are specified in the U.S. by the FCC.

**Chroma**—An abbreviation of chrominance. Color signals. A reference to a combination of hue, purity and saturation.

**Circular polarization**—A form of polarization of electromagnetic signals (such as from a satellite) in which the electric field of the signal is made to assume helical form, either clockwise or counterclockwise.

**Clarke belt**—The orbital path followed by geosynchronous satellites named after Arthur Clarke, noted science-fiction writer who made the original suggestion about the possibility of geostationary satellites. The orbit is 22,300 miles.

**C/N**—Carrier-to-noise ratio—The ratio of the satellite-signal carrier strength to the power of the received noise, measured in decibels.

**Color Edging**—Extraneous colors that appear along the edges of video pictures, but that don't have any color relationship to those areas.

**Color subcarrier**—A subcarrier (3.58 MHz) of a composite-video signal. Also called chrominance subcarrier.

**Decoder**—Device for unscrambling video signals which have been encoded.

**Dish**—A device that reflects received satellite microwave signals to a feedhorn. Sometimes incorrectly referred to as an antenna.

**Dish illumination**—The area of a dish as seen by the feedhorn.

**Dithering**—The process of equalizing the video signal. The 6-MHz satellite signal is shifted up and down the 36-MHz satellite transponder spectrum to distribute the energy of the video signal. The purpose is to reduce the interference that any terrestrial microwave transmitter could cause to the satellite transmission.

**Downconverter**—The part of a satellite receiving system that converts the downlink signals to a 70-MHz intermediate frequency that is used by the receiver. Although it is sometimes part of the receiver, it is more often externally mounted directly at the LNA so that inexpensive coaxial cable can bring the signal to the receiver.

**Downlink signals**—The signals that are transmitted from a satellite's transponder to earth.

**Dual feedhorn**—A waveguide feed system designed for both vertically and horizontally polarized signals.

**Dual orthomode coupler**—A dish-mounted device that allows reception of both vertically and horizontally polarized signals.

**Earth station**—A station equipped with transmitting equipment for the production of uplink signals, and also a complete receiving system for picking up downlink signals. Sometimes used synonymously, but incorrectly, with TVRO.

**EIRP**—An abbreviation for effective isotropic radiated power. The energy level of a transmitted signal expressed in dBW.

**Elevation**—The vertical angular displacement of a dish with the earth considered as a horizontal frame of reference.

**Encoding**—The scrambling of a signal to prevent viewing of a program by non-subscribers.

**F/D ratio**—The ratio of the focal length of a dish to its diameter. A method for indicating the depth of a dish.

**Feedhorn**—The entrance to the waveguide used to channel signals from the focal point of the dish to the LNA. See Horn.

**Figure of merit**—A quality factor comparing dish gain to system noise and written as  $G/T$  where T is the system noise in °K and G is the gain of the dish in dB.

**Focal length**—The distance from the center of the dish to its focal point.

**Focal point**—The point at which all the signals reflected by a dish join or cross.

**Footprint**—The area covered by downlink signals transmitted from a satellite.

**Frequency coordinator**—A test procedure that is part of a site survey to determine interference-signal levels.



# ELECTRONICS BOOK CLUB

The Best Source for Hobbyists and Professionals  
for Over 20 Years!

Time- and Money-Saving Advice . . .  
Practical Troubleshooting & Repair Tips . . .  
State-of-the-art Technology . . . Hundreds  
of Projects . . . Plus, Exceptional Savings

## Select 5 Books for Only \$2<sup>95</sup>




1536  
List \$14.95



1393P  
List \$14.50 (paper)



1542  
List \$21.95

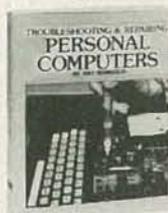

1539P  
List \$15.95 (paper)



1013  
List \$14.95



1245P  
List \$16.95 (paper)



1777  
List \$21.95



1599P  
List \$15.95 (paper)




1199  
List \$21.95



1532P  
List \$12.95 (paper)



1113P  
List \$7.95 (paper)

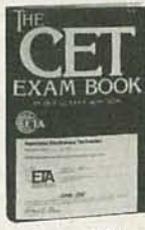

1670  
List \$14.95



1316P  
List \$12.50 (paper)



1909  
List \$21.95




1183  
List \$16.95



1234  
List \$12.95



1474P  
List \$12.95 (paper)

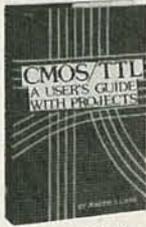

1650  
List \$19.95



1339P  
List \$7.95 (paper)



1699  
List \$19.95




1529P  
List \$14.95 (paper)



1431  
List \$17.95



1875  
List \$21.95

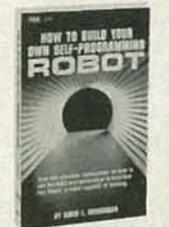

1241P  
List \$10.25 (paper)



1719  
List \$18.95



1672  
List \$18.95



1602  
List \$15.95



1690  
List \$19.95

FREE guide to  
mail order sources  
for electronic parts  
and components

A \$6.95  
Value!



## FREE When You Join Now

### 7 very good reasons to join the Electronics Book Club

- **Big Savings.** Save 20% to 75% on books sure to increase your electronics know-how
- **No-Risk Guarantee.** All books returnable within 10 days without obligation
- **Club News Bulletins.** All about current selections—mains, alternates, extras—plus bonus offers. Comes 13 times a year with hundreds of up-to-the-minute titles to pick from
- **Automatic Order.** Do nothing, and the Main selection will be shipped automatically! But . . . if you want an Alternate selection—or no books at all—we'll follow the instructions you give on the reply form provided with every News Bulletin
- **Bonus Books.** Immediately get Dividend Certificates with every book purchased and qualify for big discounts of 60% to 80%.
- **Extra Bonuses.** Take advantage of added-value promotions, plus special discounts
- **Exceptional Quality.** All books are first-rate publisher's editions selected by our Editorial Board and filled with useful up-to-the-minute information.

## ELECTRONICS BOOK CLUB

P.O. Box 10,  
Blue Ridge Summit, PA 17214

Please accept my membership in the Electronics Book Club and send the 5 volumes circled below, plus my FREE copy of *The Electronics Buyer's Guide* billing me only \$2.95 plus shipping and handling charges. If not satisfied, I may return the books within ten days without obligation and have my membership canceled. I agree to purchase 4 or more books at regular Club prices (plus shipping/handling) during the next 12 months, and may resign any time thereafter.

1013 1113P 1183 1199 1234 1241P 1245P 1316P 1339P  
1393P 1431 1474P 1529P 1532P 1536 1539P 1542 1599P 1602  
1650 1670 1672 1690 1699 1719 1777 1875 1909

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_ Phone \_\_\_\_\_

Valid for new members only. Foreign applicants will receive ordering instructions. Canada must remit in U.S. currency. This order subject to acceptance by the Electronics Book Club.

RE-1185

CIRCLE 276 ON FREE INFORMATION CARD

NOVEMBER 1985

**Frequency reuse**—A method that allows two different TV channels to be broadcast simultaneously on the same transponder by vertically polarizing one channel and horizontally polarizing the other. Another method of frequency reuse is to space satellites about 4° apart. A TVRO pointed at one satellite will not detect any signal from the other satellite, even if it is operating at the same frequency.

**Geodetic north**—A reference to the non-magnetic poles. Also called true north.

**Geostationary**—Geosynchronous. Fixed relative to the Earth. A satellite in the Clarke belt is geostationary.

**Global beam**—A broad pattern of signal radiation from a satellite that covers one third the Earth's surface. Used by INTELSAT satellites.

**G/T**—A figure of merit that describes the capability of a TVRO system to receive a signal from a satellite. The ratio (in decibels) of the gain of a receiving system to the noise temperature of the system.

**Horn**—A type of waveguide with a flared end. Its shape is selected so as to provide a better impedance match between the feed and open air. See Feedhorn.

**Hyperboloidal subreflector**—The secondary reflector used in a Cassegrain antenna system.

**Impedance**—The algebraic sum of resistance and reactance. Represented by the letter Z.

**Isolator**—A device that allows the transmission of signals in one direction while blocking or attenuating them in the other.

**Ku Band**—Also K band. A band of frequencies that extends from 11.7 to 12.7 GHz. The band is separated into two portions: 11.7–12.2 GHz (fixed satellite services—intended for point-to-point services) and 12.2–12.7 (for broadcasting satellite service or DBS).

**Line amplifier**—An amplifier inserted in any part of the transmission line following the downconverter to compensate signal losses caused by long lengths of coaxial cable or the insertion of passive devices such as splitters. Line amplifiers are also used when the signal must drive a number of television receivers.

**Look angle**—The positioning angle of a mount that permits a dish to focus on ("see") a satellite.

**Low-noise amplifier**—Abbreviated as LNA. A wide band, non-tunable amplifier that accepts satellite signals from an antenna probe and delivers them to a downconverter.

**Luminance signal**—Also known as a brightness signal. The monochrome portion of a color television signal.

**Microwaves**—Generally considered to be RF waves in the frequency range of 3 GHz to 30 GHz.

**Multiple LNA's**—A pair of LNA's with one used for the amplification of vertically polarized signals, the other for horizontally polarized signals.

**Noise**—Any unwanted disturbance (can be mechanical or electrical).

**Noise factor**—The ratio of output S/N to input S/N.

**Noise figure**—The ratio of output noise level to input noise level.

**Noise temperature**—Noise of a component expressed in degrees Kelvin, ordinarily used with reference to an LNA. The thermal noise that the LNA adds to the TVRO system.

**Path loss**—Also known as space loss. The attenuation of a signal as it travels through space.

**Perigee**—The point in an elliptical orbit that is closest to the earth.

**Petalized dish**—A receiving dish that is shipped in sections "petals" and assembled at the installation site.

**Polar mount**—A support for a dish that permits simultaneous movements in azimuth and elevation.

**Polarization**—A property of a radiated electromagnetic wave that describes the direction of its electric field.

**Prime focus feed**—An arrangement in which the entrance to a section of a waveguide is positioned at the signal focal point.

**Reception window**—An imaginary rectangle in front of a dish defining the limits of dish movement for reception from a satellite.

**Remodulation**—The process of modulating the recovered (demodulated) baseband signals in a satellite receiver.

**Satellite receiver**—A component used for tuning in a selected satellite transponder. It may contain one or two downconverters, or none. The receiver recovers the original baseband signals and delivers them to a remodulator. The receiver can also supply the DC operating voltages for an external LNA and downconverter.

**Scalar feed**—A series of concentric rings positioned at the mouth of the feedhorn that act as an aid in picking up reflected signals from the dish.

**Slot**—The longitudinal position of a satellite in geosynchronous orbit.

**S/N**—Signal-to-noise ratio. Ratio of the magnitudes of a signal to that of the noise. Usually expressed in decibels.

**Spherical dish**—A dish whose surface is a section of a sphere.

**Splitter**—A device with one input that provides two or more outputs to allow multiple receiver hookups to one antenna. Can be passive (an antenna coupler) or active, providing gain.

**Thermal noise**—Noise that occurs in all transmission media and communications equipment as a result of random electron motion (which is a function of temperature). Thermal noise sets the lower limit for the sensitivity of a receiving system.

**Translation frequency**—The 2220-MHz (2.2-GHz) frequency difference between an uplink and a downlink signal.

**Transponder**—A receiver-transmitter combination that receives (uplink) signals, and retransmits the signals on a different (downlink) carrier frequency.

**Unguided wave**—A broadcast wave.

**Uplink**—The signals transmitted from an earth station to one or more geosynchronous satellites.

**Video inversion**—A type of encoding or scrambling used in which the transmitted downlink video signals are inverted.

**Voltage standing wave ratio**—Abbreviated as VSWR. An indication of the amount of signal energy accepted by a load or reflected to the source. The best VSWR is a ratio 1:1.

**VTO**—Voltage Tuned Oscillator. In a TVRO, the local oscillator in an externally positioned downconverter whose operating frequency is changed by a DC voltage delivered from the in-home satellite receiver.

**Waveguide**—A transmission line made from a hollow conducting tube (rectangular or tubular) through which electromagnetic waves propagate.


**Wind load survival**—The amount of wind pressure tolerated by a dish.

# "As we watched the game they thought I had a new stereo TV."

My friends could not believe the thunderous sound coming from the speakers on each side of my TV. My living room seemed as if it were 300 yards wide and had 30,000 people in it. Even at low volume levels my dad was amazed at how much clearer and better he could hear the TV.


I have to explain to everyone that what they are listening to is my new Rhoades Tele-Amp® system with Stereo-Plex™. The Tele-Amp® easily connects to any TV or VCR regardless of age, and to any pair of stereo speakers.

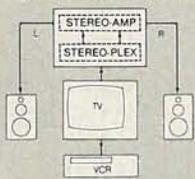The Tele-Amp® takes the audio from the TV or the VCR and processes it through three key elements. The exclusive Stereo-Plex™ generator, a true stereo amplifier (both of which are built inside every Tele-Amp® model), and then, of course, a pair of hi-fi stereo speakers of most any size.


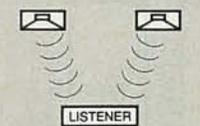
## 1st Missing TV Element

The Stereo-Plex™ generator transforms the mono-audio signal into two sparkling left and right channels of Stereo-Plex™. Mono sounds, even when played



through two speakers, appear to come from one direction—the center. Stereo and Stereo-Plex™ sounds come from two directions. If you already have a stereo TV or VCR, no problem. Just plug them in (TA-450). Since most TV and Cable programming is mono, the Stereo-Plex™ circuitry will pick up where your stereo TV or VCR stops short. When there is a stereo program present, just cut the Stereo-Plex™ off, and the stereo signal will go through the stereo amplifier only (TA-450).

## The 2nd Missing TV Element

The class A stereo amplifier inside the Tele-Amp® develops two channels of power to

drive most any size stereo speakers to room-splitting sound. Low distortion, 0.01% typical at full power, and a broad 20 to 20,000Hz frequency response assure smooth reproduction. Both Tele-Amp® models operate on 110-120V AC @ 16 watts.

## The 3rd Missing TV Element

Both Tele-Amp® models are available with or without speakers. If you choose them with speakers, you will receive two 17" x 10" x 18" beautifully manufactured speakers each with a 1½" cone tweeter, and an 8" foam edge woofer. If you choose a Tele-Amp® without speakers, that's OK, too, because each Tele-Amp® will drive most any speaker of your own choosing.

## GOOD

The input on the TA-300 easily connects to the earphone jack or alligator clips to the speaker terminal of any TV. The outputs of the TA-300 connect directly to any



left and right speakers. The balance controls on the TA-300 may be adjusted for the optimum level on each channel. Once the TA-300 is connected and adjusted, the TA-300 amplifier volume tracks up and down and goes on and off with the TV. This is doubly nice if your TV has a remote control. Because of the TA-300's size it can be mounted out of sight behind the TV or speakers and forgotten.

## BEST

The TA-450 has all the same features as the TA-300, plus a high impedance input so it can be used directly off any VCR audio output jacks; plus up to three stereo or mono inputs for other components; plus a front-mounted volume control and on/off switch; plus a Stereo-Plex™ bypass so that if a stereo component is plugged in, the

Stereo-Plex™ generator may be turned off; plus a headphone jack for private listening; plus EQX noise reduction and bass boost; plus rear-mounted balance control.



## ★ Made in America ★

No matter which Tele-Amp® you choose, they are both engineered, designed, and built here in America, to exacting qualities, by the company that started Good TV Listening 12 years ago. Your order will be taken by knowledgeable personnel that can answer your questions intelligently, and should your Tele-Amp® ever need service, you can be assured that our factory technicians will repair it quickly and correctly.

Sincerely  
*David Rhoades*  
David Rhoades

## TRY A TELE-AMP® AT NO RISK

Take the first 30 days with Tele-Amp® as a test. If you're not completely satisfied, return it for a complete refund and your mailing costs. You can't lose. Tele-Amp® is also backed with a two-year warranty on parts and labor.

**Tele-Amp® TA-300**, \$79.95 plus \$3.00 shipping and handling.

**TA-300 w/speakers**, \$179.95 plus \$9.00 shipping and handling.

**Tele-Amp® TA-450**, \$129.95 plus \$4.00 shipping and handling.

**TA-450 w/speakers**, \$229.95 plus \$9.00 shipping and handling.

**TOLL FREE 1-800-251-8608**

In Tennessee call 1-615-381-9001

24 Hours



Send mail orders to address below. Credit card and money orders processed immediately. Checks require 18 days.

# RHODES

NATIONAL CORPORATION  
Department 246  
Highway 99 East • P.O. Box 1316  
Columbia, TN 38402

## Add stereo sound to your TV with the STEREO TELE-AMP®

CIRCLE 283 ON FREE INFORMATION CARD

# DESIGNER'S NOTEBOOK



ROBERT GROSSBLATT  
CIRCUITS EDITOR

An expandable keyboard encoder and display circuit.

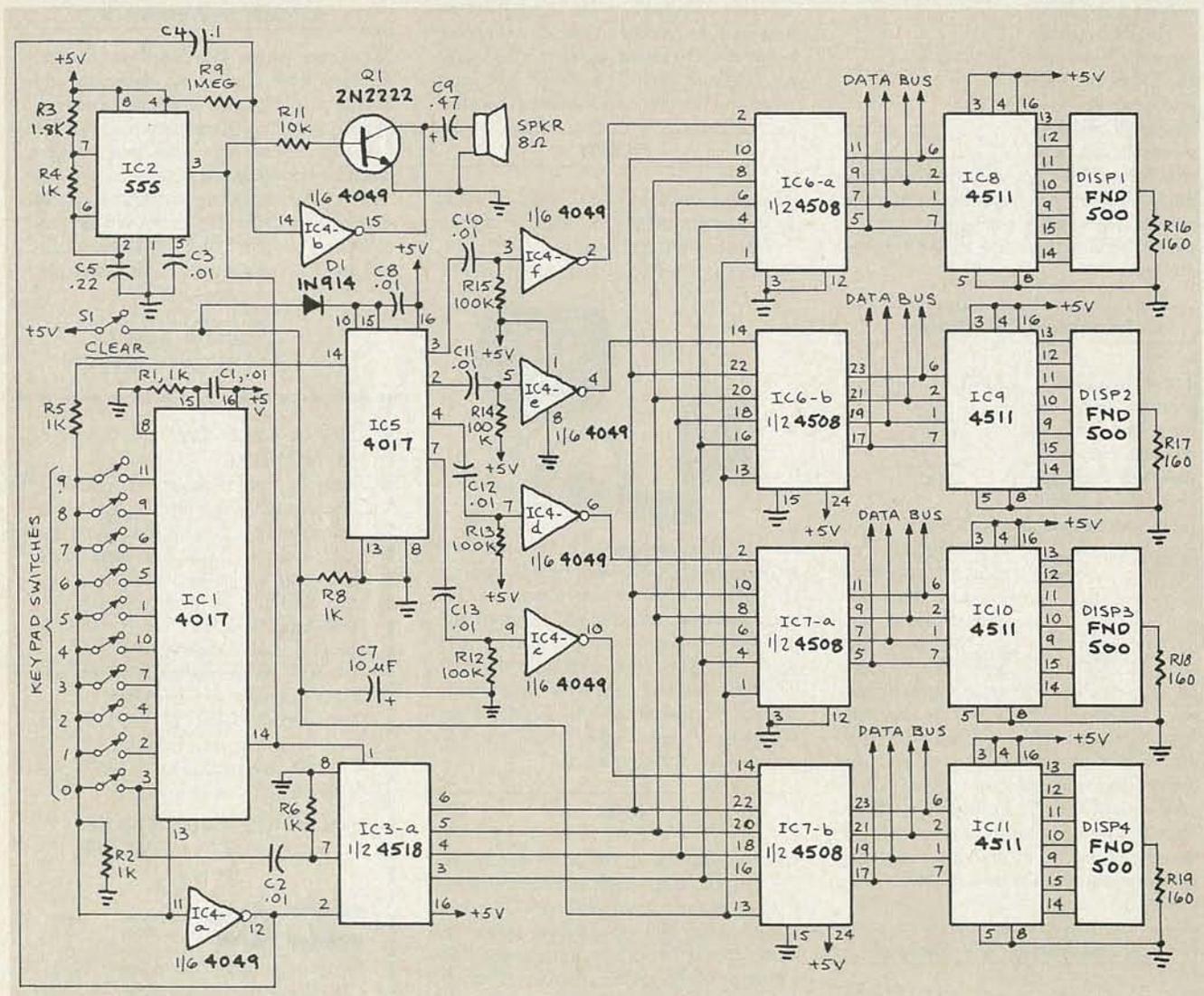



FIG. 1

A FEW MONTHS AGO IN THE "DRAWING BOARD" (see *Radio-Electronics*, April 1985), we spent some time talking about memory, and actually built a circuit to demonstrate the use of the 5101 CMOS memory

IC. Unfortunately, we goofed. We mentioned a keyboard encoder that could be used with that memory circuit, but neglected to tell you where to find it. Sorry about that.

The circuit I was referring to appeared in the "Drawing Board" columns in the February through April, 1983, issues of *Radio-Electronics*. The schematic of that circuit is shown in Fig. 1.
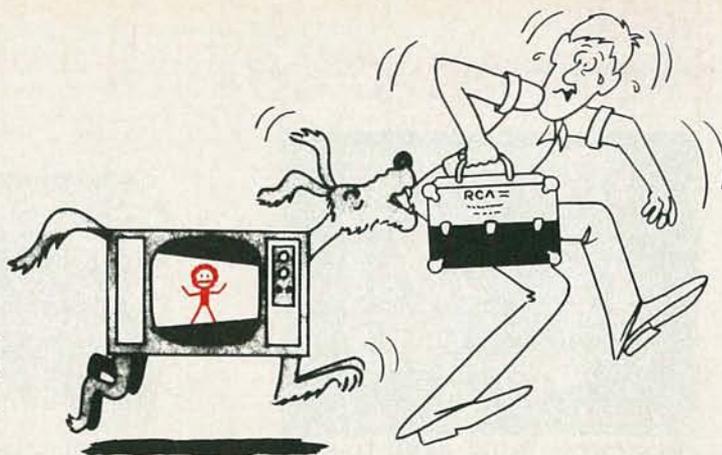
# How Many Times Do You Intend To Let "THE SAME DOG" Bite You ?



★ How many times have you worked all day long trying to diagnose the hi-voltage / LV regulator circuit of a set that is in shut down only to eventually find that a **shorted** video, color, vertical, tuner, AGC, or matrix circuit was causing the set to shut down and, to find that the hi-voltage / LV regulator circuit was working flawlessly all the time?

★ How many times have you spent the day looking for a **short** that was causing the set to shut down, only to eventually find that an **open** vertical, video, matrix circuit or, an **open** HV multiplier was to blame?

★ How many times have you worked all day on the same TV set, only to find out that the set's flyback transformer was defective?

★ How many flyback transformers have you replaced only to find that the original flyback was **not** defective?

★ How many horiz output transistors and Sony SG 613 **SCRs** have you destroyed while simply trying to figure out whether the flyback was good or bad?

★ How many times have you been deceived by your flyback "ringer"? Can you even count the number of hours that your "ringer" has caused you to waste?

★ How many times have you condemned a flyback, only to find that a shorted scan derived B+ source was causing the flyback to "appear" as though it were defective?

★ How many hours have you wasted, working on a TV set, only to find that the CRT had a dynamically shorted 2nd anode (to primary element)?

★ How many new sweep transformers have you unknowingly destroyed because a short existed in one of the scan derived B+ sources?

★ How many times have you said to yourself, "I could fix this --- thing if I could only get it to fire up long enough to lite the screen? --- without blowing an output transistor or a fuse."

★ How many additional bench jobs could you have gotten, had you been able to give an accurate, "on the spot" estimate on sets that were either in shut down or, not capable of coming on long enough for you to analyze them?

If you had been using our all new Super Tech HV circuit scanner, you would have had an accurate evaluation concerning all of the above in about one minute, at the push of **just one** single button.

It's true! Push just one test button and our HV circuit scanner will (1) Accurately prove or disprove the flyback, (2) Check for any possible shorts in any circuit that utilizes scan derived B+, (3) Check the scan derived power supplies themselves for shorted diodes and / or electrolytic capacitors, (4) Check for primary B+ collector voltage and, (5) Check the horiz output stage for defects.

Our HV circuit scanner works equally well on sets with integrated or outboard HV multipliers. It will diagnose any brand, any age, solid state TV set including Sony. The only exceptions are sets which use an SCR for trace and, another for retrace (i.e., RCA CTC 40 etc.). Our scanner will not work on these sets.

**In plain English**, our HV circuit scanner is even easier to operate than a "plain vanilla" voltmeter.

First off, when you're using a scanner, you **do not** remove the flyback in order to check it. In fact, you don't even unhook any of the wires that are connected to the flyback! All you do is:

(1) Remove the set's horiz output device, plug in the scanner's interface plug, then make one single ground connection. That's all you do to hook it up.

(2) If the primary LV supply is functional and, assuming that the emitter circuit of the horiz output stage has continuity, the scanner will tell you that it is ready to "scan" by illuminating the "ready" light, which is the white button on the test / run switch.

(3) Press the spring loaded (test) side of the test / run switch and the scanner will "look" for any type of a **short** that might exist anywhere on the secondary side of the flyback, including the HV multiplier, any circuit that relies on flyback generated B+ and, including the flyback itself (both primary and all secondary windings). It will simultaneously check for a shorted LV regulator device HV multiplier, or an open or "partially" open safety capacitor.

If a short or, an "excessive load" exists on one secondary winding, all other secondary windings will have "normal" output voltage in spite of the short. Only the shorted winding itself will have zero volts on it. This makes shorted scan derived B+ sources incredibly easy to isolate. During this test, the 2nd anode voltage is being limited to approx 5 kv by the scanner.

If a short is present, the red "flyback" light will either lite, or flash (at various speeds), depending on which type of a short exists. If no shorts exist, the "flyback" light will be green.

Assuming that the "flyback" light is green, no **shorts** exist and, it is now time (and safe), to begin looking for **open** circuits which might be causing the set to shut down due to flyback run-a-way. It only stands to reason that if no shorted conditions exist, then one (or more) circuits will have to be open, otherwise, the TV set would be working!

(4) Now that you know that no **shorts** exists, push the "run" side of the test / run switch (the side that latches). Provided all of the other circuits in the TV set are functional, the scanner will now put a picture on the set's CRT screen that has full vertical and horiz deflection, normal audio, video and color.

Keep in mind that during this test, your scanner is:

- (1) Circumventing all horiz osc/driver related shut down circuits,
- (2) Limiting the set's 2nd anode voltage to approx 20-25 kv,
- (3) Substituting the set's horiz osc/driver circuit and, as a result, eliminating any need that the set might have for an initial start up or B+ resupply circuit for the osc/driver.

Wait about 15 seconds for its filaments to warm up, then look at the CRT. Any circuits that are "**open**" will now produce an obvious symptom on the screen. Because the scanner has circumvented all of the set's shut down features, you can now use your old reliable "symptom to circuit analysis" technique to troubleshoot the problem, i.e., if the picture has no blue in it --- repair the blue video or blue matrix circuit. If the picture has only partial vertical deflection --- repair the vertical circuit, and so on. The scanner has effectively removed all of the stumbling blocks that would normally prevent you from diagnosing the problem. i.e., start up and shut down features, and allowed you to repair the TV set by using conventional techniques.

When you're using a scanner, all start up, shut down, dead set problems are easy to solve. You don't need anyone to tell you just how difficult these problems can be for those who don't have a scanner!!

## ONLY \$495.00

VISA, MASTERCHARGE, C.O.D. ORDERS WELCOME

DIEHL ENGINEERING • 6004 Estacado Ln. • Amarillo, TX 79109

PHONE (806) 359-1824 or (806) 359-0329

Phone Orders Welcome

Since the Scanner only has two buttons to press, most technicians never need it but, our "Hot Line" is available to assist new owners in the operation of their scanner. Phone (806) 359-0320.

# Radio-Electronics mini-ADS



**FREE CATALOG OF HARD-TO-FIND TOOLS** is packed with more than 2000 quality items. Your single source for precision tools used by electronic technicians, engineers, instrument mechanics, schools, laboratories and government agencies. Also contains Jensen's line of more than 40 tool kits. Send for your free copy today! **JENSEN TOOLS INC., 7815 46th St., Phoenix, AZ 85044. (602) 968-6231.**

CIRCLE 115 ON FREE INFORMATION CARD



**SPECIAL PRICE FOR RADIO ELECTRONICS SAVE \$300 ON 24" AND \$400 ON 30".** New HD TRIOK SHEAR-BRAKE-ROLL multi-purpose sheet metal machine now w/6" male dies & removable female dies. Thousands used worldwide industry/government/education. R&D prototypes in-house at 1/3rd cost. **PACIFIC ONE CORP., Ste K50 (714) 645-5962, 513 Superior Ave. Newport Beach, CA 92663 TELEX 4996168 POC NPT**


CIRCLE 118 ON FREE INFORMATION CARD




**THE WIRELESS TELEPHONE TRANSMITTER** model WTT-20 is only the size of a dime, yet transmits both sides of a telephone conversation with crystal clarity. Completely automatic Uses power from the telephone line itself. Never needs a battery! Up to ¼ mile range. Use with any FM radio. Complete kit only **\$29.95.** Tax included.

**FREE SHIPPING. DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 241-2827.**

CIRCLE 127 ON FREE INFORMATION CARD

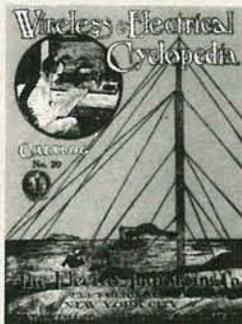


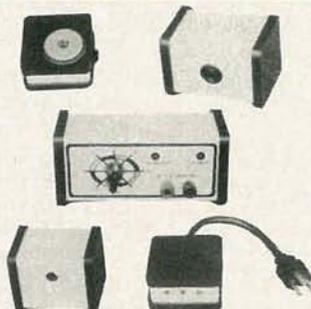**ELECTRO IMPORTING CO. CATALOG.** This reprint of the historic 176-page catalog No. 20 gives you an accurate look at the state of electronics in 1918. Contains everything from a Zinc Spark Gap to a 1000-Mile Receiving Outfit. You can get your own copy of this modern antique, profusely illustrated, for only **\$4.95** plus \$1.00 P&H. Order yours from **R-E BOOKSTORE, Radio-Electronics, 200 Park Avenue South, New York, NY 10003.**



**UNIQUE ELECTRONIC KITS**—Kits come complete with materials required to build a professional looking product that you will be proud of. Kits also come with **attractive enclosures.** Some exciting kits offered are: Fiber Optics **\$29.95**, Touch Control and Switch **\$24.95**, Wireless Microphone **\$19.95**, Guard-All Jr. Security Alarm **\$19.95**, Outlet Tester **\$9.95**, Power Supply PS-1 **\$39.95**, and more. **ALARMS, KITS & DEVICES, P.O. Box 200, Fredonia, PA 16124. (412) 962-9231.**


CIRCLE 269 ON FREE INFORMATION CARD

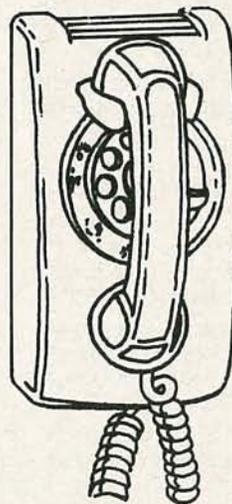
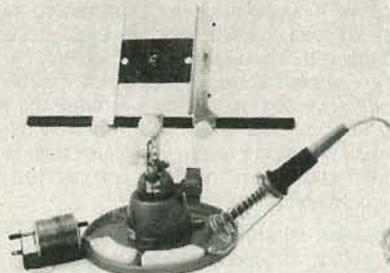
## CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$745.00 per each insertion.
- Reaches 217,425 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call **212-777-6400** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.



**MODEL 324 PANAVISE ELECTRONIC WORK CENTER.** This handy work center is convenient yet economical. Angle of solder iron holder maintains iron at proper heat and solder holder self centers wire. Sturdy, stable, yet easily mobile, the Electronic Work Center keeps everything right at hand. (Combines 315, 300, 312, 371). **\$51.95** (Solder and solder iron not included.) **PANAVISE PRODUCTS, INC., 2850 East 29th Street, Long Beach, CA 90806-2399. Telephone (213) 595-7621 Telex 18-2135.**

CIRCLE 270 ON FREE INFORMATION CARD



**DELTA DUAL TRACE OSCILLOSCOPES WITH PROBES** DX5020 20MHz **\$379.95.** Built in component tester 5MV to 20V/DIV 0.2 microsec. to 0.5s/DIV. Risetime less than 17ns one year limited warranty. Also available DX5035 35MHz **\$527.00** DX5045 45MHz **\$789.95** DX5015S 15MHZ A/C D/C **\$479.95.** CA. residents add 6.5% tax. Shipping \$8.50. Money orders, checks accepted. **DELTA DYNAMIC INC., 20955 E. Lycoming St., Walnut, Calif. 91789. Tel. (714) 594-7131. Telex: 503749 DELTAX.**

CIRCLE 252 ON FREE INFORMATION CARD




**APPLIANCE REPAIR HANDBOOKS**—13 volumes by service experts, easy-to-understand diagrams, illustrations. For major appliances (air conditioners, refrigerators, washers, dryers, microwaves, etc.), elec. housewares, personal-care appliances. Basics of solid state, setting up shop, test instruments. **\$2.65 to \$5.90 each.** Free brochure. **APPLIANCE SERVICE, PO Box 789, Lombard, IL 60148. 1-(312) 932-9550.**

CIRCLE 84 ON FREE INFORMATION CARD



**MEGURO (JAPAN) 20MHZ OSCILLOSCOPE** \$375.00 Dc-20 MHz, 5mv/div, 2 Channel, Dual Trace 6" square internal graticule CRT. Also: 35 MHz Oscilloscope with delayed sweep **\$559.00.** Signal Generators from **\$1,186.00,** Wow Flutter Meter **\$999.00.** Add **\$10.00** per unit for UPS & C.O.D. charges. To order call collect: **DIPLOMAT INTERNATIONAL, 2900 Townsgate Road, Suite 100, Westlake Village, CA 91361, (805) 495-8858.**

CIRCLE 253 ON FREE INFORMATION CARD

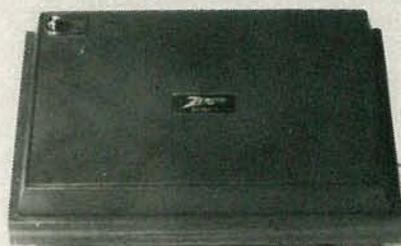


**ZENITH SSAVI DESCRAMBLERS** only **\$169.** Gated Pulse **\$189;** Sinewave **\$199** each. Reconditioned original equipment for UHF chs. 23,27,31,38,51,54,57,68, etc. Quantity discounts. Surplus TV equipment: Jerrold SB-3, Oak N-12, Zenith Z-Tac, Hamlin 1200, etc. Catalog **\$1.** 10 day satisfaction guarantee & 90 day warranty. **AIS SATELITE, P.O. Box 1226-E, Dublin, PA, 18917. 1-800-643-2001 or 215-249-9411.**

CIRCLE 271 ON FREE INFORMATION CARD
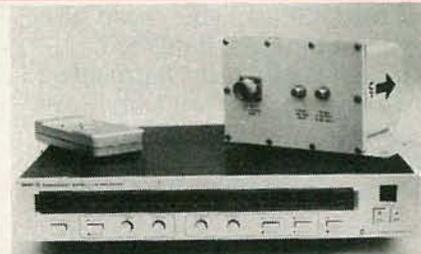
## CALL NOW AND RESERVE YOUR SPACE


- 6 × rate \$745.00 per each insertion.
- Reaches 217,425 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call **212-777-6400** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.




**SATELLITE TELEVISION RECEIVER SEMIKIT** with dual conversion downconverter. Features infrared remote control tuning, AFC, SAW filter, RF or video output, stereo output. Polorator controls, LED channel & tuning indicators. Install six factory assembled circuit boards to complete. **Semikit \$400.00.** Completed downconverter add **\$100.** Completed receiver and downconverter add **\$150.** **JAMES WALTER SATELITE RECEIVER, 2697 Nickel, San Pablo, CA 94806. Tel. 415-724-0587.**

CIRCLE 124 ON FREE INFORMATION CARD

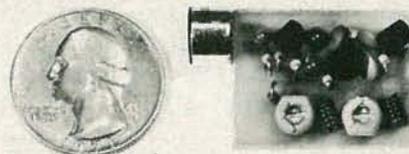

**THE MOST EXCITING KIT YOU WILL EVER BUILD** The model WAT-50 miniature FM transmitter uses a 4-stage circuit NOT to be confused with a simple wireless microphone. Up to 1 mile range. So sensitive, it will pick-up a whisper 50 feet away! Use with any FM radio. Complete kit only **\$29.95** tax incl. **FREE SHIPPING. DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 241-2827.**

CIRCLE 127 ON FREE INFORMATION CARD

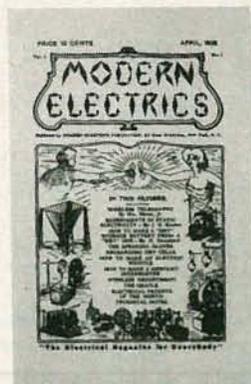


**MODERN ELECTRICS.** Miniature souvenir of the first publication ever produced by Gernsback Publications. This issue appeared in April 1908—just 75 years ago. You can own your own reprint of this unique first edition for just **\$2.50** plus 75¢ P&H. It's available from **R-E BOOKSTORE, Radio-Electronics, 200 Park Avenue South, New York, NY 10003**



**SUBSCRIPTION TV MANUAL.** This information packed book details the methods used by subscription TV companies to scramble and descramble video signals. Covers the Sinewave, Gated Pulse, SSAVI system, and the methods used by most cable companies. Includes circuit schematics, theory, and trouble shooting hints. **Only \$12.95** plus **\$2.00** first class P&H. **ELEPHANT ELECTRONICS INC., (formally Random Access) Box 41770-R, Phoenix, AZ 85080**

CIRCLE 120 ON FREE INFORMATION CARD

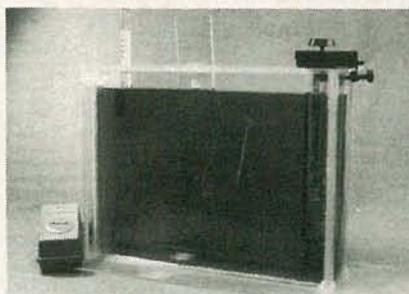

**ETCH HIGH QUALITY PC BOARDS IN MINUTES!** PROTO-ETCH is an automatic etching tank for boards up to 8 × 9 inches. Complete, easy to assemble kit includes thermostatic heater, circulating pump, hose, board clamp, precut parts, assembly and operating instructions, and more. An incredible value for the electronics enthusiast or prototyping shop at **\$74.95** ppd. **QUINTEC ELECTRONICS, 444 Lincoln Blvd., Dept. 225A, Venice, CA 90291. (213) 306-5354.**

CIRCLE 284 ON FREE INFORMATION CARD

Let's begin by looking at the major functions of the keyboard encoder. A 555, IC2, is set up to oscillate at a frequency of about 2 kHz. That signal is used to drive Q1 and SPKR, which provides an aural key-press indication. The 2 kHz signal also drives IC1, a 4017 decade counter, whose 1-of-10 outputs appear on pins 1-7 and 9-11. When one of the switches is pressed, the output from the 4017 is fed through IC4-a to the ENABLE input of IC3-a. Since IC3-a is also fed by the 2 kHz clock signal, that IC "freezes" at the current count, and its BCD output is presented to the inputs of the 4508 dual four-bit latches.

The output from IC1 is also fed through resistor R5 to IC5, another 4017, which acts as a digit selector. Each time IC5 is clocked, its output increments by one, and that provides a signal to strobe the "frozen" BCD value into the appropriate latch IC. Since we're only driving four digits, the Q4 output of IC5 (pin 10) is fed to that IC's RESET input (pin 15).

After the BCD data has been latched in IC6 or IC7, the data is presented to a 4511 seven-segment display decoder/driver. The output of that IC is fed to the displays. So the value of the first key pressed will appear in DISP1, with following entries appearing in DISP2, DISP3, and DISP4; and the next entry will appear in DISP1, and so on.


Note that we use only one resistor for current limiting in each display. Since different digits have different numbers of "on" segments, not all digits will glow with equal brightness. If that bothers you, just insert one resistor between each 4511 output and each FND500 input. That's seven resistors per display, and 28 total. You may use any low-current, common-cathode seven-segment LED for DISP1-4; you could also use discrete LED's, if desired.

Capacitors C1 and C8 provide a power-on-reset function, and IC4-b is used to turn the speaker off after about 1/10-second. The 4508 latches are three-state types,

and that allows the corresponding lines from each digit (labeled "Data Bus") to be connected together and tied to any external data bus—such as our memory-demonstration circuit.

If you're interested in displaying more digits (as many as ten), simply duplicate the group of components IC4-f, IC6-a, IC8, and DISP1, as well as C10 and R15. To add another digit, connect the capacitor to the Q4 output on IC5, and drive its RESET input with the Q5 output. You could increase the number of digits beyond ten by driving an additional 4017 from the CARRY output of IC5.

R-E

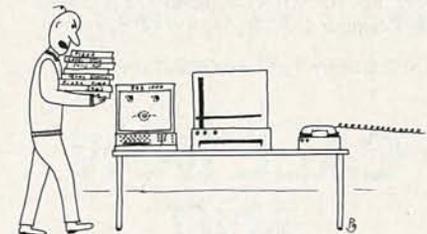

"One more stunt like this, and I'll cut your modem cord!"

QUALITY COMPONENTS - NOT MAIL ORDER "SECONDS"

Send \$1.00 postage and handling for FREE COMPLETE CATALOG which includes coupon for \$1.00 OFF purchase.


ARIES ZERO INSERTION FORCE SOCKETS -



cam actuated, true zero insertion - tin plated solder tail pins - capable of being plugged into dip sockets, including wire wrap.

Stock No.	No. Pins	1-9	10-49	50
11055	24	4.98	\$4.35	\$3.90
11056	28	5.15	4.50	4.05
11057	40	6.81	5.95	5.35
11058	64	12.02	10.50	9.45

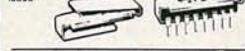IC-KOOLERS™ from UNITRACK™ dissipate over 2 watts of heat from IC's, producing longer life and better performance... just push IC-Kooler on - heat is collected from top and bottom of IC and dissipated. Won't shake loose!



WILD ROVER Touch switch capsule. Operating motion is 005" without the use of a levered arm. Extremely fast on and off with low noise. Normally open - rated 115 VAC, 1.6 amp-30 miliohm resistance - 615 radius by .160 thick.

Stock No.	1-9	10 & Up
12098	\$1.42	\$1.28

SCREW MACHINED SOCKET PINS, loose, packaged in bags of 100. Stock No. 11310 is solder tail with gold collet tin shell. Stock No. 11311 is wire wrap with gold collet gold shell.

Stock No.	Description	1 Bag	5 Bags	10 Bags
11310	Bag of 100 solder tail pins	\$ 4.95	\$ 4.45	\$3.95
11311	Bag of 100 wire wrap pins	11.95	10.75	9.50

3 X 4 Elastomeric Keyboards Each keyboard has a p.c. board, elastomeric pad with contacts, ABS bodies and double shot molded keys. Max rating: 12 VDC @ 20mA. Contact Res: less than 500 ohms. Bounce: less than 10 m sec.

Stock No.	Operating Force	Travel	Price
11251	120-140g	2.0-2.5mm	\$4.35 \$4.50
11292	601-60g	1.5-1.5mm	3.95 3.60

TI WIRE WRAP SOCKETS

Tin plated phosphor bronze contact - 3 wrap

Stock No.	No. Pins	1-99	499	500
11301	8	\$ .40	\$ .36	\$ .30
11302	14	.59	.54	.45
11303	16	.64	.58	.48
11304	18	.73	.66	.55
11305	20	.99	.90	.75
11306	22	1.12	1.02	.85
11307	24	1.25	1.14	.95
11308	28	1.52	1.38	1.15
11309	40	2.05	1.86	1.55

TI LOW PROFILE SOCKETS

Tin plated copper alloy 688 contact pins with gas tight seal.

Stock No.	No. Pins	1-24	25-99	999
11201	8	\$1.10	\$ .09	\$ .99
11202	14	.14	.13	.12
11203	16	.16	.15	.14
11204	18	.18	.17	.15
11205	20	.20	.18	.16
11206	22	.22	.20	.18
11207	24	.24	.22	.20
11208	28	.28	.26	.25
11209	40	.40	.37	.33

SUB CUB I and SUB CUB II are high quality, complete LSI Counter Modules with LCD readout. Modules plug in p.c. board (Stock No. 51071). Complete function evaluation kit (Stock No. 51070) contains: p.c. board, 4.5V battery and variable frequency oscillator to supply train of count pulses. Stock No. 51070 has LATCH, RESET and TEST functions (3 buttons). P.C. board unplugs for bread-board work.

6 Digit LSI Counter Modules with LCD Readouts and Associated Mounting Assemblies

Stock No.	Description	Price
51070	Complete Function Evaluation Kit (includes batteries but does not include display counter) Mounting P.C. Board only	7.50
51071	SUB-CUB I display counter module only	18.00
51072	SUB-CUB II display counter module only	24.00
51073	Panel Bezel	12.00
51074	Evaluation Kit for SUB-CUB II (does not include SUB-CUB II counter module) DATA SHEET	.25

SINGLE ROW SOCKETS

Strip of 25 collet sockets/pins - mount odd-center components easily. Gold plated contacts.

Stock No.	1-99	100	500	1000
10850	\$1.09	\$ .90	\$ .82	\$ .72

OPCOA

Single Digit Displays - Common Cathode

Stock No.	Color	1	100
12082	Red	\$1.12	\$ .99
12085	Green	1.84	1.63
12087	Yellow	1.92	1.70
12089	Orange	2.08	1.84

The Battery Just Wrap™ Tool New battery powered tool wraps insulated wire around .025" square posts without need for pre-cutting and pre-stripping. Complete with bit and 100 ft. 30 AWG wire.

Stock No.	Description	Price
13340	Battery just-wrap tool with bit and 100 ft. 30 AWG wire	\$59.95
13341	Replacement bit	10.35
13342	100 ft. blue replacement wire	7.54
13343	100 ft. white replacement wire	7.54
13344	100 ft. yellow replacement wire	7.54
13345	100 ft. red replacement wire	7.54

PIN FORMING TOOL puts IC's on their true row to row spacing. One side is for .300 centers. Flip tool over for devices .600 centers. Put device in tool and squeeze.

Stock No.	Price
Hand Tool	11059 \$12.95
NEW! ANTI-STATIC MODEL	10200 \$14.95

OPTEL LCD's with pins

Stock No.	Description	1	10
47005	3 1/2 dig. 5"	\$ 5.95	\$ 5.50
47006	4 dig. 5"	5.95	5.50
47007	4 dig. 7"	11.90	11.00

OK MACHINE AND TOOL

IC INSERTION/EXTRACTION KIT Includes DIP IC extractors and inserters to accommodate all ICs from 14 to 40 pins. Tools that engage conductive surfaces are CMOS safe and include grounding lugs. Stock No. 13309 \$41.34

SOCKET WRAP ID Dip socket-sized plastic panels with numbered holes in pin locations. Slip onto socket before wire wrapping to identify pins. Also write on them for location, IC part number, function, etc. Simplifies initial wire wrapping, troubleshooting and repair \$1.95 per pack.

Stock No.	Reference	Price
23010	280 CPU	\$5.95
23011	8080A/8085A	5.95
23012	6502 (6513)	5.95
23013	8048 and relatives	5.95
23014	547600 TTL Phones	5.95
23015	Basic Algorithms	5.95
23016	8086/8080A	5.95
23017	How to generalize from a sample	2.95
23018	Wordstar	5.95

Scotchflex™ Breadboard Systems Basic Kit comes with 24 various Dual Sockets, 40 various Plug Strips, wire and tools. Kit can be used with any of the six boards.

Stock No.	Description	Price
03500	Basic Kit	\$79.95
03511	Basic board, 4.5 x 5.5	19.50
03506	Intel SBC-8010 Board, 12 x 6.75	64.95
03507	Motorola M-6800 Board, 9.75 x 6	42.95
03508	S-100 Board, 10 x 5.3	36.95
03509	Z-80 Board, 7.7 x 7.5	39.95
03510	Eurocard Board, 6.3 x 3.9	21.95

SINTEC CO. 28 8th St., Box 410 Frenchtown, NJ 08825 TOLL 800-526-5960 FREE in NJ (201) 996-4093



W accept VISA, MC, C.O.D. CHECK, or M.O. \*INCLUDE SHIPPING CHARGES 0 to \$100 - \$3.00 \$100 to \$250 - \$4.00 over \$250 - \$5.00

CIRCLE 73 ON FREE INFORMATION CARD

# ROBOTICS



MARK J. ROBILLARD  
ROBOTICS EDITOR

## Ultrasonic vision

FOR A ROBOT TO EXHIBIT EVEN A modicum of intelligence, it needs some type of feedback mechanism between the "thinking" part and the "doing" part. Without some type of feedback, the "thinker" can't adjust the actions of the "doer" in response to changes in its environment.

The most useful form of feedback for human beings is visual. Machine vision, however, is limited by current technology in its ability to resolve details and in its ability to estimate distances.

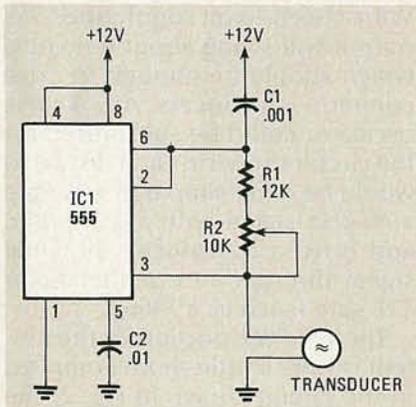


FIG. 1

There are several dozen companies now selling machine-vision systems to industrial manufacturers. Those systems are generally used to inspect finished goods. There are a few companies selling devices that will help a mobile robot get around in a cluttered room. With that type of vision, a robot can see what it is gripping, where it is going and where it has been.

Human beings have a crude, built-in distance measuring system that makes use of the eyes as well as stored knowledge of how

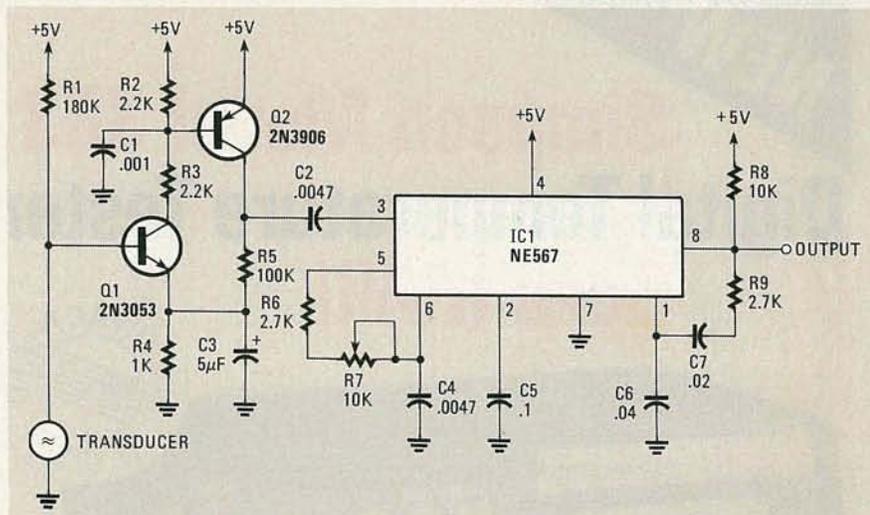


FIG. 2

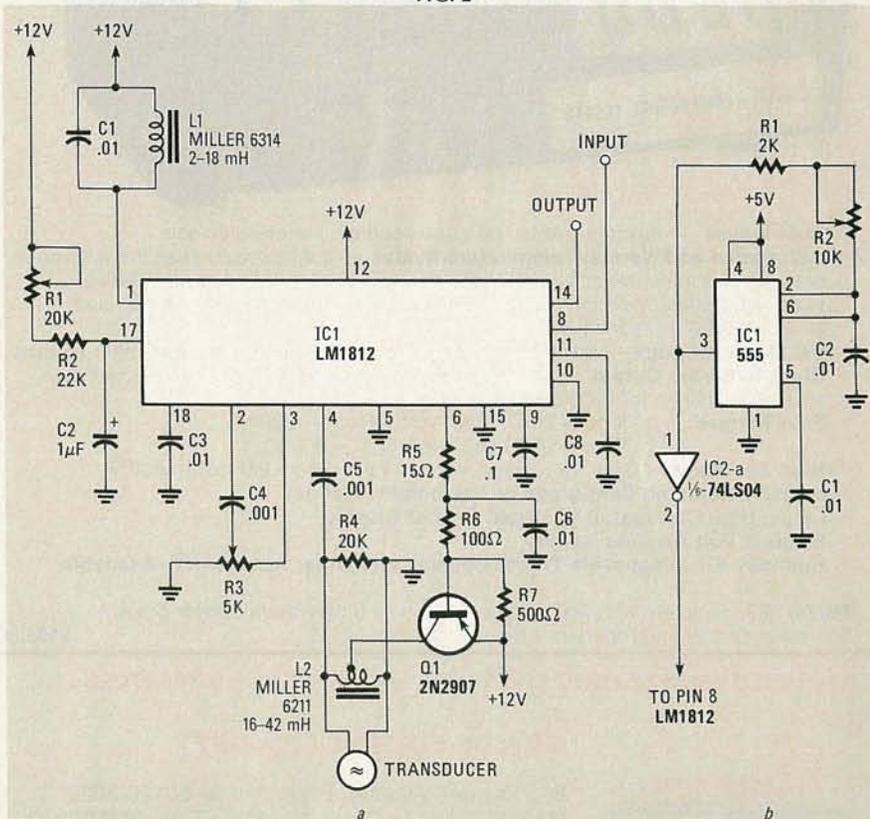


FIG. 3

an object looks at different distances. We then compare the known image to the one we are presently encountering and *voilà*—we obtain a rough estimate of the object's distance. That is the method used by systems that inspect parts on a finished-goods assembly line. We could apply that method to a robot system, but that would require auto-focusing lenses and complex image-analysis algorithms in the controlling electronics. However, there is a

simpler and more economical way to obtain distance information: *ultrasonic ranging*. That method is frequently more accurate than light-wave systems.

### Ultrasonics theory

In a typical ultrasonic ranging application, an ultrasonic transmitter starts a timer as it emits a short burst of 40-kHz sound waves through its transducer. Those sound waves spread out as they travel through free air. When they

strike an object in their path, some of the sound is deflected back toward the transducer, which now acts as a receiving device, like a conventional audio microphone. The received sound waves are sent to a discriminator circuit that stops the timer.

The value in the timer is proportional to the length of time it took the sound waves to travel to the object and return to the origin. We can determine the distance (D) from the period measured by the timer (T) by using the classic formula,  $D = V/T$ . V here stands for velocity, and is simply the velocity of sound waves in air, about 13,080 inches per second. Basically that's all that's needed to measure distance. So let's look at some practical implementations of both transmitters and receivers.

### Ultrasonic circuits


A simple 40-kHz transmitter is shown in Fig. 1. The 555 is a very inexpensive eight-pin timer IC configured as an astable multivibrator oscillating at a frequency of 40 kHz. (That frequency can be adjusted by potentiometer R2.) With a twelve-volt supply, the 555's output will swing about ten volts, which should be enough to drive common transducers. Any 40-kHz oscillator could be substituted for the circuit shown in Fig. 1. In fact, it would be quite simple to generate a 40-kHz signal with a computer, and drive a transducer with that signal through an open-collector TTL gate (such as a 7406).

The receiver portion of the system is only a little more complex. In the circuit shown in Fig. 2, the received signal is amplified by a discrete transistor amplifier, and then applied to a tone-decoder NE567. That IC, a phase-locked-loop contains its own internal oscillator that must be adjusted to match the transmit frequency. The NE567 has a comparator that will send the output high when it detects an incoming signal equal in frequency to its internal oscillator.

The circuit shown in Fig. 3-a uses a single IC specially developed by National for use as an ultrasonic transceiver. Using such a device allows you to use a single transducer for both transmit and re-

*continued on page 108*
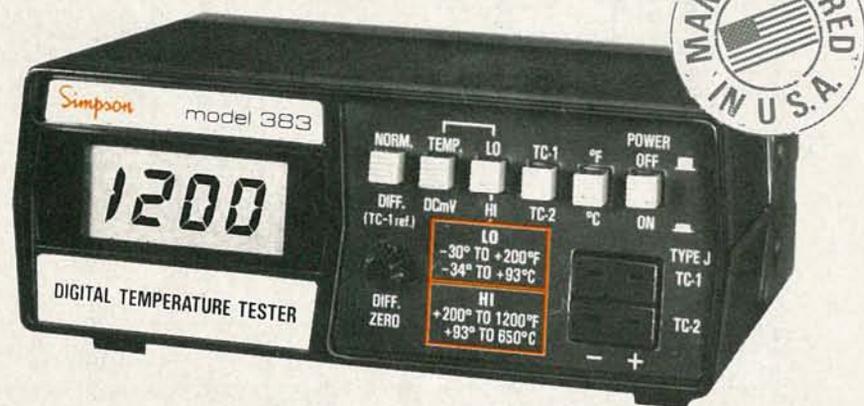
# NEW Simpson Model 383 Digital Temperature Tester Does It All!



- **Dual Inputs** — measure two temperature sources, switch-selectable
- **Differential and Normal Temperature Modes** — automatically read the difference between two temperatures or each separately. Provides for accurate relative temperature determinations. Ideal for heating and air conditioning service and environmental monitoring
- **DC Millivolt Range** — quick check of thermocouples, flame rods and other sensors
- **Chart Recorder Output** — provides 1 mV DC per degree F or C output with low source resistance for recording/controlling applications
- **Four Ranges:** -30°F to +200°F and +200°F to +1200°F  
-34°C to +93°C and +93°C to +650°C
- **High Accuracy** — 0.2% of reading + 1°C (1.8°F), from 0°F to +1000°F
- **Switch-Selectable Centigrade or Fahrenheit Readout**
- **Large, High-Contrast, 0.5" Liquid Crystal Display**
- **Single 9 Volt Alkaline Battery**
- **Humidity Kit, Disposable Thermocouples and Other Accessories Available**

Model 383, complete with test lead set, 4' J-type temperature sensor probe, 9 V alkaline battery and operator's manual, Cat. No. 12415

**\$195.00**

AVAILABLE FROM LEADING ELECTRONICS/ELECTRICAL DISTRIBUTORS



### SIMPSON ELECTRIC COMPANY

853 Dundee Avenue, Elgin, Illinois 60120-3090  
(312) 697-2260 • Telex 72-2416 • Cable SIMELCO

# FREE FIVE YEAR WARRANTY PLUS THE LOWEST HITACHI PRICES

## EQUALS **Joseph** electronics VALUE

### 20 MHZ

#### HITACHI V222

- Dual Trace
- 1MV/Div. Sens Rectangular 6" CRT with Internal Graticule
- Auto Focus
- Vert Mode Triggering
- DC Offset
- Much More
- Includes Probes and 5 Year Warranty



Joseph  
electronics


**\$521<sup>00</sup>**

(REG. \$715.00)

### 40 MHZ
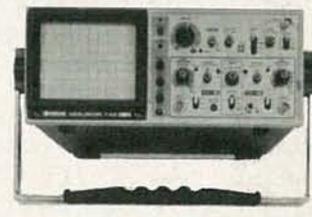
#### HITACHI V422

- This thin, light and compactly designed scope offers the same outstanding features as the V222 except greater bandwidth
- Includes Probes and 5 Year Warranty



Joseph  
electronics


**\$671<sup>00</sup>**

(REG. \$925.00)

### 60 MHZ
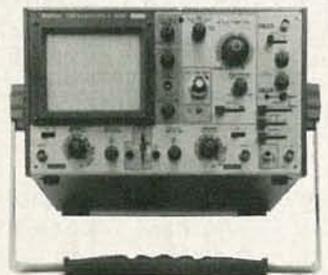
#### HITACHI V650F

- Dual Trace
- Delay Sweep
- 1MV Sens.
- Rectangular 6" CRT with Internal Graticule
- 10KV Acc.
- Triple Trace
- Channel 1 Output
- Much more
- Includes Probes and 5 Year Warranty



Joseph  
electronics


**\$931<sup>00</sup>**

(REG. \$1195.00)

### 100 MHZ
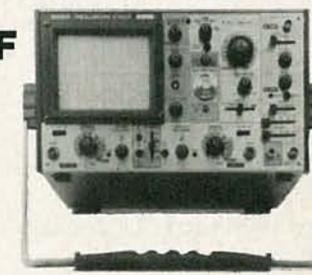
#### HITACHI V1050F

- Quad Trace
- Delayed Sweep
- 500uv Sens.
- Rectangular 6" CRT with Internal Graticule
- 20KV Acc.
- Auto Focus
- 10X Mag.
- And much more
- Includes Probes and 5 Year Warranty



Joseph  
electronics

**\$1241<sup>00</sup>**

(REG. \$1595.00)

FOR SIMILAR SAVINGS ON THE COMPLETE HITACHI LINE  
AND MORE THAN 100 OTHER MAJOR SUPPLIERS CALL

**800-323-5925** In Illinois **312-297-4200**

ORDER HANDLING CHARGES

VALUE	ADD
\$0-999	\$10.00
\$1000-2499	\$15.00
\$2500-UP	\$20.00



Joseph  
electronics

8830 N. Milwaukee, Niles, Illinois 60648

# DRAWING BOARD



ROBERT GROSSBLATT  
CIRCUITS EDITOR

## Clever hexadecimal display circuits

I HAVE TO TAKE MY HAT OFF TO YOU people out there. I've been telling everybody here that you are the smartest readers of this magazine, and you've proven me right once again. A few months ago I asked you to come up with a circuit that would drive ordinary seven-segment LED's and give hexadecimal outputs (0 through 9 and A through F) for binary inputs. To tell the truth, I expected no more than a couple of letters. Boy, was I wrong!

So far I've gotten ideas from over 100 of you, containing such a variety of circuits that it took me weeks to sort through them all. Obviously, many of you are interested in how to display hex values, so I'm going to take a month off from our discussion of the Z80 and devote this month's column to reporting some of the solutions. But before I go any further, let me remind you that I can't mention everybody's name or describe everybody's solution. Basically, the solutions I've received fall into three categories:

- A. Using special display IC's.
- B. Using elaborate decoding logic.
- C. Using PROM's for decoding.

### Dedicated IC's

There are several dedicated IC's that do the job, and, to tell the truth, I was somewhat surprised that more of you didn't suggest that solution. One person who did was Michel Peloquin from Canada. He suggested using the Motorola MC14495, which is a display decoder/driver that does just what we need: It decodes four-bit binary data into the correct output to

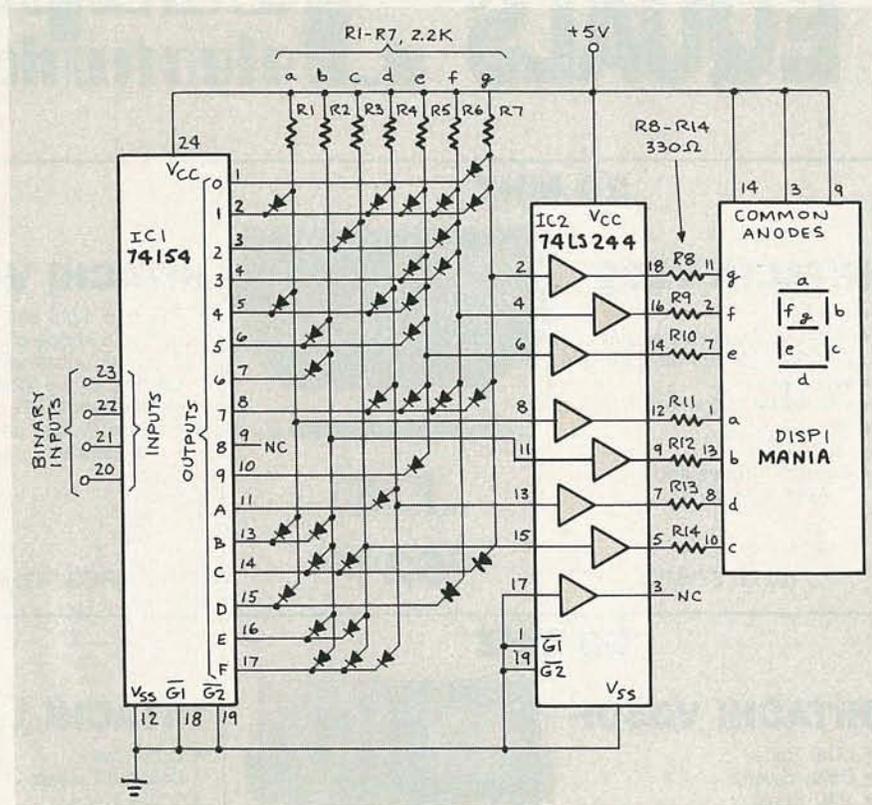


FIG. 1

drive seven-segment, common-cathode LED displays. Using that IC is no more complicated than using a 4511, or other common devices. The MC14495 is a CMOS device, so it may be used with supply voltages ranging from 4.5 to 16 volts DC. In addition, it has built-in current-limiting resistors, making the MC14495 an elegant solution to our problem.

So, you may well ask, if the MC14495 is so wonderful, why not use it? There is no problem when buying it in large quantities. But trying to find it in hobbyist quantities is murder. None of the regular mail-order houses advertise

it, and when you do find it, the price is too steep to make using the 14495 worthwhile.

A special thanks to Bob Milton for letting me know about the Fairchild 9368, another one-IC solution. The 9368 also drives seven-segment, common-cathode displays, but has no built-in current limiting resistors. However, it is easily available, and costs just over \$3.00 in small quantities.

### Gates-only solutions

I was really impressed by some of the gates-only designs you sent in. Doing a gates-only solution to a *continued on page 101*

# Name Brands at Lowest Cost

# COMPARE BEFORE

**OUR PRICES**

**YOU BUY**

**A.W. SPERRY 20 MHz DUAL TRACE SCOPE**



Probes included

- Special built-in Component Checker circuit allows voltage vs. current characteristics of de-energized circuits to be viewed. Saves hours locating defective components.

Model 620-C **\$399<sup>95</sup>**

**HITACHI 35 MHz 1MV/DIV DUAL-TRACE PORTABLE SCOPE**



Probes included

- Thin, light, compact design. • Features large 6" rectangular, internal graticule CRT. • % calibrations. • Autofocus. • Photographic bezel.

Model V-355 **\$599<sup>95</sup>** (Reg. \$899.95)

**B&K 60 MHz TRIPLE-TRACE SCOPE**



Probes included

- 1 mV/div sensitivity • 22 calibrated sweeps • Rectangular CRT with internal graticule • Delayed sweep/dual time base.

Model 1560 **\$899<sup>95</sup>** (Reg. \$1150)

**HITACHI 100 MHz QUAD-TRACE DELAYED SWEEP SCOPE**



Probes included

- Low halation dome mesh 6" rectangular CRT with internal graticule. • 500 uV/div high sensitivity design. • Delayed sweep function.

Model V-1050F **\$1249<sup>95</sup>** (Reg. \$1980)

**FLUKE HANDHELD, 4 1/2 DIGIT MULTIMETER**



- RMS measurements for AC signals to 100 kHz. • Frequency to 200 kHz. • Resistance to 300M ohm. • .04% Accuracy.

Model 8060A **\$325<sup>00</sup>** (Reg. \$349)

**SIMPSON METER AC/DC VOLTS/AMPS RESISTANCE**



- 28 time proven ranges • Direct dial reading • Multi-purpose test leads with combination probe and alligator clips

Complete with batteries, test leads, manual

Model 260-7 **\$109<sup>95</sup>**

**XCELITE ATTACHE TOOL KIT**



- Contains 53 individual tools, 31 Series 99 interchangeable screwdriver/nutdriver blades and handles, and 2 specialized screwdriver/nutdriver sets and kits. Case (19 1/2 x 13 1/2 x 6 3/4).

(Reg. \$499.95) Model TCM-100/ST **\$349<sup>95</sup>**

**UNGAR HOT VAC DESOLDERING SYSTEM**



**FREE UNGAR 9100 (\$399.95 value) with purchase of Model 4000-U**

- Self-Contained, Super-Quiet Air Pump. • Variable solid-state control adjusts tip temperature from 500° - 1000° F.
- Transient spikes fully suppressed for safe desoldering of voltage-sensitive components.

Model 4000-U **\$399<sup>95</sup>** (Reg. \$599.95)

**WELLER WTCPR CONTROLLED OUTPUT SOLDERING STATION**



- Unique 'Closed Loop' method of controlling maximum tip temperature protects temperature sensitive components • Grounded tip protects voltage and current sensitive components.

Model WTCPR **\$74<sup>95</sup>** each  
4 or more stations \$72.95 each

**SEND FOR OUR LATEST FREE CATALOG**



**Fordham**  
HAMMER SPECIAL

**WELLER SOLDERING STATION**



- Variable tip temperature from 350° to 850° F.
- Plug-in soldering irons. • Large digit LED display for accurate setting.

Model EC2000 **\$149<sup>95</sup>**

# 800-645-9518

# Fordham

260 Motor Parkway, Hauppauge, NY 11788

AMERICAN EXPRESS MasterCard VISA  
(Telephone Orders Accepted)  
In NY State:  
**800-832-1446**

NOVEMBER 1985

# STATE OF SOLID STATE



ROBERT F. SCOTT  
SEMICONDUCTOR EDITOR

## Surface-mount technology comes of age.

PRINTED-CIRCUIT BOARDS WERE WIDELY used before semiconductors began to appear in consumer-electronics products. Components were almost invariably mounted on the top of the board, with terminal leads protruding through holes to the underside of the board where components were interconnected. That technique remained an international standard as semiconductors replaced vacuum tubes.

With the advent of digital watches, business-card calculators, and portable personal computers, engineers were hard-pressed to cram more circuitry in less space. In addition, the DIP with its increasingly high pin-counts suffers from inductance, resistance, and capacitance problems that adversely affect processing speed.

One solution to those problems is *surface-mount technology*, or SMT, which makes it possible to mount both discrete and integrated semiconductor devices directly on the surface of the PC board. Cost savings are effected due to a reduction in the number of plated-through holes, improved board yields, and higher component density. Components can even be mounted on both sides of the board with little increase in volume. Using SMT, Texas Instruments has achieved space reductions between 46 and 60% over circuits previously assembled on PC boards with discrete components.

### Surface-mount transistors

Several semiconductor manufacturers are now producing

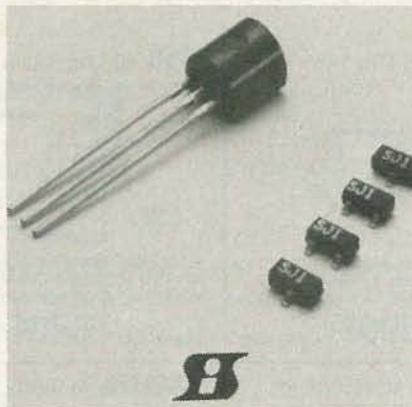


FIG. 1

transistors in the SOT-23 package—a subminiature three-lead package one-fourth the thickness of the common TO-92 package. In Fig. 1 we see four such SOT-23 devices (made by Siliconix) laid out beside a standard TO-92 device.

The SOT-23 package was originally introduced in two different heights, but Ferranti Semiconductors has introduced what they call their "optimum profile" package. Ferranti believes that their package eliminates the need for both standard and low-profile packages. The space between the device and the PC board allows for proper cleaning and also allows traces to be run beneath the device, while still permitting the device to be epoxied to the surface of the board. (Since there are no through-the-board leads, surface-mount components must be epoxied to the board before they are soldered. Soldering is usually accomplished by a solder-reflow process.)

Ferranti offers a number of devices for SMT, including both NPN

and PNP transistors, ranging from general-purpose, low-noise, and switching devices, to medium-power, high-frequency, and high-voltages types. Also included is a line of switching, Schottky, Zener, and varactor diodes.

Other SOT-23 devices made by Ferranti is the FMMT38 family of NPN Darlington transistors that feature high breakdown voltage ( $V_{CEO}$ ), and HFE ratings between 1000 and 10,000 at 500 mA and 5 volts (pulsed). Applications range from audio driver and output stages to drivers for lamps, relays, and hammers.


The 6-page "SOT-23 Transistor and Diode Selection Guide" lists key parameters of more than 250 devices for hybrid and SMT applications. Further information on the "optimum profile" package and copies of the selection guide are available from **Ferranti Semiconductors**, 87 Modular Ave., Commack, NY 11725.

A line of fifteen small-signal FET's is now being offered in SOT-23 packages by Siliconix. The devices, available in one P-channel and four N-channel configurations, are characterized as general-purpose amplifiers, low-noise amplifiers, low-leakage amplifiers, high-frequency amplifiers, and high speed analog switches. Prices are approximately 36 cents each in 5000-piece quantities.

### Surface-mount IC's

As shown in Fig. 2, surface-mount IC's are currently being offered in three SMT packages. These are SOIC (Small Outline Integrated Circuit), the PLCC (Plas-
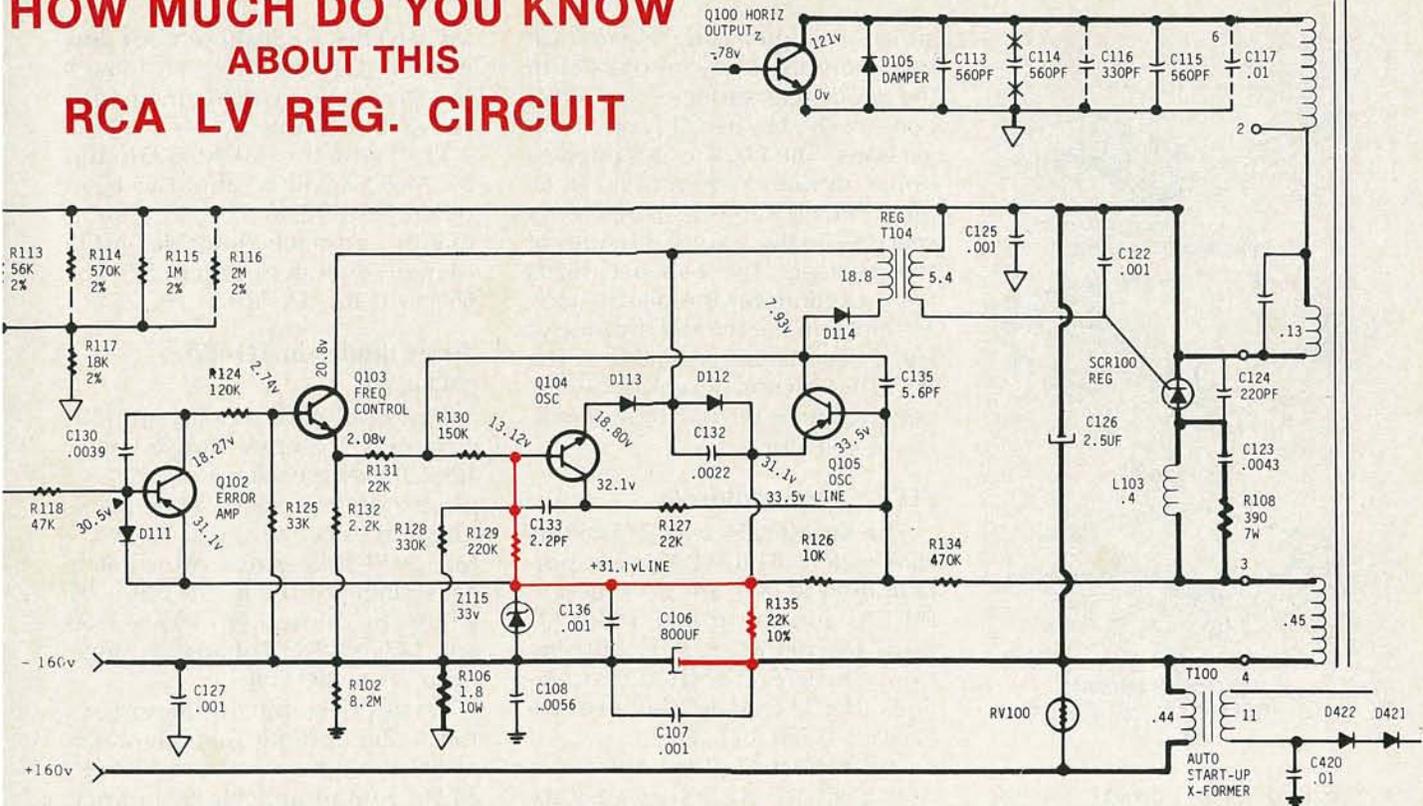
# HOW MUCH DO YOU KNOW ABOUT THIS RCA LV REG. CIRCUIT



Typical of RCA CTC 85 thru 108 LV Regulator Circuits

Schematic by Diehl Engineering

## How many of these questions can you answer ?

- (1) Every circuit has a beginning and an ending. Where does this circuit begin ?
- (2) Specifically, what is the purpose of this circuit ?
- (3) What turns it on ? What turns it off, or does it ever really turn off ?
- (4) Does this circuit have a shut down feature ? If so, which components are involved ?
- (5) What would happen if Q103 were to become shorted E to C ?
- (6) What purpose does Z115 serve ?
- (7) What would happen if D114 became shorted ?
- (8) What purpose does C126 serve ? What will happen if C126 becomes open ?
- (9) Is the winding between terminals 3 and 4 of the flyback a primary or a secondary winding ?
- (10) What purpose does C117 serve ? Exactly what does it do, and exactly how does it do it ?
- (11) Exactly what do resistors R113, 114, 115, 116, and 117 do ? What happens if they change value ?
- (12) What occurs that causes this circuit to produce an initial start up pulse ?
- (13) Why does this entire circuit become shorted and begin to destroy horiz output transistors if the regulator SCR becomes shorted ?
- (14) There is exactly one safe and practical method of circumventing this LV regulator circuit for test purposes. This technique does not involve a variac. Instead, you must disconnect one wire then connect a jumper wire from terminal #4 directly to which wire do you disconnect and where do you connect the other end of your jumper wire ?
- (15) If SCR100 is shorted, this circuit will still "eat" horiz output transistors even if you are using a variac. Why ?
- (16) Why does this circuit use a floating ground ?

We publish a monthly magazine called the Technician / Shop Owners Newsletter. Each month we take a popular circuit and absolutely dissect it.

Using color coded pictorial schematics such as the one above, we "map out" every action in the overall sequence of events that must take place during each and every cycle.

Beginning with the very first "action" in the sequence (which just happens to be depicted in the above schematic) we explain exactly what is taking place. We then explain the function of every component in that portion of the circuit. After explaining the function of each component, we show you how to troubleshoot that particular "action" or function.

After reading our newsletter on this circuit, you could answer all of the above questions as fast as anyone could ask them. In fact, you will then know everything there is to know about this circuit. Including how to troubleshoot it !!

Regardless of whether you work on TV sets, stereos, radios or computers, just having the ability to "dissect" an electronic circuit (any circuit) is worth a fortune. In reality, "dissecting" is exactly what our newsletter is designed to teach you.

Because of the manner in which our newsletter is written, the subject matter that is gained from each monthly issue is so extremely broad that it will "spill over" into your everyday troubleshooting routine, and be applied to totally unrelated circuits.

Each monthly issue sells for only \$9<sup>95</sup>, due ten days after delivery. VISA / Mastercharge welcome.

To Order: Send your name, address and phone # to Diehl Publications, 6004 Estacado Ln., Amarillo, TX 79109. Specify Issue # 3.

**For immediate Service Call: (806) 359-0329 or 359-1824.**

**Do not use the Reader Service Card in this magazine to place your order.**

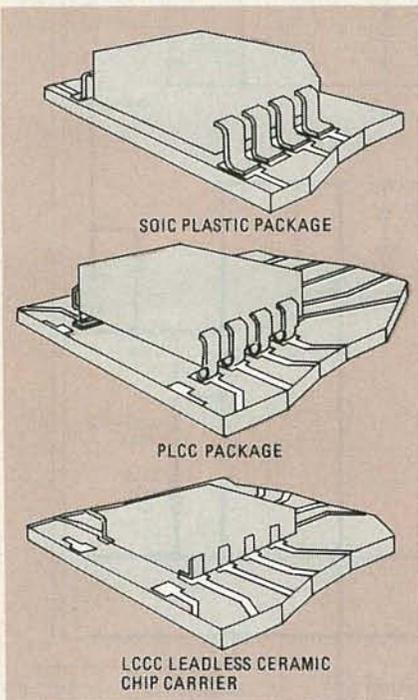


FIG. 2

tic Leaded Chip Carrier) and the LCCC (Leadless Ceramic Chip Carrier).

The SOIC has leads on two

sides. Its "gull-wing" leads are bent outward; they lie parallel to the mounting surface. The SOIC comes in 8-, 14-, 16-, 20-, and 24-pin versions. The PLCC is intended to house devices requiring 20 to 68 pins. The PLCC has J-shaped leads spaced equally around the sides of the package. The J-shaped leads are tucked under the plastic body as shown in the middle drawing of Fig. 2. The LCCC is similar to the PLCC but is considerably more expensive and is used mainly in military applications.

### PLCC's from Motorola

The MCM63256 and MCM65256 256K (32K × 8 bit) MOS mask-programmed ROM's are packaged in PLCC's, and the rolled-under "J" leads are compliant, thus reducing temperature-coefficient problems. The 32-lead devices measure 0.450 × 0.550 inches.

The MCM63256 is fabricated using Motorola's silicon-gate HMOS process; those new units are available with access times of 150 and 200 nanoseconds. The

MCM65256 is designed for low power dissipation, and uses Motorola's complementary HCMOS technology.

Prices of the MCM63256 and MCM65256 will be about \$5.65 in quantities of 1000. For more information, contact **Motorola**, MOS Memory Products Group, PO Box 6000, Austin, TX 78762.

### Zener diodes in TO-220 packages

Motorola now has 10- and 50-watt Zener diodes housed in a TO-220 plastic package that can replace more expensive metal-packaged devices. The 10-watt MZT2970-3015 series offers voltages ranging from 6.8 to 200 volts while the 50-watt MZT3305-3350 and MZT4549-4554 families range from 3.9 to 200 volts.

Retail prices for the 10-watt series of Zener diodes, in quantities of 100 and up, range from \$0.75 to \$0.96; 50-watt units range in price from \$1.10 to \$1.74.—**Motorola Semiconductor Products**, PO Box 20912, Phoenix AZ 85036. R-E

# XMAS SPECIALS!

## Jerrod Cordless Cable T.V. Converter (58 CHANNELS)

MODEL LCC-58



SPECIAL!

**\$69.95**  
ANY QUANTITY

## TEKNIKA WIRELESS REMOTE CONTROL TV TUNER CABLE CONVERTER



SPECIAL!  
WITH VOLUME CONTROL  
140 CHANNEL  
**\$139.95**

RG-59/U 75 OHM Co-Axial Cable  
Copper Braided Shield  
White or Black  
Bare copper conductor  
Branched bare copper shield  
**\$44.95/1000 ft.**

### CONNECTORS

F-59 separated ferrule



6c/1000 LOT  
11c/100 LOT


F-59ALM with attached 1/2" grip ring



7c/1000 LOT  
12c/100 LOT

F-56 AVAILABLE UPON REQUEST

MATCHING TRANSFORMER

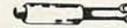

21c/100 Lot

2 WAY-75OHM U/V SPLITTER



59c/100 LOT  
89c/50 LOT  
99c/EA.

# OMNITRON

ELECTRONICS  
770 Amsterdam Ave., New York, NY 10025

Write for FREE 136 page Catalog

### SHIPPING CHARGES

For Orders	ADD
\$25 - 100	\$6.50
\$100 - \$500	\$8.50
\$500 - \$750	\$10.50
\$750 and up	\$15.00

MASTER CARD • VISA

Send Purchase Order, Check, Money Order or C.O.D.

or Call Toll Free

**800-223-0826**

in N.Y. State (212) 865-5580

# Which Way To YOUR Future?

Are you at a crossroads in your career? Have you really thought about it? Are you *planning* for your future, or perhaps refusing to face the subject? Which way will you go — down the same old road? Or are you ready for something else?

In electronics you can't stand still. If you are not moving ahead, then you're falling behind. At the crossroads of your career, various choices are available — and, yes, *decisions* have to be made.

Which road will you take — one that doesn't go where you want to be, or one that leads to hard work *but also* to the better life? Ah, decisions, decisions!

Career decisions are so important that you need all the *input* you can get before locking-in on one of them. Grantham College of Engineering offers you *one* source of input which may help you in making that decision. It's our free catalog.

Ask for our free catalog and you may be surprised to learn how it is easily possible to earn a B.S. degree in electronics without attending traditional classes. Since you are already in electronics (you are, aren't you?), you can complete your B.S. degree work with Grantham while studying at home or at any convenient place.

But don't expect to earn that degree without hard work. Any degree that's worth your effort can't be had without giving effort to the task. And of course it is what you learn in the process, as much as the degree itself, that makes you stand out above the crowd — that places you in an enviable position, prestige-wise and financially.


**Grantham College of Engineering**  
10570 Humbolt Street  
Los Alamitos, California, 90720

**This booklet  
FREE!**

This free booklet explains the Grantham B.S. Degree Program, offered by independent study to those who work in electronics.



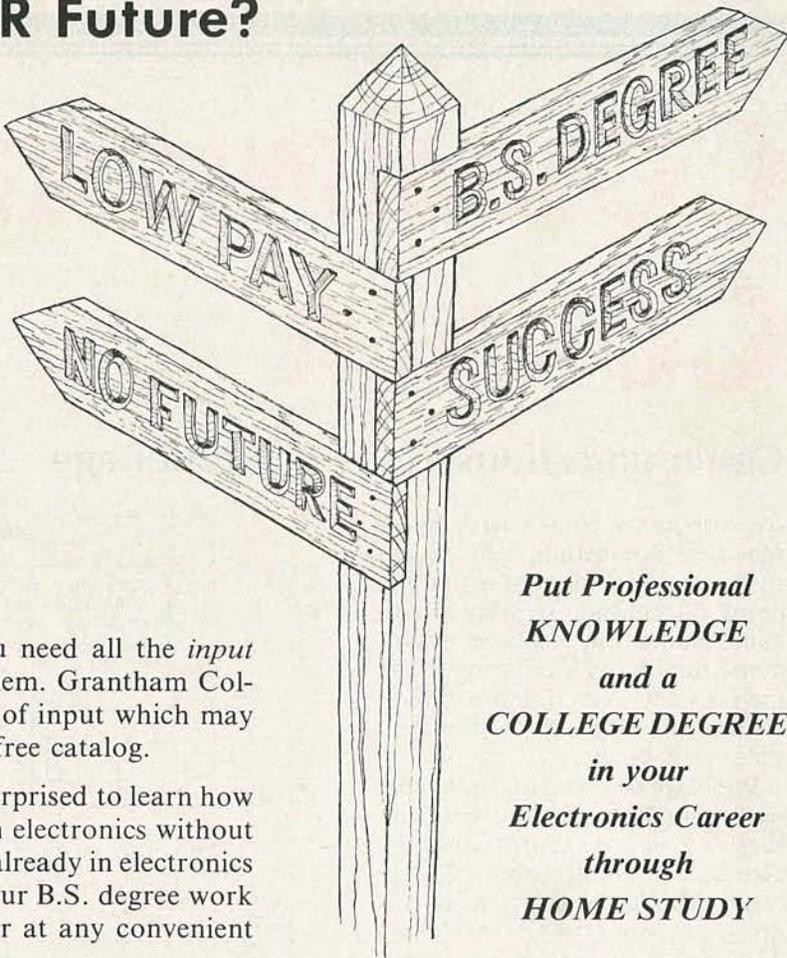for  
**FREE  
Booklet  
CLIP  
COUPON  
and mail in  
envelope or  
paste on  
postal  
card.**



*Put Professional  
KNOWLEDGE  
and a  
COLLEGE DEGREE  
in your  
Electronics Career  
through  
HOME STUDY*

Grantham offers this program, complete but without laboratory, to electronics technicians whose objectives are to upgrade their level of technical employment.

## **Recognition and Quality Assurance**

Grantham College of Engineering is accredited by the Accrediting Commission of the National Home Study Council, as a degree-granting institution.

All lessons and other study materials, as well as communications between the college and students, are in the English language. However, we have students in many foreign countries; about 80% of our students live in the United States of America.

**Grantham College of Engineering** R-11-85  
10570 Humbolt Street, Los Alamitos, CA 90720

Please mail me your free catalog which explains your B.S. Degree independent-study program.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

NOVEMBER 1985

# COMMUNICATIONS CORNER



HERB FRIEDMAN

COMMUNICATIONS EDITOR

## Communications in the computer age

THE COROLLARY TO THE OLD CLICHE that says something will always rush in to fill a vacuum is that if a need is created, someone will manufacture the required equipment. But it's really amazing to see the product created first and then a need develop simply because the product exists.


While we've come to expect that kind of thinking from the manufacturers of small appliances, and the gizmos and gadgets that fill mail-order catalogs, it's somewhat surprising to see how successful it's been in communications—particularly on the dial-up telephone system.

Have you ever wonder what happened to CB and all those who enjoyed chit-chatting over the airwaves? You'll find many of them on the telephone using a service that connects up to five semi-random callers at once. Simply dial a telephone number (usually long distance), and a computer connects you with four other users that have similar interests.

Already there are phone numbers for teenagers, young adults, and senior citizens. Once connected, if you don't like the group you're in, you can hang up, call in again (another charge), and the computer serves up a different set of callers. That scheme may eventually attract many special-interest groups, like photographers, calligraphers, or even a group out to cut the cost of their telephone bills!
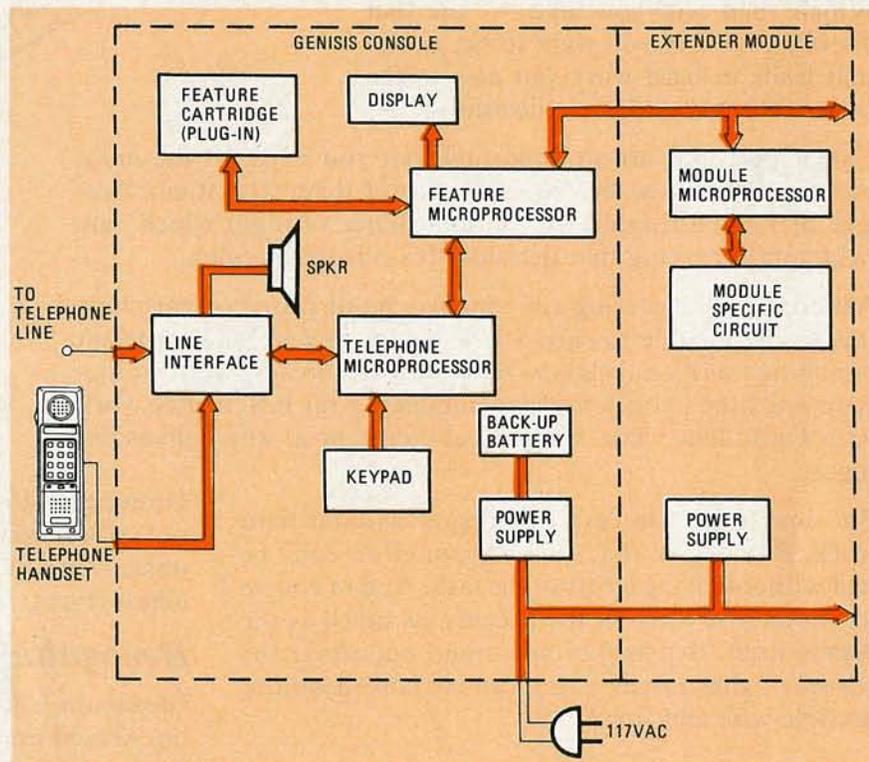
### Changes in telecommunications

Since we're in the computer age, what is more natural than to computerize family communica-



tions? Unfortunately, there's little that can be done with routine telephone calls, because the voice must move from one point to another. And users usually don't care how many computers there are between the talker and the talkee as long as it's not necessary to shout into the phone.

But as successful salespeople have been taught from the cradle: You don't sell the steak, you sell the sizzle. In other words, if you can't computerize the telephone call, computerize the instrument. Today's telephones use computers to provide services that no one dreamed of only five years ago.

The best example of how to load

a home (or business) phone with computerized functions is AT&T's *Genesis* Telesystem. *Genesis* is basically a computerized desk or wall-mounted console whose operating and convenience features can be upgraded by the user with plug-in program cartridges.

If the desired feature is too complex for a pocket-size cartridge, it can be made part of a complete extender module that connects to the base unit. Since the microprocessor and power-supply buses of the console interconnect to the extender unit, the entire system comes under the control of the console's microprocessor.

Figure 1 is a block diagram of the

# KENWOOD

...pacesetter in Amateur radio

## Scan the World



### R-2000

#### All-mode receiver.

- Covers 150 kHz-30 MHz in 30 bands.
- All mode: USB, LSB, CW, AM, FM.
- Digital VFO's. 50-Hz, 500-Hz or 5-kHz steps. F. LOCK switch.
- Ten memories store frequency, band, and mode data. Each memory may be tuned as a VFO.
- Lithium batt. memory back-up.
- Memory scan.
- Programmable band scan.
- Fluorescent tube digital display of frequency (100 Hz resolution) or time.
- Dual 24-hour quartz clocks, with timer.
- Three built-in IF filters with NARROW/WIDE selector switch. (CW filter optional.)
- Squelch circuit, all mode, built-in.
- Noise blanker built-in.
- Large front mounted speaker.
- RF step attenuator. (0-10-20-30 dB.)
- AGC switch. (Slow-Fast.)
- "S" meter, with SINPO scale.
- High and low impedance antenna terminals.
- 100/120/220/240 VAC operation.
- RECORD output jack.
- Timer REMOTE output (not for AC power).
- Muting terminals.

Specifications and prices subject to change without notice or obligation.



**R-1000** High performance receiver • 200 kHz-30 MHz in 30 bands • AM, CW, SSB • 3 IF filters • noise blanker • RF attenuator • S-meter • 120-240 VAC • muting terminals • built-in speaker • digital display/clock/timer



**R-600** General coverage receiver • 150 kHz-30 MHz in 30 bands • AM, CW, SSB • IF filters • noise blanker • RF attenuator • S-meter with SINPO scale • front mounted speaker • 3 antenna inputs • 100-240 VAC operation • record jack • muting terminals • digital display

#### Optional accessories:

- VC-10 VHF converter for R-2000 covers 118-174 MHz
- YG-455C 500 Hz CW filter for R-2000
- HS-4 Headphones
- HS-5 Deluxe headphones
- HS-6 Lightweight headphones
- HS-7 Micro headphones
- DCK-1 DC cable kit for 13.8 VDC operation
- AL-2 Lightning and static arrester
- Service manuals are available for all receivers and most accessories.

Additional information on Kenwood all-band receivers is available from authorized dealers.

## KENWOOD

TRIO-KENWOOD COMMUNICATIONS  
1111 West Walnut Street  
Compton, California 90220

Genesis system. Notice that two separate microprocessors are provided. The telephone microprocessor handles only actual telephone communications. It converts the keypad entries to pulse or *Touch-Tone* dialing (switch selectable), controls a built-in speaker that is used to monitor the line so that you know when to pick up the handset (automatically disconnecting the speaker), and controls the interfacing to the telephone line.

The feature microprocessor is interfaced to the one for the telephone. It provides 9 controls and the individual convenience features, such as a digital display of the number dialed, a digital clock/calendar/alarm and call timer, and single-touch memory dialing (of which three are reserved for emergency numbers).

As Fig. 1 shows, the power supply also includes a 9-volt transistor-radio type battery as a backup. The purpose of the battery is to keep the telephone "alive" when there's a power failure. If the AC power

fails, or the cartridge gets damaged, the telephone still works; the three programmed emergency call buttons will dial, and the remaining nine memories will retain their programming.

If both the power and the batteries fail (highly unlikely), the telephone is disabled, because it needs a local power source to operate. That's one of the prices paid for computerization. Fortunately, the microprocessor also tests the battery.

If the battery's voltage falls below a reference level, the display shows the words BATTERY LOW. And if you wait too long to replace the battery, the display shows the dreaded words BATTERY DEAD.

Notice from Figure 1 that the cartridge that provides the individual communications features is similar in concept to the plug-in game cartridges for home-and-family computers in that the instructions (program) for the microprocessor are in ROM.


The basic feature cartridge, which comes with the unit,

provides touch-tone dialing, a call timer, and hold; an clock/alarm, a ringer control, and speaker on-off.


Custom cartridges—which the user can install to replace the basic feature cartridge—can provide three-way calling, call forwarding, and call waiting, an electronic appointment reminder that displays up to 40 messages and even beeps when it's time to do something, and an electronic padlock that can lock out long-distance and operator-assisted calls.

Another module even memorizes and automatically alphabetizes a personal telephone directory. Since there's only one cartridge "slot," it's obvious that the features stack. That is, the upgrade cartridge has the features of the cartridge one level below, plus the upgrades.

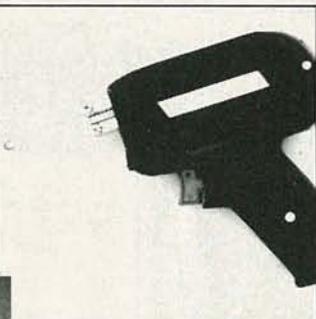If the feature is too large to fit into a cartridge, such as a speakerphone or multi-user dialer, it comes as an add-on extender that attaches to the right side of the console so that the two form an integral unit. R-E



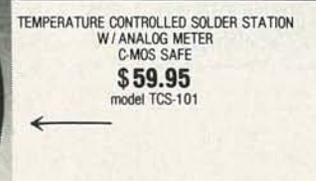**DUAL WATTAGE  
(100/140) SOLDER  
GUN W/LIGHT**  
**\$12.95**  
model WG 1400



**TEMPERATURE CONTROLLED SOLDER STATION  
W/ ANALOG METER  
C-MOS SAFE**  
**\$59.95**  
model TCS-101



**DESOLDER HANDPUMP — ALL METAL  
CONSTRUCTION W/ CONDUCTIVE TIP  
C-MOS SAFE**  
**\$4.95**  
model DP-1



**TERMS:**

- \$10 minimum order. \$1.00 charge for orders under \$10.00.
- \$20 minimum charge card order.
- Orders shipped UPS C.O.D.
- Most orders shipped within 24 hours.
- Sales office open 8:00 AM-4:00 PM.
- For prepaid orders add \$2.50 for shipping and handling.
- Should shipping and handling charges exceed \$2.50, the balance due will be sent C.O.D.
- **VISA AND MASTERCARD ACCEPTED**

**AMERICAN SOLDERING DEVICES CORP**  
P.O. BOX 24  
SHIRLEY, NY 11967 USA  
TEL: (516) 289-4735

ASD CORP. regrets the incorrect printing of our phone number in our Sept. AD. our correct phone number is 516-289-4735.

DESOLDER-IT,  
CLEAN-IT, COAT-IT,  
FREEZ-IT...SEND FOR IT!

Our new electronic problem solving catalog!





**Chemtronics**  
681 Old Willits Path  
Hauppauge, NY 11788  
800.645-5244  
In NY 516-582-3322  
Telex 968567

CIRCLE 288 ON FREE INFORMATION CARD

CIRCLE 54 ON FREE INFORMATION CARD

complex logic problem can be a tedious job. And no matter how elegant your solution, there's always another one just a bit more elegant hovering around the corner. But whatever solution you arrive at, if it works, you should be proud of yourself.


Jeff Davis sent me a complex solution that uses quite a few analog switches to decode every possible state (sixteen in all) of a four-bit binary word. A more elegant solution was sent in by Bob Milton of Canton MI. He did what a lot of you did. He used a standard decoder/driver (like the 7448) to drive the display for inputs from 0000 to 0111, and additional circuitry to drive the display for inputs from 1000 to 1111. The trick is to use the high bit of the input word to disable the display driver IC for inputs greater than or equal to 1000.

Bob hooked a 7404 inverter to the D input (pin 6) of a 7448, and fed the output to the BLANKING INPUT (pin 4) of that IC. So for any input greater than 0111, the D input goes high, the 7404 goes low, and the IC is disabled. Then the display LED may be driven with other circuitry. But be careful. Many of you confused turning off the display with three-stating it. In the case of a 4511, for example, a blank display means that the outputs are all low—and that's a far cry from being three-stated!

Since you'll drive the display with additional decoders for inputs above 0111, you should isolate both driver sections with three-state buffers. If you don't, the operation of the whole circuit is going to be flaky at best and non-existent at worst.

Many of you went the data-selector and diodes route. That's like building your own PROM, and is a sensible way to solve logic problems when you're short on time, supplies, and patience. Grey Benton of Campbell, CA sent the circuit shown in Fig. 1 as an example of that kind of approach.

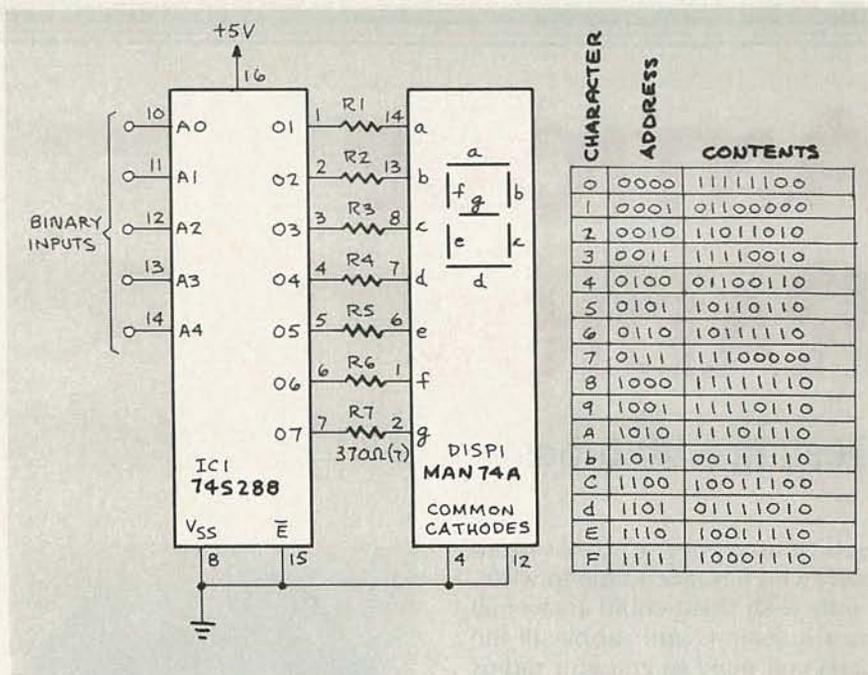Circuit operation is simple. Each four-bit word at the input will cause one and only one of the 74154's outputs to go low. The segments of the display are driven by IC2, a 74LS244 octal buffer whose inputs are held high by 2.2K re-



sistors R1 to R7. Any segment that's tied to a 74154 output through a diode will stay off when that output is selected.

There are both advantages and disadvantages to that sort of design. On the plus side, the format of the display of each digit can be changed simply by adding or removing diodes. In addition, as Grey points out, the circuit can be put together from readily available parts for about 10 bucks—including perfboard and IC sockets. The drawback is that the circuit takes a lot of connections.

### The PROM approach

Using a PROM was the most common solution to our problem. That approach is shown in Fig. 2-a. The truth table to decode sixteen binary inputs has sixteen entries, as shown in Fig. 2-b. For such a small amount of data, a small PROM will suffice. You could burn the code into an EPROM, but the smallest one available is the 1K-by-8 2708. Since we only need sixteen bytes, using a 2708 is like going after a fly with an elephant gun.

The best choice is probably a small bipolar PROM, such as the one most of you mentioned, the 74S288, which has a 32-word  $\times$  8-bit memory, costs about \$2.00 in small quantities, and is available everywhere. The 74S288 is rather

easy to program (as bipolar PROM's go).

Jackson Harris of Helena, MT sent me the truth table shown in Fig. 2-b. Burning it in a 74S288 will give you a single-IC decoder/driver for common-cathode displays. But you've still got half the PROM to play with. You could make use of that by burning an inverted truth table in the upper half of the PROM. You would then have an IC that could drive either a common-anode or a common-cathode LED display. Select the one you want by using address input A4 (pin 14) as a selector. Tie it low to drive a common-cathode display, and tie it high to drive a common-anode display.

As you know, the problem with bipolar PROM's is getting them programmed. There are many programming services that will program bipolar PROM's for you. All you have to do is provide them with the code and the cash.

But designing a circuit to burn bipolar PROM's isn't very difficult. All the specifications are given in the data books, and the problem is just complex enough to be interesting.

If you're interested in the subject, I'll spend some time on it. But for now, get ready to roll your sleeves up again because next month we're going to continue our discussion of the Z80. R-E

# ANTIQUE RADIOS

## Dealing with tubes

FIRST OF ALL, I WANT TO THANK EVERYBODY who has taken time to write. I only wish that I could answer all your questions and supply all the parts you need to get your radios restored to their original condition. Believe me, I know from first-hand experience how hard it can be. This month's column should help, though. We'll talk about tube substitution and then present some requests for help from readers. But first, let's get to the antique radio of the month.

### Antique radio of the month

The Philco *Junior Model 80* shown in Fig. 1 is this month's restoration case history. Its thin-veneered cabinet, four-tube chassis, and ability to receive only the AM broadcast band doesn't qualify it as a top-of-the-line radio. However, it does have a few interesting features, including a superheterodyne circuit, field and bucking coils on the dynamic speaker assembly, and a volume control in the antenna circuit (a common practice in many early radios).

Another interesting feature of the *Junior Model 80* is that it was originally sold with a choice of power transformers, in order to accommodate the power-line voltages available to listeners in different areas. If you come across a *Junior Model 80*, check the specifications on the rear of the chassis to make sure it will run on 117 volts. Otherwise you'll have to hook up an auto-transformer or some other kind of adapter in order to run that old radio.

My *Junior Model 80* plays well

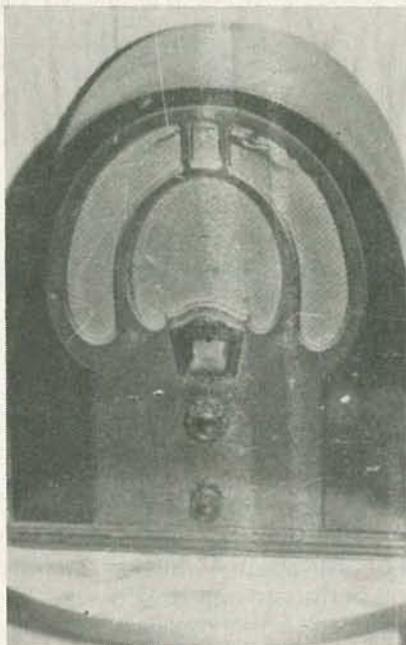


FIG. 1

now, but it needs a somewhat longer antenna than some antique radios with larger chassis. It had no serious chassis problems; it only needed to be cleaned and aligned. But that's to be expected: Many antique radios must be aligned after restoration because the settings of trimmer capacitors and coils are often disturbed when they are cleaned. The *Junior Model 80's* veneer cabinet held up well, considering its age of 50 years or more; it only needed minor touching up to complete our restoration and make the Philco Jr. *Model 80* a well-respected member of our collection.

### Testing tubes

While it's often easy to find replacements or substitutions for



RICHARD D. FITCH  
CONTRIBUTING EDITOR

most of the capacitors, coils, and resistors that are used in antique radios, it can be very difficult to do the same for tubes. In the early days of TV servicing, it was convenient to troubleshoot using the substitution method: The service man would carry a large (steamer-trunk sized) tube caddy into a customer's home. The caddy contained at least one sample of every type of TV tube. The tube caddy was often supplied by the tube manufacturer, as tubes were the backbone of the industry in those days. But now, few antique-radio fans enjoy the luxury of having one of every sort of tube available for substitution testing. That is when a tube tester comes in handy.

The problem is that the charts of modern tube testers seldom list tubes from our antique radios. If you do much restoration of antiques, it will be worth the effort to get an antique tube tester, which, by the way, is just as "collectable" as the antique radios we usually consider the primary object of our hobby. We've discussed some antique tube testers in previous columns.



When you buy an antique tube tester, make sure it has operating instructions as well as tube charts. It can be extremely difficult to find someone with a similar piece of equipment, and often the original manufacturer can't help.

There are several types of tube testers available. The most common is the emission tester. The other type, called a mutual conductance tester, is somewhat more expensive and harder to come by. The emission tester is sufficiently

**ECG® IC's for Zenith "Z" Chassis**

Philips ECG has replacement integrated circuits for the 221-175, -179 and -190 in the Zenith System 3 "Z" chassis. They are the ECG873, 874 and 875. Just three of the hundreds of integrated circuits available from Philips ECG to replace literally thousands of part numbers. All are manufactured to meet OEM specs so you know they fit and they work.

CIRCLE 310 ON FREE INFORMATION CARD

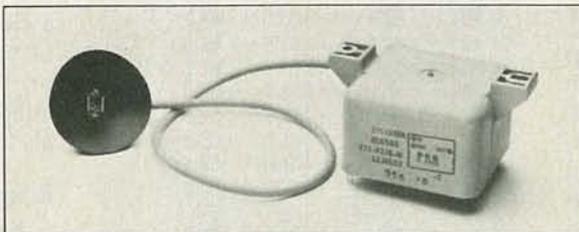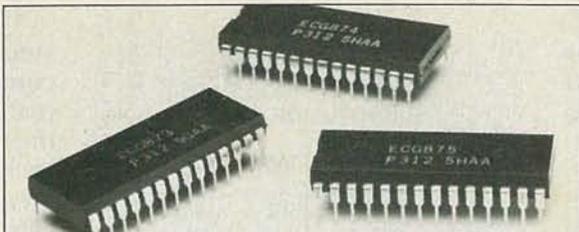

**ECG® High Voltage Triplers**

You have a choice of 29 types of high voltage triplers from Philips ECG, and these 29 triplers replace hundreds of part numbers. Six step, five step, with damper, with resistor—you name it, Philips has it. For example, the ECG559 replaces the Zenith 212-148 and the ECG560 replaces the Zenith 212-147—and only Philips ECG has replacement parts for these Zenith types.


CIRCLE 275 ON FREE INFORMATION CARD



**ECG® Bipolar Transistors**

Philips ECG replacement leadership is obvious again. The ECG 29, bipolar transistor, used as a replacement in the fan motor control system of Cadillacs, has been added to the Philips ECG line. (The ECG29 replaces Delco part numbers 139DDF and 7391-BT). There are 322 other bipolar transistors in the Philips ECG line that replace thousands of other domestic and foreign transistor types.

CIRCLE 311 ON FREE INFORMATION CARD

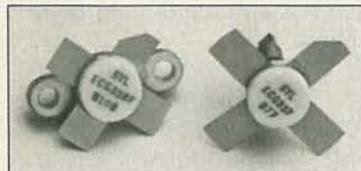

**ECG® RF Power Transistors**

Philips ECG power transistors are the ideal replacement RF power output devices for fire, police and taxi radios. They are suitable for transmitters and drivers up to 100 Watts RF power. They cover frequencies from the 13 to 30 MHz band to the UHF 806 to 870 MHz band. Most dealers will be happy to learn that Philips ECG replacement RF power transistors are designed to replace units in Asian and European equipment as well as domestic types. So, if it's ECG, it fits and it works... worldwide. Philips offers a selection of over 65 RF transistors that replace literally hundreds of domestic and foreign transistors in a broad range of frequencies.

CIRCLE 312 ON FREE INFORMATION CARD

**The one thing we make that you have to replace every year.**



**The new and expanded ECG® Semiconductors Master Guide.**

Your new Master Guide will be looking as dog-eared as the old one before long. Because this year the Master Guide has been expanded to include more than 400 new products and almost 25,000 new cross references. The Master Replacement Guide for 1985. 656 pages. Over 3,500 different ECG devices that provide replacement coverage for more than 227,000 industry types. And everything in the book is cross-referenced so you can find what you're looking for fast, and be sure it fits. Plus, everything we make meets or exceeds the original JEDEC or application specs. So it

works. It's the only book you'll need. But you'll need a new one every year.

To get a copy of the new Master Guide, go to your nearest Philips ECG distributor. For his name and location, just call: 1-800-225-8326 (in Mass., 617-890-6107).

**If it's ECG, it fits. And it works.**

**Philips ECG**

*A North American Philips Company*

*Dedicated to Excellence.*

accurate for our purposes. It does just what its name implies: it provides an indication of the number of electrons being emitted from the cathode. An emission tester is usually reliable, and can help you rank the quality of several tubes, as well as testing for shorts and opens.

When using a tube tester, stop the test and remove power at the first indication of a short. A tube with an inter-element short should not be used in an antique radio, not even just "to fill a hole." Watch the neon indicator on the tube tester for the slightest indication of leakage. If a hard-to-get tube tests "weak" (or worse, as long as it's not shorted) it can still be used "to fill a hole."

If you don't have a tube tester handy, you can make continuity tests with an ohmmeter, as we've discussed in previous columns; but such tests are limited. An ohmmeter can detect an open filament, but shorts may or may not show up on a cold tube.

### Testing tubes

The numbering system of antique radio tubes did little to identify the tubes' functions. Tubes were numbered consecutively, and unless you had an exceptional memory, it was always necessary to keep a tube-substitution guide handy. Later, even when tube numbers began to give some indication of type and function, every radio man kept his substitution guide within arm's reach because the sheer number of tubes made it a necessity.

For those who have forgotten, the numbers for tubes used in antique radios from the later 1930's give some information about the tube in the type number. The first digit(s) indicate the approximate filament voltage. The second part of the tube number consists of one or two letters. Usually, letters near the end of the alphabet (W, X, Y, Z) indicate a rectifier tube. An S as the first of two letters indicates that the tube doesn't have a grid cap, or that all elements are attached to pins in the base of the tube. The third part usually indicates the number of elements connected to the pins in the base of the tube. Of course, the number

TABLE 1-ANTIQUE TUBE SUBSTITUTION CHART

Tube	Sub	Tube	Sub
00A	01A	6F7	unknown
01A	00A 40	6G5	6U5
0Z4	0Y4	6J5	6C5
1V	6Z3	6J7	6K7
12	71A	6K5	6C5
24	35-51	6K7	6U7
26	unknown	6L5	6C5
27	56	6L6	6K6
32	34	6L7	unknown
33	1F4	6N6	6AB6
34	32	6Q7	6B6
36	39-44	6S7	6W7
37	76	6T7	6B6
38	unknown	6U7	6K7
39	44	6V6	6K6
40	01A-12	6X5	6W5
41	42	6Y5	unknown
42	41	6Z4	84
43	unknown	6Z5	unknown
44	39	7A5	7C5
45	2A3	7A7	7L7
47	unknown	7A8	unknown
55	2A6	7B5	7C5
56	27	7B7	7C7
57	58	7G7	1232
58	57	7J7	7S7
59	unknown	7L7	7A7
71A	unknown	7N7	7F7
75	85	7R7	7E7
76	37	7T7	7V7
77	1221	7V7	7C7
78	6D6	7Y4	unknown
80	5Z3-83	12SQ7	12SR7
83	5Z3	12SK7	12SG7
85	75	12SA7	12SY7
89	unknown	25A6	25B6
5W4	5Y3	25L6	25W6
5Y3	5AX4	25Y5	25Z5
5Y4	5Z4	25Z5	25Y5
5Z3	80	25Z6	35Z6
5Z4	5Y3	1232	7G7
6A7	unknown	6SA7	6SB7
6A8	6J8	6SC7	unknown
6B5	unknown	6SF7	6SV7
6B7	unknown	6SK7	6AG7
6C5	6C6	6A7**	6SA7
6D6	78	6Q7**	6SQ7
6D8	unknown	41**	6K6
6E7	6D7	42**	6F6
6F6	6V6	** = with adapter	

of elements does not necessarily correspond to the number of pins.

Letters at the end of the tube number refer to the type of construction. So, for example, a 25Z5 has a 25 volt filament, is a rectifier, and has five pins connected to tube elements. Earlier tubes (from the 1920's) have a two-letter prefix and three digits. Tubes with the UY prefix (like the UY224 or UY227) have five pins, and tubes with the UX prefix (like the UX226 and UX245) have four pins.

In Table 1 you'll see a tube-sub-

stitution guide; it is by no means complete, but does contain a list of the tubes I most commonly find in antique radios from before the second world war, along with common substitutes. You may want to clip the table and save it for future reference. Tube types marked with a double asterisk (\*\*) are functional equivalents, but their pinouts differ, so some type of adapter must be used. You could also rewire the socket.

### Reader's inquiries

Bill Fletcher (3302 Leopold Way, #111, Madison, Wis. 53713) writes looking for the schematic of the General TV And Audio model 337. Sorry Bill, I can't find that model listed anywhere, but maybe one of our readers can help. Martin Hammond (Box 1854, Huntsville, Ontario, Canada P0A 1K0) is interested in receiving information about antique radio museums and publications for collectors.

David Sharosky (1323 Jackie Lane, Mayfield Hts., Ohio 44124) has a crystal radio he'd like to sell; it has a label that says, "Martian Mfg. Co. Inc. Special, Newark, NJ Pat. Pend." Sounds interesting, Dave. If you weren't so far away I'd come and take a look at it myself. Dave also has a piece of galena he would like to sell.

David G. Weatherly (2300 Carolina Rd., Chesapeake, VA. 23322) wrote to say he has seven tubes from a Majestic model 90 for sale. Dave, if you still have the rest of that Majestic, it is as valuable as the tubes to someone needing parts.

A schematic for a Firestone Air Chief model 4-A-22, code 5-6-9023 B is needed by Michael Wilhelm (Marine Bks., Box MTM FBPO, Norfolk, VA 23593). Mike, I found some information on that radio in Sams *Photofact 11*.

Finally, one reader wrote complaining about a 1936 Silvertone 4585 console radio that whistled when new tubes were installed, especially when using the volume control. I'm sure others have had that problem; the solution is usually quite simple. Antique radios depend heavily on shielding for proper operation, so be sure to replace all shielding after working on an antique.

R-E

# Electronics Paperback Books



**SECRETS OF THE COMMODORE 64** ..... \$5.00. Masses of useful info and programming tips not found in any user's manual.




**INTRO TO PROGRAMMING THE ATARI 600/800 XL** ..... \$5.00. Perfect complement to the Atari user's manual. Even shows how to use animated graphics.



**COMPUTER TECHNOLOGY EXPLAINED** ..... \$5.00. Explanations for computer terms often encountered. A dictionary for computer lingo.



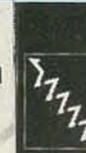**INTRO TO Z-80 MACHINE CODE** ..... \$5.75. Speed up your programs. They may be harder to write, but it's worth learning how. Some demo programs are included.



**ANTENNA PROJECTS** ..... \$5.00. Practical radio antenna designs that deliver good performance and are relatively simple and inexpensive to build.



**WHITE'S RADIO LOG** ..... \$4.94. An up-to-date directory of AM, FM and TV stations, including a section on worldwide shortwave stations.



**CONFIDENTIAL FREQUENCY LIST, 6th edition** ..... \$13.95. Latest info on usual and exotic shortwave broadcast stations.



**25 SIMPLE AMATEUR BAND ANTENNAS** ..... \$5.00. All kinds of antennas for all kinds of amateur radio reception.



**INTRODUCTION TO RADIO DXING** ..... \$5.00. Get into this fascinating hobby. This book tells you just about everything you need to know to get started.



**25 SIMPLE AMATEUR BAND ANTENNAS** ..... \$5.00. All kinds of antennas for all kinds of amateur radio reception.

## Quality Paperbacks



**LONG DISTANCE TV DXING** ..... \$5.00. A practical and authoritative introduction to this unusual aspect of electronics.



**HOW TO DESIGN ELECTRONIC PROJECTS** ..... \$5.75. How to use standard circuit elements to make custom electronic projects.



**HOW TO GET YOUR ELECTRONIC PROJECTS WORKING** ..... \$5.00. How to find the faults in your projects, repair them and get them working.



**DESIGN & MAKE YOUR OWN PC BOARDS** ..... \$5.75. Everything you need to know before you make printed circuit boards for your projects.



**INTERNATIONAL DIODE EQUIVALENTS** ..... \$5.75. Helps find replacements for rectifier diodes, triacs, thyristors, photo diodes and display diodes.



**INTERNATIONAL TRANSISTOR EQUIVALENTS** ..... \$7.50. Locates possible substitutes for a popular user-oriented selection of modern transistors, Japanese, European and American types.




**PRACTICAL ELECTRONIC BUILDING BLOCKS, Book 1** ..... \$5.75. Build the blocks and then combine them to form almost any custom project of your choice.



**PRACTICAL ELECTRONIC BUILDING BLOCKS, Book 2** ..... \$5.75. Amplifiers of all kinds to add to the circuits from Book 1 of this series.



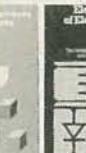**THE SIMPLE ELECTRONIC CIRCUIT, Book 1** ..... \$5.75. Elements of Electronics. Fundamental electronics theory.



**ALTERING CURRENT THEORY, Book 2** ..... \$5.75. Elements of Electronics. Needed for comprehension of speech, music, radio, TV and more.

## Affordable Prices



**SEMICONDUCTOR THEORY, Book 3** ..... \$5.75. Elements of Electronics. Leads into transistors and other semiconductor devices.



**HOW TO USE OP AMPS** ..... \$5.75. A source book of circuits and a reference book for design calculations.



**ELECTRONIC SYNTHESIZER PROJECTS** ..... \$4.50. How to assemble the elements of a synthesizer and then put them all together.



**ELECTRONIC TIMER PROJECTS** ..... \$5.00. Timing circuits to fit just about every application. Required for every experimenter.



**SINGLE IC PROJECTS** ..... \$4.25. All projects in this book are based on one IC and are simple to construct. Great way to get started with ICs.



**POPULAR ELECTRONIC PROJECTS** ..... \$4.75. A collection of a wide range of electronic projects and circuits for the experimenter.



**IC PROJECTS FOR BEGINNERS** ..... \$5.00. Written especially for the less experienced experimenter. Complete parts layouts and wiring diagrams.



**POPULAR ELECTRONIC CIRCUITS, Book 1** ..... \$5.00. More circuits for hobbyists. Audio, radio, test, music, household and more.






**555 PROJECTS** ..... \$5.00. So useful that this IC has an unparalleled reputation. Here's a book full of useful applications.



**POPULAR ELECTRONIC CIRCUITS, Book 2** ..... \$5.75. More of these projects duplicate those in Book 1 of this series.

## CHECK OFF THE BOOKS YOU WANT
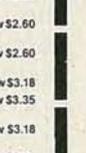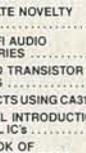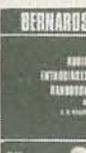
### BOOKS LISTED BELOW ARE 25% OFF REGULAR CATALOG PRICE


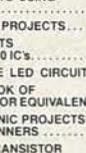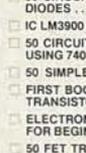
### THE MORE YOU BUY.....THE MORE YOU SAVE.....THE MORE YOU BUY.....



### SPECIAL CLEARANCE SALE OFFER ENDS DECEMBER 31, 1985

**ELECTRONIC TECHNOLOGY TODAY INC.**  
 P.O. Box 240, Massapequa Park, NY 11762-0240  
 Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Number of books ordered  \_\_\_\_\_  
 Total Price of Books ..... \$ \_\_\_\_\_  
 Sales Tax (NY State Residents) ..... \$ \_\_\_\_\_  
 \*Shipping in U.S. only (\$1.00 1st two books, 40c ea additional) ..... \$ \_\_\_\_\_  
 TOTAL ENCLOSED ..... \$ \_\_\_\_\_

\*Canadian Shipping (\$1.50 1st two books 50c ea. additional)

5-11

NOVEMBER 1985

# SERVICE CLINIC



JACK DARR  
SERVICE EDITOR

Use a function generator for audio troubleshooting.

I HAVE TO ADMIT THAT THE FIRST TIME I saw a function generator, I was a bit overwhelmed. (Perhaps it's because function generators were bigger and more imposing-looking back then than they are today; see Fig. 1.) However, I had to evaluate a unit, and that made it necessary for me to find out about function generators in a hurry. Doing so, I became so fascinated with the thing that I bought one for myself.

A function generator can be thought of as a very versatile audio-frequency generator. A function generator can produce sine-waves, squarewaves, sawtooth waves, pulses of just about any width and repetition rate, and many have built-in sweep capability.

Using a function generator for troubleshooting is not much different than using an ordinary signal generator; in fact, many times you can use it just the same way you'd use an ordinary signal generator. For example, one traditional application is signal tracing, in which a signal is applied to a low-level audio stage and traced through the inputs and outputs of successive stages, either aurally or with an oscilloscope (or both), until a distorted signal becomes evident. Then it is simply a matter of determining which component(s) are responsible for the distortion.

A triangle wave is very handy for that type of testing since any clipping is immediately apparent on the screen of the scope. The peaks of the wave will flatten out. Just be sure not to overdrive your circuit's input; I've found that 50 millivolts is usually sufficient to drive the low-level stages of most ampli-



FIG. 1

fiers. If the first stage is clipping, try reducing the output level of your generator. If the clipping doesn't disappear, you may have found the source of the distortion. Also, keep the volume control cranked up; clipping will be most evident then.

When you find a stage that is clipping, measure the grid and plate—or base and collector—voltages. Incorrect bias is a very common cause of clipping. If a stage is improperly biased, it won't be able to handle the range of signal that it should. The signal may be driven toward cutoff, saturation, or both; in any case, the signal will be clipped, and distortion will result.

Incorrect bias is often due to a resistor that has drifted off-value. Be sure to check the values of plate and collector load resistors, and in some cases, screen-grid resistors. If the screen voltage is off either way, the gain of the stage could be drastically affected.

Checking bias is best done at a low level of amplification. Bias that is a few tenths of a volt out of spec won't bother a tube circuit too much, especially if the grid is biased at about ten or fifteen volts. However, transistors are usually more sensitive than tubes to bias

changes; a transistor that loses a few tenths of a volt may be driven into complete cutoff. That is particularly true of the low-level pre-amplifier stages. By the way, that's where a precision digital VOM comes in handy. That's what the factory uses to measure the voltages marked on the service literature, and you'll want to use high-impedance, high-accuracy equipment just as they do. Otherwise, your measurements may be so far off that they're meaningless.

In power tubes, distortion may result if the grid bias is off. The best way to see if grid bias is the problem is by inserting a new tube into the circuit. Alternatively, you could use the grid current test function of your tube tester.

## Using squarewaves

The squarewave from a function generator can be used to test both low and high frequency response. Apply the squarewave to the amplifier, and examine the output on a scope. Look for any signs of "tilt" on the tops and bottoms of the signal; they should be absolutely flat and parallel to the baseline. If they tilt to the left, the low-frequency response is poor. If they tilt to the right, and the corners are rounded, the high-frequency response is poor. That rounding of the corners is easy to spot. You can also use squarewaves to check the efficiency of the tone controls; rotate them and observe the effect on the scope. In fact, that would be a good place to try out the sweep function of your generator.

To use the sweep function, all you do is feed a small voltage, preferably a 60-Hz sinewave, into

*(Continued following Computer Digest)*


# COMPUTER DIGEST

VOL. 2 NO. 11 November 1985

NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS
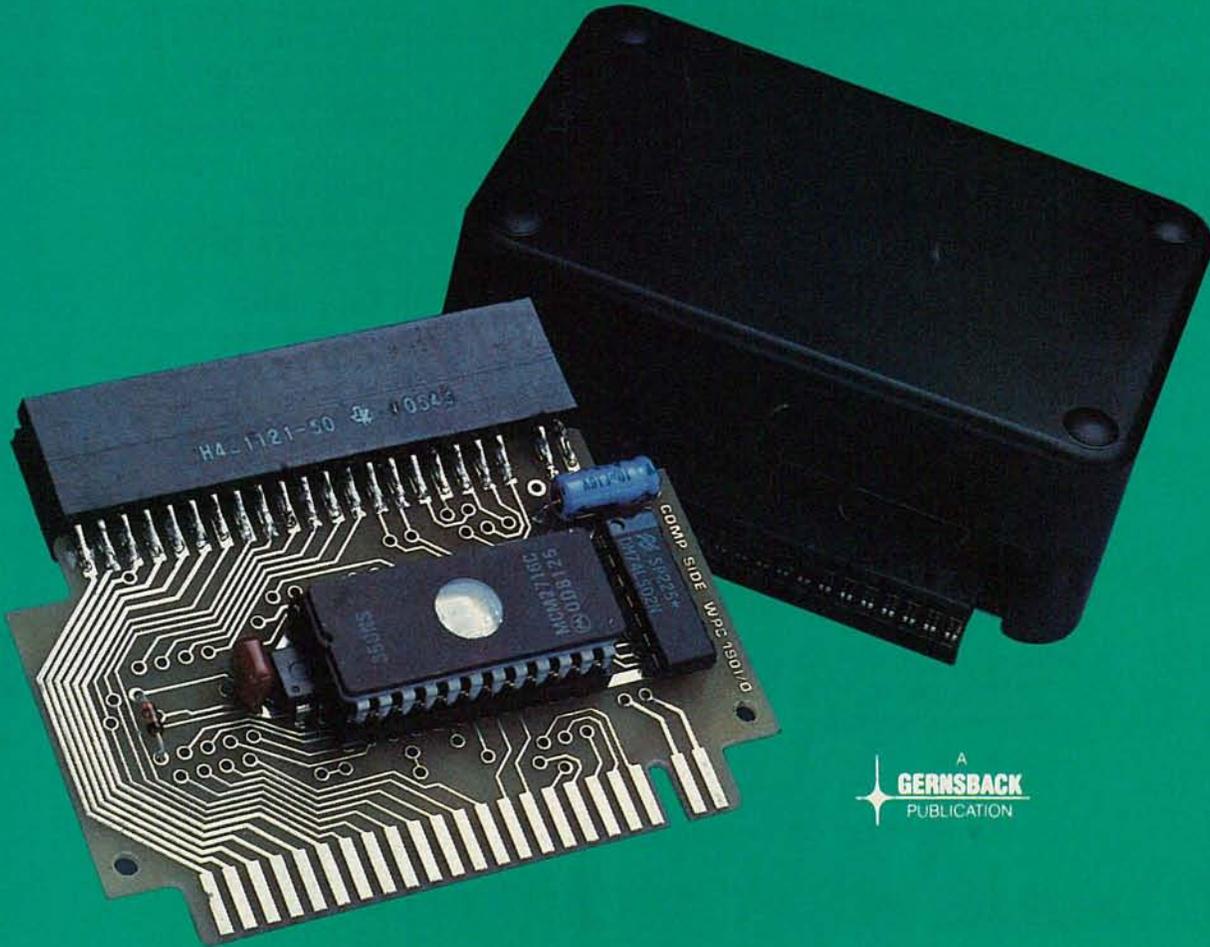
## BUILD THE FIRMWARE CARD

Place an EPROM in the USR Memory of your Timex.



A  
GERNSBACK  
PUBLICATION

## RAMDISK TECHNOLOGY

Instant-Access Mass Storage.

## BUILD THIS MODEM FOR YOUR COMMODORE 64

Part I of a Two-Part Article.

# CONTENTS

Vol. 2 No. 11

November 1985

## 4 Build The Firmware Card

Add this simple card to your Timex and you won't have to store everything above Ramtop. **Marc W. Latham**

## 6 Ramdisk Technology

While mass storage is usually considered a benefit, accessing can take time. Enter Ramdisk. **Herb Friedman**

## 9 Build a Modem For The Commodore 64

This two-part article will be completed next month. It's a money-saving idea!

## 3 Letters

## 3 Computer Products

## ON THE COVER

The Firmware Card (See page 4) will add an element of additional flexibility to your TIMEX computer. The small amount of time and cost makes the effort well-worthwhile.

## COMING NEXT MONTH

A really jam-packed issue you won't want to miss. Learn how your computer can take the drudgery out of designing attenuators and pads, How to use PERCOM to double your storage density, how to enhance and tune the 1541 disk drive the easy way, and we'll start a two-part article on building your own modem for your Commodore.

**ComputerDigest** is published monthly as an insert in Radio-Electronics magazine by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Second-Class Postage Paid at New York, N.Y. and additional mailing offices. Copyright © 1985 Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

# COMPUTER DIGEST

**Hugo Gernsback** (1884-1967)  
founder

**M. Harvey Gernsback,**  
editor-in-chief

**Larry Steckler,** CET, publisher

**Art Kleiman,** editorial director

**Byron G. Wels,** editor

**Brian C. Fenton,** technical editor

**Carl Laron,** associate editor

**Robert A. Young,** assistant editor

**Ruby M. Yee,** production manager

**Robert A. W. Lowndes,**  
production associate

**Karen Tucker,**  
production assistant

**Geoffrey S. Weil,**  
production assistant

**Andre Duzant,** Technical Illustrator

**Jacqueline P. Weaver,**  
circulation director

**Arline R. Fishman,**  
advertising coordinator

Gernsback Publications, Inc.  
200 Park Ave. South  
New York, NY 10003  
Chairman of the Board:  
M. Harvey Gernsback  
President: Larry Steckler

### ADVERTISING SALES 212-777-6400

Larry Steckler  
Publisher

### EAST/SOUTHEAST

Stanley Levitan  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003  
212-777-6400

### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen  
Radio-Electronics  
540 Frontage Road—Suite 325  
Northfield, Illinois 60093  
312-446-1444

### PACIFIC COAST Mountain States

Marvin Green  
Radio-Electronics  
15335 Morrison St., Suite 227,  
Sherman Oaks, CA 91403  
818-986-2001

# LETTERS

## Hackers

I resent your recent editorials on Hackers. Anybody that tinkers with computers is a hacker, and I've been doing this for years, trying to improve my system. I do not consider myself a moron!—B. G. Jerrolds, Waseca, MN.

*Watch my lips. You're not a hacker. You're a computer experimenter. Read some of the mail we received and see if you don't agree with me.*

## More On Hackers

I'm a hacker and a student of computer science. I do break into other systems but don't crash them. I just look around to see what they're doing and how they're doing it, then quietly leave.

All I'm really trying to do is educate myself. Is that wrong?—Monorail Red, Orlando, FL.

*And if you were studying interior decorating, would it be all right to break into your neighbor's home just to see how it was furnished?*

## Still More

I'm a hacker, and I look upon a computer system as a challenge. It's like a puzzle I'm trying to solve. If I can break in, why it simply means I solved the puzzle. What harm is there in that?—R. D. Falcon, Atlanta, GA.

*How do you feel about picking your neighbor's front-door lock? That's a puzzle, too.*

## It Goes On

Did it ever occur to you that we hackers are performing a service? If we can break into a computer system, anybody else can, too! It makes the system operator look again at his security methods. Frank Cheyney, Billings, Mont

*Sure, Frank; in the same way that a bank robber helps the bank!*

## And On

There are some very famous and important heads of business in the computer industry that started as hackers. What do you have to say about them?—Sam Pace, Indianapolis, IN.

*The same thing I say about all hackers.* ◀▶

# COMPUTER PRODUCTS

For more details use the free information card inside the back cover

**PORTABLE COMPUTER**, the *Bondwell 16*, features a 10-megabyte hard disk drive, 128K RAM memory, built-in voice synthesizer, and bundled software. It also features a 9" non-glare monitor, 91-key detached fullstroke keyboard, with a separate numeric keypad, built-in modem, and a 5½" floppy-disk drive.

Equipped with the upgraded CP/M 3.0 operating system, the 30-pound computer is better able to use its 128K RAM memory in the application of the

five business-software programs bundled with the system: WordStar, MailMerge, CalcStar, DataStar, and ReportStar. The model *Bondwell 16* is priced at \$1995.00.—*Spectravideo, Inc.*, 3300 Seldon Court #10, Fremont, CA 94539.

**DOT-MATRIX PRINTERS**, the Microline model 192 and its wide-column companion, model 193, (shown in photo), feature three different print modes, a re-inking cartridge ribbon, and user-friendly operation.

Both printers come in standard versions to interface with most personal computers, as well as specially configured IBM-compatible models. (The IBM-configured printers come with free software to work with the IBM-PC, PC Jr, and PX/XT.) The software provides type styles similar to courier, italic, gothic, and scientific characters.

The Microline model 192 comes with an adjustable pin-feed mecha-



CIRCLE 12 ON FREE INFORMATION CARD

nism, while the model 193 has a tractor feeder.

The model 192 is a compact unit, measuring 14.6" x 10.9" x 3.2.6" and weighs just 9.9 pounds. It is priced at \$499.00. The model 193 handles wide-column applications, such as spreadsheets. It prints up to 136 columns at 10 characters per inch, 163 at 12 CPI, and 17.1 at 233 CPI. It can print between 68 and 233 characters per line. It measures 20.6" x 10.9" x 5". It is priced at \$699.00.—*Okidata*, 532 Fellowship Road, Mt. Laurel, NJ 08054. ◀▶



CIRCLE 11 ON FREE INFORMATION CARD

# FIRMWARE CARD

*Build this and you don't have to store everything above RAMTOP.*

**MARK W. LATHAM**

From teletext terminals to solar heating controllers people seem to discover new uses for the Timex/Sinclair 1000 and its upgraded successors. Those who write the software for these applications often forego BASIC and program either partially or completely in machine code. Such programs not only have precise control of the computer and fast execution times, but lend themselves perfectly for placement on a firmware card.

How do you know that your program has been written completely in machine language? If it loads into the BASIC area and then transfers itself above RAMTOP,

it probably is. The area above RAMTOP is not the only place to put machine code programs. USR calls can be directed to any location in the 0-32K area.

The firmware card described here lets you place either a 2K or 4K EPROM anywhere in the USR memory area. It can serve as an interface card for custom projects. It fits into Radio Shack's smallest project box and operates much like an Atari game cartridge. Once you plug it in, all that is necessary is to call the program.


## Circuit operation

The schematic diagram is shown in Figure 1. The one-of-eight decoder, IC1, reads address lines A11-A15 and provides a decoded output. Just a few jumpers allow this IC to activate the EPROM anywhere in the USR area.


When a 2K EPROM is used, address A11 is jumpered to the decoder's least significant address input, pin 1. The decoder's eight outputs will then each represent a 2K block of memory. Address A14 is jumpered to either pin 4 or pin 6 of the decoder, allowing these eight outputs to activate for addresses in the 0-16K or 16-32K areas, respectively.

For a 4K EPROM, the decoder's pin 1 is left open and A11 is jumpered to the most significant EPROM address pin. With this jumper configuration, the decoder activates only the odd-numbered of the eight outputs, each of which represents a 4K block of memory.

Usually the decoded address signal is ORed with /MREQ (computer's memory request) before being fed to the EPROM's /CE (chip enable). Such a configuration provides for the least power dissipation possible. In this case, however, the decoded address signal is connected directly to /CE, and /MREQ is connected to the EPROM's /OE (output enable). For a rare compromise in power, access time is then extended allowing even the slow 480ns memories to work.

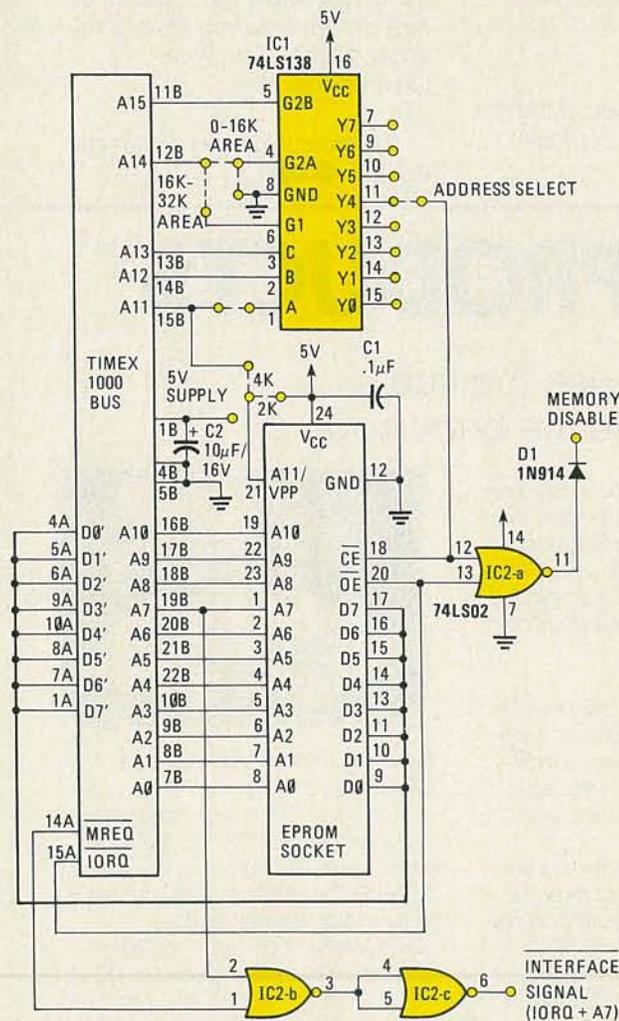

**Fig. 1—SCHEMATIC DIAGRAM OF FIRMWARE CARD** can easily be modified by cutting certain of the trace lines to suit your needs. See the text for additional information.

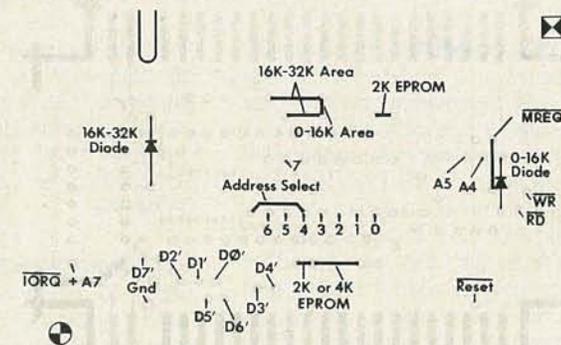

**FIG. 2—SIGNAL LOCATIONS** are called out on diagram above. Refer to text for further clarification.

## Project interface

For those readers who have built custom add-ons such as those described in "Interfacing The ZX-81" (see Radio-Electronics, July-September, 1984) or "Machine Code Development System" (see ComputerDigest, January and March, 1985) the firmware card allows you to interface your project and keep the computer bus

too. To separate the display and printer commands from the project's I/O signals, the computer's /IORQ and address A7 have been ORed to provide an interfacing signal. The locations of this and other useful signals on the firmware card is shown in Figure 2.

### Memory disable

In order for the firmware card to work properly, it must disable any other memory device working in the same area. A memory disable signal is made by NORing (via IC2a) the decoder's output with /MREQ and then connecting the NOR output through diode D1 to the control line of the memory to be disabled.

As shown in Figure 2, D1 can be placed to disable either the ROM (0-16K) or the RAM (16K-32K) of the computer's internal memories. The firmware card can also disable an external RAMPACK that cannot be

### PARTS LIST

- D1—1N914 or 4148 Switching Diode
- IC1—74LS138 One-Of-Eight Decoder
- IC2—74LS02 Quad 2-input NOR gate
- C1—.1 $\mu$ F Disc or Metalfilm Capacitor
- C2—10 $\mu$ F 16V Electrolytic Capacitor
- Miscellaneous—Edge connector, 24-pin socket, circuit board, project case, hardware.

An etched, drilled and cut printed circuit board is available for \$12.95 (price includes shipping and handling) from WILDONICS, Box 1763, Boise, ID 83701. For custom cards, write.

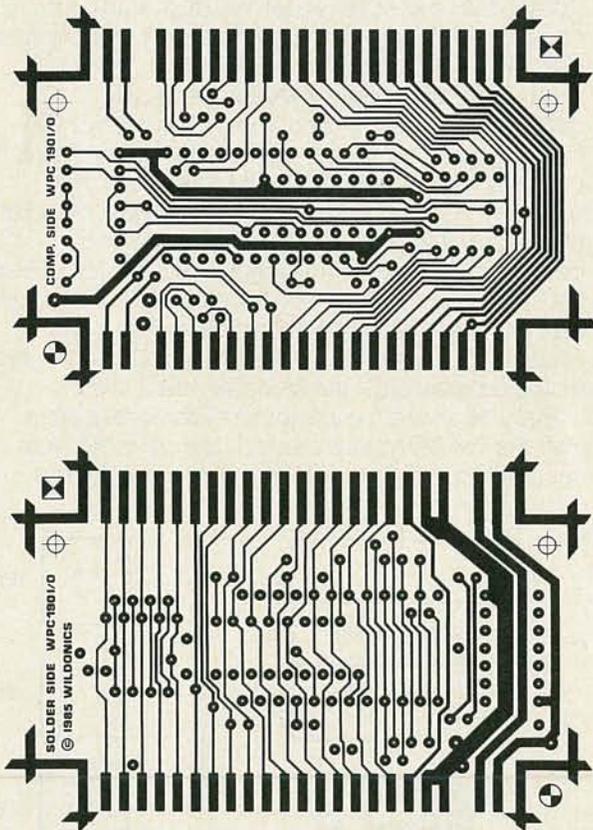


FIG. 3—IF YOU'D LIKE to make your own circuit board, full-size patterns are offered here for both sides. Above is the component side, below, the solder side.

manually switched off in the card area. This is done by replacing the /MREQ trace with a 680-ohm resistor and then connecting the 16K-32K diode's cathode to the end of that resistor. The RAM is then plugged in behind the firmware card.

### Construction

The component and solder sides for the firmware card are shown in Figure 3. This circuit board can be made at home or can be ordered from the supplier given in the parts list. The pattern shown includes jumper traces that place a 2K EPROM in the 8K-10K memory area. To change the EPROM size or memory placement, these traces must be broken and wire jumpers used as shown in Figure 2.

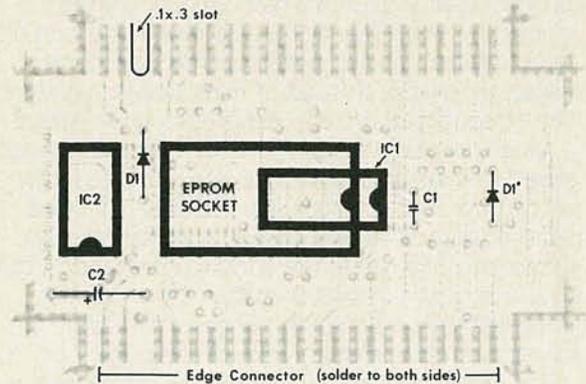


FIG. 4—PARTS PLACEMENT is shown here. Note that IC1 is mounted directly to the board beneath the EPROM. See text.

The parts placement is shown in Figure 4. Note that IC1 is mounted directly to the board under the EPROM. To allow space for this IC, the EPROM socket can be modified on one end, resulting in a U-shaped socket.

Once wired, the firmware card can be placed inside Radio Shack's smallest project case. This case should be sprayed on the inside with aluminum paint and then cut 1/2-inch up on each side to allow for the edge connectors. On one end of the aluminum cover place adhesive foam. On the other end, two holes should be drilled 1/4-inch away from parallel with the two case holes. Plastic 1/4-inch spacers and 1/2 x 4-40 screws thread directly into the board to complete the assembly.

### Other uses

The firmware card can provide many other useful functions missing on the Timex computer. A nice accessory, for instance, would be a Reset button that can be made by connecting a normally open, momentary contact switch between /RESET and ground.

The EPROM socket can also hold an HM6116 2K RAM by changing pin 21 from 5V to the /WR signal. This makes the card ideal for writing custom software in the 8K-16K area.

The interface output can also be used to power a piezo element. A little experimentation with short bursts of output commands should result in some unique sounds and musical tones. ◀▶

# RAMDISK TECHNOLOGY

*Instant-access mass storage*

**Herb Friedman**


■While it might appear that the new super-sophisticated programs do more for the same price—giving something for nothing—a super data-crunching program usually requires a great amount of mass storage. Fortunately, since mass storage in the form of double-sided floppies and hard disks now comes cheap, prodigious amounts of mass storage hardware can be squeezed into anybody's computing budget.

Usually, access time is relative to the amount of data stored: The more you store, the slower it is to locate and access specific information. Because a modern, super-sophisticated data base or spreadsheet might require more time to locate specific information it can usually end up running slower than the similar but older and smaller programs designed for 8-bit computers with a modest amount of storage.

The recommended solution to slow data access is usually something with a catchy high-tech name such as *hyperdrive*, or *superdrive*, or *turbo*drive. Regardless of what it's called, it is actually a portion of a computer's RAM that's been programmed to emulate a disk drive. Usually, the emulation is so accurate that the computer actually sees the RAMdisk as only a disk drive: As far as the computer is concerned, the RAM used for disk emulation no longer exists as free RAM.

The reason why RAMdisk data access is faster than a conventional disk is because to access data on a physical floppy or hard disk the disk must start, come up to speed, and the read/write head must be positioned before it can locate the desired data or an empty space into which new data can be written. A RAMdisk has no such delays because reads and writes are from RAM to RAM: The only delays are those of the applications program and the computer itself as it moves electrical impulses through RAM.

The way in which RAMdisk is used depends on the

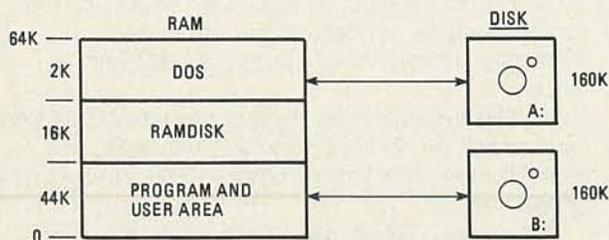

**FIG. 1A**—IN A CONVENTIONAL 8-BIT COMPUTER the RAMdisk is created from the basic 64K of memory. The memory used for the RAMdisk is no longer available to the applications program.

particular software, the computer and the user. In general, particularly with 64K 8-bit computers, the user employs special software to reserve a portion of conventional memory as a RAMdisk only as large as needed for the disk file. The computer recognizes the RAMdisk the same way it recognizes a physical disk. For example, if the computer has physical drives A: and B: the RAMdisk might be C: or D: or M: or whatever. Once the RAMdisk is established in memory the user can read or write to the RAMdisk, or copy the desired data from a physical drive to the RAMdisk by using the conventional DOS PIP or COPY command. Assuming the RAMdisk was assigned the identifier M:, if the user wanted to browse through a computerized mailing list of customers who purchased TV service contracts for the past 5 years he would copy the data file—assume its filename is CONTRACT.DAT—from the floppy or hard disk to the RAMdisk with the command:

```
PIP M: = CONTRACT.DAT (for CPM)
      or
COPY CONTRACT.DAT = M: (for PC/MS-DOS).
```


Using an in-memory word processor, a data base editor, or the computer's LIST or TYPE command, the user could browse through the mailing list—move forward and back—without having to wait for the computer to seek and load from the disk.

## How it's done


If the computer's RAM were unlimited, one could safely create a RAMdisk equal in size, at least to a conventional floppy disk and all the data of a physical disk could be copied into the RAMdisk.

Figure 1A shows how a RAMdisk is usually established in a 64K 8-bit computer having two 160K floppy disks. The program that establishes the RAMdisk positions it in an area that is not used by the disk operating system (DOS). If the user sets up a RAMdisk of 16K, only 48K of RAM is available to the user because the computer no longer "sees" the 16K of RAM that's been set aside for the disk emulation. If the DOS uses 4K, only 44K total memory is available to the applications program in contrast to a total of 60K which would be available if the RAMdisk wasn't used.

Figure 1B shows the computer's functional system after the 16K RAMdisk is created. The computer sees three disk drives: Two of 160K and one of 16K. As a

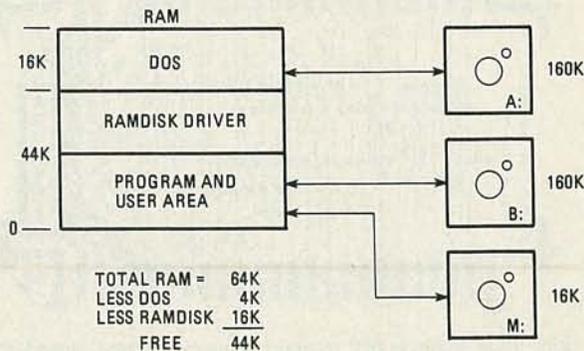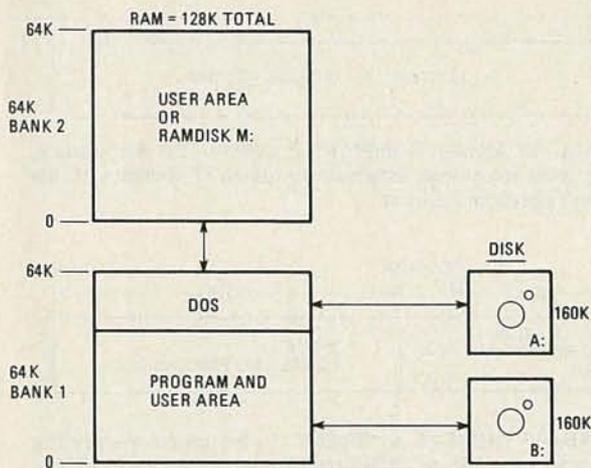

**FIG. 1B**—IF A 64K RAMDISK is created, the functional computer now has three disk drives, but 16K less RAM.

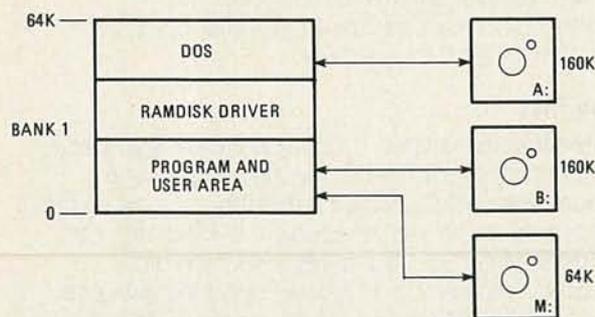


**FIG. 2A—SOME OF THE LATEST 8-bit computers provide a second bank of 64K of memory, part or all of which can be partitioned for use as a RAMdisk or as user RAM.**

general rule, this configuration lasts until the computer is turned off: The memory utilized for the RAMdisk cannot be reprogrammed for use as conventional RAM.

In a 64K computer, the RAMdisk must be as small as possible; if it is made too large, there might not be sufficient memory left to run the applications program. But if enough memory is left for the applications program, the RAMdisk is usually too small for effective handling of the associated data.

But the RAMdisk becomes more useful when the computer can address memory independent of the main computer. For example, the Radio Shack Model 4 was the first 64K machine to accommodate an extra internal 64K bank of memory which could be used for a RAMdisk independent of the main memory, leaving almost all of the conventional 64K in the first bank available for the applications program. Unfortunately, Radio Shack made no provisions for CP/M applications use of the additional 64K. Aftermarket vendors however, provided software which configured the entire extra 64K to function as a RAMdisk. As shown in Figure 2A, the RAMdisk uses the entire second bank of memory, all 64K, for the RAMdisk, while the main computer retains almost its full 64K of RAM (less a smidgen for the RAMdisk software). This results in the system configuration shown in Figure 2B, 64K of memory computer memory plus two full-size floppies




**FIG. 2B—IF THE ENTIRE 64K OF MEMORY in the second bank is used for a RAMdisk the functional computer has three disk drives, but a full 64K of memory (from the first bank of 64K).**

and a 64K RAMdisk; which is far more advantageous for conventional applications programs than the configuration shown in Figure 1B where part of the original 64K of memory is partitioned for a RAMdisk.


An even more advanced RAMdisk system for 8-bit machines uses a completely independent memory external to the original computer. As shown in Figure 3A, a RAMdisk program within main memory manages all of the external memory as a RAMdisk. Since the external memory is really under software rather than inherent computer or operating system control it can be almost any affordable size. 320K is not uncommon. Once a RAMdisk is greater than approximately 160K it can represent one or more floppy disks, and depending on the particular software that creates the RAMdisk(s) everything on the physical disk including the directory can be written or copied to the RAMdisk. If the external RAM is sufficiently large it can be software partitioned to emulate several disk drives. Figure 3B shows how 320K of external memory can represent two independent 160K RAMdisks.

Once we can create a RAMdisk at least equal in size to a conventional floppy, the speed by which an applications program works can be increased by several orders of magnitude.

But if the disk overlay files are copied to RAMdisk the program operation is almost instantaneous because the program no longer has to wait for disk access. Both the reads and writes to "virtual memory" are made to and from RAM. The value of RAMdisk is even more apparent if WordStar is used with a spelling checker. A spelling checker's dictionary—its list of words—is generally so large it must be maintained on its own disk. If the document being spell checked is being stored on a separate data disk (which is usually the way it's done) two disk drives are needed only for the spelling check, and it's often necessary that the dictionary disk be swapped with the word processing software disk in order to randomly access the spelling checker. This is slow, it's frustrating. However, if the spelling checker

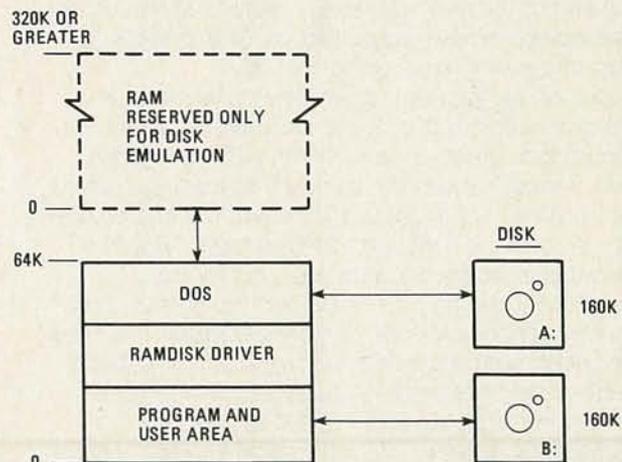

**FIG. 3A—IF EXTERNAL EXPANSION RAMdisk memory can be used almost any practical memory can be used for RAMdisks, such as 320K. These special RAMdisk expansion memories are intended specifically for use as RAMdisks, not for user (program) memory.**

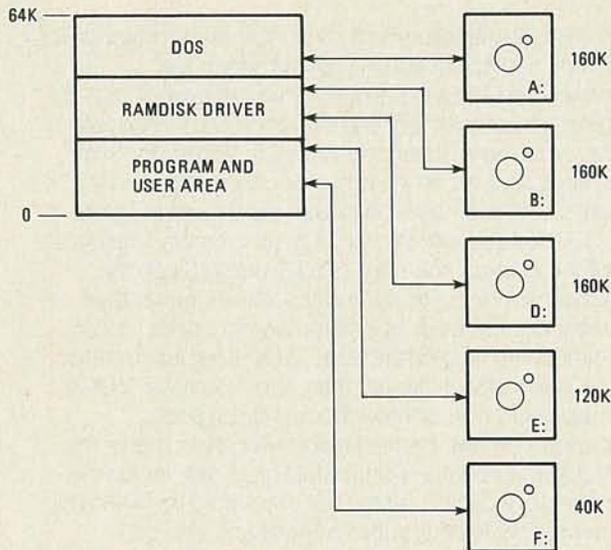

**FIG. 3B—EXPANSION RAMDISK MEMORY** can be partitioned almost any way the user wants it. For example, 320K might be configured to provide three additional drives so the computer sees a total of five.


software is copied into a RAMdisk the program can easily shift back and forth between WordStar and the RAMdisk spelling checker almost instantaneously.

### Full size RAMdisks


Disk emulation in IBM-compatible computers can be handled in several different ways, depending on the amount of installed RAM. If the computer has 256K of RAM disk emulation it's the same as for 64K computers in that part of the RAM is programmed to function as a RAMdisk. But since RAMdisks provide maximum convenience when the emulation is at least equal in size to the floppy with the computer, it makes no sense to create small RAMdisks when the computer has the capacity to emulate full-size disks, for in this way a complete floppy can be easily copied to the RAMdisk. This is easily done in an IBM-compatible computer because of the relatively large amount RAM that can be installed and addressed. (Either the 510K or 640K. To keep things simple we will use 640K.)

One of the features that simplifies RAMdisk in an IBM-compatible is that, as shown in Figure 4A, an applications program can only run with contiguous RAM. If there is a break in the RAM addressing, such as the "missing" 64K in Figure 4B, the applications program can use only the RAM up to the first break. While the RAM above the break cannot be used for the applications program it can be used for utilities, and more importantly, for one or more RAMdisks. The break itself need not be physical: Software can be used to create an artificial break—actually a ceiling beyond which the computer does not see RAM, so the applications software will automatically utilize only the RAM below the break or the ceiling. Figure 4C.


The RAM above the break can be used for a RAMdisk up to the size of the computer's conventional floppy (either 320K or 360K), or the RAM above the break can

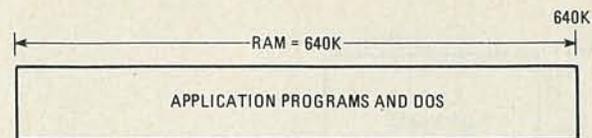

**FIG. 4A—IN AN IBM-COMPATIBLE COMPUTER** the applications program always attempts to utilize all memory to the highest possible address.

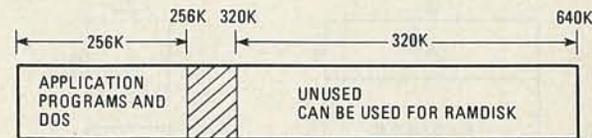

**FIG. 4B—IF THERE IS A "BREAK"** in the memory—say the memory from 256K to 320K is missing—the application program will run only in the contiguous memory starting from zero. The memory above the break can be used for RAMdisks or anything else other than the applications program.

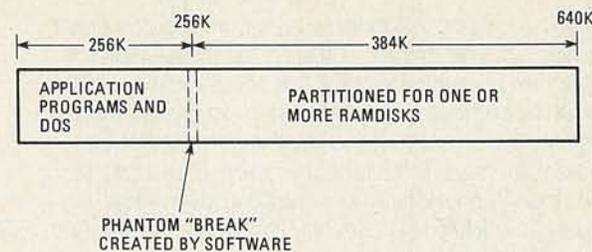

**FIG. 4C—RAMDISK SOFTWARE CREATES** a "phantom break" and configures the memory above the break for one or more RAMdisks. How and in what size the RAMdisks are created are a function of the RAMdisk software.

be partitioned into a full-size RAMdisk and a smaller RAMdisk, or several smaller RAMdisks. The precise disk emulation depends on what the user needs and the software that creates the RAMdisk(s). Others permit any amount of reserved RAM to be used for several RAMdisks of random size.

An IBM-compatible computer doesn't have to be "fully loaded" with memory to create a RAMdisk. If the computer is equipped with only 256K of RAM most of the disk emulation software will permit one or more RAMdisks to be created as long as a minimum of 128K remains for the applications program (including DOS and the RAMdisk software). Often, if the user attempts to create a RAMdisk that will leave less than 128K for the applications software the program will automatically create the largest RAMdisk coincident with 128K of applications RAM.

### Copy first

RAMdisks are volatile. Unless you are using a special kind of memory expansion adapter employing a backup battery that keeps the memory alive when the computer's normal power supply is turned off, both the RAMdisk and its data disappear when the computer is turned off. If you will need the data or a word processed document that's stored in RAMdisk for use at another time, it must be copied to a physical disk before the computer is turned off. ◀▶

# YOU CAN BUILD THIS MODEM FOR YOUR COMMODORE 64

## PART I

*Sure you can build your own modem... And save a lot in the process!*

### **JIM STEPHENS**

■ Modems are expensive but not all that complicated. In fact, they can be quite simple once the function of the main components is understood. Basic modems have two main sections, a modulator and a demodulator. Once these have been built, the rest is easy. Here's how to build your own originate-only modem and save a bundle.

What makes it possible, are two new integrated circuits sold by Radio Shack and other suppliers. The catalog description said that the XR2211 IC was an "FSK decoder used for RTTY and modems." Next to it was another IC, the XR2206 FSK Generator, which had the same caption. The result was better than expected, it worked, and it worked reliably. The circuit could do what it took several dozen IC's in other circuits to do and it did it at less than half the cost of some of the more popular modems for the Commodore 64.

A modem is a circuit that converts serial digital data coming from the computer into tones that can be sent over a single audio channel such as the telephone line. This conversion, called modulation, sends one tone for a digital one and a different tone for a digital zero. The

other section of a modem converts tones from the telephone line to either a digital one or zero depending on the tone's frequency. This function is called demodulation.

Since the telephone is built to handle voice communication, the plus and minus voltages which are generated by the computer cannot be handled by the telephone circuits. If a circuit could recognize a certain voltage and convert that voltage to either high or low tone, digital generated tones could be sent over the telephone line and could be reliably picked up at the other end.

That is exactly what the modem does.

To speed things up a bit, modems actually operate using four tones of different frequency. Two tones are used by the sending terminal and two separate tones of another frequency range are used by the receiving terminal. This way, it is possible for both units to talk at the same time and not interfere with each other's data.

The telecommunications terminal that calls up another terminal is called the originating terminal. Its tones are set at 1070 Hz and 1270 Hz for a digital zero or a one. The receiving terminal is the answering unit

and its tones are higher with a one represented by 2225 Hz and a zero represented by 2025 Hz. When the two tones are changed from one frequency to the next, they are not stopped and started, but shifted up or down in frequency. This is called "frequency shift keying" or FSK. A demodulator circuit recognizes this shift and changes the digital output at its output pin accordingly. The modulator circuit senses a digital one or zero on its keying input pin from the computer and shifts its output frequency either up or down depending on the level of voltage at this input.

Although it is possible to have both the originating and answering capability in one modem, the need for more-complicated circuits outweigh the benefit. After all, most of us would only use our computer to call up another terminal such as Compuserve. We rarely use it to answer unless we are running our own bulletin board. The simple unit shown here is an originate-only modem, but it could easily be converted to answering capability by changing the values of the components as shown in Table I and setting the output tones of the modulator to the higher set of frequencies. It might even work if a separate set of components were on the board and switched into by a set of switches. This would make the modem capable of both origination and answering.

The most expensive part of telecommunicating can be the modem software that generates and converts the digital data once the modem has accomplished its task. The unit shown here works with most of the available software for Commodore modems. It was used with Smart Terminal 64, Victerm, and with Term 64. Many good terminal programs have been published recently in several of the Commodore publications.

### The modem circuit

There are four ICs that make up this modem circuit, but the two major ones are the 2211 FSK demodulator and the 2206 FSK modulator.

As shown in Figure 1, the 2211 demodulator receives the 2225 Hz tone from the earpiece. The level of the received tone is amplified by IC3 which is an LM386 low power audio amp. The discrete components that connect to the 2211 actually set the response frequency of the demodulator. Table I shows the values of the components that set the frequencies at which the demodulator responds. Since we want the demodulator to react to the incoming 2025 Hz and 2225 Hz tones, we have chosen the values for the five components listed under the higher frequency range. Note that the capacitors here should be good quality mylar types to improve the stability of the circuit. Pins 11 and 12 of the 2211 are the oscillator control of the demodulator and this oscillator is peaked by a 5K variable resistor, R7. This is a standard linear taper pot. The tones are transmitted from the earpiece by a small inexpensive speaker.

When a tone in the proper frequency range is detected by the 2211, the demodulator's data output pin goes either high or low depending on the frequency. A tone of 2225 Hz will cause it to go high while a tone of 2025 Hz will cause it to go low.

Adjustment of R7 causes the oscillator to lock onto this frequency range and these adjustments will be discussed in detail later.

The heart of the modulator section is the 2206 FSK generator. Figure 1 shows that it appears as simple as the demodulator but its adjustment is much more complicated than the 2211. It generates a tone of either 1070 Hz or 1270 Hz at pin 2 when either a digital zero or a digital one is detected at its keying pin number 9. The 2206 is capable of producing most any frequency so exact adjustment is necessary in order to produce the correct frequency output.

Pins 7 and 8 of the 2206 connect to the timing resistors that produce the two output frequencies. The value of these resistors is set to produce the two separate tones. Two variable resistors (R13 and R14) have been chosen so that the exact frequency of the tones can be set by hand. R11 is the volume control that determines the intensity of the tone being sent to

### PARTS LIST

#### Resistors

All resistors 1/8-watt  
R1, 4—1,000,000 ohms  
R2, 10, 12—5100 ohms  
R3—510,000 ohms  
R5—200,000 ohms (see table 1)  
R6—18,000 ohms (see table 1)  
R7—5000 ohms Variable  
R8, 13, 14, 16—10,000 ohms Variable  
R9—10 ohms  
R11—25,000 ohms Variable  
R15—200 ohms

#### Capacitors

C1, 4, 7, 10—.1 $\mu$ F ceramic  
C2, 8, 11, 14—10  $\mu$ F electrolytic  
C3, 15—5  $\mu$ F electrolytic  
C5—.005  $\mu$ F ceramic  
C6—.05  $\mu$ F ceramic  
C7—.1  $\mu$ F ceramic  
C9, 12—1  $\mu$ F electrolytic  
C13—100  $\mu$ F electrolytic  
C16—.022  $\mu$ F mylar (see table 1)  
C17—.0047  $\mu$ F mylar (see table 1)


#### Semiconductors

IC1—XR2211 FSK Decoder  
IC2—XR2206 FSK Generator  
IC3, 4—LM386 Low Power Audio Amp  
IC5—4049 CMOS Hex Inverter  
Q1—2N2222 NPN Transistor

#### Miscellaneous

SW1—SPST Switch  
SPKR—8 ohm .5 watt Speaker  
Connecto-Edge Connector (Cinch #50 24A-30)  
Perfboard  
(1) 14 pin WW Socket  
(3) 16 pin WW Socket

NOTE: - A ten-minute cassette tape containing five minutes of continuous telecommunications data and examples of both originating and answering tones may be ordered by sending \$4.00 to Syntronics, 2324 Denwood Dr., Nashville, TN 37214.

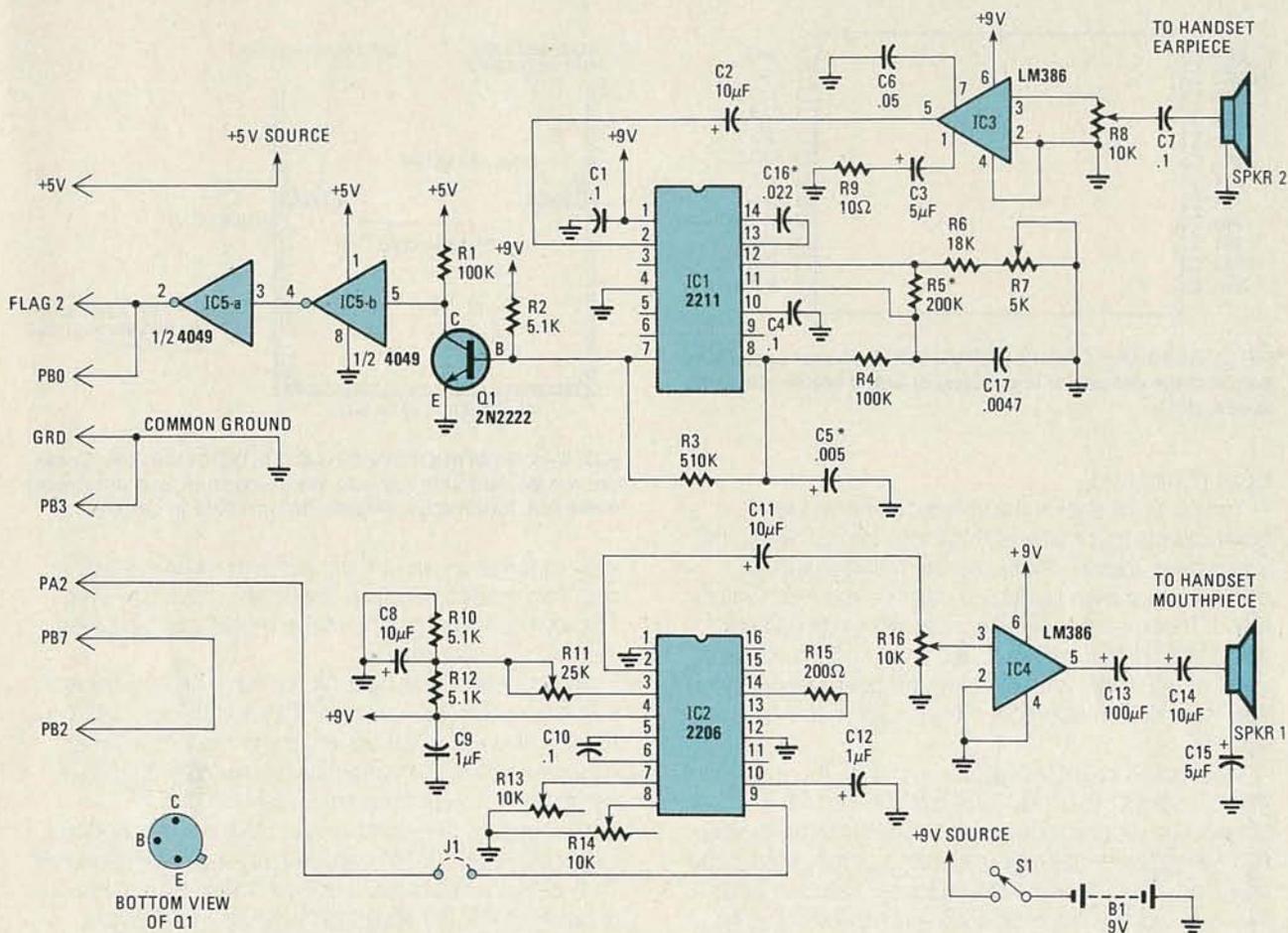

**FIG. 1—SCHEMATIC DIAGRAM OF THE MODEM.** Heart of the system is two IC's, IC1 and IC2 which are an FSK Decoder and an FSK Generator. Balance of circuit is straightforward and supports these devices. \*See Table 1 for values.

IC4 which is an LM386 low power audio amp. The audio amp also has a 10K pot that adjusts the level of the final output to the 8 ohm speaker.

### Circuit power

Notice that both the 2211 and the 2206 are powered by 9 volts. This voltage is necessary because the 2206 will not operate at less than 8.5 volts. Since direct current at 9 volts is not present on the user port of the Commodore 64, we use a 9 volt transistor battery. A small separate power supply could be built to provide this voltage. The modem only draws around 25 ma so the battery should last some time depending on use.

A transistor battery should never be placed on the user port pins. If this were done, the output port of the 64 could be harmed. The output signal of the 2211 demodulator is connected to the 64 through a 2N2222 NPN transistor which obtains its power from the 5 volts on the user port. The signal is then fed through two stages of IC3 which is a CMOS 4049 inverter. The inverter is powered by the computer's 5 volts. This IC shapes the final digital levels before they are presented to the port. Both power supplies have their ground connection in common for proper signal reference.


After extended use, it will be necessary to replace the 9-volt battery since the lower voltage level will cause the modem's output and lock-on frequency to

drift off. This will cause mis-reads in the data. If garbage starts showing up for no reason, suspect low battery voltage. Again, this would not be a problem if a small separate 9-volt supply were constructed, though it would increase the complexity and cost of the circuit. The transistor battery did fluctuate when left off for a long period and would sometimes make re-tuning necessary.

### Wiring the modem board

You must keep the components close together and the leads short or risk stray capacitance which upsets the audio circuits. This is especially true of the LM386 amplifiers. You may hear a local disk jockey coming in on the modulator circuit. This interference disappears once the final connections are made. Make sure you use flexible shielded microphone cable to the speakers. These lines should be no more than ten inches long. They tend to act as antennas and the modem will try to decode the sound of the latest rock group.

IC sockets were used for the integrated circuits and wire-wrap posts for mounting some of the discrete components. One 16 pin IC socket mounted both of the LM386 amplifiers. The sockets were inserted into a 3-inch by 2-inch perf board. Leave the jumper test point (J1) disconnected until the final adjustments have

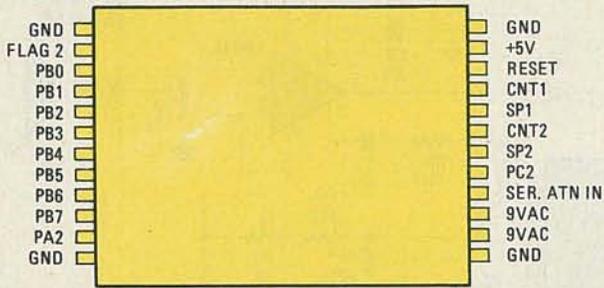

**FIG. 2—DIAGRAM OF THE COMMODORE 64 user port. Make sure that the connector is properly oriented before attaching to user port.**

been completed.

The parts list shows the values for the various components and many of these can be just within the value range shown. Those that are marked with an asterisk and shown by Table 1 must be the exact values listed. Those components connected to the LM386 amps should also be exact. You may want to diagram or label the variable resistors on the board layout since they can get confusing once final adjustments are started.


Connection to the computer is critical. It is important that the correct user port pins are selected for connection. Connections to the board is through very short lengths of hook-up wire. Some of the pins on the user port such as PBO and FLAG 2 are wired in parallel. This is necessary because of the way some software handles the output and input ports. Figure 2 shows the user port pinout which is viewed as though you were looking at the user port from the back of the computer. The connector to the port must always be inserted with the leads correctly oriented to the port pins. Never insert the connector upside down since this would place the unregulated alternating 9 volts of the port on the data lines. This could harm the port also. Some anti-reversing means such as connector keying might be necessary on the connector to prevent accidental backward insertion. I simply marked one side of the connector as "TOP."

The 9-volt power supply is switched on and off by a SPST toggle switch. The 5-volts for IC5 and Q1 are supplied by the computer and it is activated when the 64 is turned on. With this dual power arrangement, it is

**TABLE 1**

FSK BAND	COMPONENT VALUES
300 Baud frequency 1070-1270Hz	C16-.039 $\mu$ F C5-.005 $\mu$ F C17-.01 $\mu$ F R6-18K R5-100K
300 Baud frequency 2025Hz-2225Hz	C16-.022 $\mu$ F C5-.005 $\mu$ F C17-.0047 $\mu$ F R6-18K R5-200K


**TABLE 1—TABLE OF COMPONENT VALUES for the 2211 decoder. If decoder is built to be an answering device, values in the first part of the table should be used.**

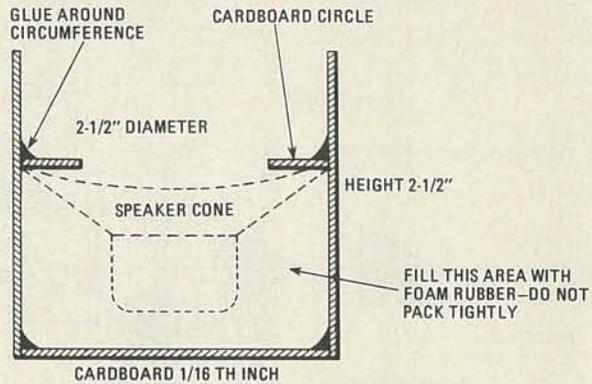

**FIG. 3—CONSTRUCTION OF ACOUSTIC COUPLER. Speakers are backed with foam to keep sound in and interfering noise out. Extraneous noises can turn data to garbage.**

easy to forget to turn off the modem when it is not in use. This tends to shorten the battery life somewhat. The low continuous tone of the modulator alerts you that the unit is operating.

The coupler is the housing for the mike and speaker and into which you insert the handset. It does not have to be elaborate. Use two lengths of heavy cardboard wrapped in a circle which fits the handset snugly. This cardboard circle is then taped around the circumference. The speaker and mike are placed into them and glued. Foam rubber is used to seal the back. The sealing is necessary since the tones are continuous and tend to be irritating after a while. In order to prevent damage to the speakers, a stiff cardboard circle was cut and glued over the speakers to keep the handset from touching them. The leads to the couplers should be short and the couplers can be permanently mounted on a board. Again, use flexible shielded mike cable here. Figure 3 shows how the couplers are constructed. See Figure 4 to examine the author's unit.

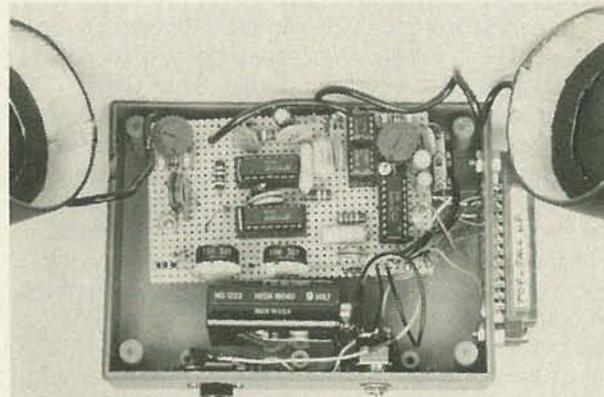

**FIG. 4—AUTHOR'S UNIT with cover removed reveals simplicity of wiring. Component placement is not critical and perfboard works well.**

That's all the room we have in this issue. However, we'll complete the Modem in the December Issue of **Computer Digest**. There's still much information to come!

the sweep jack on the back of the generator. The range of the sweep may be set by rotating RANGE and FREQUENCY controls. Many scopes have a built-in 60-Hz sweep signal that may be used to drive the function generator. Doing so will ensure a steady display on the scope.

The sweep frequency test can be used to diagnose amplifiers that have a buzz or rattle at one frequency. If you have that problem in your amplifier circuit, you'll see a sharp peak at the problem frequency on your scope. However, speakers are more often responsible for that problem than the electronics, and if the problem is in the speaker, you'll see no peaks.

You don't actually need an automatic sweep generator to perform that test; you can do it with a regular signal generator by simply executing a "manual sweep:" just rotate the frequency knob slowly over the entire audio range. At some point the rattle will become apparent, and you'll be able to trace out its source and fix it.

I had a case like that once: One of the seams of a speaker cone had come unglued and caused the speaker to rattle at about 700 Hz, if I remember correctly. At any rate, after I found that loose seam, a small dab of cement solved the problem.

A leaky tube or transistor can also cause clipping and distortion. Many times the best way to diagnose that problem is by substituting new components. That is easy with tubes, but not with transistors, unless the manufacturer was kind enough to use sockets. Many transistor testers can measure leakage; mine reads leakage in the microamp range. Once I found a power transistor with a 10- $\mu$ A leakage—but that was enough to cause distortion! R-E

## SERVICE QUESTIONS

### RESISTOR BURNING UP

*On a Sony KV1910D chassis, I've replaced the horizontal oscillator IC, the horizontal and vertical output amplifiers, and the regulator, all of which were bad. Resistor R556, which sits on the collector of Q511,*

*is burning up. In addition, I have no high voltage, and the voltage readings around the regulator are all wrong.—L.W. Baltimore, MD*

You appear to have two problems here, one of which should be taken care of before you do anything else. The resistor in the Q511 circuit (which incidentally is the starter transistor) is cooking because the transistor is being overworked. The 18-volt scan-derived supply is supposed to switch the transistor off immediately after turn-on. Apparently that 18-volt supply is not reaching the transistor, thereby causing it to stay on.

Now simply start with the basics: Hook up an external 18-volt power supply to get the sweep circuit working. (In the Sept., 1983 issue of *Radio-Electronics* an article "Servicing Horizontal Sweep Circuits" covers the procedure in some detail.) Once you get the high voltage, the regulator problem may fall into place, or at least will be easier to handle.

### AGC PROBLEMS

*A Panasonic model CT-316 that I've been working on has AGC trouble. I have changed the AGC control as well as IC101, the first IF. I've tested all the components in the AGC circuit, and have sprayed around with coolant. I wonder if IC102, the second IF, could be giving me this problem.—L.G., South Portland, ME*

Definitely!—I've seen several of instances in which that was so. And incidentally, I've also seen cases where the IC101 was the culprit, and many cases when the AGC control itself was "spotty," so you did cover all the right steps.

### ARCING AT CRT

*I have a Philco E20-107 chassis that's arcing between pins 9 and 11 of the CRT. After I changed the spark gap located on the tripler, R970 (tied onto pin 11) began to smoke. Those spark gaps have me confused. Can you help me?—T.D., Corbin, KY*

I think you have a bad tripler. An internal short is placing part or most of the high voltage at the focus terminal. That voltage (looking for the path of least resistance) will jump across the spark gap, the CRT pins or, in your case, through R970.

# McIntosh®

Get all the newest and latest information on McIntosh stereo equipment from McIntosh Laboratory.



Send For Your Stereo Information

McIntosh Laboratory Inc.  
East Side Station P.O. Box 96  
Binghamton, N.Y. 13904-0096

RE

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Phone Area Code \_\_\_\_\_

CIRCLE 67 ON FREE INFORMATION CARD

# PROBES FOR SALE

FROM THE BEST SOURCE FOR OSCILLOSCOPE PROBES AND DMM/VOM TEST LEAD SETS.

- Low Cost
- High Quality
- Excellent Performance
- Slender, Flexible Cable
- Wide Range of Choice
- Switchable X1 and X10 Attenuation Factor
- 100 MHz Bandwidth

MODEL SP100  
**\$41<sup>00</sup>**

**TEST PROBES, INC.**



Your Probe Specialists

COLINE U.S. SALES & STOCKING SOURCE


P.O. BOX 2113, LA JOLLA, CALIFORNIA 92038 (619) 459-4197

CIRCLE 123 ON FREE INFORMATION CARD
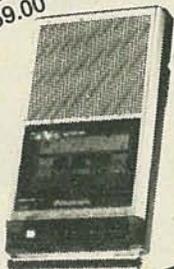
## SUPER LONG PLAY TAPE RECORDERS

10 Hour Model — \$95.00\*  
14 Hour Model — \$159.00\*

Modified Panasonic Slimline, high quality, AC-DC Recorders provide 5 or 7 continuous hours of quality recording & playback on each side of cassette for a total of 10 or 14 hours depending on model. Built-in features include • Voice level control, • Digital counter, etc. TDK DC 180 Cassette Furnished.



### PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up. **\$24.50\***



### VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike. **\$24.95\***



\*Add for ship & hdg. Phone Adapter & Vox \$1.50 ea. Recorders \$4.00 ea. Cal. Res. add tax. Mail order, VISA, M/C, COD's OK. Money Back Guarantee. Qty. disc. avail. Dealer inquiries invited. Free data. © **AMC SALES INC.** Dept A 9335 Lubec St., Box 928, Downey, CA 90421 (213) 869-8519

CIRCLE 108 ON FREE INFORMATION CARD

## CABLE TV CONVERTER REPAIR

- ▷ ALL MAKES
- ▷ ALL MODELS
- ▷ 7 DAY TURNAROUND
- ▷ FLAT RATE PRICING BY MODEL

CALL FOR INFORMATION

### "THE CONVERTER SHOP"

794 Franklin Lakes Ave.  
Franklin Lakes, NJ 07417  
Tel. (201) 848-8229

## ROBOTICS

continued from page 90

ceive functions. In addition, the same tuned circuit is used for both transmitting and receiving, so you don't have to worry about frequency mis-matching due to component drift.

Transmission is initiated by applying a logic "1" to pin 8 of the LM1812. The receiver will be disabled, and pin 14 will be low. To receive, pin 8 is simply grounded. Pin 14 will go high after the circuit receives an echo of the signal.

The time between initiating transmission and pin 14's going high is then equal to the time required to travel from the transmitter to the object and back. So to obtain the distance to the object, that time would be halved and plugged into the formula  $D=V/T$  ( $V=13,080$ ). The circuit shown in Fig. 3-a has a range from 4 inches to about 6 feet. By adding the 555 circuit shown in Fig. 3-b, the low end of the range may be decreased to 3 inches, and the high end increased to 20 feet. Potentiometer R2 should again be adjusted to a frequency of 40 kHz.

That circuit is so simple and so inexpensive that you could build several for one robot.

### Polaroid's ultrasonics

Polaroid Corporation has been using ultrasonic ranging in cameras such as the SX-70 for some time now. Distance information obtained through ultrasonics is used to focus the camera's main lens automatically. The transducer used has a larger diameter and is slimmer than the type usually found in electronics surplus stores. Several years ago Polaroid packaged the electronics from their cameras along with a good tutorial manual, as well as an interesting experimenter's board. The package is called the "Polaroid Ultrasonic Ranging System Designer's Kit," and is available for \$165 from the Polaroid Ultrasonics Components Group (Polaroid Corp., 119 Windsor Street, Cambridge, MA 02139). It comes with a special interface that displays distance information on an LED readout.

R-E

## AUDIO COMPANDING

continued from page 70

what happens when a burst of 15-kHz pulses is sent through a compander circuit. The upper trace shows the input signal; the middle trace shows the signal after it has been processed by the compressor; and the bottom trace shows how it has been restored to its original form after being processed by the expander.

### Automatic level control

The NE570/1 may be used for ALC (Automatic Level Control). In that configuration, the  $\Delta$ -G cell is placed in the feedback loop of the op-amp, and the rectifier

stant. The gain equation is:

$$A_v = \frac{R_1 R_2 I_B}{2 R_3 V_{IN(avg)}}$$

For very low input levels, ALC may not be desirable because the high gain would accentuate transmission noise. Resistor  $R_x$  has been added to limit the gain. The modified gain equation is:

$$A_v = \frac{\left( \frac{R_1 + R_x}{1.8} \right) R_2 I_B}{2 R_3}$$

The value of  $R_x$  may be calculated as follows:

$$R_x = (A_v \times 26,000) - 10,000$$

All remarks made above regarding DC biasing, maximum signal levels, AC cou-


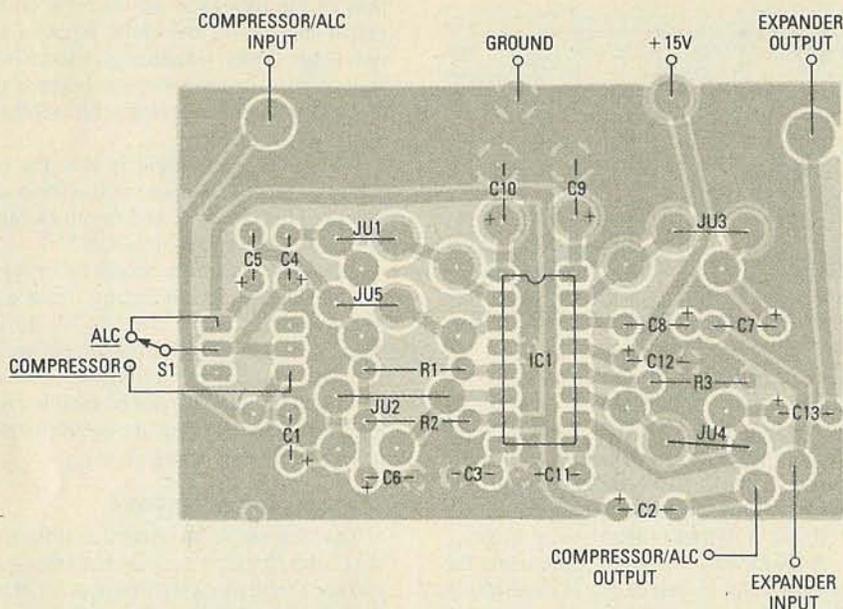


FIG. 12—COMPONENT-PLACEMENT DIAGRAM for the experimental compander circuit that is shown in Fig. 10.

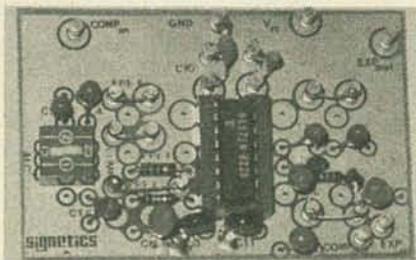

THE COMPLETED COMPANDER lets you make recordings with wide dynamic range and less noise.

is connected to the input. A sample circuit is shown in Fig. 9.

The circuit functions as follows. As the amplitude of the input signal increases above the crossover point, the gain of the  $\Delta$ -G cell decreases proportionally, and that keeps the output level constant. As the amplitude of the input decreases below the crossover point, the gain of the  $\Delta$ -G cell increases proportionally, which again keeps the output amplitude con-

pling, and attack/decay time constants may be applied to the ALC circuit.

The oscilloscope photograph in Fig. 10 shows the response of the ALC circuit.

### Experimental compander circuit

Shown in Fig. 11 is the schematic for a circuit you may use to experiment with companders. The circuit uses a NE570 or NE571 (or SA571), and provides one channel of compression and one channel of expansion. In addition, the compression channel may also be configured to function as an ALC circuit merely by flipping a switch. Full-size printed-circuit artwork is shown in the "PC Service" section of this magazine, and the component-layout diagram for that board is shown in Fig. 12.

Space has been reserved on the PC board for RC pre- and de-emphasis networks. If you have no need for them, simply install jumpers JU1 through JU4; JU5 should be installed in any case. R-E

## Versatile Lab Power Supply



MODEL 3002A

EXCEPTIONAL VALUE!

Only \$125<sup>00</sup>

- 0-30 VDC at 0-2A • Excellent Regulation
- Ripple & Noise - 500  $\mu$ V RMS • Built-in Short-Circuit and Overload Protection

Model 3002A features continuously adjustable current limiting and precision constant voltage/constant current operation with "automatic crossover." This lab-grade unit can also be used as a current regulated power source. Options: 10-Turn Voltage and Current Controls, \$25.00 ea.

DISTRIBUTOR INQUIRIES INVITED  
DOMESTIC & FOREIGN



**ELECTRO INDUSTRIES**

4201 W. Irving Pk., Chicago, IL 60641  
312/736-0999

CIRCLE 83 ON FREE INFORMATION CARD

## ELECTRONIC COMPONENTS



MANUFACTURERS OF QUALITY  
ELECTRONIC COMPONENTS

- BATTERY CLIPS & HOLDERS
- CABLE SETS • CONNECTORS • CAPACITORS
- DISPLAYS • LEDS • FUSES • JACKS & PLUGS
- KNOBS • LAMPS • POTENTIOMETERS
- RF COILS • RELAYS • RESISTORS
- SWITCHES • SEMICONDUCTORS • SPEAKERS
- TEST EQUIPMENT • TRANSFORMERS • TOOLS
- WIRE & CABLE

OVER 15,000 DIFFERENT ITEMS IN STOCK!

- Sales and Order Desk Open from 8:00a.m.(PST)
- TERMS: C.O.D., Visa, MasterCard (Open Accounts Available)
- Phone and Mail Orders Welcome
- Catalogs Mailed Outside USA Send \$2.00

**MOUSER ELECTRONICS**

11433 WOODSIDE AVE SANTEE CA 92071  
PHONE (619) 449-2222 TWX 910 331-1175

CIRCLE 117 ON FREE INFORMATION CARD

NOVEMBER 1985

109

Learn micro-processing with the new  
**MICRO-PROFESSOR 1P**



Students, engineers or technicians—  
upgrade your micro-processing skills  
with the new Micro-Professor 1P.

**The MPF-1P features:**

- extensive software support
- more built-in memory
- improved keyboard
- larger display

Three tutorial guides help cover all  
capabilities. The ideal training tool!  
MPF-1P will deliver you into the growing  
world of micro-processing. Invest now!

**Plus—FREE GIFT** Only **\$179.95**

Check this box for FREE  
Z-80 Microprocessor  
Programming and  
Interfacing textbook when  
you order within 7 days.  
\$12.95 value. (Include  
\$5.00 postage &  
handling)



Dept. RE1085  
5326 9th Ave. N.E.  
Seattle, WA 98105-3617

For immediate action call TOLL FREE:

**1-800-426-1044**

Full money back guarantee.



CIRCLE 111 ON FREE INFORMATION CARD

**Get  
professional  
quality at home.**



KeproClad is the quick, easy and inexpensive approach to home production of quality printed circuit boards. Minimum investment required.

**Complete package.**  
KeproClad comes packaged—pre-sensitized negative acting dry film photoresist. Extremely rugged yet holds fine lines. Available in two sizes with one or two-sided copper foil. Developer included.

For your local distributor write or call:  
1-800-325-3878 1-314-343-1630 (in Missouri)



Kepro Circuit Systems, Inc.

630 Axminster Drive, Fenton, MO 63026-2992

RADIO-ELECTRONICS

110 CIRCLE 268 ON FREE INFORMATION CARD

**DIGITAL IC'S**


*continued from page 76*

the present value is loaded into the counter, the circuit will increment one step for each negative-going transition of clock line **CLOCK1**.

**Down counters**

The counter circuits presented thus far are up-counters; that is, they increment one step for each active transition of the clock line. A down-counter, on the other hand, decrements for each active transition of the clock line.

Figure 7 shows an example of a base-16 down-counter. Note the difference between that circuit and the base-16 up-

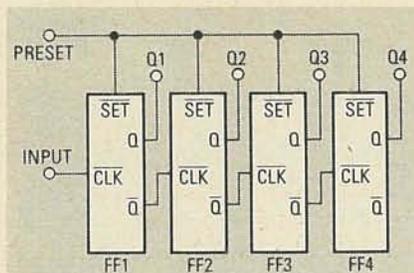

**FIG. 7—IN A DOWN COUNTER, the count decrements. Thus, the count after 0000 is 1111.**


counter of Fig. 2. In the *up* version, the flip-flops are connected in cascade by connecting the **Q** output of the driving stage to the clock input of the following stage. In the *down* counter version, the clock input of the following stage is driven from the  $\bar{Q}$  output of the driving stage.

A BCD version can be made using the BCD counter circuit of Fig. 4 modified in the same way; that is, all clock inputs are driven by the  $\bar{Q}$  (instead of the **Q**) output of the preceding stage. Also, the **NAND** output resets only the two middle flip-flops.

**Up/down counters**

An up/down counter is designed to operate as either an up-counter or a down-counter, depending upon the state of the signal (high or low) applied to a special **MODE** input. Figure 8 shows the circuit for a two-stage up/down counter.

To see how that circuit operates, recall

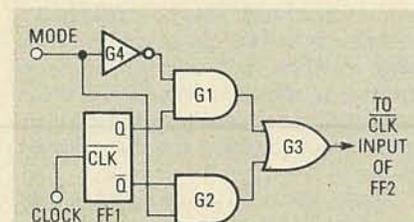

**FIG. 8—AN UP/DOWN COUNTER. The direction of the count is determined by the state of the **MODE** input.**

the differences between up and down counters: in the down-counter, the clock is driven from the  $\bar{Q}$  output, while in an up-counter the clock is driven from the **Q** output of the preceding stage. In Fig. 8, the state of the signal at the **MODE** input determines which output drives FF2.

Gates **G1** and **G2** are **AND** gates whose outputs will be high only when both inputs are high. One input for **G1** and **G2** is taken from **Q** and  $\bar{Q}$ , respectively. The **MODE** input is used to provide the second input. For **G1**, that input is first inverted and then fed to the gate; for **G2**, that input is fed directly to the gate.

When the **MODE** input is high, a low is fed to **G1** and a high is fed to **G2**. In that situation, the output of **G1** is always held low, while the output of **G2** is high when  $\bar{Q}$  is high, and low when  $\bar{Q}$  is low. The outputs of the two gates are then **OR**'ed together and fed to the clock input of the next stage. In the situation just described, the counter is a down-counter because the clock input of the next stage (**FF2**) follows the  $\bar{Q}$  output of **FF1**.

When the **MODE** input is low, the opposite occurs. The input to **G1** is high and the input to **G2** is low, and the clock input of **FF2** follows the **Q** output of **FF1**.

Of course, there are many other types of counter circuits, including those with division ratios other than 2, 10, or 16. Also, while all of the counters that we've presented thus far are decodable, some are not. Such circuits can not be used to present numerical data, but are useful for pre-scaling and other applications.

**Clocking considerations**

Thus far, we've proceeded as if the timing of the clock pulses was not critical. If you stick with clocking frequencies of under 1 MHz and pulse widths of over 1  $\mu$ s, that is indeed the case. Otherwise, there are certain timing parameters that you should be aware of. Those parameters are specified by the manufacturer, and differ for each device. They can be found on the IC's data sheet. Let's briefly go over some of those parameters and what they mean.

The *setup time* refers to the minimum time that an input must be stable before clocking occurs. The *hold time* refers to the minimum time that the input must be stable after clocking occurs. *Minimum reset time* refers to the narrowest width pulse that can be used to reset the device. *Minimum clock-high time* refers to the narrowest pulse width that can be used for clocking. *Maximum clock frequency* is the fastest clock speed that should be used. Propagation delay is the length of time between clocking and a change in the output state.

*Monostable multivibrators*, also called *one-shots*, are circuits that output just one pulse for every trigger pulse received. Next time, we'll turn our attention to those interesting circuits.

**RE**

## SATELLITE TV

continued from page 12

available on a number of satellite channels. Thus, while the ESPN numbers are surprisingly high—considerably higher than with cable TV viewers—once again no hard conclusions should be drawn from the study's figures.

TVRO owner use-patterns change with time: although 6.6% of those surveyed said news was their most-viewed type of program, that number rises to 11.1% for owners of systems three or more years old. Interest in sports programming also declines as length of ownership increases, and viewing of religious channels nearly triples with long-time viewers.

### The future

Defining who TVRO users are, why they buy, and how they use their TVRO systems is a very important task for the home-TVRO industry. That point was driven home when retail sales of home systems fell off sharply this past spring, and several long-established equipment suppliers in the receiver and antenna field found themselves requesting court protection from creditors.

The consensus is that the first 1,000,000 TVRO systems bought (a mark reached this past May) may have been "easy sales" because buyers were eager to purchase after their first exposure to TVRO. However, fears that the market may have become saturated are not supported by the study. What the study does show is that "shot-gun" sales techniques, which lack coordinated market planning and direction, may not work as well in the future as they have in the past.

The TVRO distribution chain is going through a difficult year of adjustment. Radio Shack is expected to formally announce their own line of TVRO hardware in their September catalog—and that line will be featured on the front cover. Other large distribution outlets also plan entry into the marketplace during late 1985 and early 1986, so TVRO selling patterns are going to continue changing rapidly. **R-E**

## NEW IDEAS

continued from page 8

use a 74LS14 and eliminate R2. That resistor is what gives the circuit its "snap-action," and is unnecessary with a 74LS14, as that IC has the proper circuitry built right in.

How you wire the cassette interface is not critical, but you should use a socket for IC1, and connect all unused inputs (pins 5, 9, 11, and 13) to ground. That applies whether you're using a 74LS04 or a 74LS14 for IC1. Make sure you choose plugs that match your recorder's input, output, and remote jacks. If you'll be using our circuit with a VIC, you can eliminate the relay, as VIC's don't control cassette motors. Switch S1 can be virtually any SPST or SPDT type.

After you've got the circuit wired up, check everything over! Reversing pins A1 and B2 on the computer connector could be disastrous! When you're sure everything is OK, plug PL1, PL2, and PL3 into your recorder, turn on the power, and save a *short* file to tape. Don't forget to close S1 when the prompt appears on the screen. (And always open the switch when you're done saving or loading.)

Next try loading your file back into memory. If you can't load your file, first make sure it was recorded. Rewind the tape, pull plug PL2, and listen. You should hear a high-pitched whirring sound. If that's OK, try connecting an LED through a 330-ohm resistor to pin D4 on the computer connector. With everything hooked up you should see the LED flicker on and off rather rapidly. If it doesn't, there's probably a wiring error. Trace out your connections, and if they still seem OK, IC1 may be at fault.

Disk owners may find our circuit handy as a means of backing up valuable data disks. Just load your files from disk in the usual manner, and save to tape similarly. By the way, very low-cost cassettes *don't* make good storage media for computer data. Those cassettes frequently suffer from "drop-outs." If that happens in the wrong place, a whole tape could be rendered useless—so don't scrimp on tapes!—*Micheal R. Lockwood*

SEE YOUR DEALER TODAY

FROM

**Firestik®**  
ANTENNAS  
ACCESSORIES

HERE'S A TIP  
THAT'S PERFECT!

AM/FM AUTO RADIO  
AND CB

**'Firestik®' II**  
GOLDEN SERIES

BARE-HANDS TUNABLE  
"NO TOOLS NEEDED"  
HIGH PERFORMANCE ANTENNAS

ALSO ANTENNAS FOR  
CORDLESS TELEPHONES  
MONITOR SCANNERS

Dealer & Distributor Inquiries Invited  
SEND FOR FREE CATALOG

'Firestik' Antenna Company  
2614 East Adams/Phoenix, AZ 85034

Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

Serving the CB and  
Communications Market Since 1962.

**5 YEAR REPLACEMENT WARRANTY**

CIRCLE 100 ON FREE INFORMATION CARD

## A growth market.

The kids of today are the doctors and nurses, the engineers and scientists, the teachers and journalists, the leaders of tomorrow.

It will take your company's help to assure these children a first-rate college education because today colleges are having a hard time coping with the high costs of learning.

Please give to the college of your choice.

You'll be making an investment in the best growth market of America.

Send for our free booklet: "Guidelines - How to Develop an Effective Program of Corporate Support for Higher Education." Write CFAE, 680 Fifth Avenue, New York, NY 10019.



Invest in the future of America.  
Give to the college of your choice.

A PUBLIC SERVICE OF THE PUBLICATION AND ADVERTISING COUNCIL. COUNCIL FOR FINANCIAL AID TO EDUCATION, INC. 680 FIFTH AVENUE, NEW YORK, NY 10019

NOVEMBER 1985

## NEW PRODUCTS

continued from page 42

price of 39.95.—**AP Products, Incorporated**, 9325 Progress Parkway, PO Box 540, Mentor, OH 44060.

**GRAPHIC EQUALIZER**, model *CY-SG60*, is a 7-band graphic equalizer/booster amplifier, and measures 1 inch in height. Combined with most Panasonic compact

chassis car-audio units, it fits snugly into the dashboards of many cars that are manufactured in the U.S.A.

Dual inputs allow the model *CY-SG60* to be connected to car-audio units with pre-amp output, or to units with speaker output only. A total maximum output power of 50 watts, and THD of less than 1% at 12 watts per channel helps ensure clear sound at high volume levels. A tone defeat/attenuator switch reduces volume by 20 dB to mute

sound output without changing volume-control settings. The



CIRCLE 27 ON FREE INFORMATION CARD

unit's controls are illuminated.

With the model *CY-SG60*'s remote power switch, the unit can be turned on automatically with the main car audio unit. Efficient heat dispersion is provided by a specially designed heat sink. The suggested retail price is \$119.95.—**Panasonic**, One Panasonic Way, Secaucus, NJ 07094.

**VIDEO DISPLAY TERMINAL**, the model *ADM 11plus*, incorporates all of the features of the model *ADM 11* with additional function keys and editing capabilities.

The *ADM 11plus* is compatible with the Lear Siegler *ADM 3A*, *ADM 5*, and *ADM 11*, *ADDS Viewpoint* and *Regent25*, *Hazeltine 1400*, *1420*, and *1500*, and *DEC VT52* terminals.



CIRCLE 28 ON FREE INFORMATION CARD

This conversation-mode terminal features 16 function keys for 16 programmable and 16 non-programmable functions, and will handle transmissions up to 19,200 baud without handshaking. The terminal also features three edit keys and a break key, which can be programmed to perform an additional seven functions. Editing features include character/line insert, character/line delete, line erase, and page erase.

The model *ADM 11plus* is priced at \$695.00.—**Lear Siegler, Inc.**, 901 East Ball Road, Anaheim, CA 92805. **R-E**

## Radio-Electronics REPRINT BOOKSTORE

- |   |   |
|---|---|
| <input type="checkbox"/> Radio-Electronics back issues (1985) ..... \$3.00<br>Write in issues desired _____   | <input type="checkbox"/> Special Projects #4 (Summer 1982) ..... \$4.50                                     |
| <input type="checkbox"/> Radio-Electronics back issues (1984) ..... \$3.50<br>(January 1984 not available)<br>Write in issues desired _____                     | <input type="checkbox"/> Special Projects #5 (Winter 1983) ..... \$4.50                                     |
| <input type="checkbox"/> Radio-Electronics back issues (1983) ..... \$3.50<br>(January, February 1983, May 1983 not available)<br>Write in issues desired _____ | <input type="checkbox"/> Special Projects #6 (Spring 1983) ..... \$4.50                                     |
| <input type="checkbox"/> Radio-Electronics back issues (1982) ..... \$4.00<br>Write in issues desired _____   | <input type="checkbox"/> Special Projects #7, #8, #9 ... NOT AVAILABLE                                      |
| <input type="checkbox"/> Radio-Electronics back issues (1981) ..... \$4.00<br>(Jan., Feb., March, Dec. 1981 not available)<br>Write in issues desired _____     | <input type="checkbox"/> Special Projects #10 (Spring 84) ..... \$4.50                                      |
| <input type="checkbox"/> Etch your own PC boards ..... \$3.00   | <input type="checkbox"/> Radio-Electronics Annual 1983 ..... \$3.50   |
| <input type="checkbox"/> Hands On Electronics #1 ..... \$4.00   | <input type="checkbox"/> Radio-Electronics Annual 1984 ..... \$3.50   |
| <input type="checkbox"/> Hands On Electronics #2 ..... \$4.00   | <input type="checkbox"/> Radio-Electronics Annual 1985 ..... \$2.50   |
| <input type="checkbox"/> Hands On Electronics #3 ..... \$3.50   | <input type="checkbox"/> How to Make PC Boards ..... \$2.00   |
| <input type="checkbox"/> Hands On Electronics #4 ..... \$3.50   | <input type="checkbox"/> All About Kits ..... \$2.00  |
| <input type="checkbox"/> VCR Repairs ..... \$3.00   | <input type="checkbox"/> Modern Electrics (Vol. 1, #1 ..... \$2.25<br>April 1908)                           |
| <input type="checkbox"/> IBM Typewriter to<br>Computer Interface ..... \$3.00   | <input type="checkbox"/> Electro Importing Co. Catalog ..... \$4.95<br>(1918) (176 pp)                      |
|   | <input type="checkbox"/> Low Frequency Receiving Techniques ..... \$6.00<br>Building and using VLF Antennas |
|   | <input type="checkbox"/> New ideas - 42 circuits for experimenters .. \$3.50                                |
|   | <input type="checkbox"/> Descrambler (Jan., Feb., 1981) ..... \$3.00  |
|   | <input type="checkbox"/> Descrambling (Feb., 1984) ..... \$2.00   |

To order any of the items indicated above, check off the ones you want. Complete the order form below, **include your payment**, check or money order (**DO NOT SEND CASH**), and mail to Radio-Electronics, Reprint Department, 200 Park Ave. South, New York, NY 10003. Please allow 4-6 weeks for delivery.

If you need a copy of an article that is in an issue we indicate is unavailable you can order it directly from us. We charge 50¢ per page. Indicate the issue (month & year), pages and article desired. Include payment in full, plus shipping and handling charge.

ARTICLE \_\_\_\_\_

PAGES \_\_\_\_\_

MONTH \_\_\_\_\_

YEAR \_\_\_\_\_

TOTAL PAGES \_\_\_\_\_

@50¢ each

TOTAL PRICE \_\_\_\_\_

MAIL TO: **Radio-Electronics**

Reprint Department, 200 Park Ave. South, New York, NY 10003

All payments must be in U.S. funds

Total price of order ..... \$ \_\_\_\_\_

Sales Tax (New York State Residents only) ..... \$ \_\_\_\_\_

Shipping & Handling (U.S. & Canada only) (Includes FIRST CLASS POSTAGE) \$1.00 per item ..... \$ \_\_\_\_\_

All other countries (\$2.00 per item, sea mail) ..... \$ \_\_\_\_\_

(\$4.00 per item, air mail) ..... \$ \_\_\_\_\_

Total Enclosed ..... \$ \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## PULSE GENERATOR

*continued from page 59*

Connect an oscilloscope to either the TTL or the CMOS clock output, set S1 to FREE RUN, and verify that R1 and S3 vary the clock speed as expected. Toggling switch S8 should invert the output. Next connect the scope to one of the pulse outputs. With S2 in the DIRECT position, R6 and S6 should vary the width of the pulses, and S5 their polarity. R1 and S3 vary their repetition rate, of course.

With S2 in the EXT. TRIGGER position, each low-to-high transition on jack J6 should cause a pulse of the selected width and polarity to appear at jacks J2 and J3. Similarly, with S2 in the ONE-SHOT position, each time S7 is depressed a pulse of the selected width and polarity should appear at those jacks.

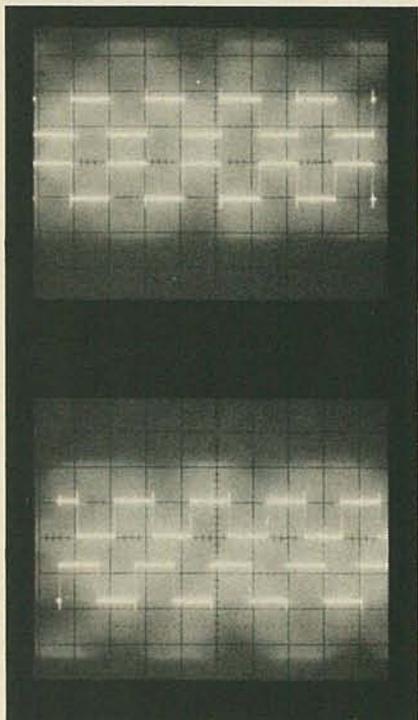


FIG. 3—THE TOP TRACE of each oscilloscope photograph shows the pulse output, while the bottom trace shows the clock output. The pulse output in *a* is direct, while that shown in *b* is delayed by about 7 microseconds.

You'll need a dual-channel scope to test the delay function. Place S2 in the DELAYED position. Connect one channel to a clock output and one channel to a pulse output. If your scope has a separate SYNC input, connect it to the pulse generator's SYNC OUTPUT jack, J1. Now by varying S4 and R8, you should be able to vary the length of time (from 1  $\mu$ S to 100  $\mu$ S) that the pulse train lags behind the clock output. Figure 3 shows two oscilloscope photographs, one showing zero delay, and the other showing a delay of about seven  $\mu$ S.

When everything checks out, mount

the PC board to the chassis with short standoffs, tighten all hardware, and screw the cabinet together.

### Practical applications

Our pulse generator may be used to troubleshoot or test already-existing equipment; it may be used to aid the design of new equipment, and it may also be used for experimental and educational purposes.

For example, the pulse generator could be used to troubleshoot a high-speed clocked-logic system that seemed to be missing pulses and giving erroneous outputs. You could disconnect the system clock from the piece of equipment under test, and then substitute the pulse generator's clock output. Then, by running that device at a slower rate—perhaps one pulse at a time—you would find it easier to trace a signal through the system. That sort of procedure won't always work; NMOS microprocessors, for example, often cannot be run below about 250 kHz. But you can usually slow things down enough to be able to see what's going on better than at the full clock rate.

You can use the pulse generator to experiment with shift registers and counters. Wire up your circuit on a solderless breadboard and single-step through all logic states.

For example, suppose you have a circuit built around a 4018 presetable divide-by-*n* counter. That IC has five "jam" inputs and five (complemented) data outputs. The outputs may be recycled, in various combinations, to the IC's DATA input, allowing division of the input clock by any ratio between two and ten. The only hitch is that division by an odd ratio (three, five, seven or nine) requires use of an external AND gate.

Anyway, suppose your design requires outputs that cycle from four to nine and then reset (i.e., start counting from four again). You have wired the circuit up, but there is a bug; the circuit counts from four to eight and then resets. Feeding the pulse generator's output to the 4018's clock input and monitoring the IC's outputs, you discover that you have forgotten to AND the  $\bar{Q}_4$  and  $\bar{Q}_5$  outputs.

To synchronize pulse output with an external clock, connect the clock to J6 and place S2 in the EXT. TRIGGER position. If you need one output pulse for a predetermined number of clock pulses, simply insert a divider IC between the clock source and J6. The 4059 is a programmable divide-by-*N* counter which can be used for that purpose. That IC can divide the frequency of the clock fed to it by any ratio between three and 15,999. If your work involves much of that sort of thing, there is room on the PC board to mount several extra IC's. You would then mount appropriate division-ratio selection switches on the front panel. **R-E**

## REMOTE-CONTROLLER

*continued from page 66*

The example circuit uses the 4029B up/down binary/BCD counter, since that is the most flexible type available. Not only is that counter capable of counting up or down, but it can count in either straight binary or BCD formats. In addition, it is presetable and cascadable. If the alternate counting format is not needed, the similar 4510B or 4516B binary counters can be used.

Whichever of the three counters is used, a single device will give a total of 10 or 16 steps. All three types can be cascaded to a second counter, giving 100 or 256 steps. One continuous command should be used to step the counter up, and a second to step it down. Gating could be added to prevent over- and under-flow by disabling the UP enable when the maximum count is reached, and disabling the DOWN enable when the all-zero state is reached.

That type of decoder could be used in a number of ways, the most flexible of which is to interface its outputs with a resistor string or an IC digital-to-analog converter to obtain an analog voltage output. A series of optocouplers and such a resistor string could be used in standard D/A format to replace a potentiometer on the controlled device.

The data port has been left out of this discussion, since it is meant primarily to carry channel numbers, tuning frequencies, and other numerical data. However, if the controller is converted to single-digit operation, another BCD or hex 1-of-*n* line decoder could be added via that port, giving 20 or 32 separate enable lines.

There are a number of methods that can be used to interface the CMOS outputs of the various decoders to the controlled device; let's examine some of those next. If the device is digital and uses a matching 5-volt supply, often the outputs can be directly connected. However, if more current is needed, power drivers such as transistors must be added to the CMOS outputs. If different voltages are used in the controlled device, either power driver IC's or optocouplers must be used. Light-duty reed relays can be used without special driver circuitry.

It's now up to you to take the 14457/14458 remote control system and use those output devices (or a system of your own) to interface it to what you want to control, be it a TV, VCR, stereo, cable tuner, CD player, computer, or any other device or circuit that you can think of. Whatever that device or circuit is, it can be controlled by an invisible beam of light or an ultrasonic wave linking the two halves of this system! **R-E**

# MARKET CENTER

## SATELLITE TELEVISION

**BUILD your own Satellite-TV receiving system and save!** Instruction manuals, schematics, circuit boards, parts kits! Send stamped envelope for complete product listing: XANDI, Box 25647, Dept. 21T, Tempe, AZ 85282.

**SATELLITE Descramblers.** Lowest prices anywhere! Dealer inquiries welcome. Send \$3.00 for catalog. We ship C.O.D.'s. **STARVIEW INC.**, P.O. Box 103, Rexford, NY 12148. (518) 785-1288.

**THE LNA specialists!** Brand name, lowest noise, lowest prices! We will not be undersold! Send for

prices: **LNA**, 201 E. Southern, Suite 100, Tempe, AZ 85282.

**SATELLITE Channels** Newsletter. Get the most from your dish! Details, sample \$2.00. **BOX 312**, Dighton, MA 02715.

**SATELLITE** system \$595.00 complete information \$1.00; color catalog \$2.00. **STARLINK, INC.**, 2603-16R, Artie, Huntsville, AL 35805.

**SATELLITE-TV** systems from \$449.00 wholesale, retail \$995.00, dealers wanted. (714)891-5479, **WHOLESALE**, P.O. Box 8040, Anaheim, CA 92802.

**E-Z** satellite kit, computer print-out of your location, 2" liquid compass, inclinometer. MasterCard/Visa. **IN-X-SALES**, Box 45, Tilton, NH 03276. (603)286-3082.

**SATELLITE** television components, huge savings contact **FORCE ONE SYSTEMS**, 120 16th N.W., Canton, OH 44703. (216) 456-0259.

**FREE** descrambler plans your choice either purchase: my Dish featured Canada's Electronics Today Magazine, manual & blueprints \$19.95. Videotape: installing and improving your satellite reception \$24.95. Information: **SOTHIS SATELLITE**, Box 7117, Station A, Saint John N.B., Canada E2L 4S5.

## BUSINESS OPPORTUNITIES

**US \$8.00** including disk, thousand name brand programs for Apple, IBM-PC, details U.S. \$1.00. **RELIANT**, P.O. Box 33610, Sheungwan, Hong Kong.

**PROJECTION TV**...Make \$\$\$s assembling projectors...Easy... Results comparable to \$2,500.00 projectors...Your total cost less than \$20.00...Plans, 8" lens & dealers' information \$17.50...Illustrated information free...**MAC-ROCOMA-GCX**, Washington Crossing, PA 18977. Creditcard orders 24 hours (215)736-2880.

**BURGLAR alarms—Booming business.** Get in now. Information package \$2.00. **DYNAMIC SECURITY** P.O. Box 1456-NR, Grand Rapids, MI 49501.

**BIG PROFITS**

**ELECTRONIC ASSEMBLY BUSINESS**

Start home, spare time. Investment knowledge or experience unnecessary. **BIG DEMAND** assembling electronic devices. Sales handled by professionals. Unusual business opportunity.

**FREE: Complete illustrated literature**  
BARTA, RE-O Box 248  
Walnut Creek, Calif. 94597

**INDEPENDENT dealer!** Get highly profitable top quality products at dealer's price. \$12.00 membership fee immediately covered by free sample of \$19.95 solderless breadboard. **CENTURY INTERNATIONAL** Box 29762, Dallas, TX 75229.

**STOCKS!** For Apple IIe. Have sharp, easy-reading charts to supplement your investment information. User-friendly, failsafe software. \$20.00 or request brochure: **THE OUTSTANDING MACHINE**, 23890 East Summit, Los Gatos, CA 95030.

**TV shop sales and service**, established business owner retiring, central Virginia. Call (703) 972-7027, after 8:00 p.m..

**MECHANICALLY** inclined individuals desiring ownership of small electronics manufacturing business—without investment. Write: **BUSINESSSES**, 92-R, Brighton 11th, Brooklyn, NY 11235.

## INVENTORS!

**CAN** you profit from your idea? Call us today regarding the marketing of your invention, or write for your free information package. Over a decade of service. **AMERICAN INVENTORS CORPORATION**, 82 Broad Street, Dept. RE, Westfield, MA 01086, (413) 568-3753. (Not an answering service.) Offices nationwide.

## CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

**Radio-Electronics Classified Ads**, 200 Park Avenue South, N.Y., N.Y. 10003

**PLEASE INDICATE** in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$20.00.

( ) Plans/Kits ( ) Business Opportunities ( ) For Sale  
( ) Education/Instruction ( ) Wanted ( ) Satellite Television

Special Category: \$20.00

### PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$37.50)
16 (\$40.00)	17 (\$42.50)	18 (\$45.00)	19 (\$47.50)	20 (\$50.00)
21 (\$52.50)	22 (\$55.00)	23 (\$57.50)	24 (\$60.00)	25 (\$62.50)
26 (\$65.00)	27 (\$67.50)	28 (\$70.00)	29 (\$72.50)	30 (\$75.00)
31 (\$77.50)	32 (\$88.00)	33 (\$82.50)	34 (\$85.00)	35 (\$87.50)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted.):

Card Number

Expiration Date

Please Print Name

Signature

**IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.**

**CLASSIFIED COMMERCIAL RATE:** (for firms or individuals offering commercial products or services) \$2.50 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS.** 5% discount for same ad in 6 issues; 10% discount for same ad in 12 issues within one year; if prepaid. **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$2.00 per word, prepaid...no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) **50¢ per word additional (20% premium).** Entire ad in boldface, **add 20% premium** to total price. **TINT SCREEN BEHIND ENTIRE AD: add 25% premium** to total price. **TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD: add 45% premium** to total price. **EXPANDED TYPE AD: \$3.75 per word prepaid.** All other items same as for STANDARD COMMERCIAL RATE. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD: add 25% premium** to total price. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD: add 45% premium** to total price. **DISPLAY ADS:** 1" x 2 1/4" — \$270.00; 2" x 2 1/4" — \$540.00; 3" x 2 1/4" — \$810.00. **General Information:** Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 15th of the third month preceding the date of the issue. (i.e., August issue copy must be received by May 12th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding working day.



**CABLE TV converters**—All major brands. Wireless remotes with volume, wired remotes. Cable and Video accessories. Cablemaster distributor. Lowest prices. Ship C.O.D.. Catalogs \$3.00. **SONE ASSOCIATES**, 5 Broadway, Suite 201, Troy, NY 12180. (518) 274-0608

**CIRCUIT boards**: Your artwork, quick delivery, reasonable. **ATLAS CIRCUITS**, Dept. A, P.O. Box 892, Lincolnton, NC 28092. (704) 735-3943.

**CATALOG**: TV descramblers, microwave converters, satellite systems, many types, kits or built, \$1.00. **MINUTE KITS**, Box 531, Westchester Sq. Sta., Bronx, NY 10461.

**CABLE-TV converters and equipment**. Plans and parts. Build or buy. Free information. **C & D ELECTRONICS**, 626 Flowerdale, Dept. RE, Ferndale, MI 48220.

**SHORTWAVE listeners!** Free info sheet for S.A.S.E. **RADIO WEST**, 3417 Purer Rd., Dept RE, Escondido, CA 92025. (619) 741-2891

**SURFACE** mount capacitor kit, over 100 chip caps. Assorted popular values in compartmented tray. Send \$24.95 to: **SMS ENTERPRISES**, P.O. Box 2417, Newport Beach, CA 92663 or call (714) 779-0154. Visa/MasterCard.

**LASERS** and nightvision surplus components. Free catalog. **M.J. NEAL COMPANY**, 6672 Mallard Ct. Orient, OH 43146.

**COMPUTERS**, inexpensive IBM kits, Apple parts, expansion cards. **KOMPUTECH**, Box 597, Alexbay, NY 13607. (613) 476-7523.

**CABLE-TV converters and descramblers**. Low prices, quality merchandise, we ship C.O.D.. Send \$2.00 for catalog. **CABLETRONICS UNLIMITED**, P.O. Box 266, South Weymouth, MA 02190.

**TECHNICAL books**. Electronics, robotics, radio. Catalog \$2.00. **KEATS COMPANY**, Box 796 STN. A, Scarborough, Ontario, Canada. MK 5C8.

**GET** information and parts straight from manufacturers. \$4.00 for the address book. **IWS**, Box 19810, Indianapolis, IN 46219-0810.

**Quality Microwave TV Antennas**

Multi-Channel 1.9 to 2.7 GHz  
40dB Gain True Parabolic 20 Inch Dish  
Complete System \$84.95 (Shipping Incl.)  
Dealerships, Qty. Pricing, Replacement Parts

**Phillips-Tech Electronics**  
P.O. Box 34772 • Phoenix, AZ 85067  
(602) 947-7700 (\$3.00 Credit all phone orders!)

LIFETIME WARRANTY  
MasterCard • Visa • COD

**ATTENTION**: looking for surplus test equipment? Have voltmeters, signal generators other types equipment. **J.B. ELECTRONICS**, 9518 Grand, Franklin Park, IL 61031. (312) 451-1750.

"TECHNICIANS do things engineers only dream of." Giant bumper sticker \$2.00. **FABIAN INTERNATIONAL**, P.O. Box 925, Hull, MA 02045.

**FREE** National Semi Conductor™ pocket calculator and catalog of car stereo, C.B.'s radar detectors, alarms, accessories. Dirt cheap! Send \$4.00 for postage and handling. **ELECTROMANIA**, 51B Sunrise Hwy, Lynbrook, NY 11563.

**CABLE** units starbase \$109.95. Hamlin MLD-1200 \$109.95. OMC/N-12 \$89.95. Z-TAC (3in 3out) \$209.95. Outdoor quality notch filters \$29.95. Send S.A.S.E. for product flyer to **LUNAR ELECTRONICS** P.O.Box 662, Hunt Valley, MD 21030

**AUTOMOTIVE Security Catalog**, new state of the art technology. Send \$2.00. Electrify your car plans. \$18.00. **ABSTRACT ELECTRONICS**, 19200 Schoolcraft, Detroit, MI 48223.

**LIGHT chasers**, color organs, rope lights. Assembled, kits. **DESIGN SPECIALTY**, Box 1995, Huntington Beach, CA 92647.

**222 PROGRAMS**, practical BASIC Computer Book, 288 pages, \$9.95. **ARCsoft**, Box 132RE, Woodsboro, MD 21798.

**MICROWONDERLAND**. Commodore computer's parts! CMOS coolers for 1541 drives! KIM-1 computers, accessories! Thousands other ICs! Discounts! Catalog—\$3.00! **K. BOUFAL-CONSULTING SERVICES**, 244 Fitzwater, Philadelphia, PA 19147. (215) 925-6469.

**TUBES** \$2.49. Send S.A.S.E. for newly expanded lists. **ADNF**, 6690 7-Mile, South Lyon, MI 48178.

**ZENITH SSAVI Manual**. Original manual used by technicians. Theory of scrambling, schematics parts list, repair for UHF and cable. For speedy delivery send \$15.00, cash or money order. **BAY STATE ELECTRONICS**, P.O. Box 263, Accord, MA 02018.

**FREE** catalog. Electronics computer handbooks all available on free trial examination! **PRENTICE-HALL B&P**, Englewood Cliffs, NJ 07632; attr: Frank Roess.

**FREE** importer accessories catalog, video audio, others. With business card write, 17 Banner Court, East Brunswick, NJ 08816.

**FINEST QUALITY SOLDER**

SN 60/40 Rosin Core (RA)

One lb. Reels	
16 swg. (.064)	\$7.95
18 swg. (.048)	\$8.45
19 swg. (.040)	\$8.95
20 swg. (.036)	\$9.45
21 swg. (.032)	\$9.95
1/2 lb. Reels	
22 swg. (.028)	\$5.95
24 swg. (.022)	\$7.95

SN 62 (2% Silver)  
Rosin Core  
21 swg. (.031) \$19.95

**FREE Freight On All Orders Over \$25**  
Under \$25 add \$2.50 per order.  
Minimum order \$10.

**FREE Desoldering Wick** with each pound of solder

Check  Money Order  VISA  
MasterCard  N.Y. State residents add appropriate sales tax.

**SolderCraft™** Call TOLL FREE 800-645-4808  
P.O. Box 608 R. Jericho, N.Y. 11753  
in NYS (516) 334-2660

# MICRO MART

508 Central Ave.  
Westfield, N.J. 07090  
(201) 654-6008

<b>15 Pin Header &amp; Mating Socket, Vert MT/PC</b>		
156 Centers	5/1.00	
Crystal Clock Oscillator	50	
Miniature Speaker, 2", 8 OHM	50	
<b>Coils For Radio Elec's Feb. 84 TV Project, Toko #S T-1, T-2, L-1 (12uH) &amp; L-2 (.071uH) Complete Set Of All 4 Coils</b>	8.50	
MC1330—Prime (Moto)	2/1.00	
BFO-85 Transistor	4/1.00	
Disc Caps 001uf	20/1.00	
74123-Prime (Nat)	3/1.00	
470uf 35V (Radial)	3/1.00	
470uf 16V (Axial)	4/1.00	
2N3904	10/1.00	
1N914	40/1.00	
1N4148	40/1.00	
1N5231 B (5.1 V Zener Diode)	5/1.00	
Voltage Regulators (Prime TO-220)	7/805	
7812, 7824, 7905, 7912—Mix or Match 3/1.00		
Mica Insulators For TO-220 Pkg	20/1.00	
Voltage Reg's (Unmarked, 60% Prime) May Include Positive/Neg & Adjust	15/1.00	
78L08 Voltage Reg (DM106, TO-92)	20/1.00	
PN2222A	20/1.00	
2N3055	50	
2N5308	20/1.00	
<b>15 Cent (.15) Per IC TTL</b>		
7403	7442	74126
7404	7450	74151
7410	7474	74183
7437	7476	74385
7438	7495	74393
7440	74107	
<b>15 Cent (.15) Per IC 74LSXX</b>		
74LS02	74LS158	
74LS08	74LS27	
74LS10	74LS257	
74LS16	74LS257	
74LS20	74LS273	
<b>20 Cent (.20) Per IC CMOS</b>		
4001B, 4011B, 4050B		
MC938 (DTL)	10/1.00	
Opto Isolator (H11G2-6PIN DIP) Specs	40	
2716 Eprom	1.45	
2732 Eprom	1.95	
2764 Eprom	2.45	
27128 EPROM	4.95	
256K Dram 150ns Prime Hitachi (Ideal For Mac Upgrades & Expansion Projects)	4.95	
8243 (I/O Expander IC) W/Specs	2.95	
UDN 6118 (Display Driver IC) Specs	95	
UDN 6128	95	
UCN 4118 (Osc/Freq Div Clock IC) Specs 5/1		
UCN 4801 (8 Chan Bi-Div Latch/Driver) 1.00		
LM339	45	
LM380 (ULN2280)	45	
555 Timers (TI)	4/1.00	
NE555 (Dual Timer/Moto)	50	
741U Op Amp (Mini Dip) Rel Pkg	4/1.00	
LM1310 (Unmarked Tested Prime)	50	

LM1889	95	
LM3900	45	
AM/FM Radio IC (#2204 W/Specs/Hobby)	15/1.00	
<b>IC Sockets</b>		
8 PIN/07	14 PIN/13	16 PIN/15
18 PIN/17	20 PIN/19	22 PIN/21
24 PIN/22	28 PIN/24	40 PIN/39
7 Segment Display (3 Common Cath)	15	
7 Segment Display (6 Common Anode)	65	
Tri State LED's	3/1.00	
Jumbo Red LED's—Diffused Lens, Prime Tri	2/1.00	
All 100% Prime—15/51, 100/56, 1.000/57.50	15/1.00	
LED Mounting Clips & Rings	15/1.00	
Texas Inst. #994A Keyboard-Int/Data For Pins Made When Each Key Depressed	4.95	
Dip Switch—12 Position	2/1.00	
Dip Switch—8 Position	4/1.00	
Keyboard Push Button Tops	30/1.00	
Audio Cable	30 Feet/1.00	
22AWG Wire	50 Feet/1.00	
27AWG Wire	50 Feet/1.00	
Mini Lubricator (& Lubricant)	1.00	
Molex Pins (7 Pin/Strip 100/\$2.50/\$4.1K/\$6)		
Clock Module—Crystal Controlled, Green Display/12VDC/Time Set Switches/Data-4.95		
Rotary Switch (5 Position, 5A 125V) 3/1.00		
<b>Giant Alpha Numeric Display 1-1/2" X 2"</b>		
7x5 (35 Total) Red LED Matrix/Specs-4.95		
<b>11 LED Bar Graph Display-2-3/4" Rect</b>		
LED's (Specify Red, Grn, Amber) Specs	2.69	
<b>Seven Amp (7 Tapped) Transformer—Can Be Wired For 7.5V, 9V, 15V, 18V Reg Shpg</b>	8.95	
Wall Plug Transformer—24V 525mA	1.50	
6.3V 1.2A Transformer	1.20	
12V Center Tap Transformer	2.50	
Mini Audio Transformers	10/1.00	
1N4007	20/1.00	
1N5059 (200V 1 Amp)	15/1.00	
1N5060 (400V 1 Amp)	10/1.00	
Zener Diodes-20V 1W	30/1.00	
Zener Diodes-13V 1W Glass	30/1.00	
2560 0K Crystal	50	
3.57 9545 Color Burst Crystal (HC-18)	50	
1.0 Mhz Crystal	1.95	
6.0 Mhz Crystal	1.95	
TO-5 Heat Sinks (Bern)	10/1.00	
TO-18 Heat Sinks (Bern)	10/1.00	
<b>Super Sub-Mini Ceramic Caps (All 100V)</b>		
0015uf 100V (152)	30/1.00	
0022uf 100V (182)	30/1.00	
0027uf 100V (272)	30/1.00	
0033uf 100V (332)	30/1.00	
0039uf 100V (392)	30/1.00	
0056uf 100V (562)	30/1.00	
0082uf 100V (822)	30/1.00	
47uf 40V Lytic (Radial)	20/1.00	
47uf 25V Lytic (Radial)	10/1.00	
1000uf 185V Twist Lock	1.00	
3200uf 50V (Ideal For Power Supplies)-1.00		
5600uf 25V (Comp Grade 3-5/8" X1)-3/1.00		
1uf 50V Monolithics	10/1.00	
22uf 50V Monolithics	20/1.00	

Chip Caps—Set of 4, 2 Each 2.7 & 3.3pf-1.00	
33uf 100V Dip Mylar	10/1.00
1,000 Pk Resistor Ass't (30 Values) 1/2W-\$3	
Pots-1 Meg. Linear Taper	5/1.00
Motion Detector Bds (Inc IC-\$2)	7/10.00
Mot Det (IC Only-ULN232A) 3/\$2-20/10.00	
Project Box/Lid For Detector	1.95
Miniature Speaker For Detector	25
Extensive Construction Article For Det. \$1	
TV Knobs	15/1.00
Ammeter (0-15 A.C. Amperes)	4.95
Volt/OHM Meter VMVMT (0-1K OHM, 0-300V)	2.95
6V Miniature Gear Motor	50
RF Chokes-1.8uH, 8.2uH, 12uH, 22uH-10/1.00	
22/44 Pin Edge Card Connector	50
34 Pin Connector (For Drives) W/Hood	75
BNC-T Connector (UG-27-4)	95
Mixed Connector Ass't	10/1.00
1.5AMP 50V Bridge (Gl, TO-5 Pkg)	50
25AMP 200V Bridge (Solder Lug Term)	1.50
<b>Zenith TV Replacement IC Special \$1 Each</b>	
221-42, 221-43, 221-45, 221-48, 221-69, 221-79, 221-87, 221-96, 221-104, 221-105, 221-106, 221-114	
2SD900 (Horiz Output W/Damper Diode)-2.95	
2SC1172B (Toshiba-Horiz Output Trans)-1.95	
Wiregard-4 Bay Bowtie UHF Antenna-19.50	
IC Storage (Burg Box (Holds) 30 IC's-1.75	
<b>Precision (Multi-Turn) Trim Pots (Copal)</b>	
100 OHM, 500 OHM, 1K, 2K, 5K, 10K, 20K, 50K, 100K, 200K, 500K, 1M-85 Each-3/\$2	
<b>Phaser PT-10V Hor Mt (Single Turn) Trimmers</b>	
100 OHM, 1K, 10K, 25K, 50K, 100K	4.95
High Sensitive Switch/150°C	10/1.00
Mixed Col Ass't	10/1.00
Buzzers	3/1.00
Chip Resistor (6.8K)	20/1.00
Chip Resistor (470K)	20/1.00
Chip Cap (330pf)	20/1.00
Jumbo Red LED W/Built In Resistor-30/\$1	
MRF901 (Hobby Grade-60% Good)	10/1.00
IC Ass't (Hobby Grade, Some Marked)-30/\$1	

**20 Cent (.20) 74SCXX Series Special**

- Octal Interface Circuits
- Equivalent To 74LSXX Series
- Low Power ISO-CMOS Technology
- Short Propagation Delay
- Improved Noise Margins
- High Current Sink/Source Capability

74SC137-1 Of 8 Inverted Decoder, Latched  
74SC138-1 Of 8 Inverted Decoder  
74SC139-1 Of 4 Inverted Decoder  
74SC237-1 Of 8 Non-Inverted, Latched  
74SC238-1 Of 8 Non-Inverted  
74SC239-1 Of 4 Non-Inverted  
74SC240-Octal Buffer/Line Driver-Inv  
74SC241-Octal Buffer/Line Driver-N/I  
74SC242-Octal Buffer/Line Driver-N/I  
74SC244-Octal Bus Transceiver-Non/I  
74SC245-3-Transoarent Latch-Non/Inv

Terms: MICRO-MART accepts Visa, MC and telephone COD's. Minimum order \$10.00. Shipping—U.S. orders \$2.00. Canada and other countries \$3.50 (includes ins.) Shipping rate adjusted where applicable. NJ residents add 6% sales tax.

**MICRO-MART • 508 CENTRAL AVE., WESTFIELD, NJ 07090 • (201) 654-6008**

74SC374-D Type Flip-Flop, Non/Inv	
74SC533-Transparent Latch-Inverted	
74SC534-D Type Flip-Flop, Inverted	
74SC540-Octal Buffer/Line Driver-Inv	
74SC541-Octal Buffer/Line Driver-N/I	
74SC563-Transparent Latch, Inverted	
74SC564-D Type Flip-Flop, Inverted	
74SC573-Transparent Latch, Non/Inv	
74SC574-D Type Flip-Flop, Non/Inv	
Data Book For All Above #s	2.50
<b>Cypher IV Micro-Controller Kit—\$129.50</b>	
4 MHz 8-Bit Microprocessor (NAT 1NSB073)	
Control Basic Interpreter On-Chip	
Auto-Start Operation At Power-On	
Fast 16-Bit Multiply And Divide	
RS-232C Supports CRT & Serial Link	
24 Bi-Directional I/O Lines (8255A)	
RAM Memory-2K Expandable To 16K	
Eprom Memory-Expandable To 16K	
Built In Eprom Programmer	
Parit (Centronic) Printer Interface	
Optional Real-Time Clock W/Backup	
<b>Pay TV Hardware Installation Kit Blow Out As Low As \$2.95 + \$3.50 Shipping Per Unit</b>	
All Kits Contain 5 F Connectors-300 to 75 OHM Balun, 300 OHM Terminal Block 2 Ft, 75 OHM Patch Cord 2 Ft 300 OHM Twin Lead, Nylon Cable Ties, And UHF Antenna	
<b>Model #4124-\$2.95</b> Includes All Of The Above Plus 25 Feet Coaxial Cable And Mounting Hardware For Indoor/Wall/Ceiling Installation	
<b>Model #4880-\$2.95</b> Includes All Of The Above Plus 25 Feet Coaxial Cable And Attractive Expandable Pole/U-Bolt For Easy Indoor Installation	
<b>Model #4845-\$3.95</b> Includes All Of The Above Plus 65 Feet Coaxial Cable And All Necessary U-Bolt Hardware	

**MODEL 705 Digital Multimeter**

DC Voltage	100uV to 1000V
AC Voltage	100uV to 750V
DC Current	0.1uA to 10A
AC Current	0.1uA to 10A
Hi-Z Resistance	0.1Ω to 20MΩ
Capacitance	1pF to 20uF
Diode Test	forward voltage testing
Hrc test	transistor testing

**\$51.95**

**UHF-TV PREAMP**  
(As featured in Radio Electronics March/May articles, 1982)

This inexpensive antenna mounted pre-amp can add more than 25 dB of gain to your system. Lots of satisfied customers and repeat orders for this high quality kit, which includes all component parts. PC BD, Case, Power Supply and Balun \$34.50 Assembled Version \$57.50

# DoKay

COMPUTER  
PRODUCTS,  
Inc.

ORDER TOLL FREE

(800)  
538-8800

(CALIFORNIA RESIDENTS)

(800)  
848-8008



## STATIC RAMS

2101	256 x 4	450ns	1.90
2102	1K x 1	450ns	.79
2102L-4	1K x 1	450ns	.89
2102L-2	1K x 1	450ns	1.29
2111	256 x 4	450ns	2.29
2112	256 x 4	450ns	2.29
2114	1K x 4	450ns	.99
2114-25	1K x 4	250ns	1.10
2114L-4	1K x 4	450ns	1.20
2114L-3	1K x 4	300ns	1.30
2114L-2	1K x 4	200ns	1.40
2147	4K x 1	55ns	3.95
2101	256 x 4	450ns	3.95
MS4044-4	4K x 1	450ns	2.95
MS4044-3	4K x 1	300ns	3.45
MS4044-2	4K x 1	200ns	3.95
MX4118	1K x 8	250ns	8.95
MM2016-20	2K x 8	200ns	2.49
MM2016-15	2K x 8	150ns	2.99
MM2016-10	2K x 8	100ns	4.49
MB116-4	2K x 8	200ns	2.49
MB116-3	2K x 8	150ns	2.99
MB116-2	2K x 8	120ns	3.49
MB116LP-4	2K x 8	200ns	2.99
MB116LP-3	2K x 8	150ns	3.49
MB116LP-2	2K x 8	120ns	3.99
-6132	4K x 8	300ns	29.95
MB264P-15	8K x 8	150ns	8.95
MB264LP-15	8K x 8	150ns	8.95
MB264LP-12	8K x 8	120ns	10.95

## DYNAMIC RAMS

MS4027	4K x 1	250ns	1.45
IPD411	4K x 1	300ns	1.95
MS5280	4K x 1	300ns	1.95
MX4108	8K x 1	200ns	.49
MS5298	8K x 1	250ns	.49
1116-20	16K x 1	200ns	.79
1116-15	16K x 1	150ns	.99
1116-12	16K x 1	120ns	1.49
1118	16K x 1	150ns	5v 3.95
1164-25	64K x 1	250ns	5v 1.50
1164-20	64K x 1	200ns	5v 1.75
1164-15	64K x 1	150ns	5v 2.00
11256-20	256 x 1	200ns	7.95
11256-15	256 x 1	150ns	8.95

## EPROMS

702	256 x 8	1 us	3.95
708	1K x 8	450ns	2.49
758	1K x 8	450ns	5.90
718	2K x 8	450ns	5v 2.95
718-1	2K x 8	350ns	5v 3.95
MS2516	2K x 8	450ns	5v 3.95
MS2716	2K x 8	450ns	6.95
MS2532	4K x 8	450ns	5v 3.95
732	4K x 8	450ns	5v 3.95
732 A-4	4K x 8	450ns	21v 3.95
732 A-35	4K x 8	350ns	21v 3.95
732 A	4K x 8	250ns	21v 5.95
732 A-2	4K x 8	200ns	21v 8.95
764	8K x 8	450ns	5v 4.25
764-25	8K x 8	250ns	5v 4.95
764-20	8K x 8	200ns	5v 7.95
MS2564	8K x 8	450ns	5v 9.95
KCM88784	8K x 8	450ns	5v 17.95
KCM88766	8K x 8	350ns	5v 19.95
7128-45	16K x 8	250ns	5v 8.95
7128-30	16K x 8	300ns	5v 9.95
7128-25	16K x 8	250ns	5v 10.95
7256-25	32K x 8	250ns	14v 24.95

## 74LS00

74LS00	.23	74LS125	.48	74LS260	.58
74LS01	.24	74LS126	.48	74LS266	.54
74LS02	.24	74LS132	.58	74LS273	1.45
74LS03	.24	74LS133	.58	74LS275	3.30
74LS04	.23	74LS136	.38	74LS279	.48
74LS05	.24	74LS137	.98	74LS280	1.95
74LS08	.27	74LS138	.54	74LS283	.68
74LS09	.28	74LS139	.54	74LS290	.88
74LS10	.24	74LS145	1.15	74LS293	.88
74LS11	.34	74LS147	2.45	74LS295	.98
74LS12	.34	74LS148	1.30	74LS298	.88
74LS13	.44	74LS151	.54	74LS299	1.70
74LS14	.58	74LS153	.54	74LS323	3.45
74LS15	.34	74LS154	1.85	74LS324	1.70
74LS20	.24	74LS155	.68	74LS352	1.25
74LS21	.28	74LS156	.68	74LS353	1.25
74LS22	.24	74LS157	.64	74LS363	1.30
74LS26	.28	74LS158	.58	74LS364	1.90
74LS27	.28	74LS160	.68	74LS365	.48
74LS28	.34	74LS161	.64	74LS366	.48
74LS30	.24	74LS162	.68	74LS367	.44
74LS32	.28	74LS163	.64	74LS368	.44
74LS33	.54	74LS164	.68	74LS373	1.35
74LS37	.34	74LS165	.94	74LS374	1.35
74LS38	.34	74LS166	1.90	74LS377	1.35
74LS40	.24	74LS168	1.70	74LS378	1.13
74LS42	.48	74LS169	1.70	74LS378	1.30
74LS47	.74	74LS170	1.45	74LS385	1.85
74LS48	.74	74LS173	.68	74LS386	.44
74LS49	.74	74LS174	.54	74LS390	1.15
74LS51	.24	74LS175	.54	74LS393	1.15
74LS54	.28	74LS181	2.10	74LS395	1.15
74LS55	.28	74LS189	8.90	74LS399	1.45
74LS63	1.20	74LS190	.88	74LS424	2.90
74LS73	.38	74LS191	.88	74LS447	.36
74LS74	.34	74LS192	.78	74LS490	1.90
74LS75	.38	74LS193	.78	74LS824	3.95
74LS76	.38	74LS194	.68	74LS840	2.15
74LS78	.48	74LS195	.68	74LS845	2.15
74LS83	.59	74LS196	.78	74LS868	1.65
74LS85	.68	74LS197	.78	74LS869	1.85
74LS86	.38	74LS221	.88	74LS870	1.45
74LS90	.54	74LS240	.94	74LS874	9.60
74LS91	.88	74LS241	.98	74LS882	3.15
74LS92	.54	74LS242	.98	74LS883	3.15
74LS93	.54	74LS243	.98	74LS884	3.15
74LS95	.74	74LS244	1.25	74LS885	3.15
74LS96	.88	74LS245	1.45	74LS888	2.35
74LS107	.38	74LS247	.74	74LS889	3.15
74LS109	.38	74LS248	.98	74LS783	23.95
74LS112	.38	74LS249	.98	81LS95	1.45
74LS113	.38	74LS251	.58	81LS96	1.45
74LS114	.38	74LS253	.58	81LS97	1.45
74LS122	.48	74LS257	.58	81LS98	1.45
74LS123	.78	74LS258	.58	25LS2521	2.75
74LS124	2.85	74LS259	2.70	25LS2569	4.20

We will try to BEAT  
All Competitor's Prices  
CALL for Quote!

## DISC CONTROLLERS

1691	6.90	2795	38.90
1771	14.90	2797	38.90
1791	22.90	6843	33.90
1793	22.90	8272	19.90
1795	22.90	M88876	22.90
1797	22.90	M88877	22.90
2143	6.90	M83470	4.90
2791	38.90	UPD765	19.90
2793	38.90		

## CRT CONTROLLERS

6845	11.90	CRT5027	18.90
6847	10.90	CRT5037	28.90
68047	23.90	DP8350	38.90
68845	18.90	HD46505	11.90
7220	38.90	MC1372	6.90
8275	28.90	TMS9918A	38.90

## UV ERASERS

QUV-T8/1 \$49.95  
ECONOMY Model



- Erases 15 EPROMS in 20 minutes
- Plastic Enclosure

## 6500

6500	4.90	6500 A	5.90
6504	6.90	6502A	5.90
6505	8.90	6522A	9.90
6507	9.90	6532A	10.90
6520	4.30	6545A	12.90
6522	4.90	6551A	10.90
6532	9.90		
6545	9.90		
6551	9.90	6502B	7.90

## 6800

1 MHz		68B00	
		2 MHz	
6800	2.90	68800	9.90
6802	7.90	68802	11.90
6803	17.90	68809	11.90
6808	12.90	68809E	11.90
6809E	8.90	68809E	11.90
6809	8.90	68810	5.90
6810	2.90	68821	5.90
6820	4.30	68840	18.90
6821	2.90	68845	18.90
6828	13.90	68850	5.90
6840	11.90		
6843	33.90		
6844	24.90		
6845	11.90		
6847	10.90	68000-8	34.90
6850	2.90	68047	23.90
6852	5.90	68488	18.90
6860	7.90	68652	14.90
6862	10.90	68661	8.90
6875	6.90	68764	17.95
6880	1.90	68766	19.95
6883	21.90		

## 8000

8031	14.90	8253	6.90
8035	5.90	8253-5	7.90
8039	5.90	8255	4.45
INS-8060	16.90	8255-5	4.90
INS-8073	29.90	8257	7.90
8080A	3.90	8257-5	8.90
8085	4.90	8259	5.90
8085A-2	11.90	8259-5	6.90
8086	24.90	8271	69.90
8087-3 (5 MHz)	159.90	8272	19.90
8087-2 (8MHz)	279.90	8274	28.90
8088	19.90	8275	28.90
8089	59.90	8279	6.90
		8279-5	7.90
		8282	6.45
		8283	6.45
8131	2.90	8284	4.90
8155	6.90	8286	6.45
8155-2	7.90	8287	6.45
8156	6.90	8288	12.90
8185	28.90	8289	44.90
8185-2	38.90	8292	12.90

## 8100

8131	2.90	8284	4.90
8155	6.90	8286	6.45
8155-2	7.90	8287	6.45
8156	6.90	8288	12.90
8185	28.90	8289	44.90
8185-2	38.90	8292	12.90

## 8200

8202	23.90	8303	2.90
8203	38.90	8304	1.90
8205	2.90	8307	2.90
8212	1.75	8308	2.90
8214	3.75	8310	3.90
8216	1.75	8311	3.90
8224	2.20		
8226	1.75		
8228	3.45	8741	28.90
8237	12.90	8748	19.90
8237-5	14.90	8749	28.90
8238	4.45	8755	23.90
8243	4.45		
8250	9.90		
8251	3.90	80186-6	99.90
8251A	4.45	80188	69.90

## Z-80

Z80-CPU	1.95	Z80A-DMA	8.95
Z80-CTC	1.95	Z80A-PIO	2.45
Z80-DART	6.95	Z80A-SIO/0	9.95
Z80-DMA	7.95	Z80A-SIO/1	9.95
Z80-PIO	1.95	Z80A-SIO/2	9.95
Z80-SIO/0	8.95	Z80A-SIO/9	9.95
Z80-SIO/1	8.95		
Z80-SIO/2	8.95	Z-80 B	
Z80-SIO/9	8.95	Z80B-CPU	7.95
		Z80B-CTC	8.95
Z-80 A		Z80B-PIO	8.95
Z80A-CPU	2.45	Z80B-DART	18.95
Z80A-CTC	2.45	Z80B-SIO/0	28.95
Z80A-DART	7.95	Z80 SIO/2	28.95

## MEMORY EXPANSION KIT

## Power Problems?

**SURGES! SPKES! INFEARS! BLACKOUTS! BROWNOUTS!**

**AEGIS™**...Power Conditioning Equipment...THE SOLUTION! Protects Computers & High-tech Equipment From Damaging Voltage Surges, Lost Data, & Costly Down Time.

### SPIKE—SPIKER®

Transient Voltage Surge & Spike Suppressors & Noise Filters • Eleven Models—All Models Rated 120V, 15A  
Priced From **\$29.95**



### LINE—SAVER™

Standby Uninterruptible & Emergency Power Systems. Self-Contained Batteries, Compact Design. Completely Automatic.  
Priced From **\$549™**

Call or write for free literature.  
Dealer inquiries invited.

### INSTANT ORDER LINE

800-524-0400  
TWX 501-651-2101  
IN PENNA. 215-837-0700



6584 Ruch Rd., Dept.  
Bethlehem, PA 18017

MADE IN USA

## DO-IT-YOURSELF TV REPAIR

**NEW!...Repair any TV...Easy.** Anyone can do it. Write, **RESEARCH**, Rt. 3, Box 601 BR, Colville, WA 99114.

## CABLE TV FILTER "CYLINDERS"

**SUPER powered notch filters.** Equivalent of able company "cylinders". Eliminate undesirable signals. Any channel 2 through 8; 14(A) through 22(I). (Please specify.) Send \$20.00 each. **Money back guarantee.** Quantity discounts, **CATV**, Box 17621, Plantation, FL 33318.

## PRINTED-CIRCUIT BOARDS

**PRINTED-circuit boards.** Quick prototypes, production, design, reflow solder. Send print or description for quote to **KIT CIRCUITS**, Box 235, Clawson, MI 48017.

**PRINTED-circuit boards,** double-sided with plated through holes or single-sided. No set-up charge. **CAUDILL, INC.**, 205 East Westwood Ave., Highpoint, NC 27262. (919) 884-0229.

## TUBES — OVER 2000 TYPES! DISCOUNT PRICES



Parts, supplies, and literature for tube type radios, including early and hard-to-find tubes.

Send \$1.00 for 24 page wholesale catalog.

### ANTIQUE ELECTRONIC SUPPLY

688-B W First St. • Tempe, AZ 85281 • (602) 894-9503

## EDUCATION & INSTRUCTION

**F.C.C. Commercial General Radiotelephone License.** Electronics home study. Fast, inexpensive! "Free" details. **COMMAND**, D-176, Box 2223, San Francisco, CA 94126.

**STIMULATE** hardware with C-64 and signet: combine real time A/D and D/A conversion, fourier analysis and network analysis of your analog circuit design. Included is **A/D-D/A** interface board, signet software package, documentation. Price \$125.00. **COMPUTER-CITY**, 467 Saratoga Ave., Suite 269, San Jose, CA 95129. (408)247-8775.

**MEXICO**, obtain almost all technical books advertised in this magazine in pesos and in Mexico from Ing. **SAMUEL THOMAS**, Tel. 533-1833, clave 2754.

## ATTENTION ELECTRONIC TECHNICIANS



Highly Effective Home Study BSEE Degree Program for Experienced Electronic Technicians  
Our New Advanced Placement Program grants Credit for previous Schooling & Professional Experience. Advance Rapidly! Our 40th Year  
FREE DESCRIPTIVE LITERATURE!

**Cook's Institute of Electronics Engineering**  
P.O. BOX 20345, JACKSON, MS 39209

**ELECTRONICS** technicians' guide to "moving up the ladder" fast. Find a better job at better pay. Send \$12.50 to: **JOHN DAVID PUBLISHING**, 121 Lyman, Springfield, MA 01103.

## WANTED

**INVENTIONS**, ideas, new products wanted! Presentation to industry. National exposition. Call **(1-800) 528-6050**. Canada (1-800) 528-6060. X831.

**INVENTORS!** AIM wants—ideas, inventions, new products, improvements on existing products. We present ideas to free manufacturers. Confidentially guaranteed. Call toll free **1-800-225-5800** for information kit.

**MASTERCARD AND VISA** are now accepted for payment of your advertising. Simply complete the form on the first page of the Market Center and we will bill.

# Govt. SURPLUS ELECTRONIC EQUIPMENT CATALOG

New ITEMS . . . New BARGAINS!  
**FREE** SEND TODAY FOR FREE COPY OF CATALOG WS-85 AND SUPPLEMENT • ADDRESS: DEPT RE

**FAIR RADIO SALES**  
1016 E EUREKA • Box 1105 • LIMA OHIO • 45802

REPLACEMENT FOR

## ECG®/GE®/SK®

### TRIPLERS Min 3 Pc/Type

500A/GE527	9.95
523/GE528	9.95
526A/GE521	9.95
528/SK3906	12.75
529/GE529	11.80

### OUTPUT TRANSISTORS

165/SK3115	2.25	1.95
238/GE37	2.25	1.95
283/SK3467	2.75	2.25
25D1341P/1500V/7A	2.25	1.90

### AUDIO POWER

152/SK3893	.30	.24
153/SK3274	.30	.24
196/SK3054	.48	.44
197/SK3083	.59	.54
291/SK3440	.48	.44
292/SK3441	.48	.44

### RECTIFIER DIODES

125 1000V/2.5A	.07	.05
156 1000V/5A	.18	.14
506 Damper-Hi Volt Fast Recovery	.29	.22

## SPECIAL OF THE MONTH

375/SK9118	44¢ 10 Pc Min	39¢ 100 Pc Min.
712 TV Sound/IF FM/DET/	75¢ 10 Pc Min	60¢ 100 Pc Min.

## SUPER SAVINGS

85	.21	.18	159	.16	.11	189	.50	.45
102A	.35	.29	160	.88	.77	190	.59	.50
108	.18	.14	161	.65	.50	191	.65	.55
123A	.18	.14	162	2.25	1.95	198	.65	.53
123AP	.13	.09	165A	2.35	1.99	199	.18	.12
128	.38	.33	171	.49	.39	234	.19	.13
129	.38	.33	184	.38	.30	287	.29	.22
130	.59	.53	185	.38	.30	288	.29	.22
154	.75	.65	187	.48	.40	376	.55	.49
157	.49	.39	188	.50	.45	398	.59	.49

FOR A COMPLETE LIST CALL OR WRITE—C.O.D. Orders Welcome (Min. Order \$25)

### DIGITRON ELECTRONICS

110 HILLSIDE AVENUE, SPRINGFIELD, NEW JERSEY 07081  
Toll Free 1-800-526-4928 In NJ 201-379-9016 Telex 138441  
PRICES SUBJECT TO CHANGE WITHOUT NOTICE. OFFER GOOD WHILE SUPPLY LASTS.  
ECG is a Trade Mark of Philips ECG.  
Digitron Electronics is not associated in any way with Philips ECG.

# NEW 1986 CATALOG

CIRCLE READER SERVICE NO. FOR FREE COPY

## THIS MONTH'S SPECIALS

MEMORIES		DYNAMIC RAMS	
4116	16K	.89	
4164	64K 150ns	1.39	
4164	64K 200ns	1.19	
41256	256K 150ns	5.49	
EPROMS		ALL NEW CURRENT PRODUCTION PRODUCTS	
2708	1K x 8	4K 5.99	
2764	8K x 8 300ns	64K 3.89	
27128	16K x 8 300ns	128K 5.99	
27256	32K x 8 250ns	256K 11.89	
27512	64K x 8 250ns	512K 53.99	
STATIC RAMS		MOTOROLA	
6264	8K x 8 150ns	64K 8.99	Advanced Micro Devices

FULL LINE OF MICROPROCESSORS AVAILABLE

WE ALSO STOCK...

- Books • Breadboard & Accessories
- Capacitors • Chemicals • Connectors
- Crystals • Plugs & Jacks • Fans
- Enclosures • Filters • Fuses • Heat Shrink Tubing • Heat Sinks • Kits
- Knobs • Peripherals • Probes • Opto
- PCB Products • Potentiometers ...



USA

P.O. BOX 9100  
WESTBOROUGH, MASS  
1-800-343-0874

**Active**

CANADA

5651 FERRIER ST.  
MONTREAL, QUEBEC  
1-800-361-5884

MAIL ORDERS PROCESSED WITHIN 24 HOURS

YOUR ELECTRONIC COMPONENTS CENTER

CURRENT DATE CODE PRODUCTS VOLUME DISCOUNTS

SELF SERVE STORES LOCATED NEAR YOU. JUST CALL...

WESTBOROUGH, MASS. 366-9684  
BELLEVUE, WASH. 881-8191  
MONTREAL, QUEBEC 731-7441/256-7538

OTTAWA, ONT. 728-7900  
TORONTO, ONT. 977-7692  
DOWNSVIEW, ONT. 630-0400

EDMONTON, ALTA. 438-5888  
CALGARY, ALTA. 235-5300  
VANCOUVER, B.C. 438-3321

CIRCLE 51 ON FREE INFORMATION CARD

# TENMA

## the Name You Can Trust in Electronic Test Equipment

### CALL TOLL FREE 1-800-543-4330

(IN OHIO 1-800-762-4315)


(IN HAWAII OR ALASKA 1-800-858-1849)



#### TENMA DROP PROOF DIGITAL MULTIMETER

- DC input impedance 10M ohm
- Shock-mounted LCD display
- Overload protection ■ Auto polarity ■ Backed by our 1-year limited warranty ■ For more specifications see MCM catalog #10, page 122

#72-057 **\$29<sup>95</sup>** each

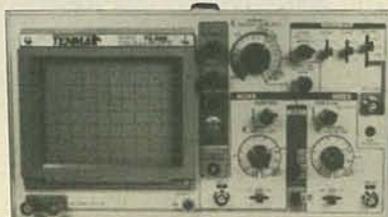

#### TENMA 20 MHZ DUAL TRACE OSCILLOSCOPE

- Two High Quality 10:1 probes included
- Backed by our 2-year limited warranty
- For specifications see MCM catalog #10, page 121


#72-320 **\$389<sup>95</sup>**



#### TENMA 3 1/2 DIGIT LCD MULTIMETER

- DC input impedance 10M ohm
- Diode and HFE transistor tests
- Overload protection ■ Auto polarity ■ Backed by our 1-year limited warranty ■ For more specifications see MCM catalog #10, page 122.
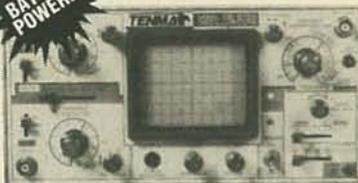
#72-050 **\$36<sup>80</sup>** (10-up)  
\$39.80 (1-9)



#### TENMA 15 MHZ DUAL TRACE BATTERY POWERED OSCILLOSCOPE

- Two High Quality 10:1 Probes included
- Backed by our 2-year limited warranty
- Internal rechargeable batteries provide 2 hours of continuous operation without the need for any outside power source.
- For specifications see MCM Catalog #10, page 121


#72-335 **\$489<sup>95</sup>**



#### TENMA DIGITAL CAPACITANCE METER

- Measures capacitors from 0.1pF to 1999mFd
- Accuracy 0.5% typical
- Fuse protected
- Checks capacitors in and out of circuit
- Backed by our 1-year limited warranty
- For more specifications see MCM catalog #10, page 122
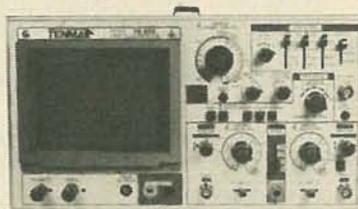
#72-040 **\$54<sup>95</sup>** (2-up)  
\$59.80 each



#### TENMA 35 MHZ DUAL TRACE OSCILLOSCOPE

- Two High Quality 10:1 probes included
- Backed by our 2-year limited warranty
- For specifications see MCM catalog #10, page 121

#72-330 **\$569<sup>00</sup>**

#### TENMA LOGIC PROBE WITH MEMORY



- Recognizes high, intermediate, or low levels, pulsing modes, open circuit
- Compatible with DTL/TTL/HTL/CMOS IC
- Detects pulses as short as 50 nanoseconds

#72-190 **\$19<sup>95</sup>** each

#### TENMA 30 Amp Power Supply



- Cross needle meter: Displays voltage, current, and power simultaneously
- Over current protection
- Output voltage: DC 9-15V variable
- Output current

- 30A one minute on three minutes off, 22A continuous
- Backed by our 2-year limited warranty
- For specifications see MCM Catalog #10, page 123

#72-030 **\$179<sup>95</sup>**

#### BE SURE TO CALL FOR YOUR FREE

### 132 PAGE CATALOG!

### OVER 5,000 ITEMS!



We have the Largest Selection of Original Japanese Semiconductor in the Country!

**We Also Have**... a full line of test equipment, computer accessories, telephone accessories, speakers, television parts, flybacks, yokes, switches, fuses, lamps, capacitors, resistors, cartridges, styli, wire, CATV equipment, and many more. **Over 5,000 items AT THE LOWEST PRICES AROUND!**

#### Terms:



- \$10 minimum order \$1.00 charge for orders under \$10
- \$20 minimum charge card order.
- Orders shipped UPS C.O.D.
- Most orders shipped within 24 hours
- Sales office open 8:30 am to 7:00 pm, Saturdays 10:00 am to 3 pm EST
- For prepaid orders add \$2.75 for shipping and handling
- Should shipping & handling charges exceed \$2.75, the balance due will be sent C.O.D.



**MCM ELECTRONICS**  
A DIVISION OF PREMIER INDUSTRIAL  
858 East Congress Park Drive  
Centerville, Ohio 45459  
513-434-0031

SOURCE NO. RE-13

CIRCLE 87 ON FREE INFORMATION CARD

NOVEMBER 1985

119


# GEMINI

THE AUTONOMOUS ROBOT

IS NOW PRICED FOR EVERYONE!



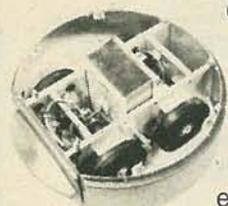Buy each subassembly as a kit or factory assembled and create your own GEMINI Robot.



Or, for convenience, start with **GEMINEX**, our starter kit, and expand to **GEMINI**

later with upgrade kits.



Either way,

Buy a piece of tomorrow **TODAY!**

CALL or WRITE For Our FREE Brochure.

**arctec systems**

9104 Red Branch Road  
Columbia, Maryland 21045  
(301)730-1237  
Telex 87-781

CIRCLE 272 ON FREE INFORMATION CARD

## A SINGER'S DREAM!



### REMOVES VOCALS FROM RECORDS!

Now You can sing with the world's best bands! The Thompson Vocal Eliminator can remove most or virtually all of a lead vocal from a standard stereo record and leave the background!

Write or call for a free brochure and demo record.

**LT Sound, Dept. R-1, P.O. Box 338,  
Stone Mountain, GA 30086 (404) 493-1258**

## PLANS AND KITS

**CATALOG:** Hobby, radio broadcasting, CB, lowfrets. Transmitters, linears, active antennas, converters, scramblers, bugging devices, more! **PANAXIS**, Box 130-F11, Paradise, CA 95969.

**DESCRAMBLER** plans. New design decodes gated sync suppressed signals—newest pilotless method. Circuit boards, most parts from Radio Shack. Detailed theory, drawings, schematics, instructions \$14.95 plus \$2.00 shipping. **DIRIJO CORP.**, Box 212, Lowell, NC 28098.

**CABLE-TV Converters:** Jerrold products include "new Jerrold Tri-Mode", SB-3, Hamlin, Oak VN-12, M-35-B, Zenith, and more. UHF Deluxe II kits. (Quantity discounts) 60 day warranty. Repairs of cable converters. For fast service C.O.D. orders accepted. Send S.A.S.E. (60 cents postage), or call for info., (312) 637-4408. **HIGGINS ELECTRONICS**, 5143 W. Diversey, Chicago, IL 60639. No Illinois orders accepted.

TV stereo adapter plans/PCB also UHF gated-pulse descrambler with simulated stereo output. For additional information—send S.A.S.E. to **SOKOLOWSKI**, Box 150, Elmont, NY 11003.

HI-FI speaker kits, auto speaker systems and speaker components from the world's finest manufacturers. For beginners and experts. Free literature. **A&S SPEAKERS**, Box 7462R, Denver, CO 80207. (303) 399-8609.

**PROJECTION TV**...Convert your TV to project 7 foot picture...Results comparable to \$2,500.00 projectors...Total cost less than \$30.00...Plans and 8" lens \$19.95...Illustrated information free. **MACROCOMA-GC**, Washington Crossing, PA 18977. Creditcard orders 24 hours (215) 736-3979.

**DIGITAL Klock** kit plays 1-of-12 melodies each quarter hour. Displays time, date, and other features. Send \$2.50 for assembly plans and pricing to **KERBER KLOCK KO.**, 36117 Hillcrest, Eastlake, OH 44094.

**FREE catalog 99-cent kits**—audio, video, TV computer parts. **ALLKIT**, 434 W. 4th St., West Islip, NY 11795.

**PAY TV and Satellite descrambling**. 54 pages. All systems. America and Canada. Theory, schematics \$11.95. Stunguns schematics \$5.00. Catalogue \$1.00. **SHOJIKI ELECTRONICS CORP.**, 1327 Niagara St., Niagara Falls, NY 14303. C.O.D.'s, (716) 282-1001.

WRITE FOR  
**McGEE'S**  
**SPEAKER & ELECTRONICS CATALOG**  
1001 BARGAINS IN SPEAKERS  
toll free 1-800-346-2433 for ordering only.  
1901 MCGEE STREET KANSAS CITY, MO. 64108

## ENJOY SATELLITE TV

### DO-IT-YOURSELF AND SAVE

Electronic Know-how not required. Easy to build from our plans or kits. Lowest prices on satellite electronics

Send \$1 for catalog or \$8.95 for "Consumer Guide to Satellite Television"  
Mail today to: **GFI-D14, Box 9108  
Missoula, MT 59807**



**UFO** detecting. Detailed book. Theories, electronic projects, and catalog, \$5.95. **UFONICS**, Box 1336-R, Patchogue, NY 11772.

**BUILD** this five digit panel meter and square wave generator including an ohms, capacitance and frequency meter. Detailed instructions \$2.50. Refundable plus 50 cents. **BAGNALL ELECTRONICS**, 179 May, Fairfield, CT 06430.

**40 Electronics projects**, practical one-niters book \$7.95 or 80 in two books \$15.90. **ARCSOFT**, Box 132 RA, Woodsboro, MD 21798.

**CABLE and Subscription-TV** secret manual. Build your own descramblers, converters—HBO, Showtime, Movie Channel, UHF, latest theory schematics, instructions, suppliers. Send \$8.95 to **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

**C-64 owners:** Upgrade your C-64 with RESET key. Plans \$2.00. Kit/plans \$5.00. **ITRONICS**, 7 West Drive, Port Washington, NY 11050.

**FREE** "National Semi Conductor" pocket calculator and catalog of Robots "MOVIE" line. Easily assembled. You control. Great fun. Educational. Send \$4.00 for postage and handling. **ELECTROMANIA**, 51A Sunrise HWY, Lynbrook, NY 11563.

**MASTERCARD AND VISA** are now accepted for payment of your advertising. Simply complete the form on the first page of the Market Center and we will bill.

**SOME OF THE  
GREATEST THINGS  
IN AMERICA  
NEVER CHANGE.**

**SOME DO.**



**Now paying 10.94%.**

U.S. Savings Bonds now pay higher variable interest rates—like money market accounts. At the current rate, you could double your money in less than seven years. You can buy Bonds at most financial institutions.

Or easier still, through your Payroll Savings Plan.

For your free booklet, write: "50 Q&A," U.S. Savings Bonds Division, Washington, DC 20226.

**U.S. SAVINGS BONDS**  
Paying Better Than Ever

Variable rates apply to Bonds purchased on and after 11/1/82 and held at least 5 years. Bonds purchased before 11/1/82 earn variable rates when held beyond 10/31/87. Bonds held less than 5 years earn lower interest.

A public service of this publication.

# Radio Shack Parts Place™

## The Builder's Store! Over 1000 Items in Stock!

### Add Synthesized Speech Output to Your Computer



(1) **Voice Synthesizer IC SPO256-AL2.** Uses programming stored in its built-in 16K ROM to synthesize natural sounding speech. Easy to interface with most microcomputers. Requires low-cost support components and 3.12 MHz clock crystal (available through Radio Shack). 28-pin DIP with detailed specs and programming data. #276-1784 ..... **12.95**

(2) **Text-to-Speech IC CTS256-AL2.** Preprogrammed 8-bit processor translates standard ASCII characters into control data for the synthesizer above. Makes it a snap to add voice output to virtually any personal computer or ASCII terminal. 40-pin DIP with complete data, schematics. Requires 10 MHz crystal (available through Radio Shack). #276-1786 ..... **16.95**

(3) **Audio Amplifier IC LM386.** Requires a minimum of support components. Perfect as an audio output stage for speech synthesizer. 400 mW output. Adjustable gain. 4 to 12 VDC. 8-pin DIP. #276-1731 ..... **1.09**

size above. Makes it a snap to add voice output to virtually any personal computer or ASCII terminal. 40-pin DIP with complete data, schematics. Requires 10 MHz crystal (available through Radio Shack). #276-1786 ..... **16.95**

(3) **Audio Amplifier IC LM386.** Requires a minimum of support components. Perfect as an audio output stage for speech synthesizer. 400 mW output. Adjustable gain. 4 to 12 VDC. 8-pin DIP. #276-1731 ..... **1.09**

### Timer IC Project Book and Parts




**99¢**      **11.95**

**Timer IC Mini-Notebook.** Learn how to use the versatile 555 and 556 timer ICs by building your own circuits. Written in simple language by Forrest Mims III. Large schematic diagrams. 32 pages. #276-5010 ..... **99¢**

**Timer Project Parts.** For above. Requires #276-174 breadboard and 9V battery. #277-061 ..... **11.95**

### Solder DIP Sockets

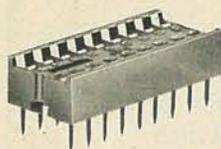


Low As  
**59¢**  
Pkg. of 2

Type	Cat. No.	Price
8-Pin	276-1995	2/59¢
14-Pin	276-1999	2/89¢
16-Pin	276-1998	2/89¢

Type	Cat. No.	Each
18-Pin	276-1992	.49
20-Pin	276-1991	.59
24-Pin	276-1989	.79
28-Pin	276-1997	.89
40-Pin	276-1996	.99


### Computer/Game Connectors

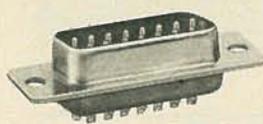

Low As  
**1.99**

Type	Positions	Cat. No.	Each
Solder Sub-D Male	9	276-1537	1.99
Solder Sub-D Female	9	276-1538	2.49
Hood for Above	9	276-1539	1.99
Solder Sub-D Male	25	276-1547	2.99
Solder Sub-D Female	25	276-1548	3.99
Hood for Above	25	276-1549	1.99
Printer Connector	36	276-1534	4.99
Card-Edge Connector	34	276-1564	4.95

### Experiment With Fiber Optics

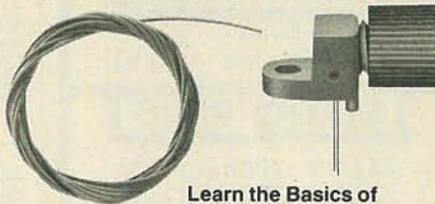

Learn the Basics of  
"Lightwave" Links

**Optical Fiber Cable.** 3-meter (approx. 9 ft.) length of high-quality optical fiber cable. #276-228 ..... **5.99**

**Infrared Emitter/Detector Set.** Use to send analog or digital signals through fiber optic cable. No special tools or hardware required for assembly. Application notes included. #276-225 ..... **4.99**


### Power Transformers

#### 120 VAC Primaries

Type	Volts	Current	Cat. No.	Each
Miniature	6.3	300 mA	273-1384	2.59
Miniature	12.6	300 mA	273-1385	2.79
Miniature	25.2	300 mA	273-1386	3.49
Miniature	12.6 CT	450 mA	273-1365	3.59
Miniature	25.2 CT	450 mA	273-1366	3.99
Standard	6.3	1.2 A	273-1351	3.99
Standard	12.6 CT	1.2 A	273-1352	4.99
Standard	25.2	1.2 A	273-1353	5.99
Heavy-Duty	12.6 CT	3.0 A	273-1511	6.99
Heavy-Duty	25.2 CT	2.0 A	273-1512	7.49
Heavy-Duty	18.0 CT	2.0 A	273-1515	6.99

CT = Center tap

### Tantalum Capacitors

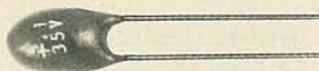

Low As **49¢**

Maximum capacity in a very small size. Standard IC pin spacing. 20% tolerance.

µF	WVDC	Cat. No.	Each
0.1	35	272-1432	.49
0.47	35	272-1433	.49
1.0	35	272-1434	.49
2.2	35	272-1435	.59
10	16	272-1436	.69
22	16	272-1437	.79

### Switch and Relay Values



(4) **Micro-Mini SPDT Relay.** Just 1 1/2 x 3/8 x 1/4". Contacts: 1 amp at 125 VAC. 12 VDC coil. #275-241 ..... **1.99**

(5) **Mercury Switch.** Rated 5 amps at 125 VAC. Style may vary. #275-027 ..... **1.19**

(6) **Illuminated Round SPDT Push-On Switch.** 3 amps at 120 VAC. Lamp requires 12 volts AC/DC. Mounts in 1/2" hole. #275-677 ..... **4.95**

(7) **Illuminated SPST Normally Open or Closed Switch.** 5 amps at 250 VAC. Lamp requires 12 volts AC/DC. With red and green lenses. Mounts in 3/8" hole. #275-678 ..... **5.95**

### We Can Replace Almost Any Industrial Or Entertainment IC or Semiconductor

#### RADIO SHACK'S NEW SPECIAL-ORDER SERVICE

No Minimum Order!  
No Postage Charge!  
Really Convenient!

If the IC or semiconductor you need is not part of our regular stock, our store manager will check our new in-store substitution guide and then special-order a replacement from our warehouse. Your order will be sent to your Radio Shack store and we'll notify you when it arrives. There's no postage to pay or other extra charges for this convenient service! Visit our store near you for details.



### SALE! 16-Range LCD Digital Multitester

Reg. 49.95  
**Save \$10 39.95**

- Compact Size ■ Easy to Use
- Fused and Overload Protected
- Diode/Semiconductor Test Mode

Step up to digital accuracy and the convenience of full auto-polarity operation at big savings! The high-contrast liquid crystal display features low-battery and over-range indicators. Measures up to 1000 volts DC, 500 volts AC, 2 amps DC and 2 megohms resistance. There are four ranges for each function. Includes test leads, owner's manual and spare fuse. 5 3/16 x 3 1/4 x 1 7/16". Batteries extra. #22-189 ..... **Sale 39.95**

Protective Case for Above. #22-153 ..... **5.95**



Over 1000 items in stock: Binding posts, Books, Breadboards, Buzzers, Capacitors, Chokes, Clips, Connectors, Fuses, Hardware, ICs, Jacks, Knobs, Lamps, Multitesters, PC Boards, Plugs, Rectifiers, Relays, Resistors, Switches, Tools, Transformers, Transistors, Wire, Zener Diodes, and more!

**Radio Shack®**  
A DIVISION OF TANDY CORPORATION

Prices apply at participating Radio Shack stores and dealers

## Saratoga Electronics

### EPROMS

2716-450ns	\$2.50
2732-450ns	\$3.25
2764-250ns	\$3.50
27128-250ns	\$4.75

### DYNAMIC RAMS

4164-150ns	\$ .90
41256-150ns	\$3.95

### STATIC RAMS

2114LP-200ns	\$1.50
2114LP-150ns	\$1.65
6116P-4	\$1.50
6264P-150ns	\$4.95
6264LP-150ns	\$6.25

### Microprocessors

8087-3	\$ 99.95
80287-3	\$225.00
8088	\$ 10.00
8085-2	\$ 4.25
8243	\$ 2.50
8250	\$ 8.95
8253-5	\$ 3.95
8255-5	\$ 5.25
8272	\$ 12.95
8274	\$ 12.95

CALL US FOR YOUR  
OTHER I.C. NEEDS!  
WE STOCK 74LS, 74S,  
7400, CMOS, LINEAR,  
AND MANY MORE I.C.'s!

### \*\*SPECIALS\*\*

74LS139 .25	74S02 .15
74LS161 .25	74S51 .25
LM350K 2.00	74S74 .30
CAP: 10000uf 25V	.50
10000uf 50V	.50
<b>TRANSFORMER: AC ADAPTOR</b>	
IN: 117/60HZ	
OUT: 12VAC(CT) 250mA	
\$ \$ 1.00 ea.	

**800-621-0854 ext. 245**

## SARATOGA ELECTRONICS

12380 SARATOGA-SUNNYVALE ROAD  
SARATOGA, CA 95070  
(408) 448-4848

CIRCLE 260 ON FREE INFORMATION CARD

COMPLETE line of video processing kits in stock. Over the air and Satellite. Super Z, Raider, Black Widow, O'Hara C. Full line of wholesale cable equipment. UPS daily, C.O.D. welcome. Call (301) 666-2755 or write to SEC, CORP., P.O. Box 912, Baltimore, MD 21030.

CB antennas: build beams—quads—ground-planes—complete manual \$4.00—KORONA'S TENNAFARM, 1117 Dewitt Terrace, Linden, NJ 07036.

THE BEST PLACE to BUY, SELL or TRADE NEW and USED EQUIPMENT  
**NUTS & VOLTS MAGAZINE**  
BOX 1111-E • PLACENTIA, CA 92670  
(714) 632-7721  
Join Thousands of Readers Nationwide Every Month  
**ONE YEAR U.S. SUBSCRIPTIONS**  
\$10.00 - 3rd Class • \$15.00 - 1st Class  
\$35.00 - Lifetime - 3rd Class

### NUTS & VOLTS

HIGH GEAR  
COMPUTERS  
SOFTWARE  
SCANNERS • OPTICS  
TEST EQUIPMENT  
MICROWAVE  
SATELLITE  
AUDIO VISUAL  
NEW PRODUCTS  
COMPONENTS • KITS  
ANTIQUA ELECT.  
PUBLICATIONS  
PLANS • SERVICES

### GRAPHIC EQUALIZERS, ETC.

NOISE eliminators, expanders, power meters, others. Twelve-24 bands/channel equalizers from \$89.00. Kit see R-E 5-6/78, 2/80, 3-4/81. Catalog: SSS, 856R Lynnrose, Santa Rosa, CA 95404. (707) 546-3895.

### CABLE-TV

DEALERS wanted: Channel 2, 3, and 4 notch filters. Money back guarantee. Send \$15.00 for sample and quantity price list. Specify channel(s). GARY KURTZ, P.O. Box 291394, Davie, FL 33329.

### EPROM PROGRAMMING

HOBBYISTS: Pretested EPROMs sold with your programming installed. Program listing provided. Fast service. Write or call: ROMULUS MICRO-CONTROL, Box 8669, Rockville, MD 20856; (301) 540-8863.

### TRS-80 GAMES

GAMES: "The Game Machine"—3 arcade style games for TRS-80 model III/IV with 1 disk drive. Only \$15.95. Send \$2.00 for more information. JAYARE PRODUCTIONS, Box 126, Caddo, TX 76029.

### HIGH PERFORMANCE AUDIO KITS

\*\*Enjoy Surround Sound at home...  
P-250-DL \$249 assem/\$179 kit  
\*\*Reduce tape noise 30 dB...  
P-522-NR \$139 assem/\$79 kit  
call or write for a free full line catalog  
PHOENIX SYSTEMS Dept 901. M/C & VISA  
P.O. Box 338-B (404) 934-9626  
Stone Mtn., Ga. 30086 add \$1 for first class

### REEL-TO-REEL TAPES


AMPEX professional series open reel tape, 1800-or 2400-feet on 7-inch reels, used once. Case of 40, \$45.00. 10 1/2 x 3600 feet and cassettes available. MasterCard/Visa. VALTECH ELECTRONICS, Box 6-RE, Richboro, PA 18954 (215) 322-4866.

# Imagine.

Imagine. With your help, our generation could be the one that beats Huntington's... forever. Please give generously to the National Huntington's Disease Association.

**H** NATIONAL HUNTINGTON'S DISEASE ASSOCIATION

# The Prettiest Picture.

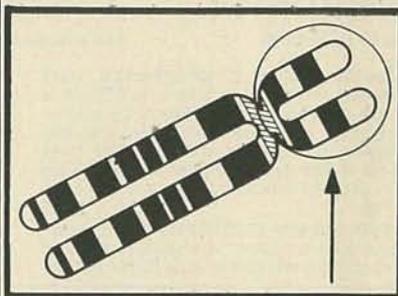

Copyright © 1981 by The New York Times Company. Reprinted by permission.

To everyone with a chance of having Huntington's Disease, the discovery of a genetic "marker" on chromosome #4 is the prettiest picture in the world. Because it means that, for the first time, scientists know on what chromosome the Huntington's gene is located. And that makes us much closer to being able to determine who will have Huntington's... and who won't.

Your contributions helped us find the marker, they can also help us find a cure. Please give generously to the National Huntington's Disease Association. Make ours the generation that wipes out Huntington's... forever.

**H** NATIONAL HUNTINGTON'S DISEASE ASSOCIATION

National Huntington's Disease Association  
1182 Broadway, Ste. 402 NY, NY 10001

# Parts

**TOLL FREE**  
**800-854-8230**  
 Calif. Residents  
**714-558-8813**

**OUR POLICY**

- NO surcharge for VISA or Mastercard.
- NO sales tax. • All shipments Insured.
- Your card is NOT charged until we ship.
- Same day FEDEX shipment is available.
- Volume purchasing agreements available.
- Government agencies, corporate and Institutional PO's accepted.
- Orders subject to availability.
- All items have manufacturer warranty. Some warranties up to 5 years.
- Pricing subject to change w/o notice.
- Returns or cancellations may be subject to restocking fee.
- ACP Retail Store pricing may vary.
- We are not responsible for typos.

### UPS POWER SUPPLY

Back Up Power for your IBM, Apple or Compatible

UPS-PC 300 Watts \$277.00  
 UPS-XT 425 Watts 455.00  
 UPS-AT 1000 Watts 975.00

### A-B PRINTER SWITCH

An AB Switch allows use of two printers with your computer system. We stock over 15 different configurations.

AB Switch (Centronics) \$69.00  
 AB Switch (DB25) 59.00

### COLOR VIDEO CARDS

Planitron Color Plus \$375.00  
 IBM Color Card 327.00  
 IBM Mono Card separator 215.00  
 STB Graphics Plus 300.00  
 Paradise Multiplay Card 345.00  
 Everex Graphics Edge 345.00

### DRIVE CABINETS

IBM Style Hard disk with power supply and fan \$195.00  
 Dual Hard Disk w/upper sup & fan 295.00  
 Dual 5 1/4" Full Height vertical mount 65.00  
 Dual 5 1/4" Full Height horizontal mount 99.00  
 Dual 5 1/4" Thinline w/upper sup & fan 60.00  
 Single 5 1/4" Full Height w/upper sup & fan 56.00  
 Single 5 1/4" Thinline w/upper sup & fan 60.00

### PERYSYST CARDS

Persyst Mono Combo - NEW! \$336.00  
 Persyst Color Combo - NEW! 336.00  
 Persyst Board Board 445.00  
 Persyst Shortport Card Call  
 Persyst Mini Mono Call  
 Persyst + 1 Time Spectrum w/4K 179.95  
 Persyst 192K Rainbow DEC Card 149.95

### CMOS

4000 \$ 26 4008 \$ 65 4059 \$ 70 4505 \$ 85  
 2012 \$ 22 4009 \$ 75 4060 \$ 85 4506 \$ 110  
 4001 \$ 24 4010 \$ 75 4061 \$ 85 4507 \$ 110  
 4002 \$ 24 4011 \$ 75 4062 \$ 85 4508 \$ 110  
 4003 \$ 24 4012 \$ 75 4063 \$ 85 4509 \$ 110  
 4004 \$ 24 4013 \$ 75 4064 \$ 85 4510 \$ 110  
 4005 \$ 24 4014 \$ 75 4065 \$ 85 4511 \$ 110  
 4006 \$ 24 4015 \$ 75 4066 \$ 85 4512 \$ 110  
 4007 \$ 24 4016 \$ 75 4067 \$ 85 4513 \$ 110  
 4008 \$ 24 4017 \$ 75 4068 \$ 85 4514 \$ 110  
 4009 \$ 24 4018 \$ 75 4069 \$ 85 4515 \$ 110  
 4010 \$ 24 4019 \$ 75 4070 \$ 85 4516 \$ 110  
 4011 \$ 24 4020 \$ 75 4071 \$ 85 4517 \$ 110  
 4012 \$ 24 4021 \$ 75 4072 \$ 85 4518 \$ 110  
 4013 \$ 24 4022 \$ 75 4073 \$ 85 4519 \$ 110  
 4014 \$ 24 4023 \$ 75 4074 \$ 85 4520 \$ 110  
 4015 \$ 24 4024 \$ 75 4075 \$ 85 4521 \$ 110  
 4016 \$ 24 4025 \$ 75 4076 \$ 85 4522 \$ 110  
 4017 \$ 24 4026 \$ 75 4077 \$ 85 4523 \$ 110  
 4018 \$ 24 4027 \$ 75 4078 \$ 85 4524 \$ 110  
 4019 \$ 24 4028 \$ 75 4079 \$ 85 4525 \$ 110  
 4020 \$ 24 4029 \$ 75 4080 \$ 85 4526 \$ 110  
 4021 \$ 24 4030 \$ 75 4081 \$ 85 4527 \$ 110  
 4022 \$ 24 4031 \$ 75 4082 \$ 85 4528 \$ 110  
 4023 \$ 24 4032 \$ 75 4083 \$ 85 4529 \$ 110  
 4024 \$ 24 4033 \$ 75 4084 \$ 85 4530 \$ 110  
 4025 \$ 24 4034 \$ 75 4085 \$ 85 4531 \$ 110  
 4026 \$ 24 4035 \$ 75 4086 \$ 85 4532 \$ 110  
 4027 \$ 24 4036 \$ 75 4087 \$ 85 4533 \$ 110  
 4028 \$ 24 4037 \$ 75 4088 \$ 85 4534 \$ 110  
 4029 \$ 24 4038 \$ 75 4089 \$ 85 4535 \$ 110  
 4030 \$ 24 4039 \$ 75 4090 \$ 85 4536 \$ 110  
 4031 \$ 24 4040 \$ 75 4091 \$ 85 4537 \$ 110  
 4032 \$ 24 4041 \$ 75 4092 \$ 85 4538 \$ 110  
 4033 \$ 24 4042 \$ 75 4093 \$ 85 4539 \$ 110  
 4034 \$ 24 4043 \$ 75 4094 \$ 85 4540 \$ 110  
 4035 \$ 24 4044 \$ 75 4095 \$ 85 4541 \$ 110  
 4036 \$ 24 4045 \$ 75 4096 \$ 85 4542 \$ 110  
 4037 \$ 24 4046 \$ 75 4097 \$ 85 4543 \$ 110  
 4038 \$ 24 4047 \$ 75 4098 \$ 85 4544 \$ 110  
 4039 \$ 24 4048 \$ 75 4099 \$ 85 4545 \$ 110  
 4040 \$ 24 4049 \$ 75 4100 \$ 85 4546 \$ 110  
 4041 \$ 24 4050 \$ 75 4101 \$ 85 4547 \$ 110  
 4042 \$ 24 4051 \$ 75 4102 \$ 85 4548 \$ 110  
 4043 \$ 24 4052 \$ 75 4103 \$ 85 4549 \$ 110  
 4044 \$ 24 4053 \$ 75 4104 \$ 85 4550 \$ 110  
 4045 \$ 24 4054 \$ 75 4105 \$ 85 4551 \$ 110  
 4046 \$ 24 4055 \$ 75 4106 \$ 85 4552 \$ 110  
 4047 \$ 24 4056 \$ 75 4107 \$ 85 4553 \$ 110  
 4048 \$ 24 4057 \$ 75 4108 \$ 85 4554 \$ 110  
 4049 \$ 24 4058 \$ 75 4109 \$ 85 4555 \$ 110  
 4050 \$ 24 4059 \$ 75 4110 \$ 85 4556 \$ 110

### SPECIAL BUY

Shugart SA 4004 14" 28MB Hard Disk  
**\$499.00**

### MODEM SPECIAL

Hayes Smartmodem Compatible  
 1200 Baud, External, Sold for \$399.00  
**\$219.00**

### INTERSL STD-BUS BOARDS

LIST	ACP
ISB3100 280 CPU	8200 369.95
ISB3101 280 Univ. CPU	8200 369.95
ISB3110 8088 CPU	200 79.95
ISB3210 16K CMOS RAM	610 99.95
ISB3310 16K Static RAM	200 39.95
ISB3320 16K CMOS RAM	750 119.95
ISB3330 280 PIO (D mating)	210 49.95
ISB3340 280 Parallel P/D	210 49.95
ISB3400 Opto Para. Input	300 119.95
ISB3400 Floppy Controller	215 79.95
ISB3410 SAS (DMA) W/Int. Interf.	255 99.95
ISB3500 Trac.	215 99.95
ISB3610 Opto-iso Input	270 119.95
ISB3620 SPTI Relay	150 99.95
ISB3630 EPROM	190 89.95
ISB3640 Arithmetic	275 149.95
ISB3650 I/O Program	260 79.95
ISB3700 Sync/Async	245 89.95
ISB3710 Univ. Sync/Async	245 89.95
ISB3720 REMO/DCS	315 149.95
ISB3800 12 Bit A/D	720 299.95

### TRANSISTORS/DIODES

PN2222A	7/5.00	2N3904	11/81.00
2N2907	3/1.00	2N3906	11/1.00
2N2908	3/1.00	2N3907	21.00
2N2910	4/5	2N3908	21.00
2N2915	4/5	2N3909	21.00
2N2920	4/5	2N3910	21.00
2N2925	4/5	2N3911	21.00
2N2930	4/5	2N3912	21.00
2N2935	4/5	2N3913	21.00
2N2940	4/5	2N3914	21.00
2N2945	4/5	2N3915	21.00
2N2950	4/5	2N3916	21.00
2N2955	4/5	2N3917	21.00
2N2960	4/5	2N3918	21.00
2N2965	4/5	2N3919	21.00
2N2970	4/5	2N3920	21.00
2N2975	4/5	2N3921	21.00
2N2980	4/5	2N3922	21.00
2N2985	4/5	2N3923	21.00
2N2990	4/5	2N3924	21.00
2N2995	4/5	2N3925	21.00
2N3000	4/5	2N3926	21.00
2N3005	4/5	2N3927	21.00
2N3010	4/5	2N3928	21.00
2N3015	4/5	2N3929	21.00
2N3020	4/5	2N3930	21.00
2N3025	4/5	2N3931	21.00
2N3030	4/5	2N3932	21.00
2N3035	4/5	2N3933	21.00
2N3040	4/5	2N3934	21.00
2N3045	4/5	2N3935	21.00
2N3050	4/5	2N3936	21.00
2N3055	4/5	2N3937	21.00
2N3060	4/5	2N3938	21.00
2N3065	4/5	2N3939	21.00
2N3070	4/5	2N3940	21.00
2N3075	4/5	2N3941	21.00
2N3080	4/5	2N3942	21.00
2N3085	4/5	2N3943	21.00
2N3090	4/5	2N3944	21.00
2N3095	4/5	2N3945	21.00
2N3100	4/5	2N3946	21.00
2N3105	4/5	2N3947	21.00
2N3110	4/5	2N3948	21.00
2N3115	4/5	2N3949	21.00
2N3120	4/5	2N3950	21.00
2N3125	4/5	2N3951	21.00
2N3130	4/5	2N3952	21.00
2N3135	4/5	2N3953	21.00
2N3140	4/5	2N3954	21.00
2N3145	4/5	2N3955	21.00
2N3150	4/5	2N3956	21.00
2N3155	4/5	2N3957	21.00
2N3160	4/5	2N3958	21.00
2N3165	4/5	2N3959	21.00
2N3170	4/5	2N3960	21.00
2N3175	4/5	2N3961	21.00
2N3180	4/5	2N3962	21.00
2N3185	4/5	2N3963	21.00
2N3190	4/5	2N3964	21.00
2N3195	4/5	2N3965	21.00
2N3200	4/5	2N3966	21.00
2N3205	4/5	2N3967	21.00
2N3210	4/5	2N3968	21.00
2N3215	4/5	2N3969	21.00
2N3220	4/5	2N3970	21.00
2N3225	4/5	2N3971	21.00
2N3230	4/5	2N3972	21.00
2N3235	4/5	2N3973	21.00
2N3240	4/5	2N3974	21.00
2N3245	4/5	2N3975	21.00
2N3250	4/5	2N3976	21.00
2N3255	4/5	2N3977	21.00
2N3260	4/5	2N3978	21.00
2N3265	4/5	2N3979	21.00
2N3270	4/5	2N3980	21.00
2N3275	4/5	2N3981	21.00
2N3280	4/5	2N3982	21.00
2N3285	4/5	2N3983	21.00
2N3290	4/5	2N3984	21.00
2N3295	4/5	2N3985	21.00
2N3300	4/5	2N3986	21.00
2N3305	4/5	2N3987	21.00
2N3310	4/5	2N3988	21.00
2N3315	4/5	2N3989	21.00
2N3320	4/5	2N3990	21.00
2N3325	4/5	2N3991	21.00
2N3330	4/5	2N3992	21.00
2N3335	4/5	2N3993	21.00
2N3340	4/5	2N3994	21.00
2N3345	4/5	2N3995	21.00
2N3350	4/5	2N3996	21.00
2N3355	4/5	2N3997	21.00
2N3360	4/5	2N3998	21.00
2N3365	4/5	2N3999	21.00
2N3370	4/5	2N4000	21.00
2N3375	4/5	2N4001	21.00
2N3380	4/5	2N4002	21.00
2N3385	4/5	2N4003	21.00
2N3390	4/5	2N4004	21.00
2N3395	4/5	2N4005	21.00
2N3400	4/5	2N4006	21.00
2N3405	4/5	2N4007	21.00
2N3410	4/5	2N4008	21.00
2N3415	4/5	2N4009	21.00
2N3420	4/5	2N4010	21.00
2N3425	4/5	2N4011	21.00
2N3430	4/5	2N4012	21.00
2N3435	4/5	2N4013	21.00
2N3440	4/5	2N4014	21.00
2N3445	4/5	2N4015	21.00
2N3450	4/5	2N4016	21.00
2N3455	4/5	2N4017	21.00
2N3460	4/5	2N4018	21.00
2N3465	4/5	2N4019	21.00
2N3470	4/5	2N4020	21.00
2N3475	4/5	2N4021	21.00
2N3480	4/5	2N4022	21.00
2N3485	4/5	2N4023	21.00
2N3490	4/5	2N4024	21.00
2N3495	4/5	2N4025	21.00
2N3500	4/5	2N4026	21.00
2N3505	4/5	2N4027	21.00
2N3510	4/5	2N4028	21.00
2N3515	4/5	2N4029	21.00
2N3520	4/5	2N4030	21.00
2N3525	4/5	2N4031	21.00
2N3530	4/5	2N4032	21.00
2N3535	4/5	2N4033	21.00
2N3540	4/5	2N4034	21.00
2N3545	4/5	2N4035	21.00
2N3550	4/5	2N4036	21.00
2N3555	4/5	2N4037	21.00
2N3560	4/5	2N4038	21.00
2N3565	4/5	2N4039	21.00
2N3570	4/5	2N4040	21.00
2N3575	4/5	2N4041	21.00
2N3580	4/5	2N4042	21.00
2N3585	4/5	2N4043	21.00
2N3590	4/5	2N4044	21.00
2N3595	4/5	2N4045	21.00
2N3600	4/5	2N4046	21.00
2N3605	4/5	2N4047	21.00
2N3610	4/5	2N4048	21.00
2N3615	4/5	2N4049	21.00
2N3620	4/5	2N4050	21.00
2N3625	4/5	2N4051	21.00
2N3630	4/5	2N4052	21.00
2N3635	4/5	2N4053	21.00
2N3640	4/5	2N4054	21.00
2N3645	4/5	2N4055	21.00
2N3650	4/5	2N4056	21.00
2N3655	4/5	2N4057	21.00
2N3660	4/5	2N4058	21.00
2N3665	4/5	2N4059	21.00
2N3670	4/5	2N4060	21.00
2N3675	4/5	2N4061	21.00
2N3680	4/5	2N4062	21.00
2			

ALL SALES SUBJECT TO THE TERMS OF OUR 90 DAY LIMITED WARRANTY. FREE COPY UPON REQUEST.


**SOLAR CELL SPECIAL:** 4 In. Diameter Rated .45 VDC At 1.2 Amps Or Better. Brand New Units, Cosmetic Seconds, But Perfect Electrically. \$3.99 6/\$20.

**THE NEW ZRT-80  
CRT TERMINAL BOARD!**

A LOW COST Z-80 BASED SINGLE BOARD THAT ONLY NEEDS AN ASCII KEYBOARD, POWER SUPPLY, AND VIDEO MONITOR TO MAKE A COMPLETE CRT TERMINAL. USE AS A COMPUTER CONSOLE, OR WITH A MODEM FOR USE WITH ANY OF THE PHONE-LINE COMPUTER SERVICES.

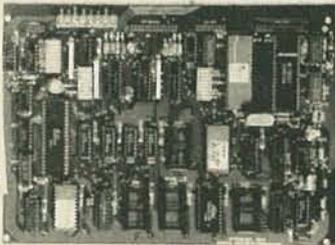**FEATURES:**

- Uses a Z80A and 6845 CRT Controller for powerful video capabilities.
- RS232 at 16 BAUD Rates from 75 to 19,200.
- 24 x 80 standard format (60 Hz).
- Optional formats from 24 x 80 (50 Hz) to 64 lines x 96 characters (60 Hz).
- Higher density formats require up to 3 additional 2K x 8 6116 RAMS.
- Uses N.S. INS 8250 BAUD Rate Gen. and USART combo IC.
- 3 Terminal Emulation Modes which are Dip Switch selectable. These include the LSI-ADM3A, the Heath H-19, and the Beehive.
- Composite or Split Video.
- Any polarity of video or sync.
- Inverse Video Capability.
- Small Size: 6.5 x 9 inches.
- Upper & lower case with descenders.
- 7 x 9 Character Matrix.
- Requires Par. ASCII keyboard.



**\$89<sup>95</sup>** #ZRT-80

(COMPLETE KIT, 2K VIDEO RAM)

BLANK PCB WITH 2716 CHAR. ROM. 2732 MON. ROM

**\$49<sup>95</sup>**

SOURCE DISKETTE - ADD \$10  
SET OF 2 CRYSTALS - ADD \$7.50

FOR 8 IN. SOURCE DISK (CP/M COMPATIBLE) ADD \$10


**Digital Research Computers**

P.O. BOX 461565 • GARLAND, TEXAS 75046 • (214) 225-2309

Call or write for a free catalog on Z-80 or 6809 Single Board Computers, SS-50 Boards, and other S-100 products.

TERMS: Add \$3.00 postage. We pay balance. Orders under \$15 add 75c handling. No C.O.D. We accept Visa and MasterCard. Texas Res. add 5-1/8% Tax. Foreign orders (except Canada) add 20% P & H. Orders over \$50 add 85c for insurance.

**Call for your FREE 1986 CATALOG**

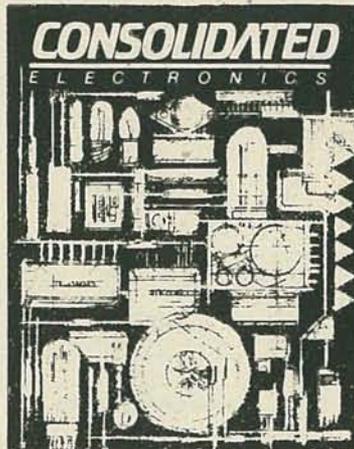

We at Consolidated Electronics have filled this 128 page catalog with the best manufacturers and the highest quality products at the best possible price, and shipped to you in 24 hrs. or less.

**CONSOLIDATED  
ELECTRONICS**

705 Watervliet Ave., Dayton, Ohio 45420-2599

**1-800-543-3568**

National & Canadian WATS

in Dayton call (513) 252-5662

Telex No. 288-229

**CIRCLE 81 ON FREE INFORMATION CARD**

**NEW ORLEANS AND WM. B. ALLEN**

**FLUKE**

- FLUKE 21 .....\$ 87
- FLUKE 23 .....\$127
- FLUKE 25 .....\$200
- FLUKE 73 .....\$ 75
- FLUKE 75 .....\$ 88
- FLUKE 77 .....\$115
- FLUKE 8020B .....\$174
- FLUKE 8060A .....\$305

**AS CLOSE AS YOUR TELEPHONE**

CALL TOLL FREE FOR SAME DAY SHIPMENT ON

**DISCOUNT PRICED TEST EQUIPMENT**

18 LEADING MANUFACTURERS IN INSTRUMENTATION INCLUDING HUNTRON

**HITACHI**

- V-212-20MHZ.....\$ 451
  - V-422-40MHZ.....\$ 679
  - V-650-60MHZ.....\$ 938
  - V-1050-100MHZ.....\$1252
  - V-6041-40MHZ DIG. STORAGE .....\$5311
  - V-1070-100MHZ QUAD TRACE  
DIGITAL DISPLAY .....\$1532
  - V-1100-100MHZ QUAD TRACE .....\$2260
- ALL PRICES INCLUDE PROBES

CALL TOLL FREE

**800 535-9593**

LOUISIANA 800 462-9520

**WM. B. ALLEN SUPPLY CO.**

ALLEN SQUARE


300 BLOCK NORTH RAMPART, NEW ORLEANS, LA 70112

**CIRCLE 103 ON FREE INFORMATION CARD**

# RAMSEY

# THE FIRST NAME IN ELECTRONIC TEST GEAR

PRICE CUT

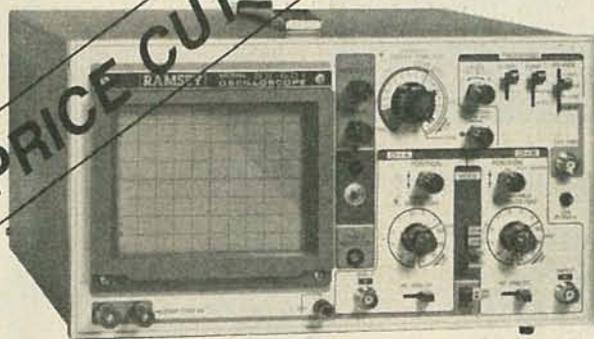


## 20 MHz DUAL TRACE OSCILLOSCOPE

Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features include a component testing circuit for resistor, capacitor, digital circuit and diode testing. • TV video sync filter • wide bandwidth & high sensitivity • internal graticule • front panel trace rotator • Z axis • high sensitivity x-y mode • regulated power supply • built-in calibrator • rock solid triggering

\*USA—Add \$10.00 per unit for postage, overseas orders add 15% of total order for insured surface mail.

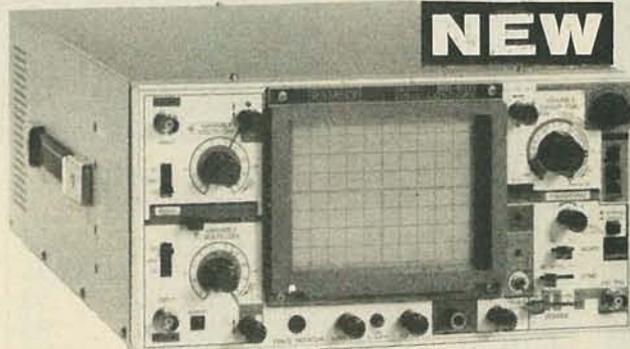~~\$399.95\*~~  
high quality hook on probes included  
**\$369.95**



NEW

## 45 MHz DUAL SWEEP OSCILLOSCOPE

The Ramsey 625 is a dual time base, delayed sweep unit that includes a built-in signal delay line to permit clear viewing during very short rise times of high frequency waveforms. Other features include: variable trigger holdoff • 20 calibrated sweep time ranges from 0.5 s/div to 0.2 μs/div • fully adjustable sweep time • X5 sweep magnification • five trigger sources: CH1, CH2, LINE EXTERNAL and INTERNAL (V mode) • front panel x-y operation, Z axis input • sum difference of CH1 and CH2 waveforms displayed as single trace • sweep gate and sweep output • auto focus • single sweep

\*Same as unit to left.

~~\$799.95\*~~  
high quality hook on probes included  
**\$669.95**



## RAMSEY D-1100 VOM MULTITESTER

Compact and reliable, designed to service a wide variety of equipment. Features include • mirror back scale • double-jeweled precision moving coil • double overload protection • an ideal low cost unit for the beginner or as a spare back-up unit


~~\$199.95~~ test leads and battery included  
**\$129.95**


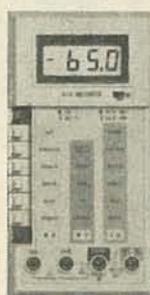
## NEW RAMSEY 1200 VOM MULTITESTER

Check transistors, diodes and LEDs with this professional quality meter. Other features include: decimal scale • 20K volt metering system • 3 1/2" mirrored scale • polarity switch • 20 measuring ranges • safety probes • high impact plastic case


~~\$249.95~~ test leads and battery included  
**\$199.95**


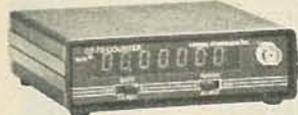
## RAMSEY D-3100 DIGITAL MULTIMETER

Reliable, accurate digital measurements at an amazingly low cost • in-line color coded push buttons, speeds range selection • abs plastic tilt stand • recessed input jacks • overload protection on all ranges • 3 1/2 digit LCD display with auto zero, auto polarity & low BAT. indicator

**\$499.95** test leads and battery included



## CT-70 7 DIGIT 525 MHz COUNTER

Lab quality at a breakthrough price. Features • 3 frequency ranges each with pre amp • dual selectable gate times • gate activity indicator • 50mV @ 150 MHz typical sensitivity • wide frequency range • 1 ppm accuracy

**\$119.95** wired includes AC adapter

CT-70 kit ..... \$99.95  
BP-4 nicad pack ..... 8.95



## CT-90 9 DIGIT 600 MHz COUNTER

The most versatile for less than \$300. Features 3 selectable gate times • 9 digits • gate indicator • display hold • 25mV @ 150 MHz typical sensitivity • 10 MHz timebase for WWV calibration • 1 ppm accuracy

**\$149.95** wired includes AC adapter

CT-90 kit ..... \$129.95  
OV-1 0.1 PPM oven timebase ..... 59.95  
BP-4 nicad pack ..... 8.95




## CT-125 9 DIGIT 1.2 GHz COUNTER

A 9 digit counter that will outperform units costing hundreds more. • gate indicator • 24mV @ 150 MHz typical sensitivity • 9 digit display • 1 ppm accuracy • display hold • dual inputs with preamps

**\$169.95** wired includes AC adapter

BP-4 nicad pack ..... 8.95

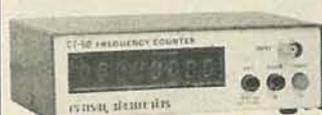

## CT-50 8 DIGIT 600 MHz COUNTER

A versatile lab bench counter with optional receive frequency adapter, which turns the CT-50 into a digital readout for most any receiver • 25 mV @ 150 MHz typical sensitivity • 8 digit display • 1 ppm accuracy

**\$169.95** wired

CT-50 kit ..... \$139.95  
RA-1 receiver adapter kit ..... 14.95



## DM-700 DIGITAL MULTIMETER

Professional quality at a hobbyist price. Features include 26 different ranges and 5 functions • 3 1/2 digit, 1/2 inch LED display • automatic decimal placement • automatic polarity

**\$119.95** wired includes AC adapter

DM-700 kit ..... \$99.95  
MP-1 probe set ..... 4.95



## PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies UP in frequency • great for PL tone measurements • multiplies by 10 or 100 • 0.01 Hz resolution & built-in signal preamp/conditioner

**\$49.95** wired

PS-2 kit ..... \$39.95




## PR-2 COUNTER PREAMP

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for shifting RF • ideal receiver/TV preamp

**\$44.95** wired includes AC adapter

PR-2 kit ..... \$34.95

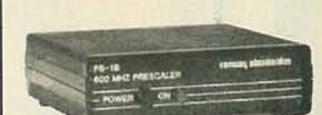

## PS-1B 600 MHz PRESCALER

Extends the range of your present counter to 600 MHz • 2 stage preamp • divide by 10 circuitry • sensitivity, 25mV @ 150 MHz • BNC connectors • drives any counter

**\$59.95** wired includes AC adapter

PS-1B kit ..... \$49.95

### ACCESSORIES FOR RAMSEY COUNTERS

- Telescopic whip antenna—BNC plug ..... \$ 8.95
- High impedance probe, light loading ..... 16.95
- Low pass probe, audio use ..... 16.95
- Direct probe, general purpose use ..... 13.95
- Tilt ball, for CT-70, 90, 125 ..... 3.95



PHONE ORDERS CALL  
**716-586-3950**  
TELEX 466735 RAMSEY CI

TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased, return in original form for refund • add 6% for shipping and insurance to a maximum of \$10.00 • overseas add 15% for surface mail • COD add \$2.50 (COD in USA only) • orders under \$15.00 add \$1.50 • NY residents add 7% sales tax • 90 day parts warranty on all kits • 1 year parts & labor warranty on all wired units.



RAMSEY ELECTRONICS, INC.  
2575 Baird Rd.  
Penfield, N.Y. 14626

NOVEMBER 1985

# CALL 1-800-245-2235 AND YOUR SEARCH IS OVER

## SPECIAL 64K DRAM FULLY FUNCTIONAL WITH SLIGHTLY SHORTER LEADS 200 NS OR FASTER

4164 .45  
4416 .90

If you are seeking hard to find part numbers at hard to find low prices.

You are probably already familiar with our low pricing and large inventory of popular ICs, but a big part of our story is what doesn't appear in our ads.

PC boards are the primary source of our IC inventory. As you know our patented process enables us to remove ICs from boards without any degradation of the ICs. We obtain the boards from a wide variety of sources, which enables us to process a wide variety of ICs. Some of the boards we obtain consist of obsolete technology. This results in a reasonable stock of replacement parts for products that might not be otherwise available.

## GROUP PRICED EPROMS

2708, 2716, 2732,  
2764, 27128

250NS 3.50  
300NS 3.00  
350NS 2.75  
450NS 2.25  
650NS 1.75

		GROUP PRICED LOGIC-TTL		GROUP PRICED LOGIC			
ADC-0804	3.50	74XX, 74LSXX	.25	ECL 10K	1.00	MC840	.75
DAC-0808	1.50	741XX, 74LS1XX, 74SXX	.35	ECL 100K	5.00	MC8506	10.00
ADC-0809	3.50	742XX, 74LS2XX	.50	CMOS 40XX	.25	8641	1.00
TLO82	.50	743XX, 74LS3XX	.50	CMOS 45XX	.50	DS8820	.50
AY5-1013	1.50	74S2XX, 74S3XX	.60			DS8832	.50
AY3-1015	1.50					DS8833	.50
TIL117	.50					MB8861	.50
MC1414	.70					MB8874	.50
1400-100	2.00					AY3-8910	2.00
1420-55	2.00					AY3-8912	2.00
MC1458	.40					8T09	.50
MC1472	.50					8T14	.50
MC1488	.50					8T20	.50
MC1489	.50					8T23	.50
FD1793	5.00					8T24	.50
ULN2003	.50					8T26	.50
2006	.70					8T28	.50
DG201	.25					8T37	.50
ULN2074	2.00					8T38	.50
2101-250	.50					FD8216	5.00
2102-450	.50					9312	.80
DG211	1.00					9314	.60
2111-250	1.00					9321	.75
2111-450	1.00					9328	1.00
2114-150	.80					9338	1.00
2114-200	.80					93419	3.00
2114-250	.80					93422	3.00
2114-300	.50					93425	3.00
2114-450	.50					936	2.00
2115-70	3.00					93L22	.50
2118-120	1.00					93L24	.75
2118-150	.75					93L422	3.00
2118-200	.50					93S16	.50
2125-45	3.00					93S46	2.00
2141-150	.80					93S48	.80
2147-45	2.00					9401	5.00
2147-55	2.00					9602	.75
2147-70	2.00					9614	.75
2148-55	2.00					9615	.75
2149-49	2.00					96L02	1.50
X2212	1.00					96LS02	1.50
MPQ2222	.75					TMS9900	3.00
25LS2519	.50					TMS9901	1.50
25S10	.60					TMS9904	3.00
25S18	.60					TMS9914	3.00
2532-450	2.25					TMS9918	20.00
2651	4.00					TMS9980	10.00
2661	4.00					Z8001	7.50
26LS31	1.00					Z80ACPU	2.00
26S10	.60					Z80ACTC	2.00
2708-500	2.00					Z80ADMA	4.50
2708-550	2.00					Z80APIO	2.00
27128-200	5.00					Z80ASIQ	3.75
FSA2719	1.25					Z80ASIO/2	4.50
27S03	.50					Z80BCPU	3.00
AM2901	7.00					Z80CPU	1.00
LM2901	3.00					Z80CTC	1.00
AM2903	5.00					Z80PIO	1.00
AM2905	1.50					Z80SIQ	3.00
Q2T2905	1.50						
LM2907	1.25						
LM2907(8 pin)	1.25						
FPQ2907	.75						
AM2910	5.00						
AM2911	5.00						
LM2917	1.25						
AM2940	2.00						
UDN2957	.50						
AM2965	.75						
AM2966	.75						
LM301(8 pin)	.25						
TP3040	5.00						
CA3054	.50	MM5060	3.50	75107	.50	MC840	.75
LM308(8 pin)	.50	MK5116	.25	75110	.50	MC8506	10.00
CA3080(8 pin)	.50	TMS5220	5.00	75113	.50	8641	1.00
LM310(8 pin)	1.00	5257-450	.50	75138	.50	DS8820	.50
LM311(8 pin)	.25	LM531(8 pin)	.75	75141	.50	DS8832	.50
LM319	1.25	TMS5501	12.00	75150	.50	DS8833	.50
LM324	.25	NE555(8 pin)	.35	75154	.50	MB8861	.50
D3232	1.00	NE558	.75	75160	.50	MB8874	.50
D3242	4.00	LM566	1.00	75161	.50	AY3-8910	2.00
LM3302	1.00	MSM5832	2.75	7524	1.00	AY3-8912	2.00
3341	2.00	MM5837	.50	75322	.50	8T09	.50
MC3346	.70	NE592	.25	75365	.50	8T14	.50
F3357	1.50	6116-100	2.00	75427	.50	8T20	.50
LM339	.45	6116-120	1.75	75450	.50	8T23	.50
MC3401	.50	6116-150	1.25	75451	.50	8T24	.50
MC3403	.50	6116-200	.90	75452	.50	8T26	.50
3441	1.00	6116-250	.85	75453	.50	8T28	.50
3450	1.00	6284-150	5.00	75454	.50	8T37	.50
3453	2.00	MPQ6502	1.00	75461	.50	8T38	.50
LM348	.45	8522	2.00	75462	.50	FD8216	5.00
3486	1.00	6522A	2.50	75497	.50	9312	.80
3487	1.50	6802	2.00	D765	4.00	9314	.60
351	.25	8809	2.00	8017	1.75	9321	.75
LF353	.50	8810	.75	8031	5.00	9328	1.00
DS3612	.50	8821	2.00	8056	4.00	9338	1.00
MB3614	.75	6840	2.00	8080A	.75	93419	3.00
3900	.75	8845	2.00	8086-2	5.00	93422	3.00
3906	1.00	6850	2.00	8123	1.00	93425	3.00
LM393	.35	6852	2.00	8200	2.50	936	2.00
LM393(8 pin)	.50	68A10	1.25	8202A	14.00	93L22	.50
40161	.80	68A21	2.50	8212	1.00	93L24	.75
MC4024	2.00	68A45	2.50	8216	1.00	93L422	3.00
4027-250	.35	68A52	2.50	8220	2.00	93S16	.50
4027-300	.35	68B09	3.00	8224	3.00	93S46	2.00
MC4044	2.00	68B21	3.00	8226	2.00	93S48	.80
4044-200	.80	68B45	3.00	8234	1.50	9401	5.00
4044-300	.50	6N138	.50	8237-4	3.00	9602	.75
40L45-450	.50	MB7052	.50	8237A	3.00	9614	.75
TMS4050	.50	LM710	.40	8238	2.50	9615	.75
TMS4060	.50	LM733	.40	8243	1.50	96L02	1.50
CD4104	1.00	LM741(8 pin)	.30	8250	4.00	96LS02	1.50
4116-120	1.00	LM748(8 pin)	.50	8251	2.00	TMS9900	3.00
4116-150	.75	74C00	.50	8251A	2.00	TMS9901	1.50
4116-200	.50	74F00	.35	8253	2.00	TMS9904	3.00
4116-250	.35	74F04	.35	8253-5	2.00	TMS9914	3.00
41256-150	5.00	74F08	.35	8255A	2.00	TMS9918	20.00
4164-120	1.75	74F157	.45	8255A-5	2.00	TMS9980	10.00
4164-150	.95	74F245	.60	8257	2.00	Z8001	7.50
4164-200	.85	74F32	.35	8257-5	2.00	Z80ACPU	2.00
4164-SPECIAL	.45	74F373	.60	8259A	2.00	Z80ACTC	2.00
MB425	2.00	74F374	.60	8262	1.75	Z80ADMA	4.50
4332-200	2.00	74F374	.60	8266	1.75	Z80APIO	2.00
4416-150	1.50	74F74	.35	D8274	9.00	Z80ASIQ	3.75
4416-SPECIAL	.90	74HC138	.45	N8274	2.50	Z80ASIO/2	4.50
MC4741	.75	74HC244	.60	8279-5	3.50	Z80BCPU	3.00
IH5010	2.50	74HC245	.60	8286	4.00	Z80CPU	1.00
IH5011	1.25	74HC373	.60	8289	4.00	Z80CTC	1.00
CRT-5027	3.00	74HC374	.60	82S16	1.00	Z80PIO	1.00
CRT-5037	5.00	74HCT08	.35	82S62	2.00	Z80SIQ	3.00
		74HCT244	.60				

### OUR POLICY

Delivery: Orders normally shipped within 2 business days. Add \$3 for UPS ground \$5 & under. Add \$4 for UPS blue jett. 2# & under. For each additional lb. pound add \$1. Arizona residents add 6% sales tax.

Payment: Visa, MC, cashiers check, certified check, money order, personal check accepted. Allow 10 days for personal checks to clear. No surcharge on credit card orders. CODs welcome with cash, certified check, cashiers check or money order. Add \$3 COD handling charge.

Pricing: Minimum order 120. 30% discount on orders over 1500. Prices subject to change without notice. All items limited to stock on hand. We reserve the right to limit quantities.

# KRUEGER Technology, Inc.

2219 South 48th Street • Tempe, AZ 85282

800-245-2235

In Arizona 602-438-1570

HOURS: 7 a.m. - 5:30 p.m.

(MOUNTAIN TIME)

Monday Thru Friday



**★ QUALITY PARTS ★ DISCOUNT PRICES ★ FAST SHIPPING!**

# ALL ELECTRONICS CORP.

SEND FOR  
**FREE**  
FALL 1985 CATALOG...  
**48 PAGES!**

**SOLID STATE BUZZER**



Star # SMB-06L  
6 vdc  
TTL compatible  
**\$1.00 each**  
10 for \$9.00

**2K 10 TURN**

MULTI-TURN POT  
SPECTROL  
#MOD 534-7161  
**\$5.00 EACH**



**SLIM LINE COOLING FAN**



Etri # 99XM182 low noise fan. Measures 3 3/4" square x 1" deep. 21 cfm. 23 db. 1700 rpm.  
**SPECIAL PRICE ... \$12.50 each**

**SOUND AND VIDEO MODULATOR FOR T.I. COMPUTER**

T.I. # UM1381-1. Designed for use with T.I. computers. Can be used with video sources. Built-in A/B switch. Channel 3 or 4 selection switch. Operate on 12 vdc. Hook-up diagram included.  
**\$10.00 EACH**



**TV REMOTE CONVERTER**

Enhance the versatility of your video equipment. Converts cable TV stations to channel 2 or 3. Use with standard TV antenna to give your TV remote tuning capability. Converter operates on 115VAC. 36 channel selector with fine tuning on 25 ft. cord. Not a decoder.

**A \$75.00 VALUE - ONLY \$27.50!**



**EDGE CONNECTORS**

ALL ARE 1.56 SPACING.



**22/44 EDGE CONNECTOR**  
PC style \$2.00 each  
10 for \$18.00

**22/44 EDGE CONNECTOR**  
solder lug \$2.50 each  
style

**28/56 EDGE CONNECTOR**  
PC style \$2.50 each  
10 for \$22.00

**36/72 EDGE CONNECTOR**  
PC style \$3.00 each

**43/86 EDGE CONNECTOR**  
PC style \$4.50 each

**TRANSISTORS**

2N706	4 for \$1.00
2N2222A	3 for \$1.00
PN2222A	4 for \$1.00
2N2904	3 for \$1.00
2N2904	3 for \$1.00
2N2905	3 for \$1.00
MJ2955	\$1.50
2N3055	\$1.00
PMD 10K40	\$1.00
TIP 121	75¢
TIP 125	75¢

**TRANSFORMERS**

120 volt primaries



5.6 volts @ 750 ma.	\$3.00
6 volts @ 150 ma.	\$1.25
12 v.c.t. @ 200 ma.	\$2.00
18 volts @ 650 ma.	\$3.50
18 volts @ 1 amp	\$4.50
24 v.c.t. @ 200 ma.	\$2.50
24 v.c.t. @ 400 ma.	\$3.00
28 v.c.t. @ 15 amps	\$20.00
30 v.c.t. @ 2 amps	\$5.00

**WALL TRANSFORMERS**

all plug directly into 120 vac outlet



4 VDC @ 70 ma.	\$2.00
6 VAC @ 500 ma.	\$3.50
6 VDC @ 750 ma.	\$6.50
9 VDC @ 500 ma.	\$5.00
12.5 VAC @ 265 ma.	\$3.00
24 VAC @ 250 ma.	\$3.00
MULTI-VOLTAGE @ 500 ma.	\$7.50
3, 4 1/2, 6, 7 1/2, 9 or 12 VDC	

**MINI-BOX**

Pomona #2104



Heavy-duty black phenolic project box with cover and screws. 2 1/4" x 1 1/2" x 1 1/2".  
**\$1.00 EACH**

**SUB-MINIATURE D TYPE CONNECTORS**

DB-15 PLUG	\$2.75
DB-15 SOCKET	\$4.00
DB-15 HOOD	\$1.50
DB-25 PLUG	\$2.75
DB-25 SOCKET	\$3.50
DB-25 HOOD	\$1.25

**PARALLEL PRINTER CONNECTORS**

Solder style 36 pin used on parallel data cables



**MALE CONNECTOR \$5.50 each**  
**FEMALE CONNECTOR \$5.50 each**

**I.D.C. CONNECTORS**

Will press fit on standard ribbon cable

DB-25 PLUG	\$6.25
DB-25 Socket	\$6.75
36 PIN MALE	\$5.50
36 PIN FEMALE	\$5.50

**TWIST-LOCK CONNECTOR**




Same as Switchcraft #12CL5M. 5 conductor in-line plug and chassis mount jack. Twist-lock style.  
**\$2.50/SET**

**8" P.A. SPEAKER**

C.T.S. Model 8B3079  
8 ohms coil  
3.0 oz. ferrite magnet  
Typical response range: 100 - 10,000 Hz.  
Power rating 15 watts max.  
Drilled to mount line matching transformers.  
**\$5.00 each**

**CASE OF 8 SPEAKERS \$32.00**

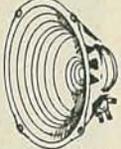

**LINE CORDS**

**TWO WIRE**

6 18/2 SPT-1 flat	3 for \$1.00
6 18/2 SPT-2 flat	
6 16/2 SJT round	\$1.25 each

**THREE WIRE**

6 18/3 flat	\$1.50 each
8 18/3 round	\$2.00 each
8 16/3 round	\$4.00 each

**COMPUTER GRADE CAPACITORS**

2,000 mfd. 200 VDC	\$2.00
1 1/4" DIA. x 5" HIGH	
3,600 mfd. 40 VDC	\$1.00
1 1/4" DIA. x 3 3/4" HIGH	
6,400 mfd. 60 VDC	\$2.50
1 1/4" DIA. x 4 1/4" HIGH	
9,700 mfd. 50 VDC	\$3.00
1 1/4" DIA. x 4 1/2" HIGH	
31,000 mfd. 15 VDC	\$2.50
1 1/4" DIA. x 4" HIGH	
72,000 mfd. 15 VDC	\$3.50
2" DIA. x 4 1/4" HIGH	
185,000 mfd. 6 VDC	\$1.50
2 1/2" DIA. x 4 1/2" HIGH	

**RELAYS**

**5 AMP SOLID STATE**

Heinemann Electric #101-5A-140-5AMP  
CONTROL: 3-32 vdc  
LOAD: 140 vac 5 amp  
SIZE 2" x 1" x 3/4" h  
**\$5.00 each 10 for \$45.00**



**ULTRA-MINIATURE 5 VDC RELAY**

Fujitsu # FBR211NE0005M20  
High sensitivity  
COIL: 120 ohms  
CONTACTS: 1 amp  
Mounts in 14 pin DIP socket  
**\$1.25 each 10 for \$10.00**



**MINIATURE 6 VDC RELAY**

Aromat #RSD-6V  
Super Small  
S.P.D.T. relay  
Gold coil  
contacts rated  
1 amp @ 30 vdc. Highly sensitive.  
TTL direct drive possible. 120 ohm coil.  
Operate from 4 - 3 - 6 vdc.  
COIL: 120 ohms  
1 1/2" x 1 1/2" x 7/16"  
**\$1.50 each 10 for \$13.50**



**13 VDC RELAY**

CONTACTS: S.P.N.C.  
10 amp @ 120 vac  
Energize coil to open contact.  
COIL: 13 vdc 650 ohms  
**SPECIAL PRICE \$1.00 each**



**4PDT RELAY**

14 pin KH style  
3 amp contacts  
USED but fully tested  
\$1.70 each  
Specify coil voltage desired  
Either 24 vdc or 120 vac  
**LARGE QUANTITIES AVAILABLE**  
**SOCKETS FOR KH RELAY 75¢ each**



**SNAP ACTION SWITCH**

Cherry elect. #E-21. N.O. or N.C.  
0.1A contacts. Suitable for alarms and other low energy circuits.  
1 1/4" size  
**45¢ EACH 10 FOR \$4.20**



**"SPECIAL PRICE" DUAL L.E.D. DISPLAYS**



560 high, 7 segment L.E.D. read-outs. Mount in 24 pin DIP sockets.  
MAN-6640 orange, c.c. 75¢ each  
FND-5148 red, c.c. 75¢ each  
DL-527 red, c.a. 75¢ each


**3 1/2" SPEAKER**

8 ohm impedance.  
Full range speaker.  
8 oz magnet  
4" diagonal mounting centers.  
**\$2.50 each 10 for \$20.00**



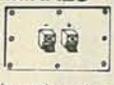**SPRING LEVER TERMINALS**

Two color coded terminals on a sturdy 2 3/4" x 3 3/4" bakelite plate.  
Great for speaker enclosures or power supplies.  
**\$1.00 each 10 for \$9.00**



**MINIATURE TOGGLE SWITCHES**

ALL ARE RATED 5 AMPS @ 125 VAC

<b>S.P.D.T. (on-on)</b> PC style non-threaded bushing 75¢ each 10 for \$7.00	<b>S.P.D.T. (on-on)</b> Solder lug terminals. \$1.00 each 10 for \$9.00 100 for \$80.00	<b>S.P.D.T. (on-off-on)</b> Solder lug terminals. \$1.00 each 10 for \$9.00 100 for \$80.00
---	---	---

<b>S.P.D.T. (on-off-on)</b> PC style non-threaded bushing 75¢ each 10 for \$7.00	<b>S.P.D.T. (on-on)</b> PC lugs threaded bushing \$1.00 each 10 for \$9.00 100 for \$80.00	<b>D.R.D.T. (on-on)</b> Solder lug terminals. \$2.00 each 10 for \$19.00 100 for \$180.00
---	--	---

**STANDARD JUMBO DIFFUSED T 1 1/2**

RED	10 for \$1.50	100 for \$13.00
GREEN	10 for \$2.00	100 for \$17.00
YELLOW	10 for \$2.00	100 for \$17.00

**FLASHER LED**  
5 volt operation red jumbo T 1 1/2 size  
**\$1.00 each**

**BI-POLAR**  
jumbo T 1 1/2 size  
2 for \$1.70

**LED HOLDERS**  
Two piece holder for jumbo LED  
10 for 65¢ 100 for \$5.00

**CLEAR CLIPLITE LED HOLDER**  
Make LED a fancy indicator Clear.  
4 for \$1.00

**D.P.S.T. LIGHTED ROCKER SWITCH**

115 vac lighted rocker, snap mounts in 7/8" x 1 1/4" hole.  
Orange lens. 16 amp contact.  
**\$1.50**



**MINI-PUSH BUTTON**


S.P.S.T. momentary normally open 1/4" bushing  
Red button  
**35¢ each 10 for \$3.00**



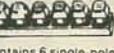**KEY ASSEMBLY**



contains 5 single-pole normally open switches. Measures 3 1/4" long.  
**5 KEY \$1.00 each**



contains 6 single-pole normally open switches. Measures 4 1/4" long.  
**6 KEY \$1.25 each**

**METAL OXIDE VARISTOR**

Popular GE # 130LA10A varistor 1/2" diameter  
**\$1.25 each**



**TI SWITCHING POWER SUPPLY**

Compact, well-regulated switching power supply designed to power Texas Instruments computer equipment

INPUT: 14 - 25 vac @ 1 amp  
OUTPUT: - 12 vdc @ 350 ma  
- 5 vdc @ 1.2 amp  
- 5 vdc @ 200 ma

SIZE: 4 1/4" x 4 1/4" x 1 1/4" high  
**\$5.00 each**



**13.8 VDC REGULATED POWER SUPPLY**

These are solid state, fully regulated 13.8 vdc power supplies. Both feature 100% solid state construction; fuse protection, and L.E.D. power indicator. U.L. listed.

2 amp constant, 4 amp surge	\$18.00 each
3 amp constant, 5 amp surge	\$25.00 each



**D.C. CONVERTER**

Designed to provide a steady, 5 vdc @ 240 ma. from a battery supply of 3.5 to 6.25 volts.  
2 1/8" x 1 1/2" x 1 1/2"  
**\$1.50 each**



**7 CONDUCTOR RIBBON CABLE**

Spectra-strip red marker strip.  
28 ga. stranded wire.  
**\$5.00 per 100 roll**



**ALL ELECTRONICS CORP.**  
LOS ANGELES, CA STORE  
905 S. Vermont Ave.  
213 380-8000

VAN NUYS, CA STORE  
6228 Sepulveda Blvd  
818 997 1806

MAIL ORDERS TO  
P.O. BOX 20406  
Los Angeles, CA 90006

TWX 51010163 ALL ELECTRONIC  
EASYLINK MBX 6288748



TOLL FREE ORDERS ONLY  
1-800-826-5432  
(ORDER ONLY)  
(IN CALIFORNIA 1-800-258-6666)

ALASKA, HAWAII, OR INFORMATION  
(213) 380-8000 NO C.O.D.

QUANTITIES LIMITED  
MINIMUM ORDER \$10.00  
USA \$3.00 SHIPPING

FOREIGN ORDERS:  
INCLUDING SUFFICIENT SHIPPING  
CALIF RES. ADD 6 1/2%

NOVEMBER 1985

4164 49¢ ea. 41256 \$2.95 ea.

**STATIC RAMS**

2101	256x4	(450ns)	1.95
5101	256x4	(450ns)(CMOS)	3.95
2102L-4	1024x1	(450ns)(LP)	.99
2102L-2	1024x1	(250ns)(LP)	1.45
2112	256x4	(450ns)	2.99
2114	1024x4	(450ns)	.99
2114L-4	1024x4	(450ns)(LP)	1.09
2114L-2	1024x4	(200ns)(LP)	1.49
2114L-15	1024x4	(150ns)(LP)	1.95
TMS4044-4	4096x1	(450ns)	1.95
TMM2016-150	2048x8	(150ns)	1.69
TMM2016-100	2048x8	(120ns)	2.49
HM6116-4	2048x8	(200ns)(CMOS)	1.79
HM6116-3	2048x8	(150ns)(CMOS)	1.89
HM6116LP-4	2048x8	(200ns)(CMOS)(LP)	1.89
HM6116LP-3	2048x8	(150ns)(CMOS)(LP)	1.99
HM6116LP-2	2048x8	(120ns)(CMOS)(LP)	2.95
HM6264P-15	8192x8	(150ns)(CMOS)	4.75
HM6264LP-15	8192x8	(150ns)(CMOS)(LP)	4.95
HM6264LP-12	8192x8	(120ns)(CMOS)(LP)	5.95

LP-Low power

**DYNAMIC RAMS**

4116-250	16384x1	(250ns)	.49
4116-200	16384x1	(200ns)	.69
4116-150	16384x1	(150ns)	.89
4116-120	16384x1	(120ns)	1.49
MK4332	32768x1	(200ns)	6.95
4164-200	65536x1	(200ns)(5V)	.49
4164-150	65536x1	(150ns)(5V)	.69
4164-120	65536x1	(120ns)(5V)	1.95
MCM6665	65536x1	(200ns)(5V)	1.95
TMS4164	65536x1	(150ns)(5V)	1.95
4164-REFRESH	65536x1	(150ns)(5V)(REFRESH)	2.95
TMS4416	16384x4	(150ns)(5V)	4.95
41128-150	131072x1	(150ns)(5V)	5.95
41256-200	262144x1	(200ns)(5V)	2.95
41256-150	262144x1	(150ns)(5V)	2.95

5V-Single 5 Volt Supply  
REFRESH-Pin 1 Refresh

★★★★HIGH-TECH★★★★

**NEG V20  $\mu$ PD70108 \$20<sup>95</sup>**

- REPLACES 8088 TO SPEED UP IBM PC 10-40%
- \* HIGH-SPEED ADDRESS CALCULATION IN HARDWARE
  - \* PIN COMPATIBLE WITH 8088
  - \* SUPERSET OF 8086/8088 INSTRUCTION SET
  - \* LOW POWER CMOS

★★★★SPOTLIGHT★★★★

- \* COMPUTER MANAGED INVENTORY - VIRTUALLY NO BACK ORDERS!
- \* VERY COMPETITIVE PRICES
- \* FRIENDLY STAFF
- \* FAST SERVICE - MOST ORDERS SHIPPED WITHIN 24 HOURS!
- \* WE ACCEPT VISA AND MASTERCARD




**EPROMS**

2708	1024x8	(450ns)	3.95
2716-6	2048x8	(650ns)	2.29
2716	2048x8	(450ns)(5V)	2.49
2716-1	2048x8	(350ns)(5V)	3.95
TMS2532	4096x8	(450ns)(5V)	3.95
2732	4096x8	(450ns)(5V)	2.49
2732A-2	4096x8	(250ns)(5V)(21V PGM)	2.69
2732A-2	4096x8	(200ns)(5V)(21V PGM)	4.95
27C64	8192x8	(250ns)(5V)(CMOS)	7.95
2764	8192x8	(450ns)(5V)	2.29
2764-250	8192x8	(250ns)(5V)	2.49
2764-200	8192x8	(200ns)(5V)	4.95
TMS2564	8192x8	(450ns)(5V)	8.95
MCM68766	8192x8	(350ns)(5V)(24 PIN)	17.95
27128	16384x8	(250ns)(5V)	3.49
27C256	32768x8	(250ns)(5V)(CMOS)	15.95
27256	32768x8	(250ns)(5V)	9.95

5V-Single 5 Volt Supply  
21V PGM-Program at 21 Volts

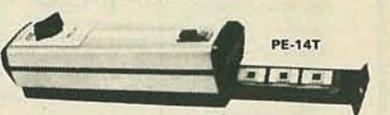**SPECTRONICS CORPORATION EPROM ERASERS**



Model	Timer	Capacity Chip	Intensity (uW/Cm <sup>2</sup> )	Unit Price
PE-14	NO	9	8,000	\$83.00
PE-14T	YES	9	8,000	\$119.00
PE-24T	YES	12	9,600	\$175.00

**8000**

8035	1.95
8039	2.95
8080	2.95
8085	2.95
8087-2	139.95
8087	109.00
8088	7.95
8088-2	9.95
8155	2.95
8155-2	3.95
8748	4.95
8755	19.95
80286	129.95
80287	185.00

**6500 1.0 MHz**

6502	2.79
65C02 (CMOS)	12.95
6507	9.95
6520	1.95
6522	4.95
6526	26.95
6532	6.95
6545	6.95
6551	5.95
6561	19.95
6581	34.95

**2.0 MHz**

6502A	2.95
6520A	2.95
6522A	5.95
6532A	11.95
6545A	7.95
6551A	6.95

**GRT CONTROLLERS**

6845	4.95
68845	8.95
6847	11.95
HD46505SP	6.95
MC1372	2.95
8275	26.95
7220	19.95
CRT5027	12.95
CRT5037	9.95
TMS9918A	19.95

**CRYSTALS**

32.768 KHz	.95
1.0 MHz	2.95
1.8432	2.95
2.0	1.95
2.097152	1.95
3.2768	1.95
3.579545	1.95
4.0	1.95
4.032	1.95
5.0	1.95
5.0688	1.95
6.0	1.95
6.144	1.95
6.5536	1.95
8.0	1.95
10.0	1.95
10.738635	1.95
12.0	1.95
14.31818	1.95
15.0	1.95
16.0	1.95
17.430	1.95
18.0	1.95
18.432	1.95
20.0	1.95
22.1184	1.95
24.0	1.95
32.0	1.95

**74LS00**

74LS00	.16
74LS01	.18
74LS02	.17
74LS03	.18
74LS04	.16
74LS05	.18
74LS08	.18
74LS09	.18
74LS10	.16
74LS11	.22
74LS12	.22
74LS13	.26
74LS14	.39
74LS15	.26
74LS20	.17
74LS21	.22
74LS22	.22
74LS27	.23
74LS28	.26
74LS30	.17
74LS32	.18
74LS33	.28
74LS37	.26
74LS38	.26
74LS42	.39
74LS47	.59
74LS48	.89
74LS51	.17
74LS73	.29
74LS74	.24
74LS75	.29
74LS76	.29
74LS83	.49
74LS85	.49
74LS86	.22
74LS90	.39
74LS92	.49
74LS93	.39
74LS95	.49
74LS107	.34
74LS112	.29
74LS122	.45
74LS123	.49
74LS124	2.75
74LS125	.39
74LS126	.39
74LS132	.39
74LS133	.49
74LS136	.39
74LS138	.39
74LS139	.39
74LS145	.99
74LS147	.99
74LS148	.99
74LS151	.39
74LS153	.39
74LS154	1.49
74LS155	.59
74LS156	.49
74LS157	.35
74LS158	.29
74LS160	.29
25LS221	2.80
25LS269	2.80
26LS31	1.95
26LS32	1.95

**HIGH SPEED CMOS**

A new family of high speed CMOS logic featuring the speed of low power Schottky (8ns typical gate propagation delay), combined with the advantages of CMOS: very low power consumption, superior noise immunity, and improved output drive.

**74HC00**

74HC: Operate at CMOS logic levels and are ideal for new, all-CMOS designs.

74HC00	.59	74HC148	1.19
74HC02	.59	74HC151	.89
74HC04	.59	74HC154	2.49
74HC08	.59	74HC157	.89
74HC10	.59	74HC158	.95
74HC14	.79	74HC163	1.15
74HC20	.59	74HC175	.99
74HC27	.59	74HC240	1.89
74HC30	.59	74HC244	1.89
74HC32	.69	74HC245	1.89
74HC51	.59	74HC257	.85
74HC74	.75	74HC259	1.39
74HC85	.35	74HC273	1.89
74HC86	.69	74HC299	4.99
74HC93	1.19	74HC368	.99
74HC107	.79	74HC373	2.29
74HC109	.79	74HC374	2.29
74HC112	.79	74HC390	1.39
74HC125	1.19	74HC393	2.39
74HC132	1.19	74HC4017	1.99
74HC133	.69	74HC4020	1.39
74HC138	.99	74HC4049	.89
74HC139	.99	74HC4050	.89

**74HC200**

74HC: Direct, drop-in replacements for LS TTL and can be intermixed with 74LS in the same circuit.

74HC200	.69	74HC166	3.05
74HC202	.69	74HC174	1.09
74HC204	.69	74HC193	1.39
74HC208	.69	74HC194	1.19
74HC210	.69	74HC240	2.39
74HC211	.69	74HC241	2.19
74HC227	.69	74HC244	2.19
74HC230	.69	74HC245	2.19
74HC232	.79	74HC257	.99
74HC274	.85	74HC259	1.59
74HC275	.95	74HC273	2.09
74HC278	1.15	74HC367	1.09
74HC279	1.15	74HC373	2.49
74HC284	2.99	74HC374	2.49
74HC285	.99	74HC393	1.59
74HC286	.99	74HC4017	2.19
74HC287	1.29	74HC4040	1.59
74HC288	1.39	74HC4060	1.49

**8200**

8203	34.95
8205	3.29
8212	1.49
8216	1.49
8224	2.25
8237	4.95
8237-5	6.95
8250	6.95
8251	1.95
8251A	2.49
8253	1.95
8253-5	2.49
8255	1.95
8255-5	2.49
8259	2.49
8259-5	2.95
8272	4.95
8279	2.95
8279-5	3.49
8282	3.95
8284	2.95
8286	3.95
8288	4.95

**3.0 MHz**

6502B	6.95
-------	------

**6800 1.0 MHz**

6800	1.95
6802	4.95
6803	9.95
6809	5.95
6809E	5.95
6810	1.95
6820	2.95
6821	1.95
6840	6.95
6843	19.95
6844	12.95
6845	4.95
6847	11.95
6850	1.95
6883	22.95

**DISK CONTROLLERS**

1771	4.95
1781	9.95
1793	9.95
1795	12.95
1797	12.95
2791	19.95
2793	19.95
2797	29.95
6843	19.95
8272	4.95

**BIT RATE GENERATORS**

MC14411	9.95
BR1941	4.95
4702	9.95
COM8116	8.95
MMS307	4.95

**CRYSTAL OSCILLATORS**

1.0MHz	5.95
1.8432	5.95
2.0	5.95
2.4576	5.95
2.5	4.95
4.0	4.95
5.0688	4.95
6.0	4.95
6.144	4.95
8.0	4.95
10.0	4.95
12.0	4.95
12.480	4.95
15.0	4.95
16.0	4.95
18.432	4.95
20.0	4.95
24.0	4.95

**74LS00**

74LS165	.65
74LS166	.95
74LS169	.95
74LS173	.49
74LS174	.39
74LS175	.39
74LS191	.49
74LS192	.69
74LS193	.69
74LS194	.69
74LS195	.69
74LS196	.69
74LS197	.59
74LS221	.59
74LS240	.69
74LS241	.69
74LS242	.69
74LS243	.69
74LS244	.69
74LS245	.79
74LS251	.49
74LS253	.49
74LS256	1.79
74LS257	.39
74LS258	.39
74LS259	1.29
74LS260	.49
74LS266	.39
74LS273	.79
74LS279	.39
74LS280	1.98
74LS283	.59
74LS290	.89
74LS291	.89
74LS299	1.49
74LS322	3.95
74LS323	2.49
74LS364	1.95
74LS365	.39
74LS367	.39
74LS368	.39
74LS373	.79
74LS374	.79
74LS375	.95
74LS377	.79
74LS378	1.18
74LS390	1.19
74LS393	.79
74LS624	

## CMOS

4001	.19	14419	4.95
4011	.19	14433	14.95
4012	.25	4503	.49
4013	.35	4511	.69
4015	.29	4516	.79
4016	.29	4518	.85
4017	.49	4522	.79
4018	.69	4526	.79
4020	.59	4527	1.95
4021	.69	4528	.79
4024	.49	4529	2.95
4025	.25	4532	1.95
4027	.39	4538	.95
4028	.65	4541	1.29
4035	.69	4553	5.79
4040	.69	4585	.75
4041	.75	4702	12.95
4042	.59	74C00	.29
4043	.85	74C14	.59
4044	.69	74C74	.59
4045	1.39	74C83	1.95
4046	.69	74C85	1.49
4047	.69	74C95	.99
4049	.29	74C150	5.75
4050	.29	74C151	2.25
4051	.69	74C161	.99
4052	.69	74C163	.99
4053	.69	74C164	1.39
4056	2.19	74C192	1.49
4060	.69	74C193	1.49
4066	.29	74C221	1.75
4069	.19	74C240	1.89
4076	.59	74C244	1.89
4077	.29	74C374	1.99
4081	.22	74C905	10.95
4085	.79	74C911	8.95
4086	.89	74C917	8.95
4093	.49	74C922	4.49
4094	2.49	74C923	4.95
14411	9.95	74C926	2.95
14412	6.95	80C97	.95

## 7400/9000

7400	.19	74147	2.49
7402	.19	74148	1.20
7404	.19	74150	1.35
7406	.29	74151	.55
7407	.29	74153	.69
7408	.24	74154	1.49
7410	.19	74155	.75
7411	.25	74157	.55
7414	.49	74159	1.65
7416	.25	74161	.69
7417	.25	74163	.69
7420	.19	74164	.85
7423	.29	74166	1.00
7430	.19	74166	1.00
7432	.29	74175	.89
7438	.29	74177	.75
7442	.49	74178	1.15
7445	.69	74181	2.25
7447	.89	74182	.75
7470	.35	74184	2.00
7473	.34	74191	1.15
7474	.33	74192	.79
7475	.45	74194	.85
7476	.35	74196	.79
7483	.50	74197	.75
7485	.59	74199	1.35
7486	.35	74221	1.35
7489	2.15	74246	1.35
7490	.39	74247	1.25
7492	.50	74248	1.85
7493	.35	74249	1.95
7495	.55	74251	.75
7497	2.75	74265	1.35
74100	2.29	74273	1.95
74121	.29	74278	3.11
74123	.49	74367	.65
74125	.45	74368	.65
74141	.65	9368	3.95
74143	5.95	9602	1.50
74144	2.95	9637	2.95
74145	.60	96502	1.95

## 74S00

74500	.29	74S163	1.29
74502	.29	74S168	3.95
74503	.29	74S174	.79
74504	.29	74S175	.79
74505	.29	74S188	1.95
74508	.35	74S189	1.95
74510	.29	74S195	1.49
74515	.35	74S196	1.49
74530	.29	74S197	1.49
74532	.35	74S226	3.99
74537	.69	74S240	1.49
74538	.69	74S241	1.49
74574	.49	74S244	1.49
74585	.95	74S257	.79
74586	.35	74S253	.79
745112	.50	74S258	.95
74S124	2.75	74S280	1.95
74S138	.79	74S287	1.69
74S140	.55	74S288	.59
74S151	.79	74S289	2.95
74S153	.79	74S373	1.69
74S157	.79	74S374	1.69
74S158	.95	74S471	4.95
74S161	1.29	74S571	2.95

## VOLTAGE REGULATORS

TO-220 CASE		
7805T	.49	7905T .59
7808T	.49	7908T .59
7812T	.49	7912T .59
7815T	.49	7915T .59
TO-3 CASE		
7805K	1.39	7905K 1.49
7812K	1.39	7912K 1.49
TO-92 CASE		
78L05	.49	79L05 .69
78L12	.49	79L12 .69

## OTHER VOLTAGE REGS

LM323K	5V 3A	TO-3	4.79
LM338K	A4.5A	TO-3	3.95
78H05K	5V 5A	TO-3	7.95
78H12K	12V 5A	TO-3	8.95
78P05K	5V 10A	TO-3	14.95

## LINEAR

TL066	.99	LM733	.98
TL071	.69	LM741	.29
TL072	1.09	LM747	.69
TL074	1.95	LM748	.59
TL081	.59	MC1330	1.69
TL082	.99	MC1350	1.19
TL084	1.49	MC1372	6.95
LM301	.34	LM1414	1.59
LM309K	1.25	LM1458	.49
LM311	.59	LM1488	.49
LM311H	.89	LM1489	.49
LM317K	3.49	LM1496	.85
LM317T	.95	LM1812	8.25
LM318	1.49	LM1889	1.95
LM319	1.25	ULN2003	.79
LM320	see 7900	XR2206	3.75
LM322	1.65	XR2211	2.95
LM323K	4.79	XR2240	1.95
LM324	4.49	MPO2907	1.95
LM331	3.95	LM2917	1.95
LM334	1.19	CA3046	.89
LM335	1.40	CA3081	.99
LM336	1.75	CA3082	.99
LM337K	3.95	CA3086	.80
LM338K	3.95	CA3089	1.95
LM339	.59	CA3130E	.99
LM340	see 7800	CA3146	1.25
LM350T	4.60	CA3160	1.19
LF353	.59	MC3470	1.95
LF356	.99	MC3480	8.95
F357	.99	MC3487	2.95
LM358	.59	LM3900	.49
LM380	.89	LM3909	.98
LM383	1.95	LM3911	2.25
LM386	.89	LM3914	2.39
LM393	.45	MC4024	3.49
LM394H	4.60	MC40	3.99
TL494	4.20	RC4136	1.25
TL497	3.25	RC4558	.69
NE555	.29	LM13600	1.49
NE556	.49	75107	1.49
NE558	1.29	75110	1.25
NE564	1.95	75150	1.95
LM565	.95	75154	1.95
LM566	1.49	75188	1.25
LM567	.79	75189	1.25
NE570	2.95	75451	.39
NE590	2.50	75452	.39
NE592	.98	75453	.39
LM710	.75	75477	1.29
LM723	.49	75492	.79
H-TO-5 CAN, K-TO-3, T-TO-220			

## DATA ACQ INTERFACE

ADC0800	15.55	8T26	1.29
ADC0804	3.49	8T28	1.29
ADC0809	4.49	8T96	.89
ADC0816	14.95	8T98	.89
ADC0817	9.95	8T97	.59
ADC0831	8.95	8T98	.89
DAC0800	4.49	DM8131	2.95
DAC0806	1.95	DP8304	2.29
DAC0808	2.95	DS8833	2.25
DAC1020	8.25	DS8835	1.99
DAC1022	5.95	DS8836	.99
MC1408L8	2.95	DS8837	1.65

## IC SOCKETS

1-99			100
8 PIN ST	.13	.11	
14 PIN ST	.15	.12	
16 PIN ST	.17	.13	
18 PIN ST	.20	.18	
20 PIN ST	.29	.27	
22 PIN ST	.30	.27	
24 PIN ST	.30	.27	
28 PIN ST	.40	.32	
40 PIN ST	.49	.39	
64 PIN ST	4.25	CALL	
ST-SOLDERTAIL			
8 PIN WW	.59	.49	
14 PIN WW	.69	.52	
16 PIN WW	.69	.58	
18 PIN WW	.99	.90	
20 PIN WW	1.09	.98	
22 PIN WW	1.39	1.12	
24 PIN WW	1.49	1.35	
28 PIN WW	1.69	1.49	
40 PIN WW	1.99	1.80	
WW-WIREWRAP			
16 PIN ZIF	4.95	CALL	
24 PIN ZIF	5.95	CALL	
28 PIN ZIF	6.95	CALL	
40 PIN ZIF	9.95	CALL	
ZIF-TEXT TOOL (ZERO INSERTION FORCE)			
LM723	.49	75492	.79

## EDGE CARD CONNECTORS

100 PIN ST	S-100	.125	3.95
100 PIN WW	S-100	.125	4.95
62 PIN ST	IBM PC	.100	1.95
50 PIN ST	APPLE	.100	2.95
44 PIN ST	STD	.156	1.95
44 PIN WW	STD	.156	4.95

## 36 PIN CENTRONICS

MALE		FEMALE	
IDCEN36	RIBBON CABLE		6.95
CEN36	SOLDER CUP		4.95
CEN36PC	RT ANGLE PC MOUNT		4.95
IDCEN36/F	RIBBON CABLE		7.95


## INTERSIL

ICL7106	9.95
ICL7107	12.95
ICL7660	2.95
ICL8038	4.95
ICM7207A	5.95
ICM7208	15.95

## DIP CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS								
		8	14	16	18	20	22	24	28	40
HIGH RELIABILITY TOOLED ST IC SOCKETS	AUGATxxST	.62	.79	.89	1.09	1.29	1.39	1.49	1.69	2.49
HIGH RELIABILITY TOOLED WW IC SOCKETS	AUGATxxWW	1.30	1.80	2.10	2.40	2.50	2.90	3.15	3.70	5.40
COMPONENT CARRIES (DIP HEADERS)	ICCx	.49	.59	.69	.99	.99	.99	.99	1.09	1.49
RIBBON CABLE DIP PLUGS (IDC)	IDPx	---	.95	.95	---	---	---	---	1.75	2.95

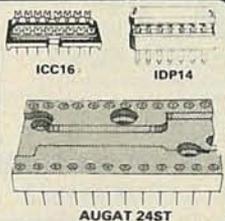FOR ORDERING INSTRUCTIONS SEE D-SUBMINIATURE BELOW



## DIODES/OPTO/TRANSISTORS


1N751	.25	4N26	.69
1N759	.25	4N27	.69
1N4148	25/1.00	4N28	.69
1N4004	10/1.00	4N33	.89
1N5402	.25	4N37	1.19
KBPO4	.55	MCT-2	.59
RL8A	.95	MCT-6	1.29
MDA990-2	.35	TIL-111	.99
N2222	.25	2N3906	.10
PN2222	.10	2N4401	.25
2N2905	.50	2N4402	.25
2N2907	.25	2N4403	.25
2N3055	.79	2N6045	1.75
2N3904	.10	TIP31	.49

## D-SUBMINIATURE

DESCRIPTION	ORDER BY	CONTACTS						
		9	15	19	25	37	50	
SOLDER CUP	MALE	DBxxP	.82	.90	1.25	1.25	1.80	3.48
	FEMALE	DBxxS	.95	1.15	1.50	1.50	2.35	4.32
RIGHT ANGLE PC SOLDER	MALE	DBxxPR	1.20	1.49	---	1.95	2.65	---
	FEMALE	DBxxSR	1.25	1.55	---	2.00	2.79	---
WIRE WRAP	MALE	DBxxPWW	1.69	2.56	---	3.89	5.60	---
	FEMALE	DBxxSww	2.76	4.27	---	6.84	9.95	---
IDC RIBBON CABLE	MALE	IDBxxP	2.70	2.95	---	3.98	5.70	---
	FEMALE	IDBxxS	2.92	3.20	---	4.33	6.76	---
HOODS	METAL	MHOODxx	1.25	1.25	1.30	1.30	---	---
	GREY	HOODxx	.65	.65	---	.65	.75	.95

ORDERING INSTRUCTIONS: INSERT THE NUMBER OF CONTACTS IN THE POSITION MARKED "xx" OF THE "ORDER BY" PART NUMBER LISTED.  
EXAMPLE: A 15 PIN RIGHT ANGLE MALE PC SOLDER WOULD BE DB15PR.

MOUNTING HARDWARE \$1.00

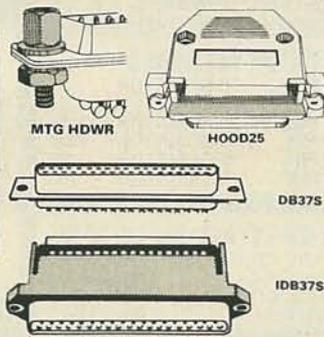

ORDER TOLL FREE

800-538-5000

800-662-6279 (CA)

**WIRE WRAP PROTOTYPE CARDS**  
FR-4 EPOXY GLASS LAMINATE  
WITH GOLD-PLATED EDGE-CARD FINGERS



IBM-PR2

**IBM**

BOTH CARDS HAVE SILK SCREENED LEGENDS  
AND INCLUDES MOUNTING BRACKET

IBM-PR1 WITH -5V AND GROUND PLANE . . . \$27.95  
IBM-PR2 AS ABOVE WITH DECODING LAYOUT \$29.95

**S-100**

P100-1 BARE - NO FOIL PADS . . . . . \$15.15  
P100-2 HORIZONTAL BUS . . . . . \$21.80  
P100-3 VERTICAL BUS . . . . . \$21.80  
P100-4 SINGLE FOIL PADS PER HOLE . . . . . \$22.75

**APPLE**

P500-1 BARE - NO FOIL PADS . . . . . \$15.15  
P500-3 HORIZONTAL BUS . . . . . \$22.75  
P500-4 SINGLE FOIL PADS PER HOLE . . . . . \$21.80  
7060-45 FOR APPLE IIe AUX SLOT . . . . . \$30.00

**PAGE WIRE WRAP WIRE**  
PRECUT ASSORTMENT  
IN ASSORTED COLORS \$27.50

100ea: 5.5", 6.0", 6.5", 7.0"  
250ea: 2.5", 4.5", 5.0"  
500ea: 3.0", 3.5", 4.0"

**SPOOLS**

100 feet \$4.30 250 feet \$7.25  
500 feet \$13.25 1000 feet \$21.95

Please specify color:  
Blue, Black, Yellow or Red

**EMI FILTER**

\$4.95

• MANUFACTURED BY CORCOM  
• LOW COST  
• FITS LC-HP BELOW  
• 6 AMP 120/240 VOLT



**6 FOOT LINE CORDS**

LC-2 2 CONDUCTOR . . . . . .39  
LC-3 2 CONDUCTOR . . . . . .99  
LC-HP 3 CONDUCTOR W/ STD FEMALE SOCKET 1.49

**MUFFIN FANS**

3.15" SQ ROTRON 14.95  
3.63" SQ ETRI 14.95  
3.18" SQ MASUSHITA 16.95

**SWITCHING POWER SUPPLIES**

**PS-IBM \$99.95**

• FOR IBM PC-XT COMPATIBLE  
• 130 WATTS  
• +5V @ 15A, +12V @ 4.2A  
• -5V @ .5A, -12V @ .5A  
• ONE YEAR WARRANTY



PS-IBM/150

**PS-IBM-150 \$129.95**

• 150 WATTS  
• FOR IBM PC-XT COMPATIBLE  
• +12 @ 5.2A, +5 @ 16A  
• -12 @ .5A, -5 @ .5A  
• ONE YEAR WARRANTY



PS-100/130

**PS-100 \$89.95**

• 100 WATTS  
• SWITCH ON REAR  
• FOR USE IN OTHER IBM TYPE MACHINES  
• 90 DAY WARRANTY



PS-A

**PS-130 \$99.95**


• 130 WATTS  
• SWITCH ON REAR  
• FOR USE IN OTHER IBM TYPE MACHINES  
• 90 DAY WARRANTY



PS-3

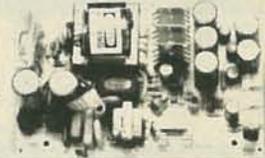**PS-A \$49.95**


• USE TO POWER APPLE TYPE SYSTEMS  
• +5V @ 4A, +12V @ 2.5A  
• -5V @ .5A, -12V @ .5A  
• APPLE POWER CONNECTOR



PS-ASTEC

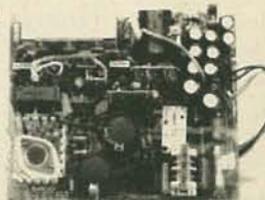**PS-3 \$39.95**

• AS USED IN APPLE III  
• +5V @ 4A, +12V @ 2.5A  
• -5V @ .25A, -12V @ .30A,  
• 15.5" x 4.5" x 2.0", .884 LBS.



PS-TDK

**PS-ASTEC \$19.95**

• CAN POWER TWO 5 1/4" FDDS  
• +5V @ 2.5A, +12V @ 2A  
• -12V @ .1A  
• +5V @ 5A IF +12V IS NOT USED  
• 6.3" x 4.0" x 1.9", 1 LB.

**PS-TDK \$29.95**


• +5V @ 4A, +12V @ 2A  
• +12V @ 2.8A, -12V @ .30A  
• 6.2" x 7.4" x 1.7", 1.6 LBS.

**SOCKET-WRAP I.D.™**

• SLIPS OVER WIRE WRAP PINS  
• IDENTIFIES PIN NUMBERS ON WRAP SIDE OF BOARD  
• CAN WRITE ON PLASTIC, SUCH AS IC #

PINS	PART#	PCK. OF	PRICE
8	IDWRAP 08	10	1.95
14	IDWRAP 14	10	1.95
16	IDWRAP 16	10	1.95
18	IDWRAP 18	5	1.95
20	IDWRAP 20	5	1.95
22	IDWRAP 22	5	1.95
24	IDWRAP 24	5	1.95
28	IDWRAP 28	5	1.95
40	IDWRAP 40	5	1.95

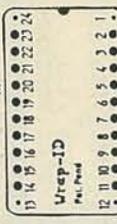PLEASE ORDER BY NUMBER OF PACKAGES (PCK. OF)



ID WRAP 24

**FRAME STYLE TRANSFORMERS**

12.6V AC CT 2 AMP 5.95  
12.6V AC CT 4 AMP 7.95  
12.6V AC CT 8 AMP 10.95  
25.2V AC CT 2 AMP 7.95

**25 PIN D-SUB GENDER CHANGERS**

\$7.95



**CAPACITORS**

**TANTALUM**

1.0µf	15V	.35	.47µf	35V	.45
6.8	15V	.70	1.0	35V	.45
10	15V	.80	2.2	35V	.65
22	15V	1.35	4.7	35V	.85
22	35V	.40	10	35V	1.00

**DISC**

10pf	50V	.05	680	50V	.05
22	50V	.05	.001µf	50V	.05
27	50V	.05	.0022	50V	.05
33	50V	.05	.005	50V	.05
47	50V	.05	.01	50V	.07
68	50V	.05	.02	50V	.07
100	50V	.05	.05	50V	.07
220	50V	.05	.1	12V	.10
*60	50V	.05	.1	50V	.12

**MONOLITHIC**

.01µf	50V	.14	.1µf	50V	.18
.047µf	50V	.15	.47µf	50V	.25

**ELECTROLYTIC**

RADIAL		AXIAL			
1µf	25V	.14	1µf	50V	.14
2.2	35V	.15	10	50V	.16
4.7	50V	.15	22	16V	.14
10	50V	.15	47	50V	.20
47	35V	.18	100	35V	.25
100	16V	.18	220	25V	.30
220	35V	.20	470	50V	.50
470	25V	.30	1000	16V	.60
2200	16V	.70	2200	16V	.70
4700	25V	1.45	4700	16V	1.25
COMPUTER GRADE	44,000µf	30V	3.95		

**DATARASE EPROM ERASER**

\$34.95

• ERASES TWO EPROMS IN 10 MINUTES  
• COMPACT-NO DRAWER  
• THIN METAL SHUTTER PREVENTS UV LIGHT FROM ESCAPING



**1/4 WATT RESISTORS**

5% CARBON FILM ALL STANDARD VALUES  
FROM 1 OHM TO 10 MEG. OHM  
10 PCS same value .05 100 PCS same value .02  
50 PCS same value .025 1000 PCS same value .015

**RESISTOR NETWORKS**

SIP	10 PIN	9 RESISTOR	.69
SIP	8 PIN	7 RESISTOR	.59
DIP	16 PIN	8 RESISTOR	1.09
DIP	16 PIN	15 RESISTOR	1.09
DIP	14 PIN	7 RESISTOR	.99
DIP	14 PIN	13 RESISTOR	.99

**SPECIALS ON BYPASS CAPACITORS**

.01 µf CERAMIC DISC 100/\$5.00  
.01 µf MONOLITHIC 100/\$10.00  
.1 µf CERAMIC DISC 100/\$6.50  
.1 µf MONOLITHIC 100/\$12.50

**NEW BOOKS BY STEVE CIARCIA**

BUILD YOUR OWN Z80 COMPUTER \$19.95  
CIRCUIT CELLAR VOL 1 \$17.95  
CIRCUIT CELLAR VOL 2 \$18.95  
CIRCUIT CELLAR VOL 3 \$18.95  
CIRCUIT CELLAR VOL 4 \$18.95

**MICROCOMPUTER HARDWARE HANDBOOK FROM ELCOMP**

\$14.95  
OVER 800 PAGES OF DATA SHEETS ON THE MOST COMMONLY USED ICs. INCLUDES TTL, CMOS, 74LS00, MEMORY, CPUs, MPU SUPPORT, AND MUCH MORE!

**IC MASTER \$79.95 THE INDUSTRY STANDARD**

A complete listing of currently manufactured ICs from over 225 manufacturers. It includes a part # index, an alternative source guide as well as specification and application notes on thousands of devices.




**WISH SOLDERLESS BREADBOARDS**

PART NUMBER	DIMENSIONS	DISTRIBUTION STRIP(S)	TIE POINTS	TERMINAL STRIP(S)	TIE POINTS	BINDING POSTS	PRICE
WBU-D	.38 x 6.50"	1	100	---	---	---	2.95
WBU-T	1.38 x 6.50"	---	---	1	630	---	6.95
WBU-204-3	3.94 x 8.45"	1	100	2	1260	2	17.95
WBU-204	5.13 x 8.45"	4	400	2	1260	3	24.95
WBU-206	6.88 x 9.06"	5	500	3	1890	4	29.95
WBU-208	8.25 x 9.45"	7	700	4	2520	4	39.95

**RELAYS**


VOLTAGE	CONTACTS	FITS	PRICE
5 VDC	SPST REED	DIP	3.95
12 VDC	DPDT 2 AMP	DIP	3.95
6 VDC	6PDT 3 AMP	RELAY SOC	2.95
12 VDC	4PDT 3 AMP	RELAY SOC	3.95
24 VDC	DPDT 3 AMP	RELAY SOC	3.95
48 VDC	4PDT 3 AMP	RELAY SOC	3.95
120 VAC	4PDT 3 AMP	RELAY SOC	3.95

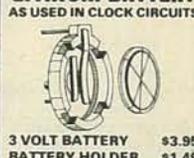**LITHIUM BATTERY AS USED IN CLOCK CIRCUITS**



3 VOLT BATTERY \$3.95  
BATTERY HOLDER \$1.49

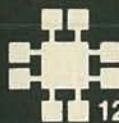VISIT OUR RETAIL STORE LOCATED AT 1256 SOUTH BASCOM AVENUE IN SAN JOSE



**JDR Microdevices**

1224 S. Bascom Avenue, San Jose, CA 95128

800-538-5000 • 800-662-6279 (CA) • (408) 995-5430

FAX (408) 275-8415 • Telex 171-110

ALL MERCHANDISE 100% GUARANTEED

HOURS: M-W-F, 9-5

TU-TH, 9-9

SAT, 10-3

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING

TERMS: Minimum order \$10.00. For shipping and handling include \$2.50 for UPS Ground and \$3.50 for UPS Air. Orders over 1 lb. and foreign orders may require additional shipping charges - please contact our sales department for the amount. CA residents must include applicable sales tax. All merchandise is warranted for 90 days unless otherwise stated. Prices are subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturer. All merchandise subject to prior sale.

© COPYRIGHT 1985 JDR MICRODEVICES


## PRINTER BUFFERS

- FREE'S COMPUTER FOR OTHER TASKS WHILE PRINTING LONG DOCUMENTS.
- STANDALONE DESIGN - WORKS WITH ANY COMPUTER OR PRINTER.
- ALL MODELS FEATURE PRINT PAUSE, MEMORY CHECK AND GRAPHICS CAPABILITY.

**SP120P PARALLEL \$139.95**  
• 64K UPGRADABLE TO 256K  
• LED INDICATOR SHOWS VOLUME OF DATA IN BUFFER

**SP120S RS232 SERIAL \$159.95**  
• 64K UPGRADABLE TO 256K  
• SIX SELECTABLE BAUD RATES FROM 600B - 19,200B

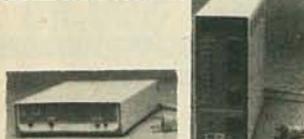**SP110 PARALLEL \$249.95**  
• 64K UPGRADABLE TO 512K  
• SPOOLS OUTPUT OF UP TO THREE COMPUTERS  
• LED BARGRAPH DISPLAYS AMOUNT OF DATA IN BUFFER  
• RESET FUNCTION CLEARS DATA IN BUFFER  
• REPEAT FUNCTION CAN PRODUCE MULTIPLE COPIES OF A DOCUMENT



SP120 SP110

## 3-WAY SWITCH BOXES

- SERIAL OR PARALLEL
- CONNECTS 3 PRINTERS TO 1 COMPUTER OR 3 COMPUTERS TO 1 PRINTER
- ALL LINES SWITCHED
- HIGH QUALITY ROTARY SWITCH MOUNTED ON PCB
- GOLD CONTACTS
- STURDY METAL ENCLOSURE



**SWITCH-3P CENTRONICS PARALLEL 99.95**  
**SWITCH-3S RS232 SERIAL 99.95**

## IBM PRINTER CABLE

- DB25 TO CENTRONICS
- SHIELDED CABLE

**\$9.95**

## JOYSTICKS



**\$7.95**

**\$4.95**

## NASHUA DISKETTE SPECIALS

**5 1/4" SOFT SECTOR DS/DD WITH HUB RINGS**  
**\$9.90 BOX OF 10**    **89¢ea BULK QTY 50**    **79¢ea BULK QTY 250**

NASHUA DISKETTES WERE JUDGED TO HAVE THE HIGHEST POLISH AND RECORDED AMPLITUDE OF ANY DISKETTES TESTED. SEE "COMPARING FLOPPY DISKS", BYTE 9-84

## DISKETTE FILE



**\$8.95**

HOLDS 70 5 1/4" DISKETTES

## FLOPPY DISK DRIVES

**TEAC**  
**FD-55B 1/2 HEIGHT DS/DD \$89.95**  
**FD-55F 1/2 HEIGHT DS/QUAD \$99.95**




TEAC FD-55B

**SHUGART**  
**SA460 5 1/4" (80 TRACK) DS/QUAD \$199.95**

**TANDON**  
**TM100-2 5 1/4" (FOR IBM) DS/DD \$99.95**

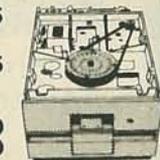**MPI**  
**MPI-B52 5 1/4" (FOR IBM) DS/DD \$89.95**



TANDON TM100-2

## SIEMENS 8" DISK DRIVES

**FD100-8 SS/DD SA801 EQUIV. \$119.00**  
**FD200-8 DS/DD SA851 EQUIV. \$159.00**  
**JFORMAT-2 SOFTWARE \$49.95**  
SUPPORT FOR QUAD DENSITY DRIVES FROM TALL TREE SYSTEMS

## DISK DRIVE CABINETS

### 5 1/4" DRIVE ENCLOSURES

**CAB-APPLE APPLE TYPE DRIVE CABINET WITHOUT POWER SUPPLY \$24.95**  
**CAB-1FH5 FULL HEIGHT 5 1/4" BEIGE DRIVE CABINET WITH POWER SUPPLY \$69.95**  
**CAB-2SV5 DUAL SLIMLINE 5 1/4" CABINET WITH POWER SUPPLY - VERTICAL MOUNT \$49.95**

### 8 INCH DRIVE ENCLOSURES BY JTR

**CAB-2SV8 DUAL SLIMLINE 8" DRIVE CABINET WITH POWER SUPPLY - VERTICAL MOUNT \$209.95**  
**CAB-2FH8 DUAL FULL HEIGHT 8" DRIVE CABINET WITH POWER SUPPLY - HORIZONTAL \$219.95**



CAB-2SV5



CAB-2FH8

## DISKETTES

### NASHUA 5 1/4"

**N-MD2D DS/DD SOFT SECTOR \$9.90**  
**N-MD2F DS/QUAD SOFT SECTOR \$34.95**  
**N-MD2H DS/HIGH DENSITY FOR AT \$49.95**

### NASHUA 8"

**N-FD1 SS/DD SOFT SECTOR \$27.95**  
**N-FD2D DS/DD SOFT SECTOR \$34.95**

### NASHUA 3.5"

**N-3.5SS 3.5" SS/DD FOR MACINTOSH \$32.95**

### VERBATIM 5 1/4"

**V-MD1D SS/DD SOFT SECTOR \$23.95**  
**V-MD2D DS/DD SOFT SECTOR \$29.95**  
**V-MD110D SS/DD 10 SECTOR HARD \$23.95**

## IBM STYLE COMPUTER CASE

ATTRACTIVE STEEL CASE, WITH HINGED LID, FITS POPULAR PC/XT COMPATIBLE MOTHER-BOARDS.

- SWITCH CUT-OUT ON SIDE FOR PC/XT STYLE POWER SUPPLY
- CUT-OUT FOR 8 EXPANSION SLOTS
- ALL HARDWARE INCLUDED


**ONLY \$59.95**



## IBM COMPATIBLE KEYBOARDS

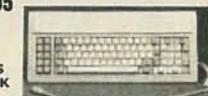**DKM-2000 \$79.95**

- FULLY IBM COMPATIBLE
- 83 KEY WITH CAPACITANCE TYPE SWITCHES
- LED STATUS INDICATORS FOR CAPS, NUMBER LOCK
- AUDIBLE CLICK



**KB-5151 \$99.95**

- ENHANCED IBM COMPATIBLE
- SEPARATE CURSOR AND NUMERIC KEYPADS
- CAPS LOCK & NUMBER LOCK INDICATORS
- IMPROVED KEYBOARD LAYOUT



## EXTENDER CARDS

**IBM-PC \$45.00**  
**IBM-AT \$68.00**  
**APPLE II \$45.00**  
**APPLE IIe \$45.00**  
**MULTIBUS \$86.00**

## POWER STRIPS

• UL APPROVED  
• 15A CIRCUIT BREAKER  
**\$12.95**



## KEYBOARD-AP

- REPLACEMENT FOR APPLE II KEYBOARD
- CAPS LOCK KEY
- AUTO-REPEAT
- ONE KEY ENTRY OF BASIC OR CPM COMMANDS

**\$49.95**



## CASE WITH KEYBOARD

FOR APPLE MOTHER-BOARD MODEL KB-1000

- USER DEFINED FUNCTION KEYS
- NUMERIC KEYPAD WITH CURSOR CONTROL
- CAPS LOCK
- AUTO-REPEAT


**ONLY \$79.95**



## HIGH QUALITY TEST EQUIPMENT FROM JDR INSTRUMENTS

### 20 MHz DUAL TRACE OSCILLOSCOPE

**MODEL 2000 \$389**

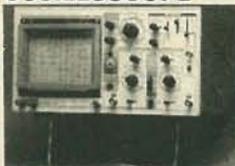

- BAND WIDTH - DC: TO 20 MHz (-3db) AC: 10 Hz TO 20MHz (-3db)
- SWEEP TIME - 2 μSEC TO .5 SEC/DIV ON 20 RANGES
- COMPLETE MANUAL AND HIGH QUALITY HOOK-ON PROBES INCLUDED
- INPUT IMPEDANCE: 1 MEG OHM
- TV VIDEO SYNC FILTER
- X-Y AND Z AXIS OPERATION
- 110/220 VOLT OPERATION
- COMPONENT TESTER
- LP CONSUMPTION - 19 WATTS
- BUILT-IN CALIBRATOR
- AUTOMATIC OR TRIGGERED TIMEBASE

### 35 MHz DUAL TRACE OSCILLOSCOPE

**MODEL 3500 \$549**



- BAND WIDTH - DC: TO 35MHz (-3db) AC: 10 Hz TO 35MHz (-3db)
- SWEEP TIME - .1 μSEC TO .5 SEC/DIV ON 21 RANGES
- DELAYED TRIGGER - 100 mSEC TO 1 μSEC WITH INTENSIFIED AND DELAYED MODES
- COMPLETE MANUAL AND 1X-10X COMPENSATED HOOK-ON PROBES INCLUDED
- VARIABLE HOLD OFF FOR VIEWING COMPLEX WAVES
- TV VIDEO SYNC FILTER
- TRIGGERING OF CH-A, CH-B, ALTERNATING, LINE OR EXTERNAL
- X-Y AND Z AXIS OPERATION

### DIGITAL MULTIMETER PEN MODEL DPM-1000



**\$49.95**

AUTO RANGING, POLARITY AND DECIMAL!

- LARGE 3.5" DISPLAY
- DATA HOLD SWITCH FREEZES READING
- FAST, AUDIBLE CONTINUITY TEST
- LOW BATTERY INDICATOR
- OVERLOAD PROTECTION
- ONLY 1 1/4 x 6 1/4 x 3/4"
- DC VOLTS 1mV-500V
- AC VOLTS 1mV-500V
- .1 OHM - 2 MEG OHM
- WEIGHS ONLY 2.3 OUNCES
- LOW PARTS COUNT-CUSTOM 80 PIN LSI INSURES RELIABILITY
- INCLUDES MANUAL, BATTERIES, HARD CASE, AND ALLIGATOR CLIP

**CALL FOR VOLUME QUOTES**

© COPYRIGHT 1985 JDR MICRODEVICES

CIRCLE 266 ON FREE INFORMATION CARD

## IBM COMPATIBLE INTERFACE CARDS ALL WITH A ONE YEAR WARRANTY

**MULTIFUNCTION CARD \$129.95**  
ALL THE FEATURES OF AST'S 6 PACK PLUS AT HALF THE PRICE



- CLOCK / CALENDAR
- 0-384K RAM
- SERIAL PORT
- PARALLEL PORT
- GAME PORT
- SOFTWARE INCLUDED

PRINTER CABLE \$9.95 64K RAM UPGRADE 9/\$7.11

**COLOR GRAPHICS ADAPTOR \$99.95**

FULLY COMPATIBLE WITH IBM COLOR CARD



- 4 VIDEO INTERFACES: RGB, COMPOSITE COLOR, HI-RES COMPOSITE MONOCHROME, CONNECTOR FOR RF MODULATOR
- COLOR GRAPHICS MODE: 320 x 200
- MONO GRAPHICS MODE: 640 x 200
- LIGHT PEN INTERFACE

**MONOCHROME GRAPHICS CARD \$129.95**

FULLY COMPATIBLE WITH IBM MONOCHROME ADAPTOR AND HERCULES GRAPHICS CARD



- LOTUS COMPATIBLE
- TEXT MODE: 80 x 25
- GRAPHICS MODE: 720 x 348
- PARALLEL PRINTER INTERFACE
- OPTIONAL SERIAL PORT

**FLOPPY DISK DRIVE ADAPTOR \$59.95**



- INTERFACES UP TO FOUR STANDARD FDDs TO IBM PC OR COMPATIBLES
- INCLUDES CABLE FOR TWO INTERNAL DRIVES

## 1200 BAUD INTERNAL MODEM FOR IBM

INCLUDES PC TALK III COMMUNICATIONS SOFTWARE



- Hayes COMPATIBLE
- AUTO DIAL / AUTO ANSWER
- AUTO RE-DIAL ON BUSY
- INCLUDES SERIAL PORT!
- ONE YEAR WARRANTY

**EASYDATA-12B \$195**

## 300 BAUD MODEM FOR APPLE OR IBM CLOSE-OUT SPECIAL NOW ONLY



**\$49.95**

INCLUDES ASCII PRO-EZ SOFTWARE (A \$100 VALUE IN ITSELF)

- FCC APPROVED
- BELL SYSTEMS 103 COMPATIBLE
- INCLUDES AC ADAPTOR
- AUTO DIAL / AUTO ANSWER
- DIRECT CONNECT

CABLE FOR APPLE IIc \$14.95

## 100 CPS ESPRIT PRINTER




**\$149.95**

- 9 x 9 DOT MATRIX
- 100 CPS - BIDIRECTIONAL
- FRICTION AND TRACTOR FEED
- PROPORTIONAL SPACING
- 80 COLUMN
- PARALLEL AND SERIAL INTERFACES
- 8 CHARACTER SETS AND GRAPHICS

CABLE TO IBM PC \$9.95  
REPLACEMENT RIBBON CARTRIDGE SZ-44 \$11.95

**PS-IBM 130 WATTS \$99.95**

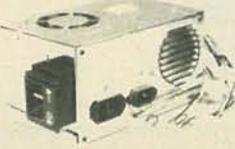

## TEAC DISK DRIVES FOR IBM PCs



FD-55B DS/DD \$89.95  
FD-55F DS/QUAD \$99.95

## UNBELIEVABLE MONITOR DEALS



**TAXAN RGB VISION III MODEL 415**

- 18 MHz BAND WIDTH
- 640 x 262 PIXEL RESOLUTION
- 16 COLORS WITH INTENSITY CONTROL
- 12" BLACK MATRIX
- IBM AND LOTUS COMPATIBLE

CABLE FOR IBM \$15.95

**\$289.95**



**SAKATA COMPOSITE COLOR MODEL SC-100**

- TOP RATED FOR APPLE
- 13" COMPASITE VIDEO
- RESOLUTION: 280H x 300V
- INTERNAL AUDIO AMPLIFIER
- ONE YEAR WARRANTY

**\$169.95**



**SAMWOO MONOCHROME MODEL DM-216B**

- PERFECT COSMETIC MATCH FOR IBM PC
- IBM COMPATIBLE TTL INPUT
- 12" NON-GLARE SCREEN
- P39 GREEN PHOSPHOR
- HI-RES 22 MHz BAND WIDTH

**\$99.95**

## MONITOR STAND TILTS AND SWIVELS



**\$12.95**

## APPLE COMPATIBLE INTERFACE CARDS

**EPROM PROGRAMMER \$79.95**



MODEL RP525

- DUPLICATE OR BURN ANY STANDARD 27xx SERIES EPROM
- EASY TO USE MENU-DRIVEN SOFTWARE INCLUDED
- MENU SELECTION FOR 2716, 2732, 2732A, 2764 & 27128
- HIGH SPEED WRITE ALGORITHM
- LED INDICATORS FOR ACTIVITY
- NO EXTERNAL POWER SUPPLY REQUIRED
- ONE YEAR WARRANTY



**16K RAMCARD \$39.95**

- FULL TWO YEAR WARRANTY
- EXPAND YOUR 48K APPLE TO 64K
- USE IN PLACE OF APPLE LANGUAGE CARD

BARE PC CARD W/ INSTRUCTIONS \$9.95



**IC TEST CARD \$99.95**

- QUICKLY TESTS MANY COMMON ICs
- DISPLAYS PASS OR FAIL
- ONE YEAR WARRANTY
- TESTS: 4000 SERIES CMOS 74HC SERIES CMOS 7400; 74LS, 74L, 74H, 74S, SOME PROMS AND RAMS

## DISK DRIVES

FOR APPLE COMPUTERS



**BAL-525 \$99.95**

- 1/2 HEIGHT-ALPS MECHANISM
- 100% APPLE COMPATIBLE
- FULL 1 YEAR WARRANTY




**BAL-500 \$129.95**

- TEAC MECHANISM- DIRECT DRIVE
- 100% APPLE COMPATIBLE
- FULL 1 YEAR WARRANTY



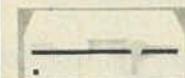**AP-135 \$129.95**

- FULL HT. SHUGART MECHANISM
- DIRECT REPLACEMENT FOR APPLE DISK II
- SIX MONTH WARRANTY



FOR APPLE IIc  
**AD-3C \$139.95**

- 100% APPLE IIc COMPATIBLE, READY TO PLUG IN W/ SHIELDED CABLE & MOLDED 15 PIN CONNECTOR
- FAST, RELIABLE SLIMLINE DIRECT DRIVE
- SIX MONTH WARRANTY



FOR MACINTOSH  
**MAC 535 \$299.95**

- 3.5" ADD-ON DISK DRIVE
- 100% MACINTOSH COMPATIBLE
- SINGLE SIDED 400K BYTE STORAGE
- HIGH RELIABILITY DRIVE FEATURES AUTO-EJECT MECHANISM
- FULL ONE YEAR WARRANTY

## DISK DRIVE ACCESSORIES

DISK CONTROLLER CARD \$49.95  
APPLE IIc ADAPTOR CABLE \$19.95  
ADAPTS STANDARD APPLE DRIVES FOR USE WITH APPLE IIc

## COMREX CR-1000 DUAL SLIMLINE DISK DRIVE FOR APPLE COMPUTERS

**\$189.95**

SPACE SAVING DESIGN STACK BETWEEN COMPUTER AND MONITOR

- QUIET, RELIABLE 1/2 HEIGHT DRIVES
- TOTAL STORAGE CAPACITY: 286K BYTES
- AUTO-EJECT MECHANISM
- SHIELDED CABLE INCLUDED

INCLUDES CONTROLLER AND DOS 3.3 WITH DISK UTILITIES

ALL MERCHANDISE 100% GUARANTEED

© COPYRIGHT 1985 JDR MICRODEVICES



12 MILLION PC IC CLEARANCE - CALL FOR QUANTITY DISCOUNTS -

RED-HOT RAM & EPROM PRICES

NEW EEPROM

Table with columns: Part No., Price, and 7400 series ICs.

Table with columns: Part No., Description, Price, and 21C14, 27C16, 4164N-200, 6116P-4, 6116L-4.

Table with columns: Part No., Description, Price, and 6264LP-15, MC146818, 27128-25, 41266-150, 68764, 68766.

Table with columns: Part No., Price, and 2816A, DT1050, DT1050 Processor Chip, DT1057.

MICROPROCESSOR COMPONENTS

Table with columns: Part No., Price, and MICROPROCESSOR CHIPS including 8080, 8085, 8088, 8088A, 8088P, 8088P.

Table with columns: Part No., Price, and DYNAMIC RAMS including 1163, 4027, 4116N-15, 4116N-20, 4116N-25, 4116N-30, 4116N-35, 4116N-40, 4116N-45, 4116N-50, 4116N-55, 4116N-60, 4116N-65, 4116N-70, 4116N-75, 4116N-80, 4116N-85, 4116N-90, 4116N-95, 4116N-100, 4116N-110, 4116N-120, 4116N-990, 4116N-1000.

Table with columns: Part No., Price, and 2816A, DT1050, DT1050 Processor Chip, DT1057.

Table with columns: Part No., Price, and 74LS series ICs.

Table with columns: Part No., Price, and 6500/8000/8000 SERIES including 6502, 6502A, 6502B, 6502C, 6502D, 6502E, 6502F, 6502G, 6502H, 6502I, 6502J, 6502K, 6502L, 6502M, 6502N, 6502O, 6502P, 6502Q, 6502R, 6502S, 6502T, 6502U, 6502V, 6502W, 6502X, 6502Y, 6502Z, 6503, 6503A, 6503B, 6503C, 6503D, 6503E, 6503F, 6503G, 6503H, 6503I, 6503J, 6503K, 6503L, 6503M, 6503N, 6503O, 6503P, 6503Q, 6503R, 6503S, 6503T, 6503U, 6503V, 6503W, 6503X, 6503Y, 6503Z, 6504, 6504A, 6504B, 6504C, 6504D, 6504E, 6504F, 6504G, 6504H, 6504I, 6504J, 6504K, 6504L, 6504M, 6504N, 6504O, 6504P, 6504Q, 6504R, 6504S, 6504T, 6504U, 6504V, 6504W, 6504X, 6504Y, 6504Z, 6505, 6505A, 6505B, 6505C, 6505D, 6505E, 6505F, 6505G, 6505H, 6505I, 6505J, 6505K, 6505L, 6505M, 6505N, 6505O, 6505P, 6505Q, 6505R, 6505S, 6505T, 6505U, 6505V, 6505W, 6505X, 6505Y, 6505Z, 6506, 6506A, 6506B, 6506C, 6506D, 6506E, 6506F, 6506G, 6506H, 6506I, 6506J, 6506K, 6506L, 6506M, 6506N, 6506O, 6506P, 6506Q, 6506R, 6506S, 6506T, 6506U, 6506V, 6506W, 6506X, 6506Y, 6506Z, 6507, 6507A, 6507B, 6507C, 6507D, 6507E, 6507F, 6507G, 6507H, 6507I, 6507J, 6507K, 6507L, 6507M, 6507N, 6507O, 6507P, 6507Q, 6507R, 6507S, 6507T, 6507U, 6507V, 6507W, 6507X, 6507Y, 6507Z, 6508, 6508A, 6508B, 6508C, 6508D, 6508E, 6508F, 6508G, 6508H, 6508I, 6508J, 6508K, 6508L, 6508M, 6508N, 6508O, 6508P, 6508Q, 6508R, 6508S, 6508T, 6508U, 6508V, 6508W, 6508X, 6508Y, 6508Z, 6509, 6509A, 6509B, 6509C, 6509D, 6509E, 6509F, 6509G, 6509H, 6509I, 6509J, 6509K, 6509L, 6509M, 6509N, 6509O, 6509P, 6509Q, 6509R, 6509S, 6509T, 6509U, 6509V, 6509W, 6509X, 6509Y, 6509Z, 6510, 6510A, 6510B, 6510C, 6510D, 6510E, 6510F, 6510G, 6510H, 6510I, 6510J, 6510K, 6510L, 6510M, 6510N, 6510O, 6510P, 6510Q, 6510R, 6510S, 6510T, 6510U, 6510V, 6510W, 6510X, 6510Y, 6510Z, 6511, 6511A, 6511B, 6511C, 6511D, 6511E, 6511F, 6511G, 6511H, 6511I, 6511J, 6511K, 6511L, 6511M, 6511N, 6511O, 6511P, 6511Q, 6511R, 6511S, 6511T, 6511U, 6511V, 6511W, 6511X, 6511Y, 6511Z, 6512, 6512A, 6512B, 6512C, 6512D, 6512E, 6512F, 6512G, 6512H, 6512I, 6512J, 6512K, 6512L, 6512M, 6512N, 6512O, 6512P, 6512Q, 6512R, 6512S, 6512T, 6512U, 6512V, 6512W, 6512X, 6512Y, 6512Z, 6513, 6513A, 6513B, 6513C, 6513D, 6513E, 6513F, 6513G, 6513H, 6513I, 6513J, 6513K, 6513L, 6513M, 6513N, 6513O, 6513P, 6513Q, 6513R, 6513S, 6513T, 6513U, 6513V, 6513W, 6513X, 6513Y, 6513Z, 6514, 6514A, 6514B, 6514C, 6514D, 6514E, 6514F, 6514G, 6514H, 6514I, 6514J, 6514K, 6514L, 6514M, 6514N, 6514O, 6514P, 6514Q, 6514R, 6514S, 6514T, 6514U, 6514V, 6514W, 6514X, 6514Y, 6514Z, 6515, 6515A, 6515B, 6515C, 6515D, 6515E, 6515F, 6515G, 6515H, 6515I, 6515J, 6515K, 6515L, 6515M, 6515N, 6515O, 6515P, 6515Q, 6515R, 6515S, 6515T, 6515U, 6515V, 6515W, 6515X, 6515Y, 6515Z, 6516, 6516A, 6516B, 6516C, 6516D, 6516E, 6516F, 6516G, 6516H, 6516I, 6516J, 6516K, 6516L, 6516M, 6516N, 6516O, 6516P, 6516Q, 6516R, 6516S, 6516T, 6516U, 6516V, 6516W, 6516X, 6516Y, 6516Z, 6517, 6517A, 6517B, 6517C, 6517D, 6517E, 6517F, 6517G, 6517H, 6517I, 6517J, 6517K, 6517L, 6517M, 6517N, 6517O, 6517P, 6517Q, 6517R, 6517S, 6517T, 6517U, 6517V, 6517W, 6517X, 6517Y, 6517Z, 6518, 6518A, 6518B, 6518C, 6518D, 6518E, 6518F, 6518G, 6518H, 6518I, 6518J, 6518K, 6518L, 6518M, 6518N, 6518O, 6518P, 6518Q, 6518R, 6518S, 6518T, 6518U, 6518V, 6518W, 6518X, 6518Y, 6518Z, 6519, 6519A, 6519B, 6519C, 6519D, 6519E, 6519F, 6519G, 6519H, 6519I, 6519J, 6519K, 6519L, 6519M, 6519N, 6519O, 6519P, 6519Q, 6519R, 6519S, 6519T, 6519U, 6519V, 6519W, 6519X, 6519Y, 6519Z, 6520, 6520A, 6520B, 6520C, 6520D, 6520E, 6520F, 6520G, 6520H, 6520I, 6520J, 6520K, 6520L, 6520M, 6520N, 6520O, 6520P, 6520Q, 6520R, 6520S, 6520T, 6520U, 6520V, 6520W, 6520X, 6520Y, 6520Z, 6521, 6521A, 6521B, 6521C, 6521D, 6521E, 6521F, 6521G, 6521H, 6521I, 6521J, 6521K, 6521L, 6521M, 6521N, 6521O, 6521P, 6521Q, 6521R, 6521S, 6521T, 6521U, 6521V, 6521W, 6521X, 6521Y, 6521Z, 6522, 6522A, 6522B, 6522C, 6522D, 6522E, 6522F, 6522G, 6522H, 6522I, 6522J, 6522K, 6522L, 6522M, 6522N, 6522O, 6522P, 6522Q, 6522R, 6522S, 6522T, 6522U, 6522V, 6522W, 6522X, 6522Y, 6522Z, 6523, 6523A, 6523B, 6523C, 6523D, 6523E, 6523F, 6523G, 6523H, 6523I, 6523J, 6523K, 6523L, 6523M, 6523N, 6523O, 6523P, 6523Q, 6523R, 6523S, 6523T, 6523U, 6523V, 6523W, 6523X, 6523Y, 6523Z, 6524, 6524A, 6524B, 6524C, 6524D, 6524E, 6524F, 6524G, 6524H, 6524I, 6524J, 6524K, 6524L, 6524M, 6524N, 6524O, 6524P, 6524Q, 6524R, 6524S, 6524T, 6524U, 6524V, 6524W, 6524X, 6524Y, 6524Z, 6525, 6525A, 6525B, 6525C, 6525D, 6525E, 6525F, 6525G, 6525H, 6525I, 6525J, 6525K, 6525L, 6525M, 6525N, 6525O, 6525P, 6525Q, 6525R, 6525S, 6525T, 6525U, 6525V, 6525W, 6525X, 6525Y, 6525Z, 6526, 6526A, 6526B, 6526C, 6526D, 6526E, 6526F, 6526G, 6526H, 6526I, 6526J, 6526K, 6526L, 6526M, 6526N, 6526O, 6526P, 6526Q, 6526R, 6526S, 6526T, 6526U, 6526V, 6526W, 6526X, 6526Y, 6526Z, 6527, 6527A, 6527B, 6527C, 6527D, 6527E, 6527F, 6527G, 6527H, 6527I, 6527J, 6527K, 6527L, 6527M, 6527N, 6527O, 6527P, 6527Q, 6527R, 6527S, 6527T, 6527U, 6527V, 6527W, 6527X, 6527Y, 6527Z, 6528, 6528A, 6528B, 6528C, 6528D, 6528E, 6528F, 6528G, 6528H, 6528I, 6528J, 6528K, 6528L, 6528M, 6528N, 6528O, 6528P, 6528Q, 6528R, 6528S, 6528T, 6528U, 6528V, 6528W, 6528X, 6528Y, 6528Z, 6529, 6529A, 6529B, 6529C, 6529D, 6529E, 6529F, 6529G, 6529H, 6529I, 6529J, 6529K, 6529L, 6529M, 6529N, 6529O, 6529P, 6529Q, 6529R, 6529S, 6529T, 6529U, 6529V, 6529W, 6529X, 6529Y, 6529Z, 6530, 6530A, 6530B, 6530C, 6530D, 6530E, 6530F, 6530G, 6530H, 6530I, 6530J, 6530K, 6530L, 6530M, 6530N, 6530O, 6530P, 6530Q, 6530R, 6530S, 6530T, 6530U, 6530V, 6530W, 6530X, 6530Y, 6530Z, 6531, 6531A, 6531B, 6531C, 6531D, 6531E, 6531F, 6531G, 6531H, 6531I, 6531J, 6531K, 6531L, 6531M, 6531N, 6531O, 6531P, 6531Q, 6531R, 6531S, 6531T, 6531U, 6531V, 6531W, 6531X, 6531Y, 6531Z, 6532, 6532A, 6532B, 6532C, 6532D, 6532E, 6532F, 6532G, 6532H, 6532I, 6532J, 6532K, 6532L, 6532M, 6532N, 6532O, 6532P, 6532Q, 6532R, 6532S, 6532T, 6532U, 6532V, 6532W, 6532X, 6532Y, 6532Z, 6533, 6533A, 6533B, 6533C, 6533D, 6533E, 6533F, 6533G, 6533H, 6533I, 6533J, 6533K, 6533L, 6533M, 6533N, 6533O, 6533P, 6533Q, 6533R, 6533S, 6533T, 6533U, 6533V, 6533W, 6533X, 6533Y, 6533Z, 6534, 6534A, 6534B, 6534C, 6534D, 6534E, 6534F, 6534G, 6534H, 6534I, 6534J, 6534K, 6534L, 6534M, 6534N, 6534O, 6534P, 6534Q, 6534R, 6534S, 6534T, 6534U, 6534V, 6534W, 6534X, 6534Y, 6534Z, 6535, 6535A, 6535B, 6535C, 6535D, 6535E, 6535F, 6535G, 6535H, 6535I, 6535J, 6535K, 6535L, 6535M, 6535N, 6535O, 6535P, 6535Q, 6535R, 6535S, 6535T, 6535U, 6535V, 6535W, 6535X, 6535Y, 6535Z, 6536, 6536A, 6536B, 6536C, 6536D, 6536E, 6536F, 6536G, 6536H, 6536I, 6536J, 6536K, 6536L, 6536M, 6536N, 6536O, 6536P, 6536Q, 6536R, 6536S, 6536T, 6536U, 6536V, 6536W, 6536X, 6536Y, 6536Z, 6537, 6537A, 6537B, 6537C, 6537D, 6537E, 6537F, 6537G, 6537H, 6537I, 6537J, 6537K, 6537L, 6537M, 6537N, 6537O, 6537P, 6537Q, 6537R, 6537S, 6537T, 6537U, 6537V, 6537W, 6537X, 6537Y, 6537Z, 6538, 6538A, 6538B, 6538C, 6538D, 6538E, 6538F, 6538G, 6538H, 6538I, 6538J, 6538K, 6538L, 6538M, 6538N, 6538O, 6538P, 6538Q, 6538R, 6538S, 6538T, 6538U, 6538V, 6538W, 6538X, 6538Y, 6538Z, 6539, 6539A, 6539B, 6539C, 6539D, 6539E, 6539F, 6539G, 6539H, 6539I, 6539J, 6539K, 6539L, 6539M, 6539N, 6539O, 6539P, 6539Q, 6539R, 6539S, 6539T, 6539U, 6539V, 6539W, 6539X, 6539Y, 6539Z, 6540, 6540A, 6540B, 6540C, 6540D, 6540E, 6540F, 6540G, 6540H, 6540I, 6540J, 6540K, 6540L, 6540M, 6540N, 6540O, 6540P, 6540Q, 6540R, 6540S, 6540T, 6540U, 6540V, 6540W, 6540X, 6540Y, 6540Z, 6541, 6541A, 6541B, 6541C, 6541D, 6541E, 6541F, 6541G, 6541H, 6541I, 6541J, 6541K, 6541L, 6541M, 6541N, 6541O, 6541P, 6541Q, 6541R, 6541S, 6541T, 6541U, 6541V, 6541W, 6541X, 6541Y, 6541Z, 6542, 6542A, 6542B, 6542C, 6542D, 6542E, 6542F, 6542G, 6542H, 6542I, 6542J, 6542K, 6542L, 6542M, 6542N, 6542O, 6542P, 6542Q, 6542R, 6542S, 6542T, 6542U, 6542V, 6542W, 6542X, 6542Y, 6542Z, 6543, 6543A, 6543B, 6543C, 6543D, 6543E, 6543F, 6543G, 6543H, 6543I, 6543J, 6543K, 6543L, 6543M, 6543N, 6543O, 6543P, 6543Q, 6543R, 6543S, 6543T, 6543U, 6543V, 6543W, 6543X, 6543Y, 6543Z, 6544, 6544A, 6544B, 6544C, 6544D, 6544E, 6544F, 6544G, 6544H, 6544I, 6544J, 6544K, 6544L, 6544M, 6544N, 6544O, 6544P, 6544Q, 6544R, 6544S, 6544T, 6544U, 6544V, 6544W, 6544X, 6544Y, 6544Z, 6545, 6545A, 6545B, 6545C, 6545D, 6545E, 6545F, 6545G, 6545H, 6545I, 6545J, 6545K, 6545L, 6545M, 6545N, 6545O, 6545P, 6545Q, 6545R, 6545S, 6545T, 6545U, 6545V, 6545W, 6545X, 6545Y, 6545Z, 6546, 6546A, 6546B, 6546C, 6546D, 6546E, 6546F, 6546G, 6546H, 6546I, 6546J, 6546K, 6546L, 6546M, 6546N, 6546O, 6546P, 6546Q, 6546R, 6546S, 6546T, 6546U, 6546V, 6546W, 6546X, 6546Y, 6546Z, 6547, 6547A, 6547B, 6547C, 6547D, 6547E, 6547F, 6547G, 6547H, 6547I, 6547J, 6547K, 6547L, 6547M, 6547N, 6547O, 6547P, 6547Q, 6547R, 6547S, 6547T, 6547U, 6547V, 6547W, 6547X, 6547Y, 6547Z, 6548, 6548A, 6548B, 6548C, 6548D, 6548E, 6548F, 6548G, 6548H, 6548I, 6548J, 6548K, 6548L, 6548M, 6548N, 6548O, 6548P, 6548Q, 6548R, 6548S, 6548T, 6548U, 6548V, 6548W, 6548X, 6548Y, 6548Z, 6549, 6549A, 6549B, 6549C, 6549D, 6549E, 6549F, 6549G, 6549H, 6549I, 6549J, 6549K, 6549L, 6549M, 6549N, 6549O, 6549P, 6549Q, 6549R, 6549S, 6549T, 6549U, 6549V, 6549W, 6549X, 6549Y, 6549Z, 6550, 6550A, 6550B, 6550C, 6550D, 6550E, 6550F, 6550G, 6550H, 6550I, 6550J, 6550K, 6550L, 6550M, 6550N, 6550O, 6550P, 6550Q, 6550R, 6550S, 6550T, 6550U, 6550V, 6550W, 6550X, 6550Y, 6550Z, 6551, 6551A, 6551B, 6551C, 6551D, 6551E, 6551F, 6551G, 6551H, 6551I, 6551J, 6551K, 6551L, 6551M, 6551N, 6551O, 6551P, 6551Q, 6551R, 6551S, 6551T, 6551U, 6551V, 6551W, 6551X, 6551Y, 6551Z, 6552, 6552A, 6552B, 6552C, 6552D, 6552E, 6552F, 6552G, 6552H, 6552I, 6552J, 6552K, 6552L, 6552M, 6552N, 6552O, 6552P, 6552Q, 6552R, 6552S, 6552T, 6552U, 6552V, 6552W, 6552X, 6552Y, 6552Z, 6553, 6553A, 6553B, 6553C, 6553D, 6553E, 6553F, 6553G, 6553H, 6553I, 6553J, 6553K, 6553L, 6553M, 6553N, 6553O, 6553P, 6553Q, 6553R, 6553S, 6553T, 6553U, 6553V, 6553W, 6553X, 6553Y, 6553Z, 6554, 6554A, 6554B, 6554C, 6554D, 6554E, 6554F, 6554G, 6554H, 6554I, 6554J, 6554K, 6554L, 6554M, 6554N, 6554O, 6554P, 6554Q, 6554R, 6554S, 6554T, 6554U, 6554V, 6554W, 6554X, 6554Y, 6554Z, 6555, 6555A, 6555B, 6555C, 6555D, 6555E, 6555F, 6555G, 6555H, 6555I, 6555J, 6555K, 6555L, 6555M, 6555N, 6555O, 6555P, 6555Q, 6555R, 6555S, 6555T, 6555U, 6555V, 6555W, 6555X, 6555Y, 6555Z, 6556, 6556A, 6556B, 6556C, 6556D, 6556E, 6556F, 6556G, 6556H, 6556I, 6556J, 6556K, 6556L, 6556M, 6556N, 6556O, 6556P, 6556Q, 6556R,

**Commodore Accessories**



**RS232 Adapter for VIC-20 and Commodore 64**

The JE232CM allows connection of standard serial RS232 printers, modems, etc. to your VIC-20 and C-64. A 4-pole switch allows the inversion of the 4 control lines. Complete installation and operation instructions included.  
• Plugs into User Port • Provides Standard RS232 signal levels • Uses 8 signals (Transmit, Receive, Clear to Send, Request to Send, Data Terminal Ready, Data Set Ready).  
**JE232CM** ..... \$39.95

**VOICE SYNTHESIZER FOR COMMODORE VIC-20 AND C-64**  
Plug-In - Talking in Minutes!  
**JE520CM** ..... \$99.95

**TRS-80 Accessories**

**MPI 5 1/4" DISK DRIVE**

Use as a second disk drive • Single-sided • Single/double density • Full-height drive • 48 TPI • Documentation included • Weight: 3.7 lbs

**MPI51S** ..... \$89.95

**EXPAND TRS-80 MEMORY TRS-80 MODEL I, III**

Each Kit comes complete with eight MMS290 (UPD4161/11) 16K Dynamic RAMs and documentation for conversion. Model I 16K equipped with Expansion Interface can be expanded to 48K with 2 Kits. Model III can be expanded from 16K to 48K using 2 Kits. Each Kit will expand computer by 16K increments.

**TRS-16K3 200s (Model III)** ..... \$6.29  
**TRS-16K4 250s (Model I)** ..... \$5.49

**TRS-80 COLOR AND COLOR II**  
Easy to install Kit comes complete with 8 each 4164-20 (200s) 64K Dynamic RAMs and documentation for conversion. Converts TRS-80 Color Computers with D, E, ET, F and NC circuit boards to 32K. Also converts TRS-80 Color Computer II to 64K. Flex DOS or OS-9 required to utilize full 64K RAM on all computers.  
**TRS-64K-2** ..... \$11.95

**Update! TRS-80 MODEL IV, 4P Update!**  
Easy to install Kits come complete with: TRS-64K-2 (8 ea. 4164-20 (200s) 64K Dynamic RAMs); TRS-64K-2PAL (8 ea. 4164's plus PAL chip) and documentation for conversion.

**TRS-64K-2** Expands Model IV from 16K-64K or Model IV 4P from 64K-128K (w/Mem. Disk) ..... \$11.95  
**TRS-64K-2PAL** Expands Model IV (w/Black & White Monitors only) from 64K to 128K ..... \$29.95

**• TRS-80 Model 100 • NEC • Olivetti**  
Easy to install module plugs right into the socket increasing memory in 8K increments. Complete with module and documentation for installation.  
**M1008K (TRS-80 Model 100 Expansion)** ..... \$39.95 ea. or 3 for \$99.95  
**NEC8KR (NEC PC-8201A & Olivetti M10)** ..... \$39.95 ea. or 3 for \$99.95

**NEW! NEW! TANDY 200 NEW! NEW! NEW!**  
Easy to install module plugs right into the socket increasing memory in 24K increments. Complete with module & documentation for installation.  
**M200R (Tandy 200 Expansion)** ..... \$149.95 ea. or 2 for \$274.95

**PROMETHEUS MODEMS**

**Intelligent 300/1200 Baud Modem with Real Time Clock/Calendar**

The ProModem™ is a Bell 212A (300/1200) intelligent stand-alone modem • Hayes command set compatible plus an additional extended command set • Shown with alphanumeric display option.  
**PM1200 RS-232 Stand-Alone Unit** ..... \$299.95

**OPTIONS For ProModem 1200**  
**PM-COM (ProCom Communication Software)** ..... \$79.95  
Please specify Operating System.  
**PM-OP (Options Processor)** ..... \$79.95  
**PMO-64K (Options Processor Memory - 64K)** ..... \$ 8.49  
**PM-ALP (Alphanumeric Display)** ..... \$79.95

(Incl. Options Processor, 64K Memory and Alphanumeric Display).  
**PM-Special** ..... \$149.95

**DATA BOOKS**


- 30099 **Intel® Data Book (1984)** ..... \$9.95  
Complete Line (985 pages).
- 30013 **Zilog Data Book (1984)** ..... \$9.95  
Microprocessors and Support Chips (849 pages).
- 210830 **Intel Memory Components Hndbk. (1983/84)** ..... \$14.95  
Contains all Applications Notes, Article Requests, Data Sheets & other design information on Intel's RAMs, DRAMs, EPROMs, EEPROMs and Bubble Memories (850 pages).
- 230843 **Intel Microsystem Components Hndbk. (1983/84)** ..... \$19.95  
Contains Data Sheets on all of Intel's Microprocessors & peripheral - 2 volumes (2575 pages).
- 30022 **National Logic Data Book Set (1984)** ..... \$24.95  
Volumes 1 & 2 (3485 pages).  
Contains information on National's TTL, product line and CD4000 family. This includes 7400, 74L, 8, AD, LS and ALS Series devices, and MM54HC™ 74HC™ 74BCT™ High Speed Micro CMOS family, MM54C™ 74C™ family and CMOS LSJ / VLSJ.

**Muffin-Style & Sprite-Style Fans**

- MUF60 (SPN3-15-2482)**  
Howard Industries (4.68" sq, 60cm). .... \$9.95
- ESG27 Reverse Flow**  
EG&G Rotron (3.125" sq, 32cm). .... \$9.95

\*\*\*\*\* **APPLE Accessories** \*\*\*\*\*

**JAMECO's APPLE® Compatible Products**

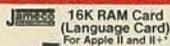


**16K RAM Card (Language Card) For Apple II and II+**

The JE660 RAM Card allows the Apple II and II+ computers to support from 48K to 64K. Fully compatible with Microsoft Software, Home Appointments, 200K CP/M and many other applications.  
**JE660 (AMC-16K-MEM-1)** ..... \$39.95



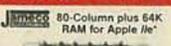**Controller Card For Apple II, II+ & IIe**

The JE875 is a standard Apple® Controller Card. Capable of handling up to two drives. Easy to install. Fully compatible with CP/M and other applications.  
**JE875 (MCC-1)** ..... \$49.95



**80-Column plus 64K RAM for Apple IIe**

The JE664 is an enhanced 80-column/64K RAM card. This effectively doubles the amount of data that your Apple IIe can store. Fully compatible with Apple IIe software. Easy to install. Fully compatible with CP/M and other applications.  
**JE664** ..... \$69.95



**Five Key Software Programs! For Apple II, II+ and IIe**



**128K RAM Card For Apple II, II+ and IIe**



**RAM Disk!**



**Parallel Printer Card For Apple II, II+ and IIe**



**Parallel/Serial Buffer Card For Apple II, II+ and IIe**

The JE868 is a functionally compatible with the Apple II language card and can be utilized with all software that can be used with a standard 16K card. The JE868 requires no modifications to your Apple computer. Five key software programs are included: Memory Management System, Utilities, diagnostics, disks, and RAM disk emulators for DOS 3.3, CP/M and Apple Pascal. Also features DOS relocater. Complete with instructions. Key (a,b).  
**JE868 (Expand-A-RAM)** ..... \$119.95

**Applesure Diagnostic Disk Controller Card Prevents Crashes! For Apple II, II+ and IIe**

The JE877 serves as a diagnostic tool, an applesure maintenance tool and a dual disk drive controller. The JE877 will verify and check the operating hardware of your system each time you turn on your Apple II, II+ or IIe. Test your RAM, ROM, CPU, and disk drives. Diagnostic routines may be cancelled at the touch of a key. Complete with instructions. Key (a,b).  
**JE877 (DRV-1/Applesure II)** ..... \$69.95

**Parallel Printer Card For Apple II, II+ and IIe**

The JE890 Printer interface board is an intelligent interface to most of today's popular dot matrix graphics printers. The JE890 is fully compatible with Apple IIe, Apple Pascal (or FORTRAN), and most other operating systems and software. The JE890 is standard and can be re-configured for other standards if necessary. Advanced test printing features include: video screen echo ON or OFF, auto-disable (enabled after carriage return, set at the bit of the output data), set left margin and more! Complete with instructions. Key (a,b).  
**JE890 (PRT-1)** ..... \$59.95

**Parallel/Serial Buffer Card For Apple II, II+ and IIe**

The JE883 provides the user with up to 64K of additional or buffered memory (18 pages of information). Using the parallel jumper cable supplied, the JE883 will attach to the JE850 (above). Parallel card needed for operation. The JE883 includes a standard parallel port with both parallel and serial (RS232) buffered outputs. With these features you may access and buffer information to two types of printers: one serial, one parallel simultaneously. Complete with instructions. Key (a,b).  
**JE883 (P/S Buffer)** ..... \$79.95

**EPROM PROGRAMMERS**

**JE670 GANG EPROM PROGRAMMER 8K TO 512K (E)EPROMS**



The JE670 is a stand-alone programmer that gang programs most EPROMs and EEPROMs (up to 512K) from your Master IC. Operation is simple, foolproof and fast.  
• Program capacity of 10 EPROMs at one time. Status indicator for each socket.  
• Fully automatic Blank-testing, Programming and Margin-testing EPROMs.  
• Fully automatic verification against Master, both after programming and during Margin-testing at two VCC's.  
• Uses "Intelligent" algorithms to minimize programming times.  
• All device sockets are Zero Insertion Force Testout sockets.

**OPERATION:** The JE670 Gang Programmer is fully operated with just 4 pushbuttons. Operation is simplified by employing Jumper Modules ("J" Series) for the different type devices. The JE670 is ideal for program programming and testing of IC's. • Input: 115VAC, 60Hz, 15W • Size: 19 1/2" x 8 1/2" x 3 1/2" • Weight: 6.8 lbs.

**JE670 GANG (EPROM PROGRAMMER) (Assembled and Tested) (Includes JM C16A Modules)** ..... \$695.00

**JE670 JUMPER MODULES "J" SERIES (PERSONALITY MODULES) Partial Listing - New JM's to Be Announced**

PRICE	DESCRIPTION	PRICE	DESCRIPTION
\$18.95	JM 044B TMS0104	\$18.95	JM 044C TMS0104
\$18.95	JM 044D TMS0104	\$18.95	JM 044E TMS0104
\$18.95	JM 044F TMS0104	\$18.95	JM 044G TMS0104
\$18.95	JM 044H TMS0104	\$18.95	JM 044I TMS0104
\$18.95	JM 044J TMS0104	\$18.95	JM 044K TMS0104
\$18.95	JM 044L TMS0104	\$18.95	JM 044M TMS0104
\$18.95	JM 044N TMS0104	\$18.95	JM 044O TMS0104
\$18.95	JM 044P TMS0104	\$18.95	JM 044Q TMS0104
\$18.95	JM 044R TMS0104	\$18.95	JM 044S TMS0104
\$18.95	JM 044T TMS0104	\$18.95	JM 044U TMS0104
\$18.95	JM 044V TMS0104	\$18.95	JM 044W TMS0104
\$18.95	JM 044X TMS0104	\$18.95	JM 044Y TMS0104
\$18.95	JM 044Z TMS0104	\$18.95	JM 044AA TMS0104

**EPROMS ONLY**

PRICE	DESCRIPTION	PRICE	DESCRIPTION
\$18.95	JM 045A 2716	\$18.95	JM 045B 2716
\$18.95	JM 045C 2716	\$18.95	JM 045D 2716
\$18.95	JM 045E 2716	\$18.95	JM 045F 2716
\$18.95	JM 045G 2716	\$18.95	JM 045H 2716
\$18.95	JM 045I 2716	\$18.95	JM 045J 2716
\$18.95	JM 045K 2716	\$18.95	JM 045L 2716
\$18.95	JM 045M 2716	\$18.95	JM 045N 2716
\$18.95	JM 045O 2716	\$18.95	JM 045P 2716
\$18.95	JM 045Q 2716	\$18.95	JM 045R 2716
\$18.95	JM 045S 2716	\$18.95	JM 045T 2716
\$18.95	JM 045U 2716	\$18.95	JM 045V 2716
\$18.95	JM 045W 2716	\$18.95	JM 045X 2716
\$18.95	JM 045Y 2716	\$18.95	JM 045Z 2716
\$18.95	JM 045AA 2716	\$18.95	JM 045AB 2716
\$18.95	JM 045AC 2716	\$18.95	JM 045AD 2716
\$18.95	JM 045AE 2716	\$18.95	JM 045AF 2716
\$18.95	JM 045AG 2716	\$18.95	JM 045AH 2716
\$18.95	JM 045AI 2716	\$18.95	JM 045AJ 2716
\$18.95	JM 045AK 2716	\$18.95	JM 045AL 2716
\$18.95	JM 045AM 2716	\$18.95	JM 045AN 2716
\$18.95	JM 045AO 2716	\$18.95	JM 045AP 2716
\$18.95	JM 045AQ 2716	\$18.95	JM 045AR 2716
\$18.95	JM 045AS 2716	\$18.95	JM 045AT 2716
\$18.95	JM 045AU 2716	\$18.95	JM 045AV 2716
\$18.95	JM 045AW 2716	\$18.95	JM 045AX 2716
\$18.95	JM 045AY 2716	\$18.95	JM 045AZ 2716
\$18.95	JM 045BA 2716	\$18.95	JM 045BB 2716
\$18.95	JM 045BC 2716	\$18.95	JM 045BD 2716
\$18.95	JM 045BE 2716	\$18.95	JM 045BF 2716
\$18.95	JM 045BG 2716	\$18.95	JM 045BH 2716
\$18.95	JM 045BI 2716	\$18.95	JM 045BJ 2716
\$18.95	JM 045BK 2716	\$18.95	JM 045BL 2716
\$18.95	JM 045BM 2716	\$18.95	JM 045BN 2716
\$18.95	JM 045BO 2716	\$18.95	JM 045BP 2716
\$18.95	JM 045BQ 2716	\$18.95	JM 045BR 2716
\$18.95	JM 045BS 2716	\$18.95	JM 045BT 2716
\$18.95	JM 045BU 2716	\$18.95	JM 045BV 2716
\$18.95	JM 045BW 2716	\$18.95	JM 045BX 2716
\$18.95	JM 045BY 2716	\$18.95	JM 045BZ 2716
\$18.95	JM 045CA 2716	\$18.95	JM 045CB 2716
\$18.95	JM 045CC 2716	\$18.95	JM 045CD 2716
\$18.95	JM 045CE 2716	\$18.95	JM 045CF 2716
\$18.95	JM 045CG 2716	\$18.95	JM 045CH 2716
\$18.95	JM 045CI 2716	\$18.95	JM 045CJ 2716
\$18.95	JM 045CK 2716	\$18.95	JM 045CL 2716
\$18.95	JM 045CM 2716	\$18.95	JM 045CN 2716
\$18.95	JM 045CO 2716	\$18.95	JM 045CP 2716
\$18.95	JM 045CQ 2716	\$18.95	JM 045CR 2716
\$18.95	JM 045CS 2716	\$18.95	JM 045CT 2716
\$18.95	JM 045CU 2716	\$18.95	JM 045CV 2716
\$18.95	JM 045CW 2716	\$18.95	JM 045CX 2716
\$18.95	JM 045CY 2716	\$18.95	JM 045CZ 2716
\$18.95	JM 045DA 2716	\$18.95	JM 045DB 2716
\$18.95	JM 045DC 2716	\$18.95	JM 045DD 2716
\$18.95	JM 045DE 2716	\$18.95	JM 045DF 2716
\$18.95	JM 045DG 2716	\$18.95	JM 045DH 2716
\$18.95	JM 045DI 2716	\$18.95	JM 045DJ 2716
\$18.95	JM 045DK 2716	\$18.95	JM 045DL 2716
\$18.95	JM 045DM 2716	\$18.95	JM 045DN 2716
\$18.95	JM 045DO 2716	\$18.95	JM 045DP 2716
\$18.95	JM 045DQ 2716	\$18.95	JM 045DR 2716
\$18.95	JM 045DS 2716	\$18.95	JM 045DT 2716
\$18.95	JM 045DU 2716	\$18.95	JM 045DV 2716
\$18.95	JM 045DW 2716	\$18.95	JM 045DX 2716
\$18.95	JM 045DY 2716	\$18.95	JM 045DZ 2716
\$18.95	JM 045EA 2716	\$18.95	JM 045EB 2716
\$18.95	JM 045EC 2716	\$18.95	JM 045ED 2716
\$18.95	JM 045EE 2716	\$18.95	JM 045EF 2716
\$18.95	JM 045EG 2716	\$18.95	JM 045EH 2716
\$18.95	JM 045EI 2716	\$18.95	JM 045EJ 2716
\$18.95	JM 045EK 2716	\$18.95	JM 045EL 2716
\$18.95	JM 045EM 2716	\$18.95	JM 045EN 2716
\$18.95	JM 045EO 2716	\$18.95	JM 045EP 2716
\$18.95	JM 045EQ 2716	\$18.95	JM 045ER 2716
\$18.95	JM 045ES 2716	\$18.95	JM 045ET 2716
\$18.95	JM 045EU 2716	\$18.95	JM 045EV 2716
\$18.95	JM 045EW 2716	\$18.95	JM 045EX 2716
\$18.95	JM 045EY 2716	\$18.95	JM 045EZ 2716
\$18.95	JM 045FA 2716	\$18.95	JM 045FB 2716
\$18.95	JM 045FC 2716	\$18.95	JM 045FD 2716
\$18.95	JM 045FE 2716	\$18.95	JM 045FF 2716
\$18.95	JM 045FG 2716	\$18.95	JM 045FH 2716
\$18.95	JM 045FI 2716	\$18.95	JM 045FJ 2716
\$18.95	JM 045FK 2716	\$18.95	JM 045FL 2716
\$18.95	JM 045FM 2716	\$18.95	JM 045FN 2716
\$18.95	JM 045FO 2716	\$18.95	JM 045FP 2716
\$18.95	JM 045FQ 2716	\$18.95	JM 045FR 2716
\$18.95	JM 045FS 2716	\$18.95	JM 045FT 2716
\$18.95	JM 045FU 2716	\$18.95	JM 045FV 2716
\$18.95	JM 045FW 2716	\$18.95	JM 045FX 2716
\$18.95	JM 045FY 2716	\$18.95	JM 045FZ 2716
\$18.95	JM 045GA 2716	\$18.95	JM 045GB 2716
\$18.95	JM 045GC 2716	\$18.95	JM 045GD 2716
\$18.95	JM 045GE 2		

# STUN GUN

49.95



Free holster with purchase.



# EQUALIZER

- The ultimate non-lethal defense weapon.
- In five seconds can immobilize your attacker, even through heavy clothing.
- Discharges over forty thousand volts of electricity from a nine volt nickel-cadmium battery.
- \$49.95, Mass 5% sales tax, \$3.00 shipping and handling.

**1-800-225-5800**

**Cameo Enterprises, Inc.**  
P.O. Box 63, Accord, MA 02018

CIRCLE 279 ON FREE INFORMATION CARD

# cable tv

## DESCRAMBLER PARTS

We stock the exact parts and PC Board for Radio Electronic's February Article on building your own Cable TV Descrambler.

**#701 PARTS PACKAGE ..... \$29.95**

Includes all the original resistors, capacitors, diodes, transistors, integrated circuits, coils and IF transformers (BKAN-K5552AXX).

**#702 PC BOARD ..... \$12.95**

Original etched & drilled silk-screened PC Board used in the article.

**#704 AC ADAPTOR ..... \$12.95**  
(14 volts DC @ 285MA)

**Both #701 & #702 ..... \$39.00**

**FREE!!** Reprint of Radio Electronics Article on Building Your Own Cable TV Descrambler with any purchase.

Add \$4.00 Postage & Handling

TOLL FREE

1-800-227 8529 (Orders Only)

1-617-339-5372 (Information)

**J & W  
ELECTRONICS, INC.**

P.O. Box 800  
Mansfield, MA 02048

CIRCLE 65 ON FREE INFORMATION CARD

# AMAZING DEVICES

**PERSONAL DEFENSE AND PROPERTY PROTECTION UTILIZE SPACE AGE TECHNOLOGY.**  
CAUTION THESE DEVICES CAN BE HAZARDOUS AND MAY SOON BE ILLEGAL.

**POCKET PAIN FIELD GENERATOR — IPG50**

Assembled..... \$64.50

IPG5..... Plans..... \$8.00 IPG5K..... Kit/Plans..... \$44.50

**PHASOR PAIN FIELD CROWD CONTROLLER — PPF10**

Assembled..... \$250.00

PPF1..... Plans..... \$15.00 PPF1K..... Kit/Plans..... \$175.00

**BLASTER** - Provides a plasma discharge capable of puncturing a can. Produces a 100,000 WATT PULSE.

BLS10..... ASSEMBLED..... \$89.50

BLS1..... PLANS..... \$10.00 BLS1K..... KIT/PLANS..... \$69.50

**PLASMA STUN GUN** - Very intimidating and effective 5 to 10 feet 100,000 VOLTS

ITM10..... ASSEMBLED..... \$99.50

ITM1..... PLANS..... \$10.00 ITM1K..... KIT/PLANS..... \$69.50

**RUBY LASER RAY GUN** — Intense visible red beam burns and welds hardest of metals. **MAY BE HAZARDOUS.**

**RUB3 All Parts Available for Completing Device** \$20.00

**CARBON DIOXIDE BURNING, CUTTING LASER** — Produces a continuous beam of high energy. **MAY BE HAZARDOUS.**

**LC5. All Parts Available for Completing Device.** \$20.00

**VISIBLE LASER LIGHT GUN** — produces intense red beam for sighting, spotting, etc. Hand held complete.

LGU3..... Plans..... \$10.00 (Kit & Assembled Units Available)

**IR PULSED LASER RIFLE** — Produces 15-30 watt infra-red pulses at 200-2000 per sec.

LRG3..... All Parts & Diodes Available..... \$10.00

**BEGINNERS LOW POWER VISIBLE LASER** — Choice of red, yellow, green — provides an excellent source of monochromatic light.

LHC2..... Plans..... \$5.00 LHC2K..... Kit..... \$34.50

**SNOOPER PHONE** — Allows user to call his premises and listen in without phone ever ringing.

SNP20..... Assembled..... \$89.50

SNP2..... Plans..... \$9.00 SNP2K..... Plans/Kit..... \$59.50

**LONG RANGE WIRELESS MIKE** — Miniature device clearly transmits well over one mile. Super sensitive, powerful.

MFT1..... Plans..... \$7.00 MFT1K..... Plans/Kit..... \$49.50

**WIRELESS TELEPHONE TRANSMITTER** — Transmits both sides of phone conversation over one mile, shuts off automatically.

VWPM5..... Plans..... \$8.00 VWPM5K..... Plans/Kit..... \$39.50

**PWM5—LONG RANGE SUPER EAR WITH WIRELESS ATTACHMENT**

PWM5..... Plans..... \$10.00 PWM5K..... Kit..... \$139.50

PWM50..... Assembled and Tested..... \$169.50

Our phone is open for orders anytime. Technicians are available 9-11 a.m., Mon-Thurs for those needing assistance or information. Send \$1.00 for catalog of hundreds more similar devices. Send check, cash, MO, Visa, MC. COD to: **INFORMATION UNLIMITED**

DEPT RB, P.O. Box 716, Amherst, N.H. 03031 Tel: 603-673-4730

CIRCLE 72 ON FREE INFORMATION CARD

**SECURITY**

**PHASORS**

**LASERS**

**AMAZING DEVICES**

**PERSONAL DEFENSE AND PROPERTY PROTECTION**

**UTILIZE SPACE AGE TECHNOLOGY.**

**CAUTION THESE DEVICES CAN BE HAZARDOUS AND MAY SOON BE ILLEGAL.**

**POCKET PAIN FIELD GENERATOR — IPG50**

Assembled..... \$64.50

IPG5..... Plans..... \$8.00 IPG5K..... Kit/Plans..... \$44.50

**PHASOR PAIN FIELD CROWD CONTROLLER — PPF10**

Assembled..... \$250.00

PPF1..... Plans..... \$15.00 PPF1K..... Kit/Plans..... \$175.00

**BLASTER** - Provides a plasma discharge capable of puncturing a can. Produces a 100,000 WATT PULSE.

BLS10..... ASSEMBLED..... \$89.50

BLS1..... PLANS..... \$10.00 BLS1K..... KIT/PLANS..... \$69.50

**PLASMA STUN GUN** - Very intimidating and effective 5 to 10 feet 100,000 VOLTS

ITM10..... ASSEMBLED..... \$99.50

ITM1..... PLANS..... \$10.00 ITM1K..... KIT/PLANS..... \$69.50

**RUBY LASER RAY GUN** — Intense visible red beam burns and welds hardest of metals. **MAY BE HAZARDOUS.**

**RUB3 All Parts Available for Completing Device** \$20.00

**CARBON DIOXIDE BURNING, CUTTING LASER** — Produces a continuous beam of high energy. **MAY BE HAZARDOUS.**

**LC5. All Parts Available for Completing Device.** \$20.00

**VISIBLE LASER LIGHT GUN** — produces intense red beam for sighting, spotting, etc. Hand held complete.

LGU3..... Plans..... \$10.00 (Kit & Assembled Units Available)

**IR PULSED LASER RIFLE** — Produces 15-30 watt infra-red pulses at 200-2000 per sec.

LRG3..... All Parts & Diodes Available..... \$10.00

**BEGINNERS LOW POWER VISIBLE LASER** — Choice of red, yellow, green — provides an excellent source of monochromatic light.

LHC2..... Plans..... \$5.00 LHC2K..... Kit..... \$34.50

**SNOOPER PHONE** — Allows user to call his premises and listen in without phone ever ringing.

SNP20..... Assembled..... \$89.50

SNP2..... Plans..... \$9.00 SNP2K..... Plans/Kit..... \$59.50

**LONG RANGE WIRELESS MIKE** — Miniature device clearly transmits well over one mile. Super sensitive, powerful.

MFT1..... Plans..... \$7.00 MFT1K..... Plans/Kit..... \$49.50

**WIRELESS TELEPHONE TRANSMITTER** — Transmits both sides of phone conversation over one mile, shuts off automatically.

VWPM5..... Plans..... \$8.00 VWPM5K..... Plans/Kit..... \$39.50

**PWM5—LONG RANGE SUPER EAR WITH WIRELESS ATTACHMENT**

PWM5..... Plans..... \$10.00 PWM5K..... Kit..... \$139.50

PWM50..... Assembled and Tested..... \$169.50

Our phone is open for orders anytime. Technicians are available 9-11 a.m., Mon-Thurs for those needing assistance or information. Send \$1.00 for catalog of hundreds more similar devices. Send check, cash, MO, Visa, MC. COD to: **INFORMATION UNLIMITED**

DEPT RB, P.O. Box 716, Amherst, N.H. 03031 Tel: 603-673-4730

CIRCLE 72 ON FREE INFORMATION CARD

**SECURITY**

**PHASORS**

**LASERS**

**AMAZING DEVICES**

**PERSONAL DEFENSE AND PROPERTY PROTECTION**

**UTILIZE SPACE AGE TECHNOLOGY.**

**CAUTION THESE DEVICES CAN BE HAZARDOUS AND MAY SOON BE ILLEGAL.**

**POCKET PAIN FIELD GENERATOR — IPG50**

Assembled..... \$64.50

IPG5..... Plans..... \$8.00 IPG5K..... Kit/Plans..... \$44.50

**PHASOR PAIN FIELD CROWD CONTROLLER — PPF10**

Assembled..... \$250.00

PPF1..... Plans..... \$15.00 PPF1K..... Kit/Plans..... \$175.00

**BLASTER** - Provides a plasma discharge capable of puncturing a can. Produces a 100,000 WATT PULSE.

BLS10..... ASSEMBLED..... \$89.50

BLS1..... PLANS..... \$10.00 BLS1K..... KIT/PLANS..... \$69.50

**PLASMA STUN GUN** - Very intimidating and effective 5 to 10 feet 100,000 VOLTS

ITM10..... ASSEMBLED..... \$99.50

ITM1..... PLANS..... \$10.00 ITM1K..... KIT/PLANS..... \$69.50

**RUBY LASER RAY GUN** — Intense visible red beam burns and welds hardest of metals. **MAY BE HAZARDOUS.**

**RUB3 All Parts Available for Completing Device** \$20.00

**CARBON DIOXIDE BURNING, CUTTING LASER** — Produces a continuous beam of high energy. **MAY BE HAZARDOUS.**

**LC5. All Parts Available for Completing Device.** \$20.00

**VISIBLE LASER LIGHT GUN** — produces intense red beam for sighting, spotting, etc. Hand held complete.

LGU3..... Plans..... \$10.00 (Kit & Assembled Units Available)

**IR PULSED LASER RIFLE** — Produces 15-30 watt infra-red pulses at 200-2000 per sec.

LRG3..... All Parts & Diodes Available..... \$10.00

**BEGINNERS LOW POWER VISIBLE LASER** — Choice of red, yellow, green — provides an excellent source of monochromatic light.

LHC2..... Plans..... \$5.00 LHC2K..... Kit..... \$34.50

**SNOOPER PHONE** — Allows user to call his premises and listen in without phone ever ringing.

SNP20..... Assembled..... \$89.50

SNP2..... Plans..... \$9.00 SNP2K..... Plans/Kit..... \$59.50

**LONG RANGE WIRELESS MIKE** — Miniature device clearly transmits well over one mile. Super sensitive, powerful.

MFT1..... Plans..... \$7.00 MFT1K..... Plans/Kit..... \$49.50

**WIRELESS TELEPHONE TRANSMITTER** — Transmits both sides of phone conversation over one mile, shuts off automatically.

VWPM5..... Plans..... \$8.00 VWPM5K..... Plans/Kit..... \$39.50

**PWM5—LONG RANGE SUPER EAR WITH WIRELESS ATTACHMENT**

PWM5..... Plans..... \$10.00 PWM5K..... Kit..... \$139.50

PWM50..... Assembled and Tested..... \$169.50

Our phone is open for orders anytime. Technicians are available 9-11 a.m., Mon-Thurs for those needing assistance or information. Send \$1.00 for catalog of hundreds more similar devices. Send check, cash, MO, Visa, MC. COD to: **INFORMATION UNLIMITED**

DEPT RB, P.O. Box 716, Amherst, N.H. 03031 Tel: 603-673-4730

CIRCLE 72 ON FREE INFORMATION CARD

**SECURITY**

**PHASORS**

**LASERS**

**AMAZING DEVICES**

**PERSONAL DEFENSE AND PROPERTY PROTECTION**

**UTILIZE SPACE AGE TECHNOLOGY.**

**CAUTION THESE DEVICES CAN BE HAZARDOUS AND MAY SOON BE ILLEGAL.**

**POCKET PAIN FIELD GENERATOR — IPG50**

Assembled..... \$64.50

IPG5..... Plans..... \$8.00 IPG5K..... Kit/Plans..... \$44.50

**PHASOR PAIN FIELD CROWD CONTROLLER — PPF10**

Assembled..... \$250.00

PPF1..... Plans..... \$15.00 PPF1K..... Kit/Plans..... \$175.00

**BLASTER** - Provides a plasma discharge capable of puncturing a can. Produces a 100,000 WATT PULSE.

BLS10..... ASSEMBLED..... \$89.50

BLS1..... PLANS..... \$10.00 BLS1K..... KIT/PLANS..... \$69.50

**PLASMA STUN GUN** - Very intimidating and effective 5 to 10 feet 100,000 VOLTS

ITM10..... ASSEMBLED..... \$99.50

ITM1..... PLANS..... \$10.00 ITM1K..... KIT/PLANS..... \$69.50

**RUBY LASER RAY GUN** — Intense visible red beam burns and welds hardest of metals. **MAY BE HAZARDOUS.**

**RUB3 All Parts Available for Completing Device** \$20.00

**CARBON DIOXIDE BURNING, CUTTING LASER** — Produces a continuous beam of high energy. **MAY BE HAZARDOUS.**

**LC5. All Parts Available for Completing Device.** \$20.00

**VISIBLE LASER LIGHT GUN** — produces intense red beam for sighting, spotting, etc. Hand held complete.

LGU3..... Plans..... \$10.00 (Kit & Assembled Units Available)

**IR PULSED LASER RIFLE** — Produces 15-30 watt infra-red pulses at 200-2000 per sec.

LRG3..... All Parts & Diodes Available..... \$10.00

**BEGINNERS LOW POWER VISIBLE LASER** — Choice of red, yellow, green — provides an excellent source of monochromatic light.

LHC2..... Plans..... \$5.00 LHC2K..... Kit..... \$34.50

**SNOOPER PHONE** — Allows user to call his premises and listen in without phone ever ringing.

SNP20..... Assembled..... \$89.50

SNP2..... Plans..... \$9.00 SNP2K..... Plans/Kit..... \$59.50

**LONG RANGE WIRELESS MIKE** — Miniature device clearly transmits well over one mile. Super sensitive, powerful.

MFT1..... Plans..... \$7.00 MFT1K..... Plans/Kit..... \$49.50

**WIRELESS TELEPHONE TRANSMITTER** — Transmits both sides of phone conversation over one mile, shuts off automatically.

VWPM5..... Plans..... \$8.00 VWPM5K..... Plans/Kit..... \$39.50

**PWM5—LONG RANGE SUPER EAR WITH WIRELESS ATTACHMENT**

PWM5..... Plans..... \$10.00 PWM5K..... Kit..... \$139.50

PWM50..... Assembled and Tested..... \$169.50

Our phone is open for orders anytime. Technicians are available 9-11 a.m., Mon-Thurs for those needing assistance or information. Send \$1.00 for catalog of hundreds more similar devices. Send check, cash, MO, Visa, MC. COD to: **INFORMATION UNLIMITED**

DEPT RB, P.O. Box 716, Amherst, N.H. 03031 Tel: 603-673-4730

CIRCLE 72 ON FREE INFORMATION CARD

**SECURITY**

**PHASORS**

**LASERS**

**AMAZING DEVICES**

**PERSONAL DEFENSE AND PROPERTY PROTECTION**

**UTILIZE SPACE AGE TECHNOLOGY.**

**CAUTION THESE DEVICES CAN BE HAZARDOUS AND MAY SOON BE ILLEGAL.**

**POCKET PAIN FIELD GENERATOR — IPG50**

Assembled..... \$64.50

IPG5..... Plans..... \$8.00 IPG5K..... Kit/Plans..... \$44.50

**PHASOR PAIN FIELD CROWD CONTROLLER — PPF10**

Assembled..... \$250.00

PPF1..... Plans..... \$15.00 PPF1K..... Kit/Plans..... \$175.00

**BLASTER** - Provides a plasma discharge capable of puncturing a can. Produces a 100,000 WATT PULSE.

BLS10..... ASSEMBLED..... \$89.50

BLS1..... PLANS..... \$10.00 BLS1K..... KIT/PLANS..... \$69.50

**PLASMA STUN GUN** - Very intimidating and effective 5 to 10 feet 100,000 VOLTS

THE MOST POPULAR KITS IN EUROPE & ASIA ARE COMING NOW! 50 HOT ITEMS FOR YOUR SELECTION. SEND \$1.00 FOR MARK V CATALOG, REFUND UPON ORDER

TY-47 SUPERIOR ELECTRONIC ROULETTE




This roulette employs three CMOS IC to drive thirty-six LEDs. It includes sound effect circuit and automatic power on/off switch. Its feature can be comparable to real Roulette. It is simple in construction and easy to build.

- Deluxe colour face panel is free of charge.

Kit..... \$16.92

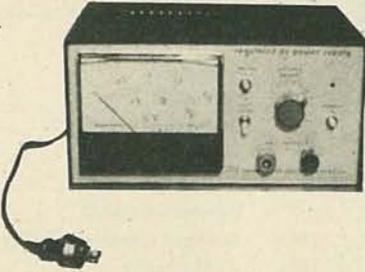TR-100 0-15V 2 AMP. REGULATED POWER SUPPLY KIT



This is a professional power supply kit. Output voltage adjustable from 0-15VDC. Output current also can be limited to two range sections such as 200mA and 2A. An elaborate protection system also designed to give out a beeping sound and a flashing LED warning will appear when output was over loaded or short circuited. High stability and reliability resulting from employing a high quality voltage regulator IC. The front panel of the power supply is well designed with output terminals, on/off switch, voltage adjusting control, jumbo size meter for reading both AMPs and VOLTS. Also with a voltmeter switch as well as current limit select switch. Kit comes with refined metal case, silver color with sand brushed front panel, all electronic parts, p.c. board, 3" jumbo size meter transformer, circuit diagram and instructions.

Kit..... \$59.50 Assembled with tested..... \$69.50

TY-238 COLOR LIGHT CONTROLLER




As a result of the advanced technology, this unit can control various colorful light bulbs, the visual effect of which is most suitable in places like at home party, disco, electronic game centre and also in lightings for advertisement. Total output power is 3000W (1000W/CH) which means that it can control 30 pieces of 100W or 600 pieces of 5W color light which is enough for most usages.

**FEATURE:**

- "Music" mode. Audio signal is divided into high, middle and low frequency to drive 3 groups of light, it has separate sensitive controller.
- "Chasing" mode. Electronic circuit automatically controls 3 groups of color light in sequential ON and OFF; also it has a speed controller. Build one of these light controller today and enjoy watching your music. Great for school projects! all electronic parts, metal case, predrilled p.c. board and instructions are come with the kit.

Kit..... \$65.00 Assembled with tested..... \$75.00

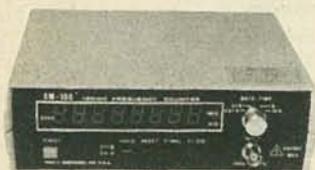SM-100 150MHz UNIVERSAL DIGITAL FREQUENCY COUNTER



SM-100 is an accurate, easy-operated digital frequency counter. Few pieces of advanced, high technical LSI integrated circuit are used, thus, circuit structure is reliable. SM-100 can give you up to 8 digits of resolution for a wide frequency range of 10Hz to 150MHz. Besides, a memorize system is available, the last input digits can be held on the panel, as compare to the other or even observation.

Input sensitivity: KHz range 10Hz - 10MHz 50mVrms  
MHz range 1MHz - 150MHz 40mVrms

Response time: 0.2 sec.  
Hold: Hold the last input signal  
Power supply: DC5V Battery or DC5V 250MA Adaptor  
Assembled with tested..... \$99.00

TA-2400A ELECTRONIC ECHO AND REVERBERATION AMPLIFIER



This unit combines the most advanced computer V.L.S.I. technique with high quality Japan made component, so it has the following FEATURES:

It can generate various reflection and reverberation effect such as that in valley and music hall. It has a 3 section effect control which includes reverberation control, delay control and depth control. All kinds of infield sound effect can be obtained by skilful use of this control. It has LED display to show reflection and reverberation.

Assembled with tested..... \$99.85

TA-323A HIGH QUALITY 30W + 30W STEREO AMPLIFIER



This amplifier employs newly designed symmetrical output circuit which uses high efficiency Darlington transistor, so it has good efficiency and excellent characteristic. The driver transistor will never overheat. It is easy to build and no alignment is required.

**Specifications:**  
Power Output: 30W + 30W (8 ohm)  
Total Harmonic distortion: Less than 0.1% between 100Hz & 10KHz

Pre amplifier: 3mV at 47K RIAA or Mic. Equalized  
Input Sensitivity: 130mV at 47K TAPE, TUNER

S/N Ratio: 80dB  
Output Impedance: 4.8 ohm  
Power Voltage: DC 30-50V  
AV 22.36V x 2.3A  
Kit..... \$24.60

The Best Kit for Hi-Fi Beginner!

SM-48 4 1/2 HI-PRECISION D. P. M.



4 1/2 digit, each with a large red LED indication of 0.6" Auto flash whenever it is overloaded

- Range: DC current ± 1uA - ± 20A  
DC voltage ± 1mV - ± 2000V
- Stability: DC ± 0.025% ± 2 digit
- Power supply: DC 5-6V 200mA
- Size: 4 1/2" (W) x 3 1/4" (D) x 1 3/4" (H)
- Various functions are available: output terminal of BCD, BUSY, STROBE etc., which are suitable for working with microcomputer.
- Temperature Compensated Regulator of 100ppm/°C is employed as to upset this unit's stability.
- The memory system can hold the latest reading, for the convenience of comparison and observation.

Kit..... \$38.00 Assembled with tested..... \$43.00


TA-2500 HIGH QUALITY MULTIPURPOSE PRE-AMPLIFIER



This specially designed pre amplifier includes a professional GRAPH EQUALIZER TONE control system and has a gain of ± 12dB. Frequency response extends from 5Hz to 20KHz, so even in bad listening condition it can improve well. It can accept input from various magnetic cartridge, record deck and tuner, its output can be connected to all kinds of power amplifier.

Assembled with tested..... \$90.00

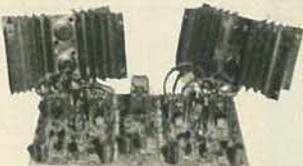TA-802 80W + 80W PURE DC STEREO POWER AMPLIFIER



This power amplifier employs pure DC mirror circuit and several current stabilizers, so it has high stability. No AC bypass capacitor included in feedback network, so frequency response is extended to DC and there is no phase distortion, it can reproduce high level bass faithfully.

- It uses FET differential input to improve S/N ratio and input impedance.
- It is compatible with all kinds of preamplifier.
- It has a multipurpose protection system, including high sensitive DC output protection circuit, high speed output short-circuit, overload protection, and an automatic temperature control system. It can protect the loudspeakers and amplifier against damage.

Kit..... \$39.95

TA-3000 STEREO SIMULATOR



You can own a STEREO TV from today! This simulator is a special design of using the most advanceable mono-paired L.S.I. It produces a superior analog stereo effect since the L.S.I. is equalled to 60 pct. of LOW NOISE FET & TRANSISTOR. The simulator can even help you to promote your television from a normal one to a special one with a Hi-Fi STEREO function. Our simulator is also applicable to any other 'mono sources' in converting it to ANALOG STEREO. Undoubtedly, it is the most advanced equipment for every family, while it should contribute to your listening pleasure.

**Specifications:**  
Frequency Response: 10Hz-20KHz  
Signal-to-noise ratio: 60dB (L.H.C.) 56dB (R.H.C.)  
Distortion (Both ch.): 0.1%  
Input Sources: High Input Impedance: AM tuner, Mono cassette Low Impedance: Radio, TV, VCR  
Power Consumption: 6VA 110V  
Assembled with tested..... \$30.00

TA-2800 LOW TIM DC STEREO PRE-AMP KIT



Incorporates brand new DC design that gives a frequency response from 0-100KHz ± 0.5dB. Added features like tone defat and loudness control let you tailor your own frequency supplies to eliminate power fluctuations!

**Specifications:**  
THD/TIM less than .005%  
Frequency response DC to 100KHz ± 5dB  
RIAA deviation ± 0.2dB  
S/N ratio better than 70dB  
Sensitivity: phone 2mV 47KΩ, Aux 100mV 100KΩ  
Output Level: 1.3V  
Max output: 15V  
Tone controls: Bass ± 10dB @ 50Hz  
Treble ± 10dB @ 15kHz

Power supply: ± 24VDC 90.5A  
It is compatible with any power amplifier which made by our company such as TA-802, TA-477, TA-1000A  
Kit..... \$44.50

TY-45 20 STEPS BAR/DOT AUDIO LEVEL DISPLAY KIT



This new designed audio level display unit is using a new integrated circuit from National Semiconductor to drive 20 pieces of color LED's (green, yellow and red) on each channel. It provides two types of display methods for selection 'bar' or 'dot'. The display range is from 3.76dB to 0dB. Kit is good for any amplifier from 2 watts to 2000W. Power supply requires 12VAC or DC. So, it is great for cars as well. Kit comes with printed circuit board, all LED's electronic components, switches and silk screen printed professional front panel.

Kit..... \$34.95

WE CAN SUPPLY METAL CABINETS AND POWER TRANSFORMERS FOR OUR KITS! PLEASE REFER TO OUR CATALOG.

TERMS:  
Min order: \$10.00  
Charge card order: \$20.00  
NO C. O. D. ! Cashier's check, phone orders accept.  
Calif. Res Add 6.5% Sales Tax.  
Prices are subject to change without notice.

All merchandises are subject to prior sale.  
Shipping & Handling: Inside L. A. 5% of total order, (Min 1.50). Outside L. A. 10% of total order, (Min 2.50). Outside U.S.A. 20% of total order, (Min 5.00).



MARK V ELECTRONICS INC.  
248E. Main Street,  
Suite 100,  
Alhambra, CA91801  
For information (818) 282-1130  
For orders, (818) 282-1196

# SPARTAN Electronics Inc



CALL MAIL  
(516) 499-9500

6094 Jericho Tpke.  
Commack, N.Y. 11725

**T V ACCESSORIES**

JERROLD LCC-58 CONVERTER	84.95
JERROLD LCC-91 remote	104.95
PHILIPS CV-1000 CONVERTER W/VOLUME CONTROL	169.95
PHILIPS CTC9R CONVERTER	129.95
<b>WINEGUARD</b>	
ANTENNA ROTOR WR-5000	69.95
DA-8150 VHF-UHF AMP	45.95
BC-7820 4-SET BOOSTER	49.95
<b>TUSA</b>	
CVU-40 BLOCK CONVERTER	28.95
CVU-1000 BLOCK CONV.	38.95
COAX CABLE 59'U 500'	35.00
ROTOR CABLE 20'4 500'	35.00

**TEST EQUIPMENT**

<b>BECKMAN</b>			
DM-10	\$39	DM-45	\$89
DM-20	65	DM-73	63
DM-25	79	DM-77	75
DM-40	69	CM-20	129
<b>TRIPLETT</b>			
P/N 3400	\$122	P/N 50	\$59
3500	108	630NA	169
3550A	79		
<b>B&amp;K</b>			
P/N 820	\$170	P/N 3300	\$339
2802	47	111	39
2815	140	116	64
2816	128	1042	19
		1045	336

**POCKET TECHNOLOGY, INC.**  
LogicScope 136  
w/ Probes \$599  
w/o Probes \$499

**RS232 TRANSMISSION LINE TESTER**  
All 25 signal lines accessible. Dual color LED's (red/green) Jumpers and case incl. \$169.95

**COMPONENTS**

**PHILIPS ECG SEMICONDUCTORS**  
We have a complete line of ECG replacement semiconductors for all your electronic needs.

**DISCOUNT PRICES—**

EGG (EQUIV) 1155	\$4.95
EGG (EQUIV) 123	.59
EGG (EQUIV) 4016	.99
EGG (EQUIV) 5070	1.29

**CONNECTORS**  
RS-232C (SOLDER TYPE)

BNC	Male \$1.50 Female \$1.95
UHF	Male 9.95 per 10
F	Male 9.90 per 10
RCA	Male 2.50 per 10
GENDER	Male 2.95 per 10
CHANGER RS232 M-M	19.95
CHANGER RS232 F-F	19.95

**SECURITY**

**WOLDO AUTO ALARMS**

FA-CM Current monitor	\$37.50
FA-AP Keyless/Passive	67.50
CAR-CALL Pager alarm	90.00
MIGHTY-MO Keyed alarm	22.50
GLASS BREAKAGE DETECTOR	21.00
IGNITION KILLER	12.50
HOOD-LOCK/IGNITION CUTOFF	32.25

**AUTO**

**MINI-DASH COMPUTER \$89.95**  
LCD display monitors oil pressure water temp., engine RPM, Battery Voltage, inside/outside temp. and stopwatch

**PC ACCESS**

IBM PRINTER CABLE	\$22
SAKATA 12" AMBER MONITOR	129
12" GREEN MONITOR	119
ZENITH 135 13" COLOR COMPOSITE-RGB AUDIO H-RES	524
<b>HAYES SMARTMODEMS</b>	
300 BAUD	\$234
1200/300 BAUD	469
1200H INTERNAL (IBM)	389
2400/1200 BAUD	739

**TOOLS**

**XCELITE**

99-PR Roll Kit	\$33.00
PS-88 Screwdriver Set	13.90
PS-120 Nutdriver Set	16.90
101-S Wirestripper	4.75

Debits Welcome  
Visa MC BAC Antex All above  
prices include 4% cash discount  
C.O.D. money order check Add for  
Shipping

**Volume Discounts**

Min. Order \$25.00	to 75.00	\$2.50
International shipping Add'l.	76.00 to 250.00	\$4.50
Prices subject to change without notice	251.00 to 500.00	\$6.00
COD 2.00 Extra	501.00 to 750.00	\$8.50
Add'l shipping for monitors	751.00 to 1000.00	\$12.00
	Over 1000.00	\$12.50

(516) Mon Th Tu W F Sa  
499-9500 9-8 9-6 9:30-5

## ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	—	NTS		
271	AIS Satellite	87	289	New-Tone Electronics	21
108	AMC Sales	108	285	Omnitron	96
76	AP Products	CV3	—	Pacific Cable	115
288	ASD	100	118	Pacific One	86
51	Active Electronics	118	270	PanaVise	86
—	Advance Electronics	39,40,41	280	Panasonic	13
106	Advanced Computer Products	123	68,275	Philips ECG	103
107	All Electronics	127	284	Quintec	87
72	Amazing Devices	136	126	RAG Electronics	5
84	Appliance Service	87	257	RAG Electronics	27
272	Arctec Systems	120	258	RAG Electronics	28,29
77	B&K Precision	43	259	RAG Electronics	31
98,251	Beckman Industrial	14,15	78	Radio Shack	121
81	CEI	124	70	Ramsey	125
—	CIE	52	278	Regency	33
279	Cameo Enterprises	136	283	Rhoades	83
54	Chemtronics	100	260	Saratoga Electronics	122
—	Command Productions	32	277	Simpson	90
79,281	Communications Electronics	3,44	73	Sintec	88
—	Coop's Satellite Digest	12	75	Spartan Electronics	138
127	Deco Industries	86,87	—	Tektronix	CV2
252	Deltax Dynamic	86	123	Test Probes	108
—	Dick Smith Electronics	22,23	102	Trio-Kenwood	99
286,287	Diehl Engineering	85,95	261	U.S. Instrument Rentals	79
82	Digi-Key	133	66	W.S. Jenks	30
—	Digital Research Computers	124	103	Wm B Allen	124
57	Digitron	118	262	Yours Truly	30
253	Diplomat International	87			
110	Dokay	117			
83	Electro Industries	109			
276	Electronics Book Club	81			
120	Elephant Electronics	87			
111	Etronix	110			
100	Firestik II	111			
254	Fluke Manufacturing	7			
—	Fordham Radio	25,93, CV4			
—	Franklin Lakes Stereo	108			
269	Grace Industries	86			
—	Grantham College of Engineering	97			
—	Harbor Freight Salvage	26			
86	Heath	43			
65	J & W	136			
113	JDR Instruments	9			
263,264	JDR Microdevices	128-129			
265,266	JDR Microdevices	130-131			
267	JDR Microdevices	132			
—	JS&A	11			
114	Jameco	134,135			
124	James Walter Satellite Rec.	87			
104	Jan Crystals	32			
115	Jensen Tools	86			
—	Joseph Electronics	91			
268	Kepro Circuit Systems	110			
256	Krueger Technology	126			
87	MCM Electronics	119			
105	MFJ	136			
255	Mark V. Electronics	137			
67	McIntosh Labs	107			
282	Micro Linear Controls	24			
273	Micro-Mart	116			
117	Mouser	109			
—	NRI	16			

Gernsback Publications, Inc.  
200 Park Ave. South  
New York, NY 10003  
(212) 777-6400  
Chairman of the Board:  
M. Harvey Gernsback  
President: Larry Steckler

**ADVERTISING SALES 212-777-6400**

Larry Steckler  
publisher  
Arlene Fishman  
advertising coordinator  
Shelli Weinman  
advertising associate  
Lisa Strassman  
credit manager  
Donna Sala  
credit associate  
Naomi Matten  
advertising assistant

**Sales Offices**

**EAST/SOUTHEAST**

Stanley Levitan  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003  
718-428-6037, 212-777-6400

**MIDWEST/Texas/Arkansas/Okla.**

Ralph Bergen  
Radio-Electronics  
540 Frontage Road—Suite 325  
Northfield, IL 60093  
312-446-1444

**PACIFIC COAST/ Mountain States**

Marvin Green  
Radio-Electronics  
15335 Morrison St.—Suite 227  
Sherman Oaks, CA 91403  
818-986-2001